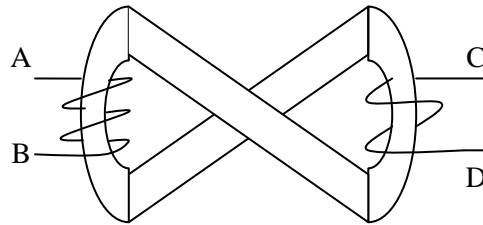


Name: _____


EE 303, Quiz 3, Spring 2019, Dr. McCalley. Time: 20 minutes, closed book, closed notes, no communication devices

1. (30 pts) Determine the placement of the dots for the coupled coils shown in figure below.



Solution: (A and D) or (B and C)

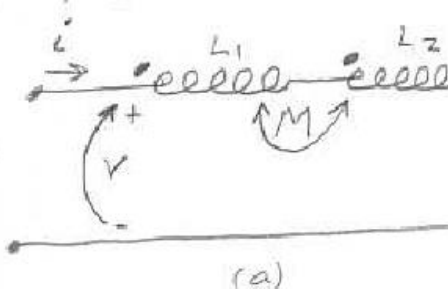
2. (40 pts) A pair of coupled inductors is connected as shown below. Find the differential equation relating $v(t)$ and $i(t)$, and then find the equivalent inductance “seen” at the terminals looking into the circuit.



$$v(t) = L_1 \frac{di(t)}{dt} + M \frac{di(t)}{dt} + L_2 \frac{di(t)}{dt} + M \frac{di(t)}{dt} = [L_1 + 2M + L_2] \frac{di(t)}{dt}$$

$$\Rightarrow L_{eq} = L_1 + 2M + L_2$$

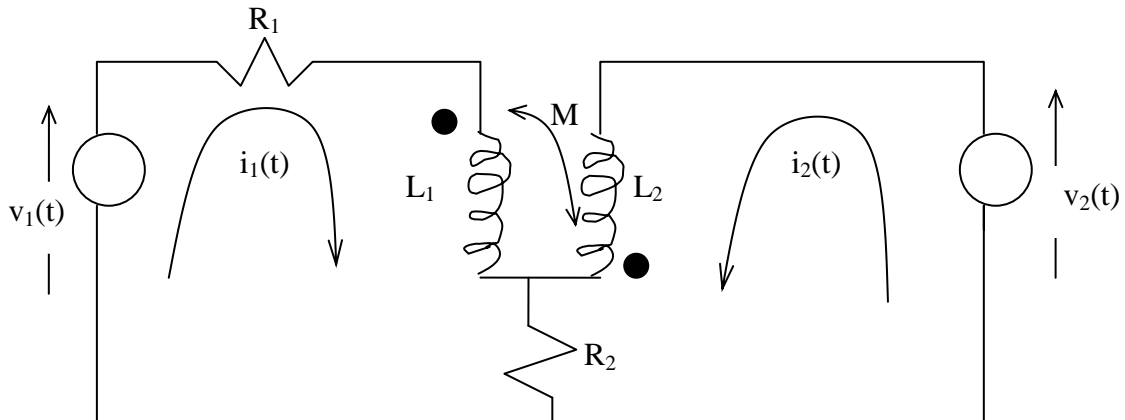3. (30 pts) For the circuit below, express (a) $v_1(t)$ and (b) $v_2(t)$ as a function of: mesh currents $i_1(t)$ and $i_2(t)$, associated current derivatives, and other parameters indicated on the diagram.



- a. Left loop: $v_1(t) = [i_1(t) + i_2(t)]R_2 + L_1 \frac{di_1(t)}{dt} - M \frac{di_2(t)}{dt} + R_1 i_1(t)$
 b. Right loop: $v_2(t) = [i_1(t) + i_2(t)]R_2 + L_2 \frac{di_2(t)}{dt} - M \frac{di_1(t)}{dt}$