
Module G1

Solution to problem 1

(a)

$$V_t = \frac{30kV}{\sqrt{3}} = 17.32kV$$

$$P = 50MW$$

$$pf = 0.8 = \cos \theta$$

$$\Rightarrow \theta = 36.87^\circ$$

$$P = 3|V_t||I_a|\cos \theta \Rightarrow \frac{P}{3 \cdot |V_t|\cos \theta} = \frac{50 \times 10^6}{3(17.32 \times 10^3) \cdot (0.8)} = |I_a| = 1202.8A$$

$$\Rightarrow I_a = 1202.8 \angle -36.87^\circ A$$

$$E_f = V_t + I_a(jX_s) = 17.32 \times 10^3 \angle 0^\circ + (1202.8 \angle -36.87^\circ) \cdot (j0.9)$$

$$= 17970.0 + j866V$$

$$= 17991 \angle 2.759^\circ V$$

$$Q_{out} = \frac{3|V_t| \cdot |E_f|}{X_s} \cos \delta - \frac{3|V_t|^2}{X_s} = 37.5MVar$$

(b)

$$P_{out} = 25MW$$

$$\Rightarrow P_{out} = 25M = \frac{3(17.32 \times 10^3)(17990)}{0.9} \sin \delta$$

$$\Rightarrow \delta = \sin^{-1}(0.0241) = 1.38^\circ$$

$$Q_{out} = \frac{3(17.32 \times 10^3)(17.99 \times 10^3)}{0.9} \cos(1.38^\circ) - \frac{3(17.32 \times 10^3)^2}{0.9} = 38.38MVar$$


(c)

With $|E_f| = 14,248.8$ volts, we need to find new angle

$$P = \frac{3|V_t||E_f|}{X_s} \sin \delta \Rightarrow \frac{(50 \times 10^6) \cdot 0.9}{3(17.32 \times 10^3)(14248)} = 0.060 \Rightarrow \delta = 3.48^\circ$$

$$Q_{out} = \frac{3 \cdot (17.32 \times 10^3) \cdot (14,248)}{0.9} \cos(3.48^\circ) - \frac{3(17.32 \times 10^3)^2}{0.9} = -178.867MVar$$

Solution to problem 4

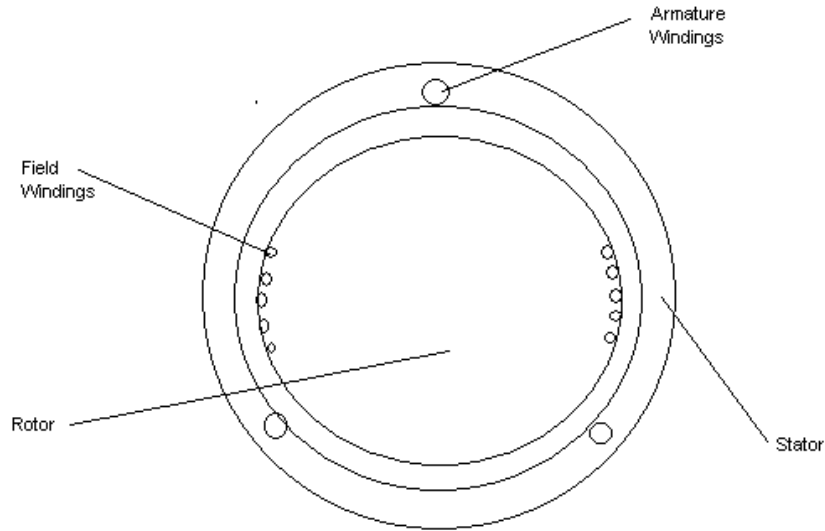

Solution to problem 8

a)

$$P = \frac{3 \cdot |V_t| \cdot |E_f|}{2} \cdot \sin(\delta) = \frac{3 \cdot |127.02| \cdot |132.98|}{2} \cdot \sin(10.23^\circ) = 4499.8$$


b)

$$Q = \frac{3 \cdot |V_t| \cdot |E_f|}{2} \cdot \cos(\delta) - \frac{3 \cdot |V_t|^2}{2} = \frac{3 \cdot |127.02| \cdot |132.98|}{2} \cdot \cos(10.23^\circ) - \frac{3 \cdot |127.02|^2}{0.95} = 732.8 \text{ var}$$

c)

$$I_a = \frac{E_f - V_t}{jX_s} = \frac{(132.98 \angle 10.23^\circ) - (127.02 \angle 0^\circ)}{2 \angle 90^\circ} = 11.96 \angle -9.25^\circ$$

d)

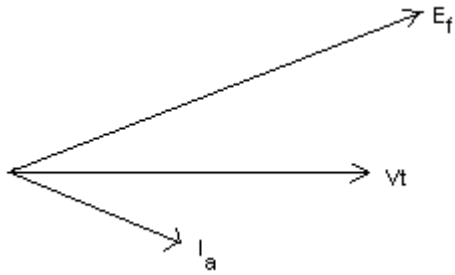

e) lagging

f)

$$Q = \frac{3 \cdot |V_t| \cdot |E_f|}{2} \cdot \cos(\delta) - \frac{3 \cdot |V_t|^2}{2} = \frac{3 \cdot |127.02| \cdot |132.98|}{2} \cdot \cos(\delta) - \frac{3 \cdot |127.02|^2}{0.95} = 0$$

$$(25336.7) \cos(\delta) - (24201.1) = 0$$

$$\delta = 17.22^\circ$$

Solution to problem 9

a)


$$Q = 3 \left(\frac{E_f V_t}{X_s} \cos \delta - \frac{|V_t|^2}{X_s} \right) = 3 \left(\frac{132.98 \times \frac{220}{\sqrt{3}}}{2} \cos(10.23) - \frac{\left(\frac{220}{\sqrt{3}} \right)^2}{2} \right) = 733.319 \text{Var}$$

$$\text{b) } I_p^* = \frac{1000 + j200}{\frac{220}{\sqrt{3}} \angle 0^\circ} = 7.873 + j1.575 = 8.0289 \angle 11.31^\circ$$

$$E_f = \frac{220}{\sqrt{3}} \angle 0^\circ + I_p \cdot j2 = \frac{220}{\sqrt{3}} \angle 0^\circ + (7.873 - j1.575) \cdot j2 = 130.166 + j15.75 \\ = 131.115 \angle 6.897^\circ \text{V}$$

Solution to problem 10

a)

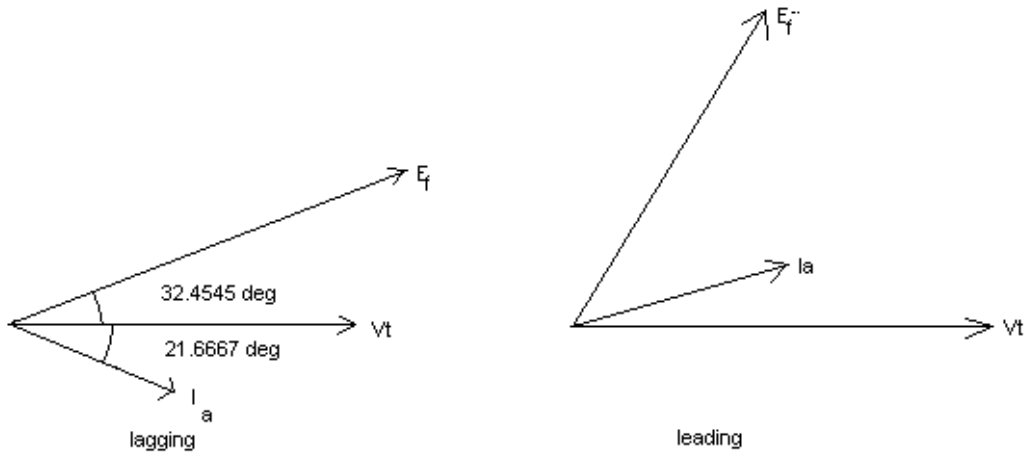

b) To get the below answers in MW and MVAR, multiply by the 3-phase power base, which is specified in the problem to be 100 MVA.

$$P = \frac{|V_1||E_g|}{X_g} \sin(\delta) = \frac{|1.0||1.5136|}{0.95} \sin(30.4545) = 0.8076$$

$$Q = \frac{|V_1||E_g|}{X_g} \cos(\delta) - \frac{|V_1|^2}{X_g} = \frac{|1.0||1.5136|}{0.95} \cos(30.4545) - \frac{|1.0|^2}{0.95} = 0.3208$$

c)

$$S_{3,2} = VI^* = (0.9713 \angle -4.7692)(0.8689 \angle -21.6667) = 0.8075 + j0.2453$$

d) P is the same because the transformer has no 'R' to cause real power loss. Q is not the same due to the losses in X_x .

Solution to problem 11

(a)

$$V_t = \frac{13.8kV}{\sqrt{3}} = 7967.4Volts$$

$$E_f = V_t + j \cdot X_s \cdot I_a = 7967.4V + (j \cdot 3) \cdot (400 \angle -30^\circ) = 7967.4V + 1200 \angle 60^\circ$$

$$E_f = 8630.2 \angle 6.92^\circ$$

(b) At $Q = 0$,

$$|E_f| \cdot \cos \delta = V_t \Rightarrow |E_f| = \frac{|V_t|}{\cos \delta} = \frac{7967.4V}{\cos 6.92^\circ} = 8025.9Volts$$