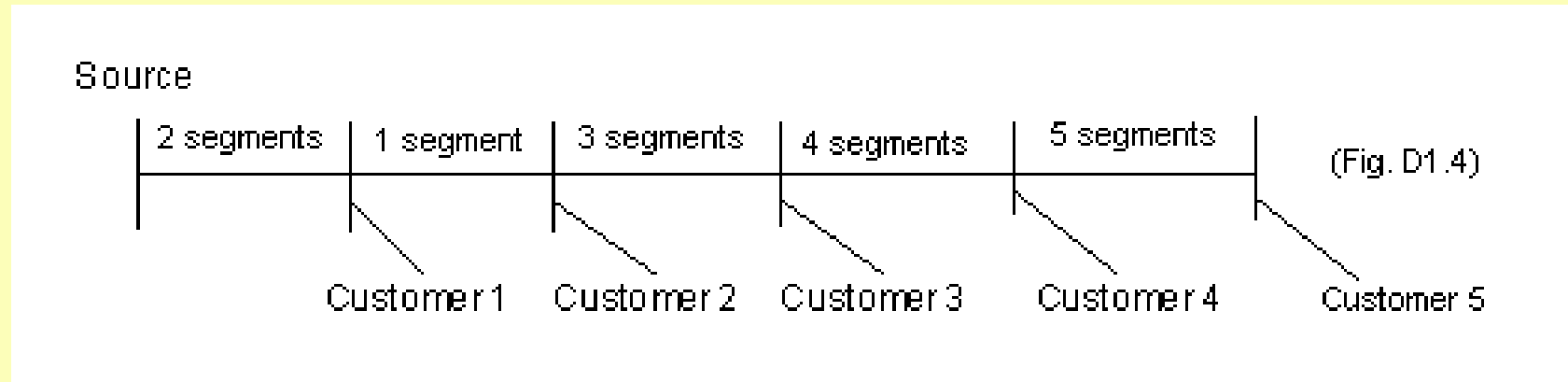


# Module D1-b

## Introduction to Distribution Systems (Continued)

Example: Determine  $V_s$  required to hold  $V_5=11$  kV (L-L)



- 1 segment = 1000 ft
- Need to use table to get impedance of each section
- All lines use 4 AWG conductors
- System is 3 phase

Load data is as follows:


bus 1:  $120+j30$  kVA

bus 2:  $80+j20$  kVA

bus 3:  $40+j5$  kVA

bus 4:  $12,000+j4000$  ohms/phase (Y)

bus 5:  $10+j2$  kVA

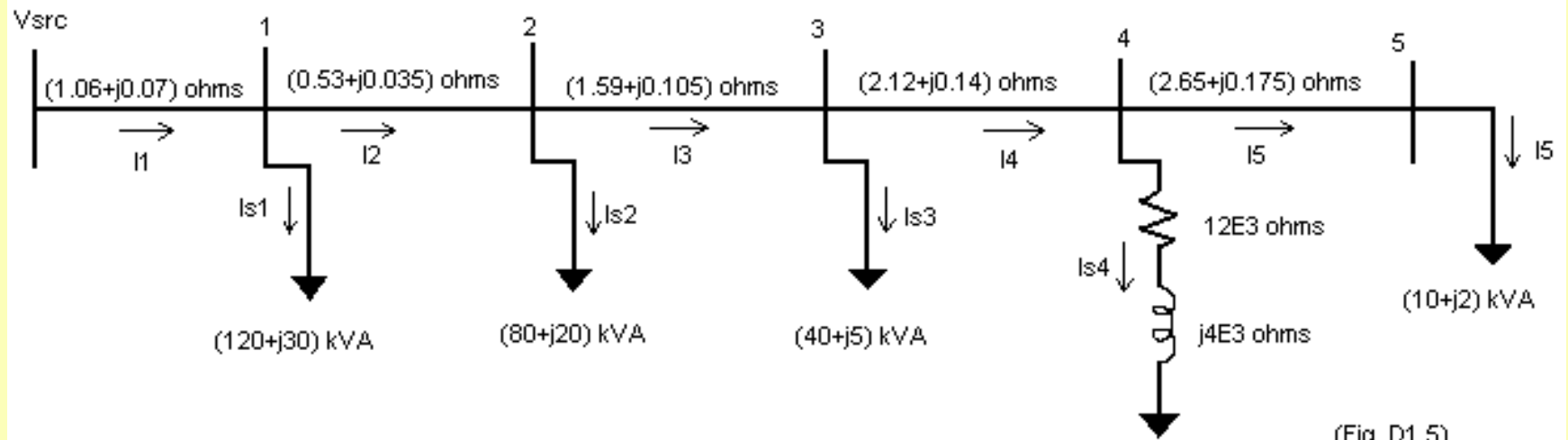

(Fig. D1.5)

## Basic algorithm for problem solution:

1.  $i=5$
2. Find  $I_i$  (current flowing into bus  $i$ )


$$I_i = I_{i+1} + I_{si}$$

If constant power load,  $I_{si} = (S_i / V_i)^*$

If constant  $Z$  load,  $I_{si} = V_i / Z_i$

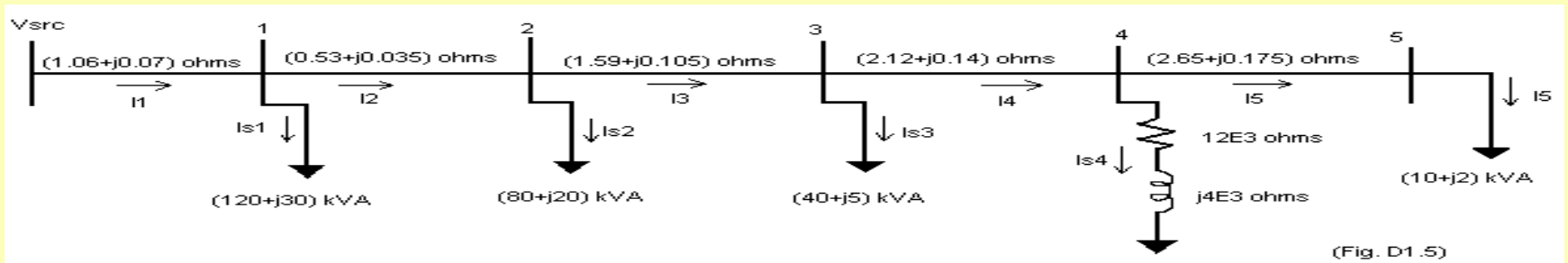3. Find  $V_{i-1} = V_i + I_i(Z_{i-1,i})$
4.  $i=i-1$ , if not done, go to 2


Note: powers are per phase (or pu) and voltages are L-N (or pu)



We normally use L-N voltage as reference. This time we will use L-L voltage as reference. Our choice will only affect the angles in our calculations.

$$V_5 = \frac{11000 \angle -30^\circ}{\sqrt{3}} = 6350 \angle -30^\circ$$
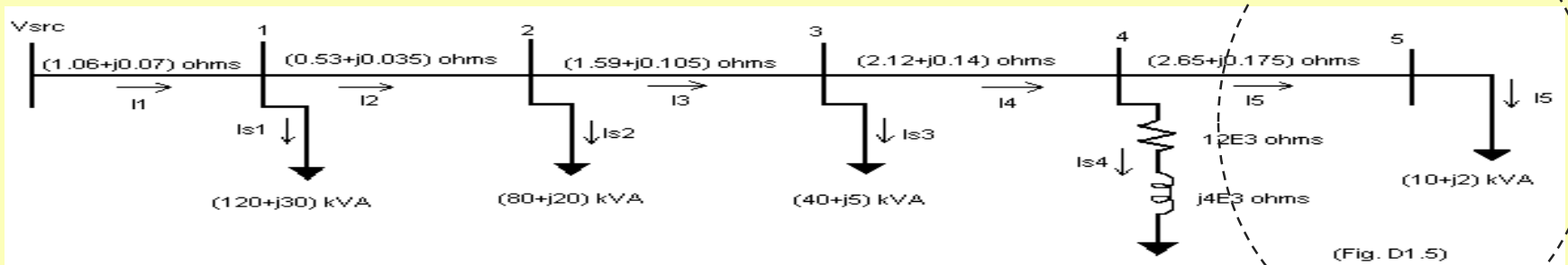
$$I_5 = \left( \frac{S}{V} \right)^* = \left( \frac{\left( \frac{10 - j2}{3} \right) \cdot 10^3}{6350 \angle 30^\circ} \right) = 0.4021 - j0.3533 \text{ A}$$




$$\begin{aligned}
 V_4 &= V_5 + I_5 \cdot Z_{45} \\
 &= (6350 \angle -30^\circ) + (0.4021 - j0.3533)(2.65 + j0.175) \\
 &= 6352.3 \angle -30.002^\circ
 \end{aligned}$$

$$\Rightarrow V_{4LL} = 11002.44 \angle -0.002^\circ$$

$$I_{S4} = \frac{V_4}{Z_4} = \frac{6352.3 \angle -30.002^\circ}{12000 + j4000} = 0.33318 - j0.37575$$
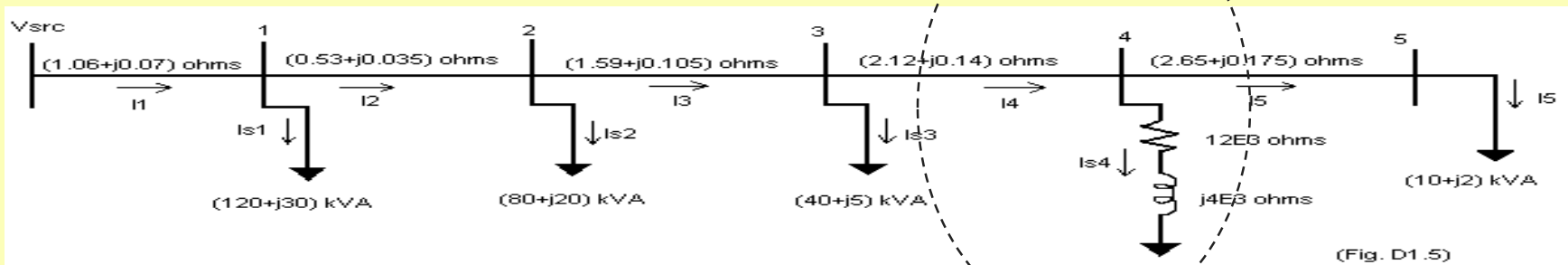
$$\begin{aligned}
 I_4 &= I_5 + I_{S4} = (0.4021 - j0.3533) + (0.33318 - j0.37575) \\
 &= (0.7353 - j0.7291)
 \end{aligned}$$



$$V3 = V4 + I4 \cdot Z34$$

$$= (6352.3 \angle -30.002^\circ) + (0.7353 - j0.7291)(2.12 + j0.14)$$


$$= 6354.46 \angle -30.006^\circ$$

$$\Rightarrow V3_{LL} = 11006.25 \angle -30.006^\circ$$

$$IS3 = \frac{\left( \frac{40 - j5}{3} \right) \cdot 10^3}{6354.46 \angle 30.006^\circ} = 1.6859 - j1.2765$$

$$I3 = I4 + IS3 = (0.7353 - j0.7291) + (1.6859 - j1.2765)$$

$$= (2.4212 - j2.0055)$$

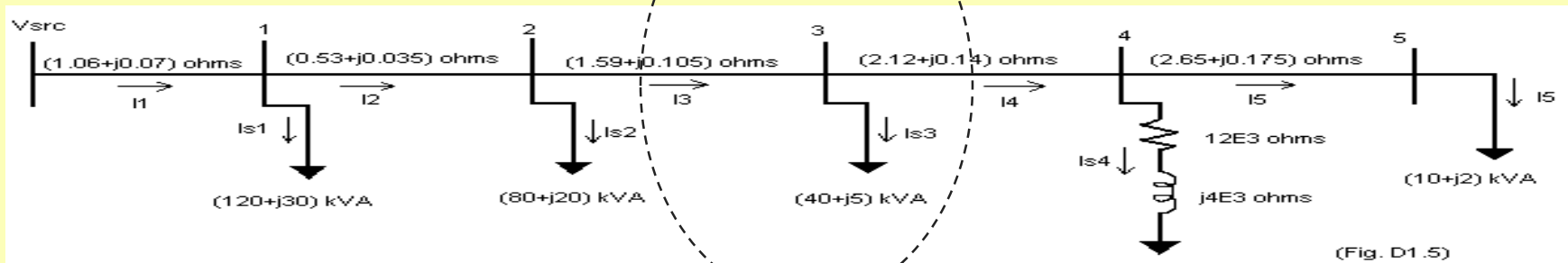




$$V2 = V3 + I3 \cdot Z23 = (6354.46 \angle -30.006^\circ) \\ + (2.4212 - j2.0055)(1.59 + j0.105) \\ = 6359.44 \angle -30.0106^\circ$$

$$\Rightarrow V2LL = 11014.88 \angle -30.0106^\circ$$

$$IS2 = \frac{\left(\frac{80 - j20}{3}\right) \cdot 10^3}{6359.44 \angle 30.0106^\circ} = 3.10674 - j3.00506$$
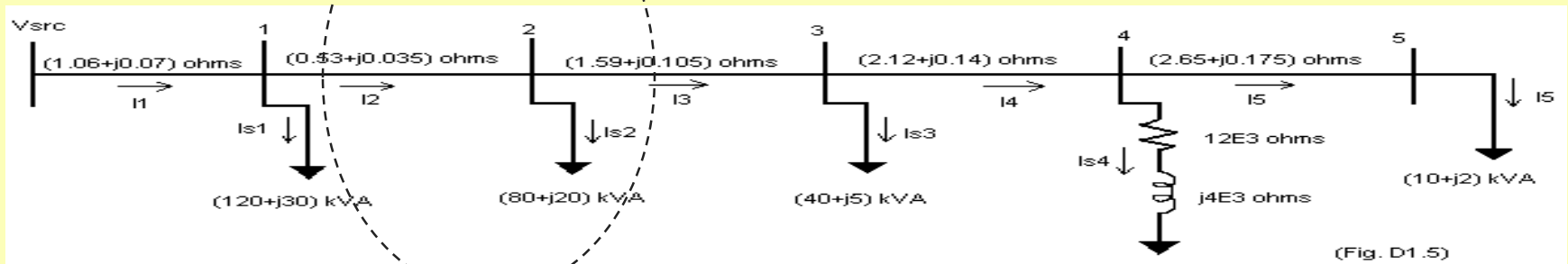
$$I2 = I3 + IS2 = (2.4212 - j2.0055) \\ + (3.10674 - j3.00506) \\ = (5.5299 - j5.0106)$$




$$\begin{aligned}
 V_1 &= V_2 + I_2 \cdot Z_{12} \\
 &= (6359.44 \angle -30.0106^\circ) + (5.5299 - j5.0106)(0.53 + j0.035) \\
 &= 6363.36 \angle -30.0158^\circ
 \end{aligned}$$

$$\Rightarrow V_{1LL} = 11021.66 \angle -30.0158^\circ$$

$$I_{S1} = \frac{\left( \frac{120 - j30}{3} \right) \cdot 10^3}{6363.36 \angle 30.0158} = 4.6568 - j4.50523$$
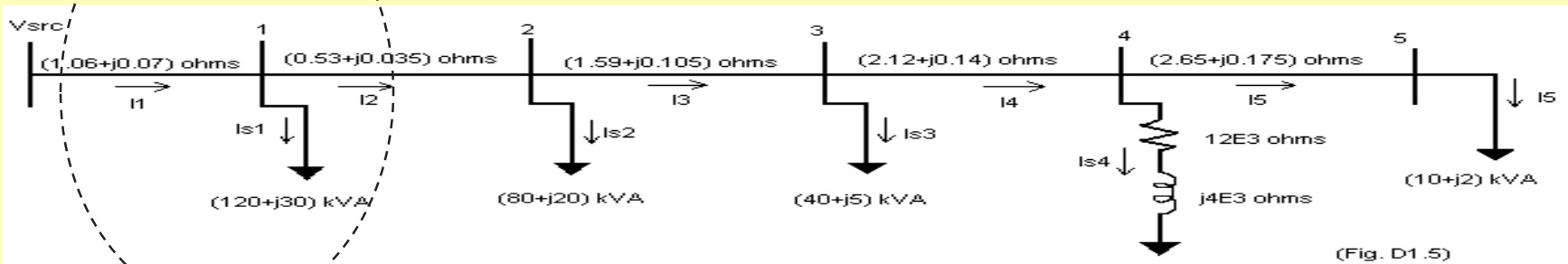
$$\begin{aligned}
 I_1 &= I_2 + I_{S1} = (5.5279 - j5.0106) + (4.6568 - j4.50523) \\
 &= (10.1847 - j9.5158)
 \end{aligned}$$



$$V_{SRC} = V_1 + I_1 \cdot Z_{S1}$$

$$= (6363.36 \angle -30.0158^\circ) + (10.1847 - j9.5158)(1.06 + j0.07)$$


$$= 6377.97 \angle -30.0372^\circ$$

$$\Rightarrow V_{SRC, LL} = 11046.98 \angle -30.0372^\circ$$

$$I_{SRC} = I_1$$

$$P_{SRC} = P_{IN} = 3 \operatorname{Re} \left\{ (V_{SRC})(I_{SRC})^* \right\} = \operatorname{Re} \left\{ \left( (6377.97 \angle -30.0372^\circ)(10.1847 - j9.5158)^* \right) \right\}$$
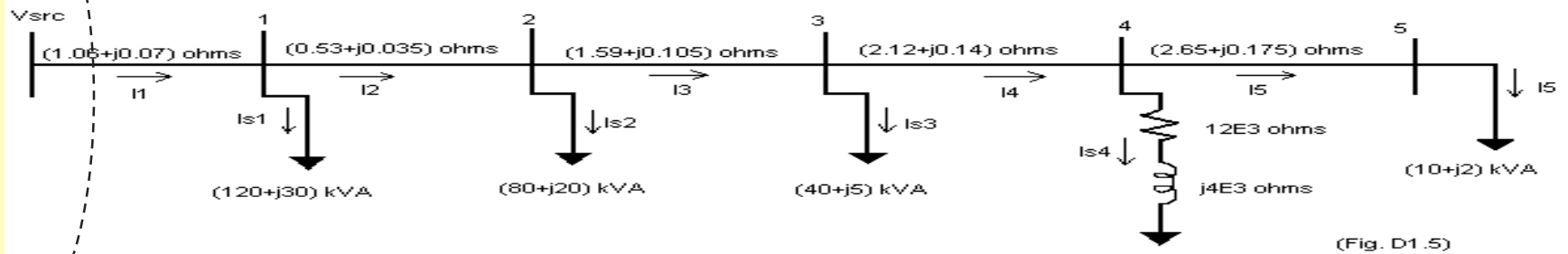
$$= 3 \operatorname{Re} \{ (86,613.79 + j20025.28) \} = 3(86,613.79) = 259,841.4 \text{ watts}$$



*Losses :*

$$I5^2 \cdot R45 = .7592$$

$$I4^2 \cdot R34 = 2.273$$

$$I3^2 \cdot R23 = 15.716$$

$$I2^2 \cdot R12 = 29.502$$

$$I1^2 \cdot RS1 = 205.935$$

$$TOTAL = 3(254.19) = 762.57 = P_{LOSS}$$

*Efficiency ( $\eta$ ):*

$$\eta = \frac{P_{IN} - P_{LOSS}}{P_{IN}} \times 100\%$$


$$\eta = \frac{259814.4 - 762.57}{259814.4} \times 100\% = 99.71\%$$

*regulation %reg :*

$$\%reg = \frac{|VLL, SRC| - |VLL, 5|}{|VLL, SRC|} \times 100\%$$

$$\%reg = \frac{11046.98 - 11000}{11046.98} \times 100\% = 0.425\%$$

# Two Port Networks

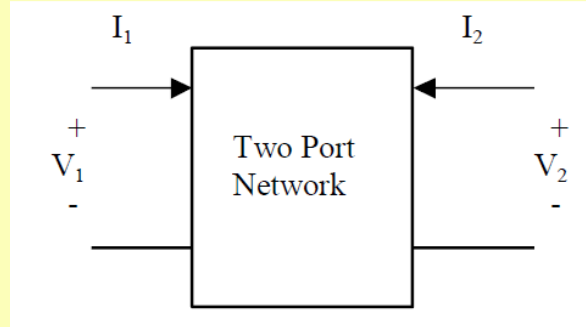


A two-port network is a linear network having two pairs of terminals: input and output.

It can contain any of the following components:

- R, L, C
- Transformers
- Op-amps
- Dependent sources

But it cannot contain *independent* sources.

# Two Port Networks

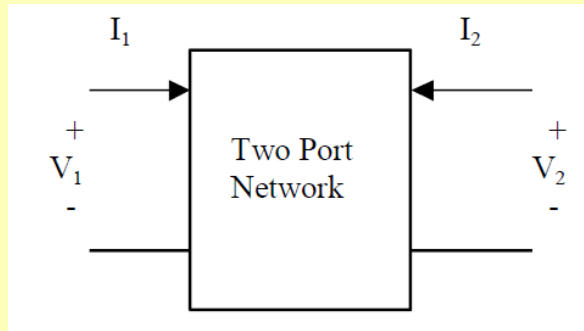


We may use two-ports to describe a number of different types of circuits including:

- Transistor circuits
- Transformers
- Transmission lines
- Distribution lines

Two ports are attractive because, no matter how complex what is inside the box, we may describe it with only four parameters! There are six “4-parameter sets” as given on the next slide.



# Two Port Networks

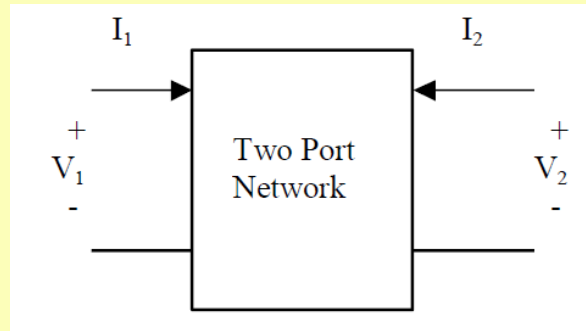

Z (impedance) parameters 
$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = Z \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

Y (admittance) parameters 
$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = Y \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

H (hybrid) parameters 
$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix} = H \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

G (inverse hybrid) parameters 
$$\begin{bmatrix} I_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = G \begin{bmatrix} V_1 \\ I_2 \end{bmatrix}$$

a (transmission) parameters 
$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} a_{11} & a_{12} \\ a_{21} & a_{22} \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix} = A \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$

b (inverse transmission) parameters 
$$\begin{bmatrix} V_2 \\ I_2 \end{bmatrix} = \begin{bmatrix} b_{11} & b_{12} \\ b_{21} & b_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = B \begin{bmatrix} V_1 \\ I_1 \end{bmatrix}$$

a-parameters and ABCD parameters are the same except in ABCD, we reverse the direction of the current  $I_2$ .

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix} = T \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$

# Two Port Networks

Given two-port equations, each different set of parameters may be determined, one parameter at a time, according to the following procedure:

1. Pull out the equation containing the parameter of interest;
2. Solve the equation for the parameter of interest.
3. Set to zero the current or voltage necessary to eliminate the remaining parameter from the equation.

# Example

Consider the Y-parameters.

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

Let's determine  $y_{21}$ .

Step1: Pull out the equation containing the parameter of interest:

$$I_2 = y_{21}V_1 + y_{22}V_2$$

Step2: Solve the equation for parameter of interest:

$$y_{21} = \frac{I_2 - y_{22}V_2}{V_1}$$

Step3: Set to zero the current or voltage necessary to eliminate the remaining parameter from the equation:

$$y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0}$$

# Your turn

Consider the Y-parameters.

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

Let's determine  $y_{11}$ .

Step1: Pull out the equation containing the parameter of interest:

Step2: Solve the equation for parameter of interest:

Step3: Set to zero the current or voltage necessary to eliminate the remaining parameter from the equation:

# Your turn

Consider the Y-parameters.

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

Let's determine  $y_{11}$ .

Step1: Pull out the equation containing the parameter of interest:

$$I_1 = y_{11}V_1 + y_{12}V_2$$

Step2: Solve the equation for parameter of interest:

$$y_{11} = \frac{I_1 - y_{12}V_2}{V_1}$$

Step3: Set to zero the current or voltage necessary to eliminate the remaining parameter from the equation:

$$y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0}$$

# Another example

Consider the Z-parameters.

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

Let's determine  $z_{11}$ .

Step1: Pull out the equation containing the parameter of interest:

$$V_1 = z_{11}I_1 + z_{12}I_2$$

Step2: Solve the equation for parameter of interest:

$$z_{11} = \frac{V_1 - z_{12}I_2}{I_1}$$

Step3: Set to zero the current or voltage necessary to eliminate the remaining parameter from the equation:

$$z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0}$$

# Conclusion

Repeated application of this procedure results in following relations:

$$z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} \quad z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0} \quad z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0} \quad z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0} \quad (\text{D1.24})$$

$$y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0} \quad y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0} \quad y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0} \quad y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0} \quad (\text{D1.25})$$

$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0} \quad h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0} \quad h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0} \quad h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0} \quad (\text{D1.26})$$

$$g_{11} = \left. \frac{I_1}{V_1} \right|_{I_2=0} \quad g_{12} = \left. \frac{I_1}{I_2} \right|_{V_1=0} \quad g_{21} = \left. \frac{V_2}{V_1} \right|_{I_2=0} \quad g_{22} = \left. \frac{V_2}{I_2} \right|_{V_1=0} \quad (\text{D1.27})$$

$$a_{11} = \left. \frac{V_1}{V_2} \right|_{I_2=0} \quad a_{12} = \left. \frac{V_1}{I_2} \right|_{V_2=0} \quad a_{21} = \left. \frac{I_1}{V_2} \right|_{I_2=0} \quad a_{22} = \left. \frac{I_1}{I_2} \right|_{V_2=0} \quad (\text{D1.28})$$

$$b_{11} = \left. \frac{V_2}{V_1} \right|_{I_1=0} \quad b_{12} = \left. \frac{V_2}{I_1} \right|_{V_1=0} \quad b_{21} = \left. \frac{I_2}{V_1} \right|_{I_1=0} \quad b_{22} = \left. \frac{I_2}{I_1} \right|_{V_1=0} \quad (\text{D1.29})$$

Question1: What does it mean to set a voltage to 0?

→ Short the two terminals across which that voltage appears!


Question2: What does it mean to set a current to 0?

→ Open the branch through which that current flows!

# Question 1: What does it mean to set a voltage to 0?

→ Short the two terminals across which that voltage appears!

## How to obtain parameters: example 1.

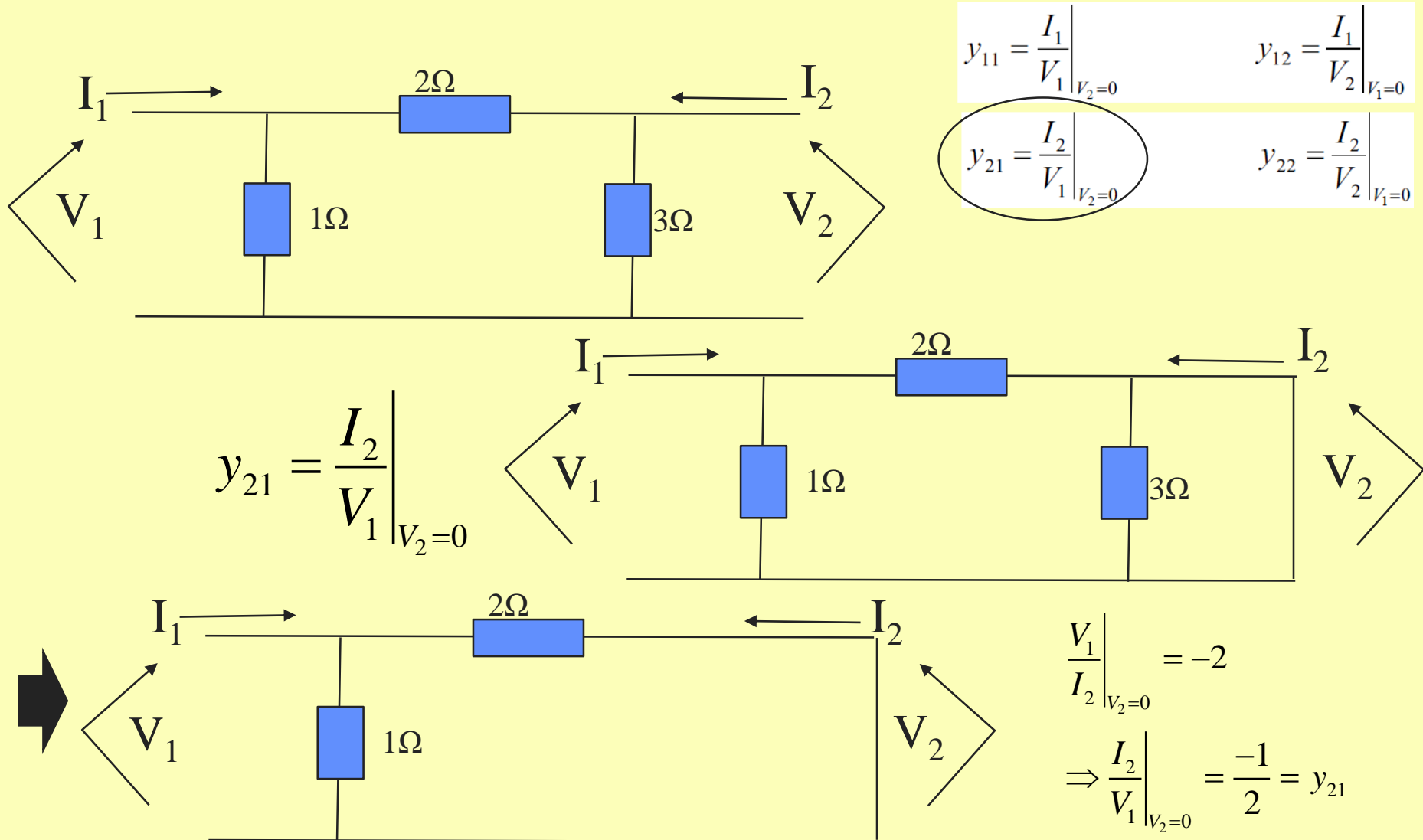




# Question 1: What does it mean to set a voltage to 0?

→ Short the two terminals across which that voltage appears!


## How to obtain parameters: example 1.

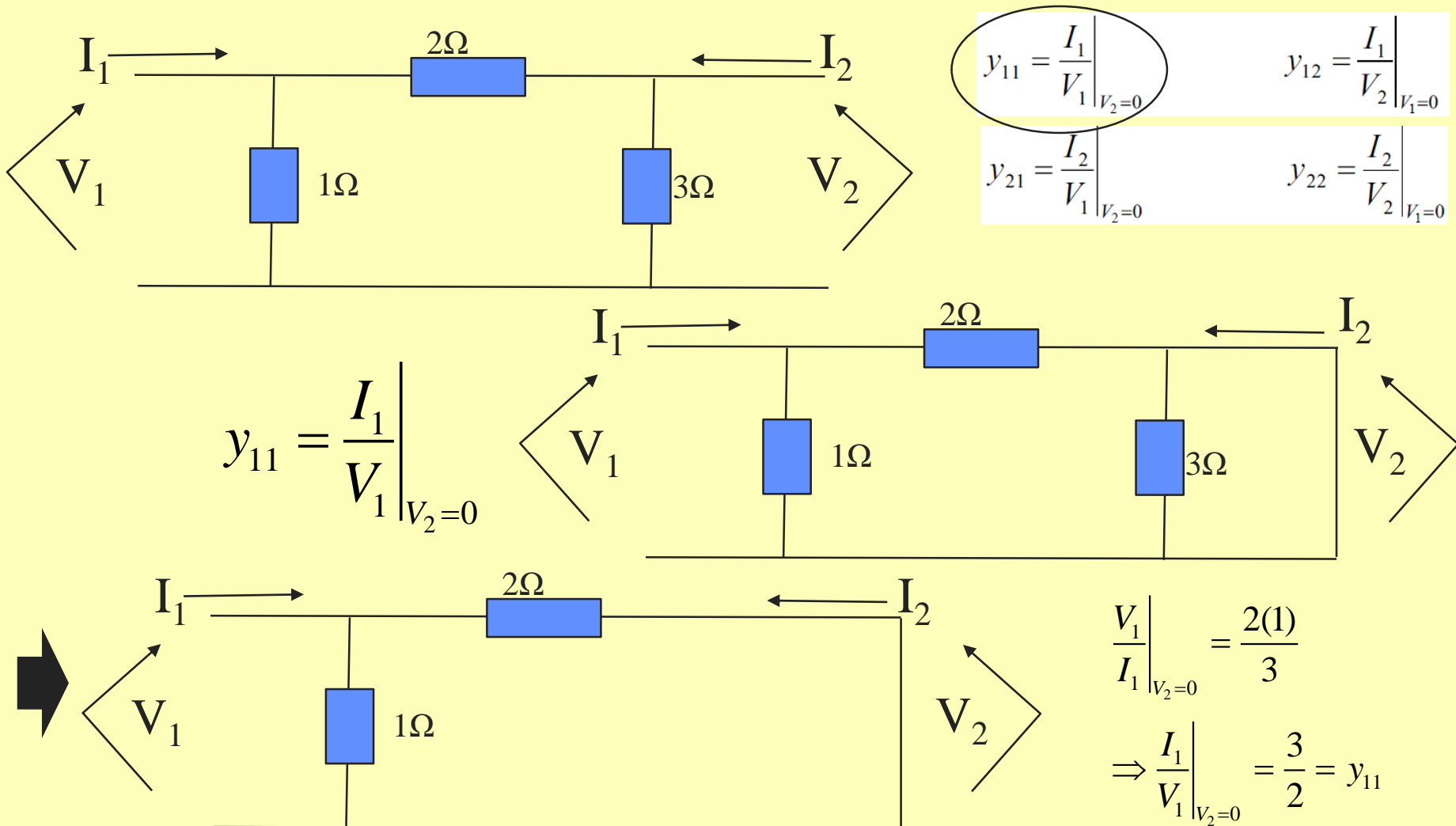

# Question 1: What does it mean to set a voltage to 0?

→ Short the two terminals across which that voltage appears!

## How to obtain parameters: example 1.

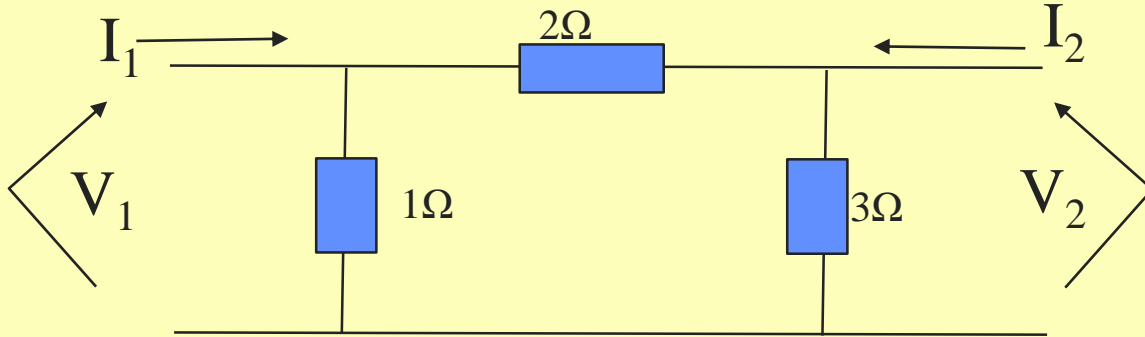



$$y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0}$$

$$y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0}$$

$$y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0}$$

$$y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0}$$

$$y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0}$$

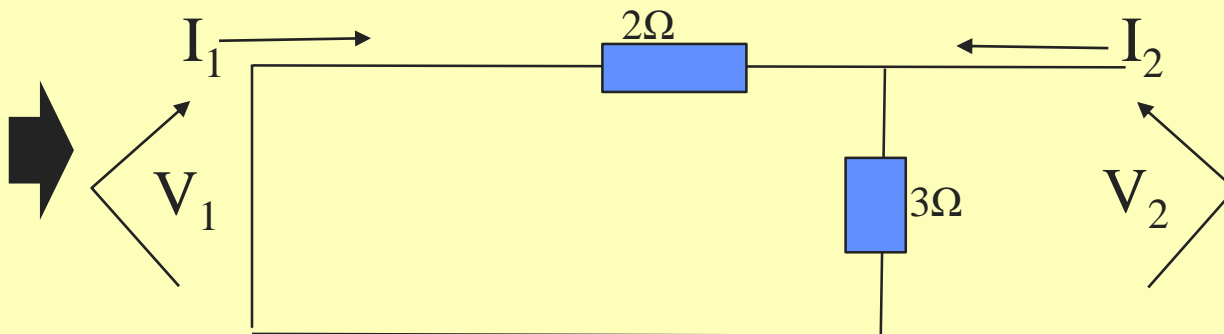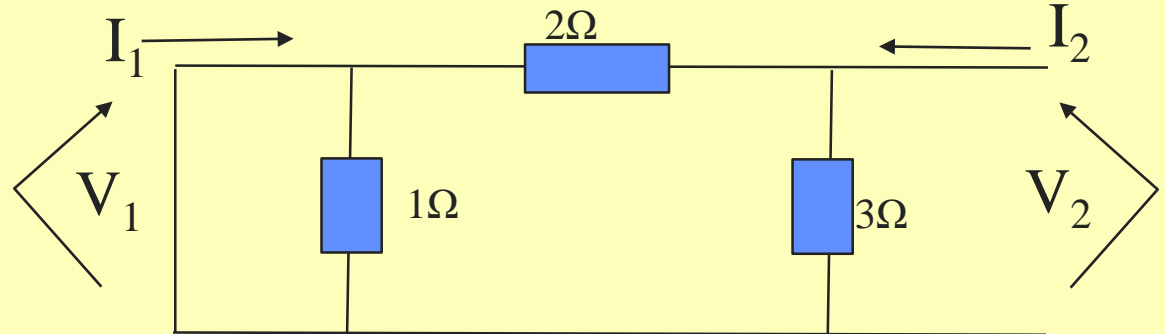


$$\frac{V_2}{I_1} \Big|_{V_1=0} = -2$$

$$\Rightarrow \frac{I_1}{V_2} \Big|_{V_1=0} = \frac{-1}{2} = y_{12}$$

# Question 1: What does it mean to set a voltage to 0?

→ Short the two terminals across which that voltage appears!

## How to obtain parameters: example 1.

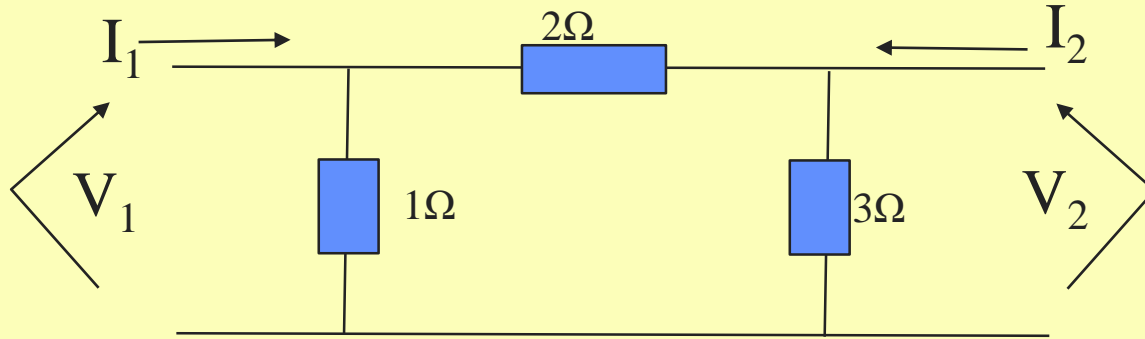



$$y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0}$$

$$y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0}$$

$$y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0}$$

$$y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0}$$

$$y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0}$$

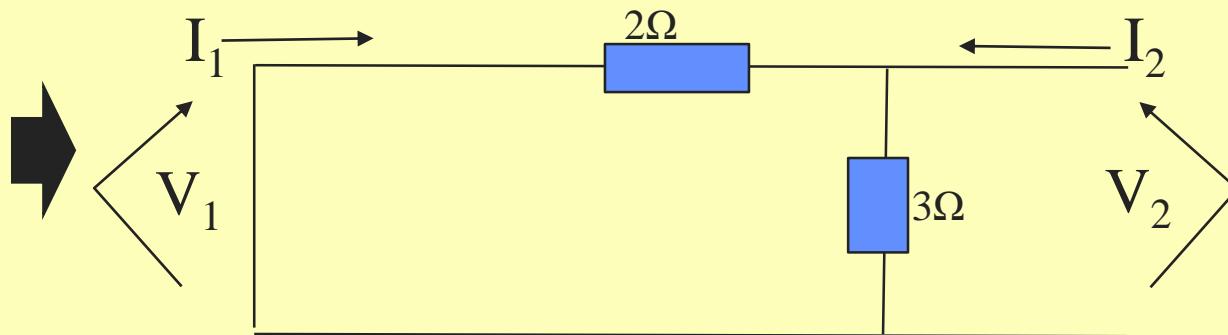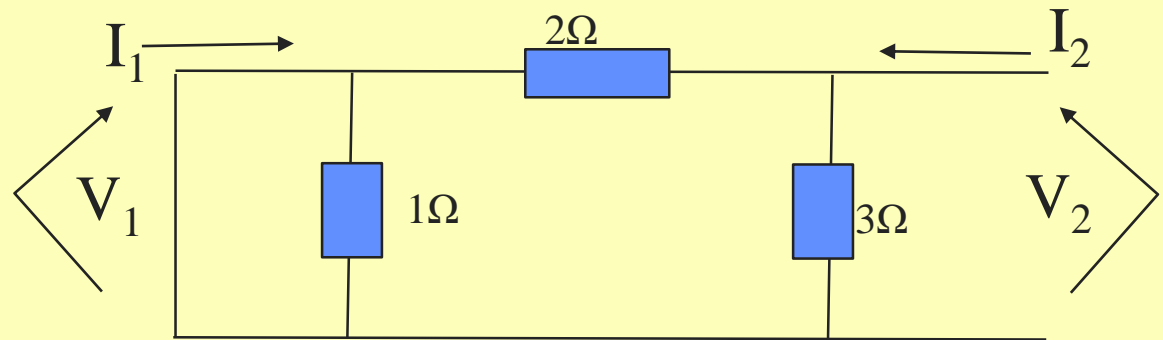

$$\left. \frac{V_2}{I_2} \right|_{V_1=0} = \frac{2(3)}{5} = \frac{6}{5}$$

$$\Rightarrow \left. \frac{I_2}{V_2} \right|_{V_1=0} = \frac{5}{6} = y_{22}$$

# Summary

How to obtain parameters: example 1.

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} \quad \longrightarrow \quad \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} \frac{3}{2} & \frac{-1}{2} \\ \frac{-1}{2} & \frac{5}{6} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$


Aside (to connect to previous work): Recall Y-bus construction:

(1) off-diagonal Y-bus elements are negated admittances of lines connecting buses corresponding to Y-bus row/column nums.

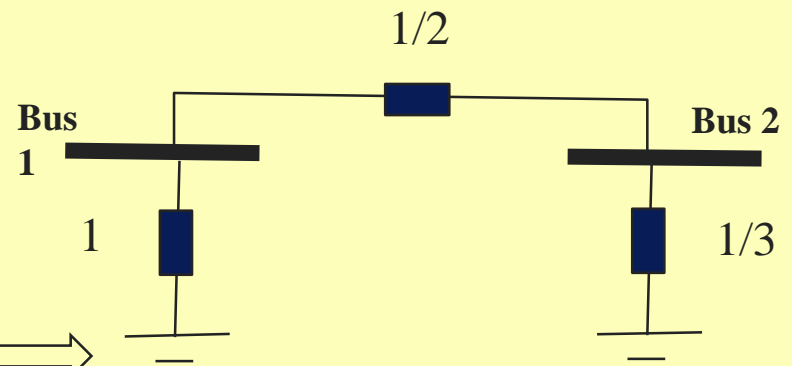(2) diagonal Y-bus elements are sum of all admittances connected to bus with corresponding bus num.

$$\rightarrow 3/2 = y_{1s} + 1/2 \rightarrow y_{1s} = 1$$

$$\rightarrow 5/6 = y_{2s} + 1/2 \rightarrow y_{2s} = 2/6 = 1/3$$




Y-bus: see next slide to see if network is same!!!

# Summary

How to obtain parameters: example 1.


The original network

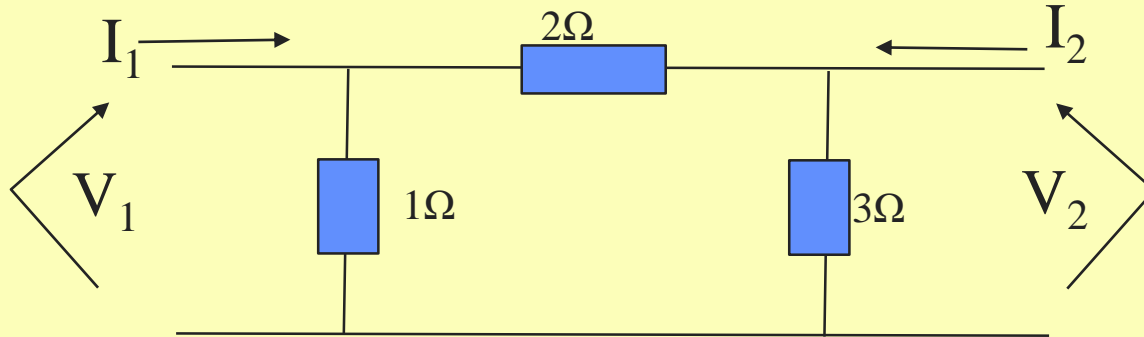

Are they the same?

→ Note the numbers in the top network are impedances whereas the numbers in the bottom network are admittances.

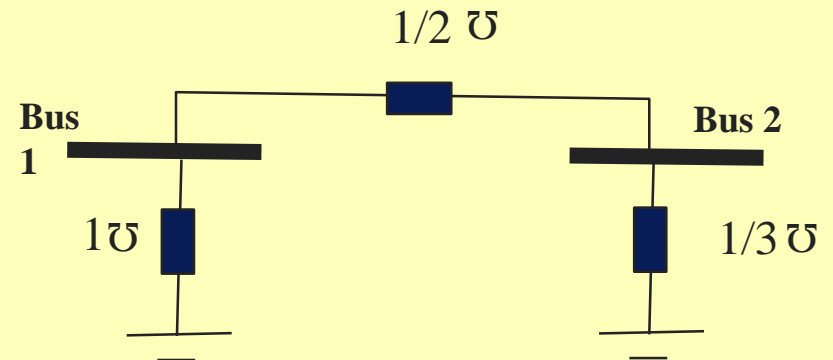
The Y-bus resulting from the two-port calculations



# Question2: What does it mean to set a current to 0?

→ Open the branch through which that current flows!

## How to obtain parameters: example 2.

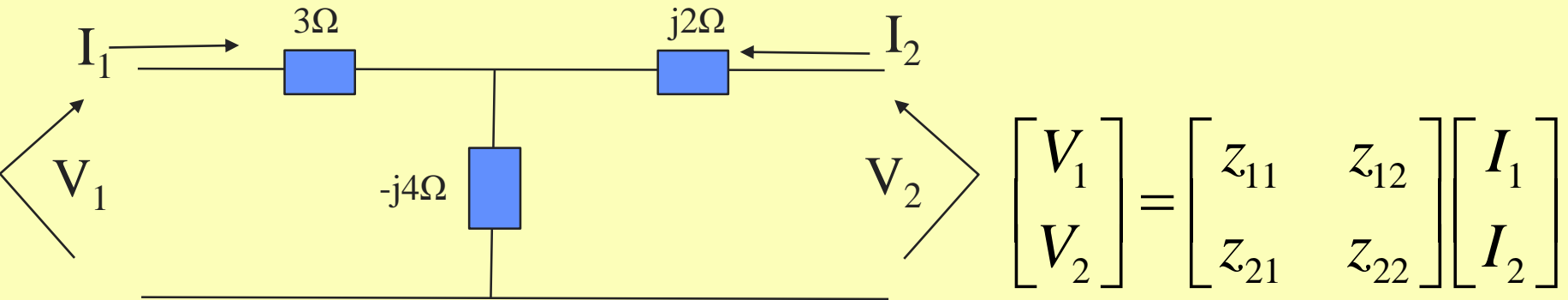

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$V_1 = z_{11}I_1 + z_{12}I_2$$



$$z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} = 3 - j4$$

The series combination of the  $3\Omega$  and the  $-j4\Omega$  impedances.

$$z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0} = -j4$$

The voltage across and current through the  $-j4\Omega$  impedance.

$$V_2 = z_{21}I_1 + z_{22}I_2$$



$$z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0} = -j4$$


The voltage across and current through the  $-j4\Omega$  impedance.

$$z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0} = j2 - j4 = -j2$$


The series combination of the  $j2\Omega$  and the  $-j4\Omega$  impedances.
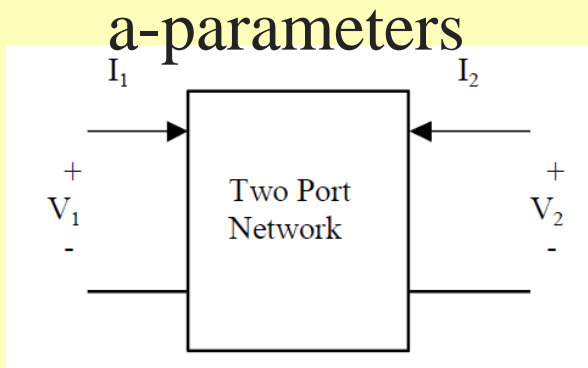
# a-parameters and ABCD parameters

The “a-parameters” (also called “transmission parameters” and “ABCD parameters”) are useful for analysis of dist ccts because they provide the ability to compute input voltage and current as a function of output voltage and current.


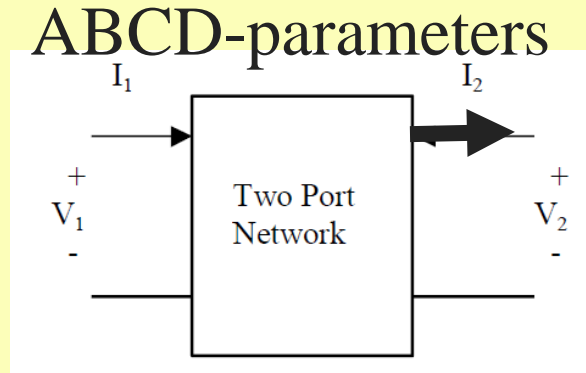
$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} a_{11} & a_{12} \\ a_{21} & a_{22} \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$



$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$

The ABCD parameters are the same except for the direction of  $I_2$ .

The a-parameters are more common in circuit theory, including electronic cct design; the ABCD parameters are common in power.

# ABCD parameters

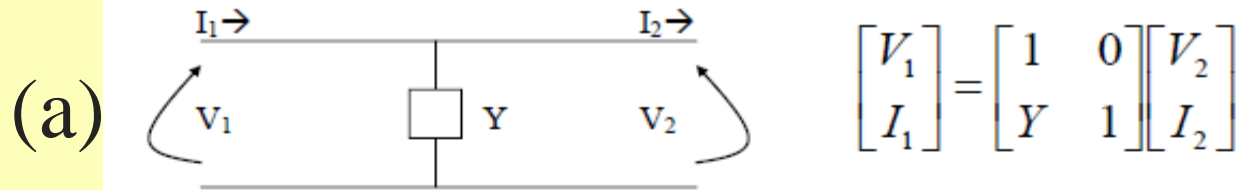


Fig. D1.14: ABCD parameters for "T" circuit

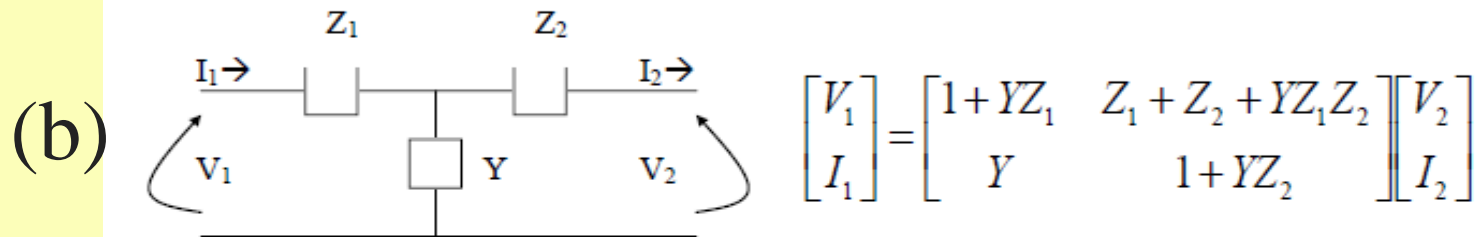


Fig. D1.15: ABCD parameters for "T" circuit

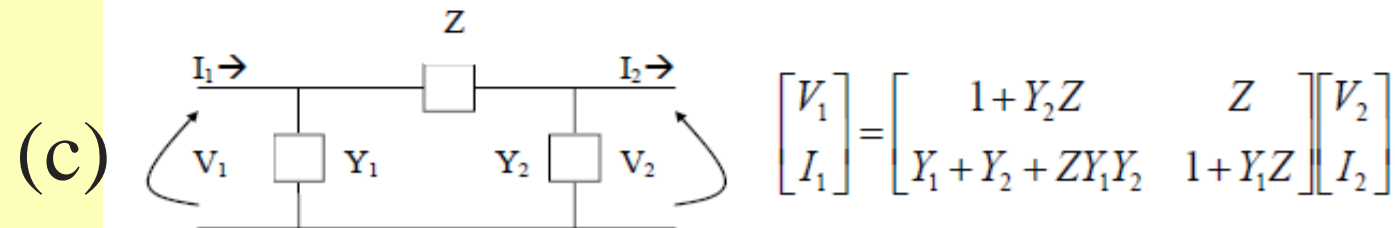


Fig. D1.16: ABCD parameters for "π" circuit

**Strong suggestion before final exam: Prove that above 3 matrices indeed give ABCD parameters for the given configuration.**




# ABCD parameters


Below, I have done (b) for you. You should first do (a) (it is easiest) and then do (c). One of these is likely to be on the exam.

(b)  $A = \frac{V_1}{V_2} \Big|_{I_2=0}$   
 use voltage division:  
 $V_2 = V_1 \left[ \frac{1/Y}{Z_1 + 1/Y} \right]$   
 $\Rightarrow \frac{V_1}{V_2} = \frac{Z_1 + \frac{1}{Y}}{1/Y} = Z_1 Y + 1 = A$

$B = \frac{V_1}{I_2} \Big|_{V_2=0}$

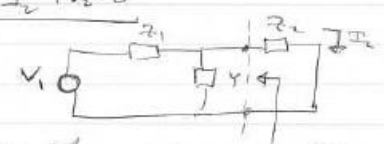


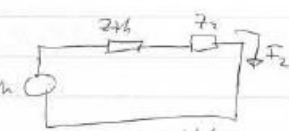Use Thevenin's:  
 $Z_{th} = \frac{Z_1 \cdot \frac{1}{Y}}{Z_1 + \frac{1}{Y}} = \frac{Z_1}{1 + Z_1 Y}$   
 $V_{th} = V_1 \left[ \frac{1/Y}{Z_1 + 1/Y} \right] = V_1 \left[ \frac{1}{1 + Z_1 Y} \right]$




$I_2 = \frac{V_{th}}{Z_{th} + Z_2} = \frac{V_1 \left[ \frac{1}{1 + Z_1 Y} \right]}{\frac{Z_1}{1 + Z_1 Y} + Z_2}$   
 $\Rightarrow \frac{V_1}{I_2} = \frac{\frac{Z_1}{1 + Z_1 Y} + Z_2}{\frac{1}{1 + Z_1 Y}} = \frac{Z_1 + Z_2(1 + Z_1 Y)}{1} = Z_1 + Z_2 + Z_1 Z_2 Y = B$

$C = \frac{I_1}{V_2} \Big|_{I_2=0}$

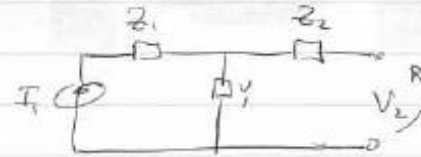


$\Rightarrow V_2 = \frac{I_1}{Y} \Rightarrow \frac{I_1}{V_2} = Y = C$

$D = \frac{I_1}{I_2} \Big|_{V_2=0}$

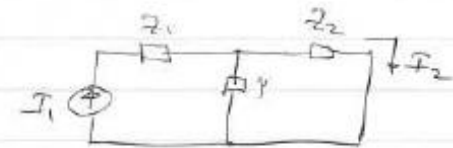

Use current division:  $I_2 = I_1 \left[ \frac{1/Y}{1/Y + Z_2} \right]$   
 $\Rightarrow I_1 = I_2 \left[ \frac{1}{1 + Y Z_2} \right] \Rightarrow \frac{I_1}{I_2} = 1 + Y Z_2 = D$
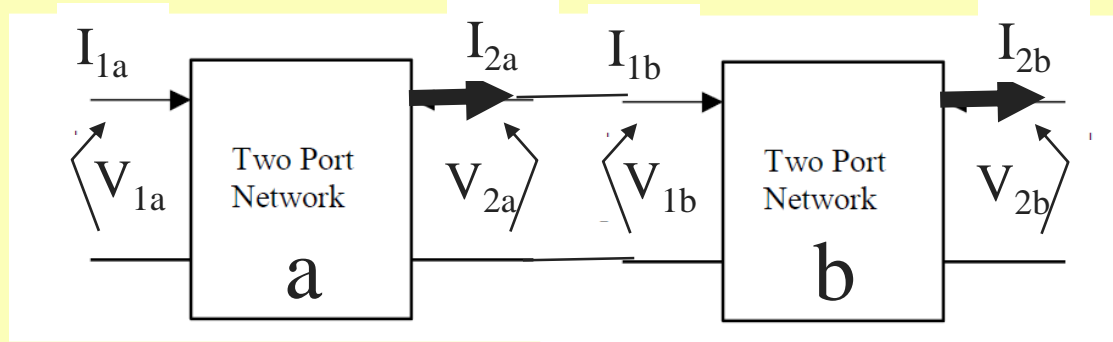
# ABCD parameters – Cascading connections



$$\begin{bmatrix} V_{1a} \\ I_{1a} \end{bmatrix} = \underbrace{\begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix}}_{T_a} \begin{bmatrix} V_{2a} \\ I_{2a} \end{bmatrix} = \begin{bmatrix} V_{1b} \\ I_{1b} \end{bmatrix} = \underbrace{\begin{bmatrix} A_b & B_b \\ C_b & D_b \end{bmatrix}}_{T_b} \begin{bmatrix} V_{2b} \\ I_{2b} \end{bmatrix}$$


These are the same, i.e.,

$$\begin{bmatrix} V_{2a} \\ I_{2a} \end{bmatrix} = \begin{bmatrix} V_{1b} \\ I_{1b} \end{bmatrix}$$

...so let's substitute RHS of right expression in for RHS vector of left expression...

$$\begin{bmatrix} V_{1a} \\ I_{1a} \end{bmatrix} = \underbrace{\begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix}}_{T_a} \underbrace{\begin{bmatrix} A_b & B_b \\ C_b & D_b \end{bmatrix}}_{T_b} \begin{bmatrix} V_{2b} \\ I_{2b} \end{bmatrix} = T_a T_b \begin{bmatrix} V_{2b} \\ I_{2b} \end{bmatrix}$$

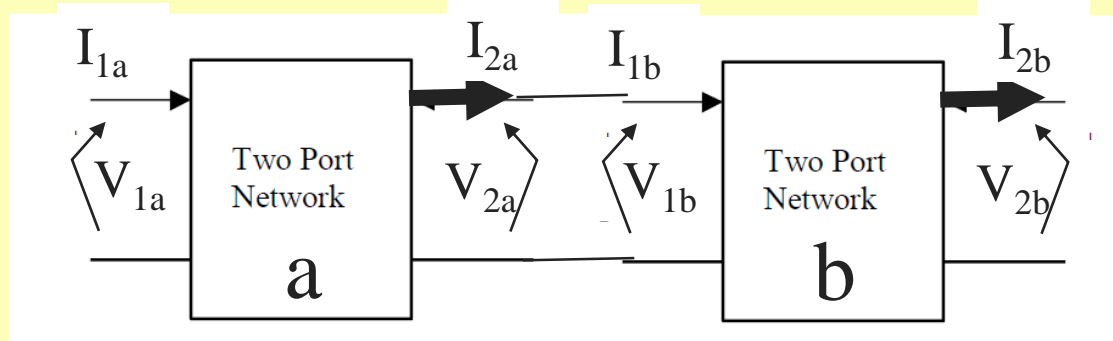
# ABCD parameters – Cascading connections




$$\begin{bmatrix} V_{1a} \\ I_{1a} \end{bmatrix} = \underbrace{\begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix}}_{T_a} \underbrace{\begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix}}_{T_a} \begin{bmatrix} V_{2a} \\ I_{2a} \end{bmatrix} = T_a T_b \begin{bmatrix} V_{2a} \\ I_{2a} \end{bmatrix}$$

So cascaded two-ports may be assessed from output (on the right) to input (on the left) by using the product of their individual ABCD parameters. Nice 😊.

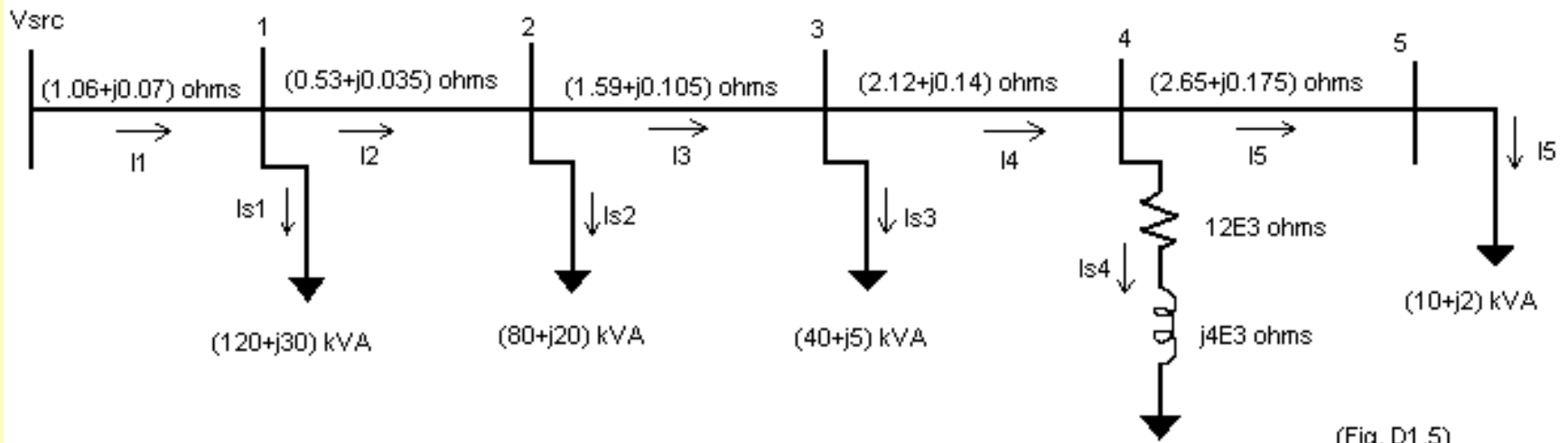We are now in position to re-work our voltage regulation problem on the 5-bus distribution feeder...see next slide. Do this in preparation for exam as well.



(Fig. D1.5)

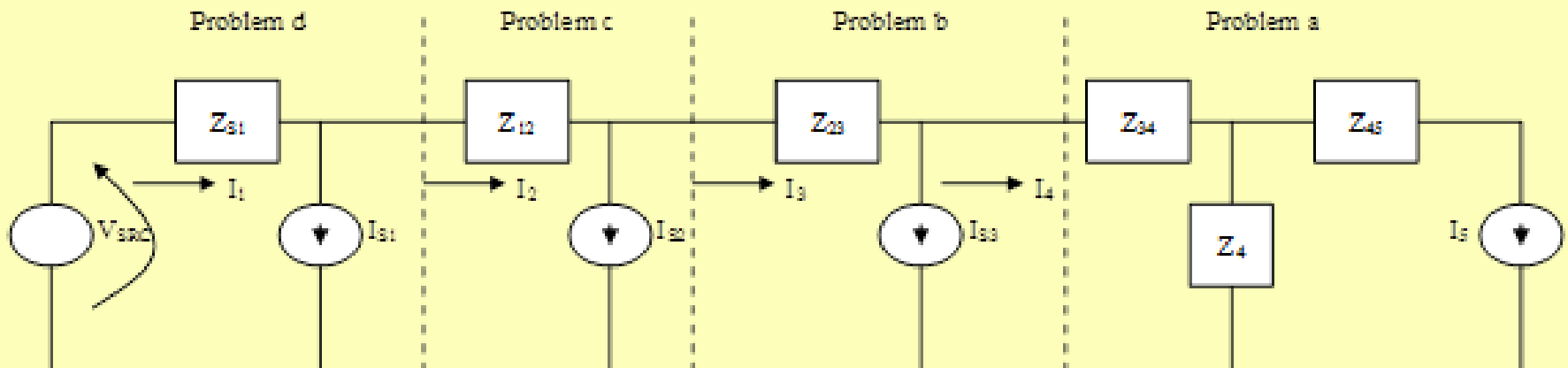

**Work Problem a:**

- Compute  $I_5$
- Get ABCD parameters
- Compute  $[V_3 \ I_4]^T$

**Work Problem b:**

- Compute  $I_{S3}$  and then  $I_3$
- Get ABCD parameters
- Compute  $[V_2 \ I_3]^T$

**Work Problem c:**

- Compute  $I_{S2}$  and then  $I_2$
- Get ABCD parameters
- Compute  $[V_1 \ I_2]^T$

**Work Problem d:**

- Compute  $I_{S1}$  and then  $I_1$
- Get ABCD parameters
- Compute  $[V_{SRC} \ I_1]^T$