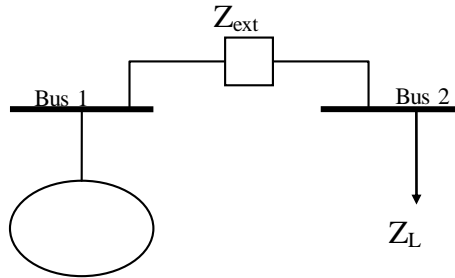


Name: _____

EE 457, Exam 1, Spring, 2015


Closed Book, Closed Notes, Closed Computer, No Communication Devices, Calculators allowed

1. (35 pts) Symmetrical Fault Analysis: Consider a single generator supplying a balanced $R+jX$ load as shown in the diagram below. The steady-state, pre-fault voltage at bus 2 is 1.02 pu.




- a. (7 pts) Draw the per-phase circuit model for this system under steady-state, pre-fault, balanced conditions. Label the steady-state generator voltage and all impedances.

Solution:

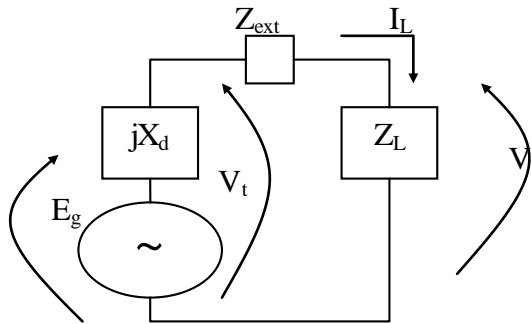

- b. (7 pts) Draw the per-phase circuit model for this system for the subtransient conditions associated with a fault at bus 2 having impedance of Z_f . Label the subtransient generator voltage and all impedances.


Solution:

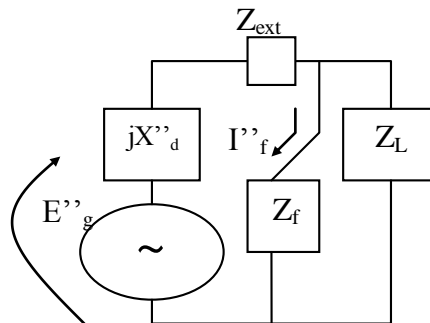

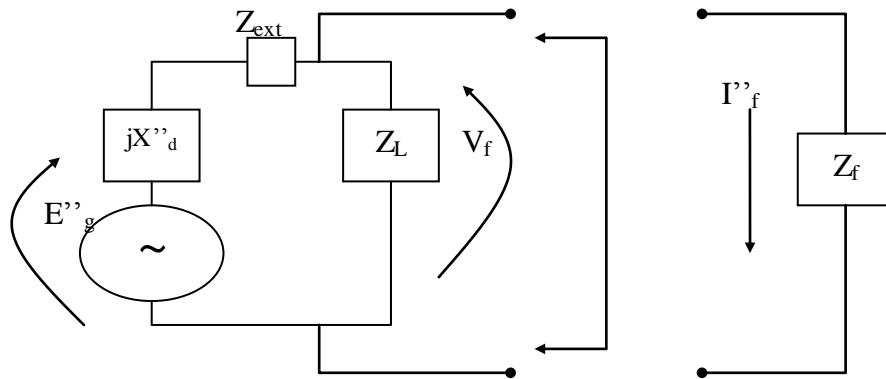
- c. (7 pts) Using the impedance values of $Z_{ext}=j0.1$ pu, $X_d=1.0$ pu, $X'_d=0.2$ pu, $X''_d=0.1$ pu, $Z_L=j10.0$, compute the Thevenin impedance and voltage of this circuit looking into the network from the fault point at bus 2.

Solution:

We compute the Thevenin equivalent circuit from the following:




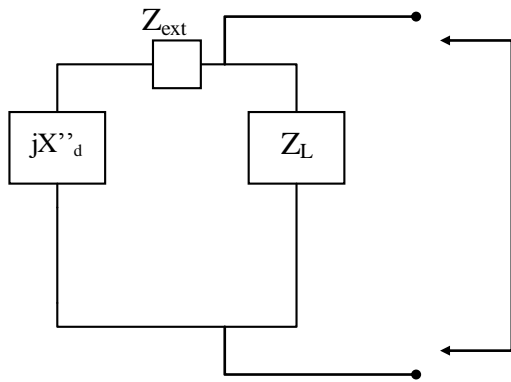The Thevenin impedance is computed from the following:



$$\begin{aligned}
 Z_{Thev} &= Z_L // (Z_{ext} + jX''_d) \\
 &= j10 * (j0.1 + j0.1) / (j10.2) \\
 &= j0.1961
 \end{aligned}$$

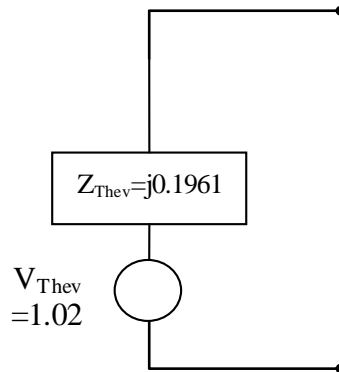The Thevenin voltage is the voltage at the fault point of the unfaulted network, which is given in the problem statement as 1.02pu. And so the Thevenin equivalent network is



- d. (7 pts) Given a fault at bus 2 through a fault impedance of $Z_f = j0.1$ pu, compute the subtransient current into the fault.

Solution:

$$I''_f = \frac{V_f}{Z_f + Z_{Thev}} = \frac{1.02}{j0.1 + j0.1961} = -j3.4448 \text{ pu}$$

- e. (7 pts) If you were to purchase a circuit breaker for bus 2, what is the minimum interruptible current rating you should ensure that it has?

Solution:

The circuit breaker must be able to interrupt 1.73 times the rms steady-state fault current, which would be (to account for the DC component), $1.73 * 3.4448 = 5.9595$ pu.

2. (21 pts) Z-bus: A three-bus network is operating so that all buses have voltage magnitudes equal to 1.0 pu. Each bus is connected to the other two buses via branches having impedance of $j0.1$ pu. The Z-bus of the network is given as:

$$\mathbf{Z} = \begin{bmatrix} j0.073 & j0.0386 & j0.0558 \\ j0.0386 & j0.0558 & j0.0472 \\ j0.0558 & j0.0472 & j0.1014 \end{bmatrix}$$

- a. (7 pts) For a bolted three-phase fault at bus 1, what is the magnitude of the short-circuit current into the fault?

Solution:

Solutions giving correct magnitude are acceptable.

$$\mathbf{I}_f^n = \frac{\mathbf{V}_f}{\mathbf{Z}_{Thev} + \mathbf{Z}_f} = \frac{\mathbf{V}_f}{\mathbf{Z}_{11}} = \frac{1.0}{j0.073} = -j13.6986 \text{ pu}$$

- b. (7 pts) For a three-phase fault through an impedance of $j0.1$ at bus 3, what is the magnitude of the short-circuit current into the fault?

$$\mathbf{I}_f^n = \frac{\mathbf{V}_f}{\mathbf{Z}_{Thev} + \mathbf{Z}_f} = \frac{\mathbf{V}_f}{\mathbf{Z}_{33} + j0.1} = \frac{1.0}{j0.1014 + j0.1} = -j4.9652 \text{ pu}$$

- c. (7 pts) We developed a formula in class for the voltage at a bus during a fault condition, for a three-phase fault, as

$$\mathbf{V}_{jf} = \mathbf{V}_j - \frac{\mathbf{Z}_{jk}}{\mathbf{Z}_{kk}} \mathbf{V}_f$$

Use the above formula to obtain the voltage at bus 2 during a three-phase fault at bus 3.


Solution:

$$\mathbf{V}_{2f} = \mathbf{V}_2 - \frac{\mathbf{Z}_{23}}{\mathbf{Z}_{33}} \mathbf{V}_f = 1.0 - \frac{.0472}{.1014} \times 1.0 = 0.5345$$

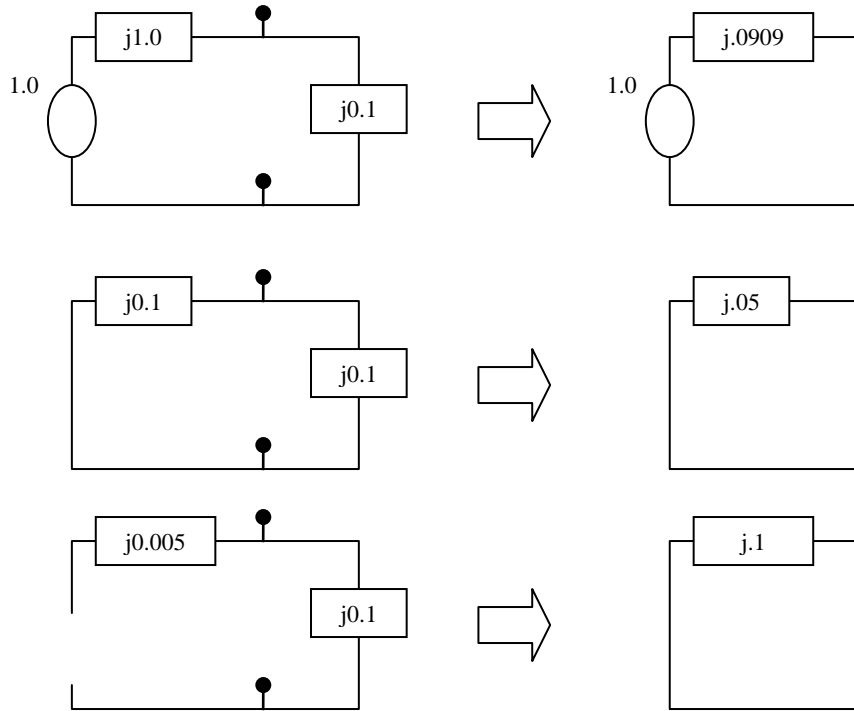
3. (24 pts) SLG fault analysis: A three-phase generator is directly connected to a balanced three-phase load having impedance of $j0.1$ per-unit, per phase. The generator impedances are $Z^+ = j1.0$, $Z^- = j0.1$, and $Z^0 = j0.005$, all in per-unit. The generator neutral is not grounded. The load neutral is grounded. A single line-to-ground fault occurs at the terminals of the generator, on phase a. Before the fault occurs, the generator is supplying positive sequence voltages and currents, with the pre-fault voltage at the fault point $\mathbf{V}_{ag} = 1.0 \angle 0^\circ$. Find the fault current \mathbf{I}_f .

SOLUTION:

Find the sequence networks and corresponding Thevenin equivalents:



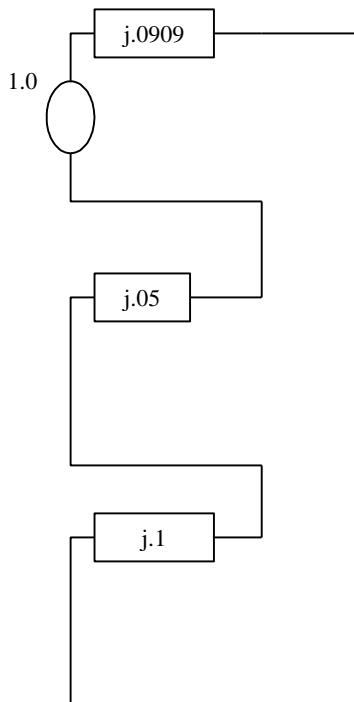Now put the three Thevenin equivalent circuits in series, according to the connections of a single-line-to-ground fault.



The resulting fault current is given as

$$I_{fa}^+ = I_{fa}^- = I_{fa}^0 = \frac{1.0}{j(.0909 + .05 + .1)} = -j4.1511$$

$$\begin{bmatrix} I_{fa} \\ I_{fb} \\ I_{fc} \end{bmatrix} = \underline{A} \begin{bmatrix} I_{fa}^0 \\ I_{fa}^+ \\ I_{fa}^- \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \begin{bmatrix} -j4.1511 \\ -j4.1511 \\ -j4.1511 \end{bmatrix}$$

$$= \begin{bmatrix} -j12.4533 \\ 0 \\ 0 \end{bmatrix}$$

So the fault current is 12.4533 pu.

4. (20 pts) True/false:

T The effect of DC offset on fault current depends on when the fault occurs relative to the voltage waveform.

F The subtransient, transient, and synchronous reactances are used to approximate the effect of the DC offset at different times following initiation of a fault.

F The Thevenin impedance for a fault at bus k is the inverse of the Y-bus element in row k, column k.

F An unsymmetrical set of 3 phasors may always be decomposed into two symmetrical positive sequence sets of phasors.

F The zero-sequence set of a set of symmetrical components are not phasors.

T Line to line voltages never have zero sequence components.

F $1+\alpha+\alpha^2=1$

T You can obtain the sequence components of the b and c phase currents from the sequence components of the a-phase currents.

F There is no coupling between the positive, negative, and zero-sequence networks unless the applied abc voltages are unbalanced.

F If zero-sequence currents flow into the primary of a transformer, then they must also flow out of the secondary of the transformer.