

Recitation Material for Week 6
 Tasks to do in the recitation section
 Assigned Date: Fifth Week

- T1. Review HW05 and solve any problems that students point out they had difficulty with.
- T2. Answer any general questions about Mid-term #1 and Lab 05 that students ask.
- T3. Solve the following problems in order until time runs out.
1. Consider a multiplexer function $Mux(X, Y, Z) = X'Y + XZ$ where X is the selection signal. Show that $Mux(X, Y, Z) = X'Y + XZ + YZ$ is equivalent to the original equation using **Boolean algebra** rules. Intuitively explain why YZ term is redundant.
 2. In the following expression, uses the equivalence of Part 1 (above) to identify groups of three product terms such that each group can be reduced into two product terms. Please write down the simplified expression.

$$Z = PQ + RS + PR' + PS + Q'S + Q'R'$$
 3. Draw a K-map for the original expression Z in Part 2 (above). Then derive the simplest SOP expression.
 4. Derive the min-cost implementation using a K-map for the function F below.

P Q R S	F
0 0 0 0	1
0 0 0 1	1
0 0 1 0	D
0 0 1 1	1
0 1 0 0	0
0 1 0 1	0
0 1 1 0	0
0 1 1 1	D
1 0 0 0	1
1 0 0 1	1
1 0 1 0	0
1 0 1 1	1
1 1 0 0	1
1 1 0 1	1
1 1 1 0	0
1 1 1 1	1

5. Demonstrate programming the functions Z in Part 2 and F in Part 4 above in a PLA. Please use as few AND gates as possible.