

CprE 281: Digital Logic
Midterm 2: Friday Oct 30, 2015

Student Name:

Student ID Number:


Lab Section: (circle one)	Mon 9-12(N) Tue 2-5(M) Thur 2-5(L)	Mon 12-3(P) Wed 8-11(J) Thur 5-8(K)	Mon 5-8(R) Wed 6-9(Y)	Tue 11-2(U) Thur 11-2(Q) Fri 11-2(G)
------------------------------	--	---	--------------------------	--

1. True/False Questions (10 x 1p each = 10p)

- (a) I forgot to write down my name and student ID number. TRUE / FALSE
- (b) Any Boolean function can be implemented using only T flip-flops. TRUE / FALSE
- (c) A D flip-flop can be implemented with a JK flip-flop and one NOT gate. TRUE / FALSE
- (d) A T flip-flop can be implemented with a D flip-flop and one XOR gate. TRUE / FALSE
- (e) A T flip-flop can be implemented with a D flip-flop and a 2-to-1 multiplexer. TRUE / FALSE
- (f) A T flip-flop can be implemented with only 6 NAND gates. TRUE / FALSE
- (g) A 1-to-2 decoder can be implemented with only one NOT gate. TRUE / FALSE
- (h) Any function $f(x,y,z)$ can be realized with a 3-to-8 decoder and one OR gate. TRUE / FALSE
- (i) The total delay through a full-adder is 2 gate delays. TRUE / FALSE
- (j) In a carry-lookahead adder all sum signals are generated after 3 gate delays. TRUE / FALSE

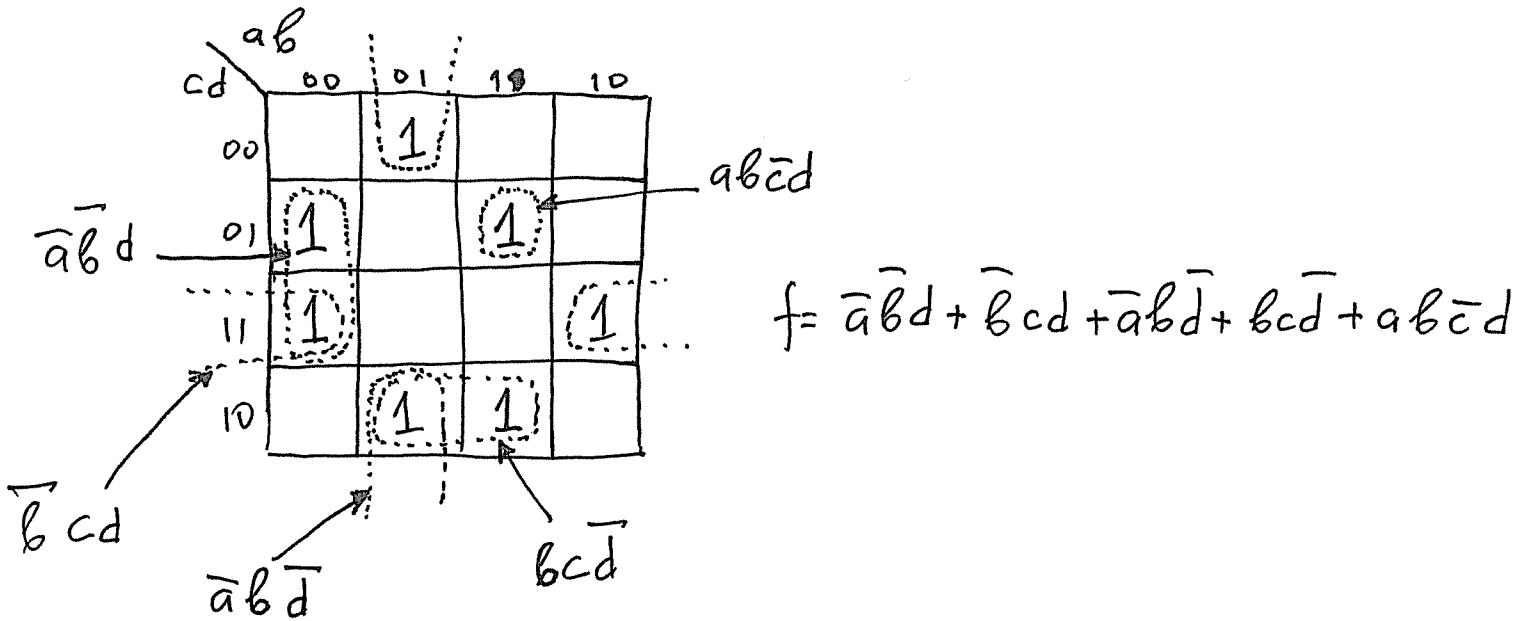2. Minimization using a K-map (5p)

Draw the K-map for the function $f(a,b,c,d) = \sum m(1,3,4,6,11,13,14)$. Then use the K-map to derive the minimized SOP expression for the function f.



3. Binary Addition and Subtraction (5 x 3p each = 15p)

Convert the following integers into binary numbers and perform the addition or subtraction using 2's complement if necessary. Write your answers and all intermediary steps to the right of each problem. Use 5-bit numbers for all problems and indicate if any bits need to be ignored.

$$\begin{array}{r}
 (+11) & 01011 \\
 + (+2) & + 00010 \\
 \hline
 +13 & 01101
 \end{array}$$

$$\begin{array}{r}
 (+9) & 01001 \\
 + (-6) & + \underline{(-00110)} \Rightarrow 2's \\
 \hline
 +3 & + 11010 \\
 & \text{ignore} \rightarrow \textcircled{1} 00011
 \end{array}$$

$$\begin{array}{r}
 (-4) & (-00100) \Rightarrow 2's & 11100 \\
 + (+10) & + 01010 & + 01010 \\
 \hline
 +6 & \text{ignore} \rightarrow \textcircled{1} 00110
 \end{array}$$

$$\begin{array}{r}
 (-2) & (-00010) \Rightarrow 2's & 11110 \\
 - (-5) & - \underline{(-00101)} \Rightarrow 2's & - 11011 \Rightarrow 2's \\
 \hline
 +3 & \text{ignore} \rightarrow \textcircled{1} 00011
 \end{array}$$

$$\begin{array}{r}
 (-12) & (-01100) \Rightarrow 2's & 10100 \\
 - (-8) & - \underline{(-01000)} \Rightarrow 2's & - 11000 \Rightarrow 2's \\
 \hline
 -4 & \text{ignore} \rightarrow \textcircled{1} 01000 \\
 & & + 10100 \\
 & & + 01000 \\
 & & \hline
 & & 11100
 \end{array}$$

4. Number Conversions (3p + 4p + 4p + 4p = 15p)

(a) Convert 196_{10} to binary:

$$\begin{array}{r} 196/2 = 98 \quad 0 \\ 98/2 = 49 \quad 0 \\ 49/2 = 24 \quad 1 \\ 24/2 = 12 \quad 0 \\ 12/2 = 6 \quad 0 \\ 6/2 = 3 \quad 0 \\ 3/2 = 1 \quad 1 \\ 1/2 = 0 \quad 1 \end{array}$$

$$11000100_2 = 196_{10}$$

$$\text{check: } 128 + 64 + 4 = 196$$

(b) Convert the following 32-bit float number (in IEEE 754 format) to decimal

$$\begin{array}{c} 1 \ 10000101 \ 10100000000000000000000 \\ \text{negative} \end{array} ; 2^{127} 2^{-2} 2^{-3}$$

$$(-1)^1 \times 2^{133-127} \times \left(1 + \frac{1}{2} + \frac{1}{8}\right) = -2^6 \times \frac{13}{8} = -2^3 \times 13 = -13 \times 8 = -104$$

(c) Write down the 32-bit floating point representation (in IEEE 754 format) for 0110_2

$$0110_2 = 6_{10}$$

The highest power of 2 less than 6 is $2^2 = 4$.

$$6/4 = 1.5$$

$$6 = (-1)^0 \times \underbrace{2^2}_{2^{129-127}} \times \left(1 + \frac{1}{2}\right)$$

$$\begin{array}{r} -4 \\ \hline 20 \\ -20 \\ \hline 0 \end{array}$$

$$\begin{array}{c} 0 \ 10000001 \ 1000 \dots \dots 0 \\ \text{positive} \end{array} \quad 22 \text{ zeros}$$

(d) Write down the 32-bit floating point representation (in IEEE 754 format) for -7_{10}

$$-7/4 = 1.75$$


$$(-1)^1 \times \underbrace{2^2}_{2^{129-127}} \times \left(1 + \frac{1}{2} + \frac{1}{4}\right)$$

$$\begin{array}{r} -4 \\ \hline 30 \\ -28 \\ \hline 20 \\ -20 \\ \hline 0 \end{array}$$

$$\begin{array}{c} 1 \ 10000001 \ 1100 \dots \dots 0 \\ \text{negative} \end{array} \quad 21 \text{ zeros}$$

5. Implementation using an Adder (7p + 3p = 10p)

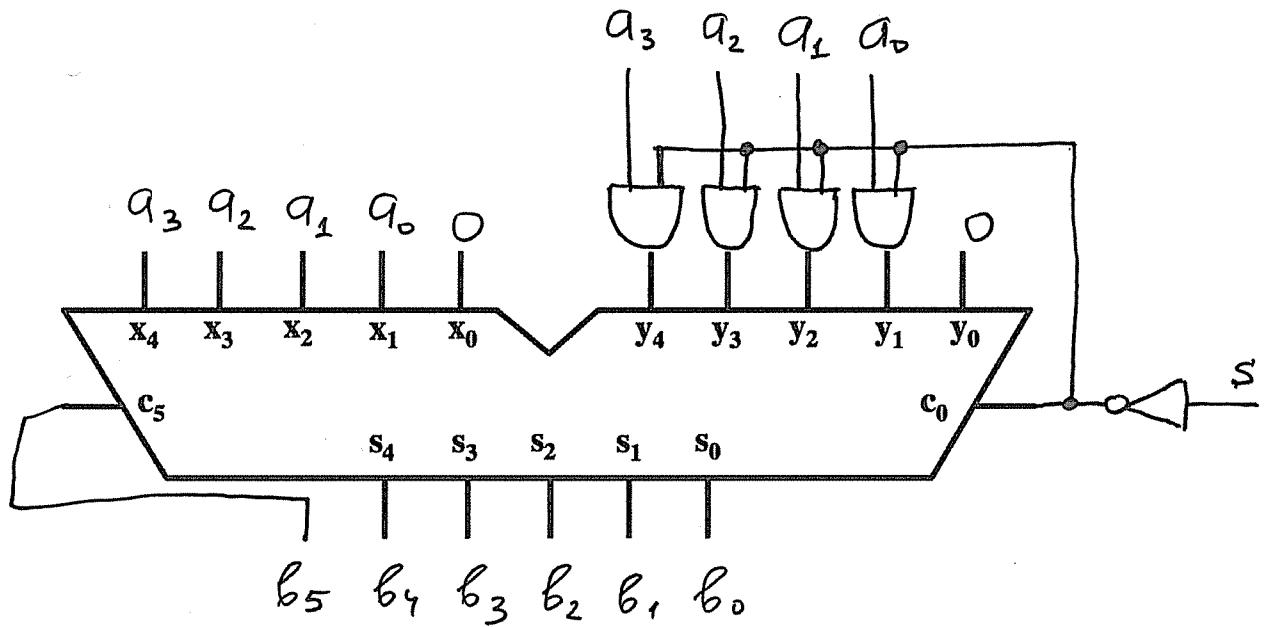- a) Let A (a_3, a_2, a_1, a_0) be a 4-bit number, let B ($b_5, b_4, b_3, b_2, b_1, b_0$) be a 6-bit number, and let s be a 1-bit number. Draw a circuit that uses the 5-bit adder shown below and any other basic logic gates (ANDs, ORs, or NOTs) to compute the value of B as follows: if $s=0$ then $B = 4A+1$; if $s=1$ then $B=2A$. Clearly label all inputs and outputs. (7p)




- b) Explain your solution. (3p)

If $s=1$, then $C_0=0$ and the four AND gates all output 0. In that case the adder will add $2A+0=2A$.


If $s=0$, then $C_0=1$ and the four AND gates reduce to repeaters of their a_i input. Thus, the adder will compute $2A+2A+1=4A+1$. In both cases the multiplication by 2 is achieved by shifting the bits of A by 1 to the left.

6. Flip-Flops and Timing Diagrams (5p + 10p = 15p)

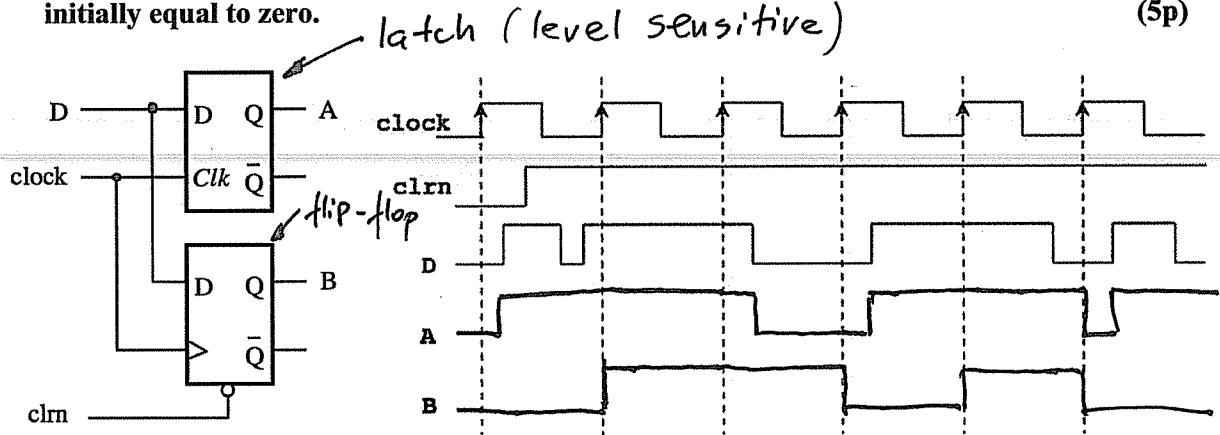- a) Complete the timing diagram for the circuit shown below. Assume that both A and B are initially equal to zero. (5p)



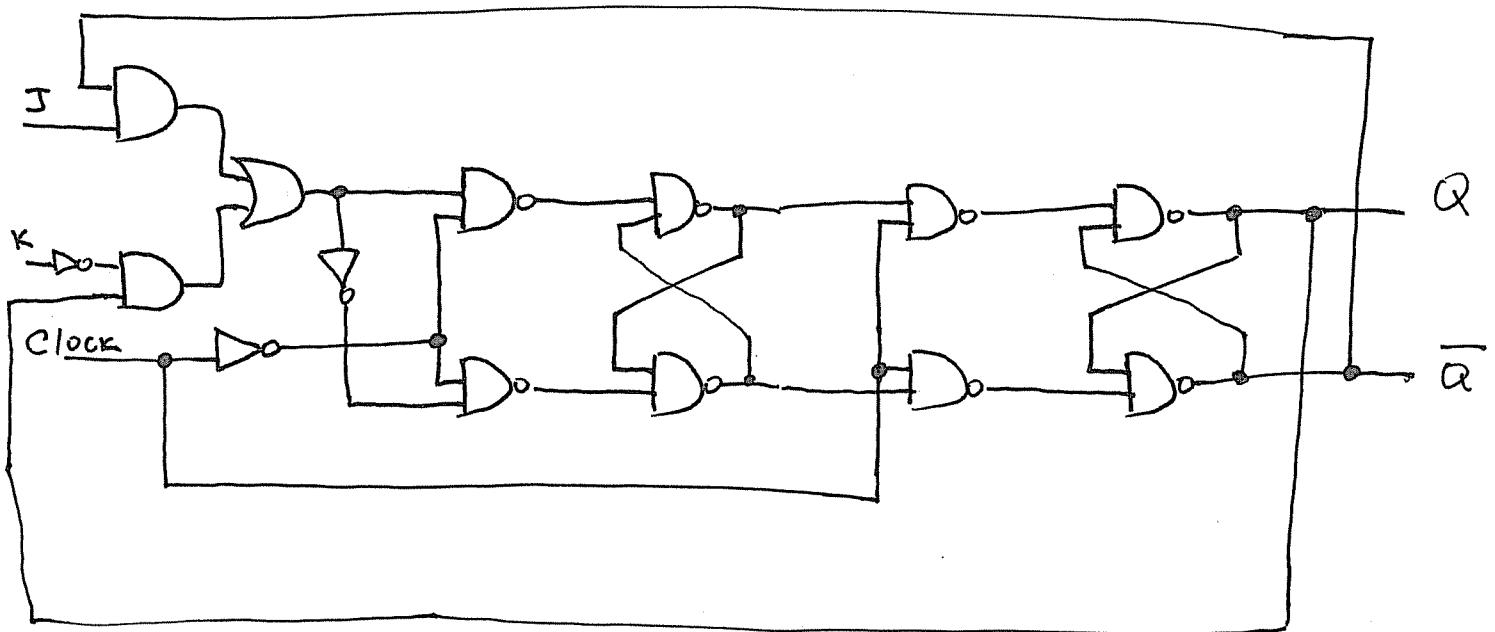- b) Draw the complete circuit diagram for a positive-edge-triggered JK flip-flop using only standard logic gates (ANDs, ORs, NOTs, NANDs, or NORs). You are not allowed to use any other high-level components in this problem. (10p)



7. Multiplexers (2p + 8p = 10p)

- a) Draw the truth table for the function $f = xy + xz + yz$ (2p)

X	Y	Z	XY	XZ	YZ	f
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	0	0	0	0
0	1	1	0	0	1	1
1	0	0	0	0	0	0
1	0	1	0	1	0	1
1	1	0	1	0	0	1
1	1	1	1	1	1	1


$$g = AND(Y, z)$$

$$h = OR(Y, z)$$

- b) Implement this function using only 2-to-1 multiplexers and no other logic gates. Assume that the signals X, Y, and Z are available only in their non-inverted form. (8p)

Y	Z	g
0	0	0
0	1	0
1	0	0
1	1	1

Y	Z	h
0	0	0
1	1	1
0	0	1
1	1	1

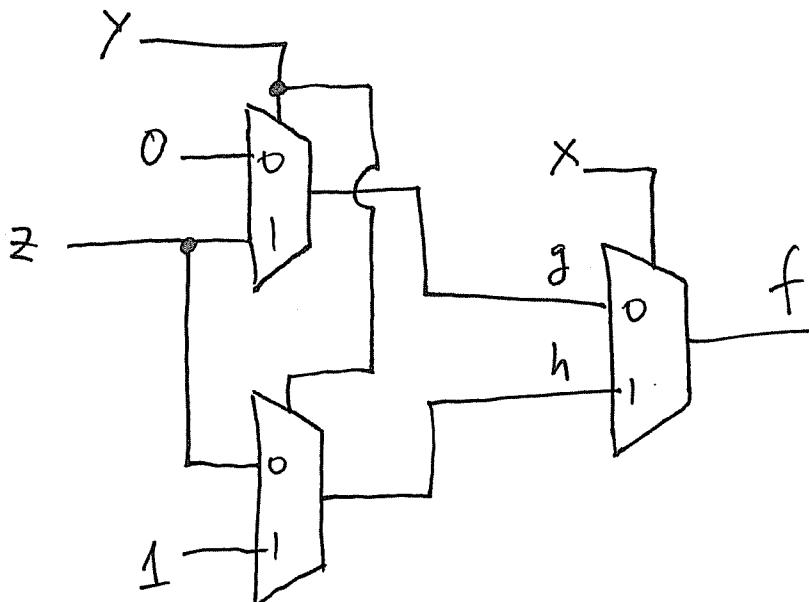

8. Comparator (3p + 7p = 10p)


A 1-bit comparator is a circuit that has two inputs (A and B) and three outputs (L, E, and G). Each of the two inputs is a 1-bit number. The first output, L, is equal to one if $A < B$ and zero otherwise. The second output, E, is equal to one if $A = B$ and zero otherwise. Finally, the third output, G, is equal to one if $A > B$ and zero otherwise.

- a) Draw the truth table for the 1-bit comparator.

(3p)

A	B	L	E	G
0	0	0	1	0
0	1	1	0	0
1	0	0	0	1
1	1	0	1	0

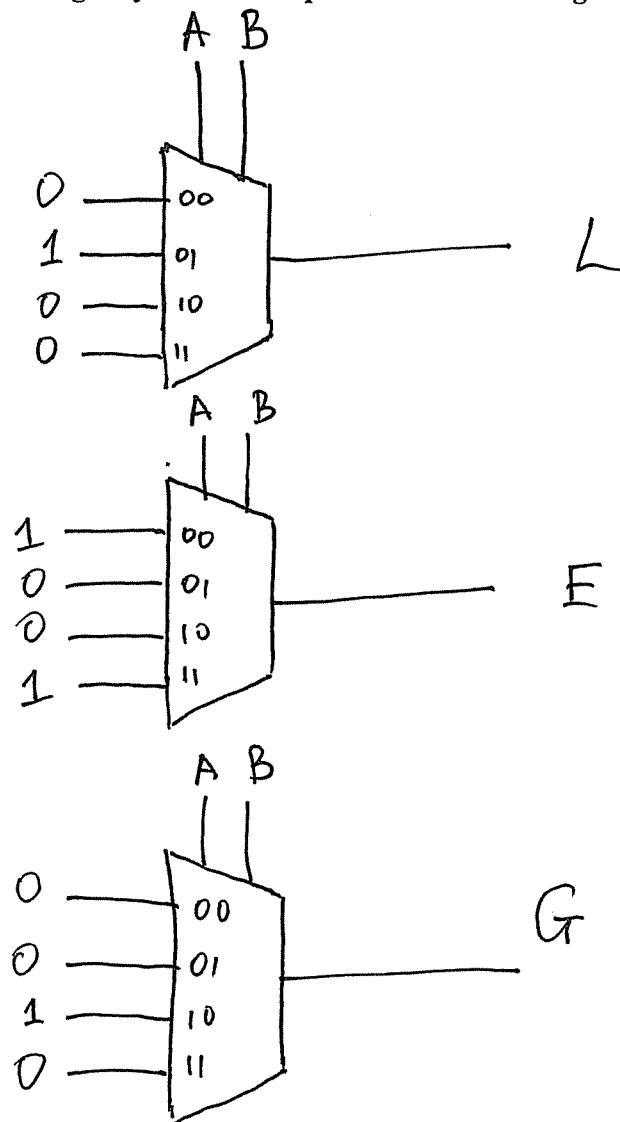- b) Draw the circuit for this comparator using only 4-to-1 multiplexers and no other gates. (7p)




9. More Multiplexers (2p + 8p = 10p)

a) Draw the truth table for the function $f = \overline{A}C + BC\bar{D} + \overline{A}\overline{B}\overline{C}\bar{D}$. (2p)

b) Implement the function f using only 2-to-1 multiplexers and no other gates. You can assume that the variables are available in both inverted and non-inverted form. Clearly label all inputs, pins, and outputs of your circuit. (8p)

A	B	C	D	$\overline{A}C$	$BC\bar{D}$	$\overline{A}\overline{B}\overline{C}\bar{D}$	f	
0	0	0	0	0	0	1	1	D
0	0	0	1	0	0	0	0	{1}
0	0	1	0	1	0	0	1	{1}
0	0	1	1	1	0	0	1	{1}
0	1	0	0	0	0	0	0	0
0	1	0	1	0	0	0	0	{0}
0	1	1	0	1	0	0	1	{1}
0	1	1	1	1	1	0	1	{1}
1	0	0	0	0	0	0	0	0
1	0	0	1	0	0	0	0	{0}
1	0	1	0	0	0	0	0	{0}
1	0	1	1	0	0	0	0	{0}
1	1	0	0	0	0	0	0	0
1	1	0	1	0	0	0	0	{0}
1	1	1	0	0	0	0	0	{0}
1	1	1	1	0	1	0	0	D

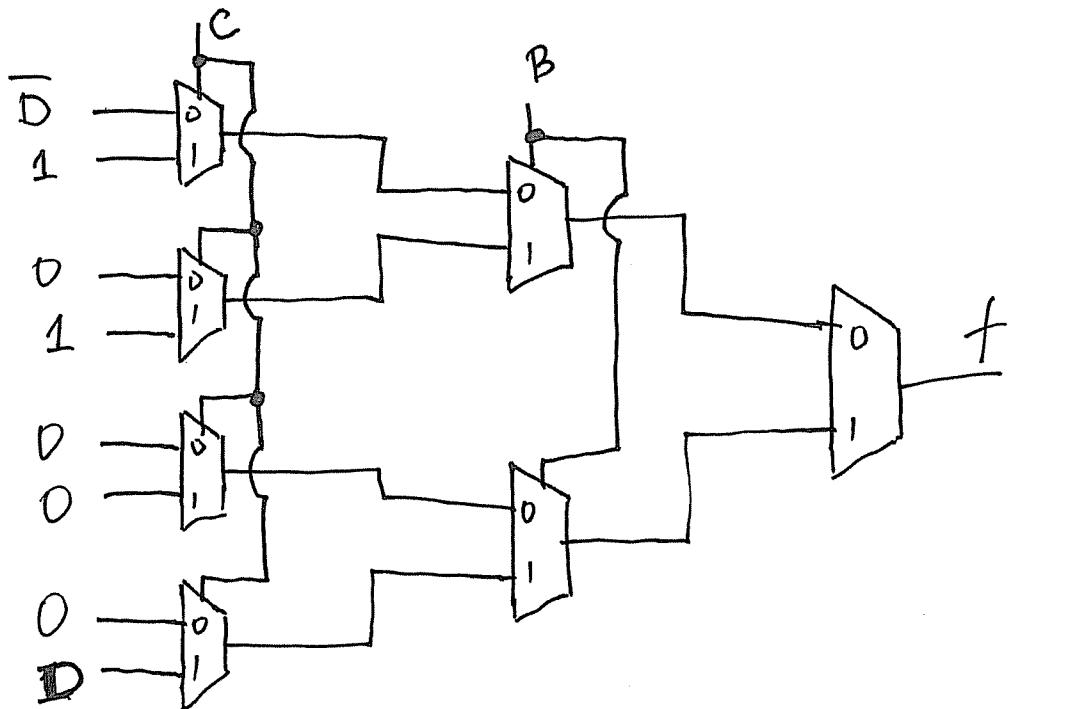

10. Product Check (3 x 5p = 15p)

The goal is to design a circuit that takes a 3-bit number A(a₂, a₁, a₀) and a 2-bit number B(b₁, b₀) and sets the output F to 1 if B ≠ 0 and A = 2B. Otherwise F=0.

a) Complete the truth table for the function F. (5p)

b) Write the logic expression for F in canonical SOP form. (5p)

c) Implement a circuit for F using one 8-to-1 multiplexer and some basic logic gates. (5p)

Please label clearly all inputs, output, and pins of your circuit. (5p)

(a)


a ₂	a ₁	a ₀	b ₁	b ₀	F
0	0	0	0	0	0
0	0	0	0	1	0
0	0	0	1	0	0
0	0	0	1	1	0
0	0	1	0	0	0
0	0	1	0	1	0
0	0	1	1	0	0
0	0	1	1	1	0
0	1	0	0	0	0
0	1	0	0	1	0
0	1	0	1	0	0
0	1	0	1	1	0
0	1	1	0	0	0
0	1	1	0	1	0
0	1	1	1	0	0
0	1	1	1	1	0
1	0	0	0	0	0
1	0	0	0	1	0
1	0	0	1	0	1
1	0	0	1	1	0
1	0	1	0	0	0
1	0	1	0	1	0
1	0	1	1	0	0
1	0	1	1	1	0
1	1	0	0	0	0
1	1	0	0	1	0
1	1	0	1	0	0
1	1	0	1	1	1
1	1	1	0	0	0
1	1	1	0	1	0
1	1	1	1	0	0
1	1	1	1	1	0

b)

$$F = \overline{a}_2 a_1 \overline{a}_0 \overline{b}_1 b_0 + \\ a_2 \overline{a}_1 \overline{a}_0 b_1 \overline{b}_0 + \\ a_2 a_1 \overline{a}_0 b_1 b_0$$


a₂ a₁ a₀

c)

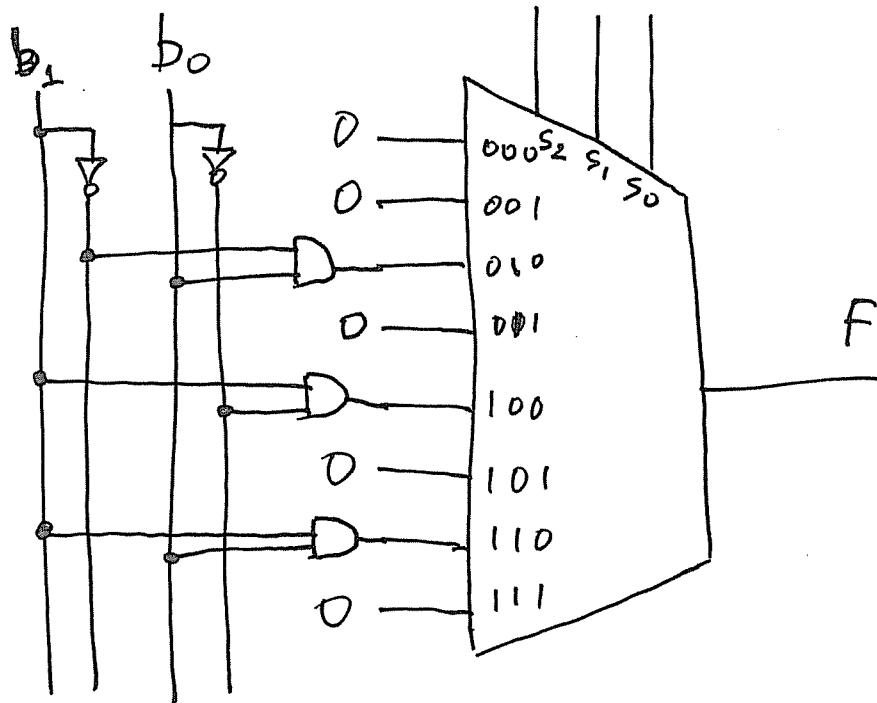

11. Implement a Multiplexer (10p + 5p = 15p)

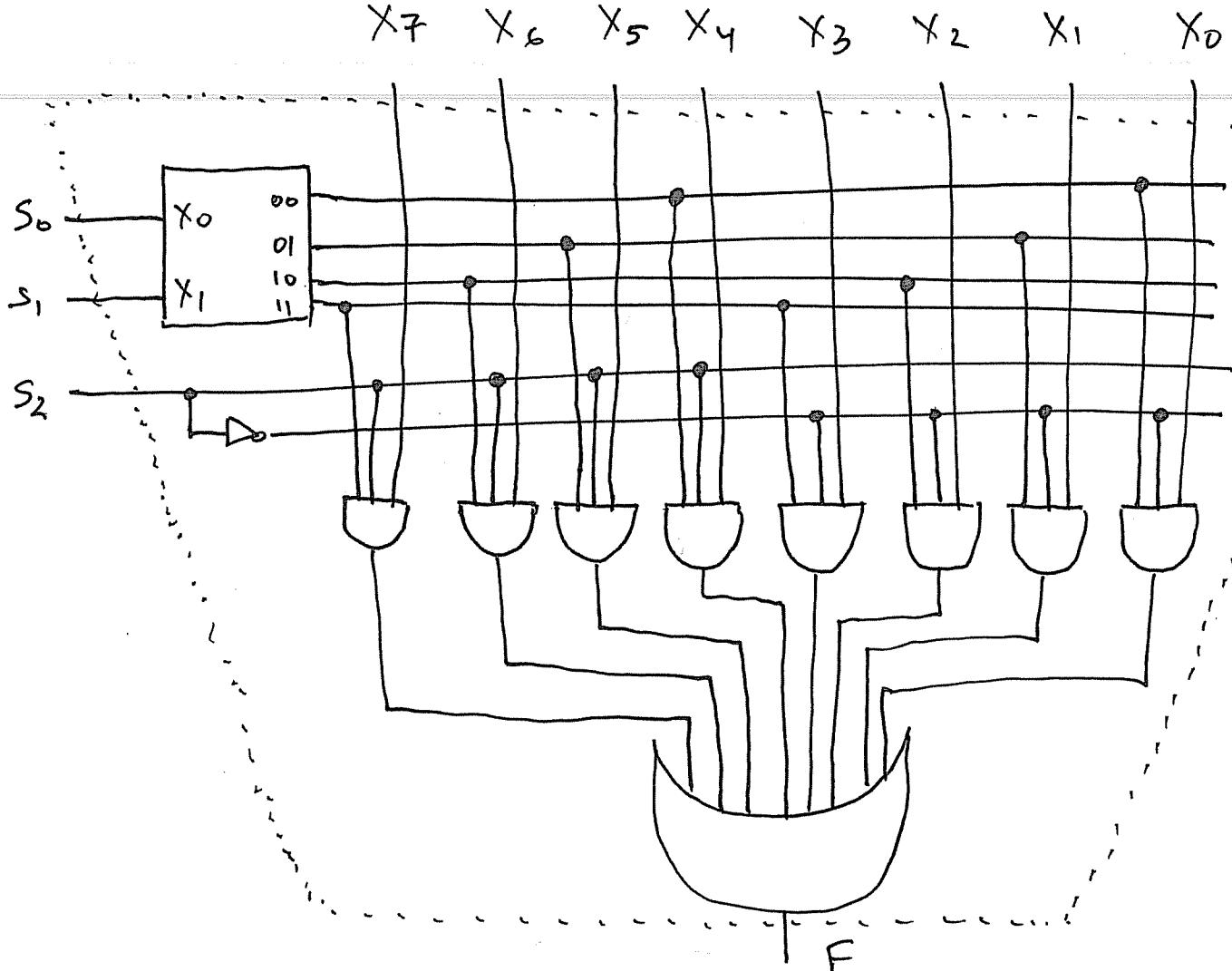a) Implement a 8-to-1 multiplexer using only one 2-to-4 decoder (without enable input) and any additional N-input AND, OR, or NOT gates. Label all inputs, pins, and outputs. (10p)



b) Explain your solution. How many additional gates are required? (5p)

This solution requires 10 additional gates, 1 NOT, 8 ANDs and 1 OR. The outputs of the decoder are one-hot encoded. This property is used for a given S_0, S_1 combination "enable" only 2 of the 8 AND gates. The select line S_2 is used to select only 1 of these two AND gates. This allows the corresponding X_i signal to reach the OR gate. The outputs of the other 7 AND gates are all zero.

Question	Max	Score
1. True/False	10	
2. K-Map Minimization	5	
3. Addition/Subtraction	15	
4. Number Conversions	15	
5. Adder Implementation	10	
6. Flip-Flops	15	
7. Multiplexers	10	
8. Comparator	10	
9. More Multiplexers	10	
10. Product Check	15	
11. Implement a Multiplexer	15	
TOTAL:	130	