



# **CprE 281: Digital Logic**

**Instructor: Alexander Stoytchev**

**<http://www.ece.iastate.edu/~alexs/classes/>**

# Code Converters

*CprE 281: Digital Logic*  
*Iowa State University, Ames, IA*  
*Copyright © Alexander Stoytchev*

# **Administrative Stuff**

- **HW 7 is out**
- **It is due next Monday (Oct 19) @ 4pm**

# **Administrative Stuff**

- **The second midterm is in 2 weeks.**

# **Administrative Stuff**

- **Midterm Exam #2**
- **When: Friday October 30 @ 4pm.**
- **Where: This classroom**
- **What: Chapters 1, 2, 3, 4 and 5.1-5.8**
- **The exam will be open book and open notes (you can bring up to 3 pages of handwritten notes).**

# Midterm 2: Format

- The exam will be out of 130 points
- You need 95 points to get an A
- It will be great if you can score more than 100 points.
  - but you can't roll over your extra points ☹️

# **Quick Review**

# Decoders




# 2-to-4 Decoder (Definition)

- Has two inputs:  $w_1$  and  $w_0$
- Has four outputs:  $y_0$ ,  $y_1$ ,  $y_2$ , and  $y_3$
- If  $w_1=0$  and  $w_0=0$ , then the output  $y_0$  is set to 1
- If  $w_1=0$  and  $w_0=1$ , then the output  $y_1$  is set to 1
- If  $w_1=1$  and  $w_0=0$ , then the output  $y_2$  is set to 1
- If  $w_1=1$  and  $w_0=1$ , then the output  $y_3$  is set to 1
- Only one output is set to 1. All others are set to 0.

# Truth Table and Graphical Symbol for a 2-to-4 Decoder


$w_1$	$w_0$	$y_0$	$y_1$	$y_2$	$y_3$
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

(a) Truth table

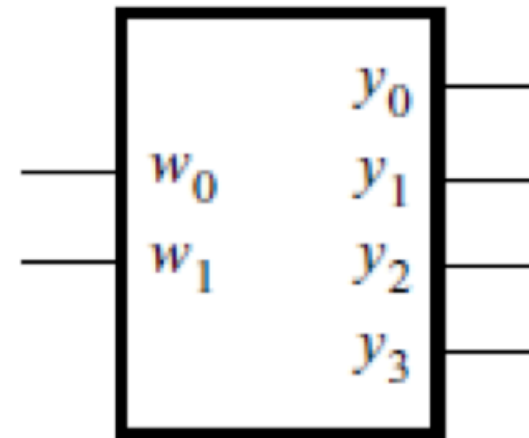


(b) Graphical symbol

# Truth Logic Circuit for a 2-to-4 Decoder

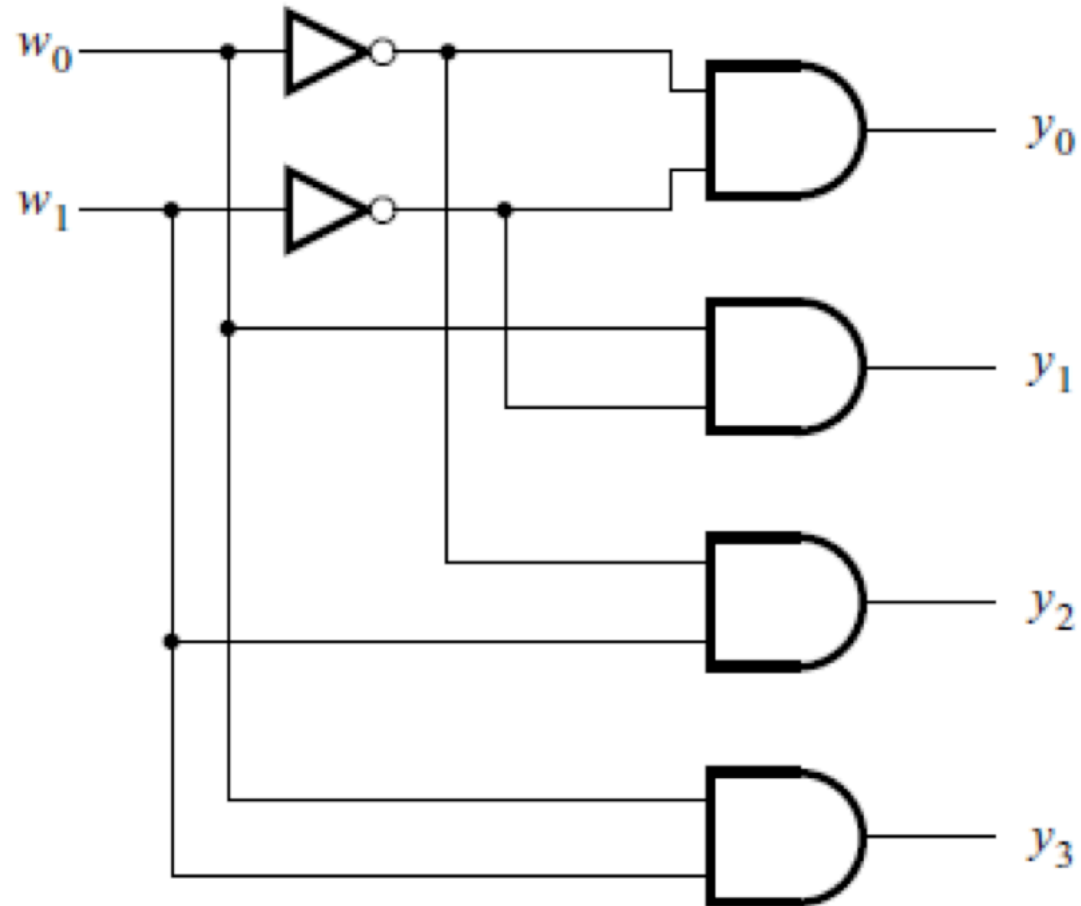

[ Figure 4.13c from the textbook ]

# Adding an Enable Input

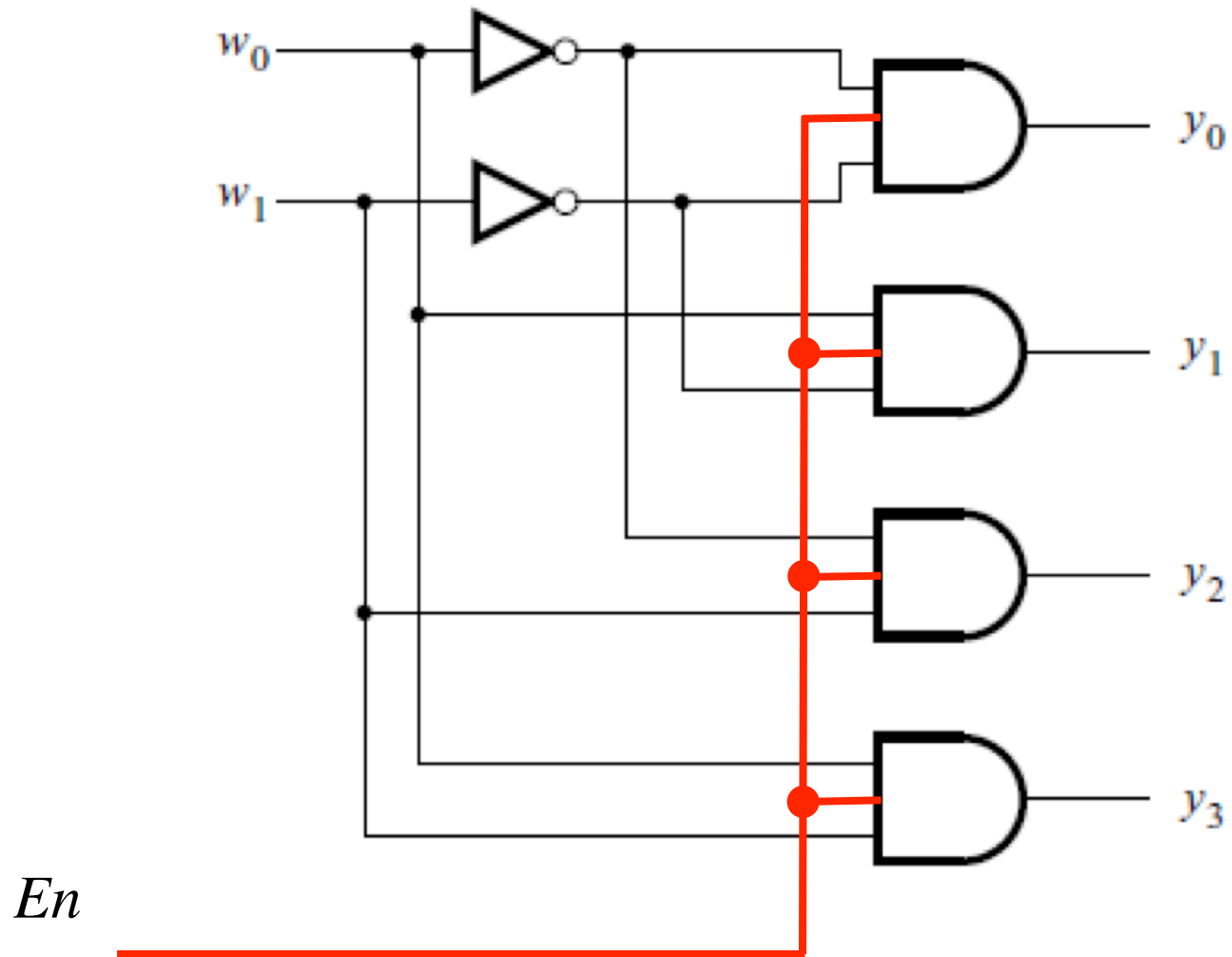


[ Figure 4.13c from the textbook ]

# Truth Table and Graphical Symbol for a 2-to-4 Decoder with an Enable Input

$En$	$w_1$	$w_0$	$y_0$	$y_1$	$y_2$	$y_3$
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1
0	x	x	0	0	0	0

(a) Truth table

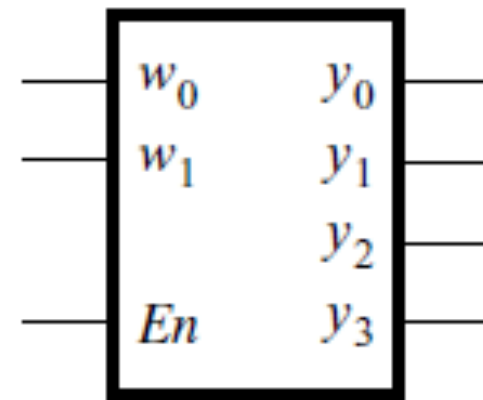


(b) Graphical symbol

# Truth Table and Graphical Symbol for a 2-to-4 Decoder with an Enable Input

$En$	$w_1$	$w_0$	$y_0$	$y_1$	$y_2$	$y_3$
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1
0	x	x	0	0	0	0


(a) Truth table

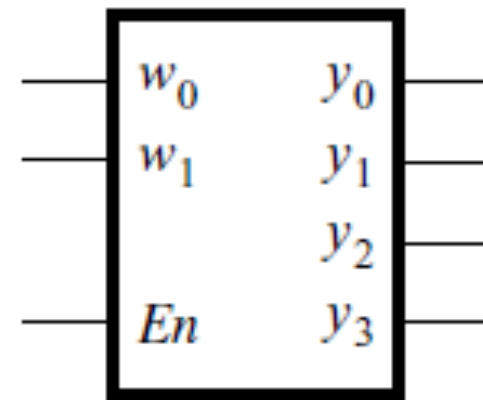

(b) Graphical symbol

x indicates that it does not matter what the value of these variable is for this row of the truth table
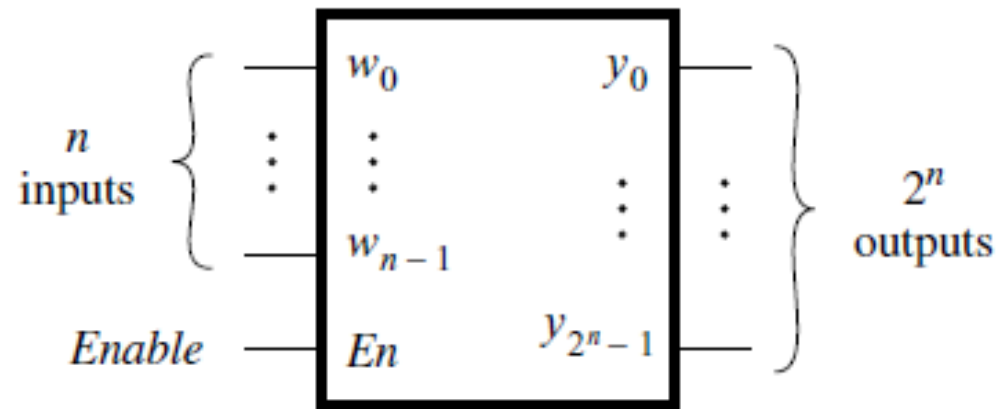
# Graphical Symbol for a Binary $n$ -to- $2^n$ Decoder with an Enable Input




(d) An  $n$ -to- $2^n$  decoder

A binary decoder with  $n$  inputs has  $2^n$  outputs

The outputs of an enabled binary decoder are “one-hot” encoded, meaning that only a single bit is set to 1, i.e., it is *hot*.


# A 3-to-8 decoder using two 2-to-4 decoders

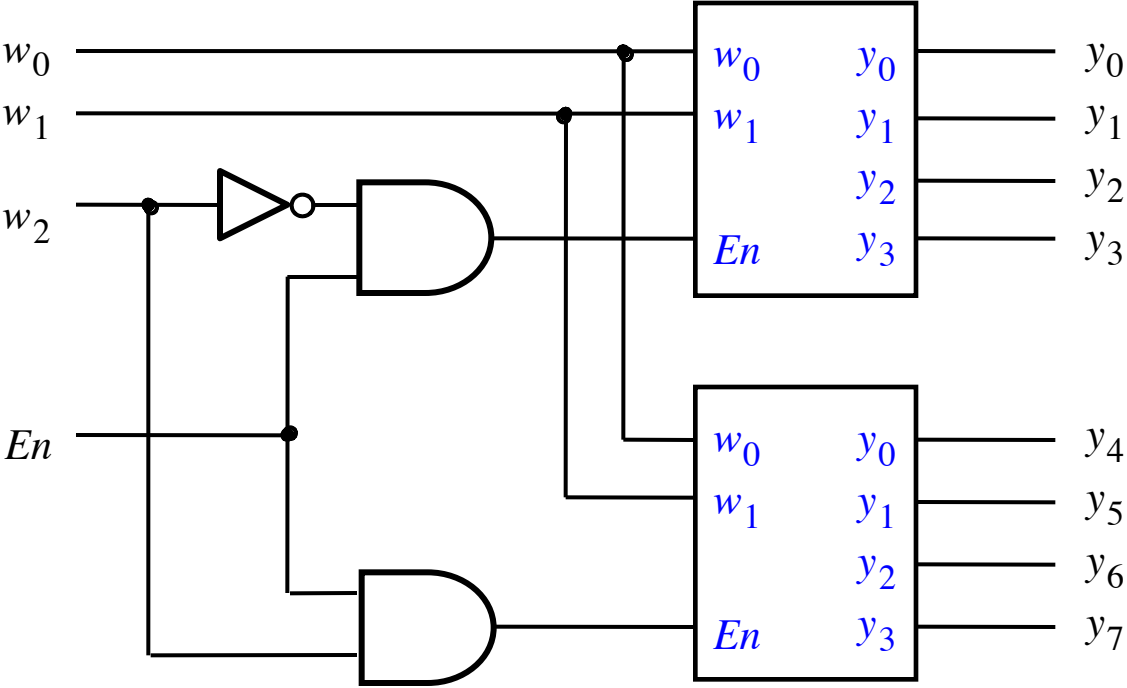

[ Figure 4.15 from the textbook ]





# A 4-to-16 decoder built using a decoder tree

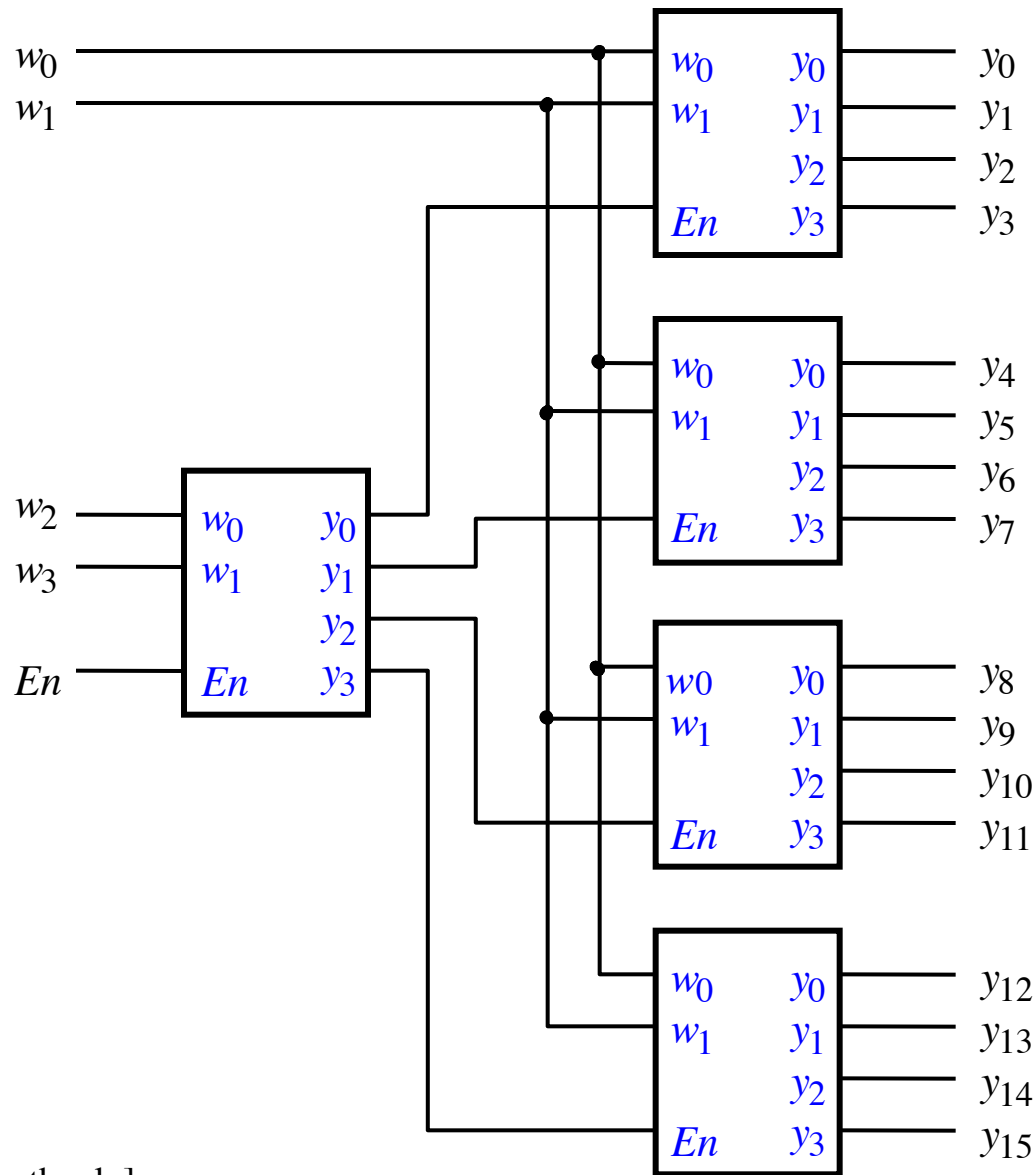


[ Figure 4.16 from the textbook ]


# Let's build a 5-to-32 decoder

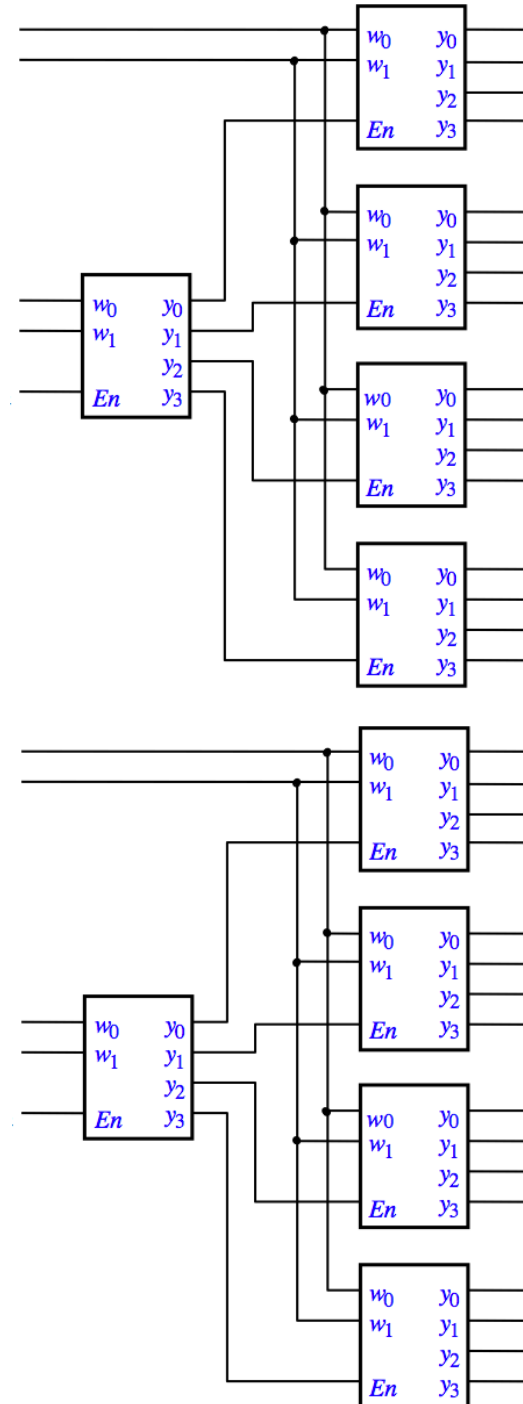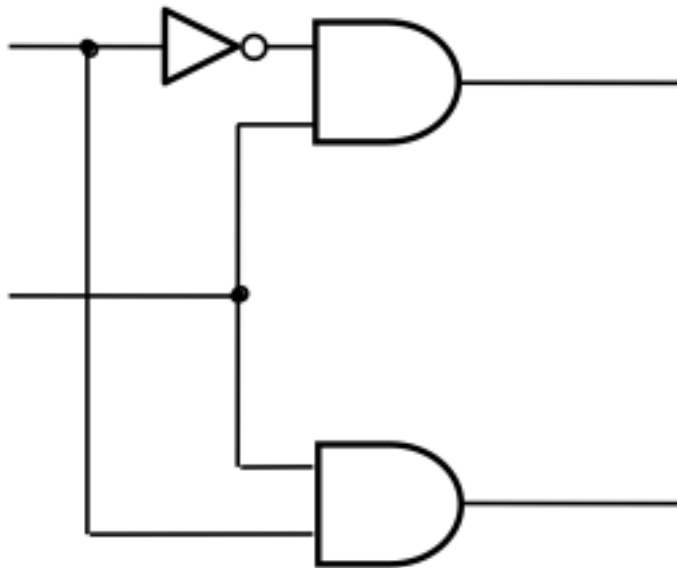

# Let's build a 5-to-32 decoder

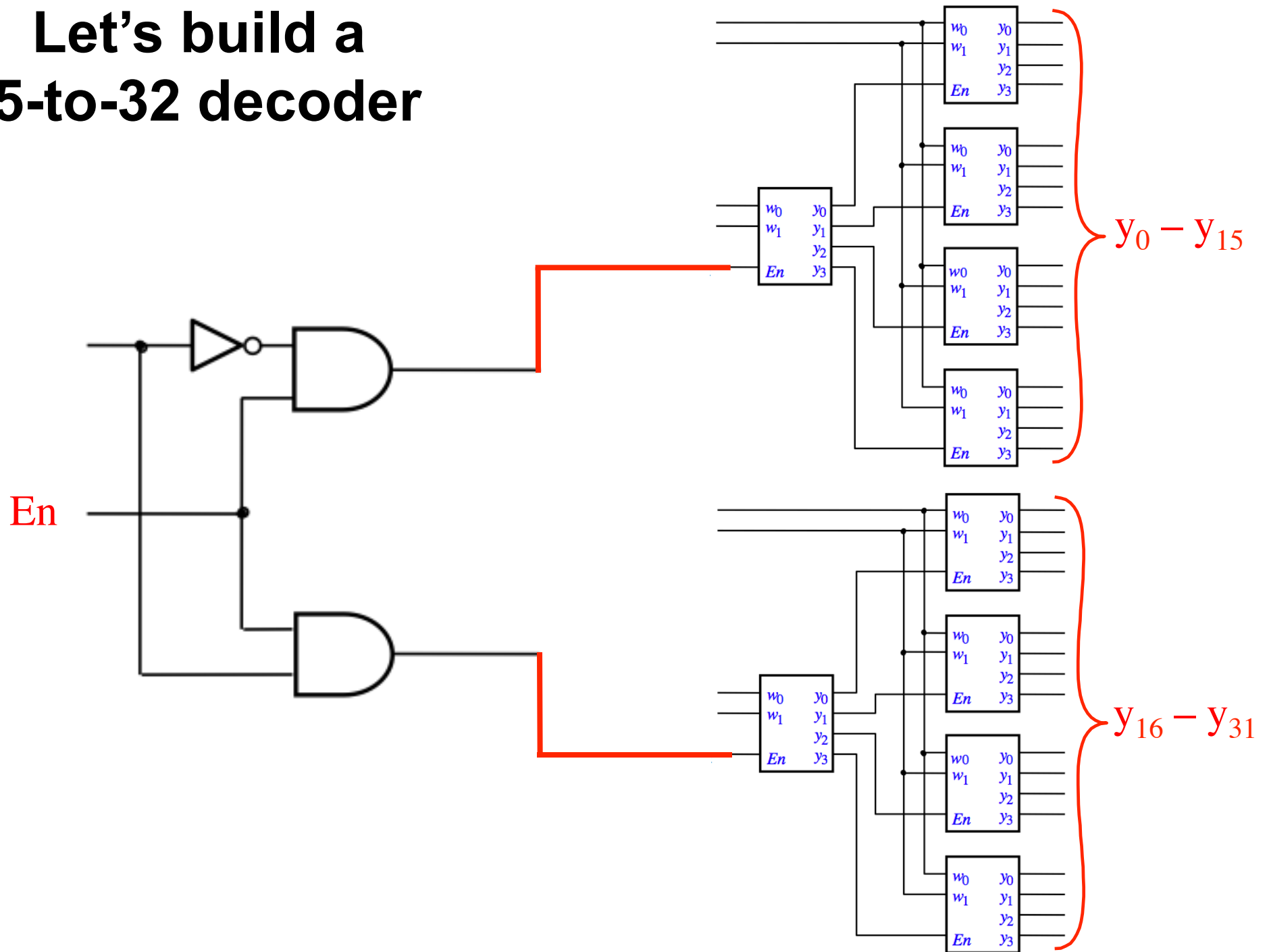

# Let's build a 5-to-32 decoder

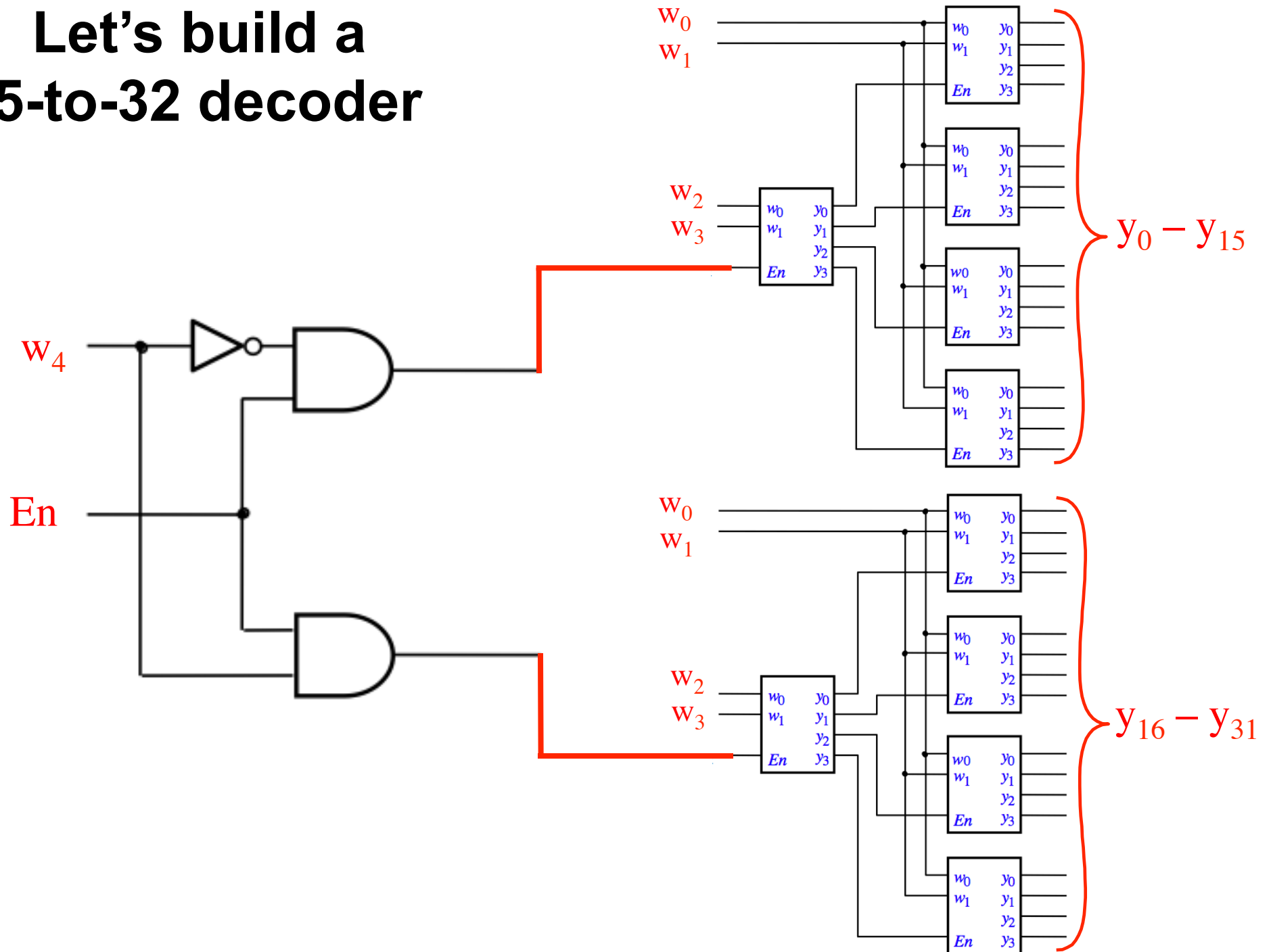


# Demultiplexers

# 1-to-4 Demultiplexer (Definition)

- Has one data input line:  $D$
- Has two output select lines:  $w_1$  and  $w_0$
- Has four outputs:  $y_0$ ,  $y_1$ ,  $y_2$ , and  $y_3$
- If  $w_1=0$  and  $w_0=0$ , then the output  $y_0$  is set to  $D$
- If  $w_1=0$  and  $w_0=1$ , then the output  $y_1$  is set to  $D$
- If  $w_1=1$  and  $w_0=0$ , then the output  $y_2$  is set to  $D$
- If  $w_1=1$  and  $w_0=1$ , then the output  $y_3$  is set to  $D$
- Only one output is set to  $D$ . All others are set to 0.


# A 1-to-4 demultiplexer built with a 2-to-4 decoder

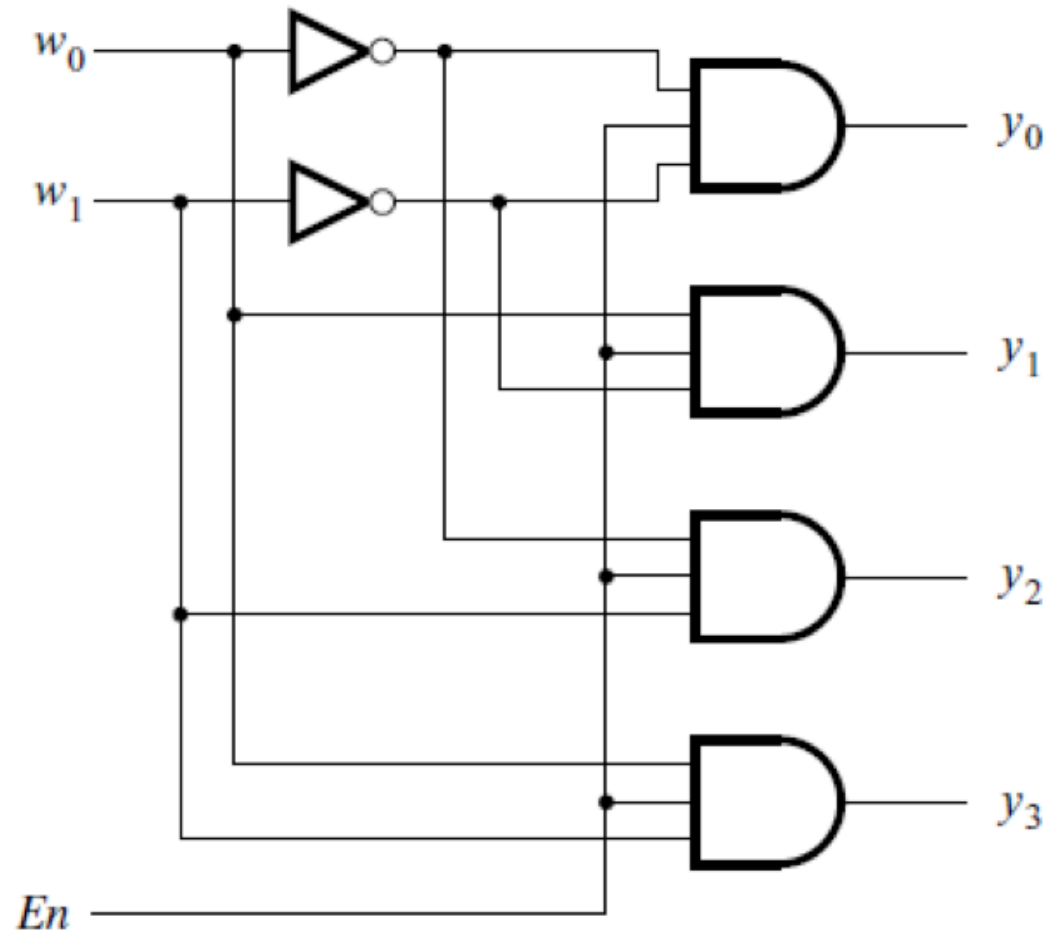

[ Figure 4.14c from the textbook ]

# A 1-to-4 demultiplexer built with a 2-to-4 decoder

output  
select  
lines

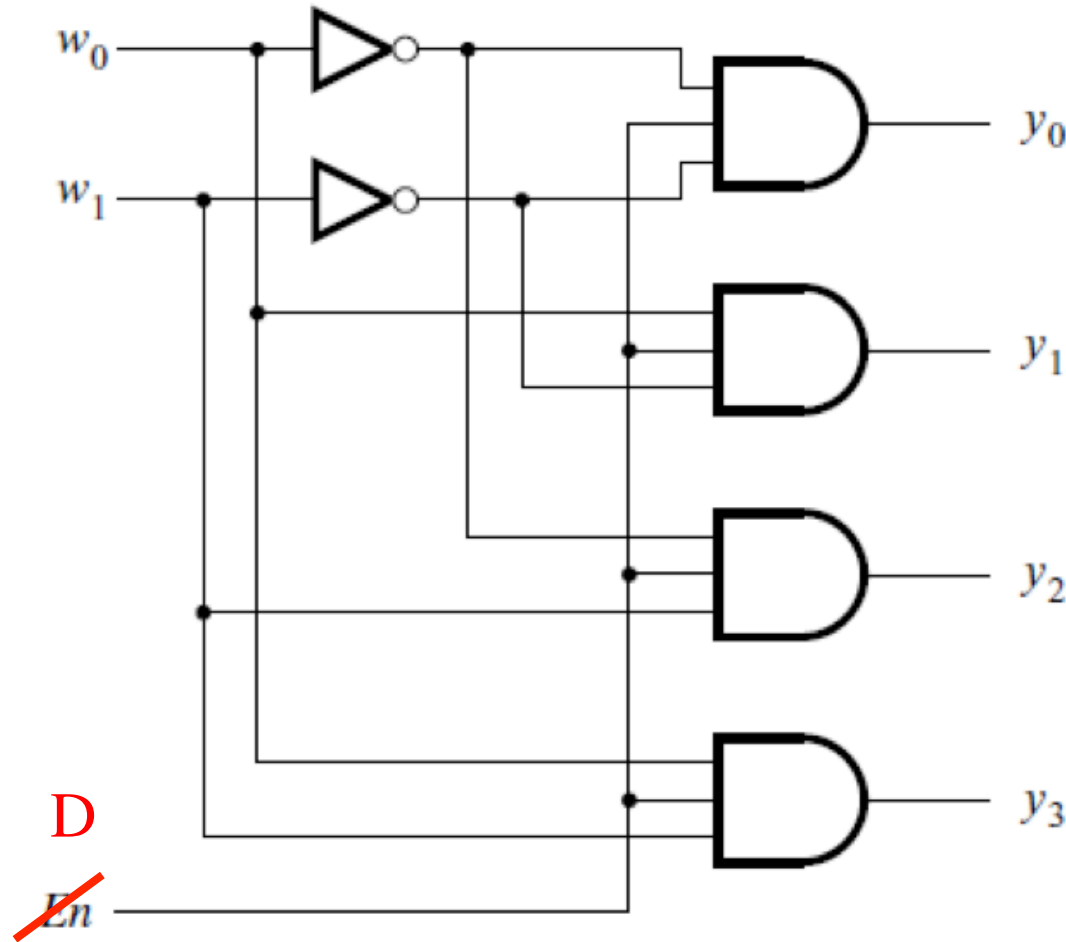


the  
four  
output  
lines

data  
input  
line



# **Multiplexers (Implemented with Decoders)**

# A 4-to-1 multiplexer built using a 2-to-4 decoder

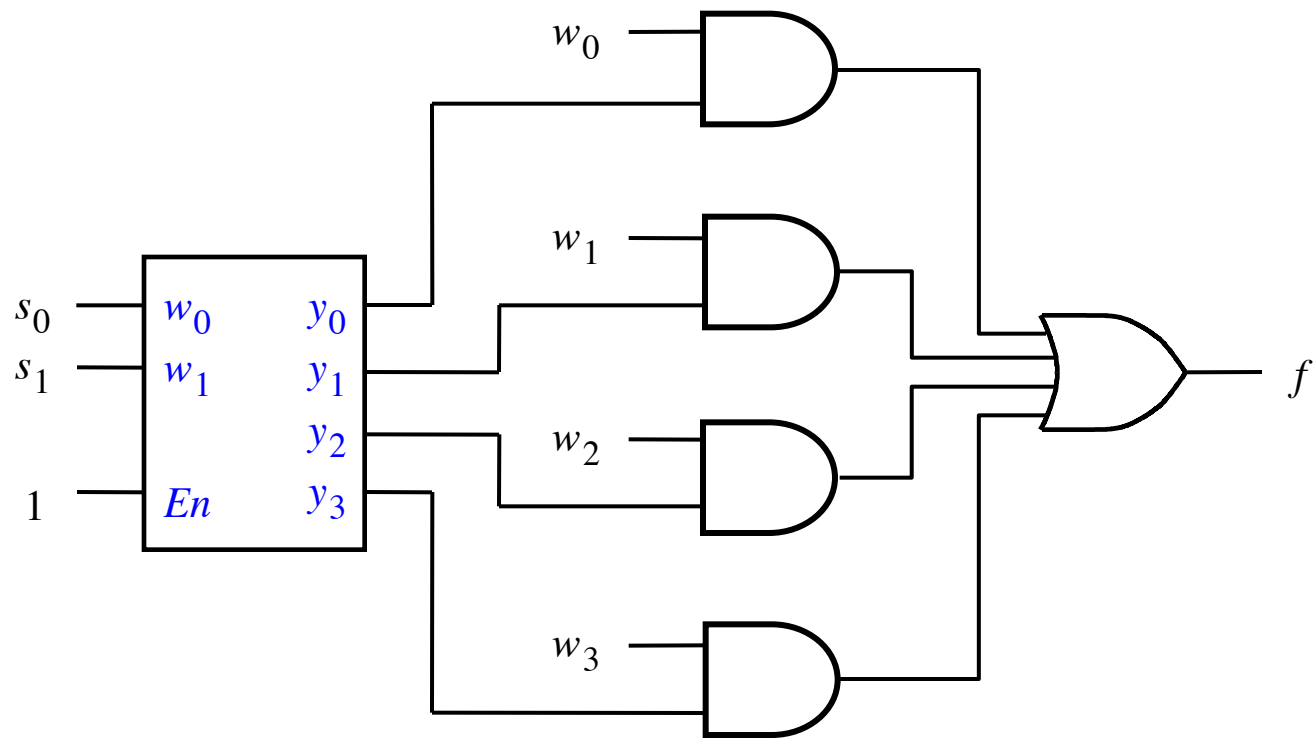


[ Figure 4.17 from the textbook ]

# Encoders

# Binary Encoders


# A $2^n$ -to- $n$ binary encoder

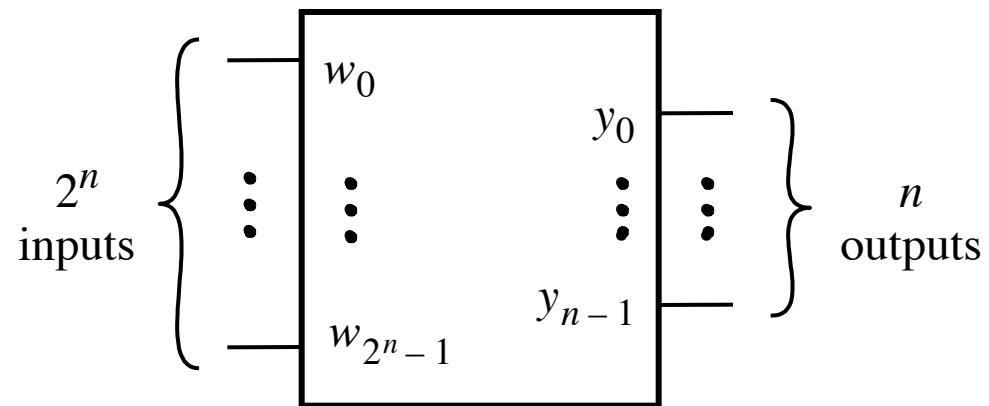

# A 4-to-2 binary encoder

$w_3$	$w_2$	$w_1$	$w_0$	$y_1$	$y_0$
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

(a) Truth table

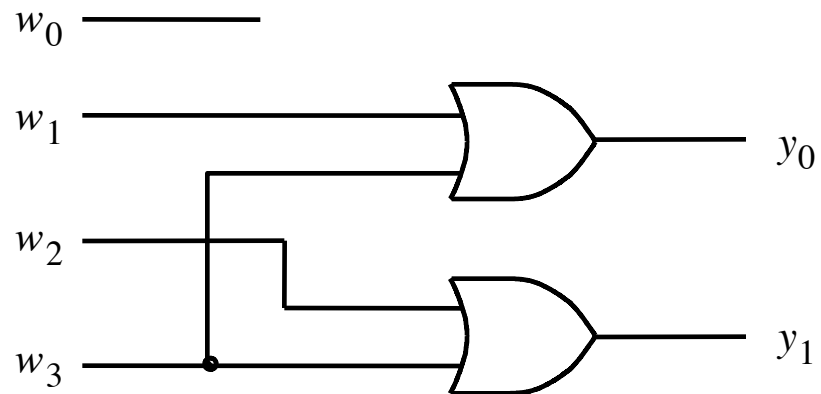


(b) Circuit

[ Figure 4.19 from the textbook ]

# A 4-to-2 binary encoder

$w_3$	$w_2$	$w_1$	$w_0$	$y_1$	$y_0$
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

(a) Truth table

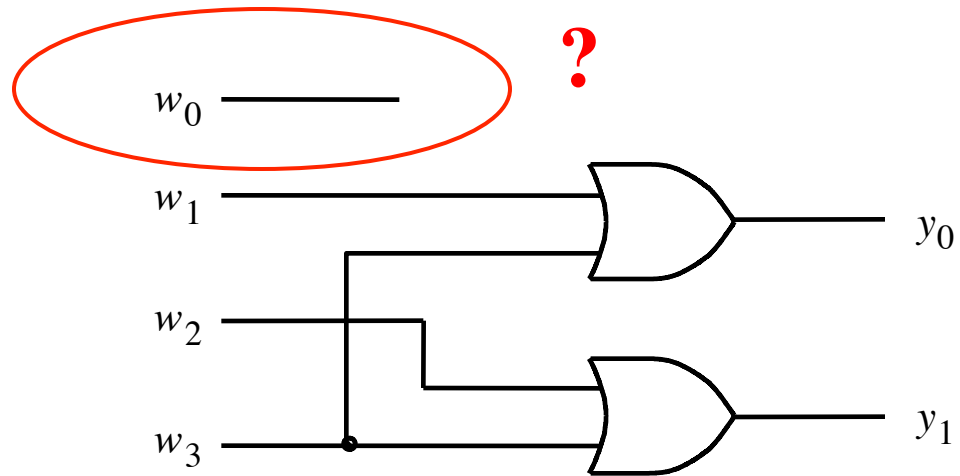


(b) Circuit

[ Figure 4.19 from the textbook ]

# A 4-to-2 binary encoder

$w_3$	$w_2$	$w_1$	$w_0$	$y_1$	$y_0$
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

(a) Truth table

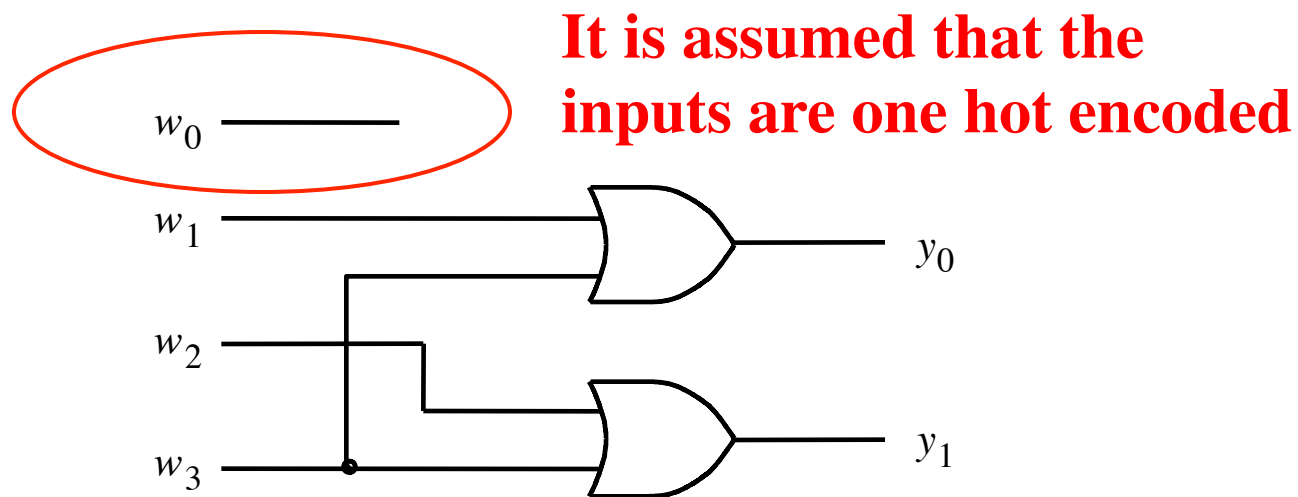

(b) Circuit

[ Figure 4.19 from the textbook ]



# Priority Encoders

# Truth table for a 4-to-2 priority encoder

$w_3$	$w_2$	$w_1$	$w_0$	$y_1$	$y_0$	$z$
0	0	0	0	d	d	0
0	0	0	1	0	0	1
0	0	1	x	0	1	1
0	1	x	x	1	0	1
1	x	x	x	1	1	1


# **Code Converter (Definition)**

- **Converts from one type of input encoding to a different type of output encoding.**


# **Code Converter (Definition)**

- **Converts from one type of input encoding to a different type of output encoding.**
- **A decoder does that as well, but its outputs are always one-hot encoded so the output code is really only one type of output code.**
- **A binary encoder does that as well but its inputs are always one-hot encoded so the input code is really only one type of input code.**
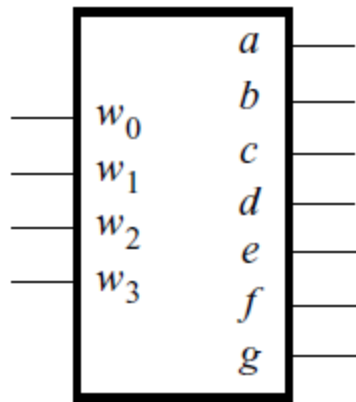
# A hex-to-7-segment display code converter



(a) Code converter

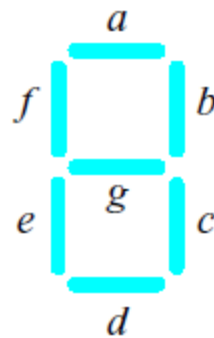


(b) 7-segment display


$w_3$	$w_2$	$w_1$	$w_0$	$a$	$b$	$c$	$d$	$e$	$f$	$g$
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1
1	0	1	0	1	1	1	0	1	1	1
1	0	1	1	0	0	1	1	1	1	1
1	1	0	0	1	0	0	1	1	1	0
1	1	0	1	0	1	1	1	1	0	1
1	1	1	0	1	0	0	1	1	1	1
1	1	1	1	1	0	0	0	1	1	1

(c) Truth table
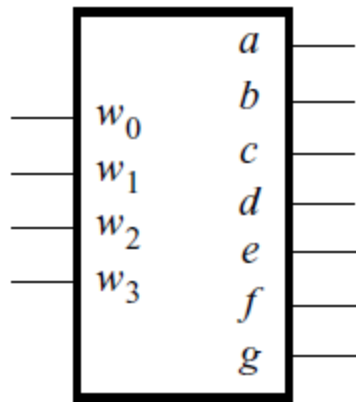
# A hex-to-7-segment display code converter



(a) Code converter

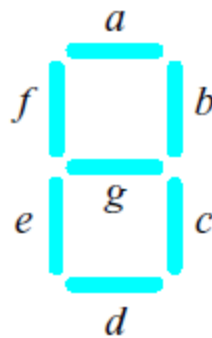


(b) 7-segment display


$w_3$	$w_2$	$w_1$	$w_0$	$a$	$b$	$c$	$d$	$e$	$f$	$g$
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1
1	0	1	0	1	1	1	0	1	1	1
1	0	1	1	0	0	1	1	1	1	1
1	1	0	0	1	0	0	1	1	1	0
1	1	0	1	0	1	1	1	1	0	1
1	1	1	0	1	0	0	1	1	1	1
1	1	1	1	1	0	0	0	1	1	1

(c) Truth table
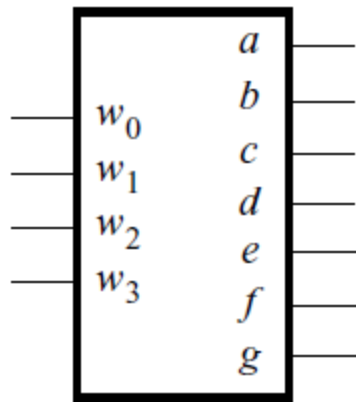
# A hex-to-7-segment display code converter



(a) Code converter

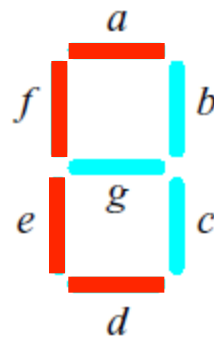


(b) 7-segment display


$w_3$	$w_2$	$w_1$	$w_0$	$a$	$b$	$c$	$d$	$e$	$f$	$g$
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1
1	0	1	0	1	1	1	0	1	1	1
1	0	1	1	0	0	1	1	1	1	1
1	1	0	0	1	0	0	1	1	1	0
1	1	0	1	0	1	1	1	1	0	1
1	1	1	0	1	0	0	1	1	1	1
1	1	1	1	1	0	0	0	1	1	1

(c) Truth table
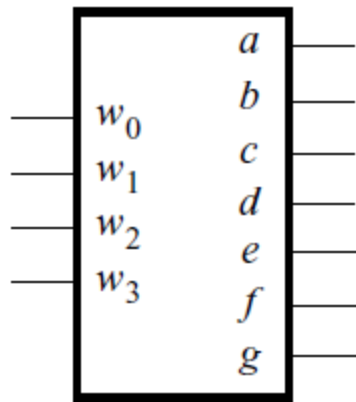
# A hex-to-7-segment display code converter



(a) Code converter

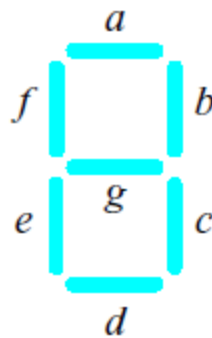


(b) 7-segment display

$w_3$	$w_2$	$w_1$	$w_0$	$a$	$b$	$c$	$d$	$e$	$f$	$g$
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1
1	0	1	0	1	1	1	0	1	1	1
1	0	1	1	0	0	1	1	1	1	1
1	1	0	0	1	0	0	1	1	1	0
1	1	0	1	0	1	1	1	1	0	1
1	1	1	0	1	0	0	1	1	1	1
1	1	1	1	1	0	0	0	1	1	1


(c) Truth table


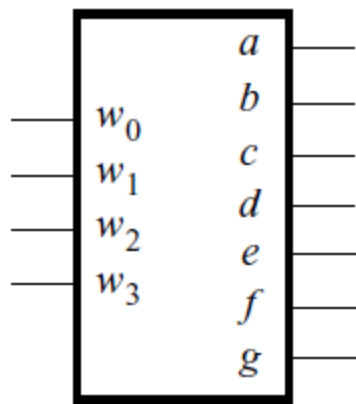
# A hex-to-7-segment display code converter



(a) Code converter

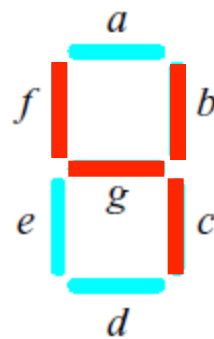

(b) 7-segment display

$w_3$	$w_2$	$w_1$	$w_0$	$a$	$b$	$c$	$d$	$e$	$f$	$g$
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1
1	0	1	0	1	1	1	0	1	1	1
1	0	1	1	0	0	1	1	1	1	1
1	1	0	0	1	0	0	1	1	1	0
1	1	0	1	0	1	1	1	1	0	1
1	1	1	0	1	0	0	1	1	1	1
1	1	1	1	1	0	0	0	1	1	1

(c) Truth table

# What is the circuit for this code converter?

$x_3$	$x_2$	$x_1$	$x_0$	$a$	$b$	$c$	$d$	$e$	$f$	$g$
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1
1	0	1	0	1	1	1	0	1	1	1
1	0	1	1	0	0	1	1	1	1	1
1	1	0	0	1	0	0	1	1	1	0
1	1	0	1	0	1	1	1	1	0	1
1	1	1	0	1	0	0	1	1	1	1
1	1	1	1	1	0	0	0	1	1	1


# What is the circuit for this code converter?

$x_3$	$x_2$	$x_1$	$x_0$	$a$	$b$	$c$	$d$	$e$	$f$	$g$
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1
1	0	1	0	1	1	1	0	1	1	1
1	0	1	1	0	0	1	1	1	1	1
1	1	0	0	1	0	0	1	1	1	0
1	1	0	1	0	1	1	1	1	0	1
1	1	1	0	1	0	0	1	1	1	1
1	1	1	1	1	0	0	0	1	1	1

$$f(x_1, x_2, x_3, x_4) = \sum m(0, 2, 3, 5, 6, 7, 8, 9, 10, 12, 14, 15)$$

# What is the circuit for this code converter?

$x_3$	$x_2$	$x_1$	$x_0$	$a$	$b$	$c$	$d$	$e$	$f$	$g$
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1
1	0	1	0	1	1	1	0	1	1	1
1	0	1	1	0	0	1	1	1	1	1
1	1	0	0	1	0	0	1	1	1	0
1	1	0	1	0	1	1	1	1	0	1
1	1	1	0	1	0	0	1	1	1	1
1	1	1	1	1	0	0	0	1	1	1

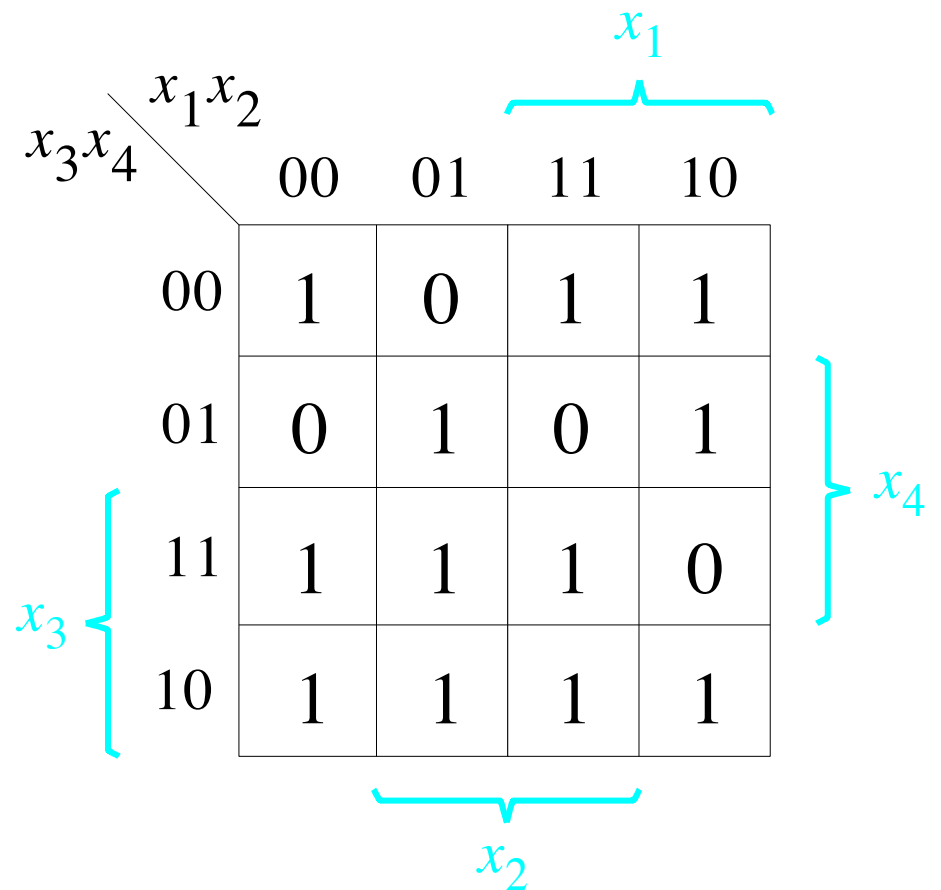


$$f(x_1, x_2, x_3, x_4) = \sum m(0, 2, 3, 5, 6, 7, 8, 9, 10, 12, 14, 15)$$

# What is the circuit for this code converter?

$x_3$	$x_2$	$x_1$	$x_0$	$a$	$b$	$c$	$d$	$e$	$f$	$g$
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1
1	0	1	0	1	1	1	0	1	1	1
1	0	1	1	0	0	1	1	1	1	1
1	1	0	0	1	0	0	1	1	1	0
1	1	0	1	0	1	1	1	1	0	1
1	1	1	0	1	0	0	1	1	1	1
1	1	1	1	1	0	0	0	1	1	1

# What is the circuit for this code converter?

$x_3$	$x_2$	$x_1$	$x_0$	$a$	$b$	$c$	$d$	$e$	$f$	$g$
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1
1	0	1	0	1	1	1	0	1	1	1
1	0	1	1	0	0	1	1	1	1	1
1	1	0	0	1	0	0	1	1	1	0
1	1	0	1	0	1	1	1	1	0	1
1	1	1	0	1	0	0	1	1	1	1
1	1	1	1	1	0	0	0	1	1	1

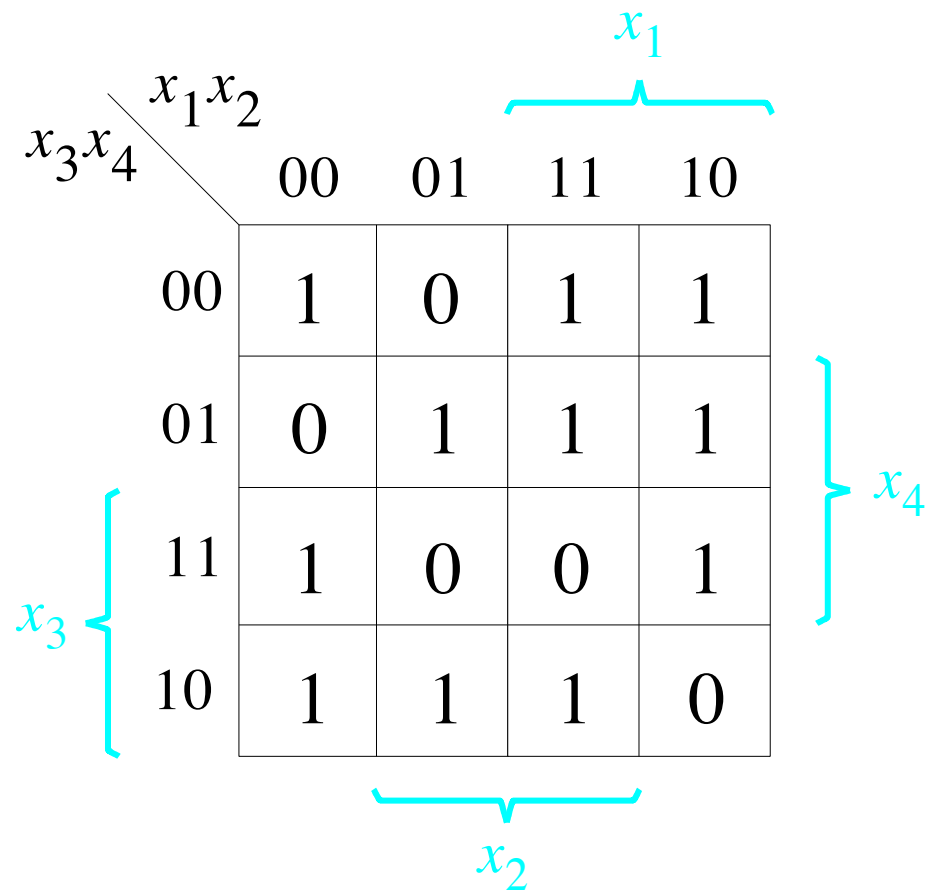

$$f(x_1, x_2, x_3, x_4) = \sum m(0, 2, 3, 5, 6, 8, 9, 11, 12, 13, 14)$$

# **Arithmetic Comparison Circuits**


# Truth table for a one-bit digital comparator

Inputs		Outputs		
$A$	$B$	$A > B$	$A = B$	$A < B$
0	0	0	1	0
0	1	0	0	1
1	0	1	0	0
1	1	0	1	0



# A one-bit digital comparator circuit

Inputs		Outputs		
$A$	$B$	$A > B$	$A = B$	$A < B$
0	0	0	1	0
0	1	0	0	1
1	0	1	0	0
1	1	0	1	0

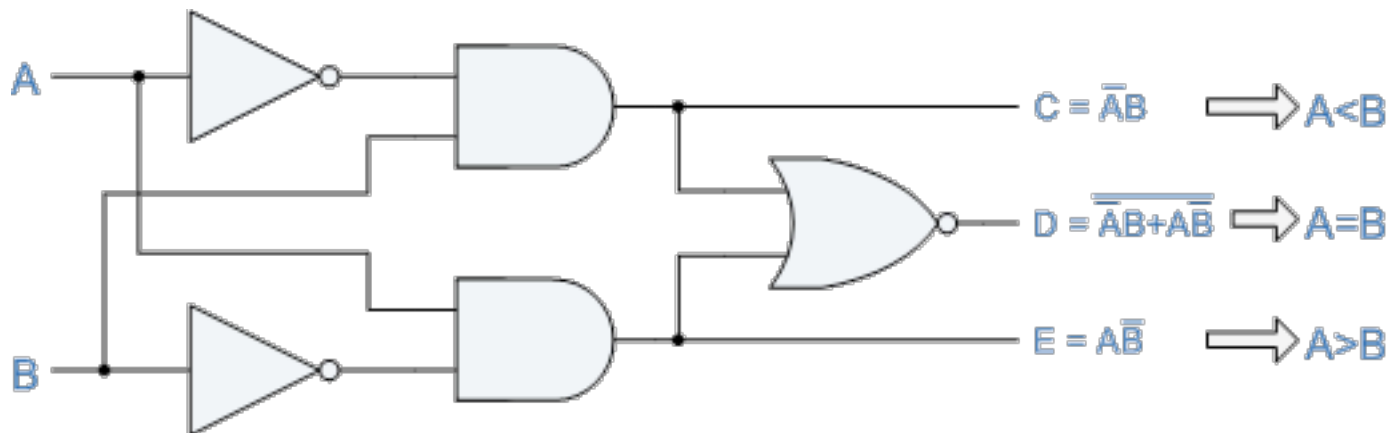


# Truth table for a two-bit digital comparator

Inputs				Outputs		
$A_1$	$A_0$	$B_1$	$B_0$	$A < B$	$A = B$	$A > B$
0	0	0	0	0	1	0
0	0	0	1	1	0	0
0	0	1	0	1	0	0
0	0	1	1	1	0	0
0	1	0	0	0	0	1
0	1	0	1	0	1	0
0	1	1	0	1	0	0
0	1	1	1	1	0	0
1	0	0	0	0	0	1
1	0	0	1	0	0	1
1	0	1	0	0	1	0
1	0	1	1	1	0	0
1	1	0	0	0	0	1
1	1	0	1	0	0	1
1	1	1	0	0	0	1
1	1	1	1	0	1	0


[[http://en.wikipedia.org/wiki/Digital\\_comparator](http://en.wikipedia.org/wiki/Digital_comparator)]

# A two-bit digital comparator circuit

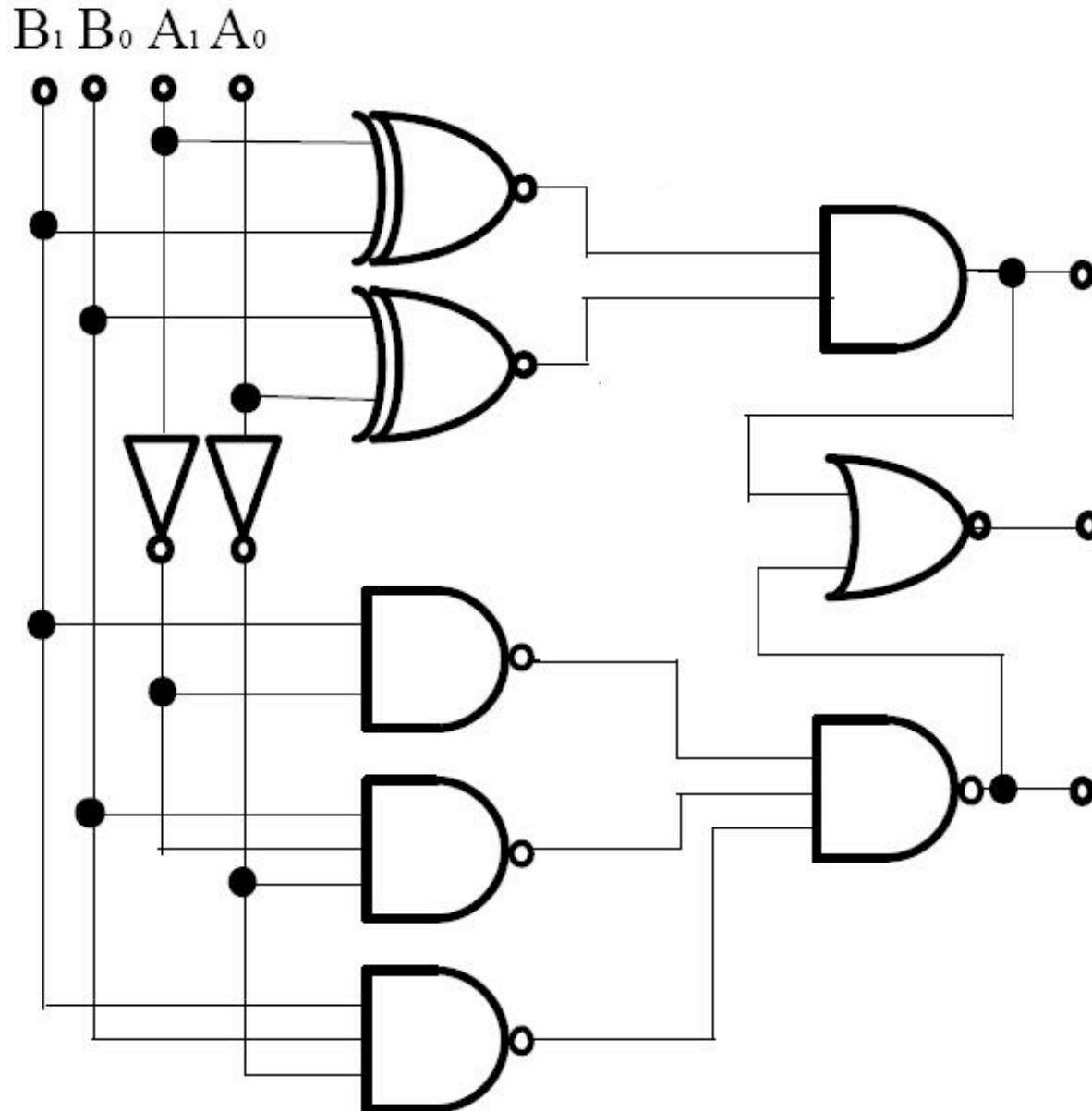

[<http://forum.allaboutcircuits.com/showthread.php?t=10561>]

# A four-bit comparator circuit

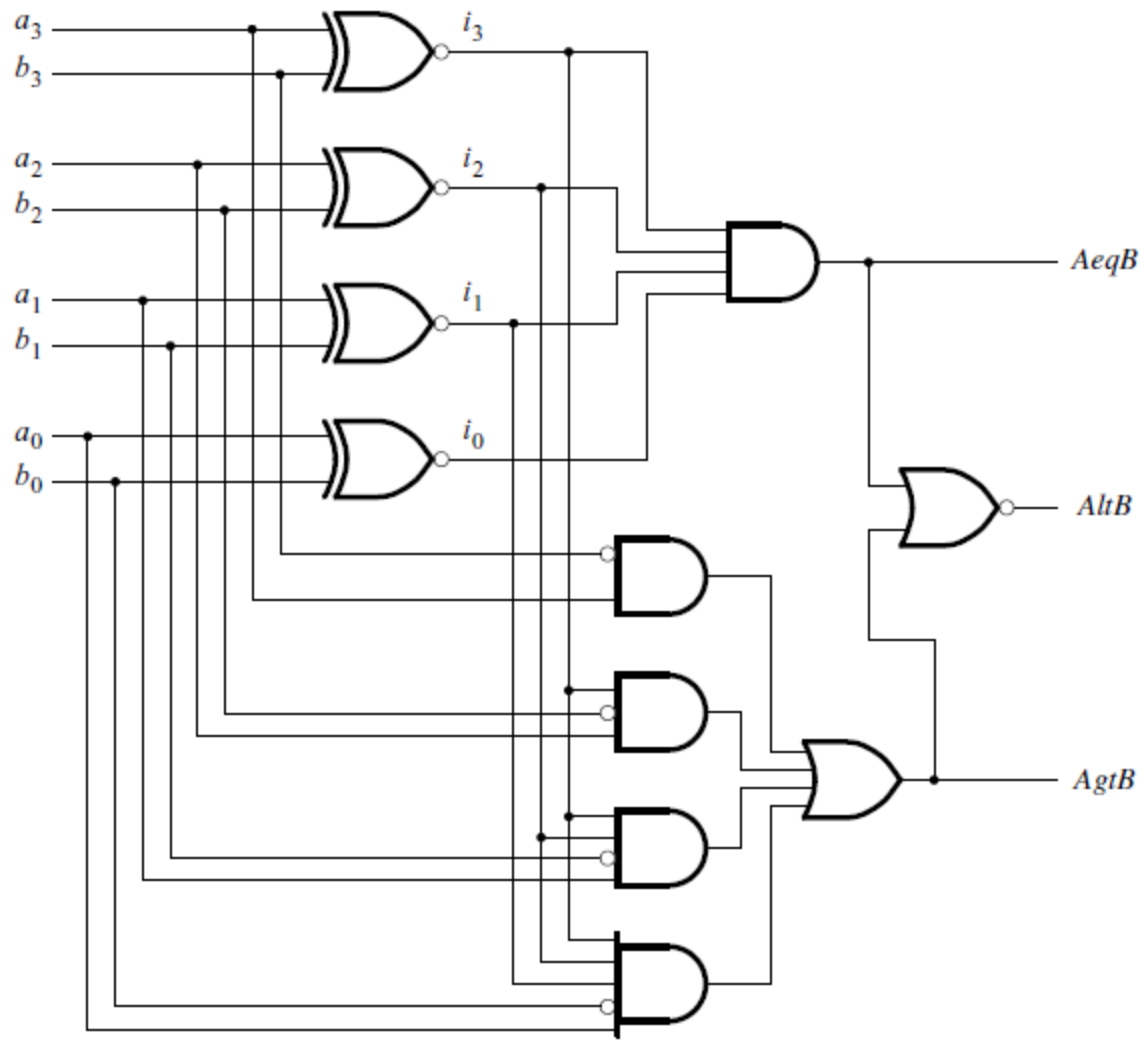

[ Figure 4.22 from the textbook ]

# **Example Problems from Chapter 4**


# Example 1: SOP vs Decoders

Implement the function

$$f(w_1, w_2, w_3) = \Sigma m(0, 1, 3, 4, 6, 7)$$

by using a 3-8 binary decoder and one OR gate.

# Solution Circuit

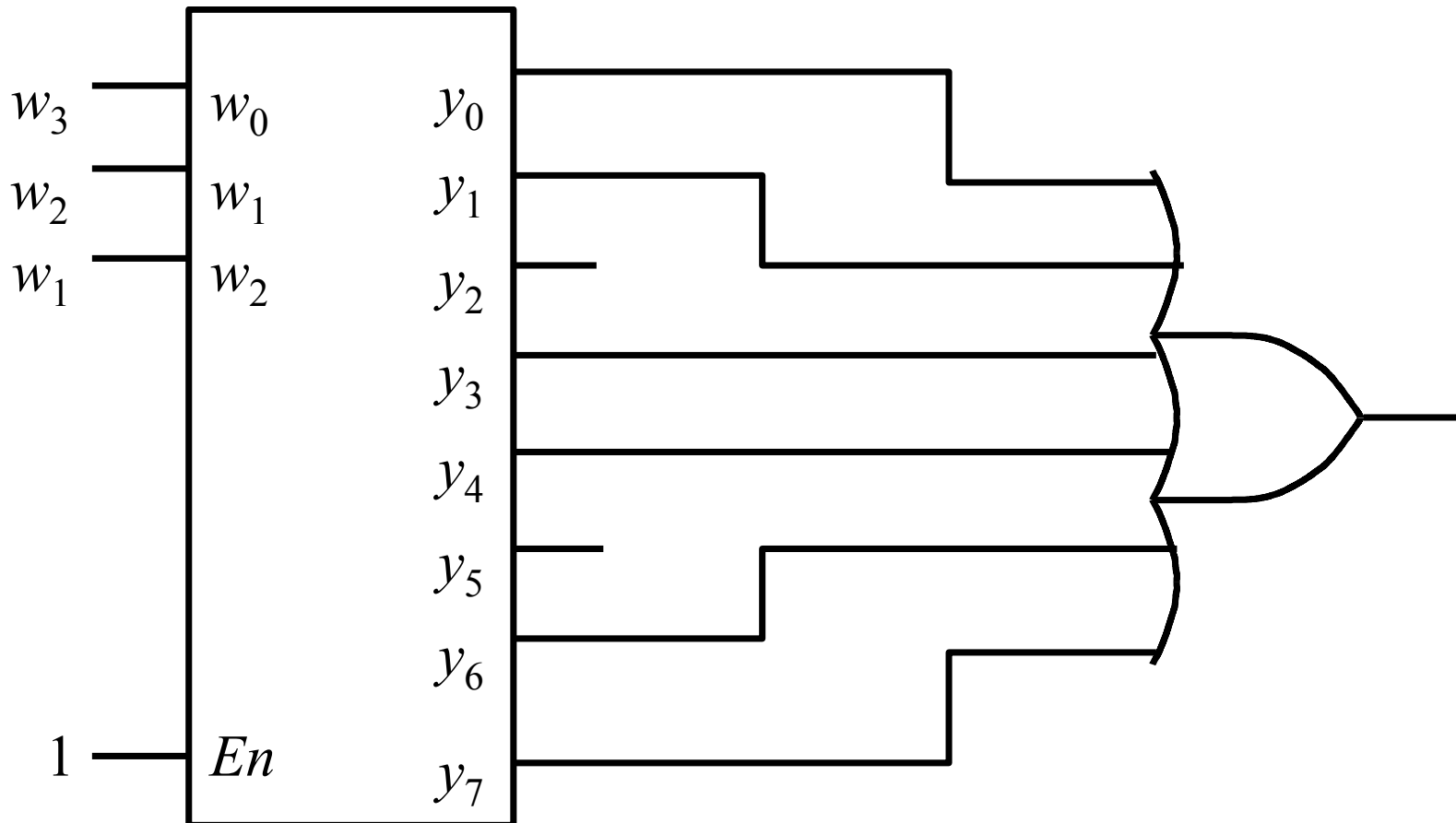

$$f(w_1, w_2, w_3) = \sum m(0, 1, 3, 4, 6, 7)$$

## Example 2: Implement an 8-to-3 binary encoder

$w_7$	$w_6$	$w_5$	$w_4$	$w_3$	$w_2$	$w_1$	$w_0$	$y_2$	$y_1$	$y_0$
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1



## Example 2: Implement an 8-to-3 binary encoder

$w_7$	$w_6$	$w_5$	$w_4$	$w_3$	$w_2$	$w_1$	$w_0$	$y_2$	$y_1$	$y_0$
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1

$$y_2 = w_4 + w_5 + w_6 + w_7$$

$$y_1 = w_2 + w_3 + w_6 + w_7$$

$$y_0 = w_1 + w_3 + w_5 + w_7$$

# Example 3: Circuit implementation using a multiplexer

Implement the function

$$f(w_1, w_2, w_3, w_4, w_5) = \bar{w}_1 \bar{w}_2 \bar{w}_4 \bar{w}_5 + w_1 w_2 + w_1 w_3 + w_1 w_4 + w_3 w_4 w_5$$

using a 4-to-1 multiplexer

# Some Boolean Algebra Leads To

$$\overline{w_1}\overline{w_2}\overline{w_4}\overline{w_5} + w_1w_2 + w_1w_3 + w_1w_4 + w_3w_4w_5$$

$$\overline{w_1}\overline{w_4}(\overline{w_5}\overline{w_2}) + w_4(w_3w_5) + w_1(w_2 + w_3) + w_1w_4(1)$$


$$\overline{w_1}\overline{w_4}(\overline{w_5}\overline{w_2}) + (\overline{w_1} + w_1)w_4(w_3w_5) + w_1(\overline{w_4} + w_4)(w_2 + w_3) + w_1w_4(1)$$

$$\overline{w_1}\overline{w_4}(\overline{w_5}\overline{w_2}) + \overline{w_1}w_4(w_3w_5) + w_1\overline{w_4}(w_2 + w_3) + w_1w_4(w_3w_5 + (w_2 + w_3) + 1)$$

$$\overline{w_1}\overline{w_4}(\overline{w_5}\overline{w_2}) + \overline{w_1}w_4(w_3w_5) + w_1\overline{w_4}(w_2 + w_3) + w_1w_4(1)$$

Note that the split is by  $w_1$  and  $w_4$ , not  $w_1$  and  $w_2$


# Solution Circuit

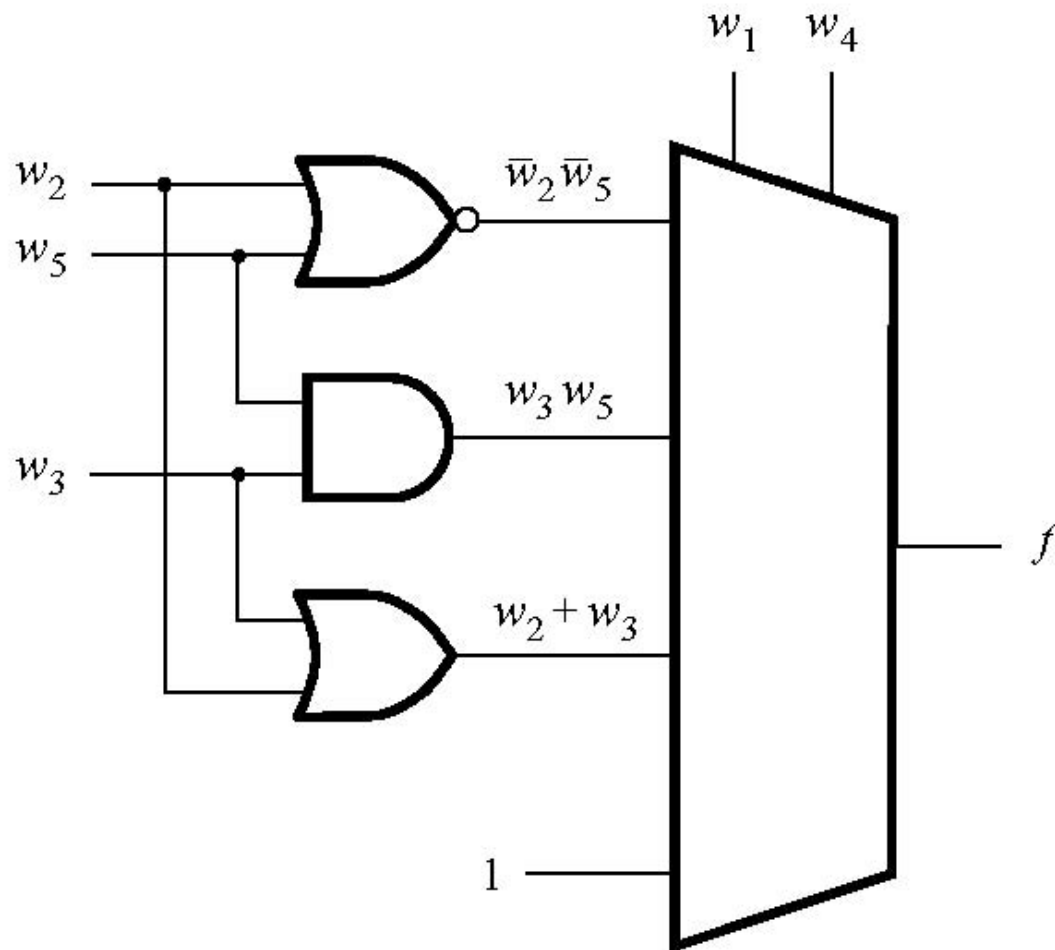

[ Figure 4.46 from the textbook ]


# **Some Final Things from Chapter 4**

# A shifter circuit

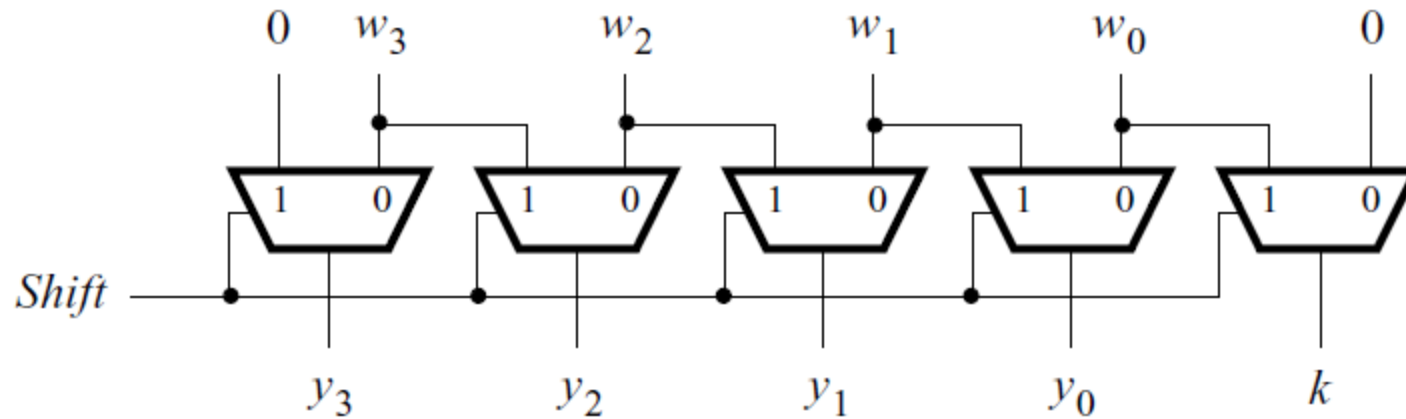


[ Figure 4.50 from the textbook ]

# A shifter circuit

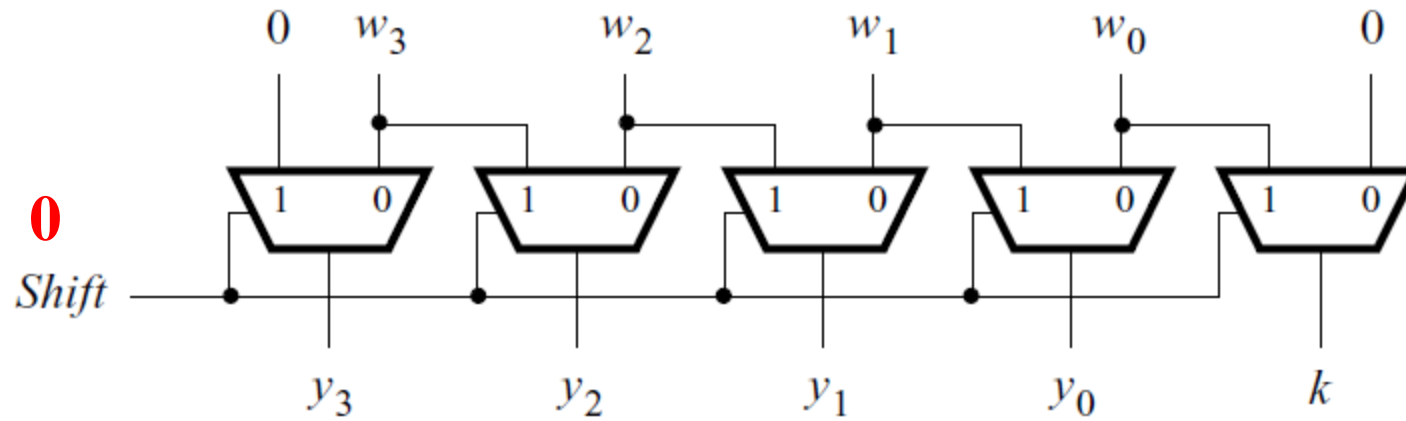


# A shifter circuit

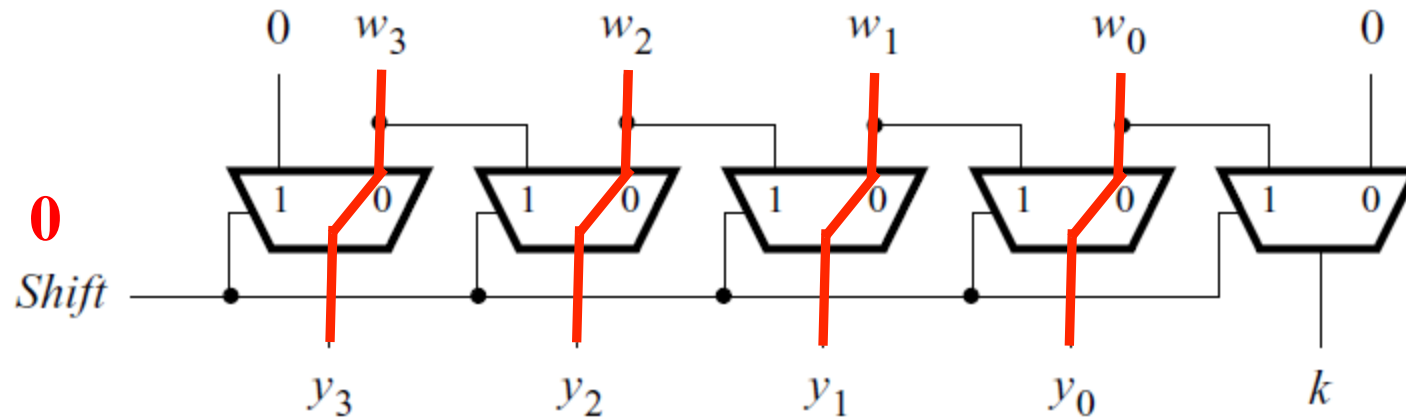




# A shifter circuit

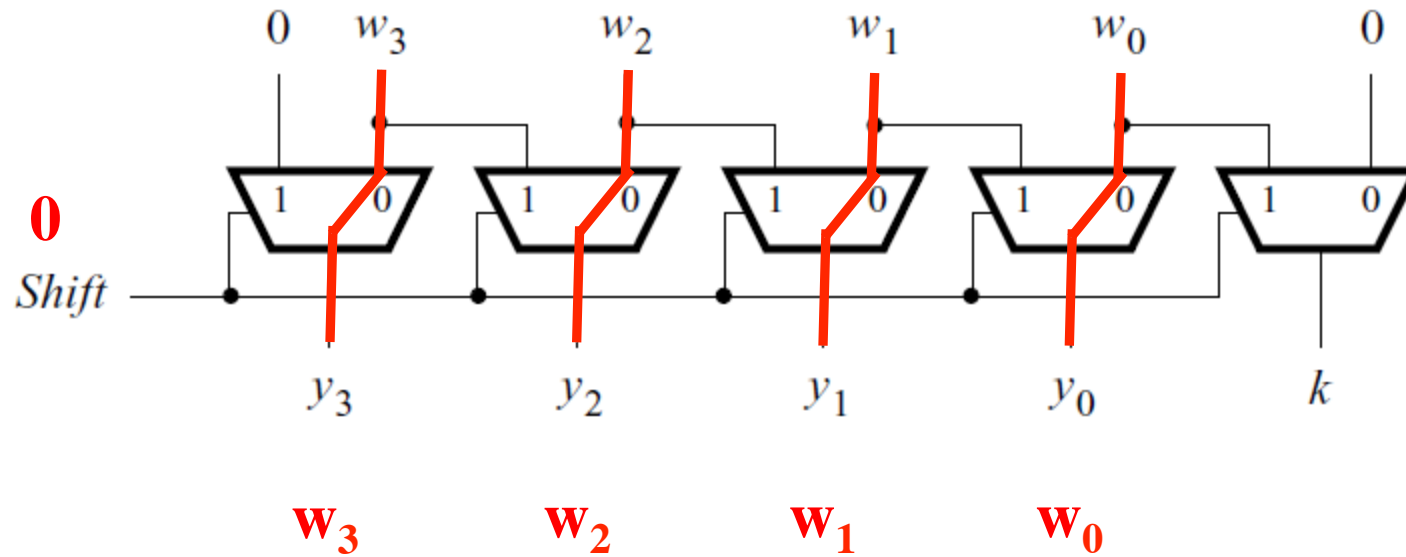


No shift in this case.


# A shifter circuit

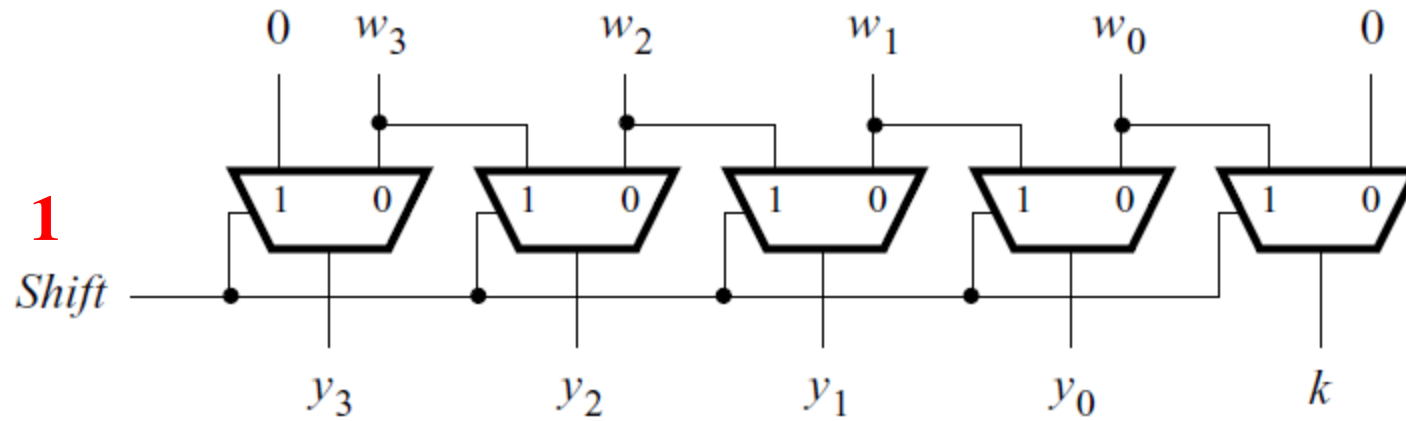

# A shifter circuit

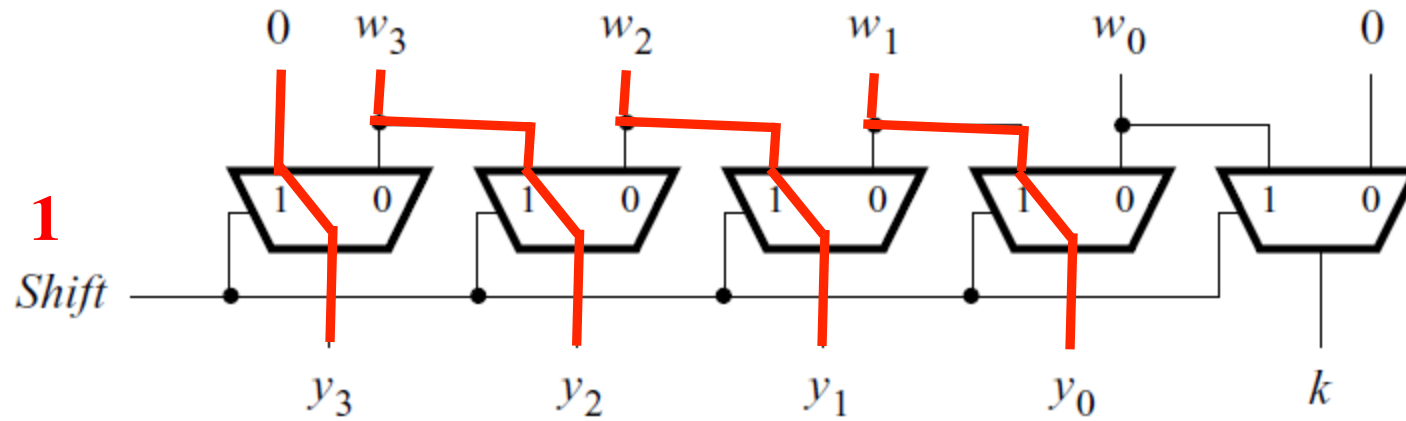


# A shifter circuit

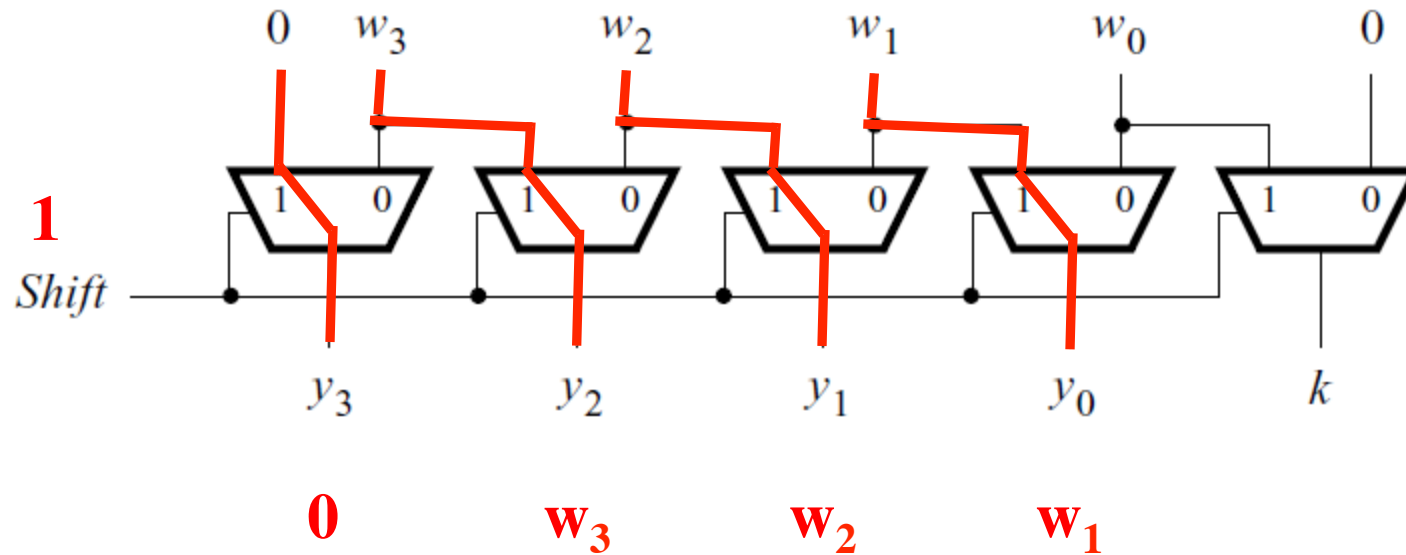

Shift to the right by 1 bit

# A shifter circuit

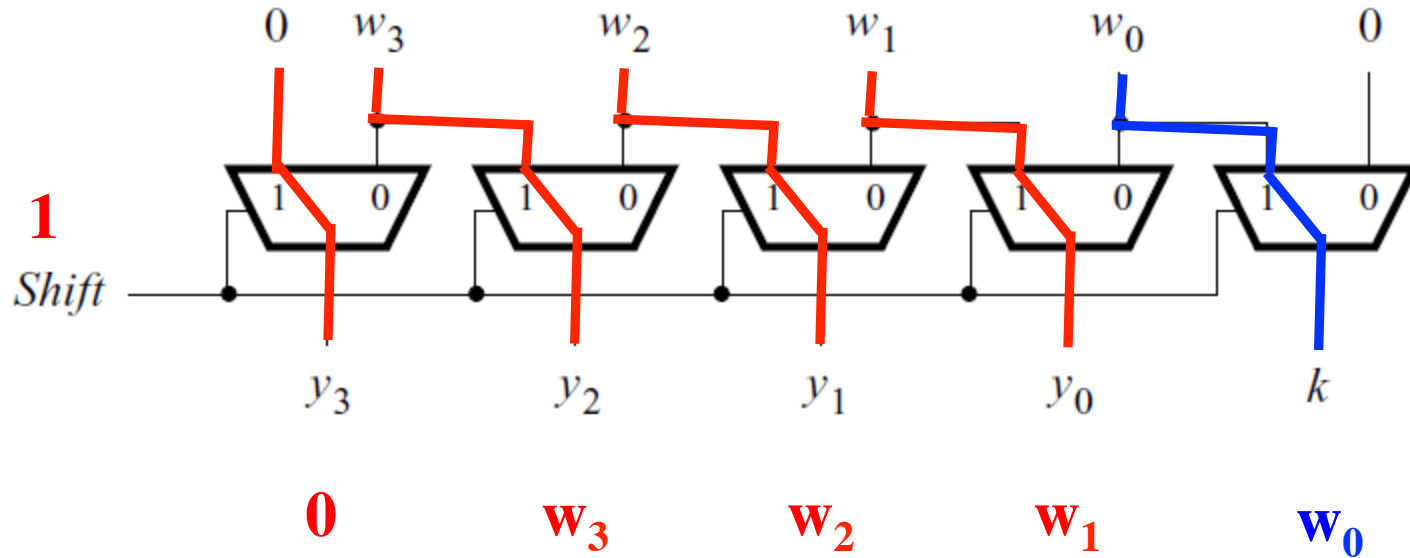


Shift to the right by 1 bit

# A barrel shifter circuit

$s_1$	$s_0$	$y_3$	$y_2$	$y_1$	$y_0$
0	0	$w_3$	$w_2$	$w_1$	$w_0$
0	1	$w_0$	$w_3$	$w_2$	$w_1$
1	0	$w_1$	$w_0$	$w_3$	$w_2$
1	1	$w_2$	$w_1$	$w_0$	$w_3$

(a) Truth table

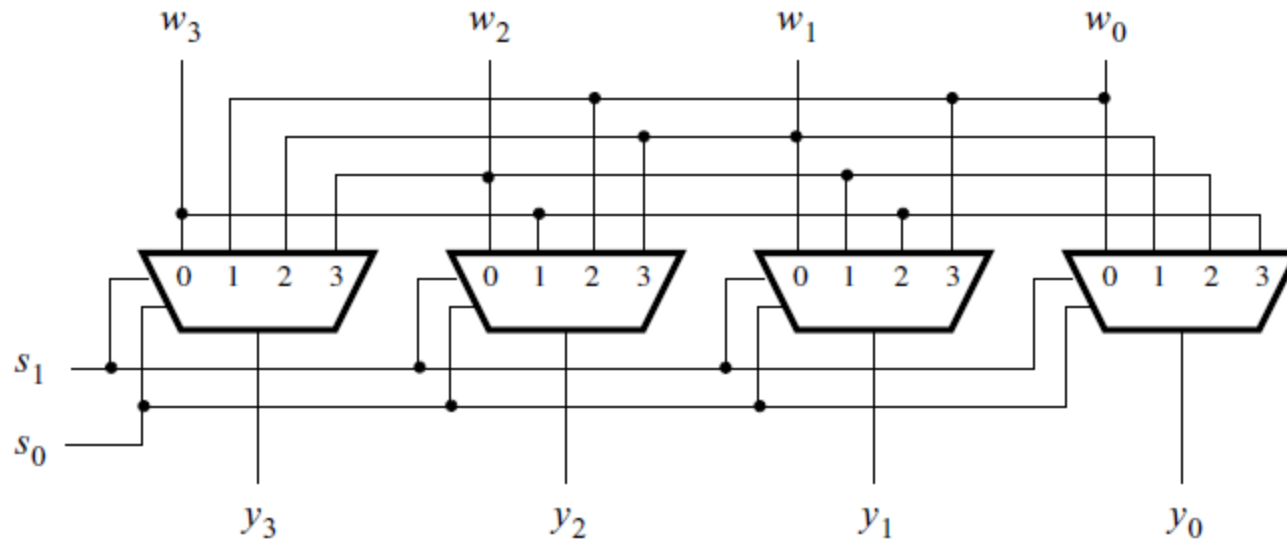

(b) Circuit

[ Figure 4.51 from the textbook ]

**Questions?**

**THE END**