



CprE 281: Digital Logic

Instructor: Alexander Stoytchev

<http://www.ece.iastate.edu/~alexs/classes/>

Mealy State Model

*CprE 281: Digital Logic
Iowa State University, Ames, IA
Copyright © Alexander Stoytchev*


Administrative Stuff

- **Homework 10 is out**
- **It is due on Monday Nov 16 @ 4pm**

Administrative Stuff


- **Final Project**

The general form of a synchronous sequential circuit

 


[Figure 6.1 from the textbook]

Moore Type

 

Mealy Type

 

Sample Problem

Implement a 11 detector. In other words, the output should be equal to 1 if two consecutive 1's have been detected on the input line. The output should become 1 as soon as the second 1 is detected in the input.

Sequences of input and output signals

Clock cycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
w :	0	1	0	1	1	0	1	1	1	0	1
z :	0	0	0	0	1	0	0	1	1	0	0

Sequences of input and output signals

Clock cycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
input w :	0	1	0	1	1	0	1	1	1	0	1
output z :	0	0	0	0	1	0	0	1	1	0	0

[Figure 6.22 from the textbook]

Sequences of input and output signals

Clock cycle:	t ₀	t ₁	t ₂	t ₃	t ₄	t ₅	t ₆	t ₇	t ₈	t ₉	t ₁₀
input w:	0	1	0	1	1	0	1	1	1	0	1
output z:	0	0	0	0	1	0	0	1	1	0	0

[Figure 6.22 from the textbook]

Sequences of input and output signals

Clock cycle:	t ₀	t ₁	t ₂	t ₃	t ₄	t ₅	t ₆	t ₇	t ₈	t ₉	t ₁₀
input w:	0	1	0	1	1	0	1	1	1	0	1
output z:	0	0	0	0	1	0	0	1	1	0	0

[Figure 6.22 from the textbook]

Sequences of input and output signals

Clock cycle:	t ₀	t ₁	t ₂	t ₃	t ₄	t ₅	t ₆	t ₇	t ₈	t ₉	t ₁₀
input w:	0	1	0	1	1	0	1	1	1	0	1
output z:	0	0	0	0	1	0	0	1	1	0	0

[Figure 6.22 from the textbook]

Sequences of input and output signals

Clock cycle:	t ₀	t ₁	t ₂	t ₃	t ₄	t ₅	t ₆	t ₇	t ₈	t ₉	t ₁₀
input w:	0	1	0	1	1	0	1	1	1	0	1
output z:	0	0	0	0	1	0	0	1	1	0	0

[Figure 6.22 from the textbook]

Sequences of input and output signals

Clock cycle:	t ₀	t ₁	t ₂	t ₃	t ₄	t ₅	t ₆	t ₇	t ₈	t ₉	t ₁₀
input w:	0	1	0	1	1	0	1	1	1	0	1
output z:	0	0	0	0	1	0	0	1	1	0	0


[Figure 6.22 from the textbook]

Sequences of input and output signals

Clock cycle:	t ₀	t ₁	t ₂	t ₃	t ₄	t ₅	t ₆	t ₇	t ₈	t ₉	t ₁₀
input w:	0	1	0	1	1	0	1	1	1	0	1
output z:	0	0	0	0	1	0	0	1	1	0	0

[Figure 6.22 from the textbook]


State diagram of an FSM that realizes the task

 

[Figure 6.23 from the textbook]


Let's Do a Simulation

Clock cycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}	
input w :	<input type="checkbox"/>	0	1	0	1	1	0	1	1	1	0	1
output z :	0	0	0	0	1	0	0	1	1	0	0	

 


Let's Do a Simulation

Clock cycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
input w :	0	1	0	1	1	0	1	1	1	0	1
output z :	0	0	0	0	1	0	0	1	1	0	0

 


Let's Do a Simulation

Clock cycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
input w :	0	1	0	1	1	0	1	1	1	0	1
output z :	0	0	0	0	1	0	0	1	1	0	0

 


Let's Do a Simulation

Clock cycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
input w :	0	1	0	1	1	0	1	1	1	0	1
output z :	0	0	0	0	1	0	0	1	1	0	0

 


Let's Do a Simulation

Clock cycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
input w :	0	1	0	1	1	0	1	1	1	0	1
output z :	0	0	0	0	1	0	0	1	1	0	0

 


Let's Do a Simulation

Clock cycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
input w :	0	1	0	1	1	0	1	1	1	0	1
output z :	0	0	0	0	1	0	0	1	1	0	0

 


Let's Do a Simulation

Clock cycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
input w :	0	1	0	1	1	0	1	1	1	0	1
output z :	0	0	0	0	1	0	0	1	1	0	0

 


Let's Do a Simulation

Clock cycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
input w :	0	1	0	1	1	0	1	1	1	0	1
output z :	0	0	0	0	1	0	0	1	1	0	0

 


Let's Do a Simulation

Clock cycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
input w :	0	1	0	1	1	0	1	1	1	0	1
output z :	0	0	0	0	1	0	0	1	1	0	0

 


Let's Do a Simulation

Clock cycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
input w :	0	1	0	1	1	0	1	1	1	0	1
output z :	0	0	0	0	1	0	0	1	1	0	0

 


Let's Do a Simulation

Clock cycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
input w :	0	1	0	1	1	0	1	1	1	0	1
output z :	0	0	0	0	1	0	0	1	1	0	0

 


Let's Do a Simulation

Clock cycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
input w :	0	1	0	1	1	0	1	1	1	0	1
output z :	0	0	0	0	1	0	0	1	1	0	0

 


Let's Do a Simulation

Clock cycle:	t ₀	t ₁	t ₂	t ₃	t ₄	t ₅	t ₆	t ₇	t ₈	t ₉	t ₁₀
input <i>w</i> :	0	1	0	1	1	0	1	1	1	0	1
output <i>z</i> :	0	0	0	0	1	0	0	1	1	0	0

 


Let's Do a Simulation

Clock cycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
input w :	0	1	0	1	1	0	1	1	1	0	1
output z :	0	0	0	0	1	0	0	1	1	0	0

 


Let's Do a Simulation

Clock cycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
input w :	0	1	0	1	1	0	1	1	1	0	1
output z :	0	0	0	0	1	0	0	1	1	0	0

 


Let's Do a Simulation

Clock cycle:	t ₀	t ₁	t ₂	t ₃	t ₄	t ₅	t ₆	t ₇	t ₈	t ₉	t ₁₀
input <i>w</i> :	0	1	0	1	1	0	1	1	1	0	1
output <i>z</i> :	0	0	0	0	1	0	0	1	1	0	0

 


Let's Do a Simulation

Clock cycle:	t ₀	t ₁	t ₂	t ₃	t ₄	t ₅	t ₆	t ₇	t ₈	t ₉	t ₁₀
input w:	0	1	0	1	1	0	1	1	1	0	1
output z:	0	0	0	0	1	0	0	1	1	0	0

 


Let's Do a Simulation

Clock cycle:	t ₀	t ₁	t ₂	t ₃	t ₄	t ₅	t ₆	t ₇	t ₈	t ₉	t ₁₀
input <i>w</i> :	0	1	0	1	1	0	1	1	1	0	1
output <i>z</i> :	0	0	0	0	1	0	0	1	1	0	0

 


Let's Do a Simulation

Clock cycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
input w :	0	1	0	1	1	0	1	1	1	0	1
output z :	0	0	0	0	1	0	0	1	1	0	0

 


 Now Let's Do the State Table for this FSM



Present state	Next state		Output z	
	$w = 0$	$w = 1$	$w = 0$	$w = 1$
A				
B				

 Now Let's Do the State Table for this FSM



Present state	Next state		Output z	
	$w = 0$	$w = 1$	$w = 0$	$w = 1$
A	A	B	0	0
B	A	B	0	1

The State Table for this FSM

Present state	Next state		Output z	
	$w = 0$	$w = 1$	$w = 0$	$w = 1$
A	A	B	0	0
B	A	B	0	1

Let's Do the State-assigned Table

Present state	Next state		Output z	
	$w = 0$	$w = 1$	$w = 0$	$w = 1$
A	A	B	0	0
B	A	B	0	1

Present state	Next state		Output	
	$w = 0$	$w = 1$	$w = 0$	$w = 1$
y	Y	Y	z	z
A 0				
B 1				

Let's Do the State-assigned Table

Present state	Next state		Output z	
	$w = 0$	$w = 1$	$w = 0$	$w = 1$
A	A	B	0	0
B	A	B	0	1

	Present state	Next state		Output	
		$w = 0$	$w = 1$	$w = 0$	$w = 1$
	y	Y	Y	z	z
A	0	0	1	0	0
B	1	0	1	0	1

The State-assigned Table

	Present state	Next state		Output	
		$w = 0$	$w = 1$	$w = 0$	$w = 1$
	y	Y	Y	z	z
A	0	0	1	0	0
B	1	0	1	0	1

The State-assigned Table

	Present state	Next state		Output	
		$w = 0$	$w = 1$	$w = 0$	$w = 1$
	y	Y	Y	z	z
A	0	0	1	0	0
B	1	0	1	0	1

$$Y = D = w \quad z = wy$$


The State-assigned Table

	Present state	Next state		Output	
		$w = 0$	$w = 1$	$w = 0$	$w = 1$
	y	Y	Y	z	z
A	0	0	1	0	0
B	1	0	1	0	1

$$Y = D = w \quad z = wy$$


This assumes D flip-flop

Circuit Implementation of the FSM

 


$$Y = D = w \quad z = wy$$

Circuit & Timing Diagram

 

(a) Circuit

 


(b) Timing diagram

[Figure 6.26 from the textbook]


What if we wanted the output signal to be delayed by 1 clock cycle?

Circuit Implementation of the Modified FSM

 


[Figure 6.27a from the textbook]

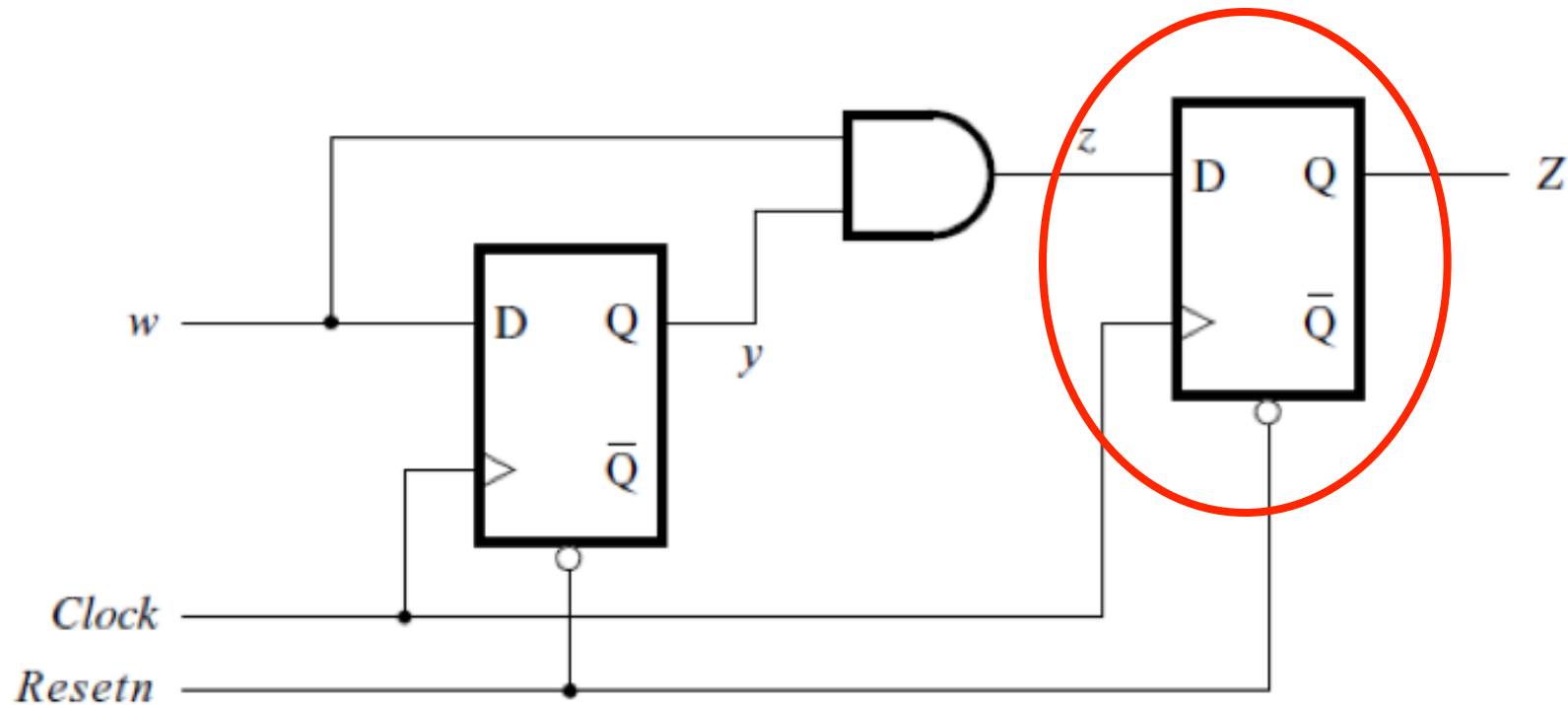Circuit Implementation of the Modified FSM




This flip-flop delays the output signal by one clock cycle

Circuit & Timing Diagram

 


(a) Circuit

 


[Figure 6.27 from the textbook]

The general form of a synchronous sequential circuit

 


[Figure 6.1 from the textbook]


Moore Type

 


Mealy Type

 


Moore

 




Mealy

 


Moore

 


Mealy

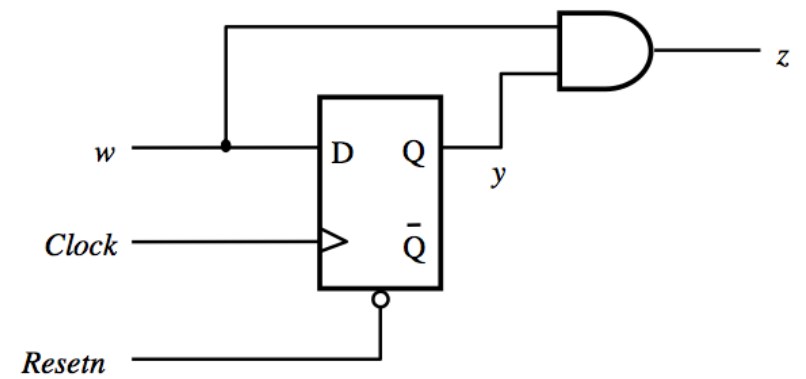  

Mealy

 


Moore

 


Notice that the output of the Moore machine is delayed by one clock cycle

Mealy

 

Moore

 

Questions?

THE END