



# **CprE 281: Digital Logic**

**Instructor: Alexander Stoytchev**

**<http://www.ece.iastate.edu/~alexs/classes/>**

# Simple Processor

*CprE 281: Digital Logic*  
*Iowa State University, Ames, IA*  
*Copyright © Alexander Stoytchev*

# **Administrative Stuff**

- **Final Project (7% of your grade)**
- **This is due this week (during your lab)**


# **Administrative Stuff**

- **Extra Credit Homework**
- **Posted on the class web page**
- **This is due this Friday @ 4pm**

# Digital System


- **Datapath circuit**
  - To store data
  - To manipulate data
  - To transfer data from one part of the system to another
  - Comprise building blocks such as registers, shift registers, counters, multipliers, decoders, encoders, adders, etc.
- **Control circuit**
  - Controls the operation of the datapath circuit
  - Designed as a FSM

# A Simple Processor

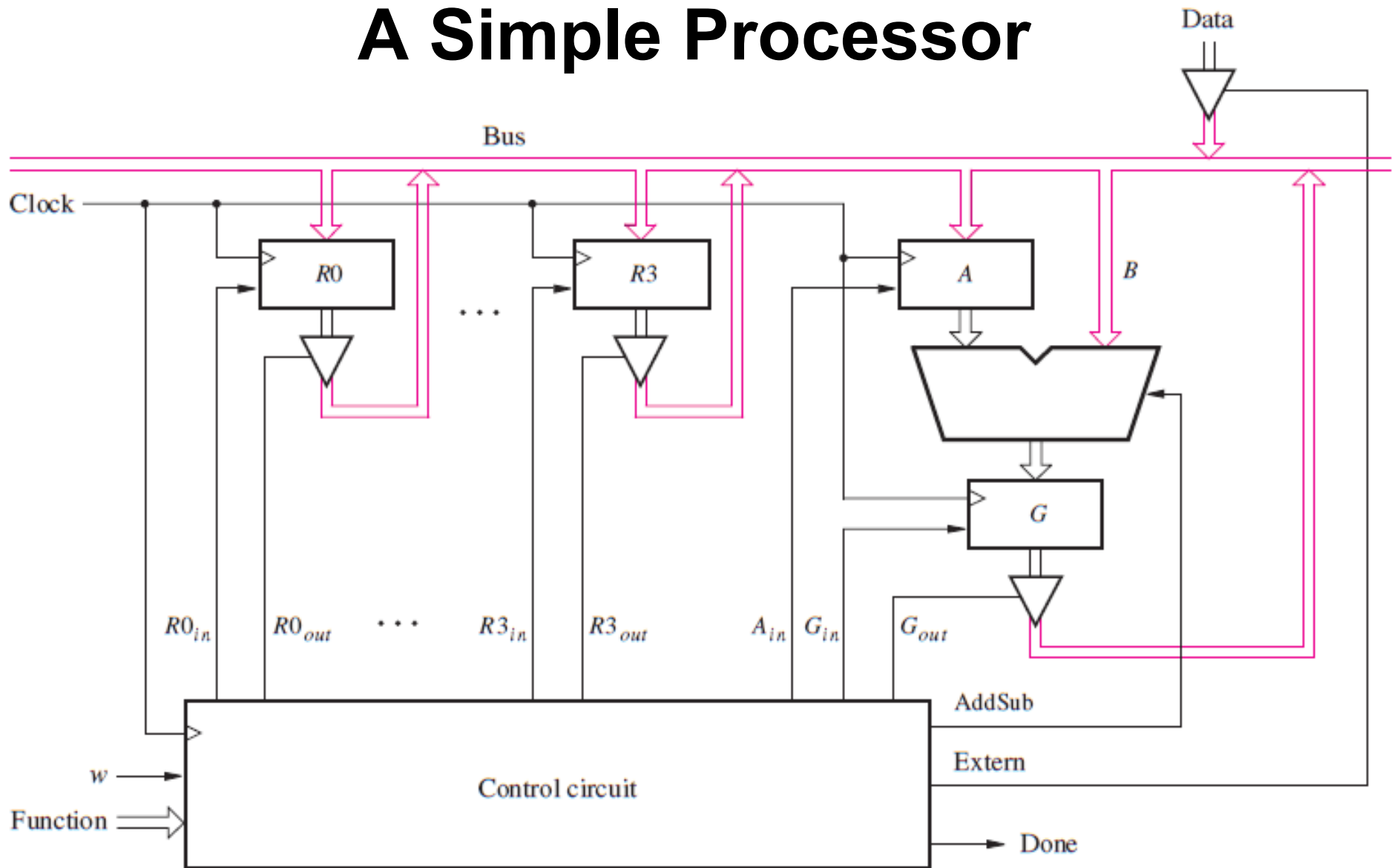


[ Figure 7.9 from the textbook ]

# What are the components?

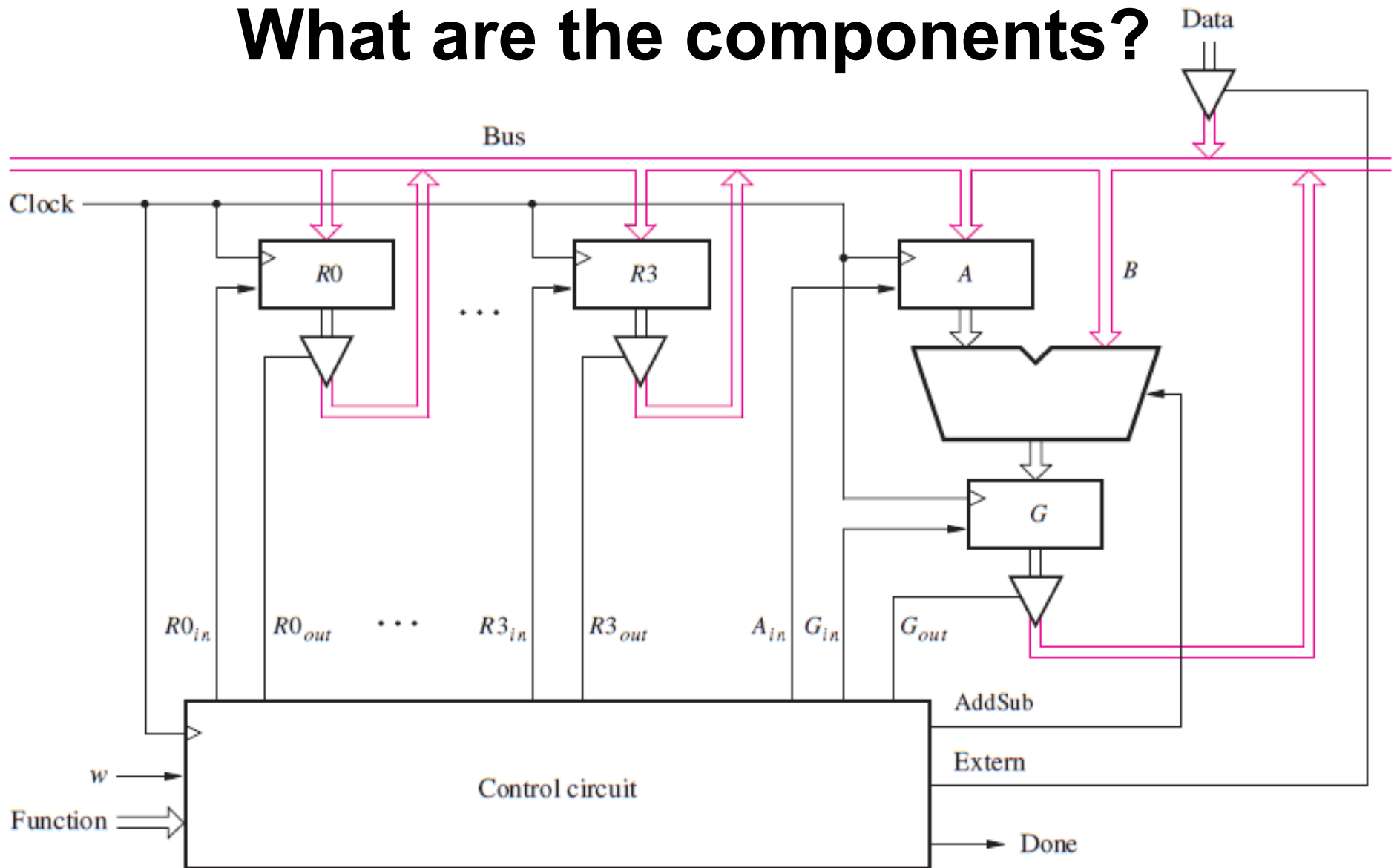

[ Figure 7.9 from the textbook ]


# Registers

 

[ Figure 7.9 from the textbook ]




# Data Bus

 


[ Figure 7.9 from the textbook ]

# Tri-State Drivers

 


[ Figure 7.9 from the textbook ]

# Arithmetic Logic Unit (ALU)

 

[ Figure 7.9 from the textbook ]


# Control Circuit

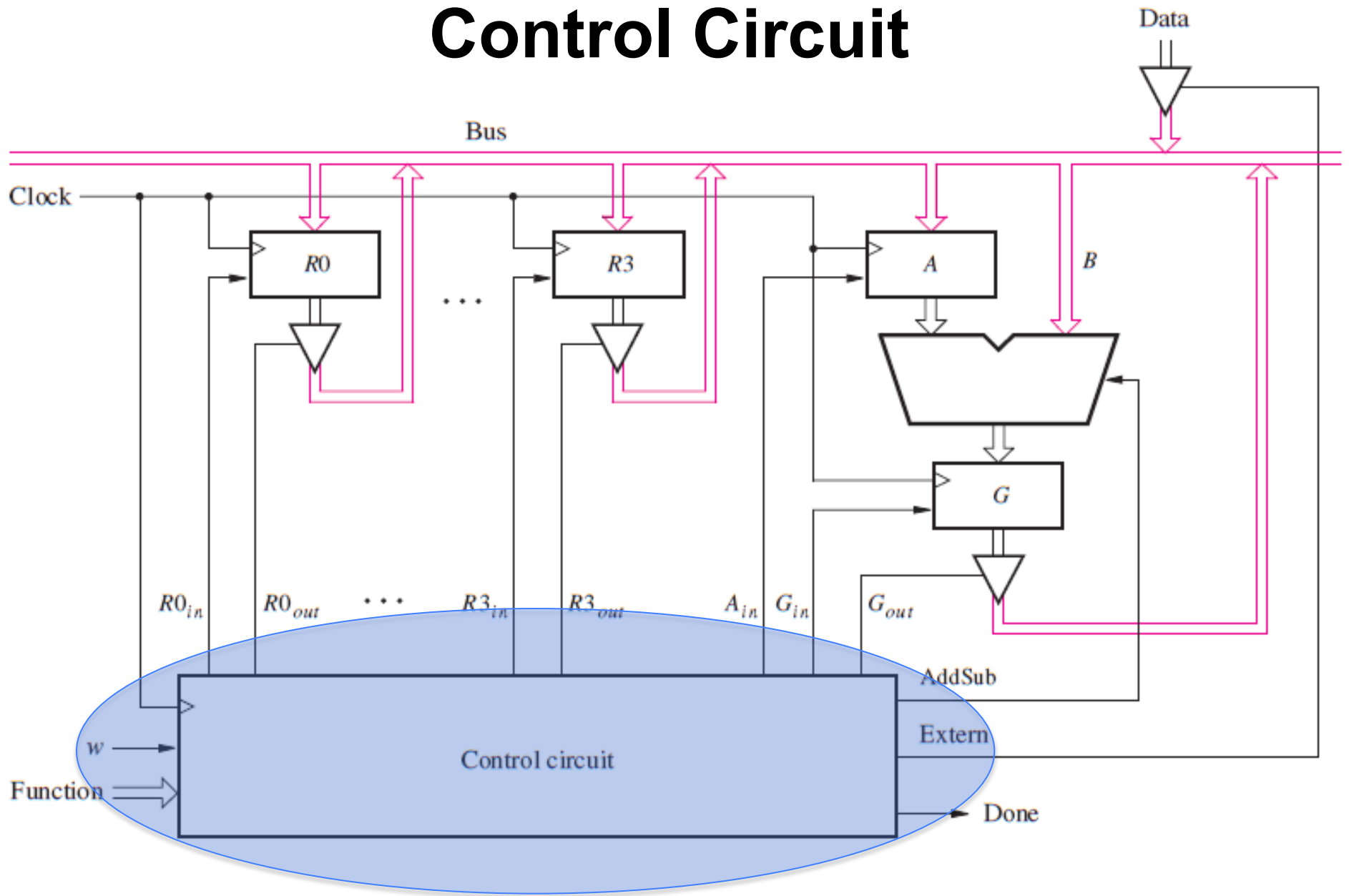

[ Figure 7.9 from the textbook ]


# **A Closer Look at the Registers**

# Register R0

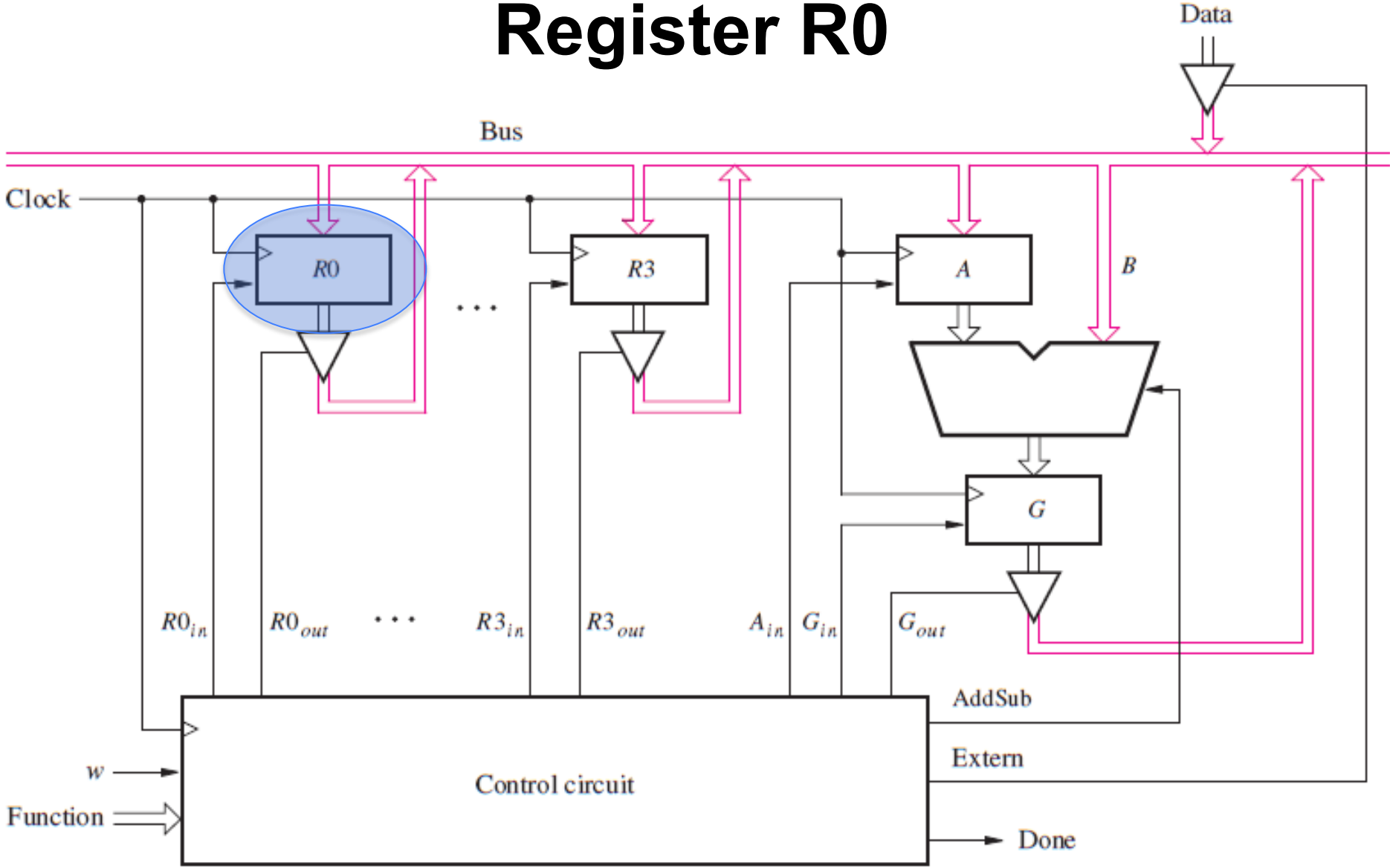


[ Figure 7.9 from the textbook ]

# All Registers

 

[ Figure 7.9 from the textbook ]


# Registers R0, R1, R2 and R3 are accessible to the programmer

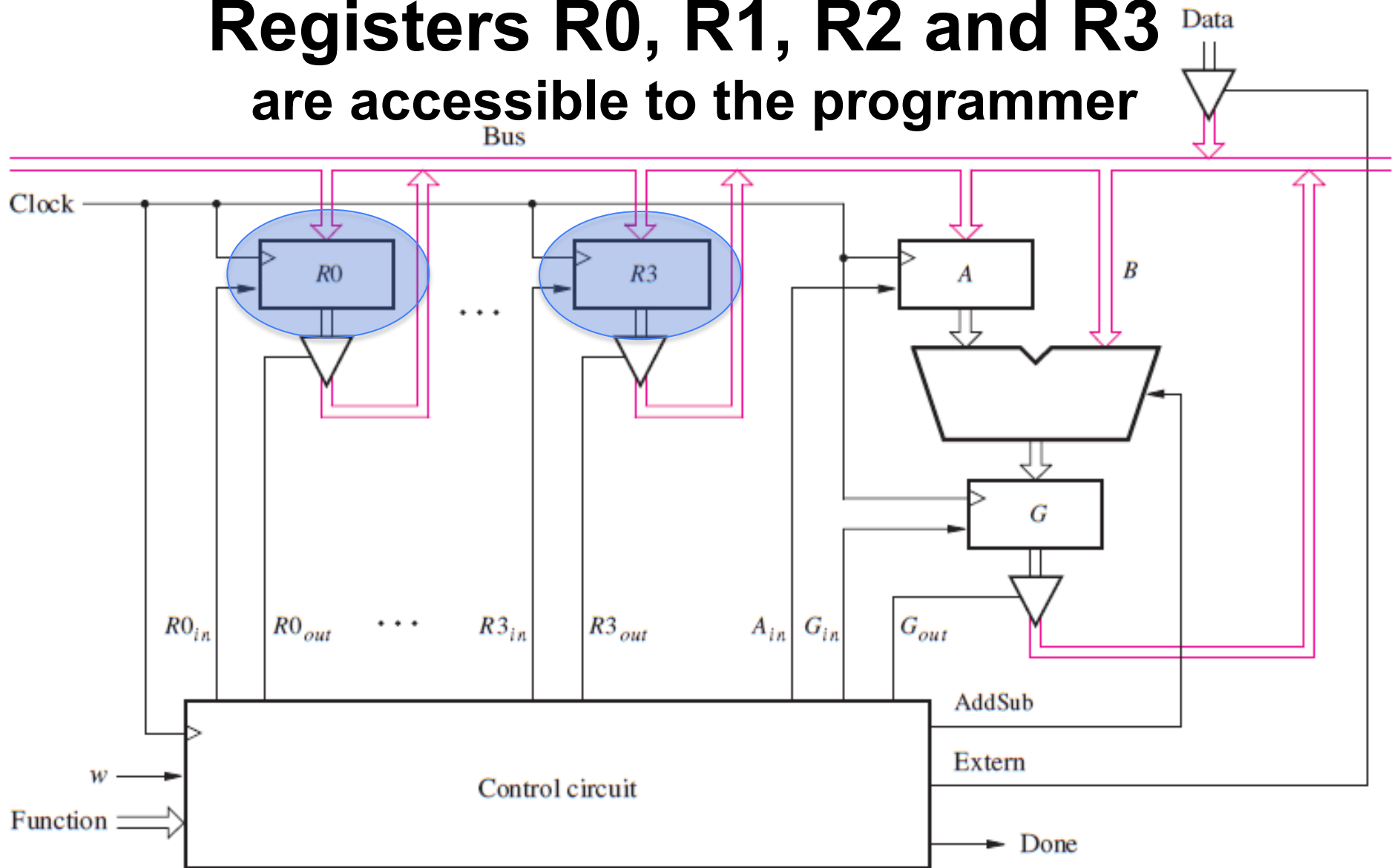

[ Figure 7.9 from the textbook ]




# Registers A and G are NOT accessible to the programmer

 


[ Figure 7.9 from the textbook ]


# 4-Bit Register

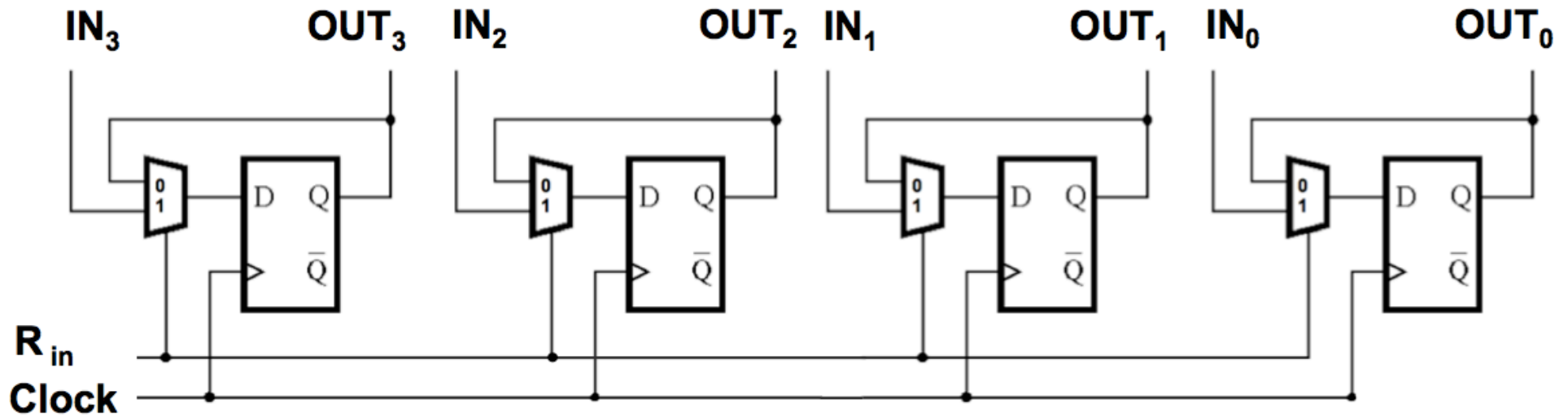


# Loading Data into the Register

 


# Loading Data into the Register

 


# Loading Data into the Register

 


# Loading Data into the Register

 

# Keeping Data into the Register

 


# Keeping Data into the Register

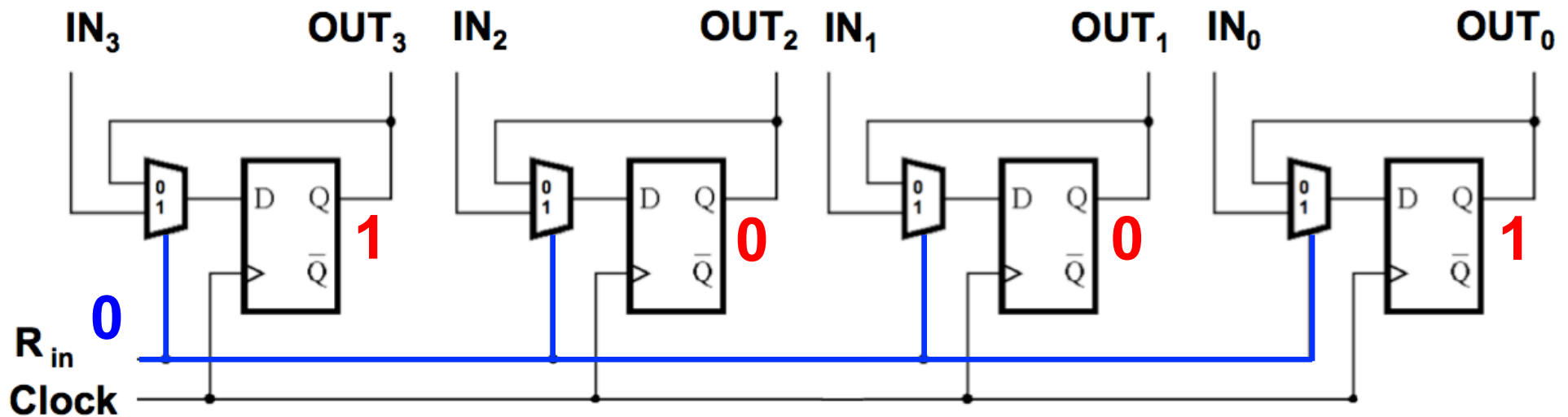



# Keeping Data into the Register

 


# **A Closer Look at the Data Bus**



 
# Bus Structure

- We need a way to transfer data from any register (device) to any other register (device)
- A bus is simply a set of  $n$  wires to transfer an  $n$ -bit data




- What if two registers write to the bus at the same time?

# One way to implement a data bus is to use multiplexers

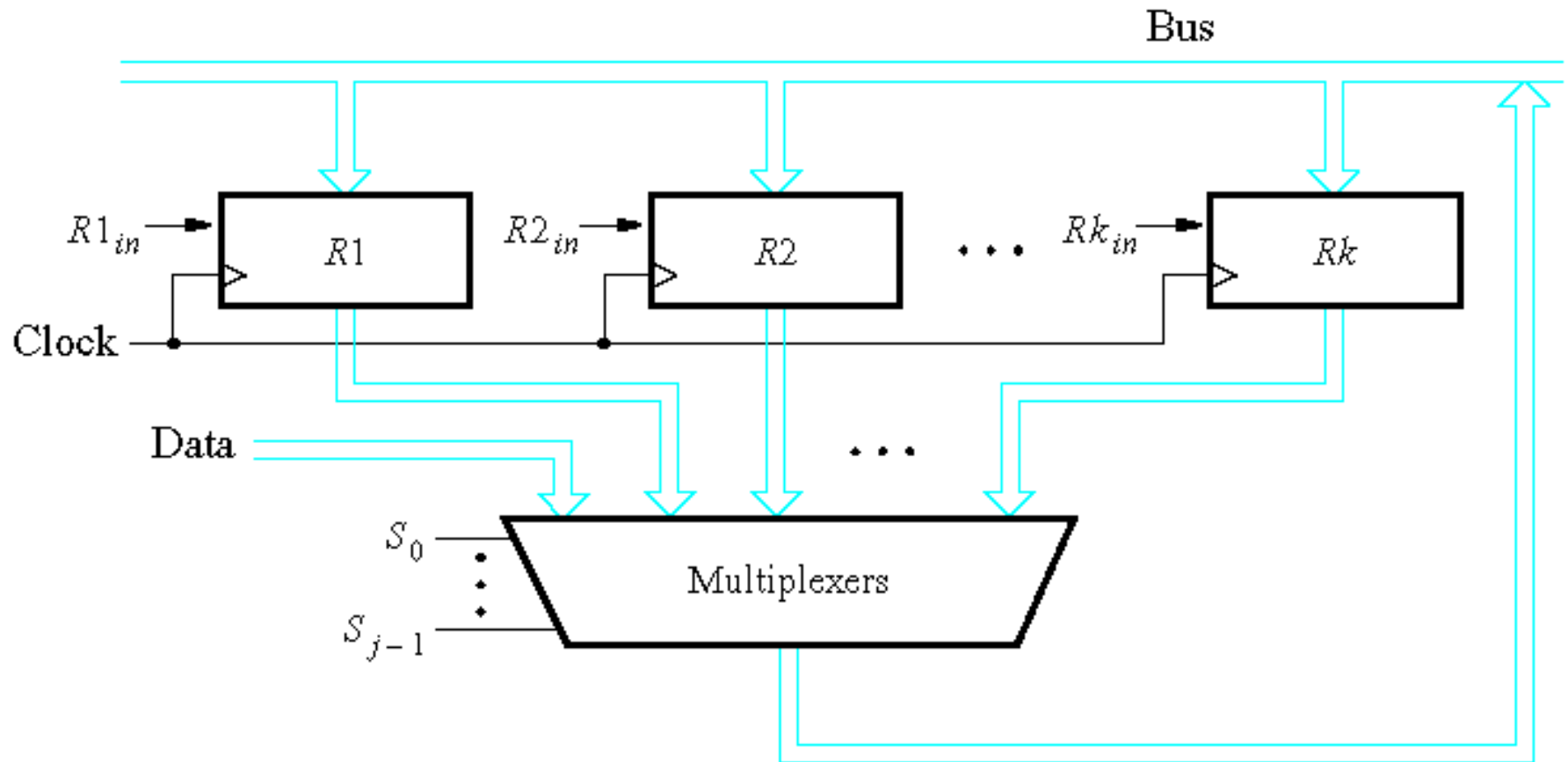


[ Figure 7.4 from the textbook ]
 
# One way to implement a data bus is to use multiplexers



This requires one multiplexer per bit.  
Assuming there are four 4-bit registers, we need four 5-to-1 multiplexers.

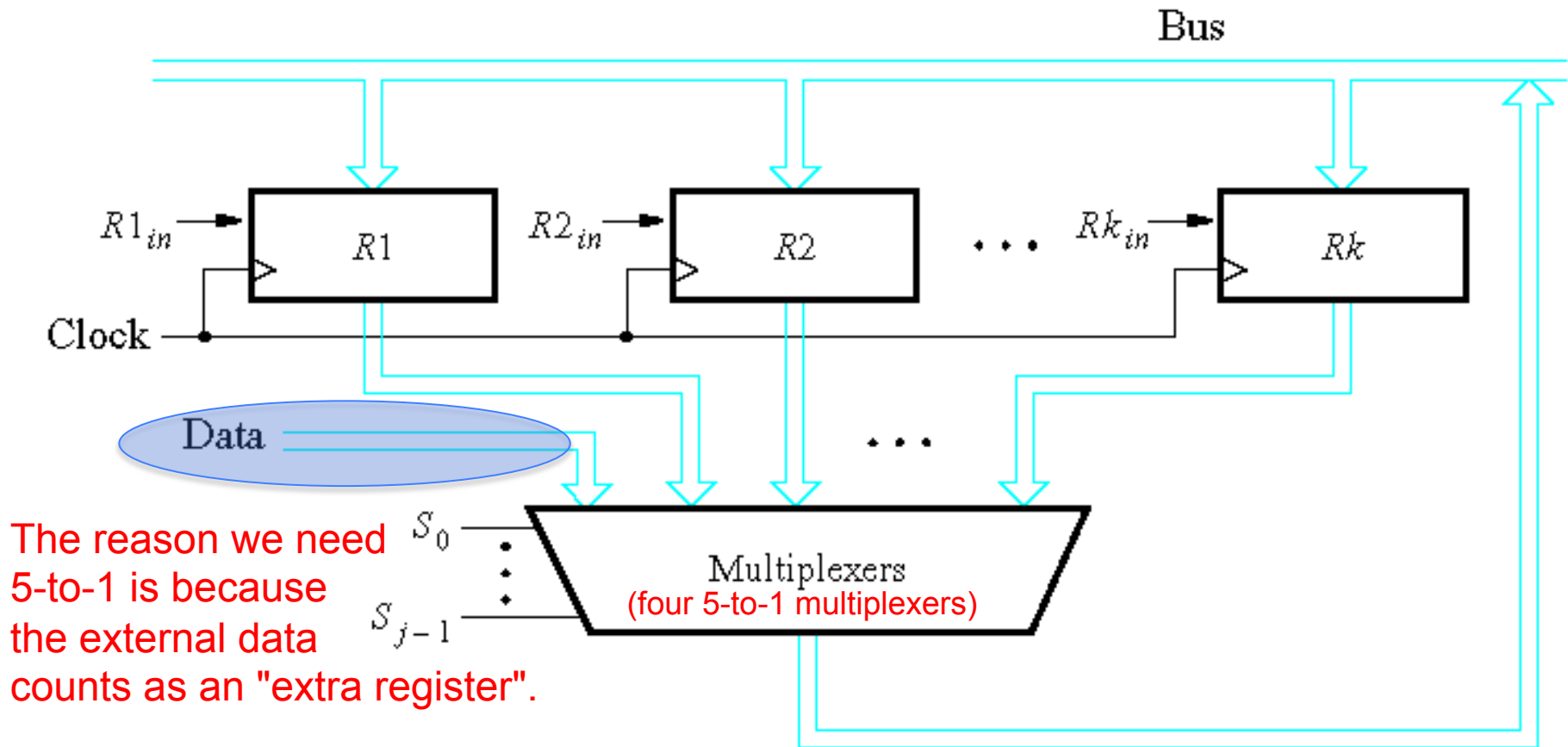
# One way to implement a data bus is to use multiplexers



# **A Closer Look at the Tri-State Driver**




# Tri-State Driver

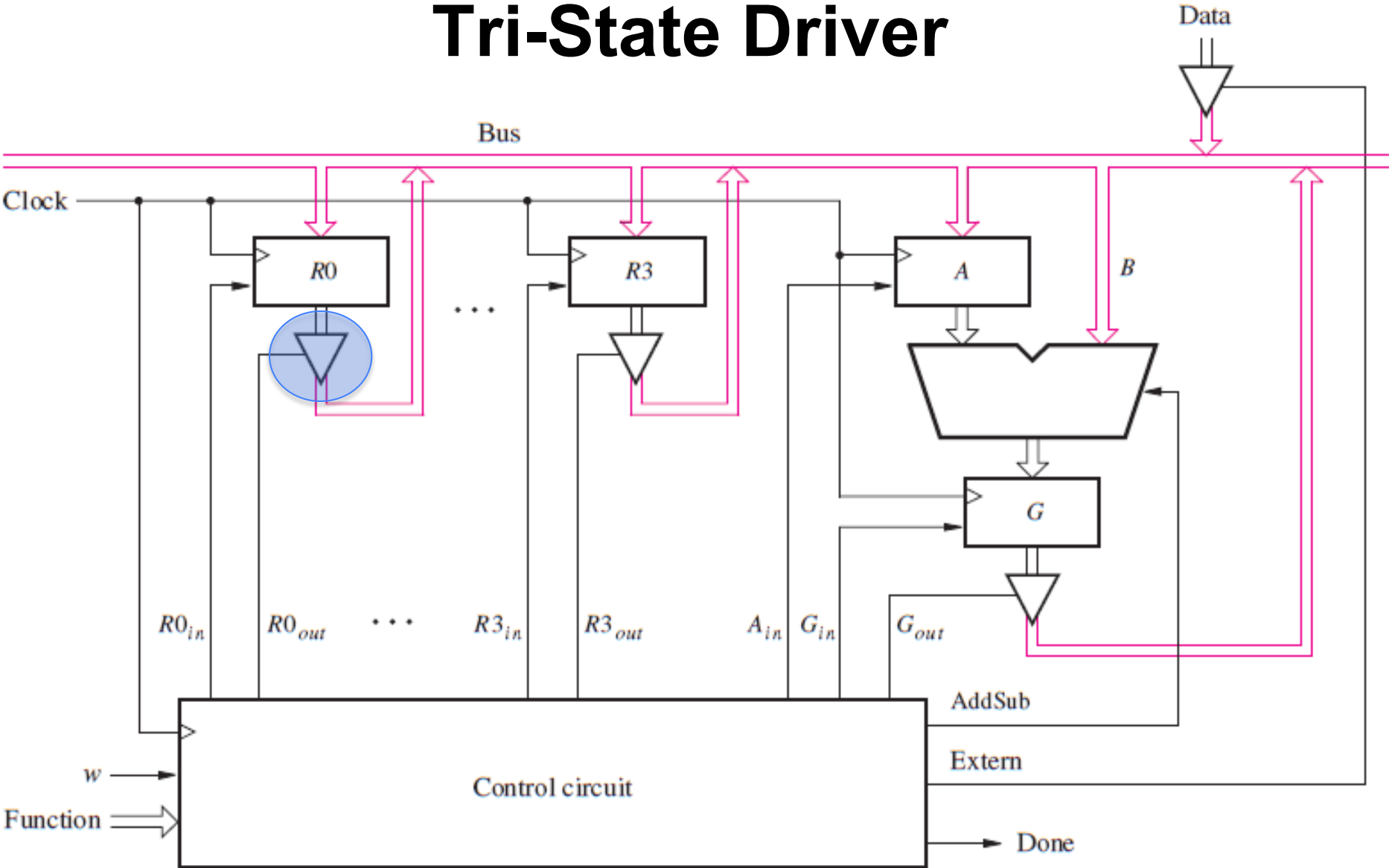

[ Figure 7.9 from the textbook ]


# All Tri-State Drivers

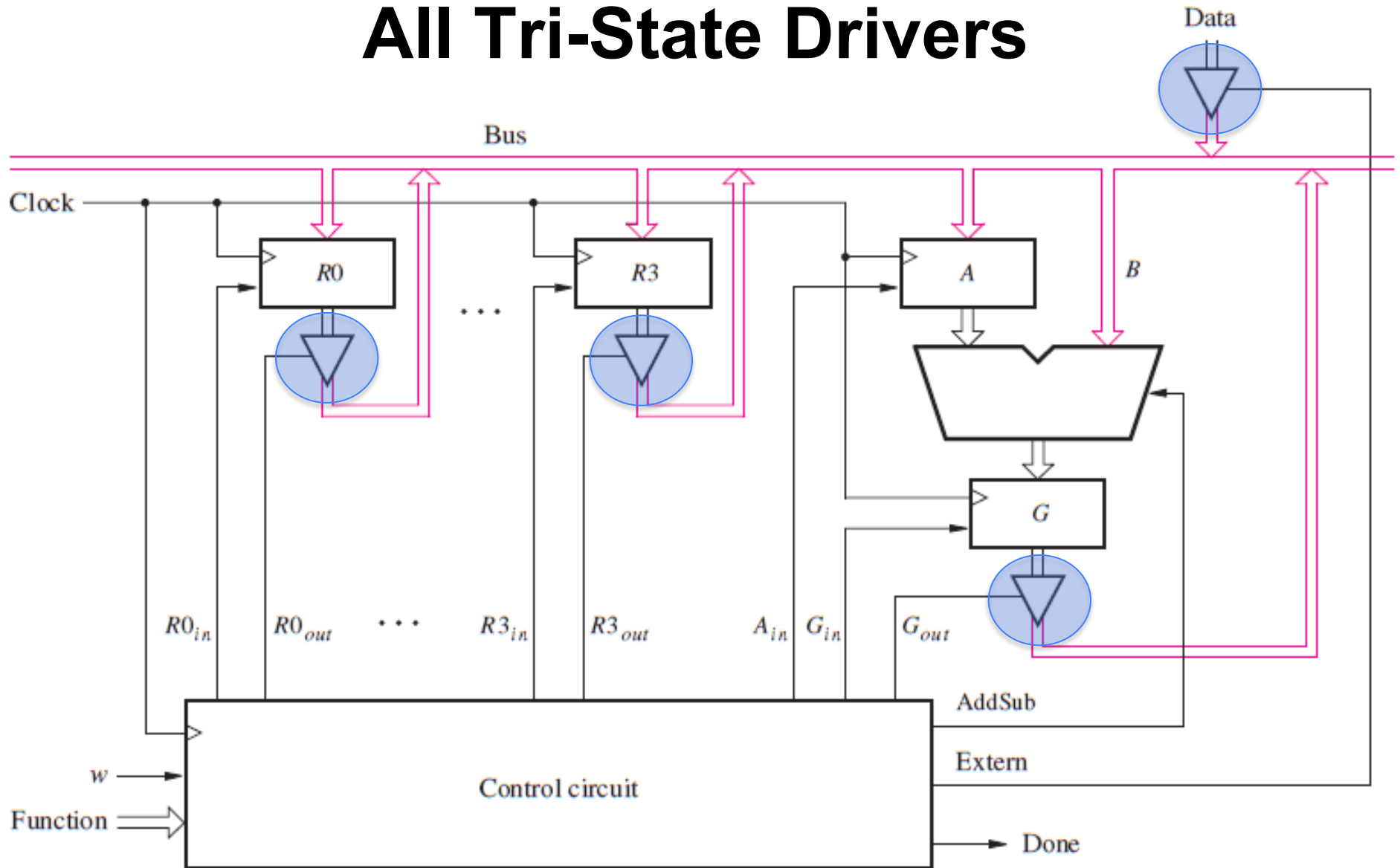


[ Figure 7.9 from the textbook ]

# Tri-state driver

(see Appendix B for more details)

 

(a) Symbol

 

(b) Equivalent circuit

Z: High impedance state


$e$	$w$	$f$
0	0	Z
0	1	Z
1	0	0
1	1	1

(c) Truth table
 
# Tri-state driver


(see Appendix B for more details)

- **Alternative way to implement a data bus**
- **Allows several devices to be connected to a single wire (this is not possible with regular logic gates because their outputs are always active; an OR gate is needed)**
- **Note that at any time, at most one of e0, e1, e2, and e3 can be set to 1**



 
# An n-bit Tri-State Driver


can be constructed using n 1-bit tri-state buffers



# 2-Bit Register

 

 
# How to connect two 2-bit registers to a bus (using tri-state drivers)



This shows only two 2-bit registers, but this design scales to more and larger registers.

# Moving the Contents of R1 to R2

 


Register 1 stores the number  $2_{10} = 10_2$

Register 2 stores the number  $1_{10} = 01_2$




# Moving the Contents of R1 to R2

 


Initially all control inputs are set to 0 (no reading or writing allowed).

# Moving the Contents of R1 to R2

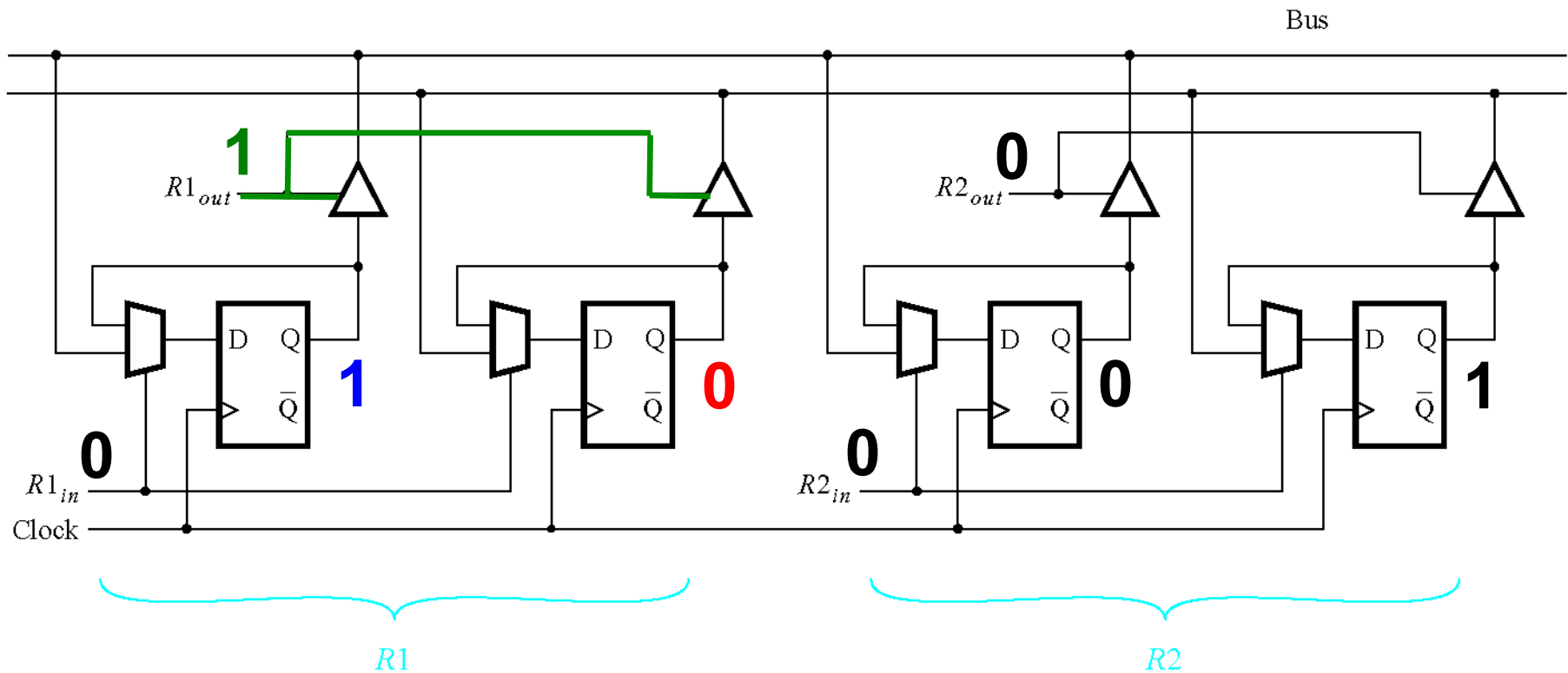


**$R1_{out}$  is set to 1 (this enables reading from register 1).**

# Moving the Contents of R1 to R2

 


The bits of R1 are now on the data bus (2-bit data bus in this case).

# Moving the Contents of R1 to R2

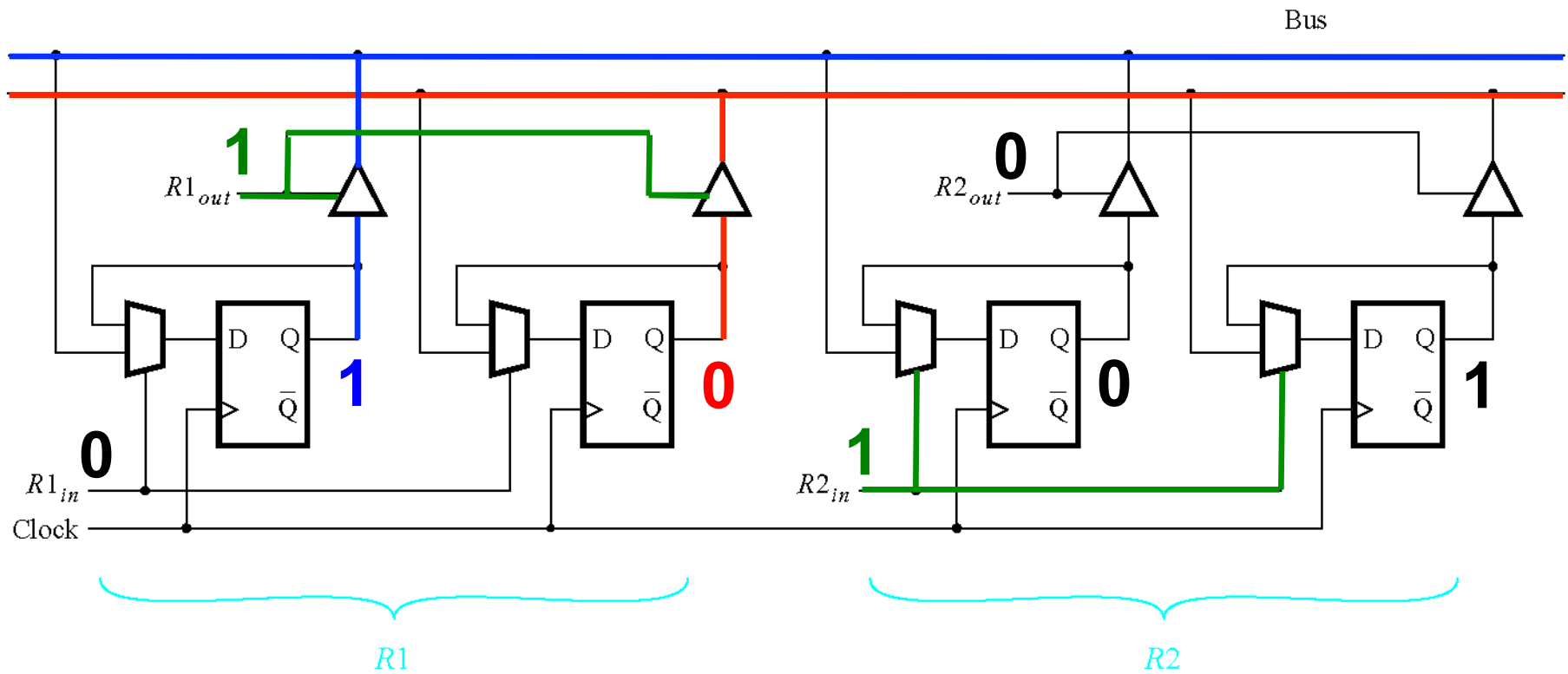


**R2<sub>in</sub> is set to 1 (this enables writing to register 2).**

# Moving the Contents of R1 to R2

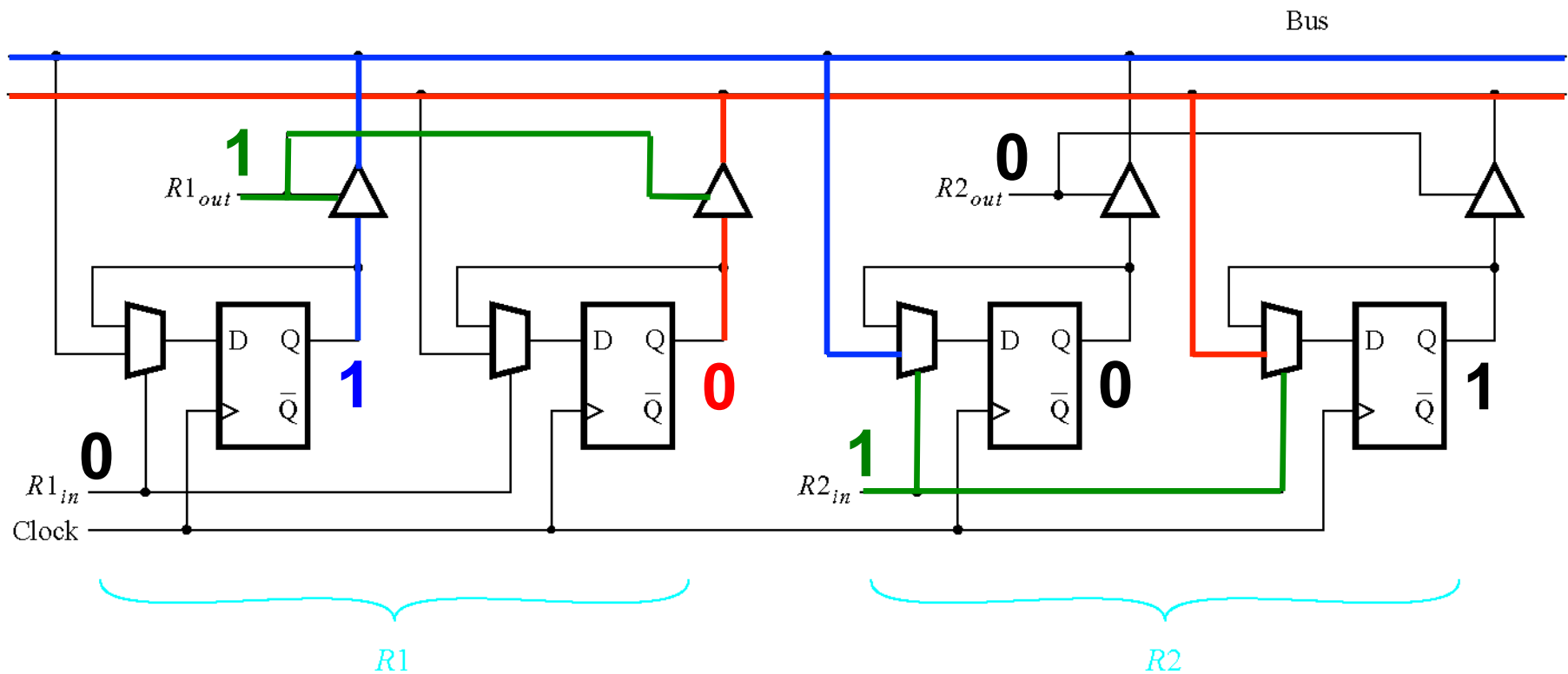


The bits of R1 are still on the bus and they propagate to the multiplexers...

# Moving the Contents of R1 to R2

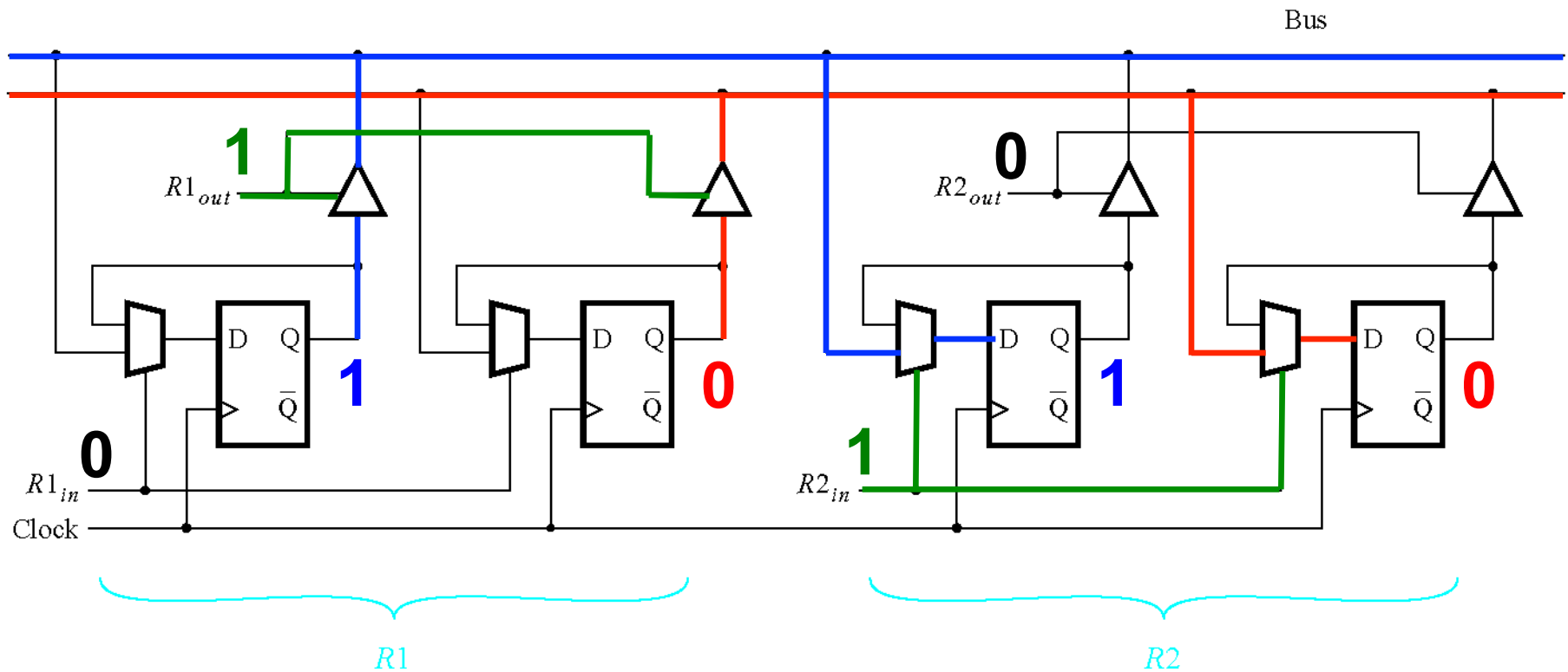


... and on the next positive clock edge to the outputs of the flip-flops of R2.

# Moving the Contents of R1 to R2

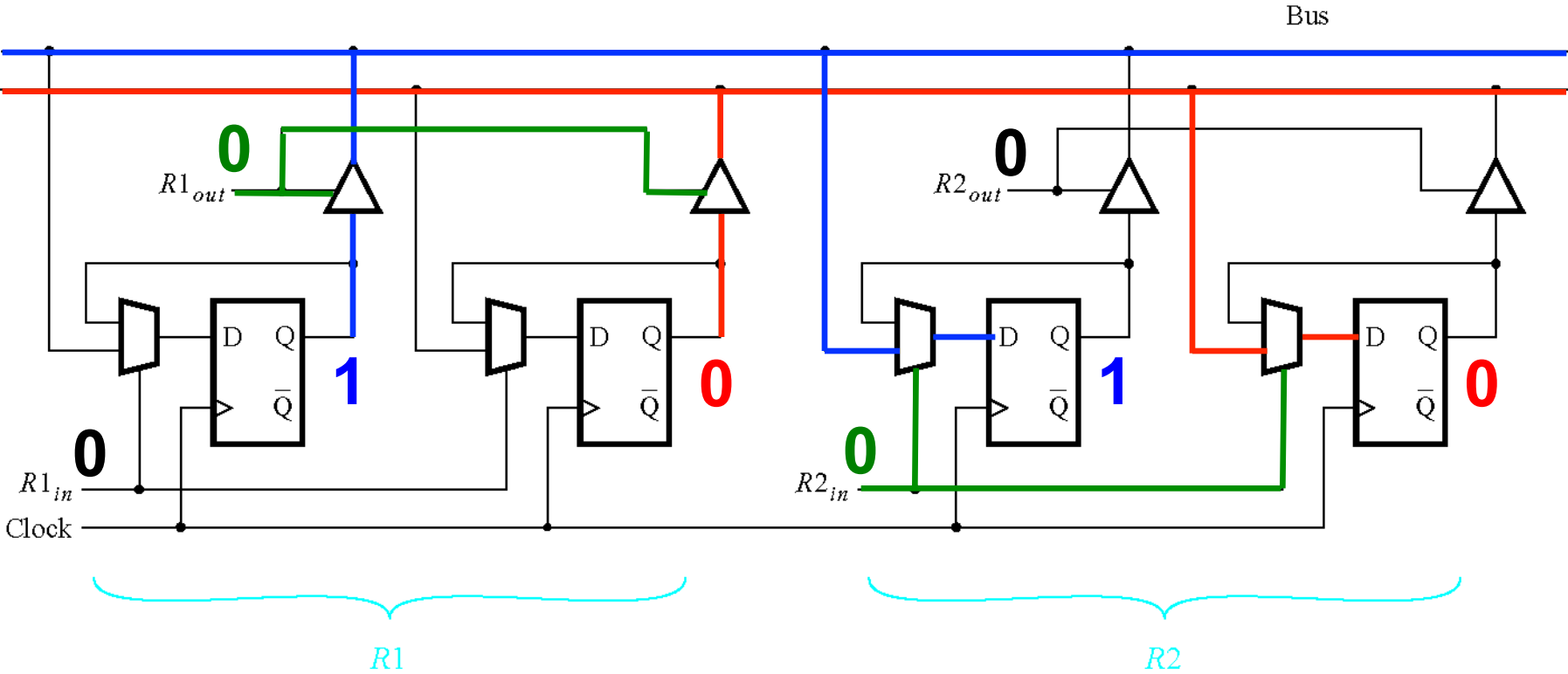

After the copy is complete  $R1_{out}$  and  $R2_{in}$  are set to 0.


# Moving the Contents of R1 to R2

 

All control inputs are now disabled (no reading or writing is allowed).




# Moving the Contents of R1 to R2

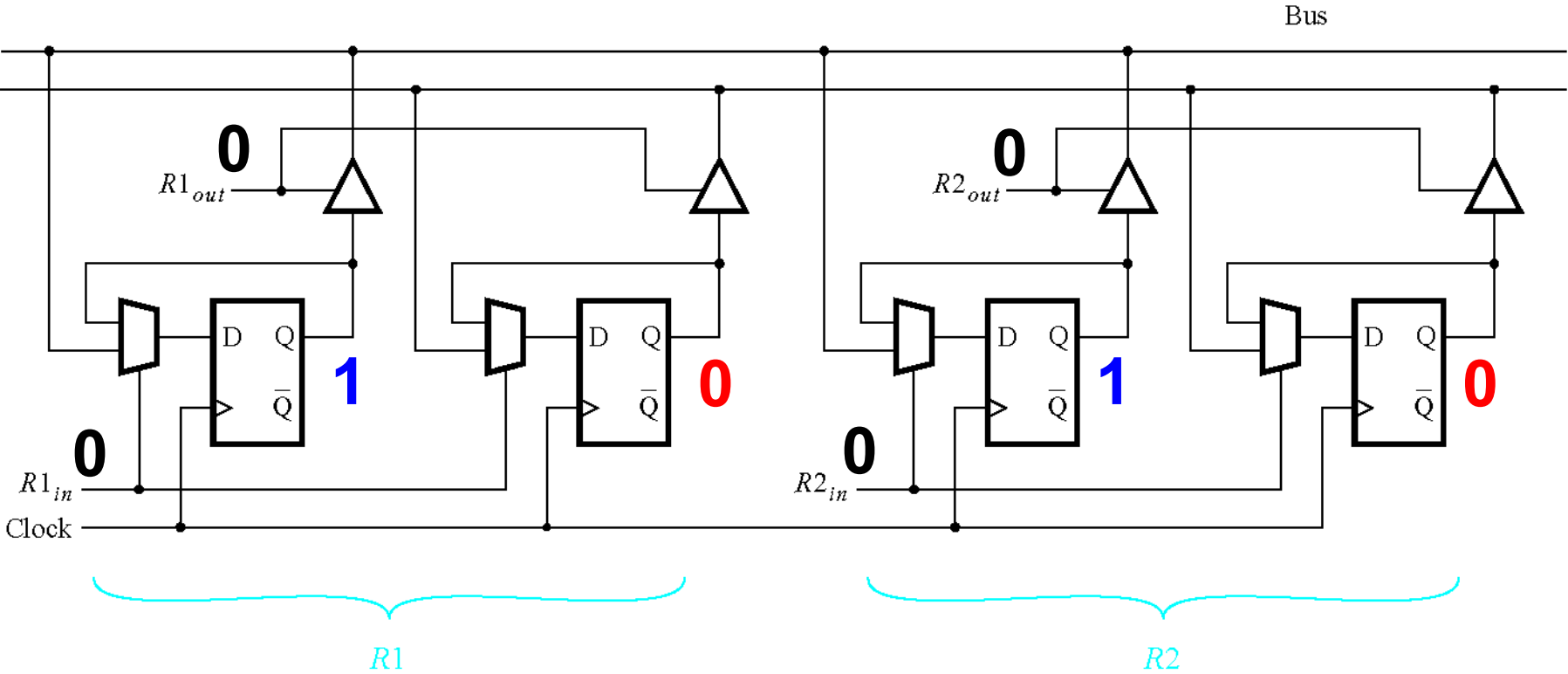

Register 2 now holds the same value as register 1.


# **Another Example**

# Loading Data From The Bus Into R2

 


Initially all control inputs are set to 0 (no reading or writing allowed).

# Loading Data From The Bus Into R2

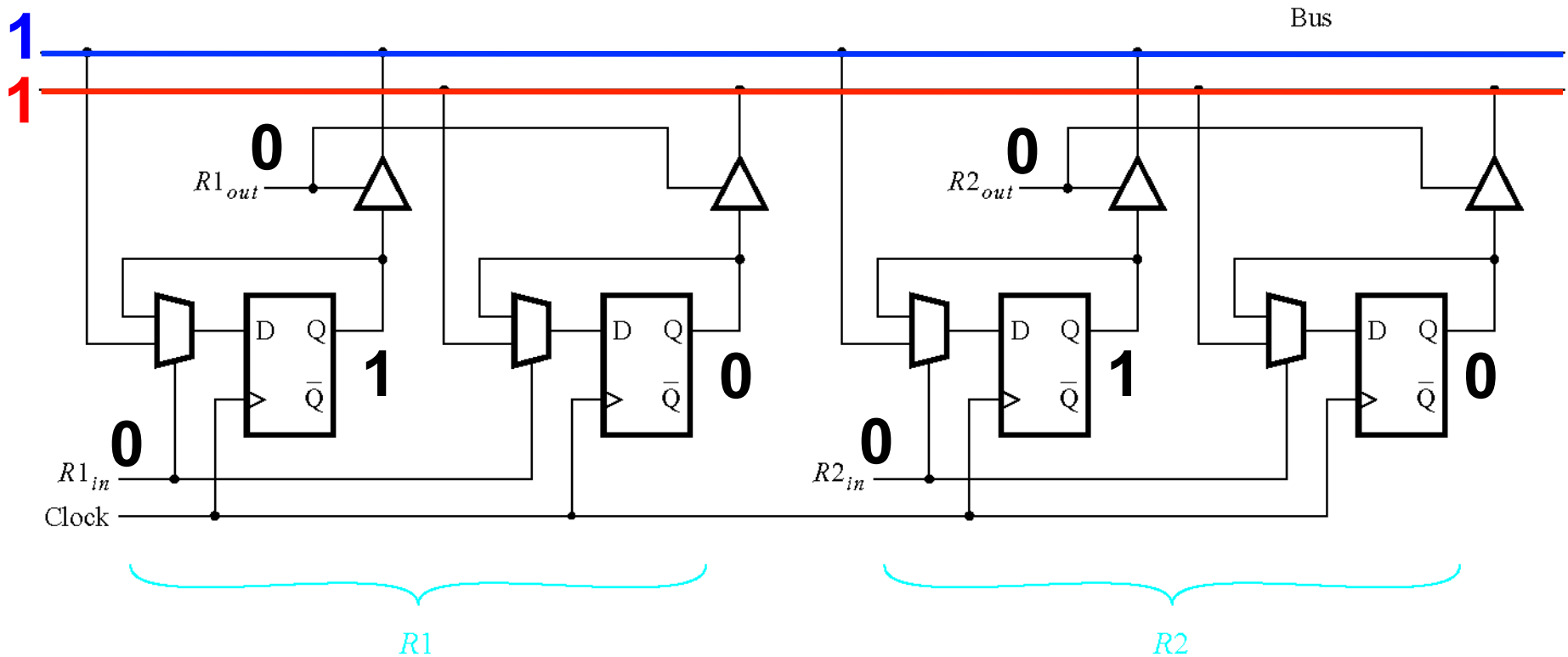


The number  $3_{10} = 11_2$  is placed on the 2-bit data bus.

# Loading Data From The Bus Into R2

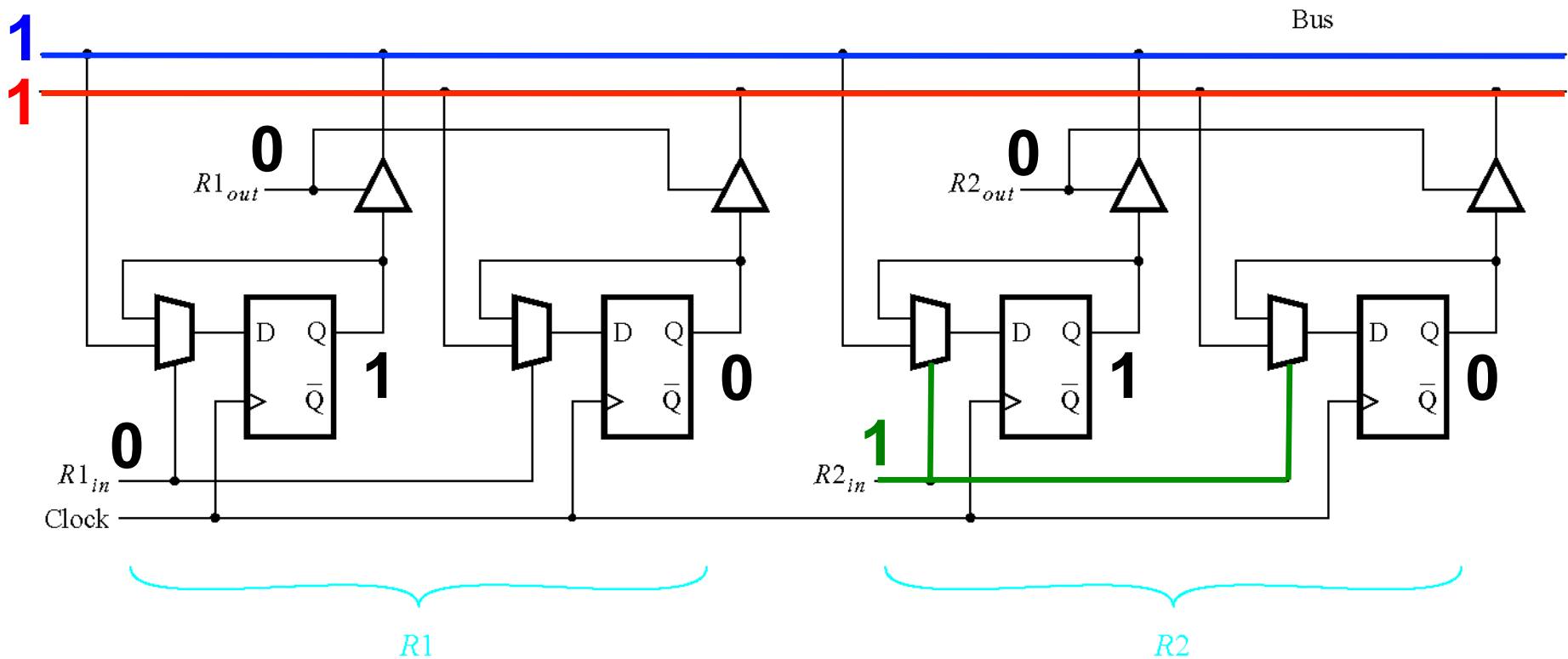


**$R2_{in}$  is set to 1 (this enables writing to register 2).**

# Loading Data From The Bus Into R2

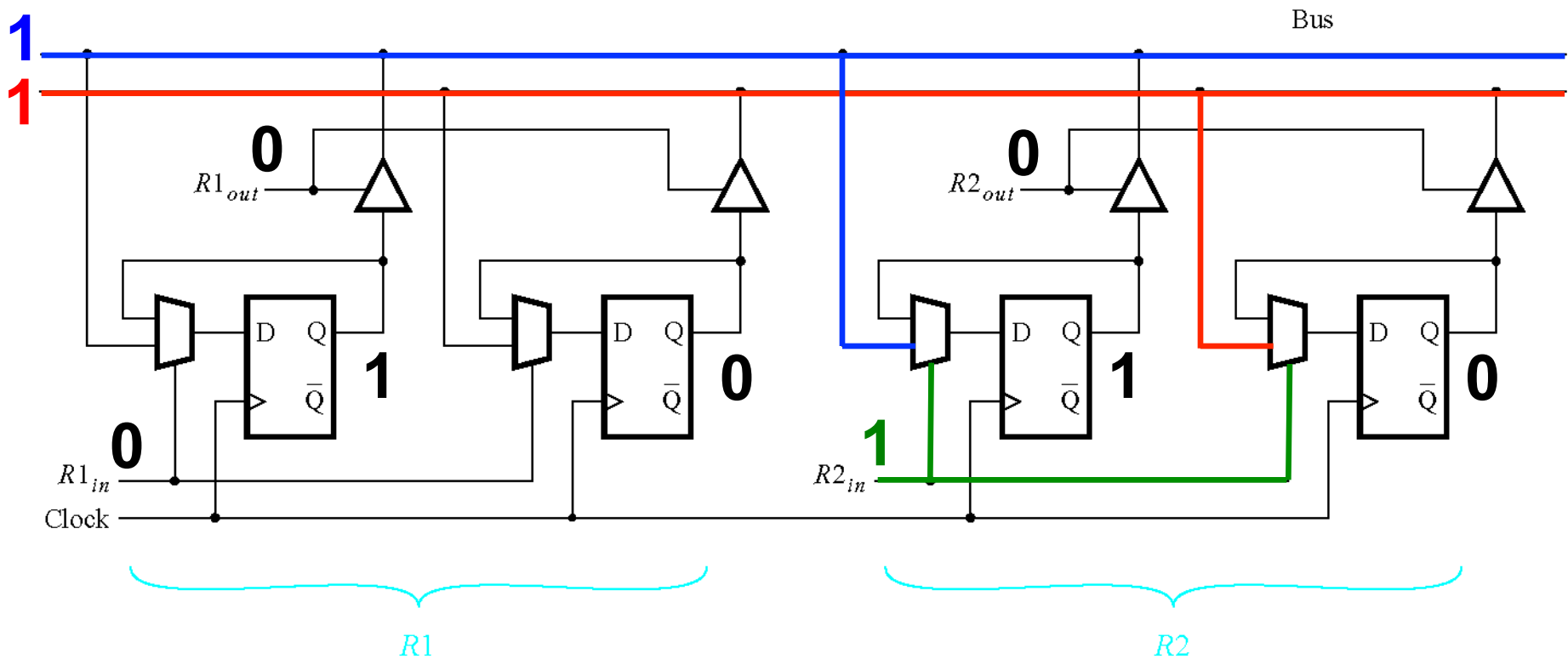


The bits of the data propagate through the multiplexers...

# Loading Data From The Bus Into R2

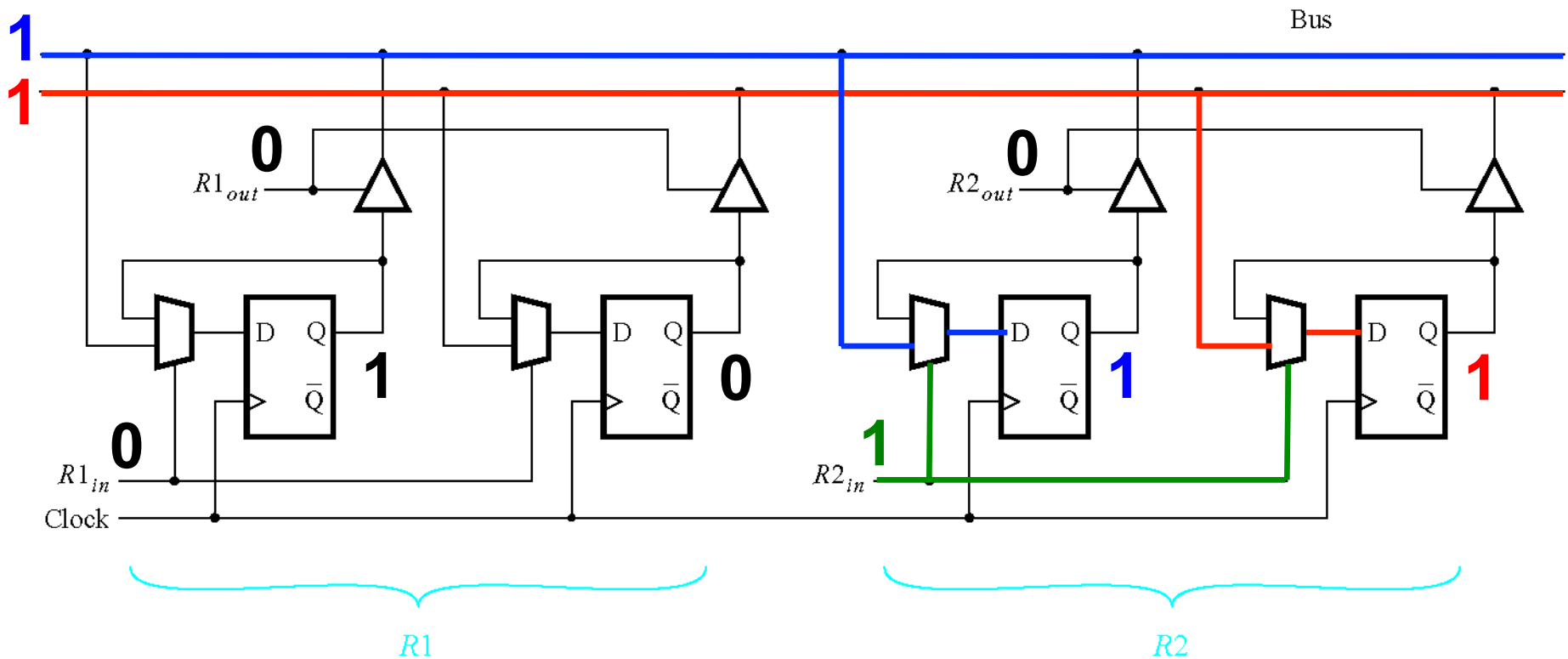

... and on the next positive clock edge to the outputs of the flip-flops of R2.


# Loading Data From The Bus Into R2

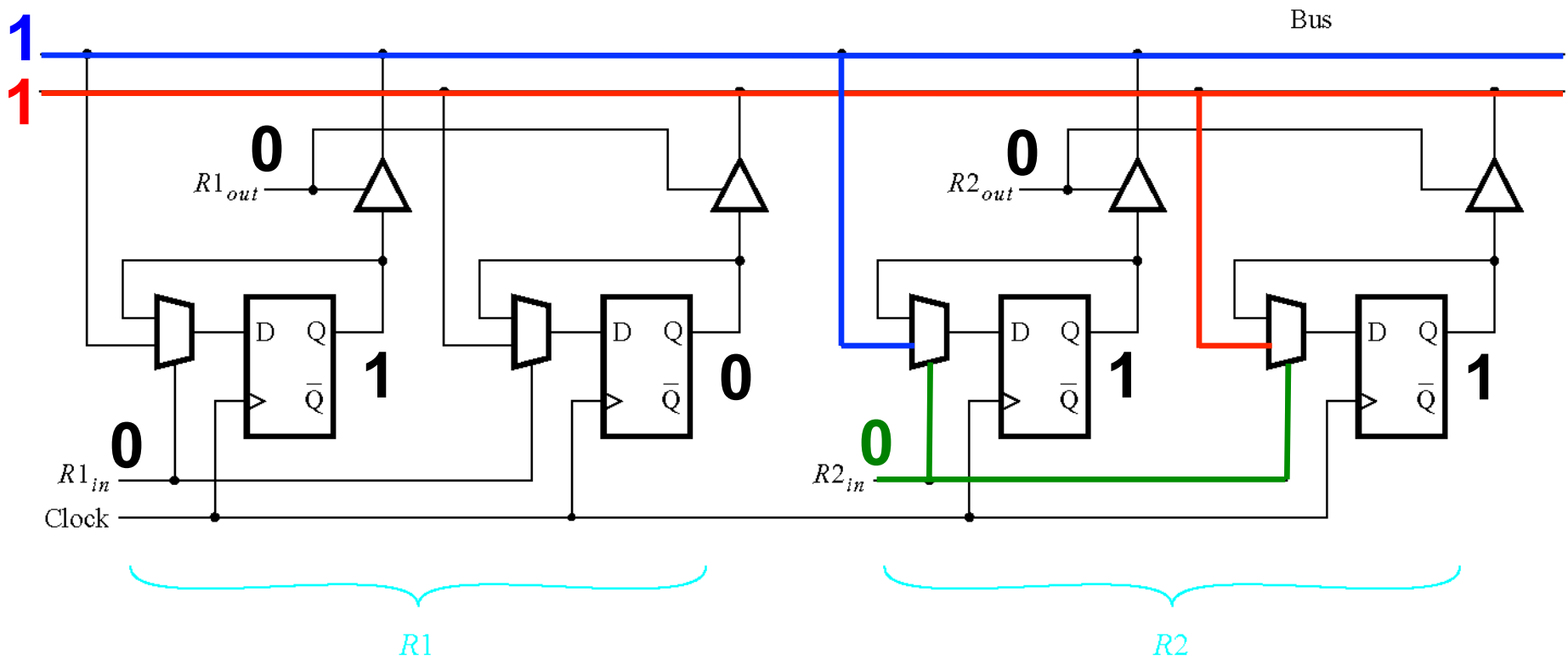

After the loading is complete R2<sub>in</sub> is set to 0.




# Loading Data From The Bus Into R2

 

Register 2 now stores the number  $3_{10} = 11_2$ .


# **A Closer Look at the Arithmetic Logic Unit (ALU)**

# Arithmetic Logic Unit (ALU)

 


[ Figure 7.9 from the textbook ]

# Two Registers

 


[ Figure 7.9 from the textbook ]

# 4-Bit Register

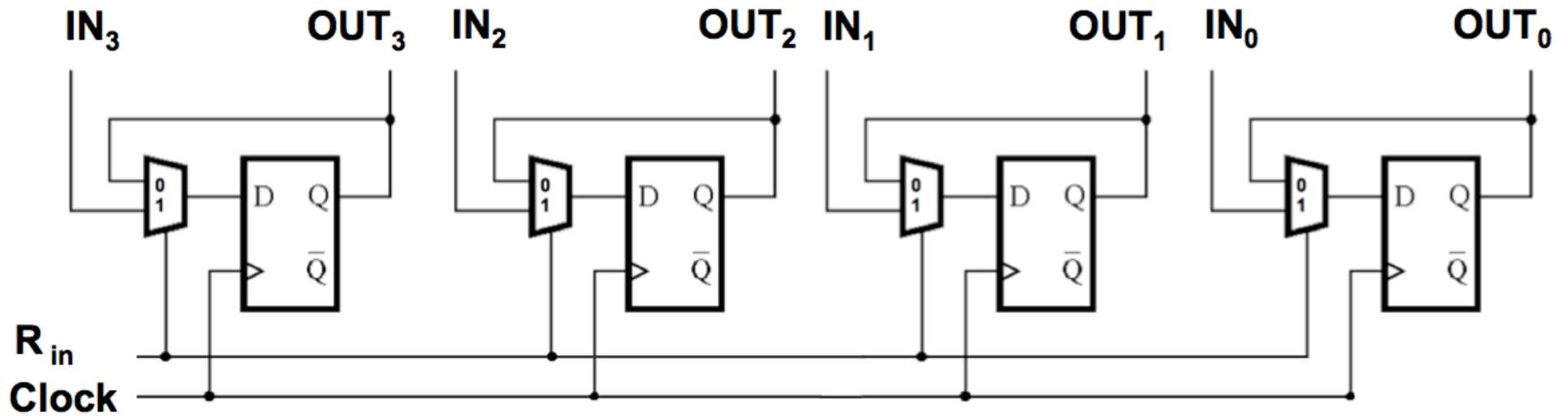


# Adder/Subtractor

 


[ Figure 7.9 from the textbook ]

# Adder/Subtractor unit

 

[ Figure 3.12 from the textbook ]
 
# The first two stages of a carry-lookahead adder




$$c_1 = g_0 + p_0 c_0$$

$$c_2 = g_1 + p_1 g_0 + p_1 p_0 c_0$$

[ Figure 3.15 from the textbook ]



# A hierarchical carry-lookahead adder

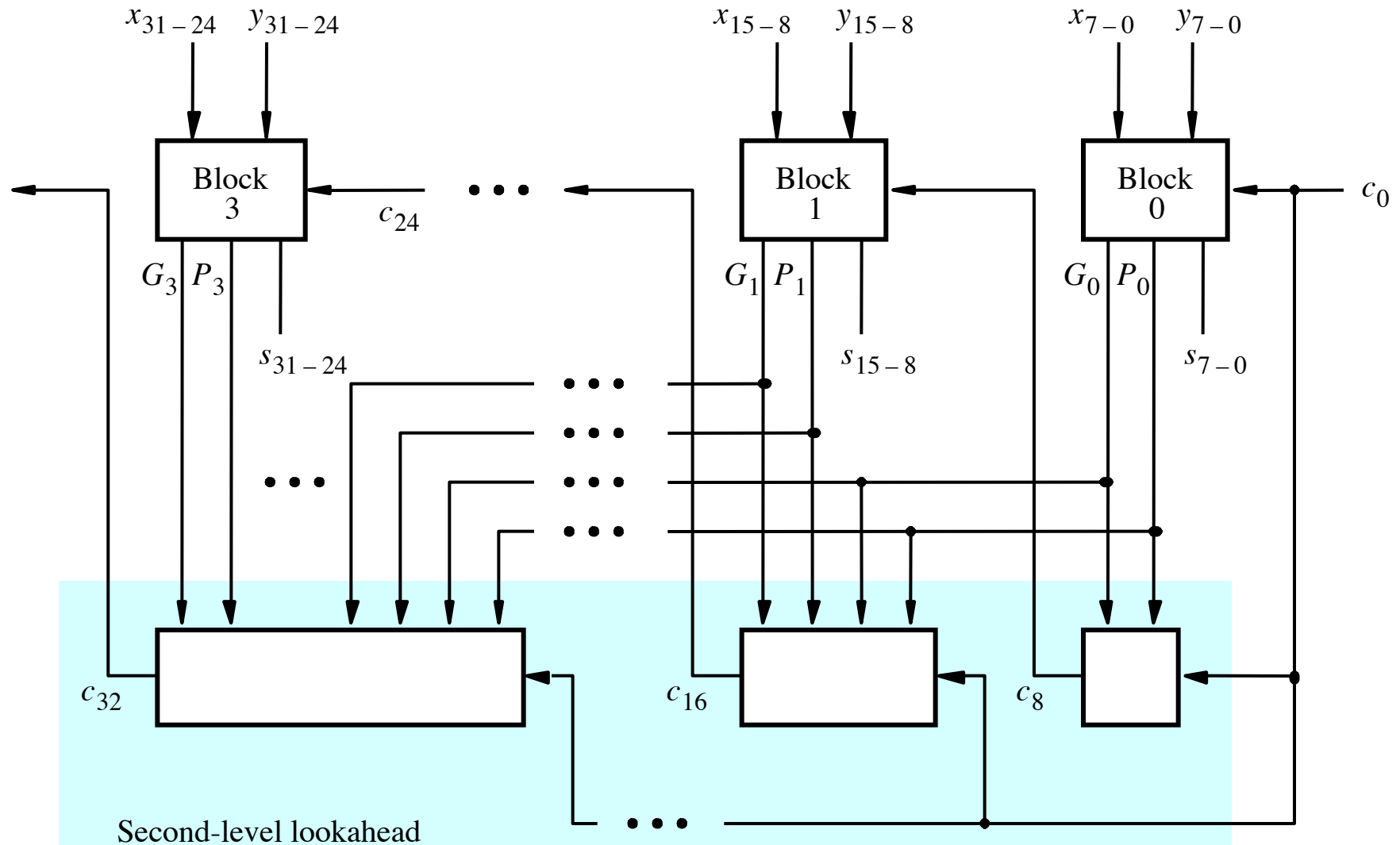


[ Figure 3.17 from the textbook ]

# **Adder/subtractor unit**

- **Subtraction can be performed by simply adding the 2's complement of the second number, regardless of the signs of the two numbers.**
- **Thus, the same adder circuit can be used to perform both addition and subtraction !!!**


# Adder/subtractor unit

 

[ Figure 3.12 from the textbook ]


# XOR Tricks

control	$y$	out
0	0	0
0	1	1
1	0	1
1	1	0

 


# XOR as a repeater

control	$y$	out
0	0	0
0	1	1
1	0	1
1	1	0

 


# XOR as an inverter

control	$y$	out
0	0	0
0	1	1
1	0	1
1	1	0

 


# Addition: when control = 0

 

[ Figure 3.12 from the textbook ]


# Addition: when control = 0

 

[ Figure 3.12 from the textbook ]




# Addition: when control = 0

 


[ Figure 3.12 from the textbook ]

# Subtraction: when control = 1

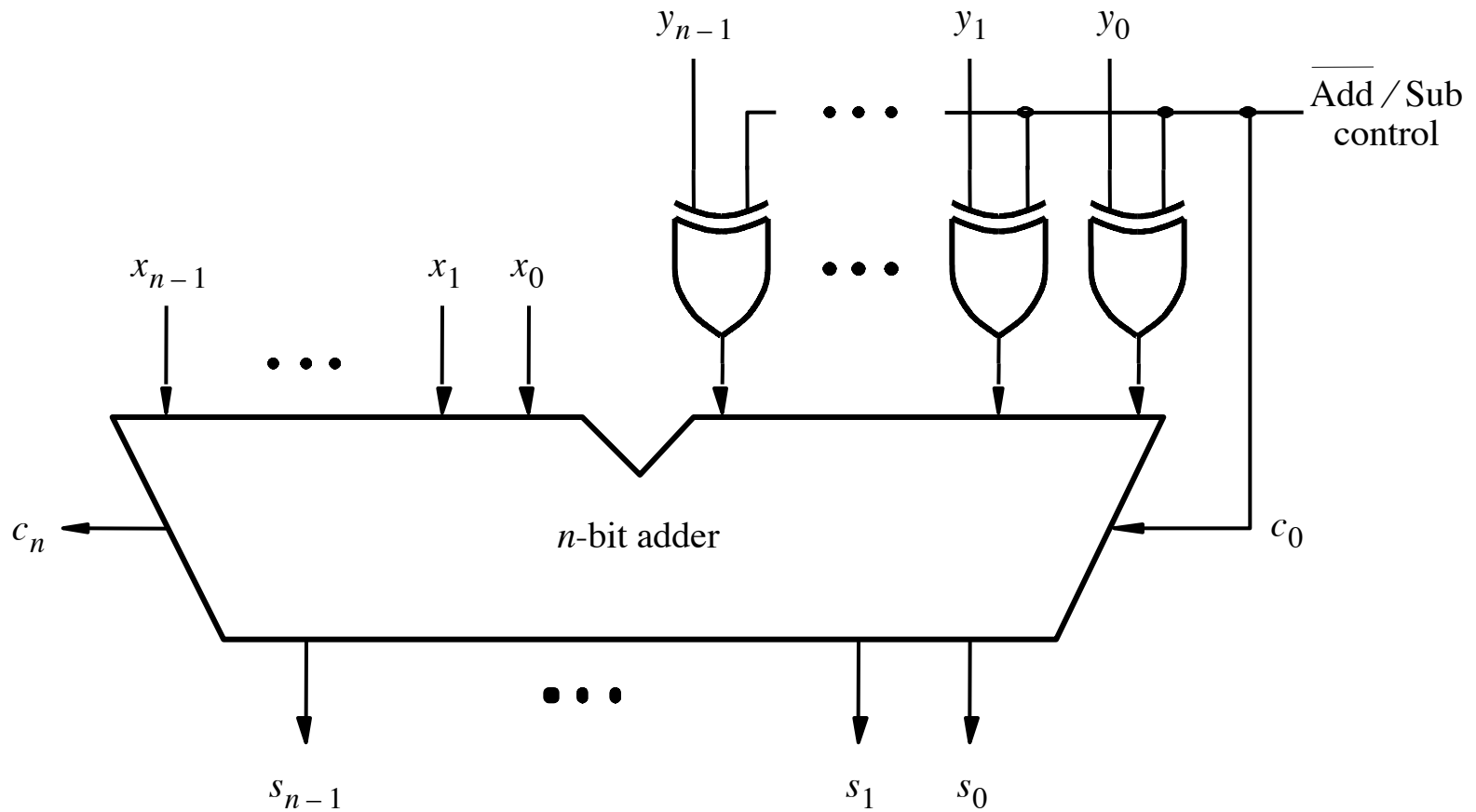


[ Figure 3.12 from the textbook ]

# Subtraction: when control = 1

 


[ Figure 3.12 from the textbook ]

# Subtraction: when control = 1

 

[ Figure 3.12 from the textbook ]


# Subtraction: when control = 1

 

[ Figure 3.12 from the textbook ]


# **A Closer Look at the Control Circuit**

# Control Circuit

 

[ Figure 7.9 from the textbook ]

# Control Signals

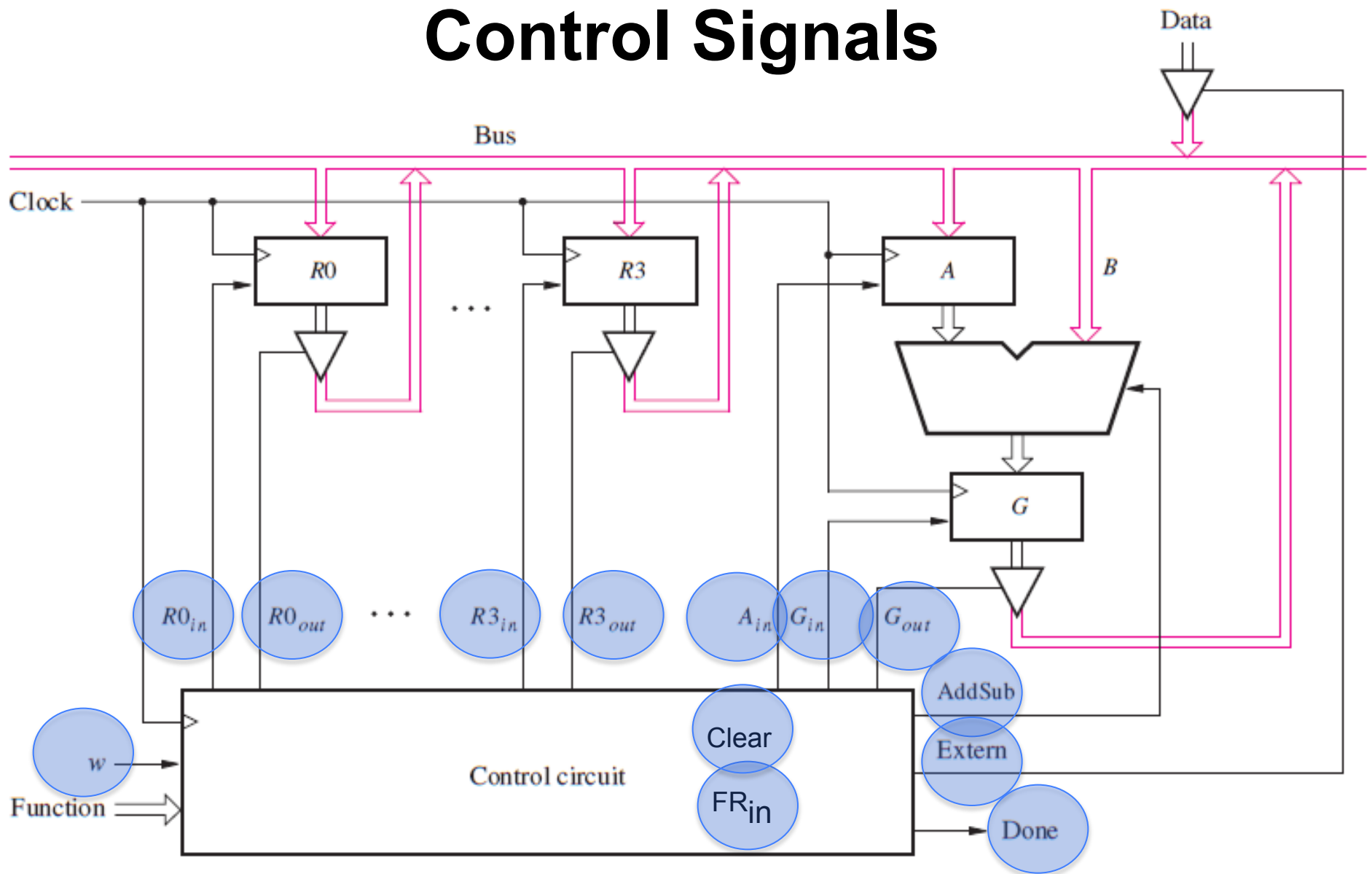

[ Figure 7.9 from the textbook ]



# Design a FSM with input w and outputs


- $R0_{in}$
- $R0_{out}$
- $R1_{in}$
- $R1_{out}$
- $R2_{in}$
- $R2_{out}$
- $R3_{in}$
- $R3_{out}$
- $A_{in}$
- $G_{in}$
- $G_{out}$
- Clear
- $FR_{in}$
- AddSub
- Extern
- Done

# Design a FSM with input w and outputs

- $R0_{in}$
- $R0_{out}$
- $R1_{in}$
- $R1_{out}$
- $R2_{in}$
- $R2_{out}$
- $R3_{in}$
- $R3_{out}$
- $A_{in}$
- $G_{in}$
- $G_{out}$
- **Clear**
- $FR_{in}$
- **AddSub**
- **Extern**
- **Done**
- $T_0$
- $T_1$
- $T_2$
- $T_3$
- $I_0$
- $I_1$
- $I_2$
- $I_3$
- $X_0$
- $X_1$
- $X_2$
- $X_3$
- $Y_0$
- $Y_1$
- $Y_2$
- $Y_3$


These are helper outputs that are one-hot encoded. They are used to simplify the expressions for the other outputs.

# The function register and decoders

 

[ Figure 7.11 from the textbook ]

# The function register and decoders

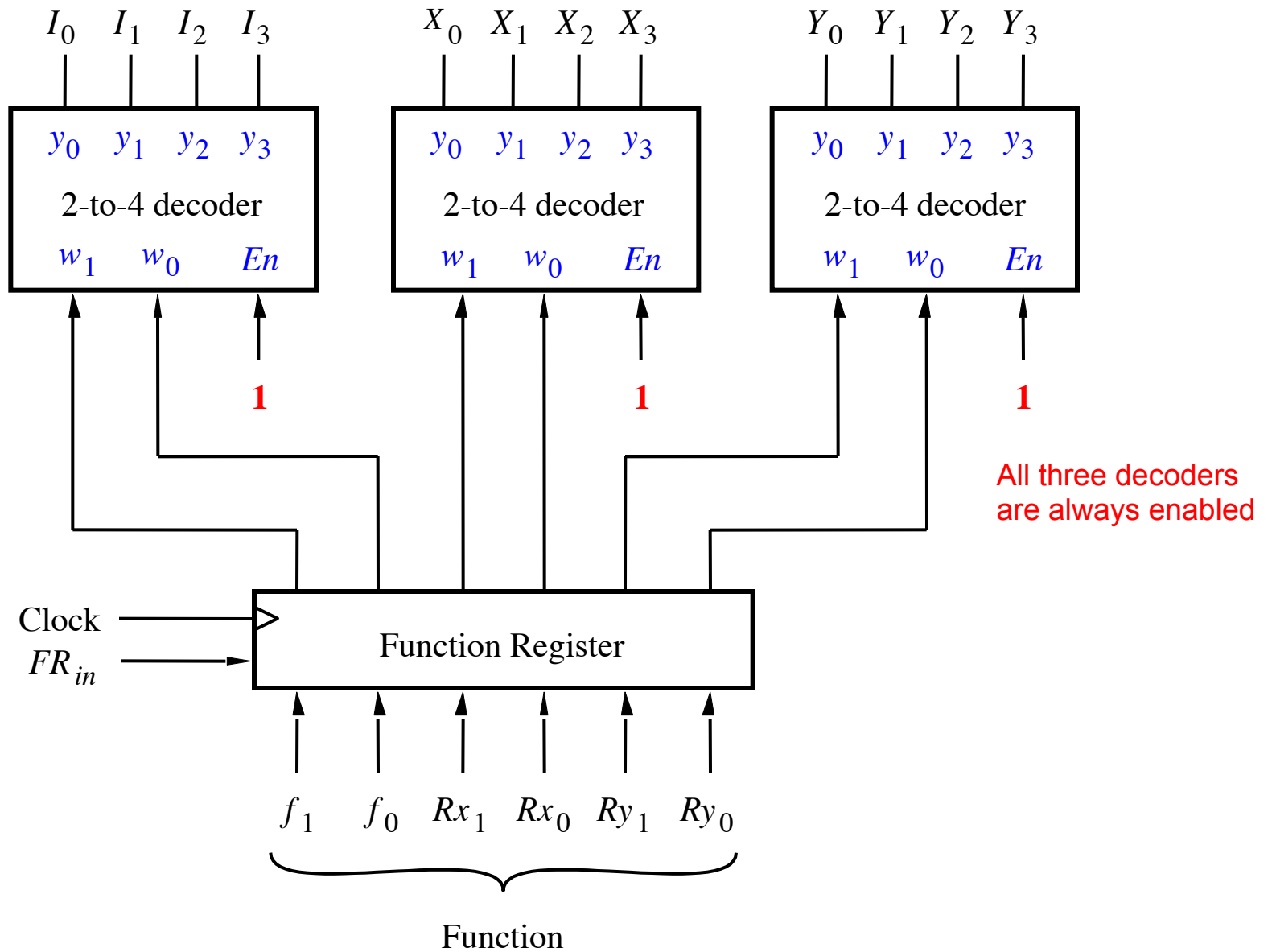

[ Figure 7.11 from the textbook ]

# Operations performed by this processor


Operation	Function Performed
<b>Load</b> Rx, Data	Rx ← Data
<b>Move</b> Rx, Ry	Rx ← [Ry]
<b>Add</b> Rx, Ry	Rx ← [Rx] + [Ry]
<b>Sub</b> Rx, Ry	Rx ← [Rx] - [Ry]

# Operations performed by this processor

Operation	Function Performed
<b>Load</b> Rx, Data	Rx ← Data
<b>Move</b> Rx, Ry	Rx ← [Ry]
<b>Add</b> Rx, Ry	Rx ← [Rx] + [Ry]
<b>Sub</b> Rx, Ry	Rx ← [Rx] - [Ry]

Where Rx and Ry can be one of four possible options: R0, R1, R2, and R3

# Operations performed by this processor

 


$f_1$	$f_0$	Function
0	0	Load
0	1	Move
1	0	Add
1	1	Sub

$Rx_1$	$Rx_0$	Register
0	0	R0
0	1	R1
1	0	R2
1	1	R3

$Ry_1$	$Ry_0$	Register
0	0	R0
0	1	R1
1	0	R2
1	1	R3

# Operations performed by this processor

 


$f_1$	$f_0$	Function
0	0	Load
<b>0</b>	<b>1</b>	<b>Move</b>
1	0	Add
1	1	Sub

$Rx_1$	$Rx_0$	Register
0	0	R0
0	1	R1
1	0	R2
<b>1</b>	<b>1</b>	<b>R3</b>


$Ry_1$	$Ry_0$	Register
<b>0</b>	<b>0</b>	<b>R0</b>
0	1	R1
1	0	R2
1	1	R3




# The function register and decoders

 


# The function register and decoders

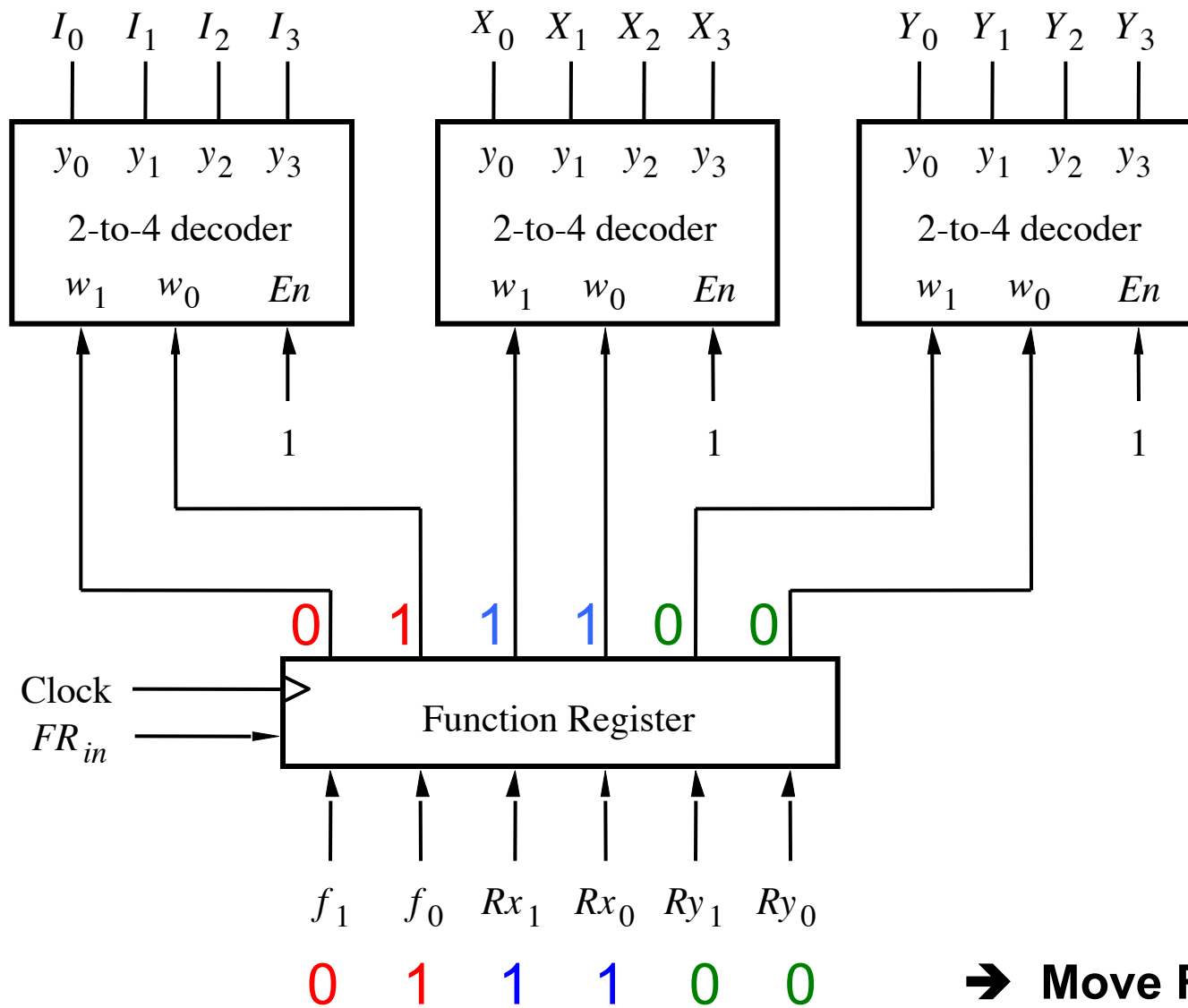


# The function register and decoders

 


# The function register and decoders

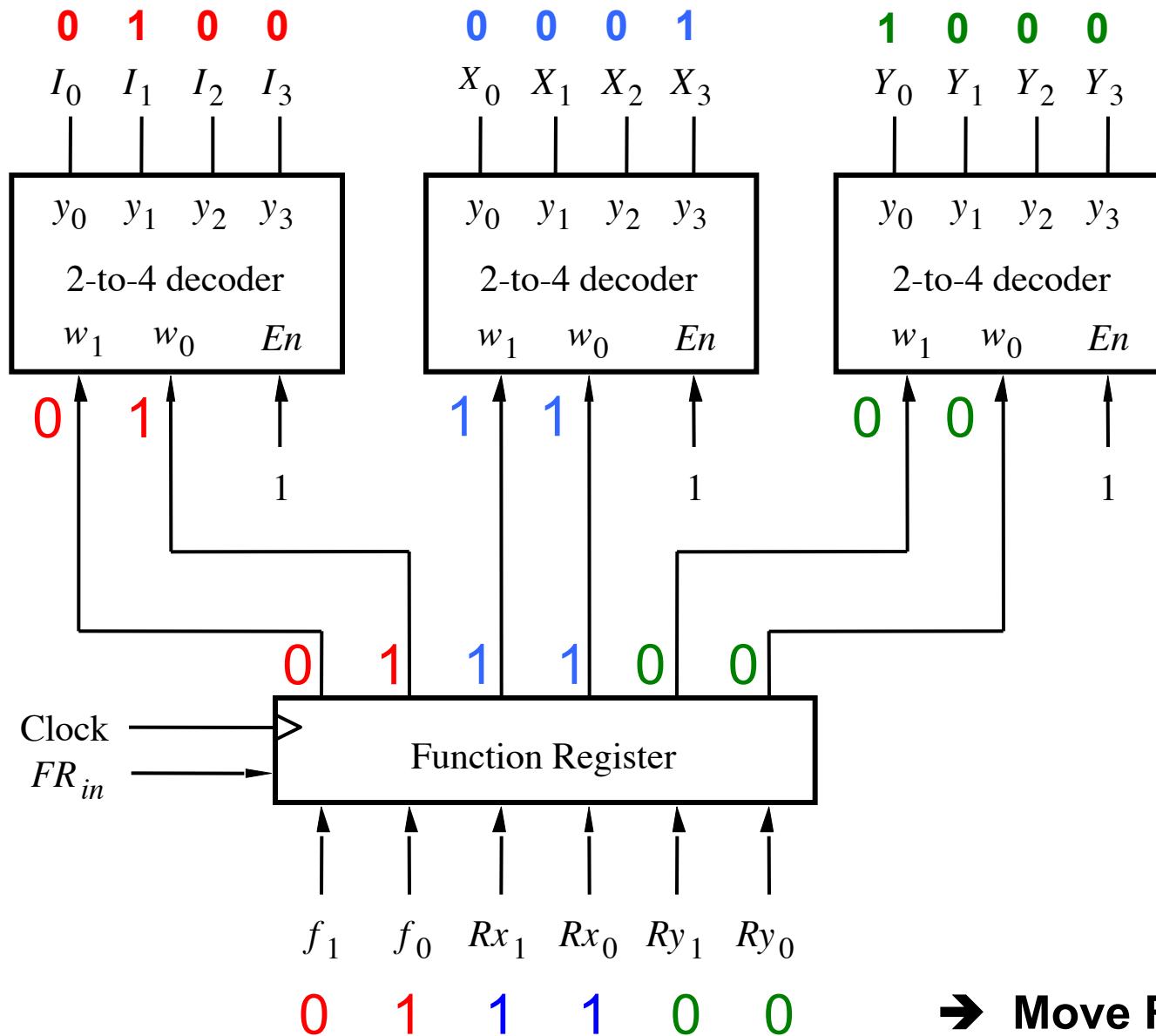

# The function register and decoders

 

# Operations performed by this processor

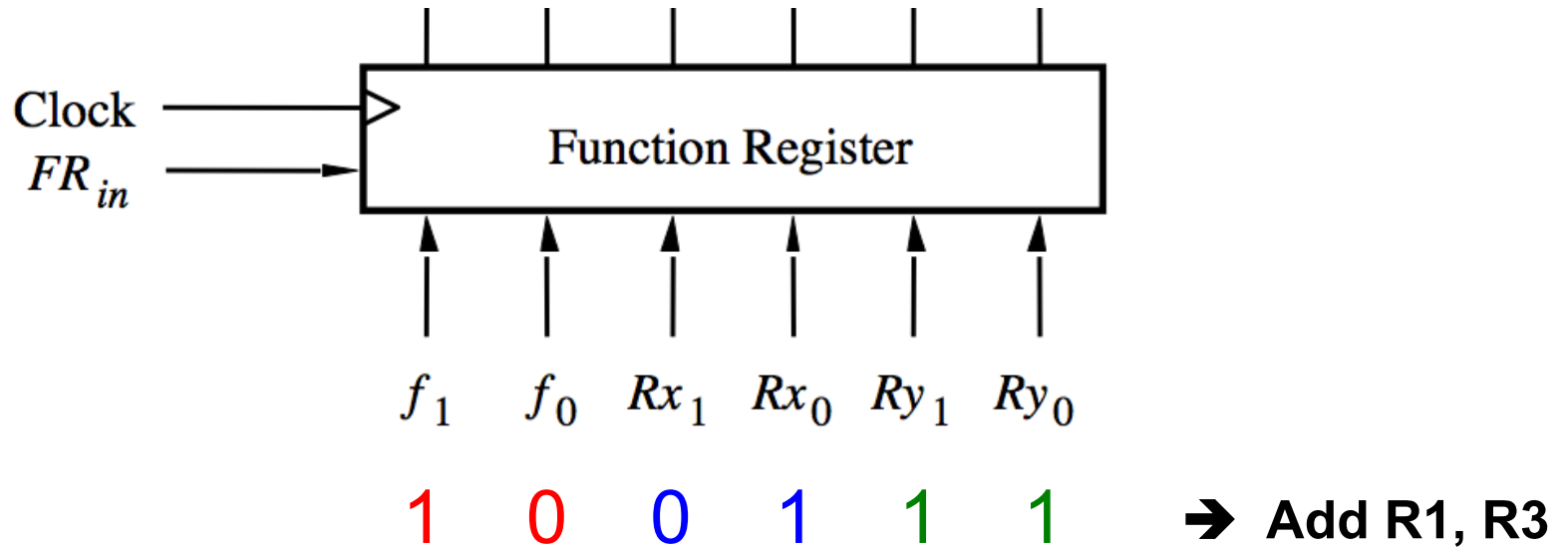


$f_1$	$f_0$	Function
0	0	Load
0	1	Move
1	0	Add
1	1	Sub

$Rx_1$	$Rx_0$	Register
0	0	R0
0	1	R1
1	0	R2
1	1	R3

$Ry_1$	$Ry_0$	Register
0	0	R0
0	1	R1
1	0	R2
1	1	R3

# Operations performed by this processor

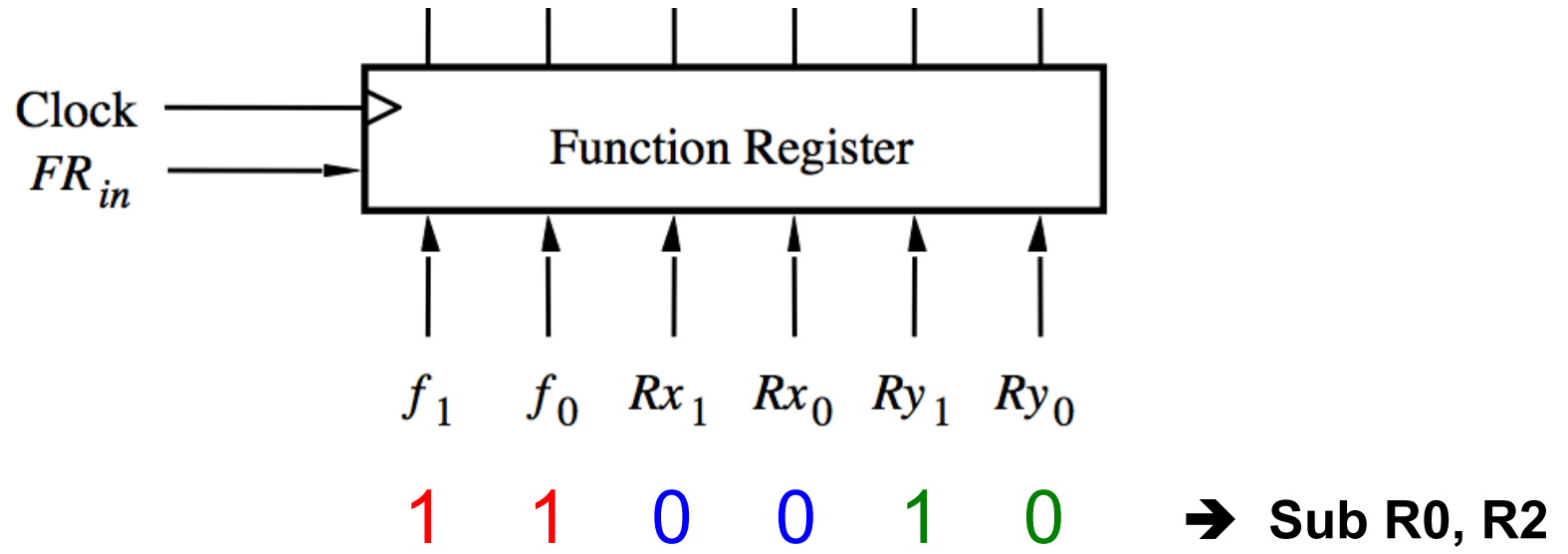


$f_1$	$f_0$	Function
0	0	Load
0	1	Move
1	0	Add
1	1	Sub

$Rx_1$	$Rx_0$	Register
0	0	R0
0	1	R1
1	0	R2
1	1	R3

$Ry_1$	$Ry_0$	Register
0	0	R0
0	1	R1
1	0	R2
1	1	R3

# Operations performed by this processor

 

0 0 1 0 X X → Load R2, Data

$f_1$	$f_0$	Function
0	0	Load
0	1	Move
1	0	Add
1	1	Sub


$Rx_1$	$Rx_0$	Register
0	0	R0
0	1	R1
1	0	R2
1	1	R3

$Ry_1$	$Ry_0$	Register
0	0	R0
0	1	R1
1	0	R2
1	1	R3



# Similar Encoding is Used by Modern Chips

## MIPS32 Add Immediate Instruction

 

Equivalent mnemonic:

**addi** \$r1, \$r2, 350

# Sample Assembly Language Program For This Processor

```
Move   R3, R0
Add    R1, R3
Sub    R0, R2
Load  R2, Data
```

# Machine Language vs Assembly Language

Machine Language	Assembly Language	Meaning / Interpretation
011100	Move R3, R0	R3 ← [R0]
100111	Add R1, R3	R1 ← [R1] + [R3]
110010	Sub R0, R2	R0 ← [R0] - [R2]
001000	Load R2, Data	R2 ← Data

# Machine Language vs Assembly Language

Machine Language	Assembly Language	Meaning / Interpretation
011100	Move R3, R0	R3 ← [R0]
100111	Add R1, R3	R1 ← [R1] + [R3]
110010	Sub R0, R2	R0 ← [R0] - [R2]
001000	Load R2, Data	R2 ← Data

# Machine Language vs Assembly Language

Machine Language	Assembly Language	Meaning / Interpretation
011100	Move R3, R0	R3 ← [R0]
100111	Add R1, R3	R1 ← [R1] + [R3]
110010	Sub R0, R2	R0 ← [R0] - [R2]
001000	Load R2, Data	R2 ← Data

For short, each line  
can be expressed as a  
hexadecimal number

# Machine Language vs Assembly Language

Machine Language	Assembly Language	Meaning / Interpretation
1C	Move R3, R0	R3 ← [R0]
27	Add R1, R3	R1 ← [R1] + [R3]
32	Sub R0, R2	R0 ← [R0] - [R2]
08	Load R2, Data	R2 ← Data

# Intel 8086

```
; _memcpy(dst, src, len)
; Copy a block of memory from one location to another.
;
; Entry stack parameters
;     [BP+6] = len, Number of bytes to copy
;     [BP+4] = src, Address of source data block
;     [BP+2] = dst, Address of target data block
;
; Return registers
;     AX = Zero
```

```
0000:1000                org     1000h        ; Start at 0000:1000h

0000:1000                _memcpy  proc
0000:1000 55              push    bp          ; Set up the call frame
0000:1001 89 E5            mov     bp,sp
0000:1003 06              push    es          ; Save ES
0000:1004 8B 4E 06        mov     cx,[bp+6]   ; Set CX = len
0000:1007 E3 11          jcxz   done         ; If len=0, return
0000:1009 8B 76 04        mov     si,[bp+4]   ; Set SI = src
0000:100C 8B 7E 02        mov     di,[bp+2]   ; Set DI = dst
0000:100F 1E            push    ds          ; Set ES = DS
0000:1010 07            pop     es

0000:1011 8A 04          loop   mov     al,[si] ; Load AL from [src]
0000:1013 88 05          mov     [di],al    ; Store AL to [dst]
0000:1015 46            inc     si          ; Increment src
0000:1016 47            inc     di          ; Increment dst
0000:1017 49            dec     cx          ; Decrement len
0000:1018 75 F7          jnz    loop        ; Repeat the loop

0000:101A 07          done  pop     es          ; Restore ES
0000:101B 5D          pop     bp          ; Restore previous call frame
0000:101C 29 C0        sub     ax,ax       ; Set AX = 0
0000:101E C3          ret                ; Return
0000:101F                end proc
```

# Intel 8086

## Memory Address

```
0000:1000                                org      1000h      ; Start at 0000:1000h

0000:1000                                _memcpy  proc
0000:1000 55                                push    bp        ; Set up the call frame
0000:1001 89 E5                            mov     bp,sp
0000:1003 06                                push    es        ; Save ES
0000:1004 8B 4E 06                            mov     cx,[bp+6] ; Set CX = len
0000:1007 E3 11                                jcxz   done      ; If len=0, return
0000:1009 8B 76 04                            mov     si,[bp+4] ; Set SI = src
0000:100C 8B 7E 02                            mov     di,[bp+2] ; Set DI = dst
0000:100F 1E                                push    ds        ; Set ES = DS
0000:1010 07                                pop     es

0000:1011 8A 04                                loop   mov     al,[si] ; Load AL from [src]
0000:1013 88 05                                mov     [di],al   ; Store AL to [dst]
0000:1015 46                                inc     si        ; Increment src
0000:1016 47                                inc     di        ; Increment dst
0000:1017 49                                dec     cx        ; Decrement len
0000:1018 75 F7                                jnz    loop      ; Repeat the loop

0000:101A 07                                done   pop     es        ; Restore ES
0000:101B 5D                                pop     bp        ; Restore previous call frame
0000:101C 29 C0                                sub     ax,ax     ; Set AX = 0
0000:101E C3                                ret                                ; Return
0000:101F                                end proc
```



# Intel 8086

```
; _memcpy(dst, src, len)
; Copy a block of memory from one location to another.
;
; Entry stack parameters
;     [BP+6] = len, Number of bytes to copy
;     [BP+4] = src, Address of source data block
;     [BP+2] = dst, Address of target data block
;
; Return registers
;     AX = Zero
```

## Machine Language

```
0000:1000                org      1000h      ; Start at 0000:1000h

0000:1000                _memcpy  proc
0000:1000 55                push    bp          ; Set up the call frame
0000:1001 89 E5             mov     bp,sp
0000:1003 06                push    es          ; Save ES
0000:1004 8B 4E 06          mov     cx,[bp+6]   ; Set CX = len
0000:1007 E3 11             jcxz   done         ; If len=0, return
0000:1009 8B 76 04          mov     si,[bp+4]   ; Set SI = src
0000:100C 8B 7E 02          mov     di,[bp+2]   ; Set DI = dst
0000:100F 1E                push    ds          ; Set ES = DS
0000:1010 07                pop     es

0000:1011 8A 04            loop   mov     al,[si] ; Load AL from [src]
0000:1013 88 05            loop   mov     [di],al ; Store AL to [dst]
0000:1015 46                loop   inc     si      ; Increment src
0000:1016 47                loop   inc     di      ; Increment dst
0000:1017 49                loop   dec     cx      ; Decrement len
0000:1018 75 F7            loop   jnz    loop    ; Repeat the loop

0000:101A 07                done   pop     es          ; Restore ES
0000:101B 5D                done   pop     bp          ; Restore previous call frame
0000:101C 29 C0            done   sub     ax,ax       ; Set AX = 0
0000:101E C3                done   ret          ; Return
0000:101F                end proc
```

# Intel 8086

```
; _memcpy(dst, src, len)
; Copy a block of memory from one location to another.
;
; Entry stack parameters
;     [BP+6] = len, Number of bytes to copy
;     [BP+4] = src, Address of source data block
;     [BP+2] = dst, Address of target data block
;
; Return registers
;     AX = Zero
```

## Assembly Language

```
0000:1000                org      1000h           ; Start at 0000:1000h

0000:1000                _memcpy  proc
0000:1000 55              push    bp             ; Set up the call frame
0000:1001 89 E5            mov     bp,sp
0000:1003 06              push    es             ; Save ES
0000:1004 8B 4E 06        mov     cx,[bp+6]     ; Set CX = len
0000:1007 E3 11          jcxz   done           ; If len=0, return
0000:1009 8B 76 04        mov     si,[bp+4]     ; Set SI = src
0000:100C 8B 7E 02        mov     di,[bp+2]     ; Set DI = dst
0000:100F 1E             push    ds             ; Set ES = DS
0000:1010 07             pop     es

0000:1011 8A 04          loop   mov     al,[si] ; Load AL from [src]
0000:1013 88 05          mov     [di],al      ; Store AL to [dst]
0000:1015 46             inc     si            ; Increment src
0000:1016 47             inc     di            ; Increment dst
0000:1017 49             dec     cx            ; Decrement len
0000:1018 75 F7          jnz    loop          ; Repeat the loop

0000:101A 07             done  pop     es           ; Restore ES
0000:101B 5D             pop     bp           ; Restore previous call frame
0000:101C 29 C0          sub     ax,ax        ; Set AX = 0
0000:101E C3             ret
0000:101F                end proc
```

# Intel 8086

```
; _memcpy(dst, src, len)
; Copy a block of memory from one location to another.
;
; Entry stack parameters
;     [BP+6] = len, Number of bytes to copy
;     [BP+4] = src, Address of source data block
;     [BP+2] = dst, Address of target data block
;
; Return registers
;     AX = Zero
```

## Comments

```
0000:1000                org      1000h           ; Start at 0000:1000h


0000:1000                _memcpy  proc
0000:1000 55              push    bp           ; Set up the call frame
0000:1001 89 E5            mov     bp,sp
0000:1003 06              push   es           ; Save ES
0000:1004 8B 4E 06          mov     cx,[bp+6]    ; Set CX = len
0000:1007 E3 11            jcxz   done         ; If len=0, return
0000:1009 8B 76 04          mov     si,[bp+4]    ; Set SI = src
0000:100C 8B 7E 02          mov     di,[bp+2]    ; Set DI = dst
0000:100F 1E              push   ds           ; Set ES = DS
0000:1010 07              pop     es

0000:1011 8A 04            loop   mov     al,[si] ; Load AL from [src]
0000:1013 88 05            mov     [di],al     ; Store AL to [dst]
0000:1015 46              inc     si           ; Increment src
0000:1016 47              inc     di           ; Increment dst
0000:1017 49              dec     cx           ; Decrement len
0000:1018 75 F7            jnz    loop         ; Repeat the loop


0000:101A 07              done   pop     es           ; Restore ES
0000:101B 5D              pop     bp           ; Restore previous call frame
0000:101C 29 C0            sub     ax,ax        ; Set AX = 0
0000:101E C3              ret
0000:101F                end proc
```

# **Another Part of The Control Circuit**

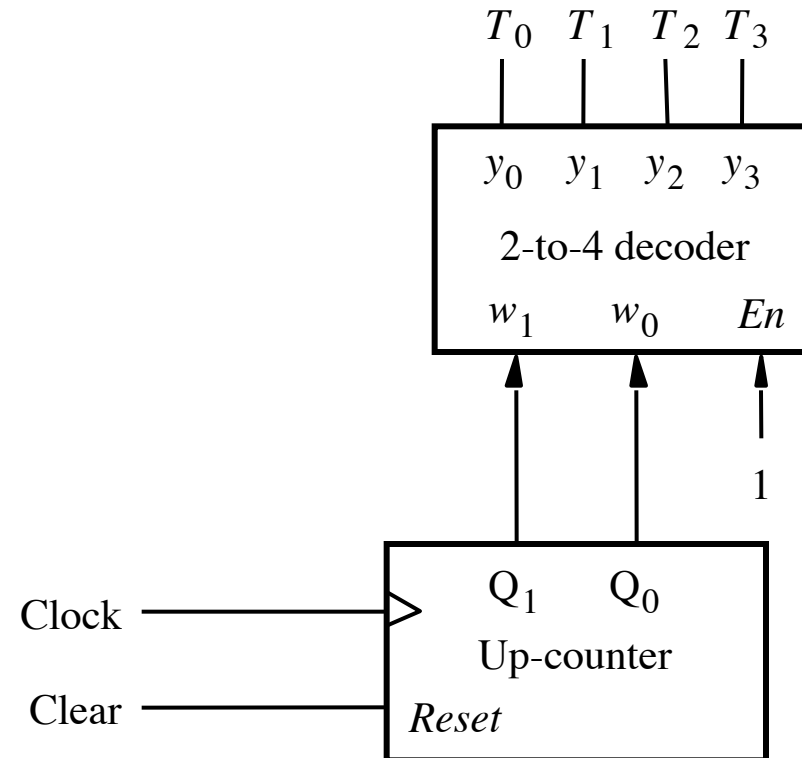
# A part of the control circuit for the processor



# What are the components?

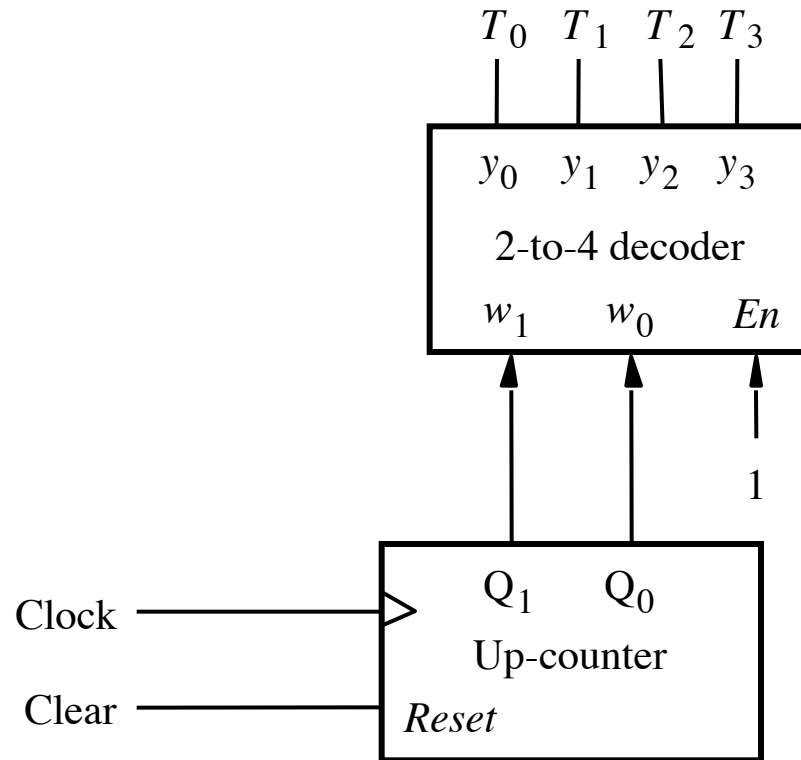


# 2-Bit Up-Counter

 


[ Figure 7.10 from the textbook ]

# 2-bit Synchronous Up-Counter

 



 
# 2-bit Synchronous Up-Counter with Enable




# 2-to-4 Decoder with Enable Input

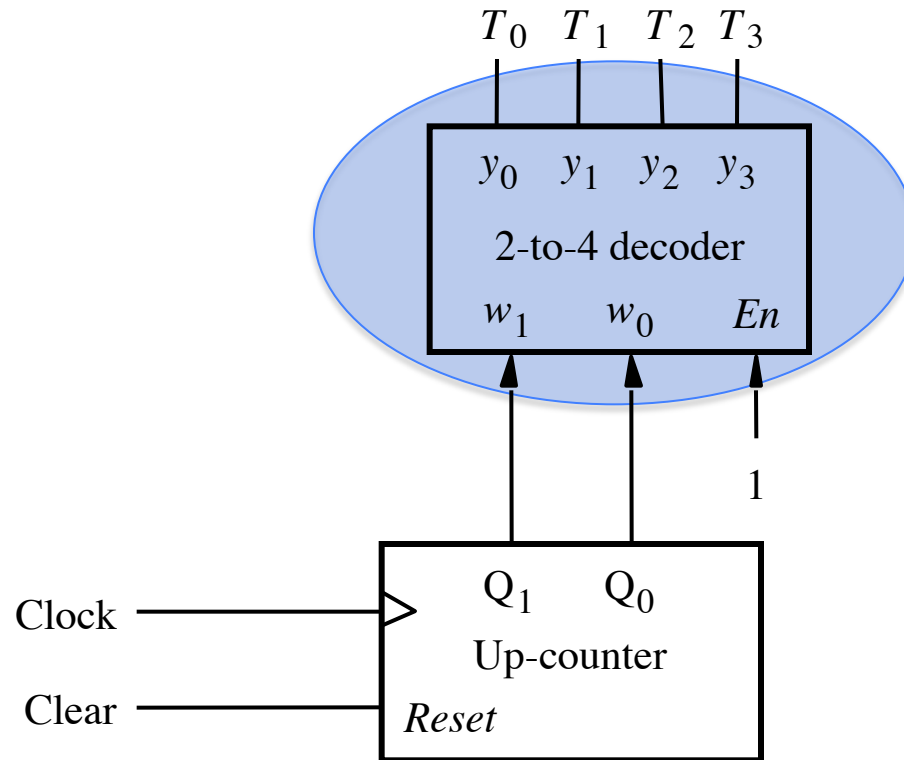


[ Figure 7.10 from the textbook ]

# 2-to-4 Decoder with an Enable Input

 


[ Figure 4.13c from the textbook ]

# 2-to-4 Decoder with an Enable Input

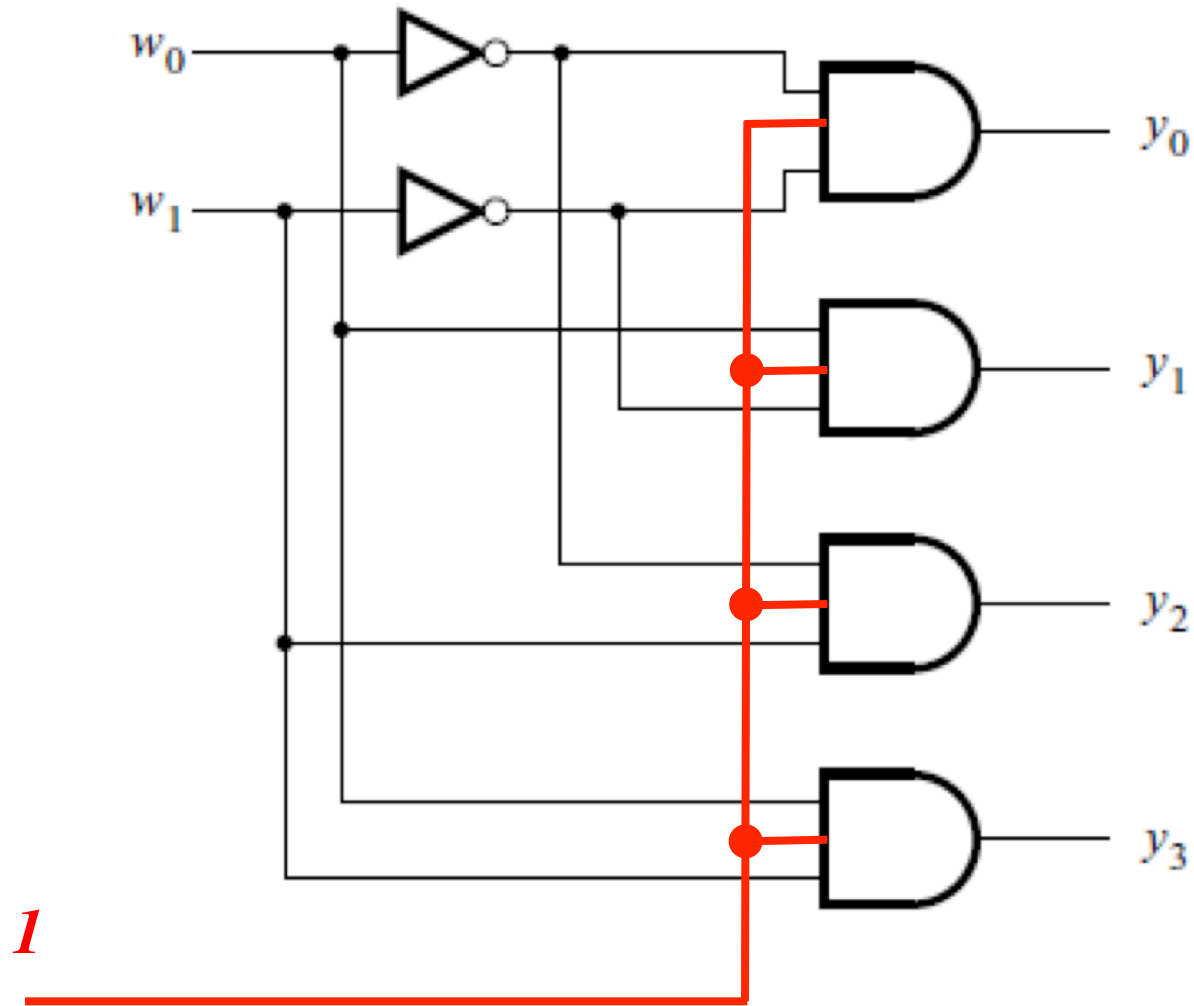


(always enabled in this example)


# So How Does This Work?

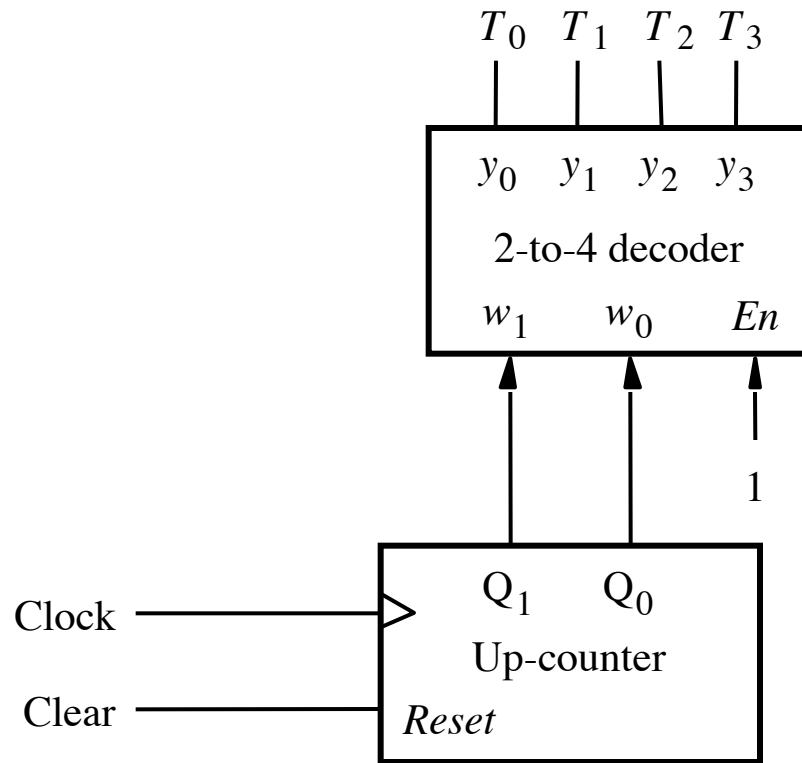


# So How Does This Work?

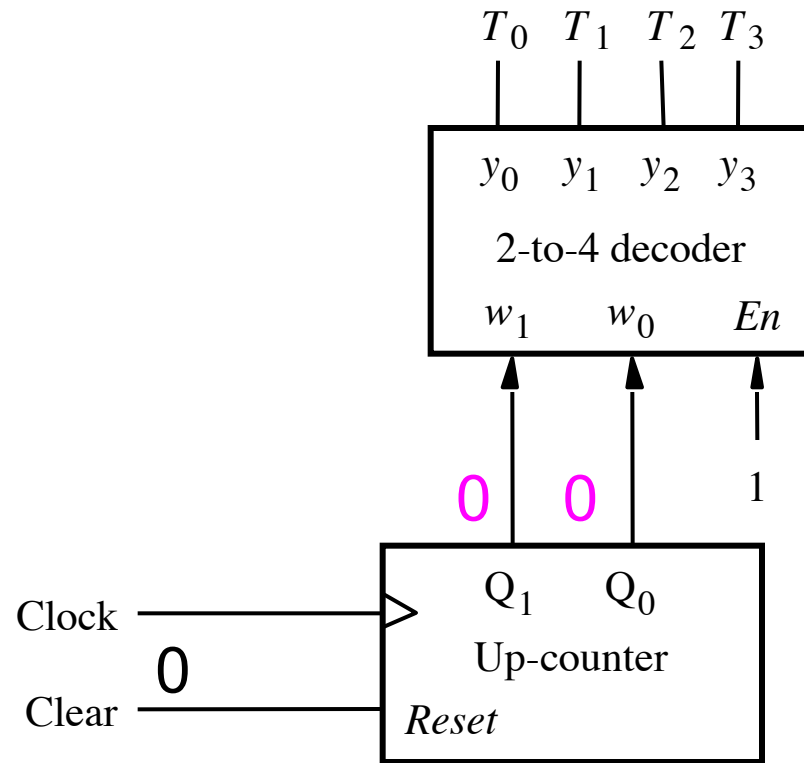

# So How Does This Work?

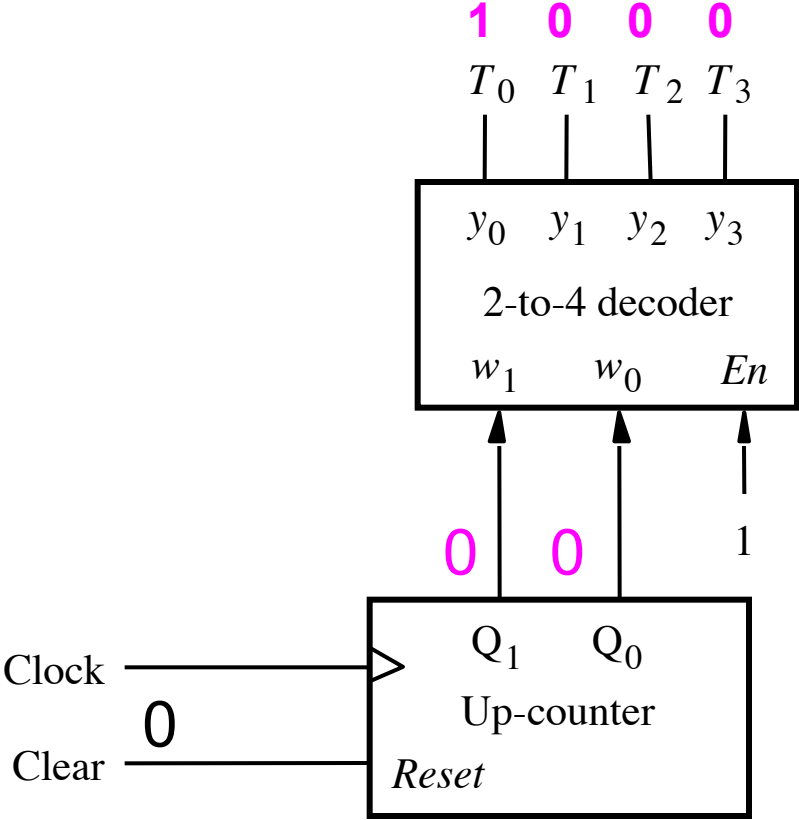


# So How Does This Work?

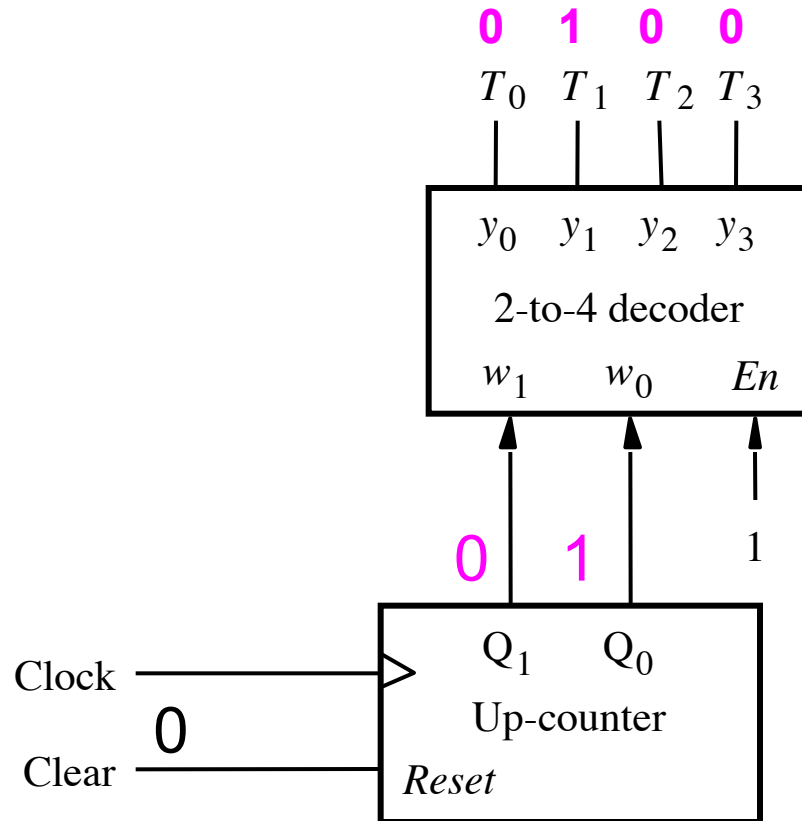





# So How Does This Work?

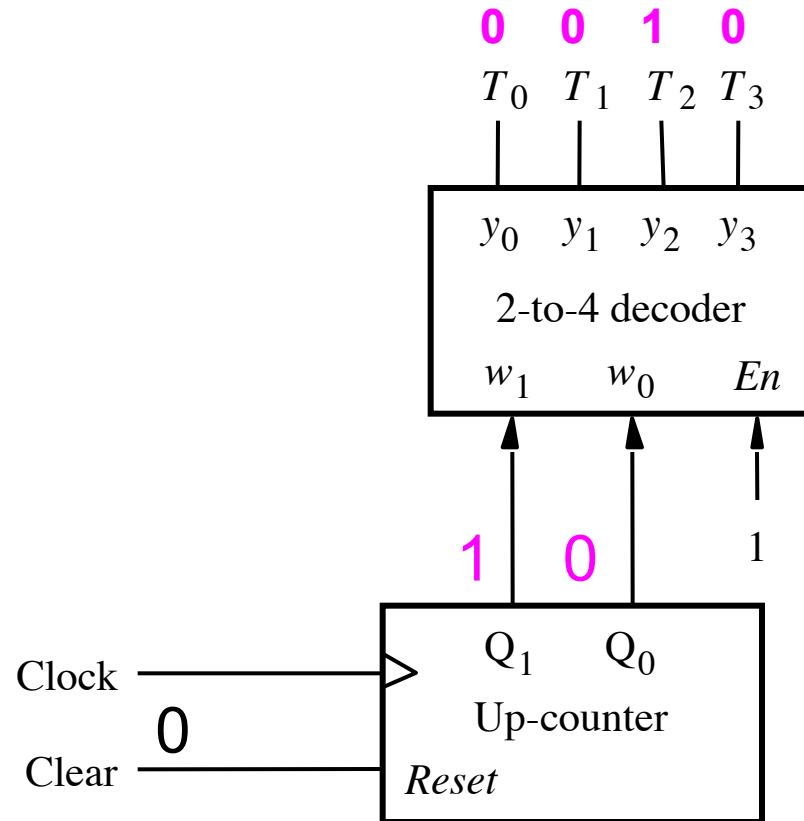


# So How Does This Work?

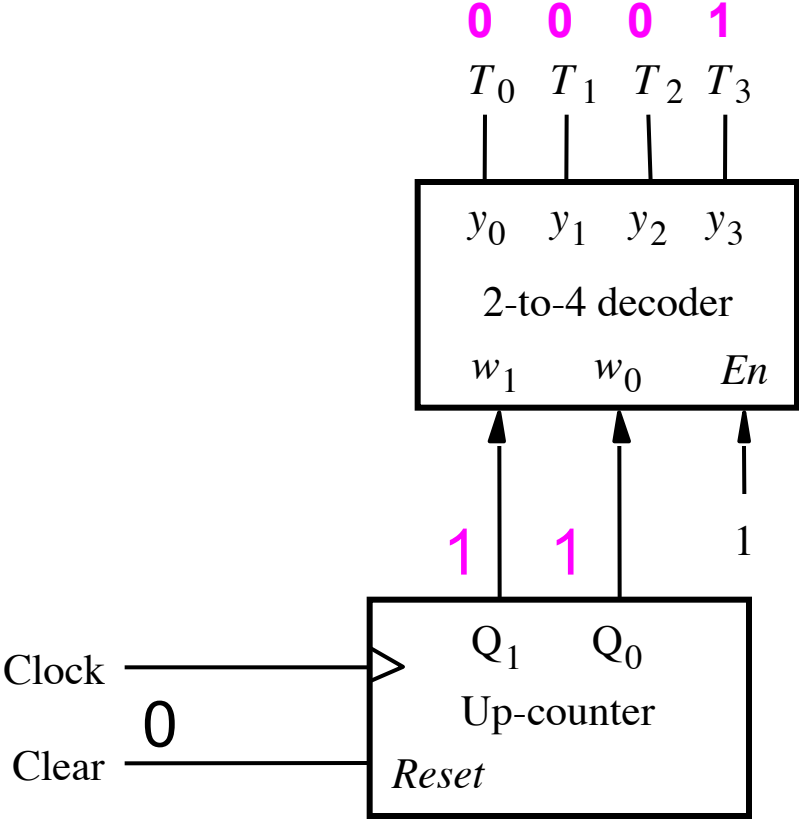


# So How Does This Work?

 


# So How Does This Work?

 

# So How Does This Work?

 

# So How Does This Work?

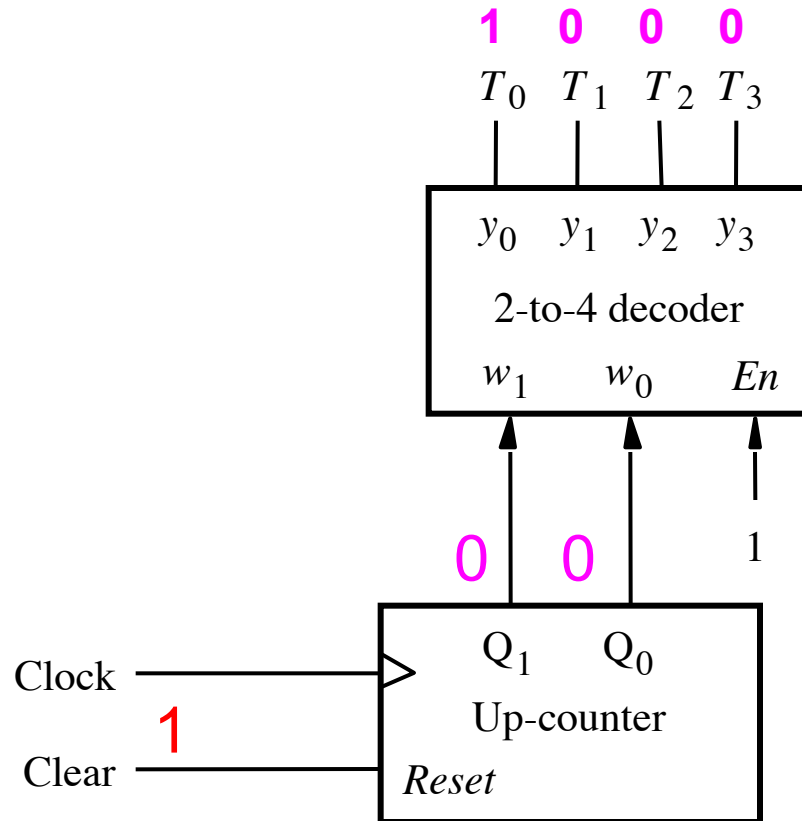

# Meaning/Explanation

- **This is like a FSM that cycles through its four states one after another.**
- **But it also can be reset to go to state 0 at any time.**
- **The implementation uses a counter followed by a decoder. The outputs of the decoder are one-hot-encoded.**
- **This is like choosing a state assignment for an FSM in which there is one Flip-Flop per state, i.e., one-hot encoding (see Section 6.2.1 in the textbook)**

# **Deriving the Control Signals**




# Design a FSM with input w and outputs

- $R0_{in}$
- $R0_{out}$
- $R1_{in}$
- $R1_{out}$
- $R2_{in}$
- $R2_{out}$
- $R3_{in}$
- $R3_{out}$
- $A_{in}$
- $G_{in}$
- $G_{out}$
- Clear
- $FR_{in}$
- AddSub
- Extern
- Done
- $T_0$
- $T_1$
- $T_2$
- $T_3$
- $I_0$
- $I_1$
- $I_2$
- $I_3$
- $X_0$
- $X_1$
- $X_2$
- $X_3$
- $Y_0$
- $Y_1$
- $Y_2$
- $Y_3$


These are helper outputs that are one-hot encoded. They are used to simplify the expressions for the other outputs.

# Control Signals

 


[ Figure 7.9 from the textbook ]

# Control Signals

 


[ Figure 7.9 from the textbook ]

# Another Control Signal

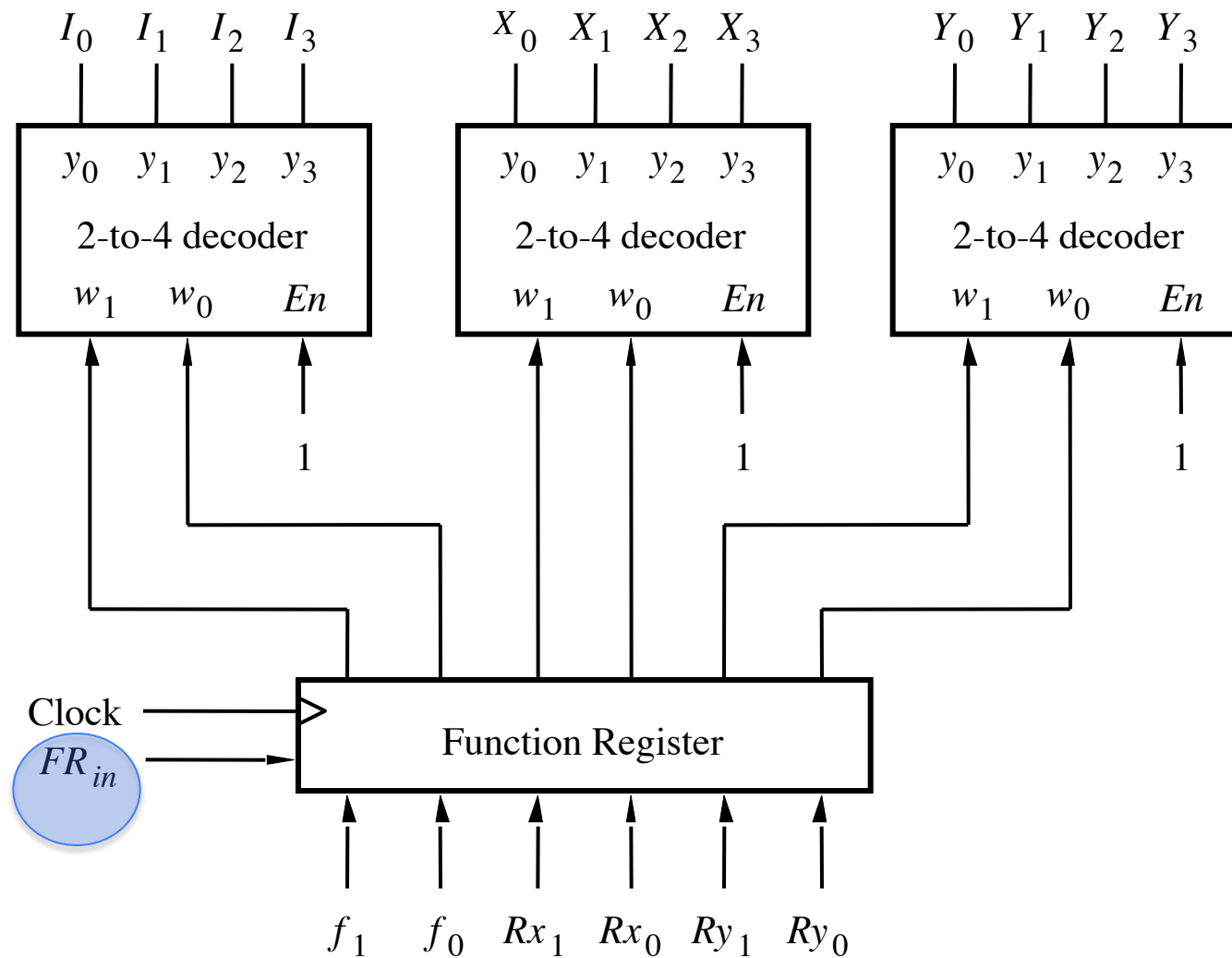


[ Figure 7.11 from the textbook ]

# Yet Another Control Signal

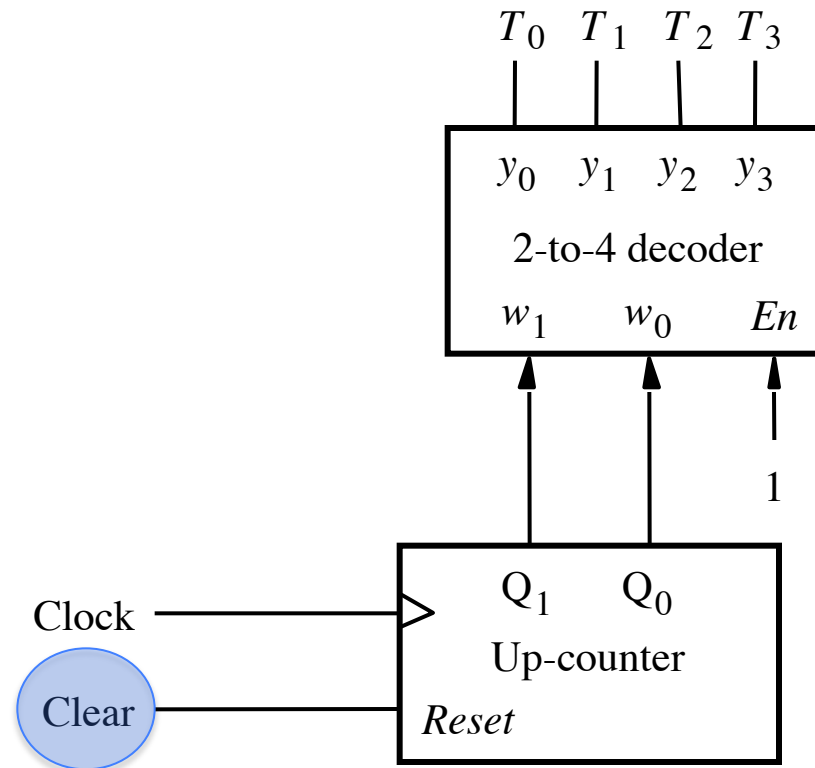

[ Figure 7.10 from the textbook ]

 
# Expressing the 'FR<sub>in</sub>' signal



$$FR_{in} = w T_0$$

Load a new operation into the function register

# Expressing the 'Clear' signal

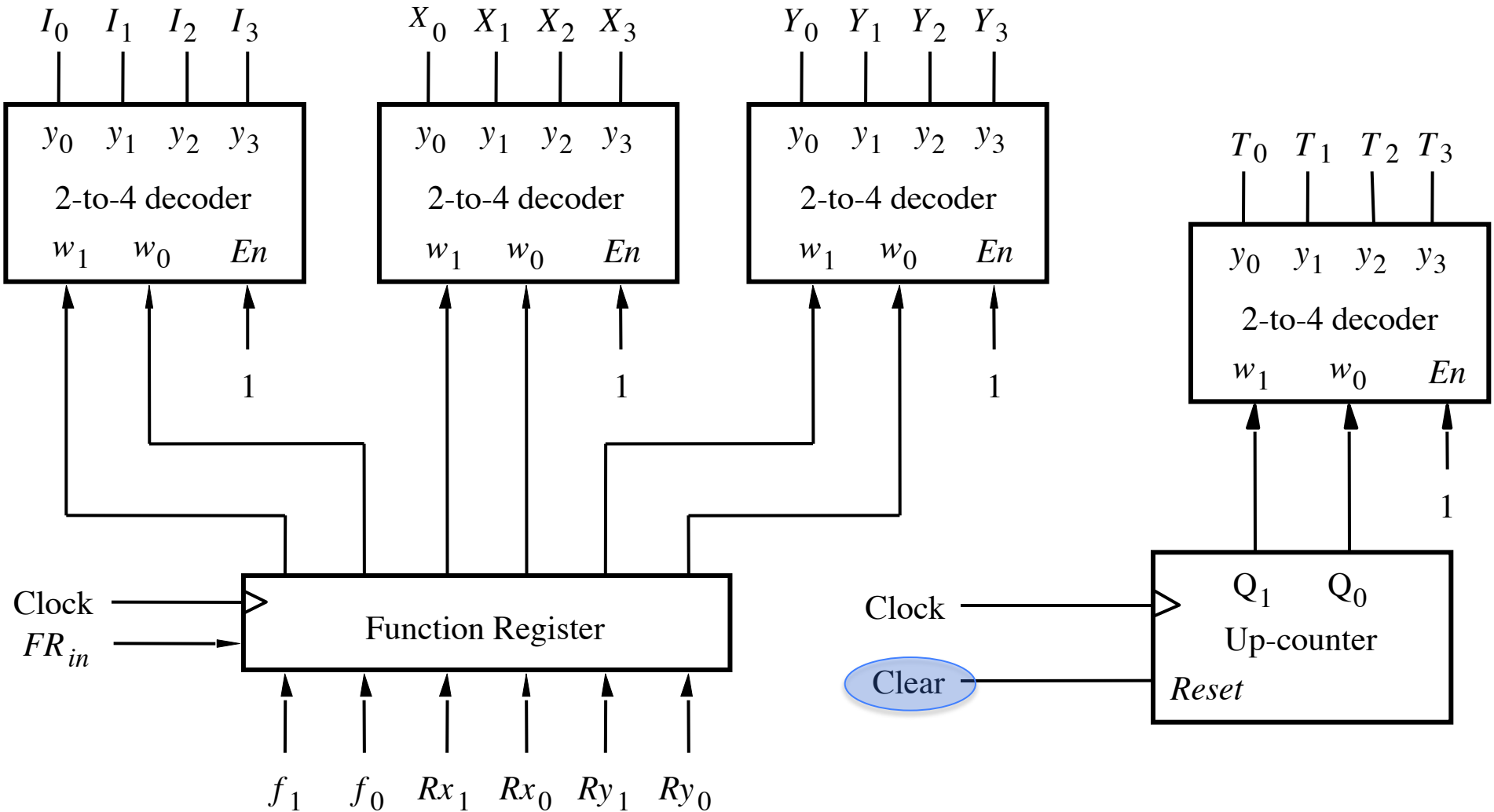

$$Clear = \overline{w} T_0 + Done$$

Reset the counter when Done or when  $w=0$  and no operation is being executed (i.e.,  $T_0=1$ ).

# Control signals asserted in each time step

	T <sub>1</sub>	T <sub>2</sub>	T <sub>3</sub>
(Load): I <sub>0</sub>	Extern R <sub>in</sub> = X Done		
(Move): I <sub>1</sub>	R <sub>in</sub> = X R <sub>out</sub> = Y Done		
(Add): I <sub>2</sub>	R <sub>out</sub> = X A <sub>in</sub>	R <sub>out</sub> = Y G <sub>in</sub> AddSub = 0	G <sub>out</sub> R <sub>in</sub> = X Done
(Sub): I <sub>3</sub>	R <sub>out</sub> = X A <sub>in</sub>	R <sub>out</sub> = Y G <sub>in</sub> AddSub = 1	G <sub>out</sub> R <sub>in</sub> = X Done



# Control signals asserted in each time step


		$T_1$	$T_2$	$T_3$
	(Load): $I_0$	Extern $R_{in} = X$ Done		
	(Move): $I_1$	$R_{in} = X$ $R_{out} = Y$ Done		
	(Add): $I_2$	$R_{out} = X$ $A_{in}$	$R_{out} = Y$ $G_{in}$ AddSub = 0	$G_{out}$ $R_{in} = X$ Done
	(Sub): $I_3$	$R_{out} = X$ $A_{in}$	$R_{out} = Y$ $G_{in}$ AddSub = 1	$G_{out}$ $R_{in} = X$ Done

Time

These come from the outputs of the 2-to-4 decoder in Figure 7.10. They are also one-hot encoded.

**These are the outputs of the first 2-to-4 decoder that is connected to the two most significant bits of the function register. They are one-hot encoded so only one of them is active at any given time (see Fig 7.11).**

# The $I_0, I_1, I_2, I_3$ and $T_0, T_1, T_2, T_3$ Signals

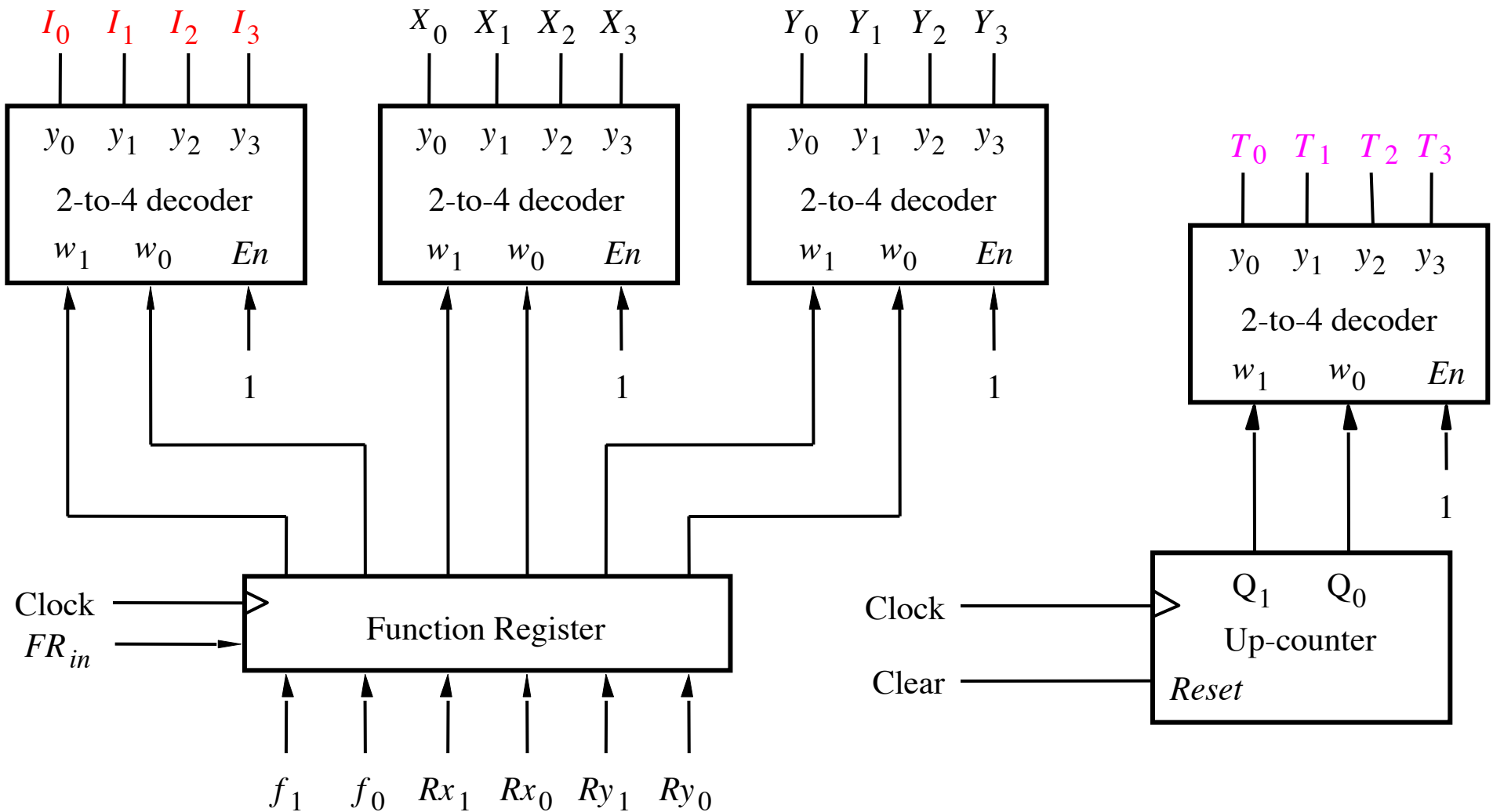

[ Figure 7.11 from the textbook ]

[ Figure 7.10 from the textbook ]

# Different Operations Take Different Amount of Time

	$T_1$	$T_2$	$T_3$	
(Load): $I_0$	Extern $R_{in} = X$ Done			1 clock cycle
(Move): $I_1$	$R_{in} = X$ $R_{out} = Y$ Done			1 clock cycle
(Add): $I_2$	$R_{out} = X$ $A_{in}$	$R_{out} = Y$ $G_{in}$ AddSub = 0	$G_{out}$ $R_{in} = X$ Done	3 clock cycles
(Sub): $I_3$	$R_{out} = X$ $A_{in}$	$R_{out} = Y$ $G_{in}$ AddSub = 1	$G_{out}$ $R_{in} = X$ Done	3 clock cycles

# Expressing the 'Extern' signal

	T <sub>1</sub>	T <sub>2</sub>	T <sub>3</sub>
(Load): I <sub>0</sub>	Extern R <sub>in</sub> = X Done		
(Move): I <sub>1</sub>	R <sub>in</sub> = X R <sub>out</sub> = Y Done		
(Add): I <sub>2</sub>	R <sub>out</sub> = X A <sub>in</sub>	R <sub>out</sub> = Y G <sub>in</sub> AddSub = 0	G <sub>out</sub> R <sub>in</sub> = X Done
(Sub): I <sub>3</sub>	R <sub>out</sub> = X A <sub>in</sub>	R <sub>out</sub> = Y G <sub>in</sub> AddSub = 1	G <sub>out</sub> R <sub>in</sub> = X Done

$$\text{Extern} = I_0 T_1$$

# Expressing the 'Done' signal

	$T_1$	$T_2$	$T_3$
(Load): $I_0$	Extern $R_{in} = X$ Done		
(Move): $I_1$	$R_{in} = X$ $R_{out} = Y$ Done		
(Add): $I_2$	$R_{out} = X$ $A_{in}$	$R_{out} = Y$ $G_{in}$ AddSub = 0	$G_{out}$ $R_{in} = X$ Done
(Sub): $I_3$	$R_{out} = X$ $A_{in}$	$R_{out} = Y$ $G_{in}$ AddSub = 1	$G_{out}$ $R_{in} = X$ Done

$$\text{Done} = (I_0 + I_1)T_1 + (I_2 + I_3)T_3$$

# Expressing the 'A<sub>in</sub>' signal

	T <sub>1</sub>	T <sub>2</sub>	T <sub>3</sub>
(Load): I <sub>0</sub>	Extern R <sub>in</sub> = X Done		
(Move): I <sub>1</sub>	R <sub>in</sub> = X R <sub>out</sub> = Y Done		
(Add): I <sub>2</sub>	R <sub>out</sub> = X A <sub>in</sub>	R <sub>out</sub> = Y G <sub>in</sub> AddSub = 0	G <sub>out</sub> R <sub>in</sub> = X Done
(Sub): I <sub>3</sub>	R <sub>out</sub> = X A <sub>in</sub>	R <sub>out</sub> = Y G <sub>in</sub> AddSub = 1	G <sub>out</sub> R <sub>in</sub> = X Done

$$A_{in} = (I_2 + I_3)T_1$$

# Expressing the 'G<sub>in</sub>' signal

	T <sub>1</sub>	T <sub>2</sub>	T <sub>3</sub>
(Load): I <sub>0</sub>	Extern R <sub>in</sub> = X Done		
(Move): I <sub>1</sub>	R <sub>in</sub> = X R <sub>out</sub> = Y Done		
(Add): I <sub>2</sub>	R <sub>out</sub> = X A <sub>in</sub>	R <sub>out</sub> = Y G <sub>in</sub> AddSub = 0	G <sub>out</sub> R <sub>in</sub> = X Done
(Sub): I <sub>3</sub>	R <sub>out</sub> = X A <sub>in</sub>	R <sub>out</sub> = Y G <sub>in</sub> AddSub = 1	G <sub>out</sub> R <sub>in</sub> = X Done

$$G_{in} = (I_2 + I_3)T_2$$

# Expressing the 'G<sub>out</sub>' signal

	T <sub>1</sub>	T <sub>2</sub>	T <sub>3</sub>
(Load): I <sub>0</sub>	Extern R <sub>in</sub> = X Done		
(Move): I <sub>1</sub>	R <sub>in</sub> = X R <sub>out</sub> = Y Done		
(Add): I <sub>2</sub>	R <sub>out</sub> = X A <sub>in</sub>	R <sub>out</sub> = Y G <sub>in</sub> AddSub = 0	G <sub>out</sub> R <sub>in</sub> = X Done
(Sub): I <sub>3</sub>	R <sub>out</sub> = X A <sub>in</sub>	R <sub>out</sub> = Y G <sub>in</sub> AddSub = 1	G <sub>out</sub> R <sub>in</sub> = X Done

$$G_{out} = (I_2 + I_3)T_3$$



# Expressing the 'AddSub' signal

	T <sub>1</sub>	T <sub>2</sub>	T <sub>3</sub>
(Load): I <sub>0</sub>	Extern R <sub>in</sub> = X Done		
(Move): I <sub>1</sub>	R <sub>in</sub> = X R <sub>out</sub> = Y Done		
(Add): I <sub>2</sub>	R <sub>out</sub> = X A <sub>in</sub>	R <sub>out</sub> = Y G <sub>in</sub> AddSub = 0	G <sub>out</sub> R <sub>in</sub> = X Done
(Sub): I <sub>3</sub>	R <sub>out</sub> = X A <sub>in</sub>	R <sub>out</sub> = Y G <sub>in</sub> AddSub = 1	G <sub>out</sub> R <sub>in</sub> = X Done

$$\text{AddSub} = I_3$$

# Expressing the 'R0<sub>in</sub>' signal

	T <sub>1</sub>	T <sub>2</sub>	T <sub>3</sub>
(Load): I <sub>0</sub>	Extern R <sub>in</sub> = X Done		
(Move): I <sub>1</sub>	R <sub>in</sub> = X R <sub>out</sub> = Y Done		
(Add): I <sub>2</sub>	R <sub>out</sub> = X A <sub>in</sub>	R <sub>out</sub> = Y G <sub>in</sub> AddSub = 0	G <sub>out</sub> R <sub>in</sub> = X Done
(Sub): I <sub>3</sub>	R <sub>out</sub> = X A <sub>in</sub>	R <sub>out</sub> = Y G <sub>in</sub> AddSub = 1	G <sub>out</sub> R <sub>in</sub> = X Done

$$R0_{in} = (I_0 + I_1)T_1 X_0 + (I_2 + I_3)T_3 X_0$$

# Expressing the 'R<sub>in</sub>' signal

	T <sub>1</sub>	T <sub>2</sub>	T <sub>3</sub>
(Load): I <sub>0</sub>	Extern R <sub>in</sub> = X Done		
(Move): I <sub>1</sub>	R <sub>in</sub> = X R <sub>out</sub> = Y Done		
(Add): I <sub>2</sub>	R <sub>out</sub> = X A <sub>in</sub>	R <sub>out</sub> = Y G <sub>in</sub> AddSub = 0	G <sub>out</sub> R <sub>in</sub> = X Done
(Sub): I <sub>3</sub>	R <sub>out</sub> = X A <sub>in</sub>	R <sub>out</sub> = Y G <sub>in</sub> AddSub = 1	G <sub>out</sub> R <sub>in</sub> = X Done

$$R_{in} = (I_0 + I_1)T_1 X_1 + (I_2 + I_3)T_3 X_1$$

# Expressing the ' $R_{in}^2$ ' signal

	$T_1$	$T_2$	$T_3$
(Load): $I_0$	Extern $R_{in} = X$ Done		
(Move): $I_1$	$R_{in} = X$ $R_{out} = Y$ Done		
(Add): $I_2$	$R_{out} = X$ $A_{in}$	$R_{out} = Y$ $G_{in}$ AddSub = 0	$G_{out}$ $R_{in} = X$ Done
(Sub): $I_3$	$R_{out} = X$ $A_{in}$	$R_{out} = Y$ $G_{in}$ AddSub = 1	$G_{out}$ $R_{in} = X$ Done

$$R_{in}^2 = (I_0 + I_1)T_1 X_2 + (I_2 + I_3)T_3 X_2$$

# Expressing the 'R<sub>3in</sub>' signal

	T <sub>1</sub>	T <sub>2</sub>	T <sub>3</sub>
(Load): I <sub>0</sub>	Extern R <sub>in</sub> = X Done		
(Move): I <sub>1</sub>	R <sub>in</sub> = X R <sub>out</sub> = Y Done		
(Add): I <sub>2</sub>	R <sub>out</sub> = X A <sub>in</sub>	R <sub>out</sub> = Y G <sub>in</sub> AddSub = 0	G <sub>out</sub> R <sub>in</sub> = X Done
(Sub): I <sub>3</sub>	R <sub>out</sub> = X A <sub>in</sub>	R <sub>out</sub> = Y G <sub>in</sub> AddSub = 1	G <sub>out</sub> R <sub>in</sub> = X Done

$$R_{3in} = (I_0 + I_1)T_1 X_3 + (I_2 + I_3)T_3 X_3$$

# Expressing the 'R0<sub>out</sub>' signal

	T <sub>1</sub>	T <sub>2</sub>	T <sub>3</sub>
(Load): I <sub>0</sub>	Extern R <sub>in</sub> = X Done		
(Move): I <sub>1</sub>	R <sub>in</sub> = X R <sub>out</sub> = Y Done		
(Add): I <sub>2</sub>	R <sub>out</sub> = X A <sub>in</sub>	R <sub>out</sub> = Y G <sub>in</sub> AddSub = 0	G <sub>out</sub> R <sub>in</sub> = X Done
(Sub): I <sub>3</sub>	R <sub>out</sub> = X A <sub>in</sub>	R <sub>out</sub> = Y G <sub>in</sub> AddSub = 1	G <sub>out</sub> R <sub>in</sub> = X Done

$$R0_{out} = I_1 T_1 Y_0 + (I_2 + I_3) (T_1 X_0 + T_2 Y_0)$$

# Expressing the 'R<sub>1</sub><sub>out</sub>' signal

	T <sub>1</sub>	T <sub>2</sub>	T <sub>3</sub>
(Load): I <sub>0</sub>	Extern R <sub>in</sub> = X Done		
(Move): I <sub>1</sub>	R <sub>in</sub> = X R <sub>out</sub> = Y Done		
(Add): I <sub>2</sub>	R <sub>out</sub> = X A <sub>in</sub>	R <sub>out</sub> = Y G <sub>in</sub> AddSub = 0	G <sub>out</sub> R <sub>in</sub> = X Done
(Sub): I <sub>3</sub>	R <sub>out</sub> = X A <sub>in</sub>	R <sub>out</sub> = Y G <sub>in</sub> AddSub = 1	G <sub>out</sub> R <sub>in</sub> = X Done

$$R_{1\text{out}} = I_1 T_1 Y_1 + (I_2 + I_3) (T_1 X_1 + T_2 Y_1)$$

# Expressing the 'R<sub>2</sub><sub>out</sub>' signal

	T <sub>1</sub>	T <sub>2</sub>	T <sub>3</sub>
(Load): I <sub>0</sub>	Extern R <sub>in</sub> = X Done		
(Move): I <sub>1</sub>	R <sub>in</sub> = X R <sub>out</sub> = Y Done		
(Add): I <sub>2</sub>	R <sub>out</sub> = X A <sub>in</sub>	R <sub>out</sub> = Y G <sub>in</sub> AddSub = 0	G <sub>out</sub> R <sub>in</sub> = X Done
(Sub): I <sub>3</sub>	R <sub>out</sub> = X A <sub>in</sub>	R <sub>out</sub> = Y G <sub>in</sub> AddSub = 1	G <sub>out</sub> R <sub>in</sub> = X Done

$$R_{2\text{out}} = I_1 T_1 Y_2 + (I_2 + I_3) (T_1 X_2 + T_2 Y_2)$$



# Expressing the 'R<sub>3</sub><sub>out</sub>' signal

	T <sub>1</sub>	T <sub>2</sub>	T <sub>3</sub>
(Load): I <sub>0</sub>	Extern R <sub>in</sub> = X Done		
(Move): I <sub>1</sub>	R <sub>in</sub> = X R <sub>out</sub> = Y Done		
(Add): I <sub>2</sub>	R <sub>out</sub> = X A <sub>in</sub>	R <sub>out</sub> = Y G <sub>in</sub> AddSub = 0	G <sub>out</sub> R <sub>in</sub> = X Done
(Sub): I <sub>3</sub>	R <sub>out</sub> = X A <sub>in</sub>	R <sub>out</sub> = Y G <sub>in</sub> AddSub = 1	G <sub>out</sub> R <sub>in</sub> = X Done


$$R_{3\text{out}} = I_1 T_1 Y_3 + (I_2 + I_3) (T_1 X_3 + T_2 Y_3)$$

# Derivation of the Control Inputs

- For more insights into these derivations see pages 434 and 435 in the textbook

# **Some Additional Topics**

# The ALU for the Simple Processor


 


[ Figure 7.9 from the textbook ]

# Another Arithmetic Logic Unit (ALU)


- Arithmetic Logic Unit (ALU) computes arithmetic or logic functions
- Example: A four-function ALU has two selection bits S1 S0 (also called OpCode) to specify the function
  - 00 (ADD), 01 (SUB), 10 (AND), 11 (OR)
- Then the following set up will work

S1	S0	Function
0	0	ADD
0	1	SUB
1	0	AND
1	1	OR

 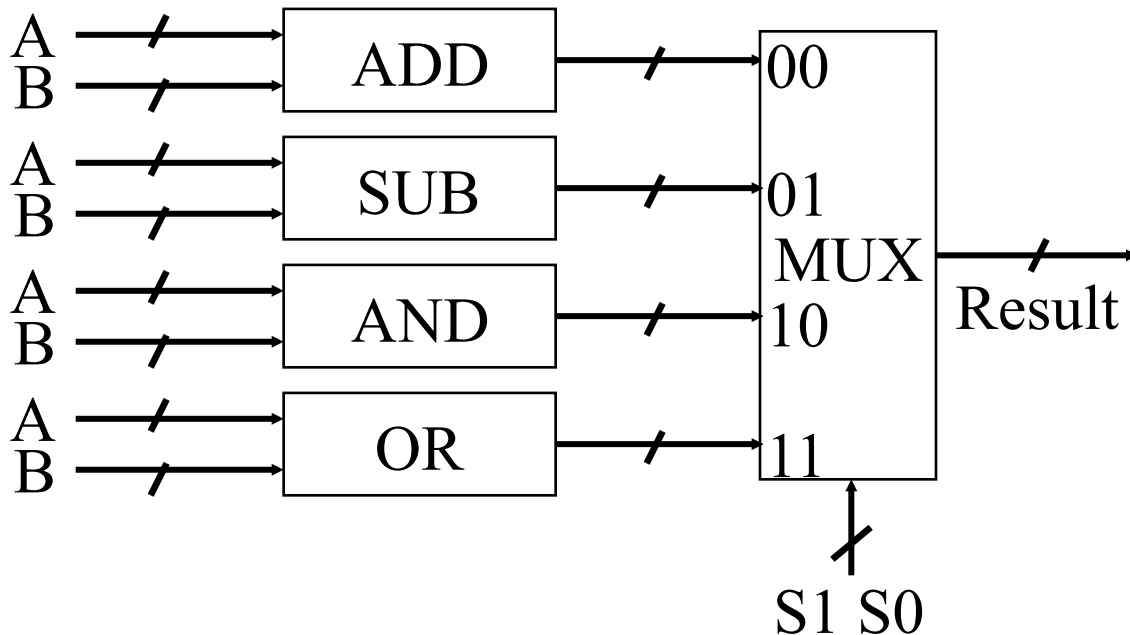
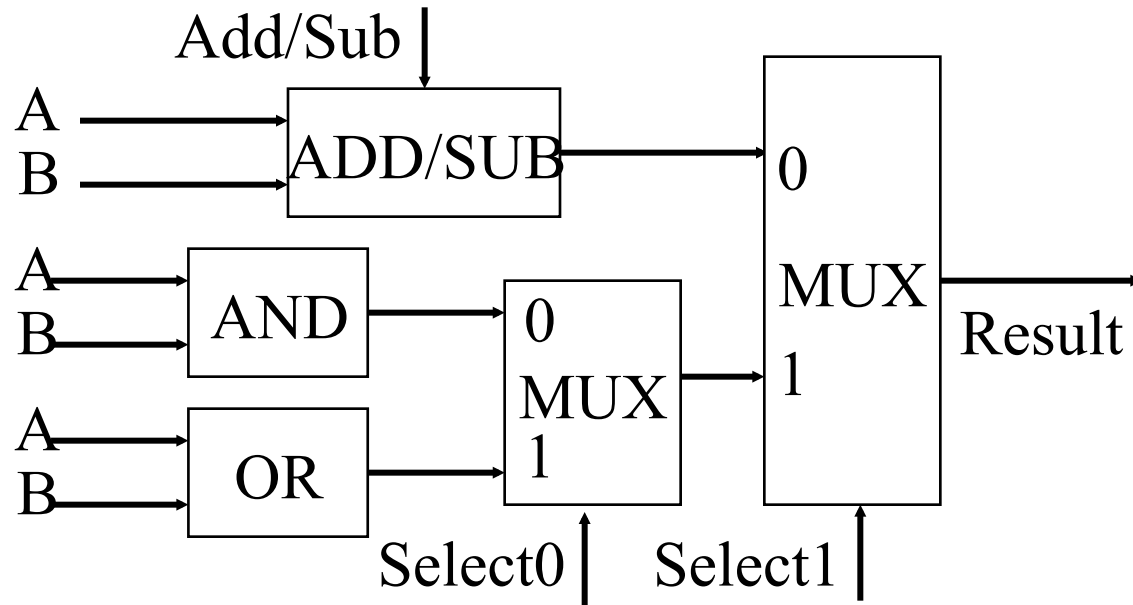
# An Alternative Design of Four-Function ALU


- The previous design is not very efficient as it uses an adder and a subtractor circuit
- We can design an add/subtract unit as discussed earlier
- Then we can design a logical unit (AND and OR) separately
- Then select appropriate output as result
- What are the control signals, Add/Sub, Select0, and Select1?



S1	S0	Function
0	0	ADD
0	1	SUB
1	0	AND
1	1	OR

# **Examples of Some Famous Microprocessors**

# Intel's 4004 Chip

 

[[http://en.wikipedia.org/wiki/Intel\\_4004](http://en.wikipedia.org/wiki/Intel_4004)]




# Technical specifications

- **Maximum clock speed was 740 kHz**
- **Instruction cycle time: 10.8  $\mu$ s  
(8 clock cycles / instruction cycle)**
- **Instruction execution time 1 or 2 instruction cycles  
(10.8 or 21.6  $\mu$ s), 46300 to 92600 instructions per  
second**
- **Built using 2,300 transistors**
 
# Technical specifications

- **Separate program and data storage.**
- **The 4004, with its need to keep pin count down, used a single multiplexed 4-bit bus for transferring:**
  - **12-bit addresses**
  - **8-bit instructions**
  - **4-bit data words**
- **Instruction set contained 46 instructions (of which 41 were 8 bits wide and 5 were 16 bits wide)**
- **Register set contained 16 registers of 4 bits each**
- **Internal subroutine stack, 3 levels deep.**



### Intel 4004 registers

<sup>1</sup><sub>1</sub> <sup>1</sup><sub>0</sub> <sup>0</sup><sub>9</sub> <sup>0</sup><sub>8</sub> <sup>0</sup><sub>7</sub> <sup>0</sup><sub>6</sub> <sup>0</sup><sub>5</sub> <sup>0</sup><sub>4</sub> <sup>0</sup><sub>3</sub> <sup>0</sup><sub>2</sub> <sup>0</sup><sub>1</sub> <sup>0</sup><sub>0</sub> (bit position)

#### Main registers

		A	Accumulator
	R0	R1	
	R2	R3	
	R4	R5	
	R6	R7	
	R8	R9	
	R10	R11	
	R12	R13	
	R14	R15	

#### Program counter

PC	Program Counter
----	-----------------


#### Push-down address call stack

PC1	Call level 1
PC2	Call level 2
PC3	Call level 3

#### Status register

C	P	Z	S	Flags
---	---	---	---	-------

# Intel's 8086 Chip

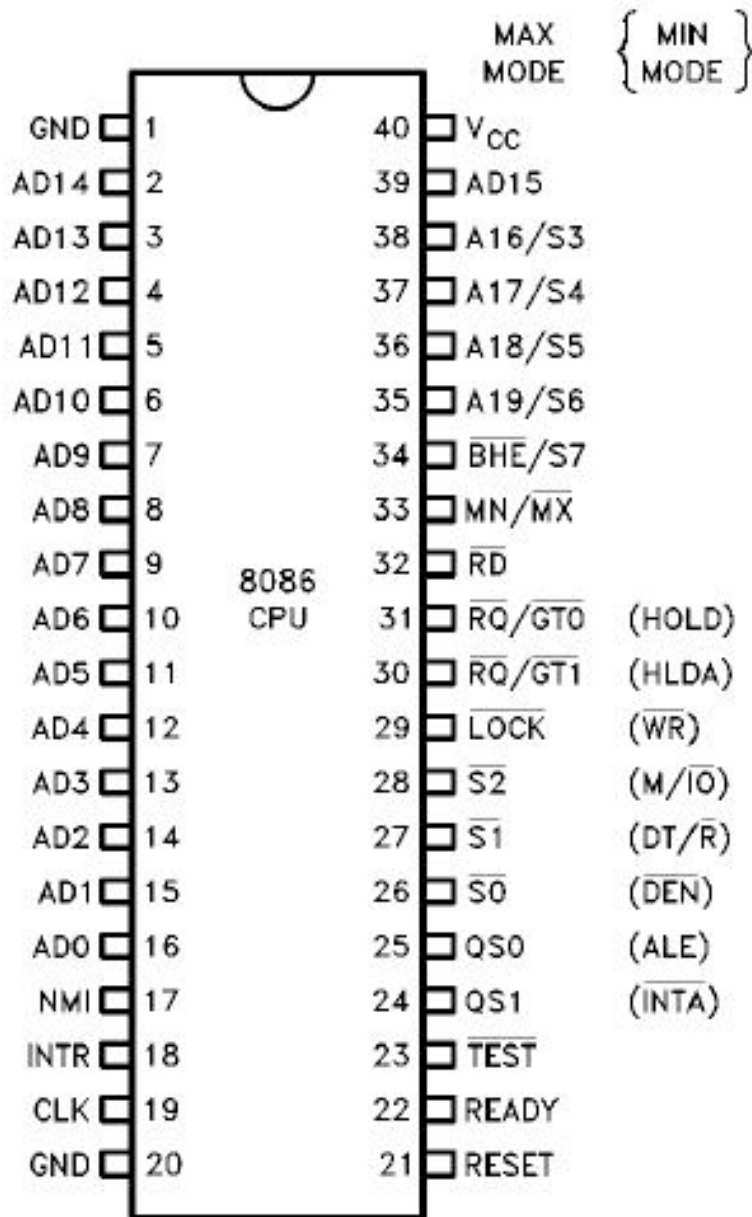

## Intel 8086 registers

1<sup>9</sup> 1<sup>8</sup> 1<sup>7</sup> 1<sup>6</sup> 1<sup>5</sup> 1<sup>4</sup> 1<sup>3</sup> 1<sup>2</sup> 1<sup>1</sup> 1<sup>0</sup> 0<sup>9</sup> 0<sup>8</sup> 0<sup>7</sup> 0<sup>6</sup> 0<sup>5</sup> 0<sup>4</sup> 0<sup>3</sup> 0<sup>2</sup> 0<sup>1</sup> 0<sup>0</sup> (bit position)

### Main registers

	AH	AL	<b>AX</b> (primary accumulator)
	BH	BL	<b>BX</b> (base, accumulator)
	CH	CL	<b>CX</b> (counter, accumulator)
	DH	DL	<b>DX</b> (accumulator, other functions)

### Index registers

0 0 0 0	SI	<b>Source Index</b>
0 0 0 0	DI	<b>Destination Index</b>
0 0 0 0	BP	<b>Base Pointer</b>
0 0 0 0	SP	<b>Stack Pointer</b>

### Program counter


0 0 0 0	IP	<b>Instruction Pointer</b>
---------	----	----------------------------

### Segment registers

CS	0 0 0 0	<b>Code Segment</b>
DS	0 0 0 0	<b>Data Segment</b>
ES	0 0 0 0	<b>ExtraSegment</b>
SS	0 0 0 0	<b>Stack Segment</b>

### Status register

- - - - O D I T S Z - A - P - C	Flags
---------------------------------	-------

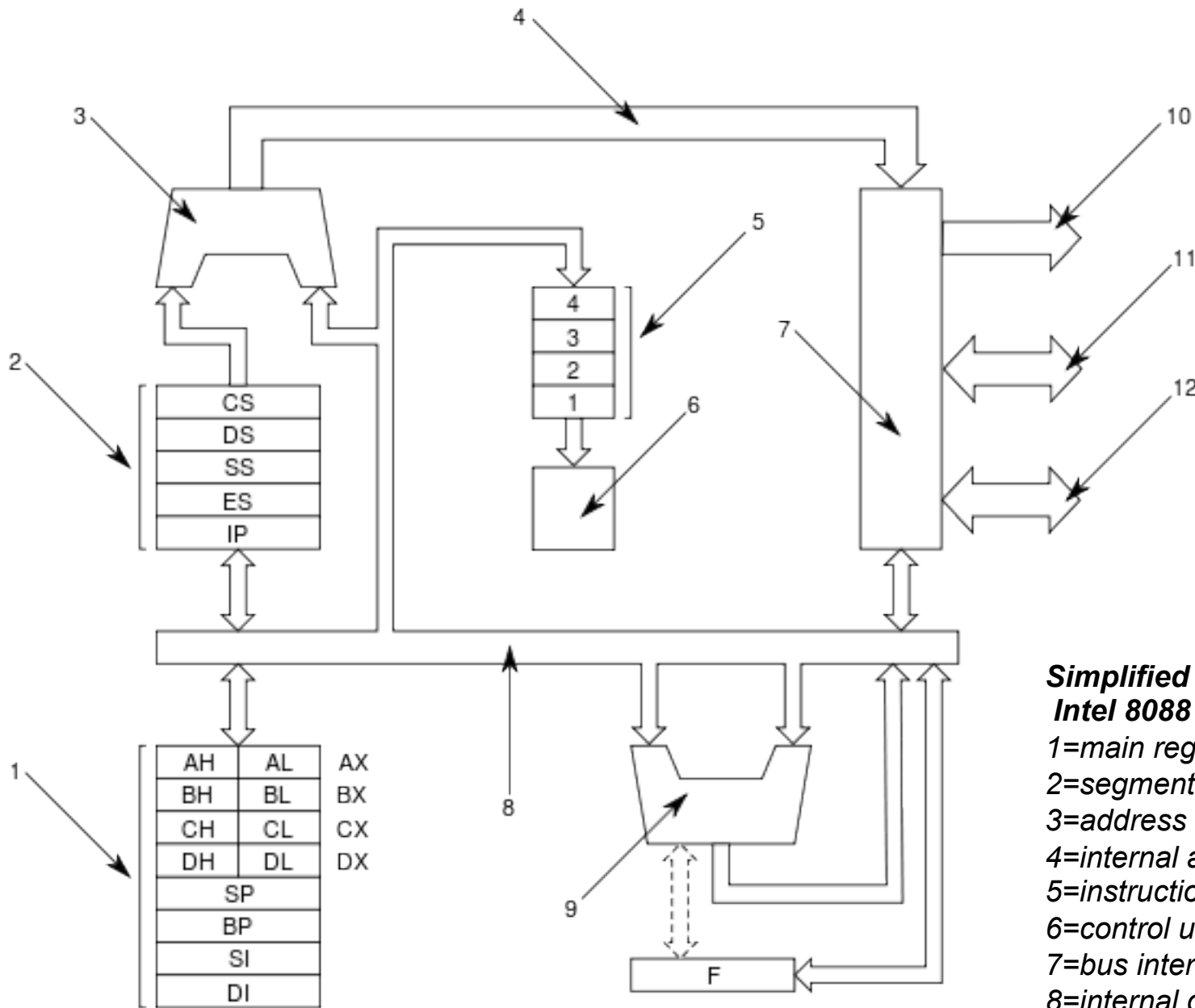

**Simplified block diagram of Intel 8088 (a variant of 8086);**  
 1=main registers;  
 2=segment registers and IP;  
 3=address adder;  
 4=internal address bus;  
 5=instruction queue;  
 6=control unit (very simplified!);  
 7=bus interface;  
 8=internal databus;  
 9=ALU;  
 10/11/12=external address/  
 data/control bus.

**Questions?**



**THE END**