



CprE 281: Digital Logic

Instructor: Alexander Stoytchev

<http://www.ece.iastate.edu/~alexs/classes/>

Simple Processor

CprE 281: Digital Logic
Iowa State University, Ames, IA
Copyright © Alexander Stoytchev

Administrative Stuff

- **Final Project (7% of your grade)**
- **This is due this week (during your lab)**


Administrative Stuff

- **Extra Credit Homework**
- **Posted on the class web page**
- **This is due this Friday @ 4pm**

Digital System


- **Datapath circuit**
 - To store data
 - To manipulate data
 - To transfer data from one part of the system to another
 - Comprise building blocks such as registers, shift registers, counters, multipliers, decoders, encoders, adders, etc.
- **Control circuit**
 - Controls the operation of the datapath circuit
 - Designed as a FSM

A Simple Processor

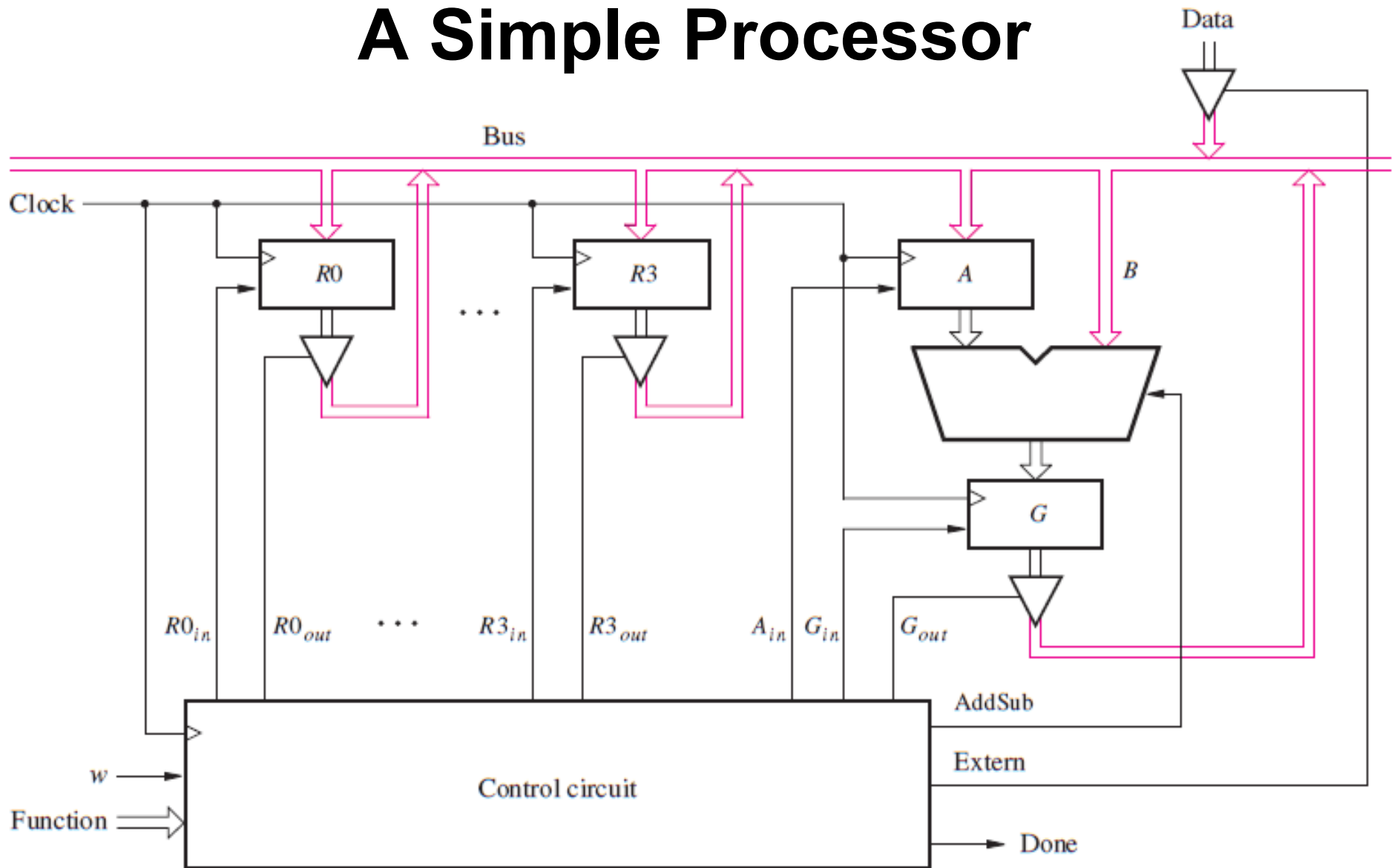


[Figure 7.9 from the textbook]

What are the components?

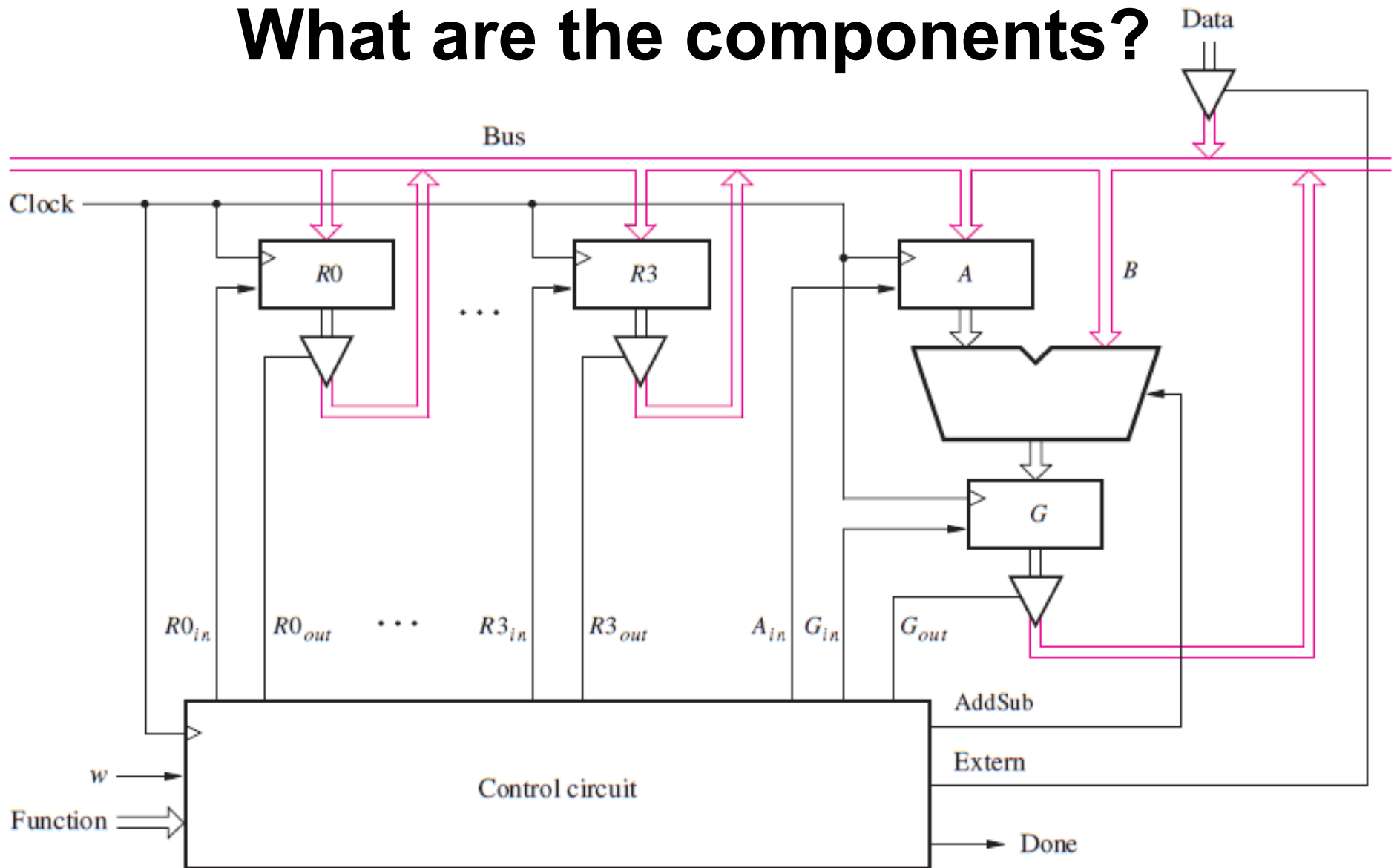


[Figure 7.9 from the textbook]

Registers

 


[Figure 7.9 from the textbook]

Data Bus

 


[Figure 7.9 from the textbook]

Tri-State Drivers

 


[Figure 7.9 from the textbook]

Arithmetic Logic Unit (ALU)

 

[Figure 7.9 from the textbook]


Control Circuit

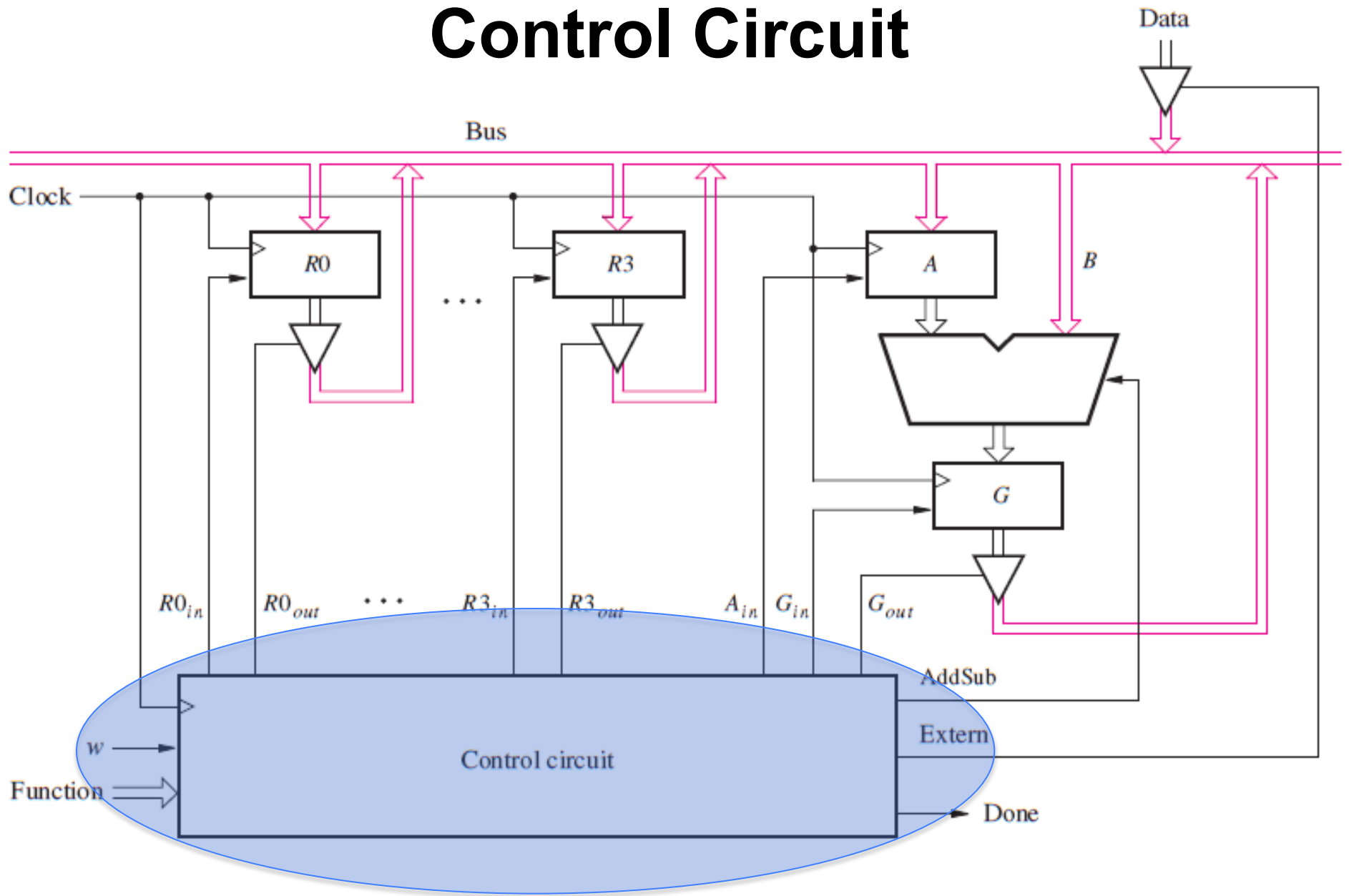

[Figure 7.9 from the textbook]


A Closer Look at the Registers

Register R0

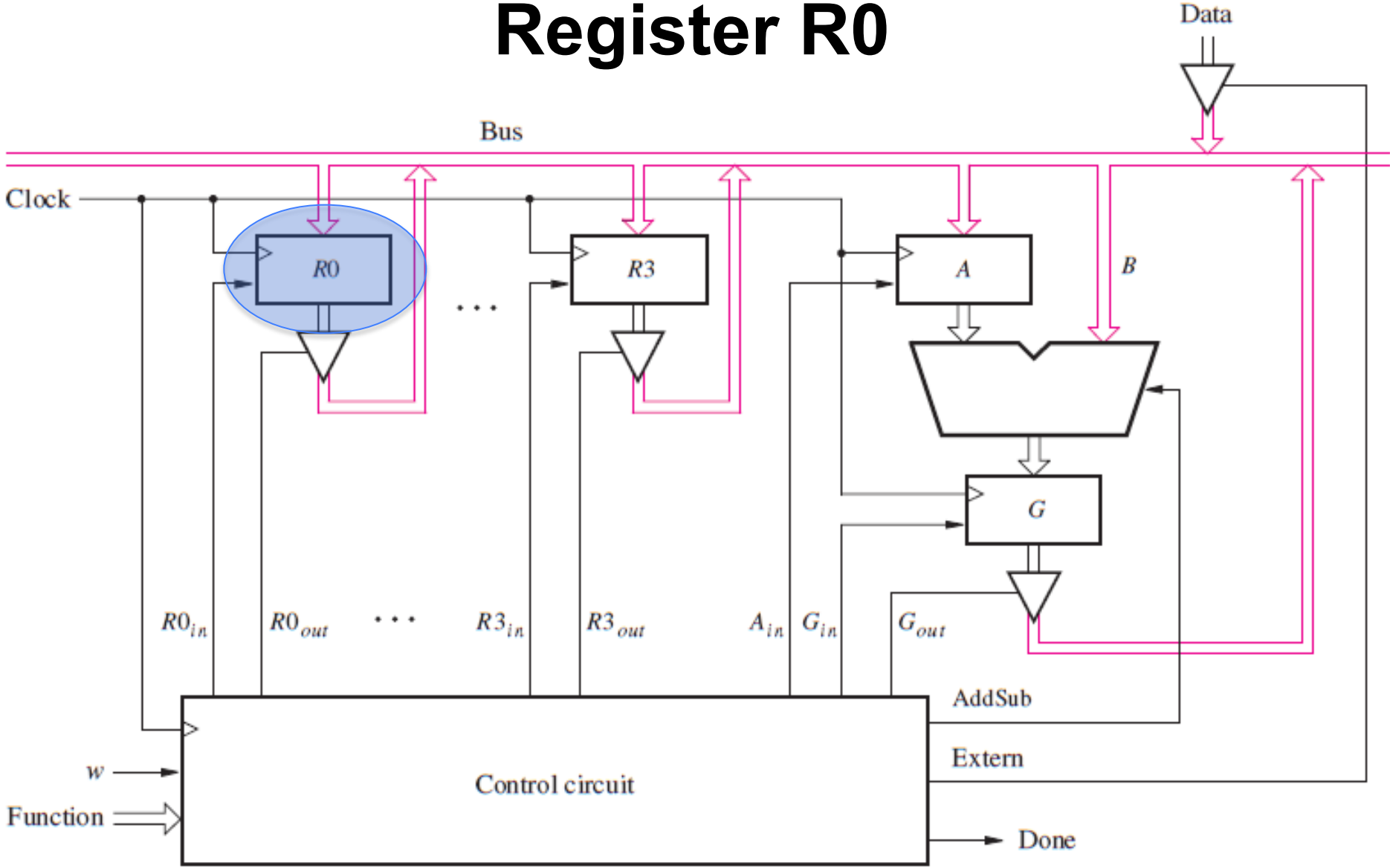


[Figure 7.9 from the textbook]

All Registers

 


[Figure 7.9 from the textbook]

Registers R0, R1, R2 and R3 are accessible to the programmer

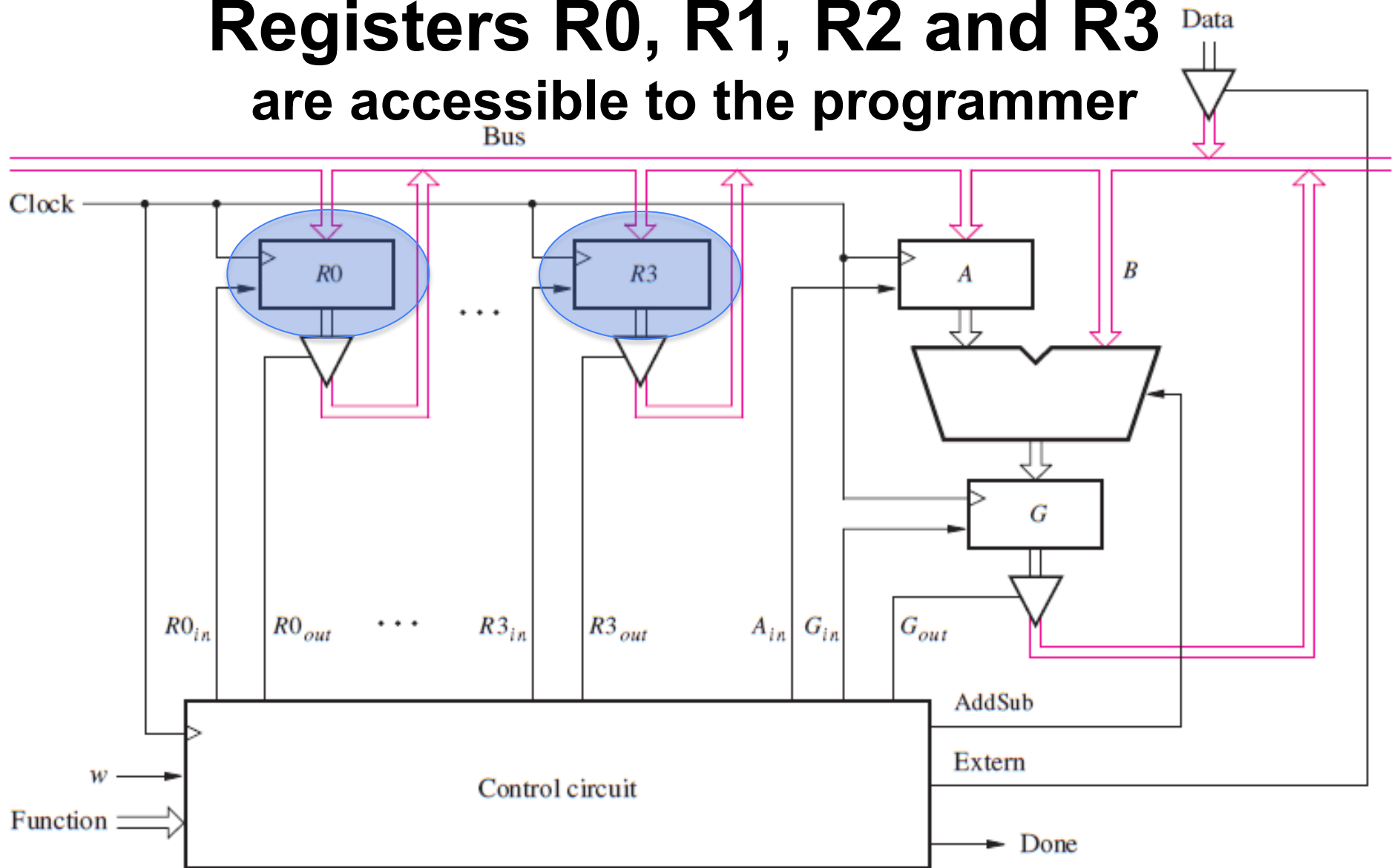


[Figure 7.9 from the textbook]

Registers A and G are NOT accessible to the programmer

 


[Figure 7.9 from the textbook]


4-Bit Register

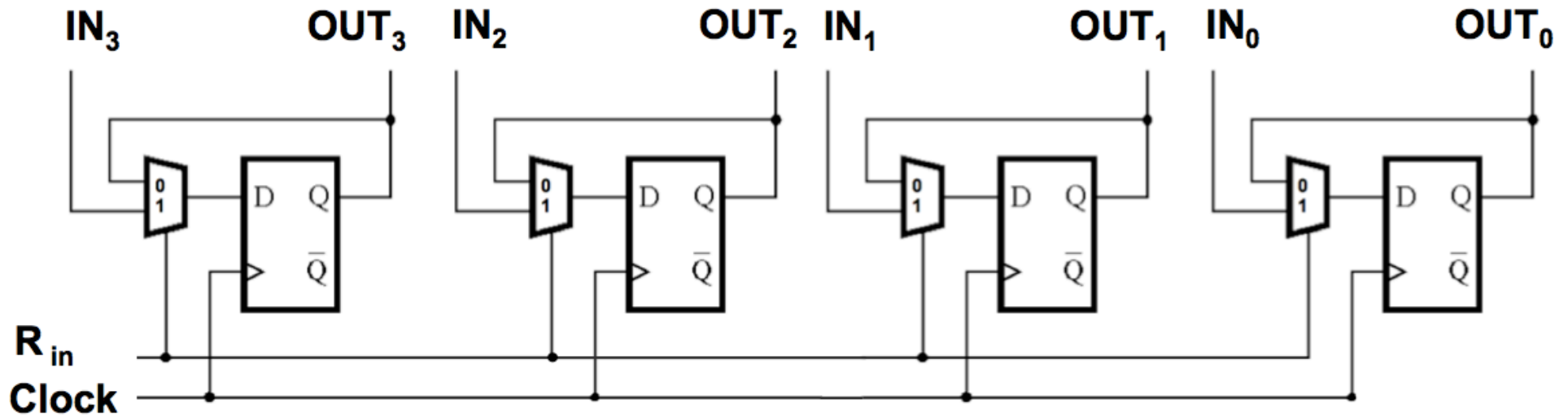


Loading Data into the Register

 


Loading Data into the Register

 


Loading Data into the Register

 


Loading Data into the Register

 


Keeping Data into the Register

 

Keeping Data into the Register

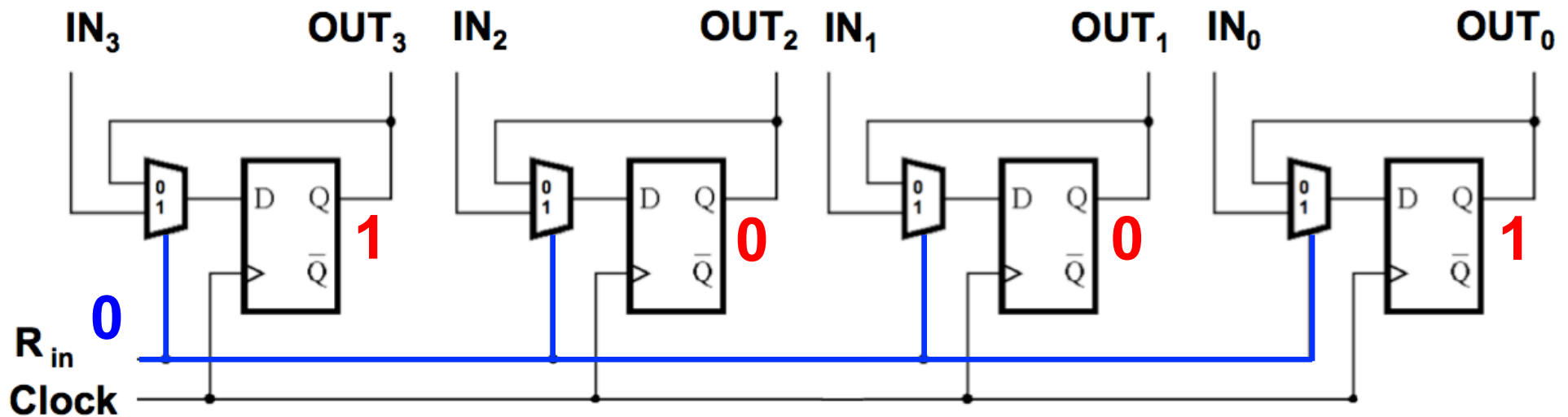


Keeping Data into the Register

 

A Closer Look at the Data Bus


Data Bus

 

[Figure 7.9 from the textbook]


Bus Structure

 - We need a way to transfer data from any register (device) to any other register (device)
- A bus is simply a set of n wires to transfer an n -bit data




- What if two registers write to the bus at the same time?

One way to implement a data bus is to use multiplexers

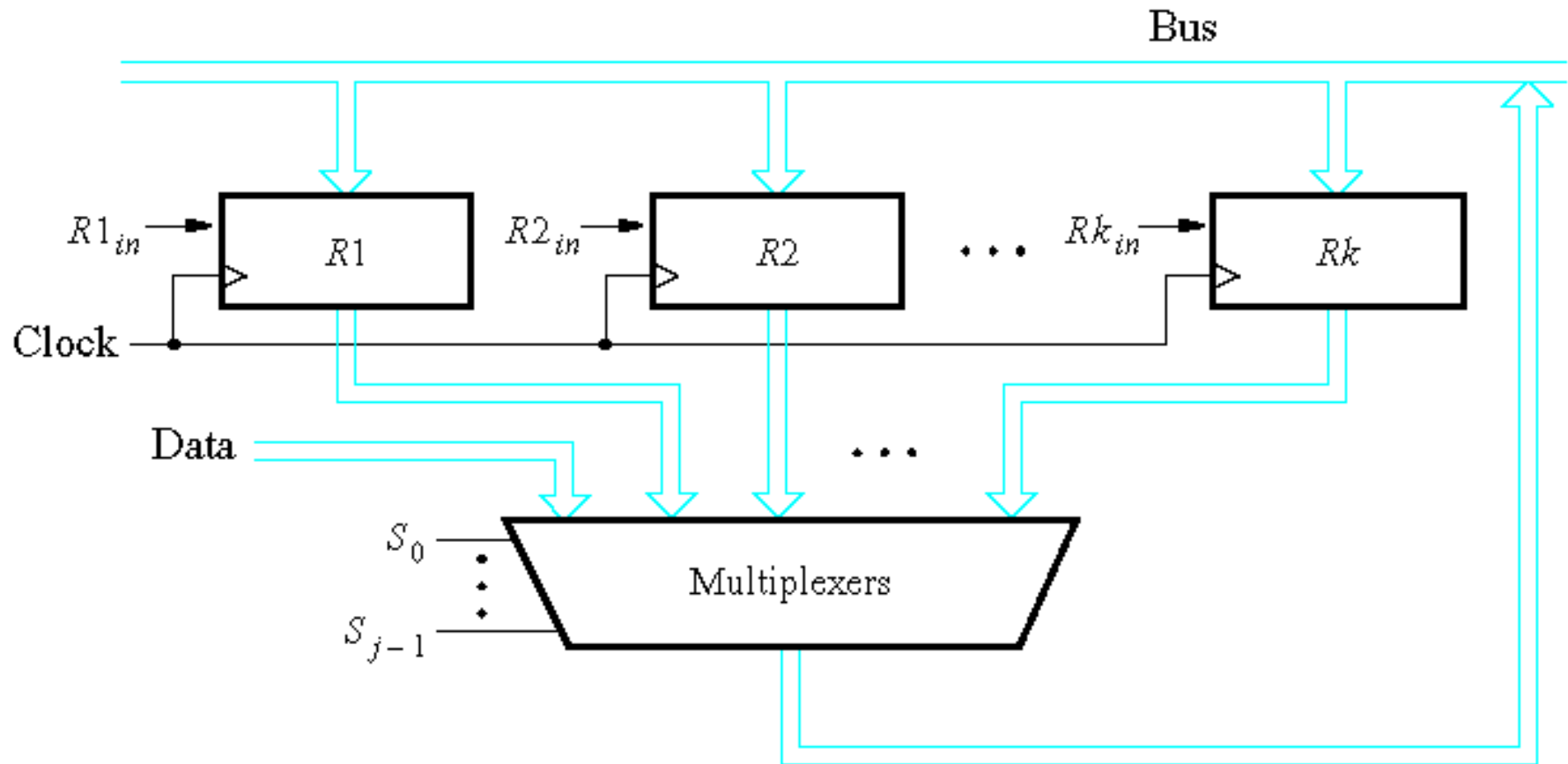


[Figure 7.4 from the textbook]

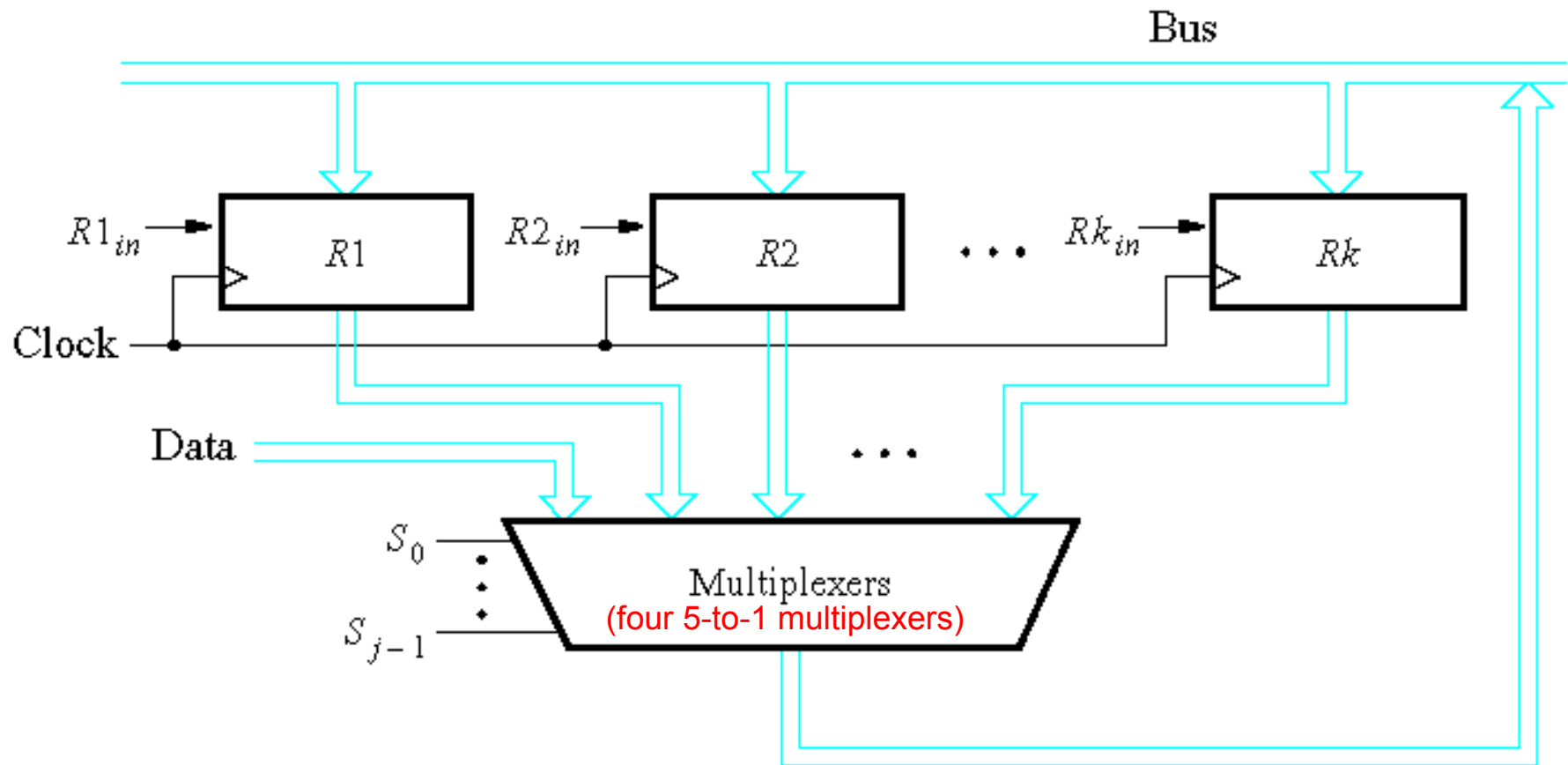One way to implement a data bus is to use multiplexers




This requires one multiplexer per bit.
Assuming there are four 4-bit registers, we need four 5-to-1 multiplexers.

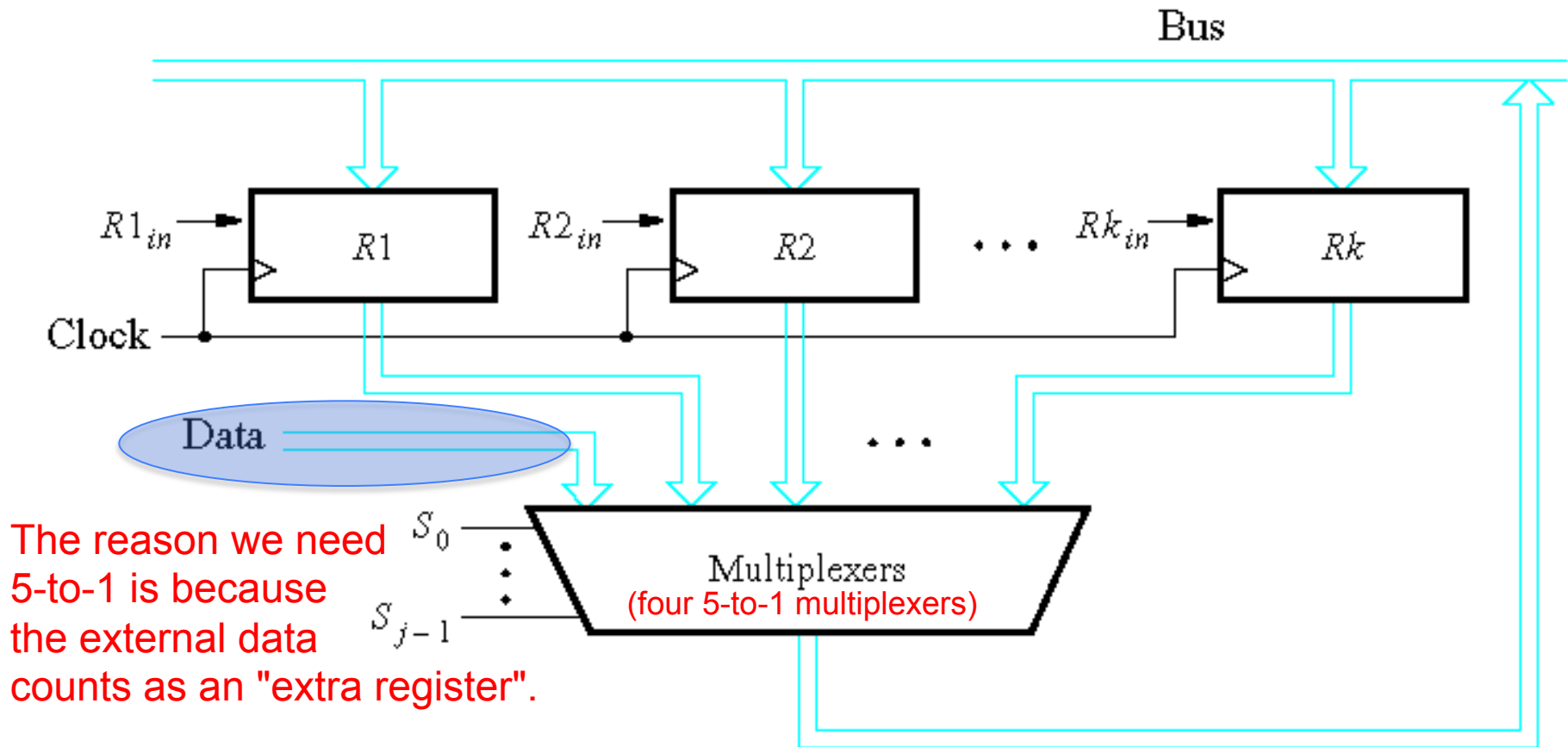One way to implement a data bus is to use multiplexers




A Closer Look at the Tri-State Driver

Tri-State Driver

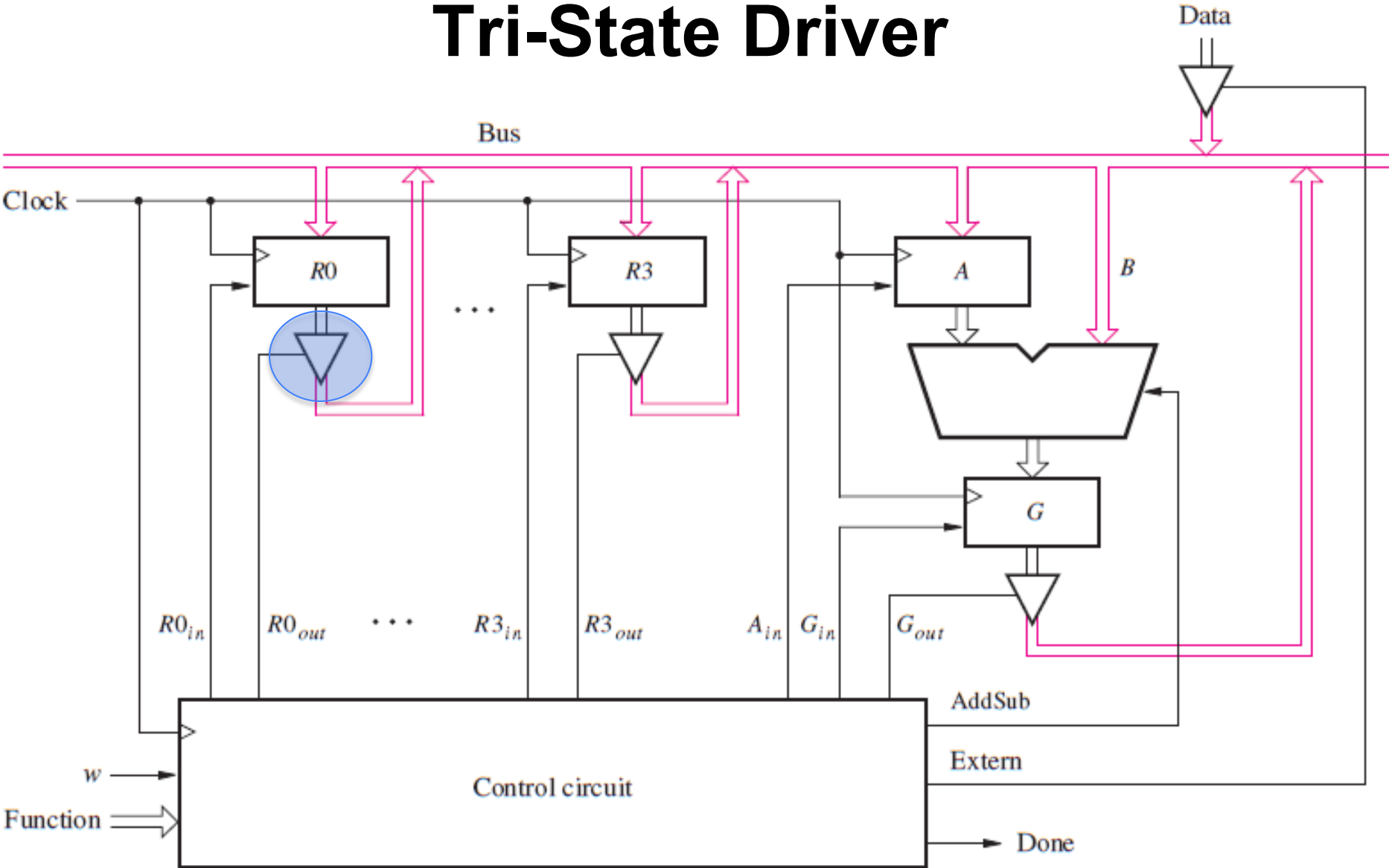

[Figure 7.9 from the textbook]


All Tri-State Drivers

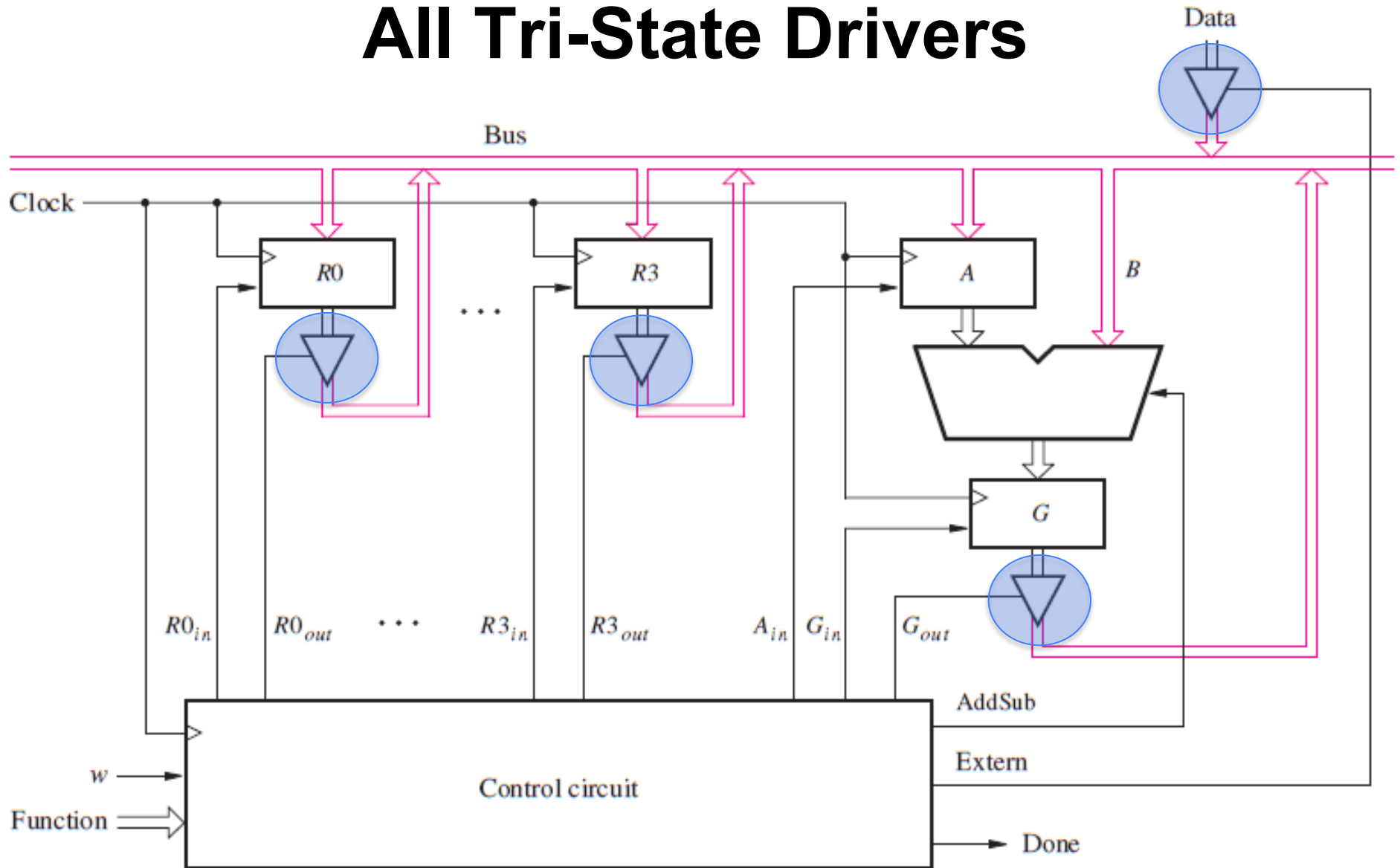


[Figure 7.9 from the textbook]

Tri-state driver

(see Appendix B for more details)

 

(a) Symbol

 

(b) Equivalent circuit

Z: High impedance state


e	w	f
0	0	Z
0	1	Z
1	0	0
1	1	1

(c) Truth table

Tri-state driver


(see Appendix B for more details)

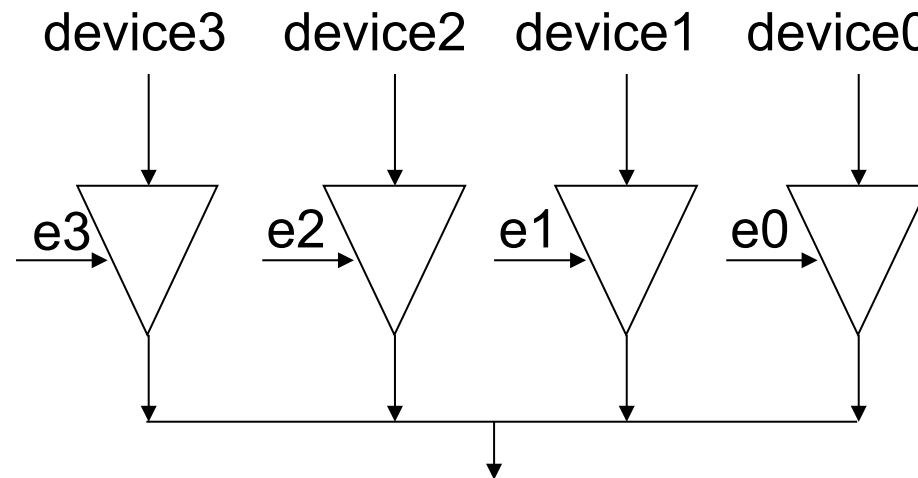- **Alternative way to implement a data bus**
- **Allows several devices to be connected to a single wire (this is not possible with regular logic gates because their outputs are always active; an OR gate is needed)**
- **Note that at any time, at most one of e0, e1, e2, and e3 can be set to 1**




An n-bit Tri-State Driver

 
can be constructed using n 1-bit tri-state buffers



2-Bit Register

 


 How to connect two 2-bit registers to a bus (using tri-state drivers)



This shows only two 2-bit registers, but this design scales to more and larger registers.


Moving the Contents of R1 to R2

 

Register 1 stores the number $2_{10} = 10_2$


Register 2 stores the number $1_{10} = 01_2$

Moving the Contents of R1 to R2

 


Initially all control inputs are set to 0 (no reading or writing allowed).

Moving the Contents of R1 to R2

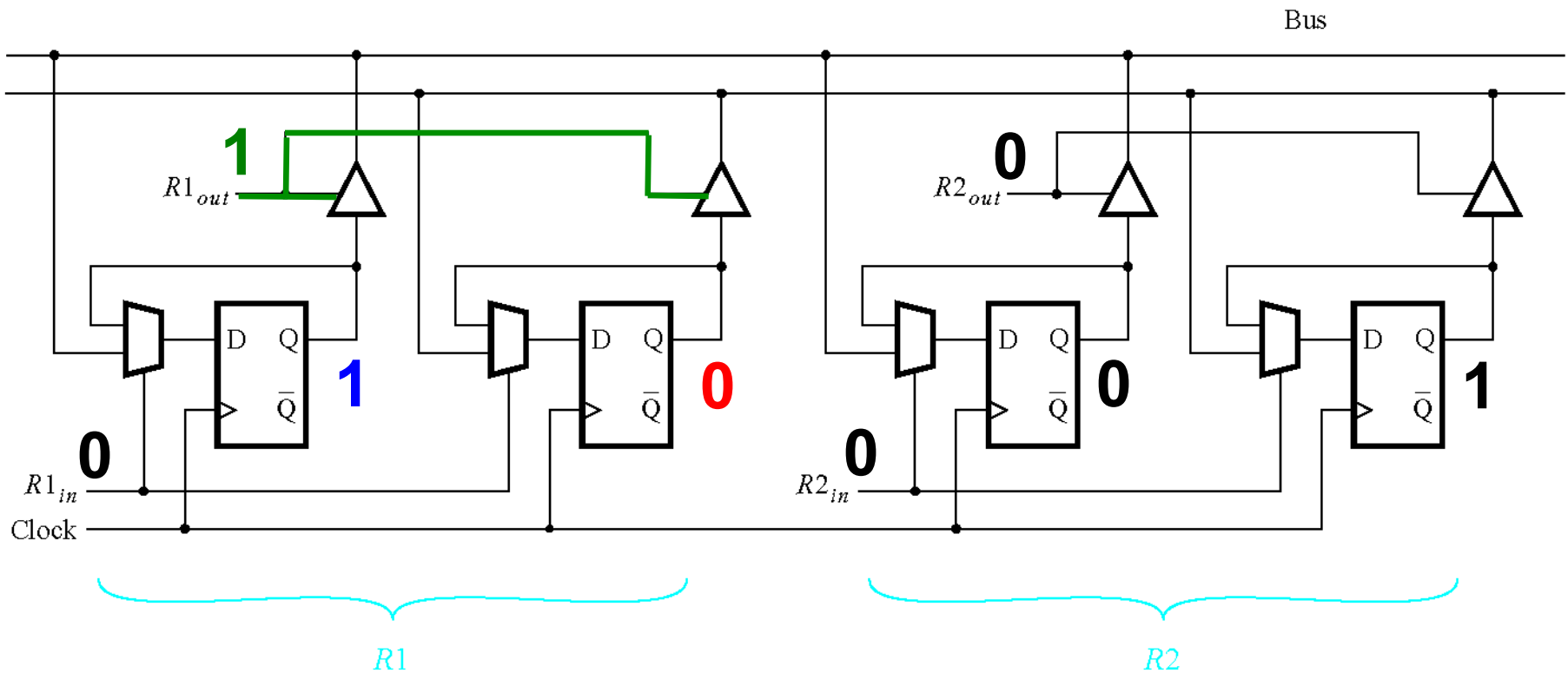


$R1_{out}$ is set to 1 (this enables reading from register 1).

Moving the Contents of R1 to R2

 


The bits of R1 are now on the data bus (2-bit data bus in this case).

Moving the Contents of R1 to R2

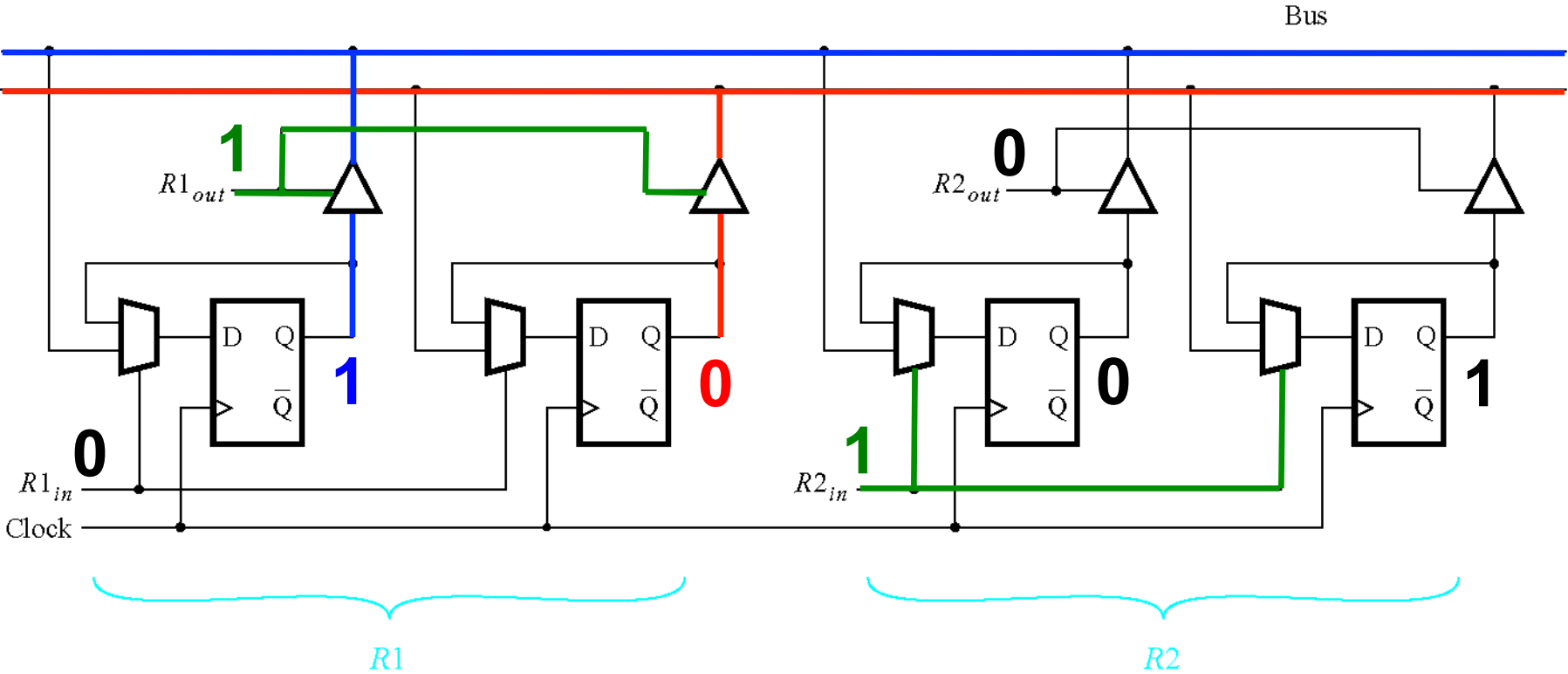


R2_{in} is set to 1 (this enables writing to register 2).

Moving the Contents of R1 to R2

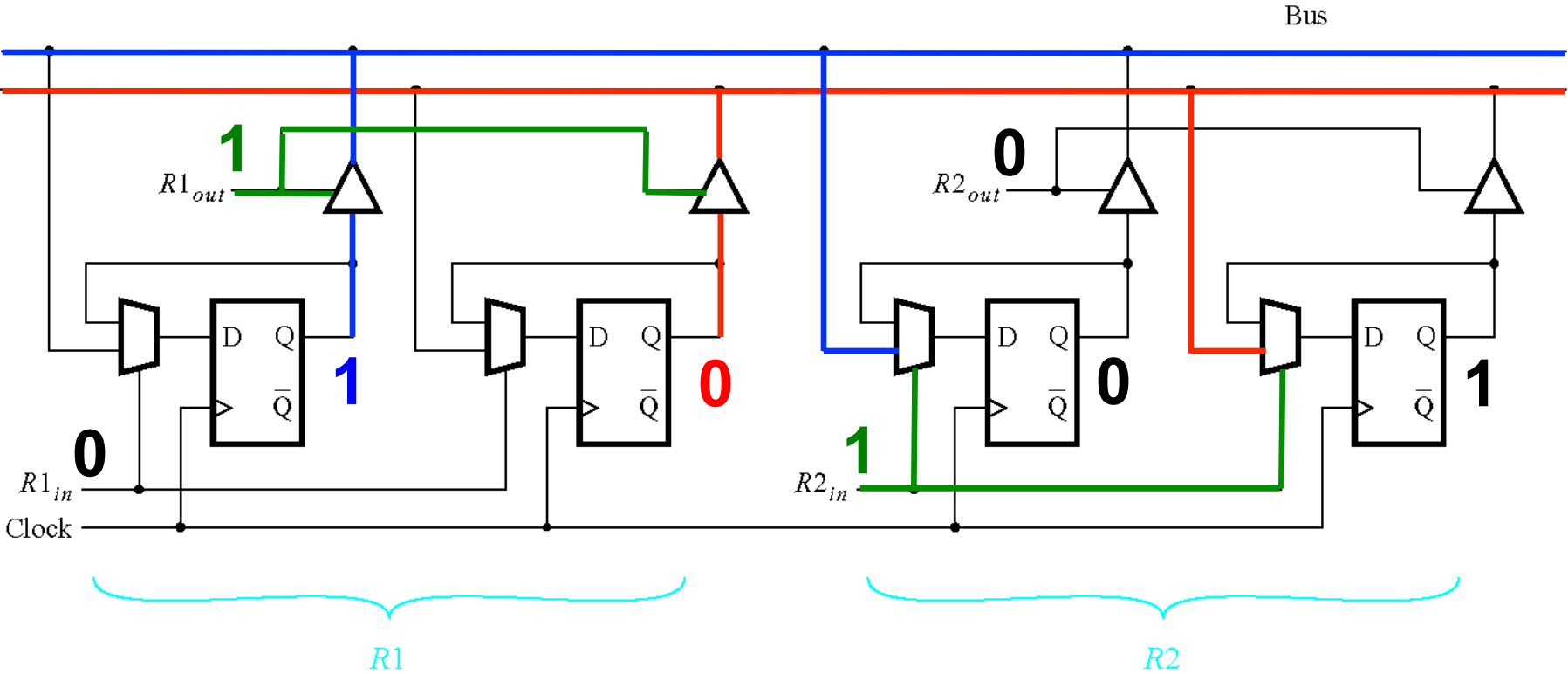


The bits of R1 are still on the bus and they propagate to the multiplexers...

Moving the Contents of R1 to R2

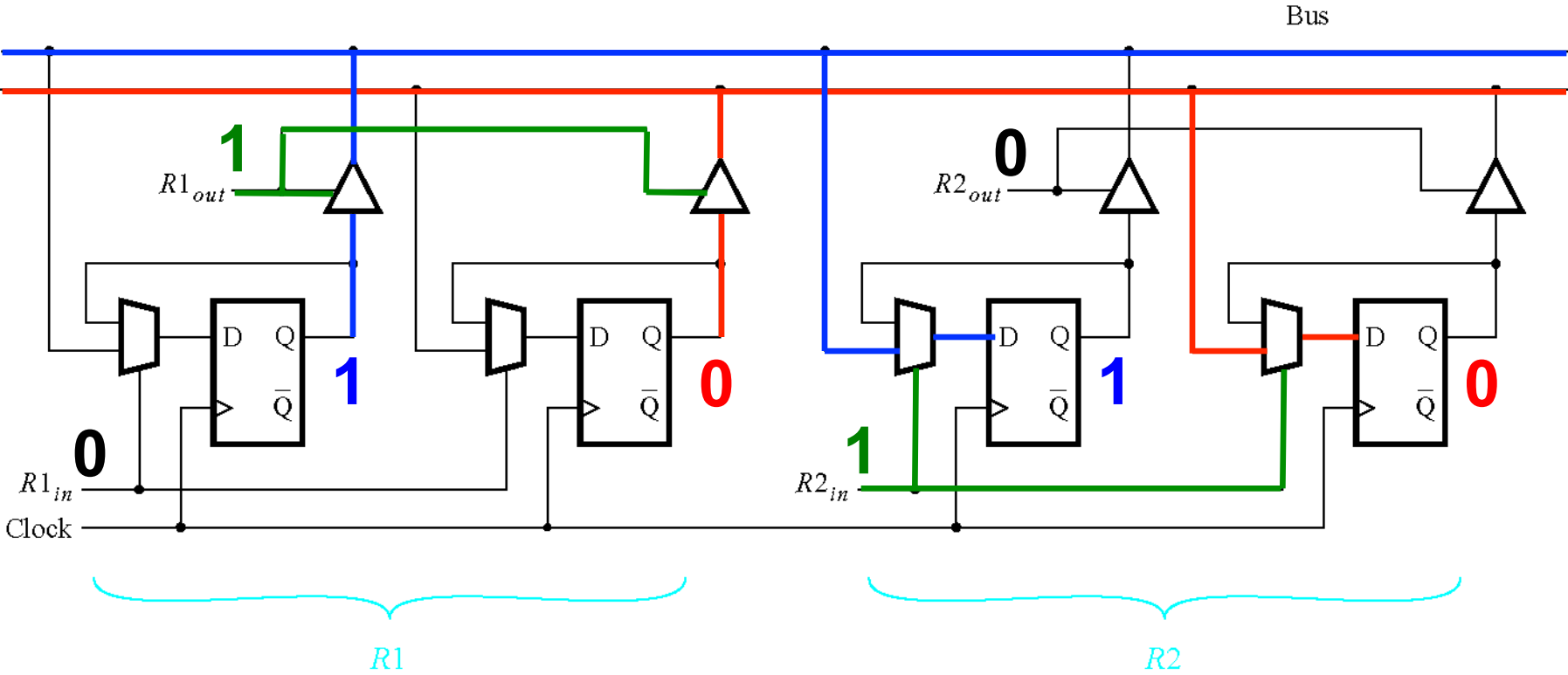


... and on the next positive clock edge to the outputs of the flip-flops of R2.

Moving the Contents of R1 to R2

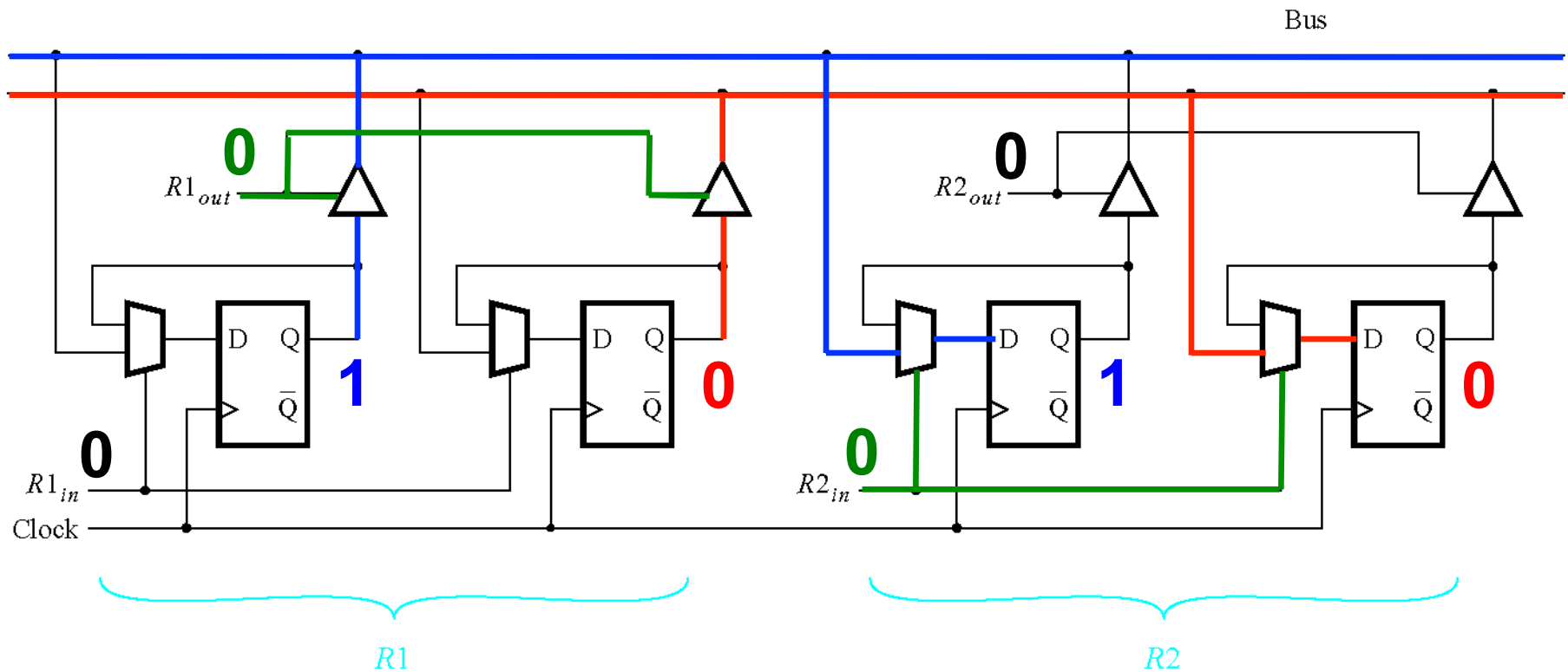


After the copy is complete $R1_{out}$ and $R2_{in}$ are set to 0.

Moving the Contents of R1 to R2

 

All control inputs are now disabled (no reading or writing is allowed).


Moving the Contents of R1 to R2

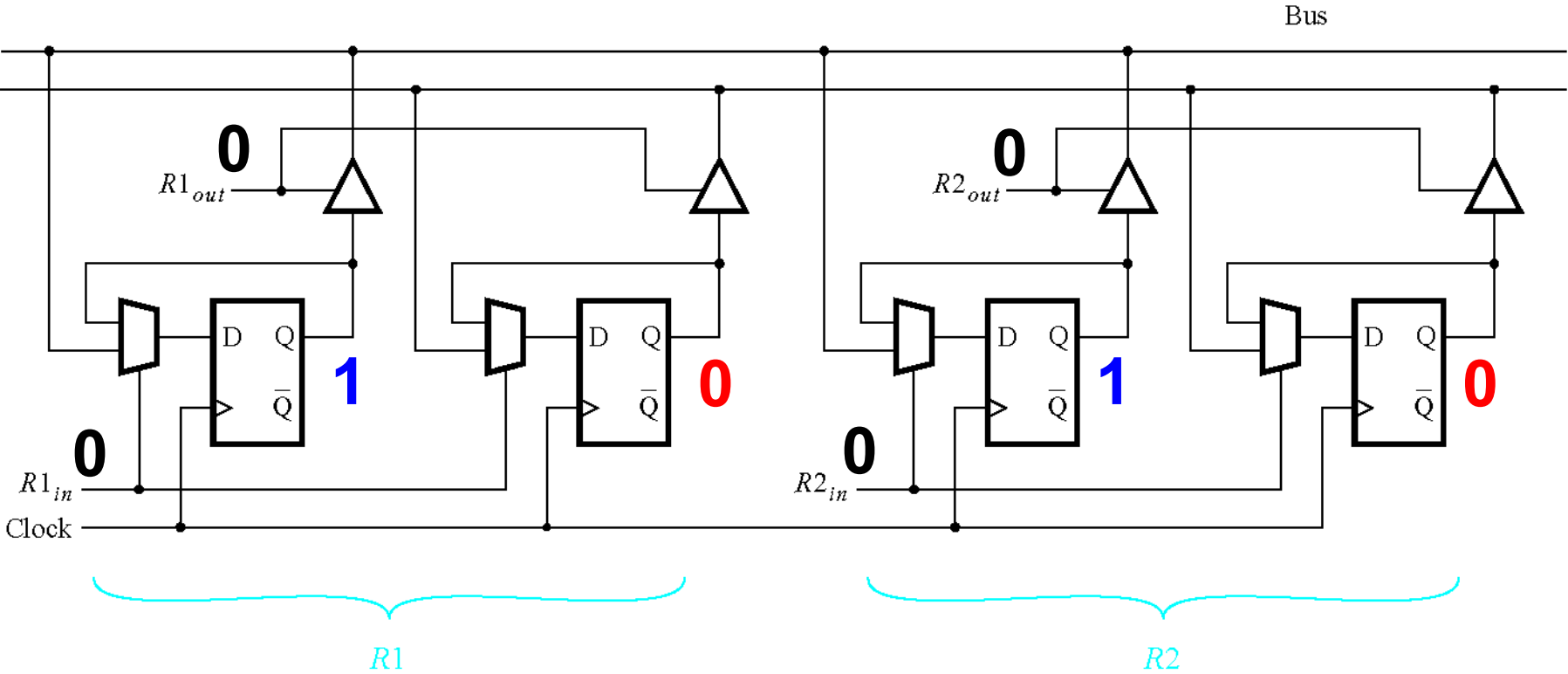

Register 2 now holds the same value as register 1.


Another Example

Loading Data From The Bus Into R2

 


Initially all control inputs are set to 0 (no reading or writing allowed).

Loading Data From The Bus Into R2

 


The number $3_{10} = 11_2$ is placed on the 2-bit data bus.

Loading Data From The Bus Into R2

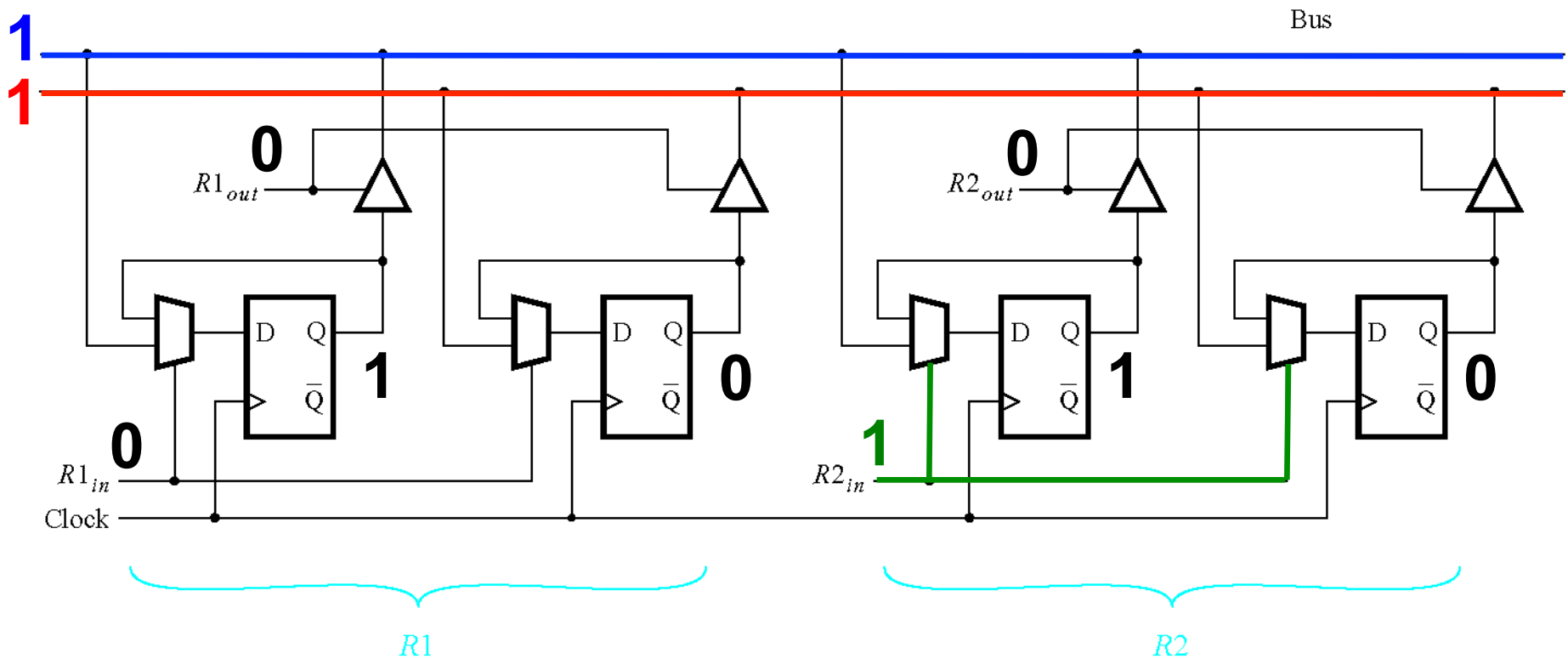


$R2_{in}$ is set to 1 (this enables writing to register 2).

Loading Data From The Bus Into R2

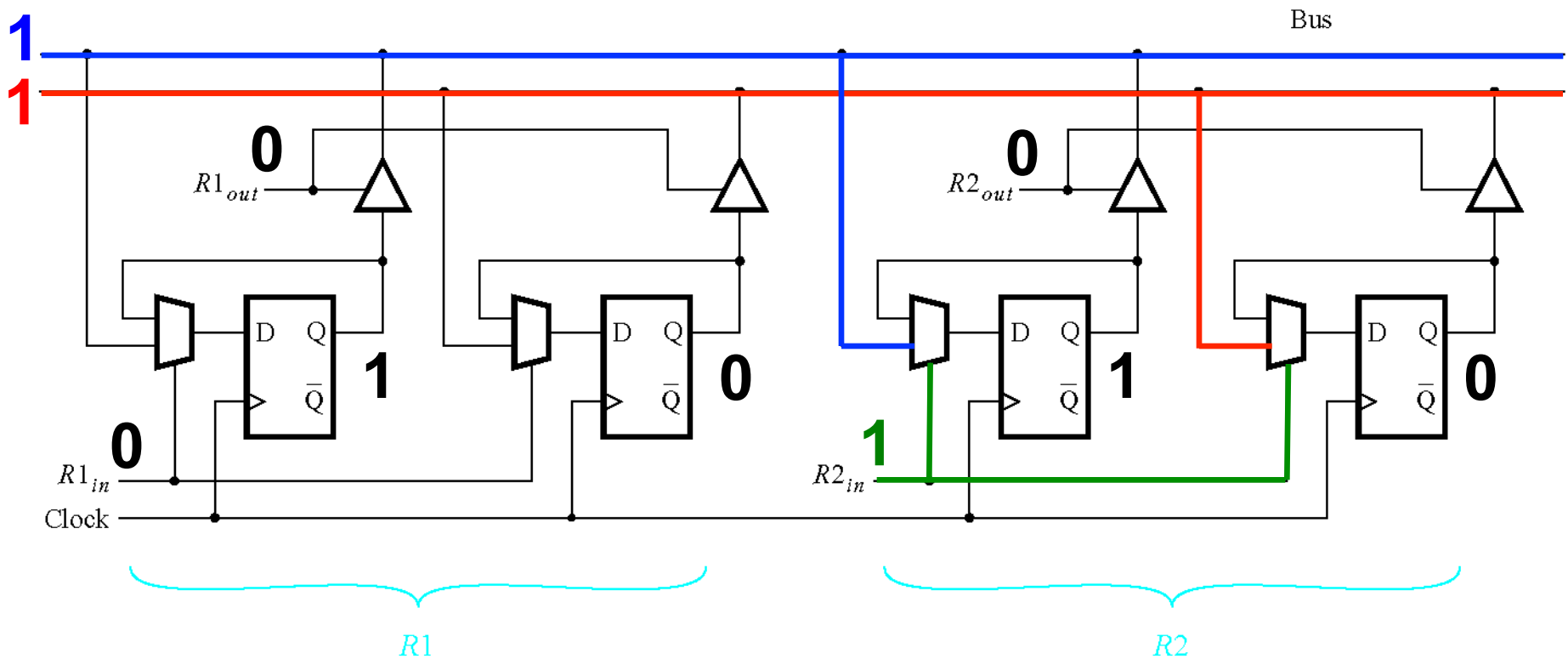


The bits of the data propagate through the multiplexers...

Loading Data From The Bus Into R2

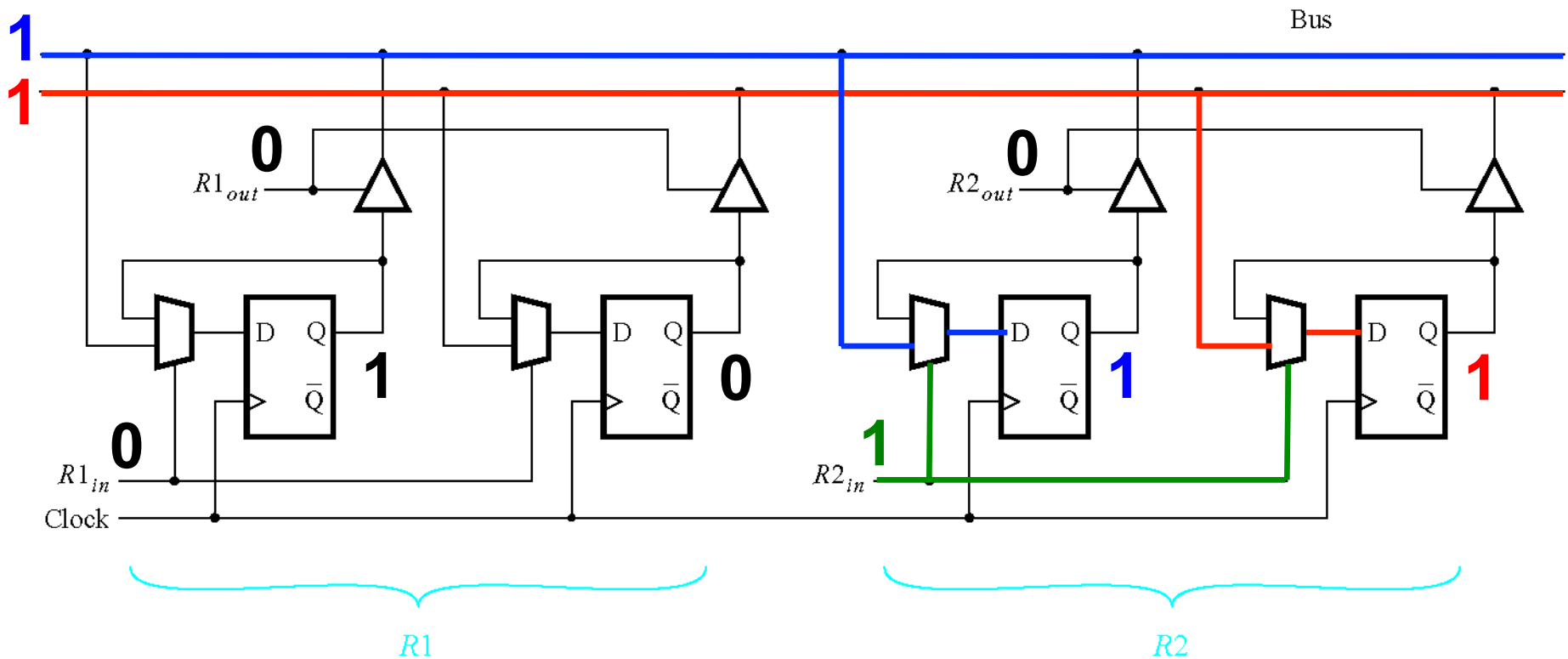


... and on the next positive clock edge to the outputs of the flip-flops of R2.

Loading Data From The Bus Into R2

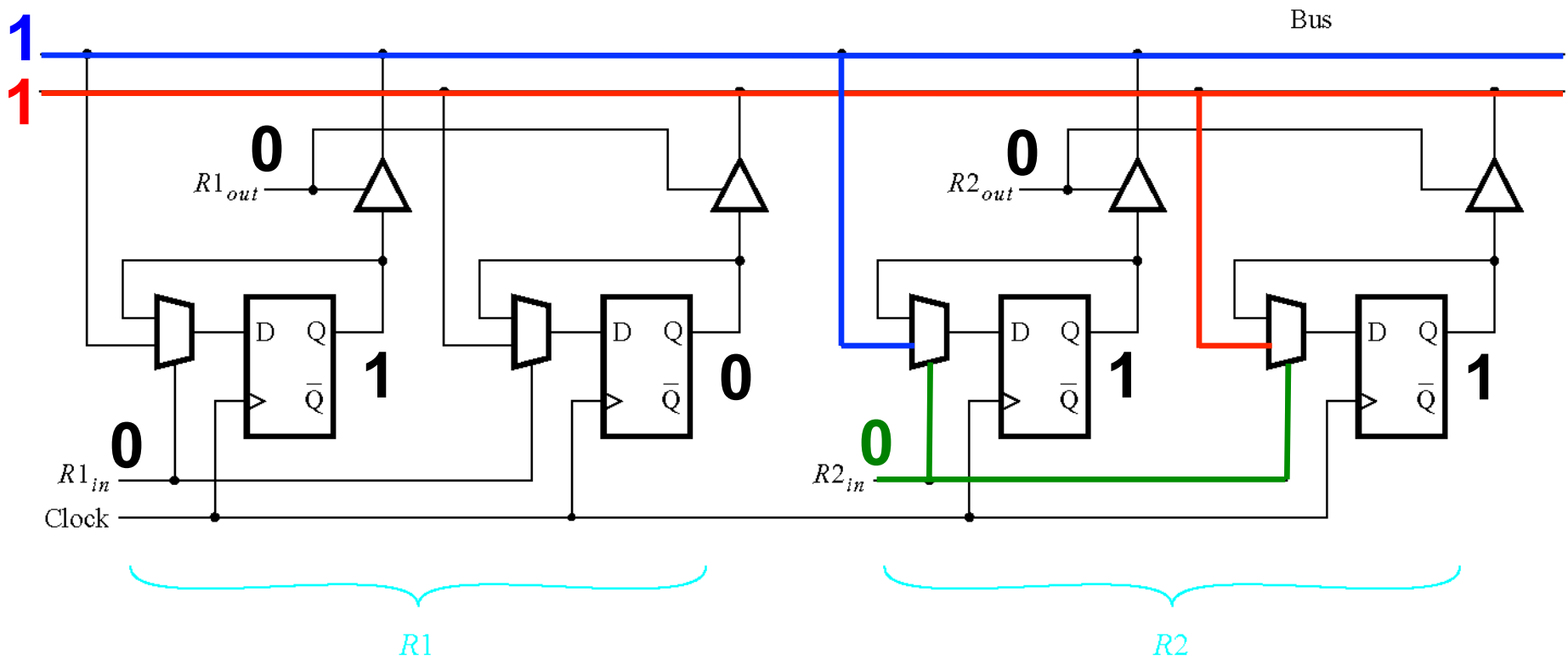

After the loading is complete $R2_{in}$ is set to 0.


Loading Data From The Bus Into R2

 

Register 2 now stores the number $3_{10} = 11_2$.


A Closer Look at the Arithmetic Logic Unit (ALU)

Arithmetic Logic Unit (ALU)

 


[Figure 7.9 from the textbook]

Two Registers

 


[Figure 7.9 from the textbook]

4-Bit Register

 


Adder/Subtractor

 


[Figure 7.9 from the textbook]

Adder/Subtractor unit

 

[Figure 3.12 from the textbook]

 The first two stages of a carry-lookahead adder




$$c_1 = g_0 + p_0 c_0$$

$$c_2 = g_1 + p_1 g_0 + p_1 p_0 c_0$$

[Figure 3.15 from the textbook]

A hierarchical carry-lookahead adder

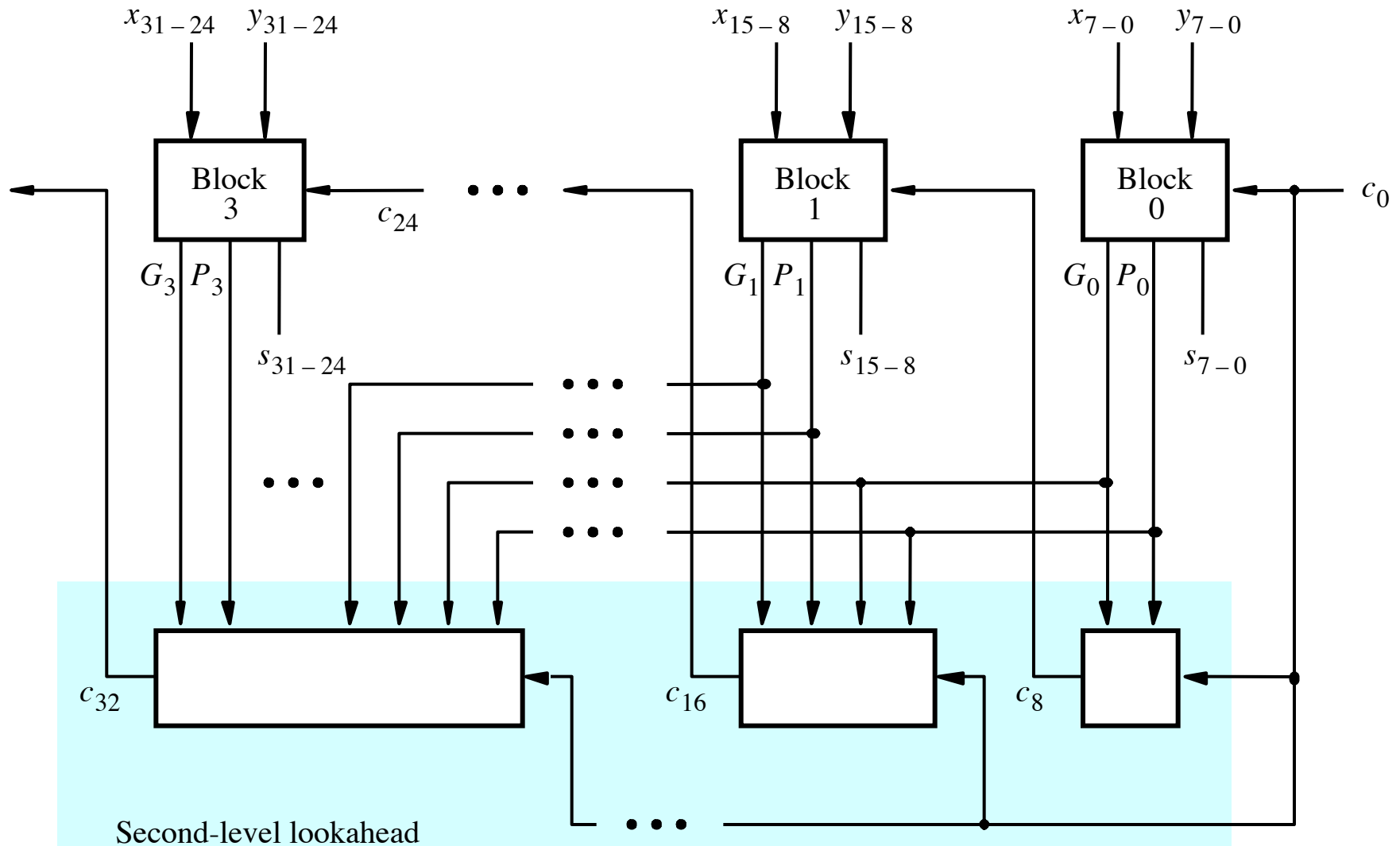


[Figure 3.17 from the textbook]

Adder/subtractor unit

- **Subtraction can be performed by simply adding the 2's complement of the second number, regardless of the signs of the two numbers.**
- **Thus, the same adder circuit can be used to perform both addition and subtraction !!!**


Adder/subtractor unit

 

[Figure 3.12 from the textbook]


XOR Tricks

control	y	out
0	0	0
0	1	1
1	0	1
1	1	0

 


XOR as a repeater

control	y	out
0	0	0
0	1	1
1	0	1
1	1	0

 


XOR as an inverter

control	y	out
0	0	0
0	1	1
1	0	1
1	1	0

 


Addition: when control = 0

 


[Figure 3.12 from the textbook]

Addition: when control = 0

 


[Figure 3.12 from the textbook]

Addition: when control = 0

 


[Figure 3.12 from the textbook]

Subtraction: when control = 1

 


[Figure 3.12 from the textbook]

Subtraction: when control = 1

 


[Figure 3.12 from the textbook]

Subtraction: when control = 1

 

[Figure 3.12 from the textbook]


Subtraction: when control = 1

 

[Figure 3.12 from the textbook]


A Closer Look at the Control Circuit

Control Circuit

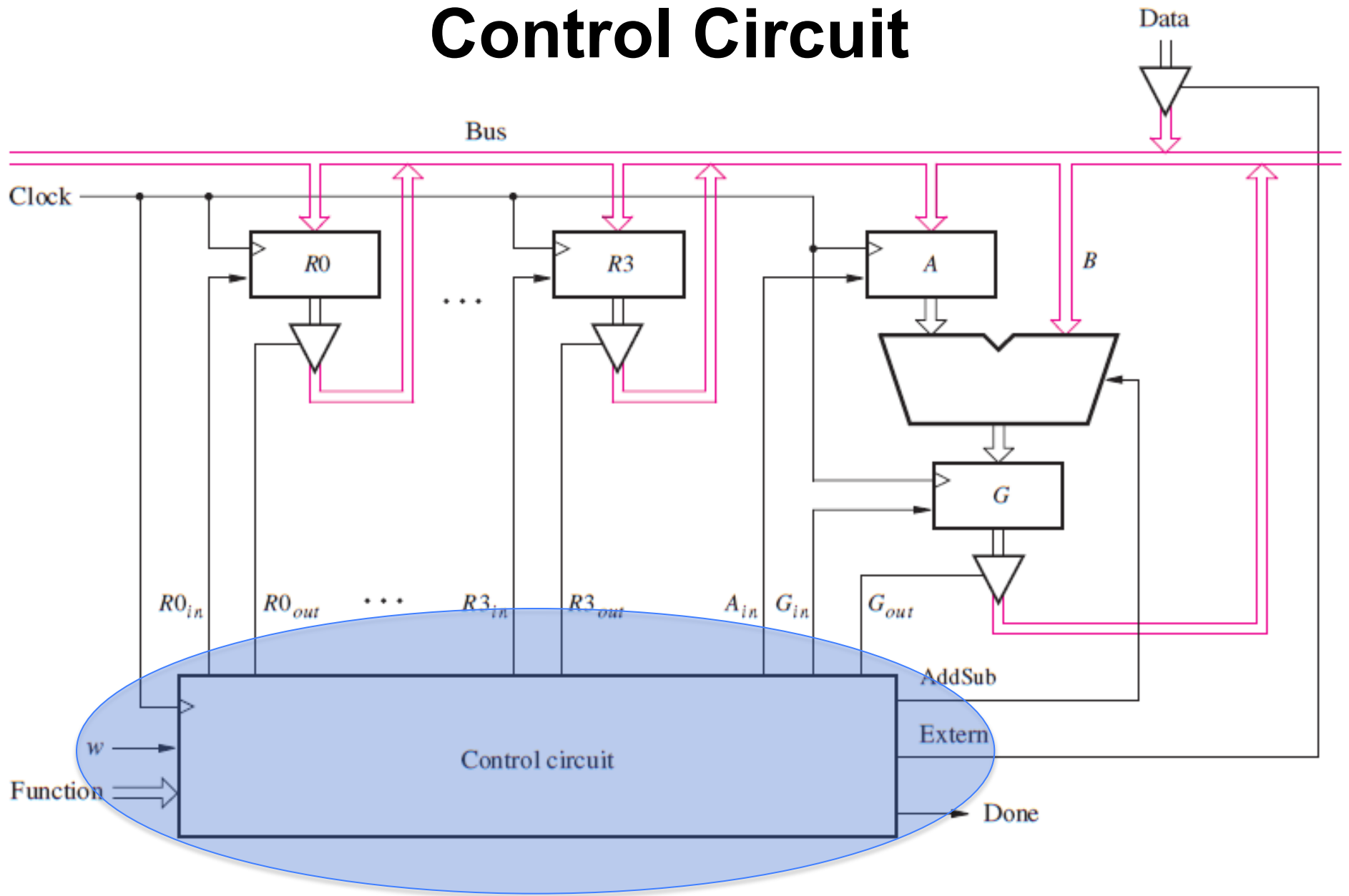

[Figure 7.9 from the textbook]

Control Signals

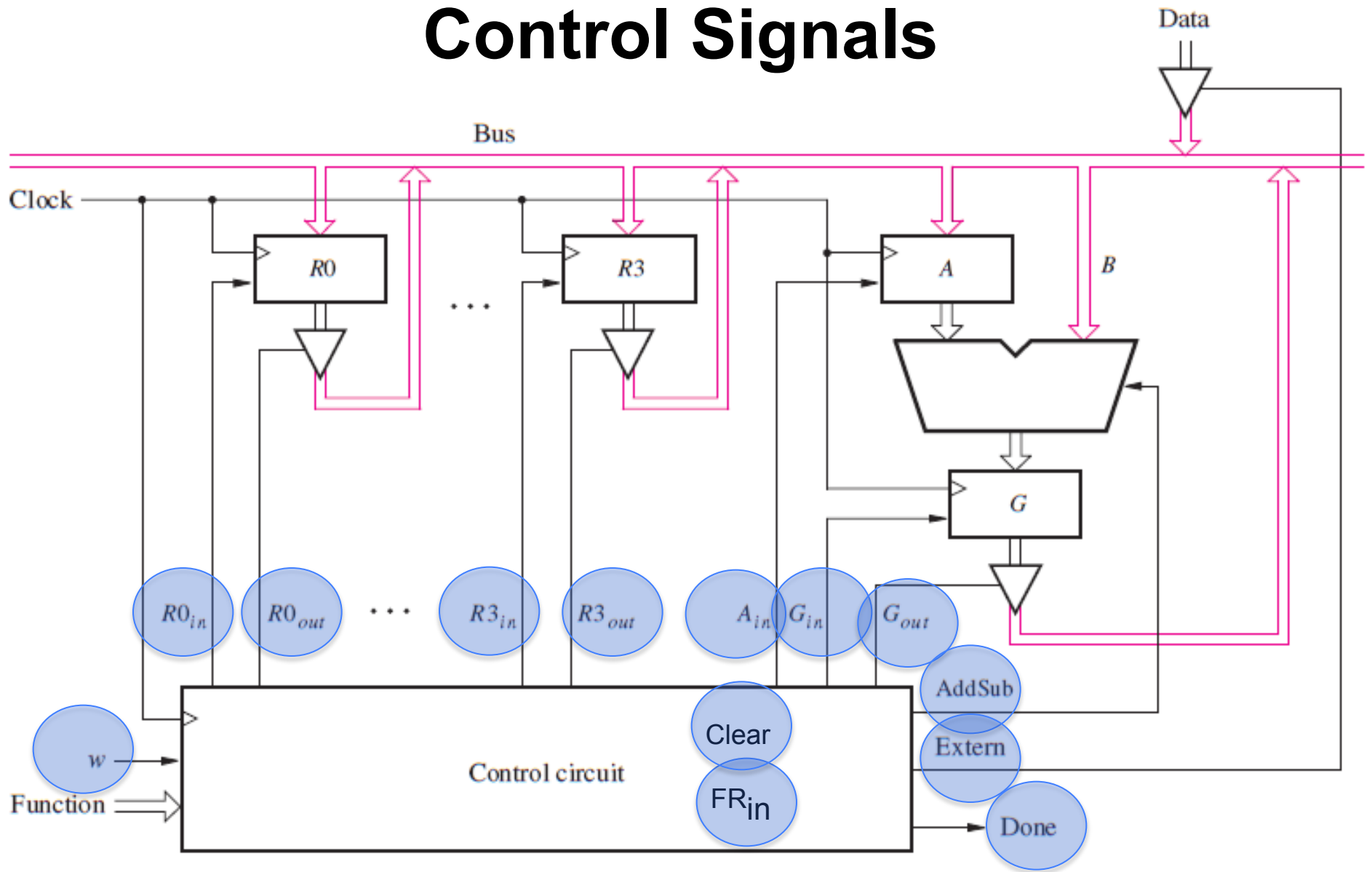

[Figure 7.9 from the textbook]

Design a FSM with input w and outputs


- $R0_{in}$
- $R0_{out}$
- $R1_{in}$
- $R1_{out}$
- $R2_{in}$
- $R2_{out}$
- $R3_{in}$
- $R3_{out}$
- A_{in}
- G_{in}
- G_{out}
- Clear
- FR_{in}
- AddSub
- Extern
- Done

Design a FSM with input w and outputs

- $R0_{in}$
- $R0_{out}$
- $R1_{in}$
- $R1_{out}$
- $R2_{in}$
- $R2_{out}$
- $R3_{in}$
- $R3_{out}$
- A_{in}
- G_{in}
- G_{out}
- **Clear**
- FR_{in}
- **AddSub**
- **Extern**
- **Done**
- T_0
- T_1
- T_2
- T_3
- I_0
- I_1
- I_2
- I_3
- X_0
- X_1
- X_2
- X_3
- Y_0
- Y_1
- Y_2
- Y_3


These are helper outputs that are one-hot encoded. They are used to simplify the expressions for the other outputs.

The function register and decoders

 

[Figure 7.11 from the textbook]

The function register and decoders

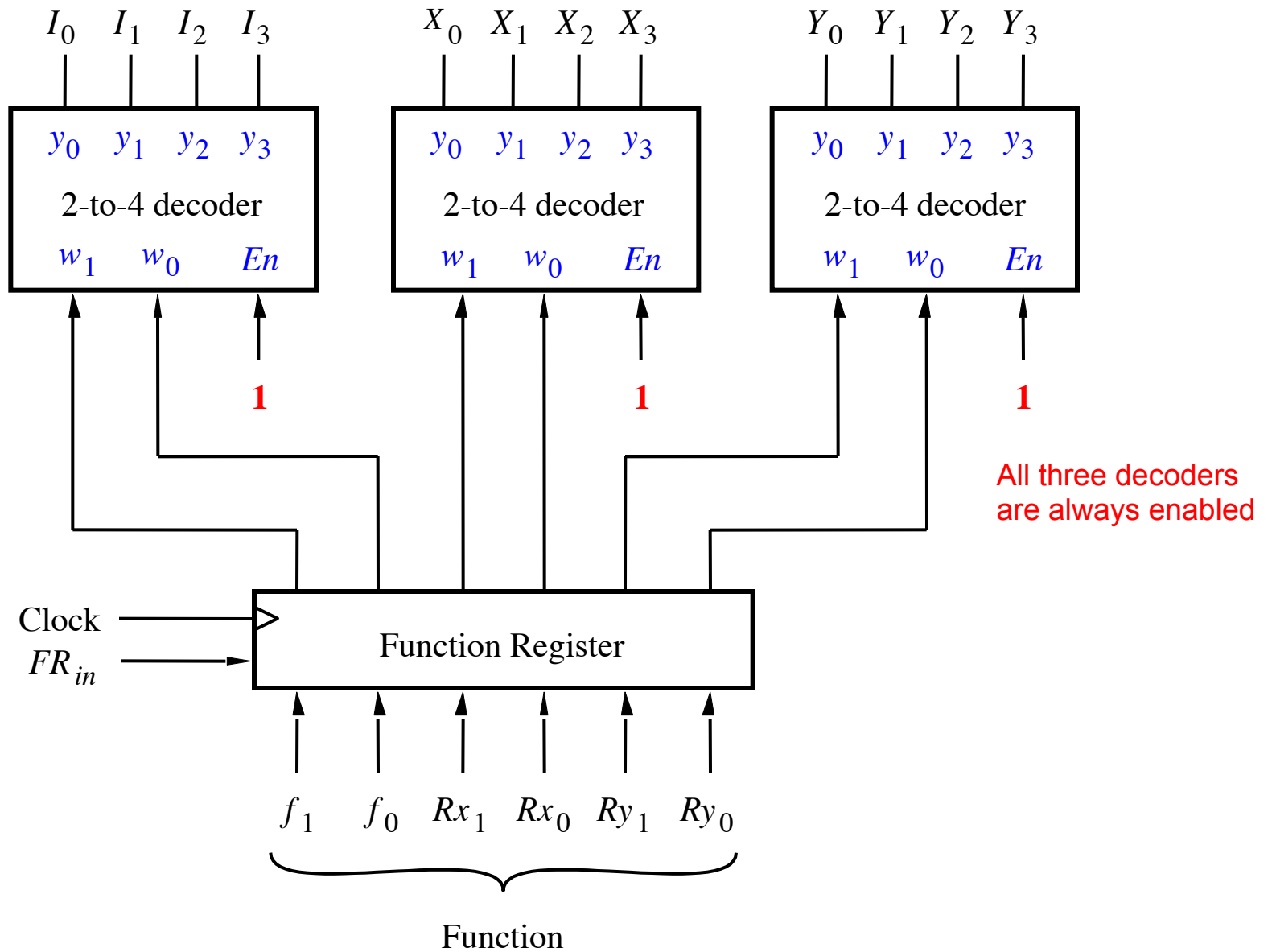

[Figure 7.11 from the textbook]

Operations performed by this processor


Operation	Function Performed
Load Rx, Data	Rx ← Data
Move Rx, Ry	Rx ← [Ry]
Add Rx, Ry	Rx ← [Rx] + [Ry]
Sub Rx, Ry	Rx ← [Rx] - [Ry]

Operations performed by this processor

Operation	Function Performed
Load Rx, Data	Rx ← Data
Move Rx, Ry	Rx ← [Ry]
Add Rx, Ry	Rx ← [Rx] + [Ry]
Sub Rx, Ry	Rx ← [Rx] - [Ry]

Where Rx and Ry can be one of four possible options: R0, R1, R2, and R3

Operations performed by this processor

 


f_1	f_0	Function
0	0	Load
0	1	Move
1	0	Add
1	1	Sub

Rx_1	Rx_0	Register
0	0	R0
0	1	R1
1	0	R2
1	1	R3

Ry_1	Ry_0	Register
0	0	R0
0	1	R1
1	0	R2
1	1	R3

Operations performed by this processor

 


f_1	f_0	Function
0	0	Load
0	1	Move
1	0	Add
1	1	Sub


Rx_1	Rx_0	Register
0	0	R0
0	1	R1
1	0	R2
1	1	R3

Ry_1	Ry_0	Register
0	0	R0
0	1	R1
1	0	R2
1	1	R3


The function register and decoders

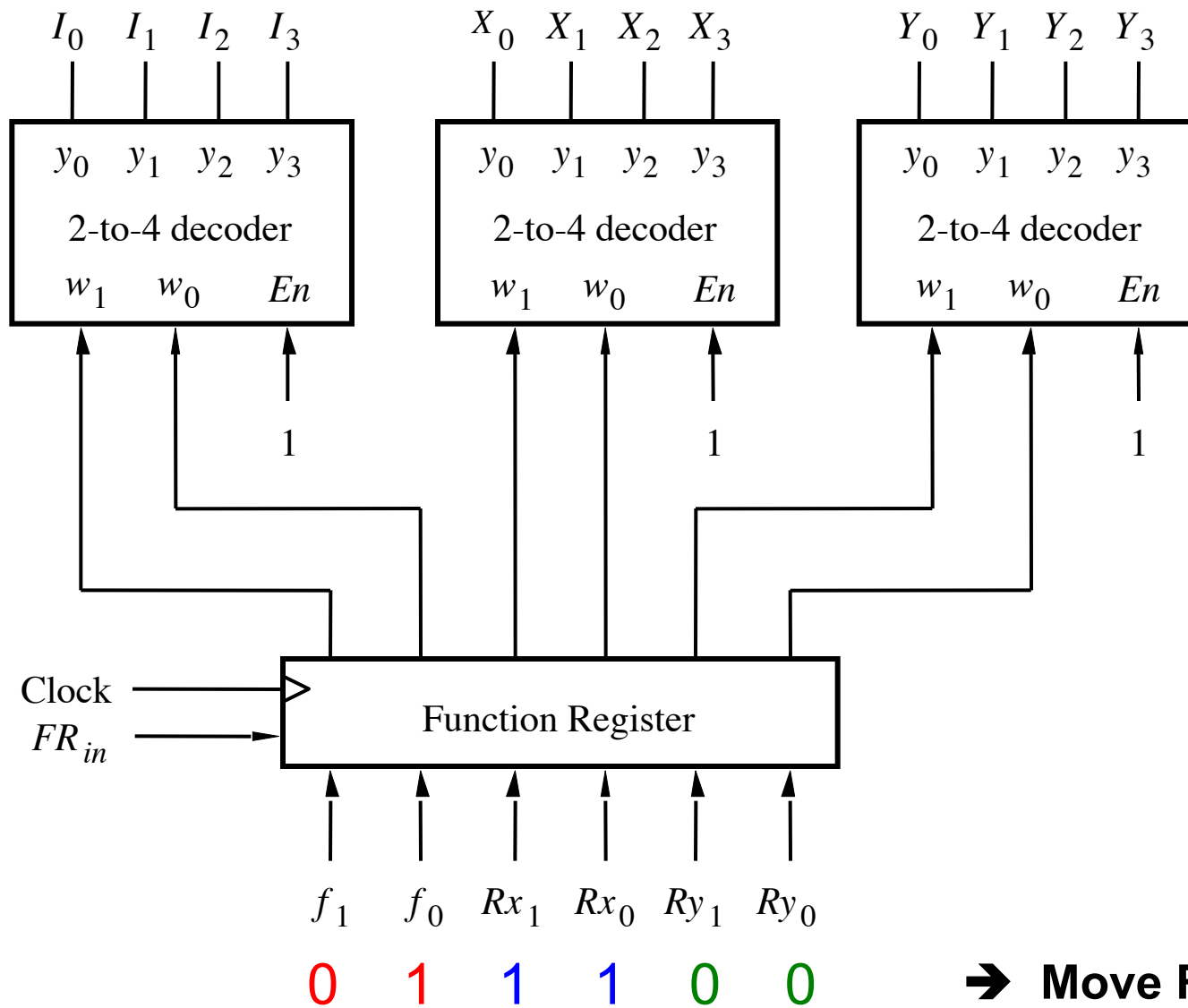


The function register and decoders

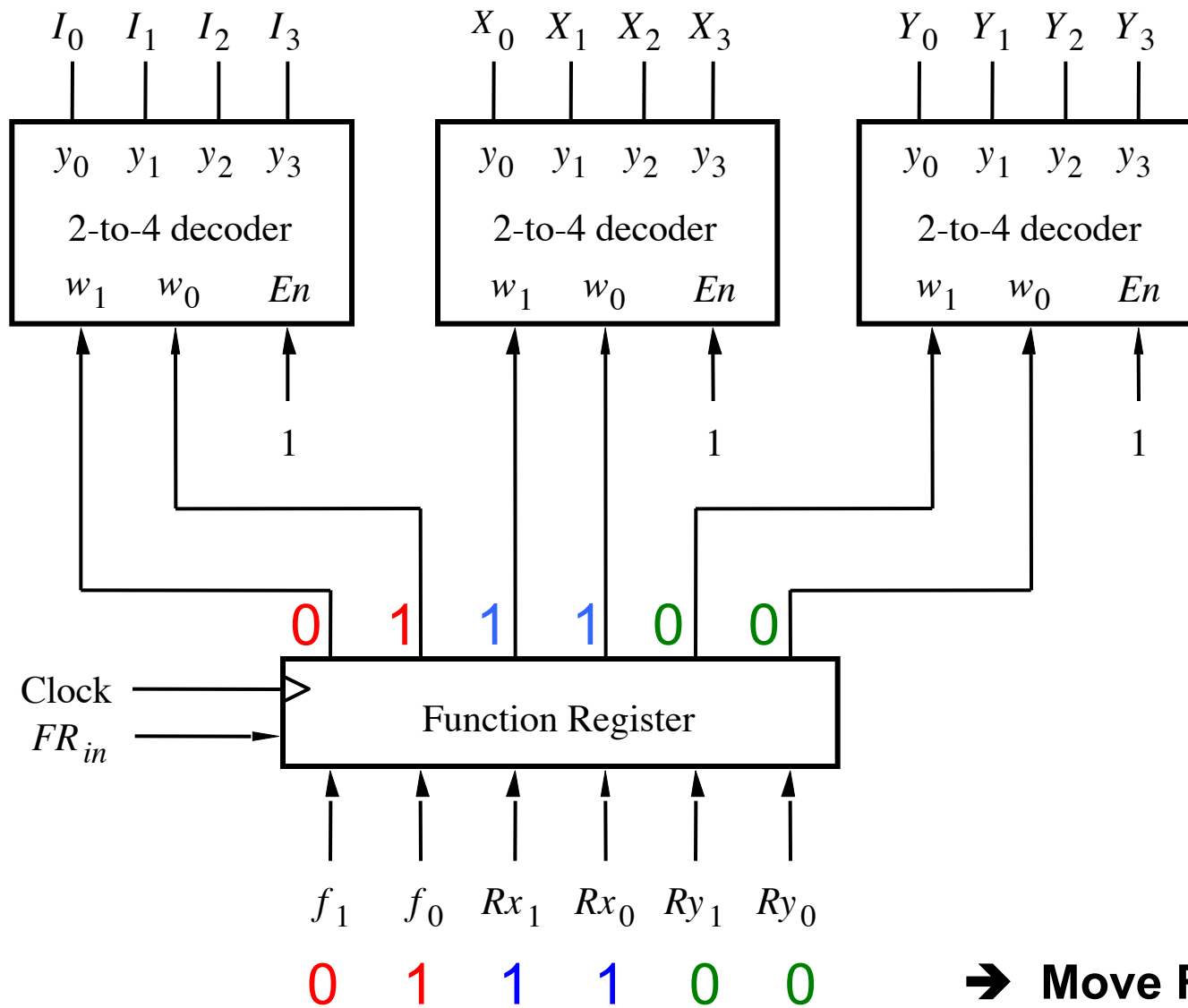


The function register and decoders

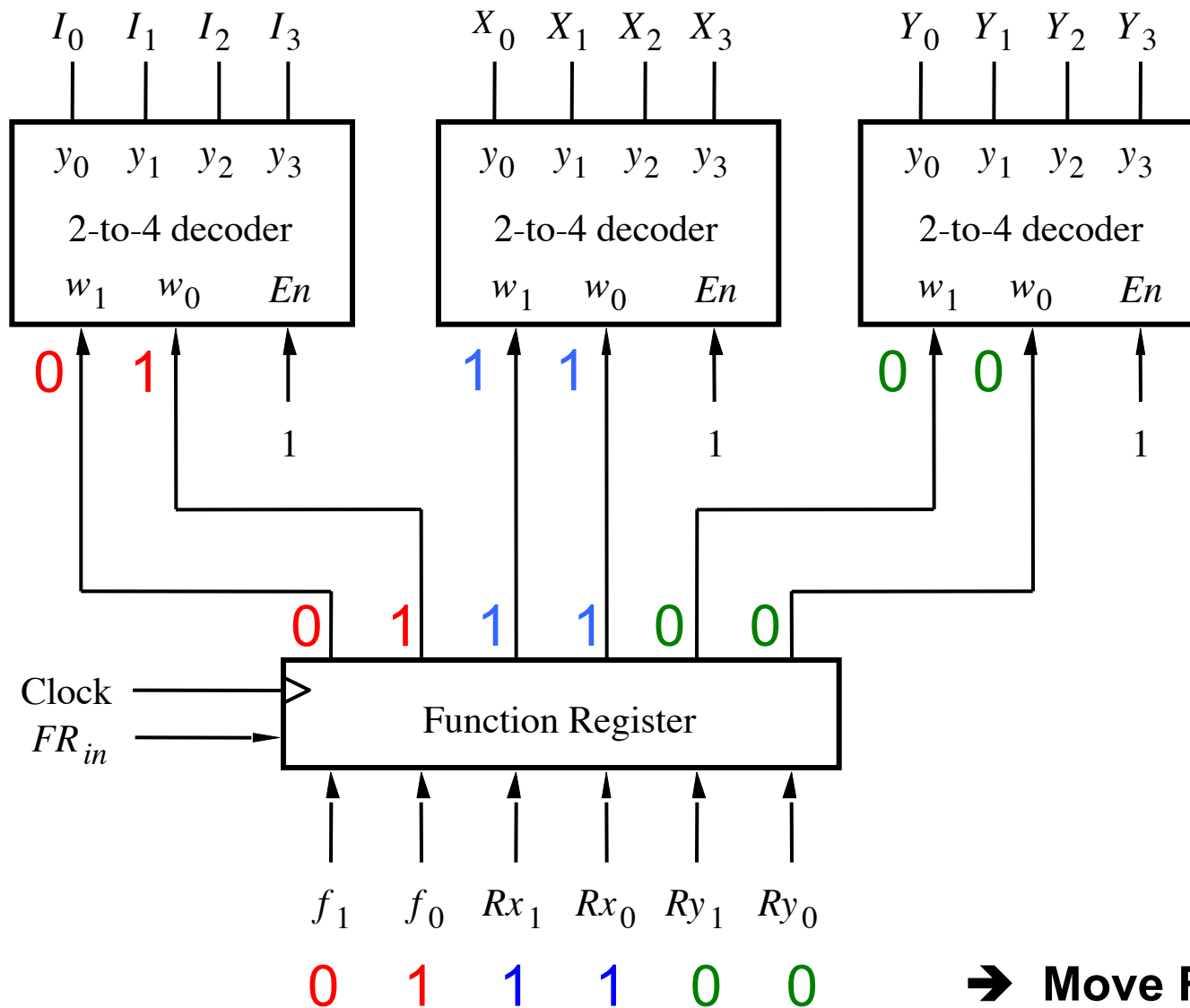


The function register and decoders

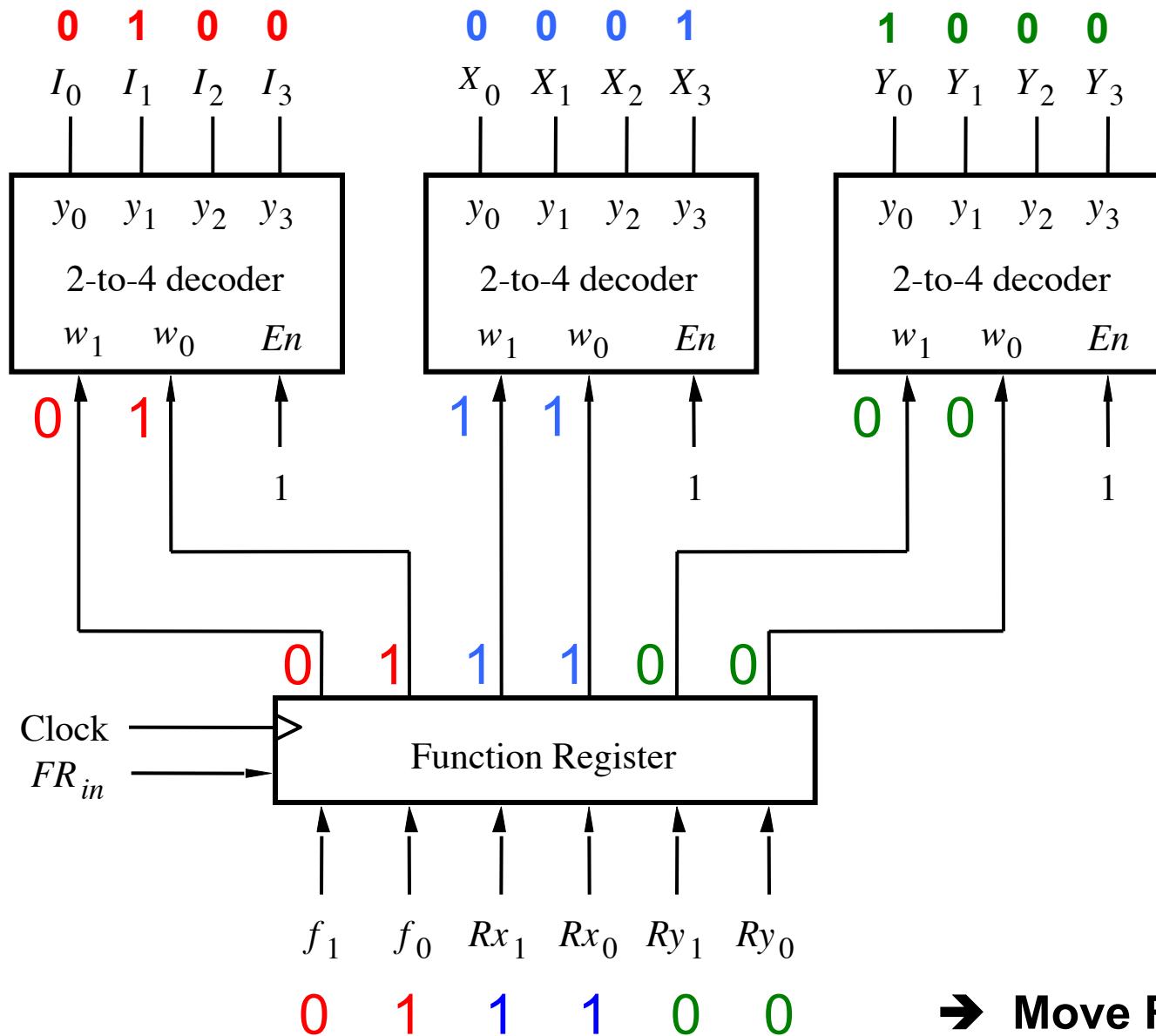

The function register and decoders

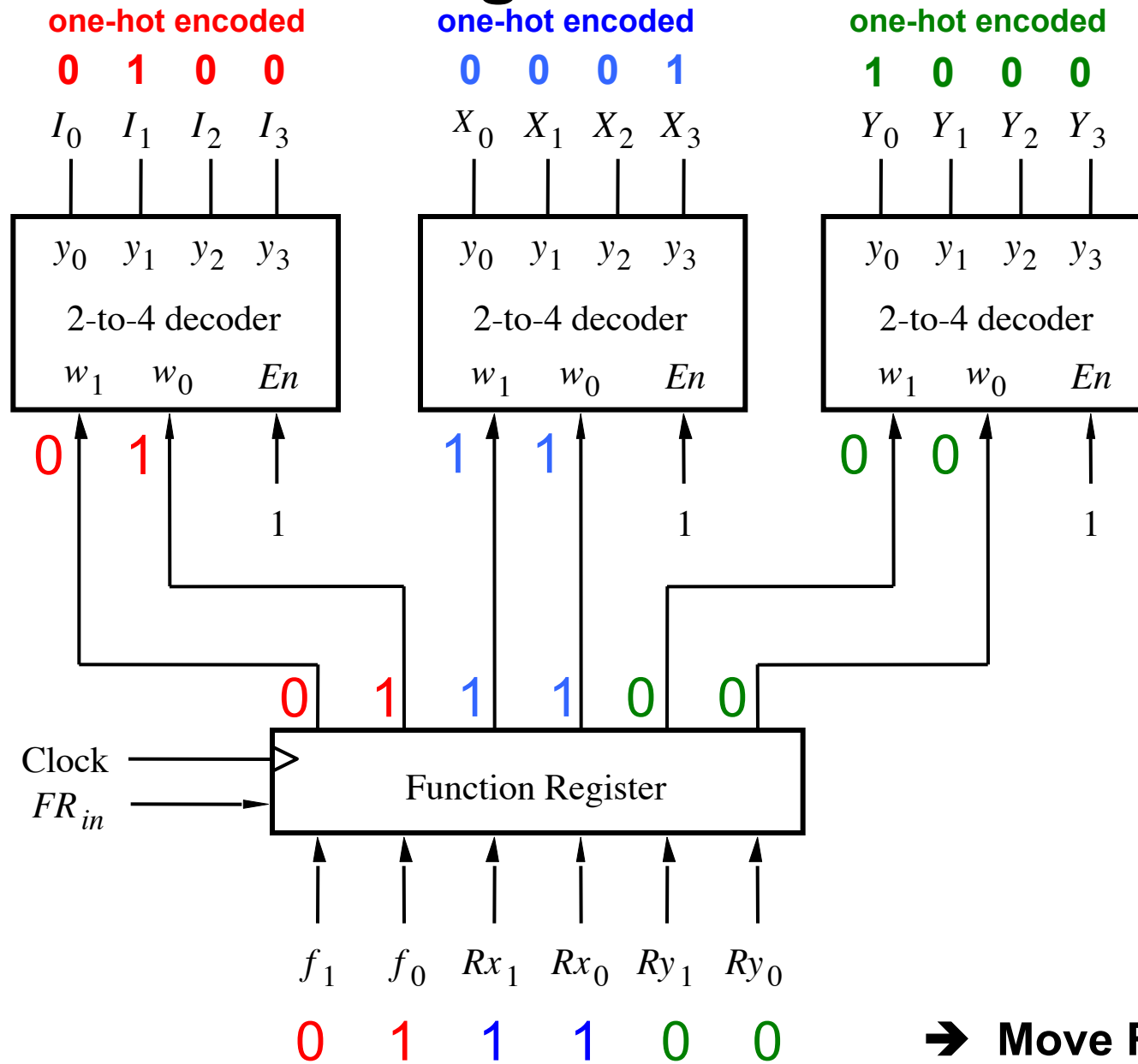

Operations performed by this processor

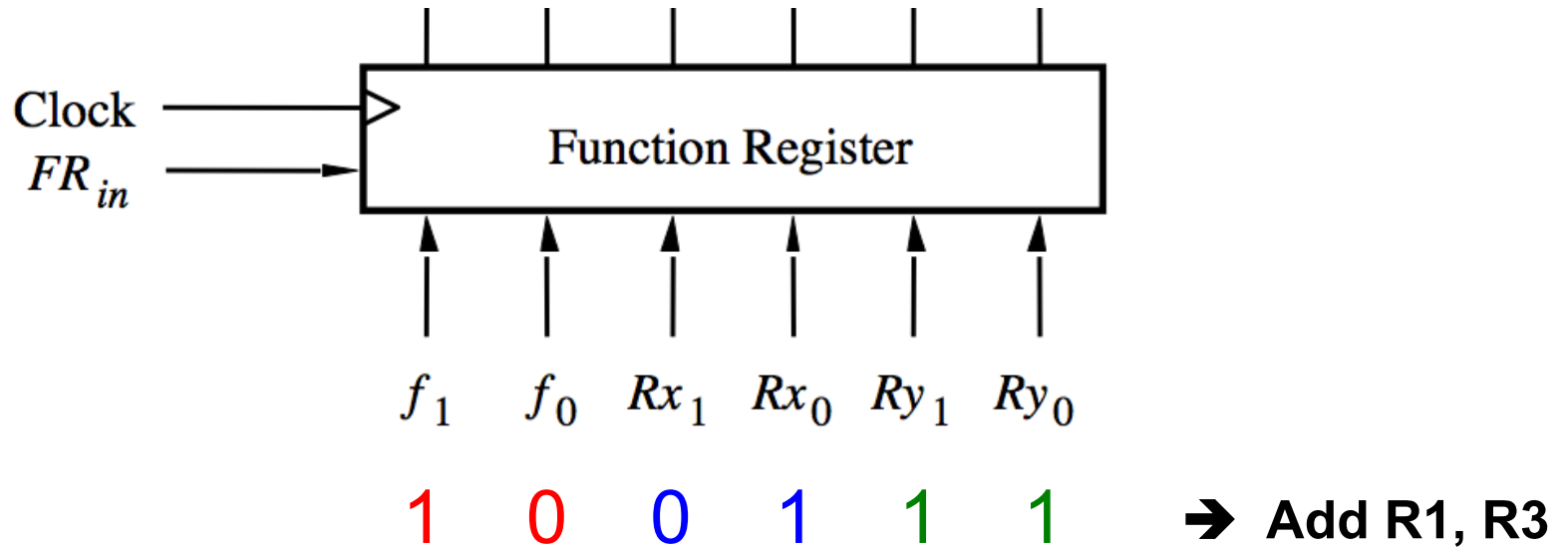


f_1	f_0	Function
0	0	Load
0	1	Move
1	0	Add
1	1	Sub

Rx_1	Rx_0	Register
0	0	R0
0	1	R1
1	0	R2
1	1	R3

Ry_1	Ry_0	Register
0	0	R0
0	1	R1
1	0	R2
1	1	R3

Operations performed by this processor

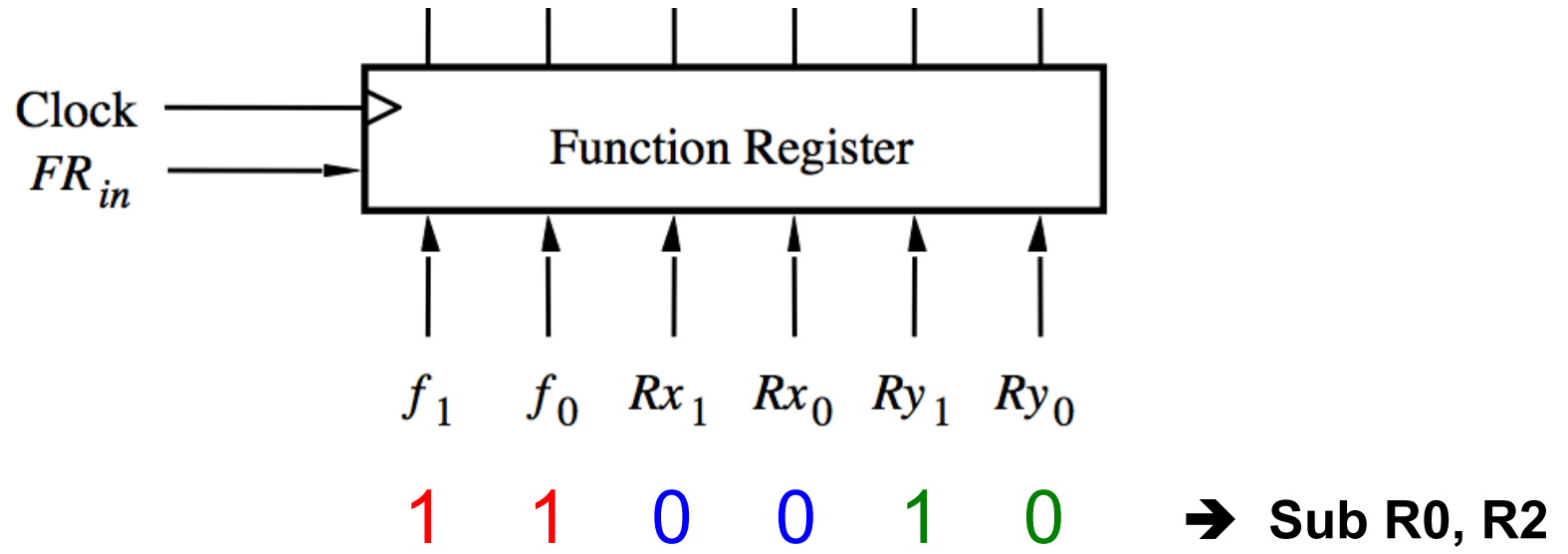


f_1	f_0	Function
0	0	Load
0	1	Move
1	0	Add
1	1	Sub

Rx_1	Rx_0	Register
0	0	R0
0	1	R1
1	0	R2
1	1	R3

Ry_1	Ry_0	Register
0	0	R0
0	1	R1
1	0	R2
1	1	R3

Operations performed by this processor

 

0 0 1 0 X X → Load R2, Data


f_1	f_0	Function
0	0	Load
0	1	Move
1	0	Add
1	1	Sub

Rx_1	Rx_0	Register
0	0	R0
0	1	R1
1	0	R2
1	1	R3

Ry_1	Ry_0	Register
0	0	R0
0	1	R1
1	0	R2
1	1	R3

Similar Encoding is Used by Modern Chips

MIPS32 Add Immediate Instruction

 

Equivalent mnemonic:

addi \$r1, \$r2, 350

Sample Assembly Language Program For This Processor

```
Move   R3, R0  
Add    R1, R3  
Sub    R0, R2  
Load   R2, Data
```

Machine Language vs Assembly Language

Machine Language	Assembly Language	Meaning / Interpretation
011100	Move R3, R0	R3 ← [R0]
100111	Add R1, R3	R1 ← [R1] + [R3]
110010	Sub R0, R2	R0 ← [R0] - [R2]
001000	Load R2, Data	R2 ← Data

Machine Language vs Assembly Language

Machine Language	Assembly Language	Meaning / Interpretation
011100	Move R3, R0	R3 ← [R0]
100111	Add R1, R3	R1 ← [R1] + [R3]
110010	Sub R0, R2	R0 ← [R0] - [R2]
001000	Load R2, Data	R2 ← Data

Machine Language vs Assembly Language

Machine Language	Assembly Language	Meaning / Interpretation
011100	Move R3, R0	R3 ← [R0]
100111	Add R1, R3	R1 ← [R1] + [R3]
110010	Sub R0, R2	R0 ← [R0] - [R2]
001000	Load R2, Data	R2 ← Data

For short, each line can be expressed as a hexadecimal number

Machine Language vs Assembly Language

Machine Language	Assembly Language	Meaning / Interpretation
1C	Move R3, R0	R3 ← [R0]
27	Add R1, R3	R1 ← [R1] + [R3]
32	Sub R0, R2	R0 ← [R0] - [R2]
08	Load R2, Data	R2 ← Data

Intel 8086

```
; _memcpy(dst, src, len)
; Copy a block of memory from one location to another.
;
; Entry stack parameters
;     [BP+6] = len, Number of bytes to copy
;     [BP+4] = src, Address of source data block
;     [BP+2] = dst, Address of target data block
;
; Return registers
;     AX = Zero
```

```
0000:1000                org     1000h        ; Start at 0000:1000h

0000:1000                _memcpy  proc
0000:1000 55              push    bp          ; Set up the call frame
0000:1001 89 E5            mov     bp,sp
0000:1003 06              push    es          ; Save ES
0000:1004 8B 4E 06        mov     cx,[bp+6]   ; Set CX = len
0000:1007 E3 11          jcxz   done        ; If len=0, return
0000:1009 8B 76 04        mov     si,[bp+4]   ; Set SI = src
0000:100C 8B 7E 02        mov     di,[bp+2]   ; Set DI = dst
0000:100F 1E            push    ds          ; Set ES = DS
0000:1010 07            pop     es

0000:1011 8A 04          loop   mov     al,[si] ; Load AL from [src]
0000:1013 88 05          mov     [di],al    ; Store AL to [dst]
0000:1015 46            inc     si          ; Increment src
0000:1016 47            inc     di          ; Increment dst
0000:1017 49            dec     cx          ; Decrement len
0000:1018 75 F7          jnz    loop        ; Repeat the loop

0000:101A 07          done  pop     es          ; Restore ES
0000:101B 5D          pop     bp          ; Restore previous call frame
0000:101C 29 C0        sub     ax,ax      ; Set AX = 0
0000:101E C3          ret                ; Return
0000:101F                end proc
```

Intel 8086

Memory Address

```
0000:1000                                org      1000h          ; Start at 0000:1000h

0000:1000                                _memcpy  proc
0000:1000 55                                push    bp             ; Set up the call frame
0000:1001 89 E5                                mov     bp,sp
0000:1003 06                                push    es             ; Save ES
0000:1004 8B 4E 06                                mov     cx,[bp+6]      ; Set CX = len
0000:1007 E3 11                                jcxz   done            ; If len=0, return
0000:1009 8B 76 04                                mov     si,[bp+4]      ; Set SI = src
0000:100C 8B 7E 02                                mov     di,[bp+2]      ; Set DI = dst
0000:100F 1E                                push    ds             ; Set ES = DS
0000:1010 07                                pop     es

0000:1011 8A 04                                loop   mov     al,[si]  ; Load AL from [src]
0000:1013 88 05                                mov     [di],al        ; Store AL to [dst]
0000:1015 46                                inc     si              ; Increment src
0000:1016 47                                inc     di              ; Increment dst
0000:1017 49                                dec     cx              ; Decrement len
0000:1018 75 F7                                jnz    loop            ; Repeat the loop

0000:101A 07                                done   pop     es        ; Restore ES
0000:101B 5D                                pop     bp             ; Restore previous call frame
0000:101C 29 C0                                sub     ax,ax          ; Set AX = 0
0000:101E C3                                ret                    ; Return
0000:101F                                end proc
```


Intel 8086

```
; _memcpy(dst, src, len)
; Copy a block of memory from one location to another.
;
; Entry stack parameters
;     [BP+6] = len, Number of bytes to copy
;     [BP+4] = src, Address of source data block
;     [BP+2] = dst, Address of target data block
;
; Return registers
;     AX = Zero
```

Machine Language

```
0000:1000                org      1000h      ; Start at 0000:1000h

0000:1000      _memcpy  proc
0000:1000  55          push     bp          ; Set up the call frame
0000:1001  89 E5       mov     bp,sp
0000:1003  06          push     es          ; Save ES
0000:1004  8B 4E 06    mov     cx,[bp+6]    ; Set CX = len
0000:1007  E3 11       jcxz   done         ; If len=0, return
0000:1009  8B 76 04    mov     si,[bp+4]    ; Set SI = src
0000:100C  8B 7E 02    mov     di,[bp+2]    ; Set DI = dst
0000:100F  1E          push     ds          ; Set ES = DS
0000:1010  07          pop     es

0000:1011  8A 04      loop    mov     al,[si]    ; Load AL from [src]
0000:1013  88 05      mov     [di],al      ; Store AL to [dst]
0000:1015  46          inc     si           ; Increment src
0000:1016  47          inc     di           ; Increment dst
0000:1017  49          dec     cx           ; Decrement len
0000:1018  75 F7      jnz    loop         ; Repeat the loop

0000:101A  07          done  pop     es          ; Restore ES
0000:101B  5D          pop     bp          ; Restore previous call frame
0000:101C  29 C0      sub     ax,ax        ; Set AX = 0
0000:101E  C3          ret
0000:101F                end proc
```

Intel 8086

```
; _memcpy(dst, src, len)
; Copy a block of memory from one location to another.
;
; Entry stack parameters
;     [BP+6] = len, Number of bytes to copy
;     [BP+4] = src, Address of source data block
;     [BP+2] = dst, Address of target data block
;
; Return registers
;     AX = Zero
```

Assembly Language

```
0000:1000                org     1000h           ; Start at 0000:1000h

0000:1000                _memcpy proc
0000:1000 55                push   bp              ; Set up the call frame
0000:1001 89 E5             mov    bp,sp
0000:1003 06                push   es              ; Save ES
0000:1004 8B 4E 06         mov    cx,[bp+6]       ; Set CX = len
0000:1007 E3 11            jcxz  done             ; If len=0, return
0000:1009 8B 76 04         mov    si,[bp+4]       ; Set SI = src
0000:100C 8B 7E 02         mov    di,[bp+2]       ; Set DI = dst
0000:100F 1E                push   ds              ; Set ES = DS
0000:1010 07                pop    es

0000:1011 8A 04           loop   mov    al,[si]   ; Load AL from [src]
0000:1013 88 05           mov    [di],al        ; Store AL to [dst]
0000:1015 46                inc    si              ; Increment src
0000:1016 47                inc    di              ; Increment dst
0000:1017 49                dec    cx              ; Decrement len
0000:1018 75 F7           jnz   loop            ; Repeat the loop

0000:101A 07           done   pop    es         ; Restore ES
0000:101B 5D           pop    bp              ; Restore previous call frame
0000:101C 29 C0         sub    ax,ax          ; Set AX = 0
0000:101E C3           ret                    ; Return
0000:101F                end proc
```

Intel 8086

```
; _memcpy(dst, src, len)
; Copy a block of memory from one location to another.
;
; Entry stack parameters
;     [BP+6] = len, Number of bytes to copy
;     [BP+4] = src, Address of source data block
;     [BP+2] = dst, Address of target data block
;
; Return registers
;     AX = Zero
```

Comments

```
0000:1000                org      1000h           ; Start at 0000:1000h


0000:1000                _memcpy  proc
0000:1000 55              push    bp           ; Set up the call frame
0000:1001 89 E5            mov     bp,sp
0000:1003 06              push    es           ; Save ES
0000:1004 8B 4E 06          mov     cx,[bp+6]    ; Set CX = len
0000:1007 E3 11            jcxz   done         ; If len=0, return
0000:1009 8B 76 04          mov     si,[bp+4]    ; Set SI = src
0000:100C 8B 7E 02          mov     di,[bp+2]    ; Set DI = dst
0000:100F 1E              push    ds           ; Set ES = DS
0000:1010 07              pop     es

0000:1011 8A 04            loop   mov     al,[si] ; Load AL from [src]
0000:1013 88 05            mov     [di],al     ; Store AL to [dst]
0000:1015 46              inc     si           ; Increment src
0000:1016 47              inc     di           ; Increment dst
0000:1017 49              dec     cx           ; Decrement len
0000:1018 75 F7            jnz    loop         ; Repeat the loop


0000:101A 07              done   pop     es           ; Restore ES
0000:101B 5D              pop     bp           ; Restore previous call frame
0000:101C 29 C0            sub     ax,ax        ; Set AX = 0
0000:101E C3              ret
0000:101F                end proc
```

Another Part of The Control Circuit

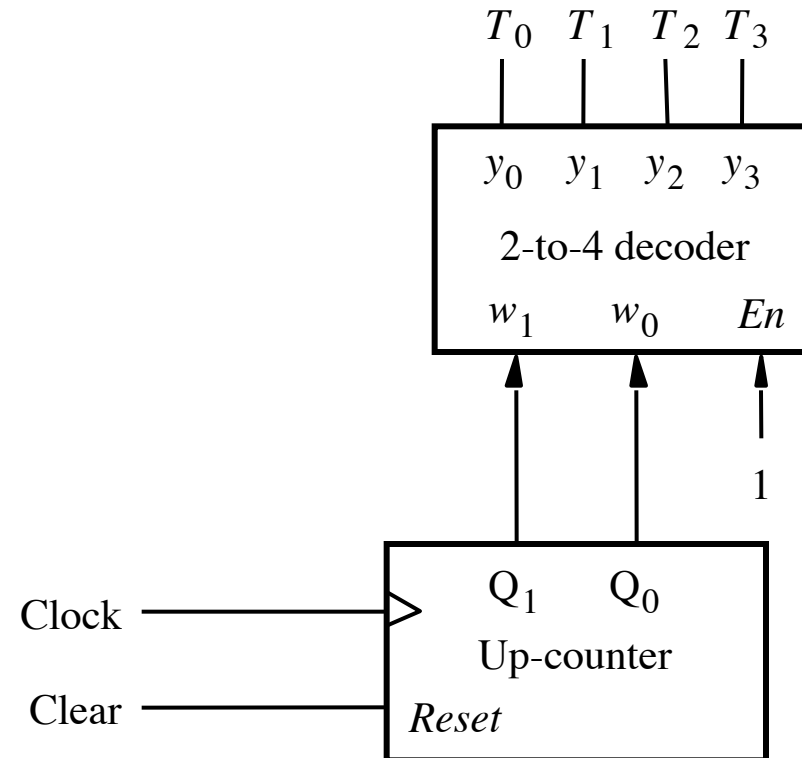
A part of the control circuit for the processor



What are the components?

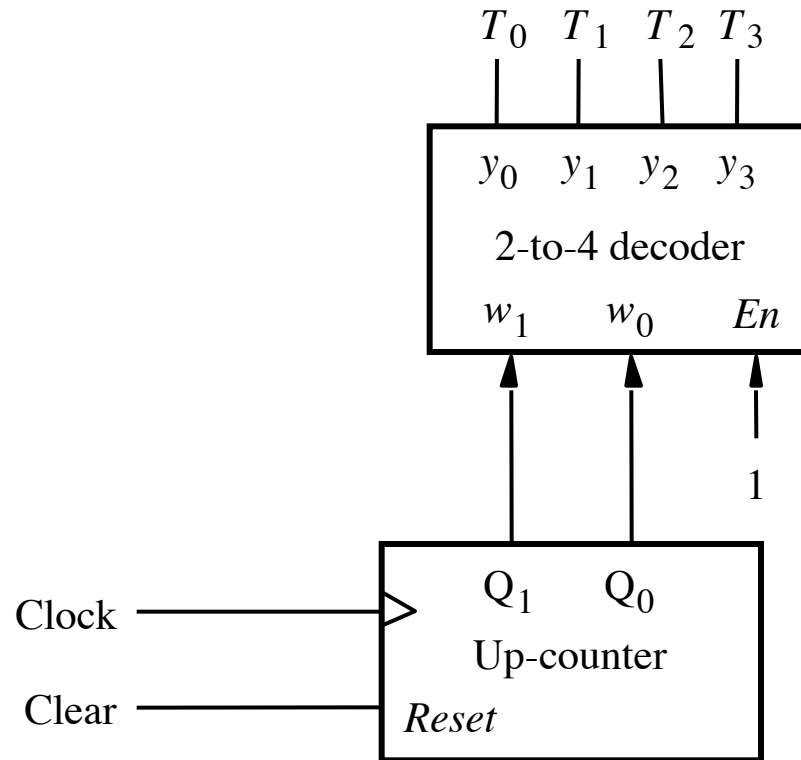


2-Bit Up-Counter

 


[Figure 7.10 from the textbook]


2-bit Synchronous Up-Counter

 

2-bit Synchronous Up-Counter with Enable

 


2-to-4 Decoder with Enable Input

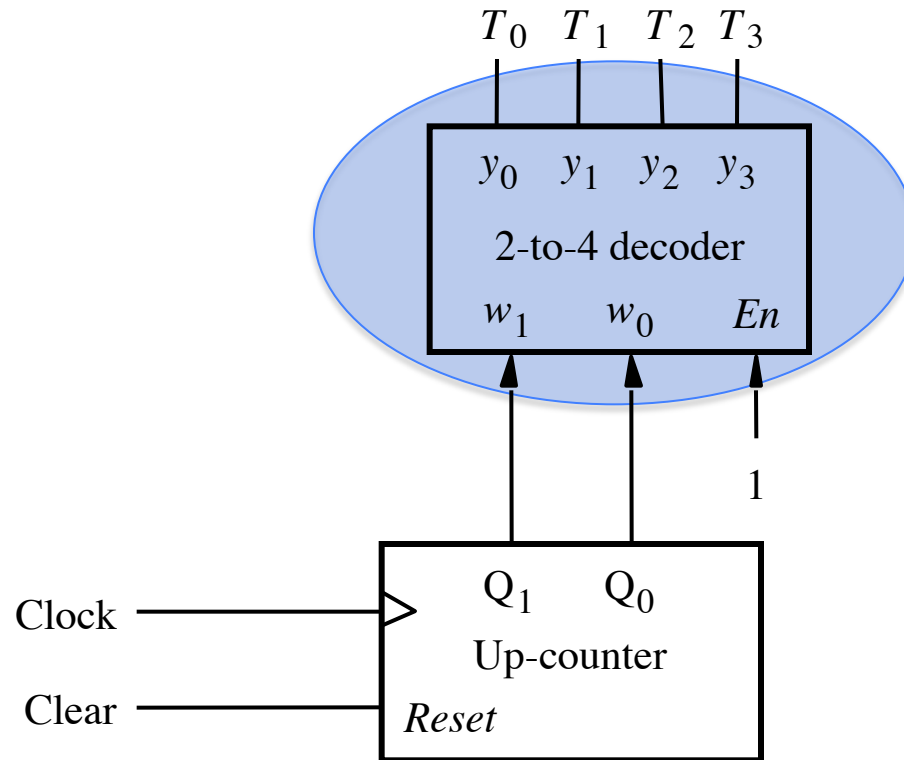


[Figure 7.10 from the textbook]

2-to-4 Decoder with an Enable Input

 


[Figure 4.13c from the textbook]

2-to-4 Decoder with an Enable Input

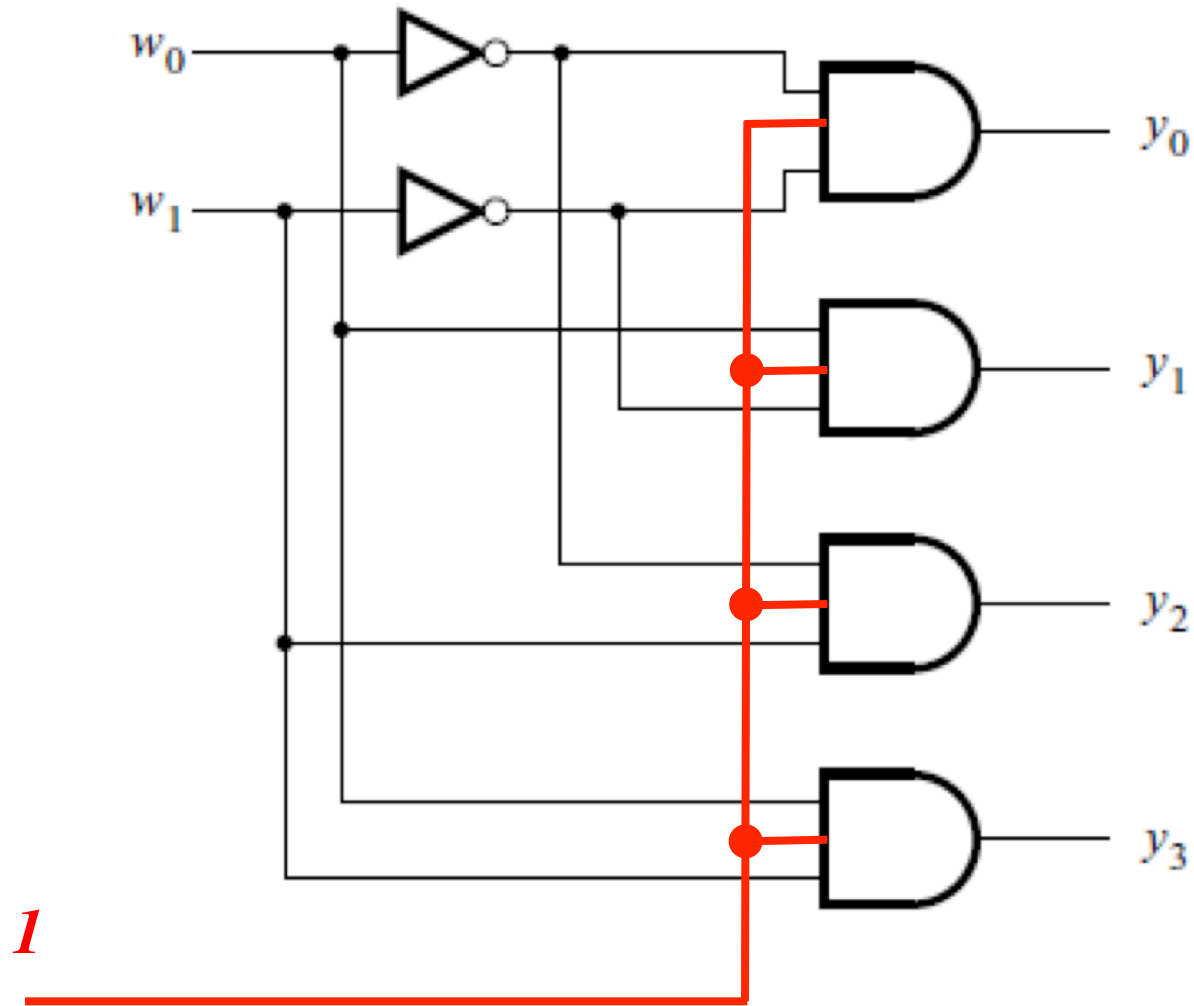


(always enabled in this example)


So How Does This Work?

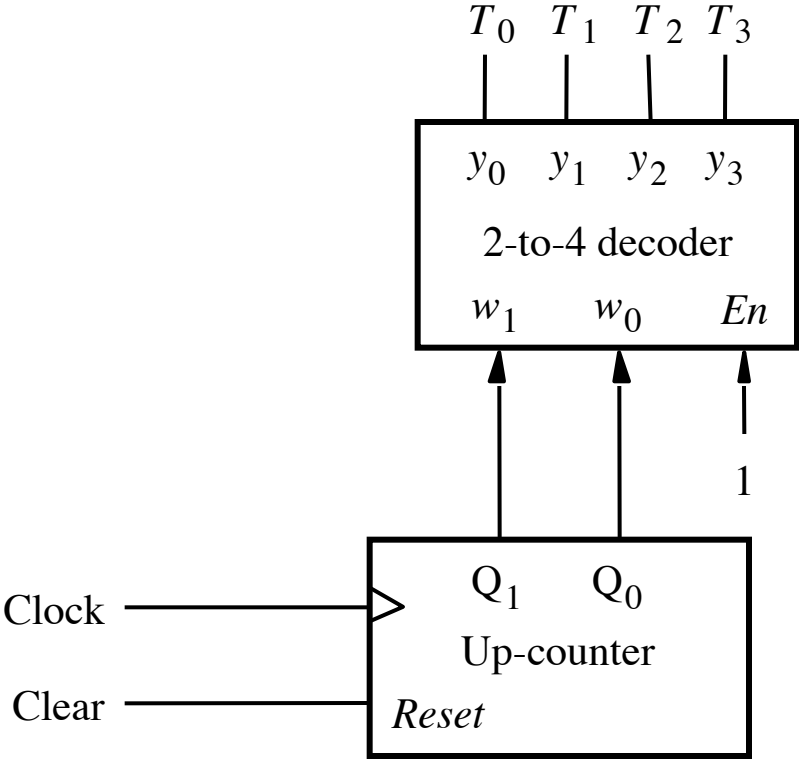


So How Does This Work?

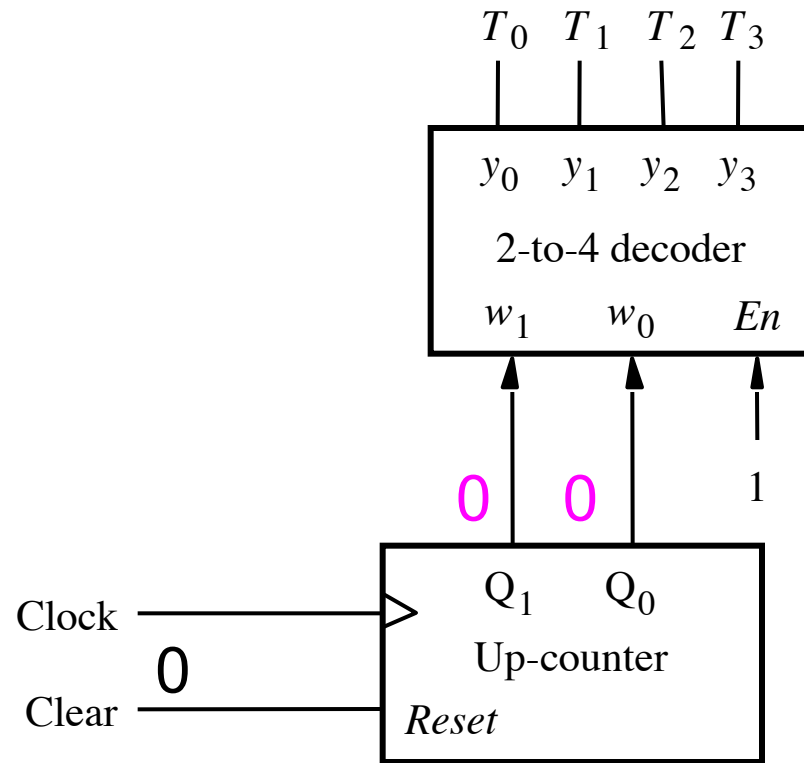


So How Does This Work?

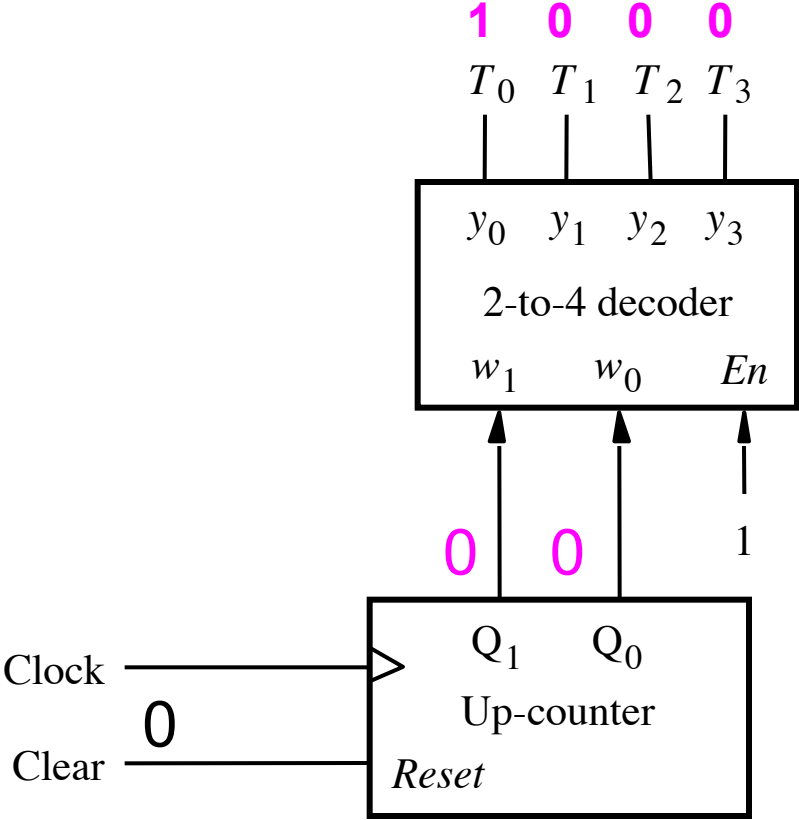


So How Does This Work?

 


So How Does This Work?

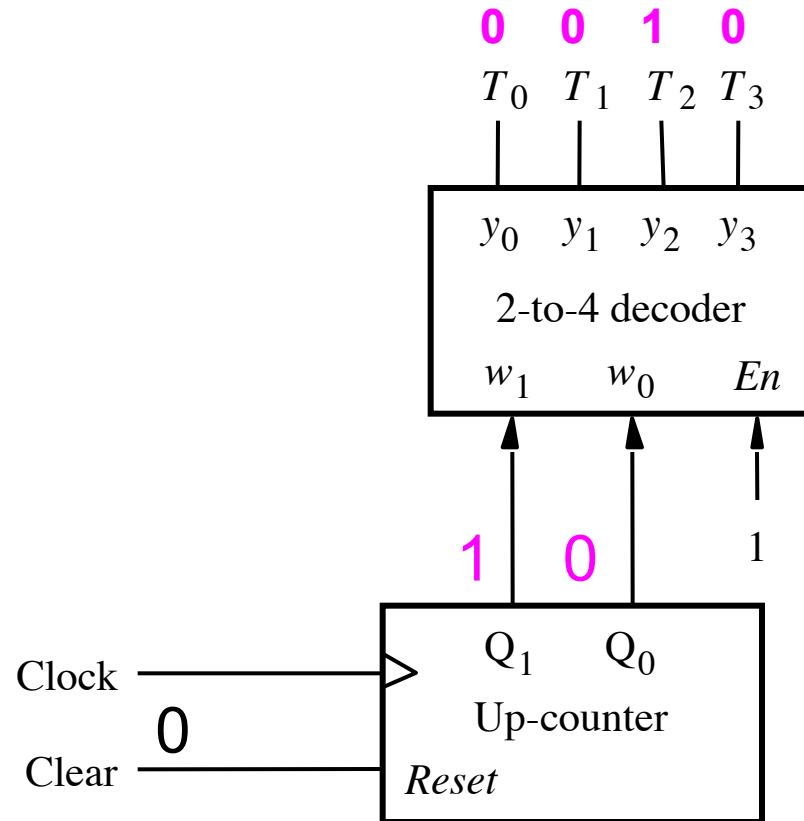


So How Does This Work?

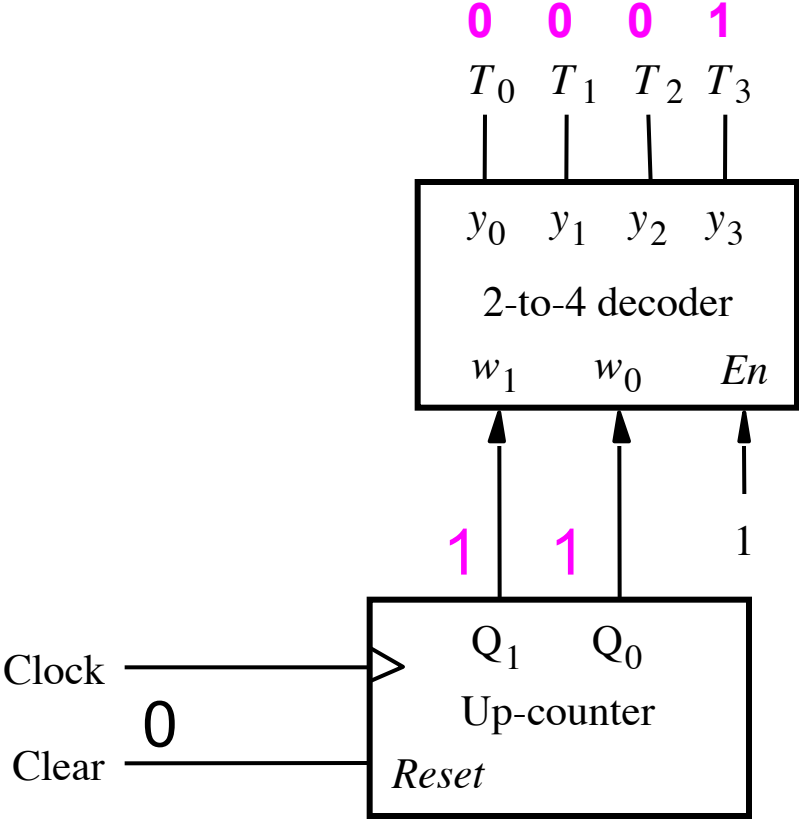


So How Does This Work?

 


So How Does This Work?

 

So How Does This Work?

 

So How Does This Work?

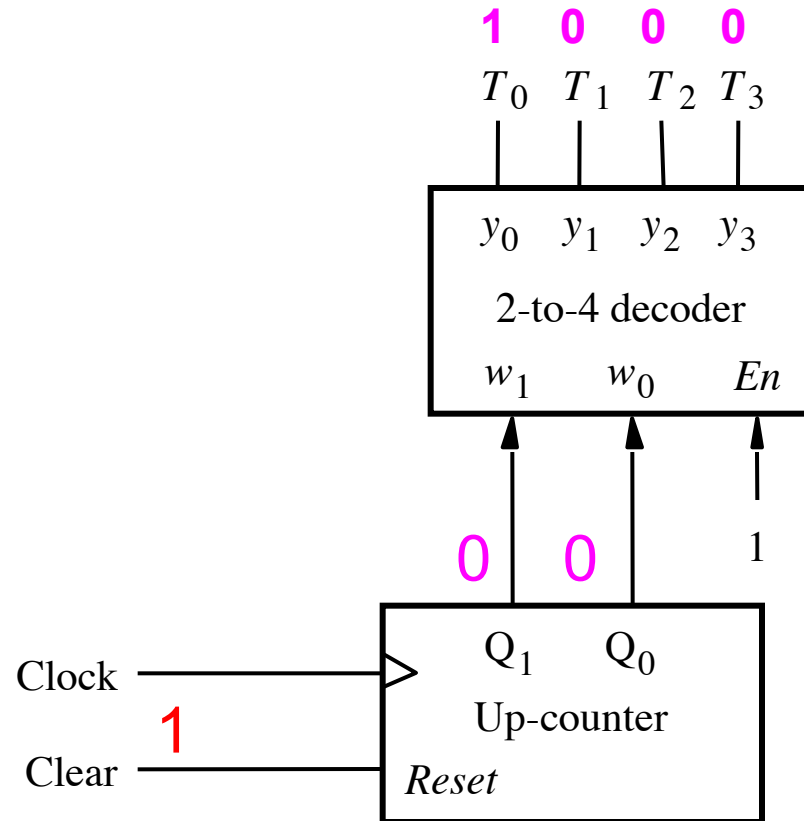

Meaning/Explanation

- **This is like a FSM that cycles through its four states one after another.**
- **But it also can be reset to go to state 0 at any time.**
- **The implementation uses a counter followed by a decoder. The outputs of the decoder are one-hot-encoded.**
- **This is like choosing a state assignment for an FSM in which there is one Flip-Flop per state, i.e., one-hot encoding (see Section 6.2.1 in the textbook)**


Deriving the Control Signals

Design a FSM with input w and outputs

- $R0_{in}$
- $R0_{out}$
- $R1_{in}$
- $R1_{out}$
- $R2_{in}$
- $R2_{out}$
- $R3_{in}$
- $R3_{out}$
- A_{in}
- G_{in}
- G_{out}
- Clear
- FR_{in}
- AddSub
- Extern
- Done
- T_0
- T_1
- T_2
- T_3
- I_0
- I_1
- I_2
- I_3
- X_0
- X_1
- X_2
- X_3
- Y_0
- Y_1
- Y_2
- Y_3


These are helper outputs that are one-hot encoded. They are used to simplify the expressions for the other outputs.

Control Signals

 


[Figure 7.9 from the textbook]

Control Signals

 


[Figure 7.9 from the textbook]

Another Control Signal

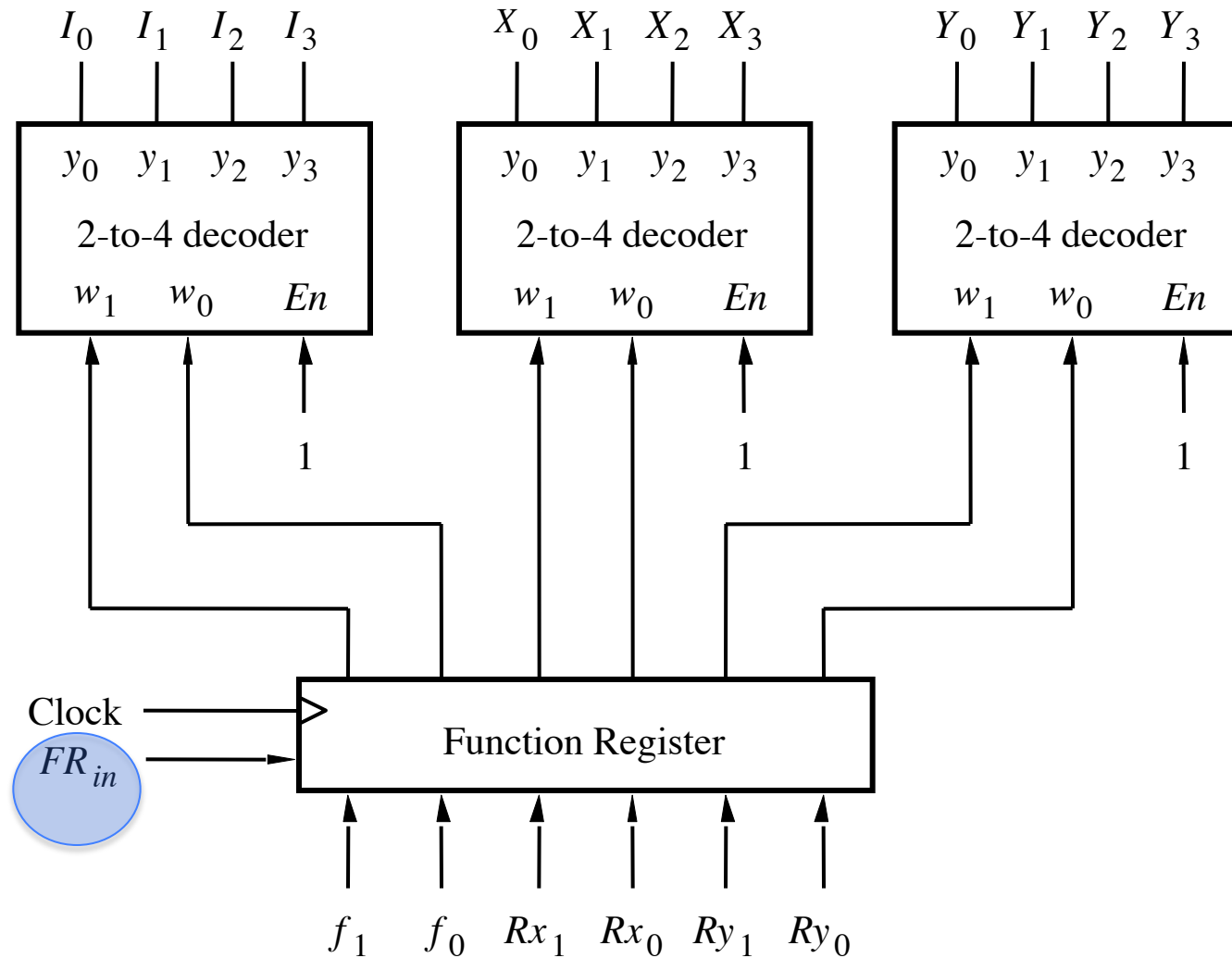


[Figure 7.11 from the textbook]

Yet Another Control Signal

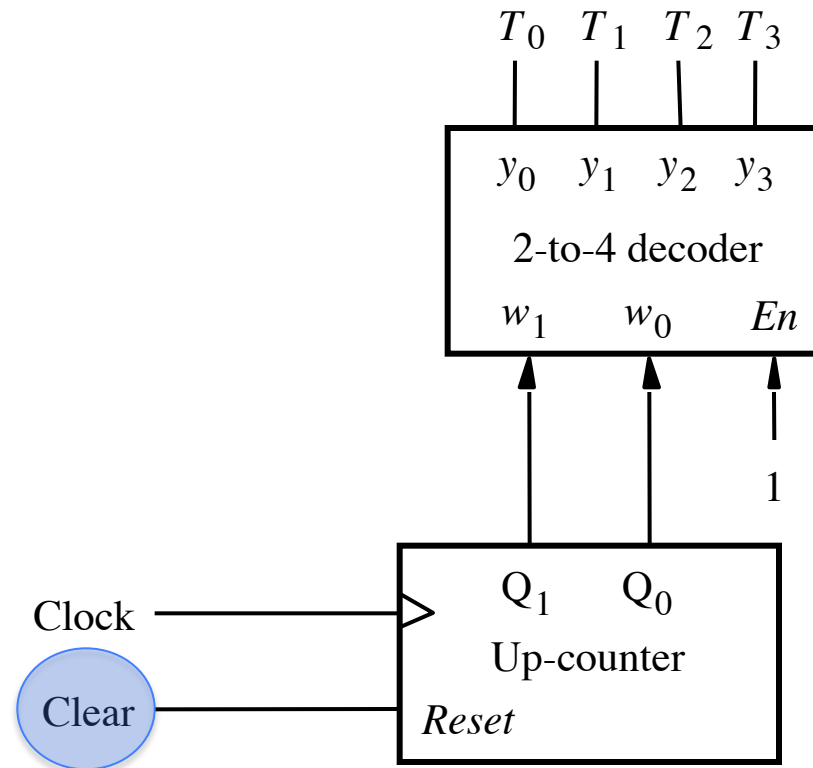


Expressing the 'FR_{in}' signal

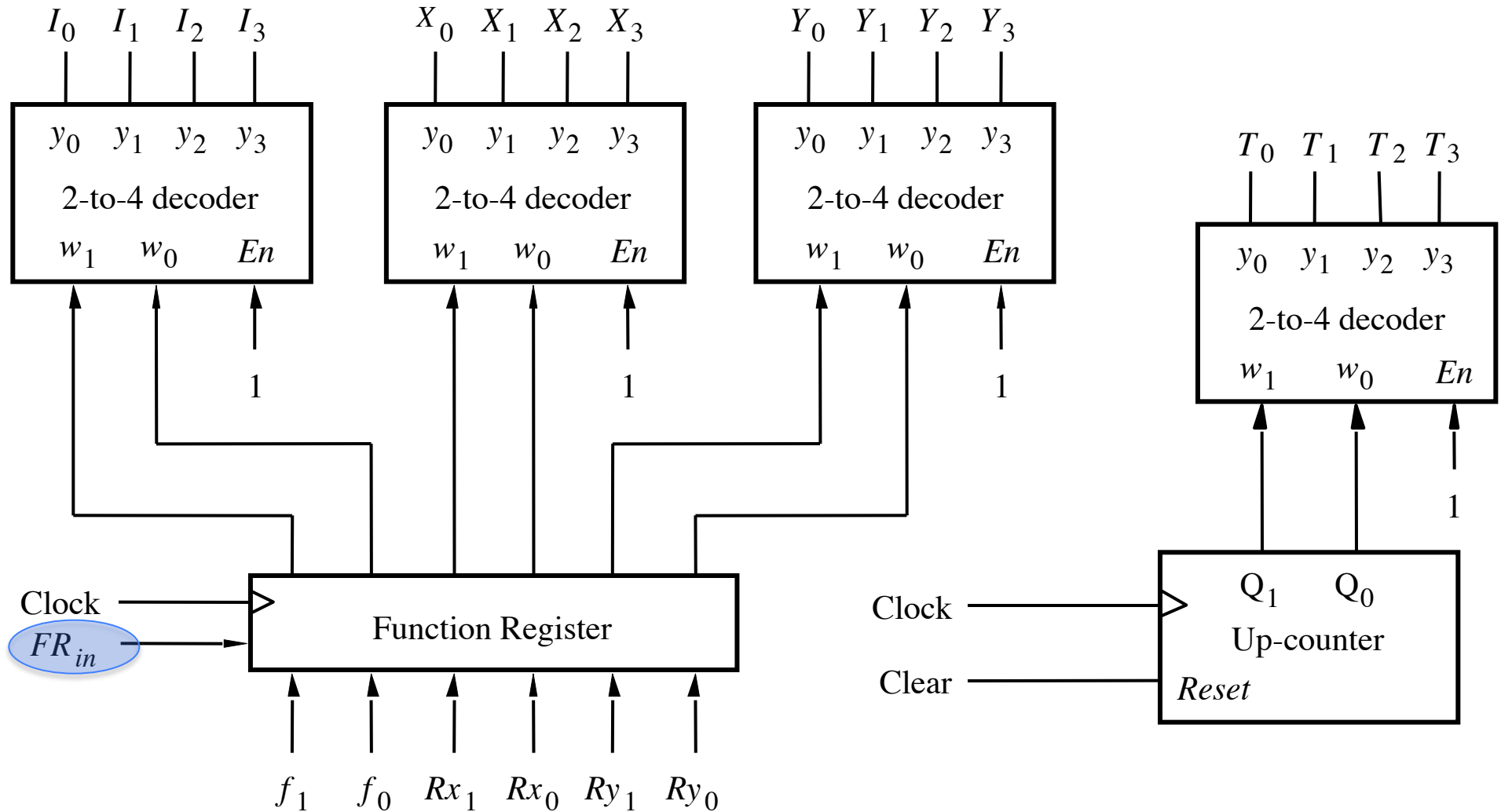

$$FR_{in} = w T_0$$

Load a new operation into the function register

Expressing the 'Clear' signal

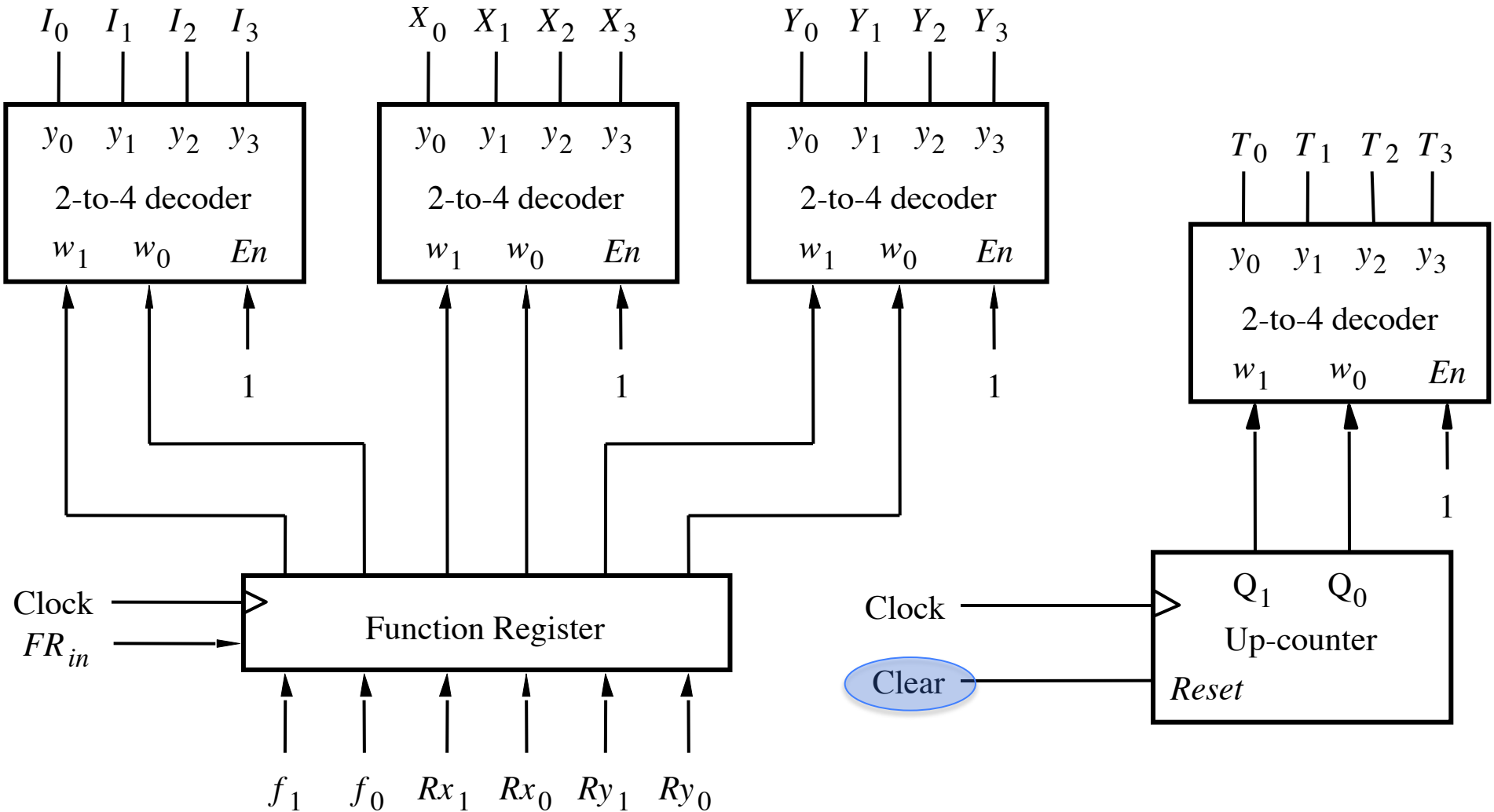

$$\text{Clear} = \overline{w} T_0 + \text{Done}$$

Reset the counter when Done or when $w=0$ and no operation is being executed (i.e., $T_0=1$).

Control signals asserted in each time step

	T ₁	T ₂	T ₃
(Load): I ₀	Extern R _{in} = X Done		
(Move): I ₁	R _{in} = X R _{out} = Y Done		
(Add): I ₂	R _{out} = X A _{in}	R _{out} = Y G _{in} AddSub = 0	G _{out} R _{in} = X Done
(Sub): I ₃	R _{out} = X A _{in}	R _{out} = Y G _{in} AddSub = 1	G _{out} R _{in} = X Done


Control signals asserted in each time step

	T_1	T_2	T_3
(Load): I_0	Extern $R_{in} = X$ Done		
(Move): I_1	$R_{in} = X$ $R_{out} = Y$ Done		
(Add): I_2	$R_{out} = X$ A_{in}	$R_{out} = Y$ G_{in} AddSub = 0	G_{out} $R_{in} = X$ Done
(Sub): I_3	$R_{out} = X$ A_{in}	$R_{out} = Y$ G_{in} AddSub = 1	G_{out} $R_{in} = X$ Done

These come from the outputs of the 2-to-4 decoder in Figure 7.10. They are also one-hot encoded.

These are the outputs of the first 2-to-4 decoder that is connected to the two most significant bits of the function register. They are one-hot encoded so only one of them is active at any given time (see Fig 7.11).

The I_0, I_1, I_2, I_3 and T_0, T_1, T_2, T_3 Signals

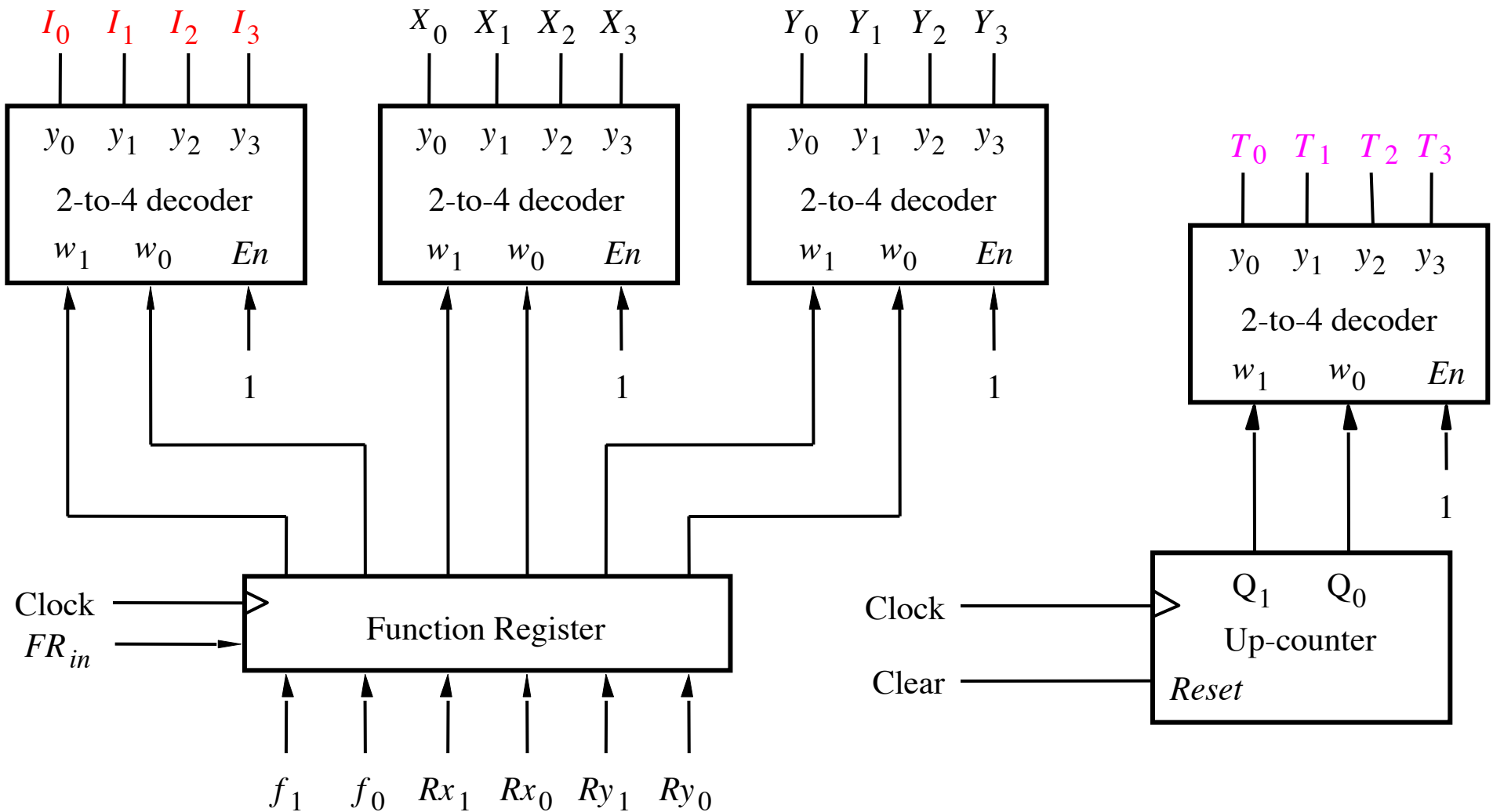

[Figure 7.11 from the textbook]

[Figure 7.10 from the textbook]

Different Operations Take Different Amount of Time


	T_1	T_2	T_3	
(Load): I_0	Extern $R_{in} = X$ Done			1 clock cycle
(Move): I_1	$R_{in} = X$ $R_{out} = Y$ Done			1 clock cycle
(Add): I_2	$R_{out} = X$ A_{in}	$R_{out} = Y$ G_{in} AddSub = 0	G_{out} $R_{in} = X$ Done	3 clock cycles
(Sub): I_3	$R_{out} = X$ A_{in}	$R_{out} = Y$ G_{in} AddSub = 1	G_{out} $R_{in} = X$ Done	3 clock cycles

Operations performed by this processor

Operation	Function Performed
Load Rx, Data	Rx ← Data
Move Rx, Ry	Rx ← [Ry]
Add Rx, Ry	Rx ← [Rx] + [Ry]
Sub Rx, Ry	Rx ← [Rx] - [Ry]

Where Rx and Ry can be one of four possible options: R0, R1, R2, and R3

Simple Processor

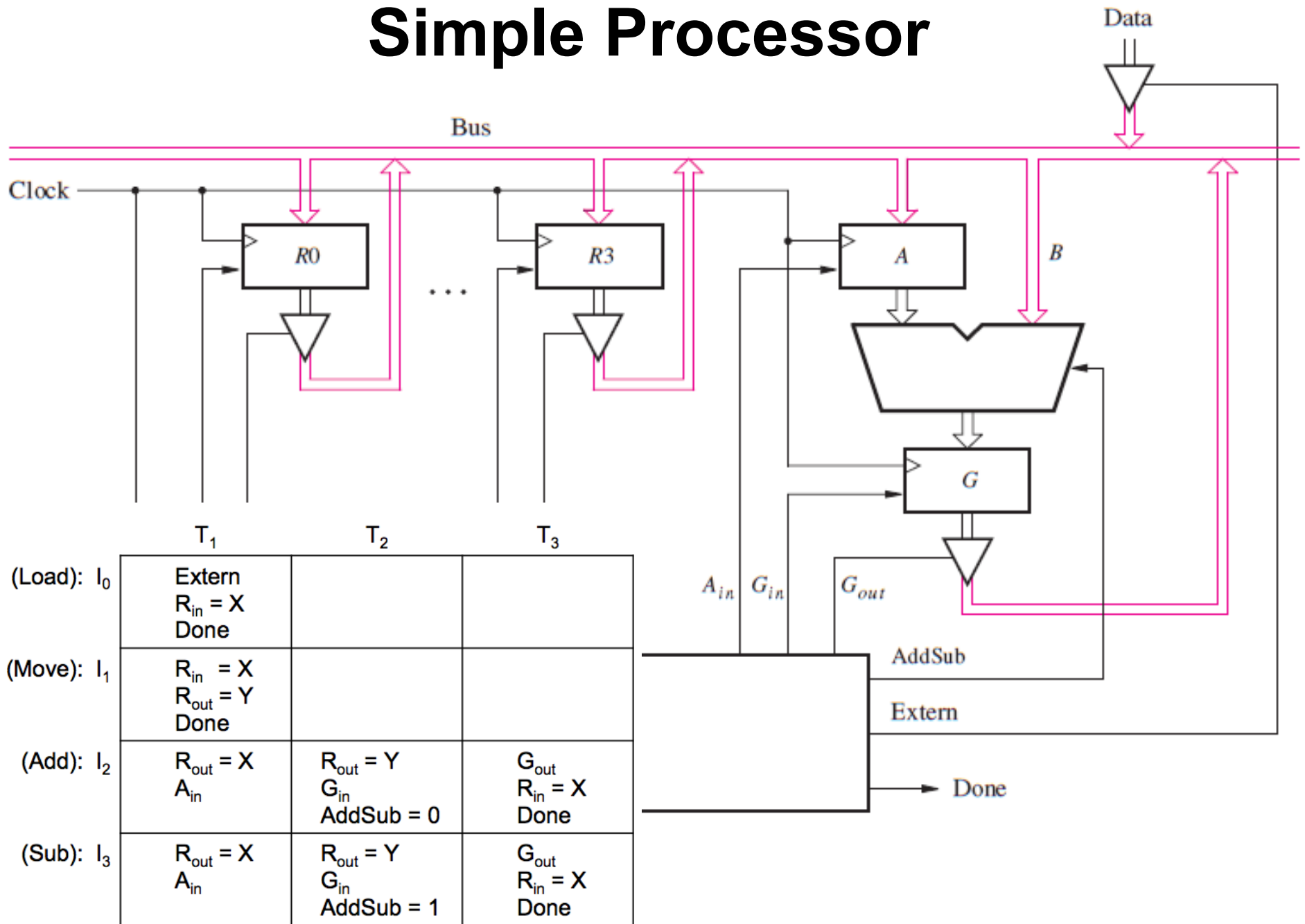

[Figure 7.9 from the textbook]

Expressing the 'Extern' signal

	T_1	T_2	T_3
(Load): I_0	Extern $R_{in} = X$ Done		
(Move): I_1	$R_{in} = X$ $R_{out} = Y$ Done		
(Add): I_2	$R_{out} = X$ A_{in}	$R_{out} = Y$ G_{in} AddSub = 0	G_{out} $R_{in} = X$ Done
(Sub): I_3	$R_{out} = X$ A_{in}	$R_{out} = Y$ G_{in} AddSub = 1	G_{out} $R_{in} = X$ Done

$$\text{Extern} = I_0 T_1$$

Expressing the 'Done' signal

	T_1	T_2	T_3
(Load): I_0	Extern $R_{in} = X$ Done		
(Move): I_1	$R_{in} = X$ $R_{out} = Y$ Done		
(Add): I_2	$R_{out} = X$ A_{in}	$R_{out} = Y$ G_{in} AddSub = 0	G_{out} $R_{in} = X$ Done
(Sub): I_3	$R_{out} = X$ A_{in}	$R_{out} = Y$ G_{in} AddSub = 1	G_{out} $R_{in} = X$ Done

$$\text{Done} = (I_0 + I_1)T_1 + (I_2 + I_3)T_3$$

Expressing the 'A_{in}' signal

	T ₁	T ₂	T ₃
(Load): I ₀	Extern R _{in} = X Done		
(Move): I ₁	R _{in} = X R _{out} = Y Done		
(Add): I ₂	R _{out} = X A _{in}	R _{out} = Y G _{in} AddSub = 0	G _{out} R _{in} = X Done
(Sub): I ₃	R _{out} = X A _{in}	R _{out} = Y G _{in} AddSub = 1	G _{out} R _{in} = X Done

$$A_{in} = (I_2 + I_3)T_1$$

Expressing the 'G_{in}' signal

	T ₁	T ₂	T ₃
(Load): I ₀	Extern R _{in} = X Done		
(Move): I ₁	R _{in} = X R _{out} = Y Done		
(Add): I ₂	R _{out} = X A _{in}	R _{out} = Y G _{in} AddSub = 0	G _{out} R _{in} = X Done
(Sub): I ₃	R _{out} = X A _{in}	R _{out} = Y G _{in} AddSub = 1	G _{out} R _{in} = X Done

$$G_{in} = (I_2 + I_3)T_2$$

Expressing the 'G_{out}' signal

	T ₁	T ₂	T ₃
(Load): I ₀	Extern R _{in} = X Done		
(Move): I ₁	R _{in} = X R _{out} = Y Done		
(Add): I ₂	R _{out} = X A _{in}	R _{out} = Y G _{in} AddSub = 0	G _{out} R _{in} = X Done
(Sub): I ₃	R _{out} = X A _{in}	R _{out} = Y G _{in} AddSub = 1	G _{out} R _{in} = X Done

$$G_{out} = (I_2 + I_3)T_3$$

Expressing the 'AddSub' signal

	T ₁	T ₂	T ₃
(Load): I ₀	Extern R _{in} = X Done		
(Move): I ₁	R _{in} = X R _{out} = Y Done		
(Add): I ₂	R _{out} = X A _{in}	R _{out} = Y G _{in} AddSub = 0	G _{out} R _{in} = X Done
(Sub): I ₃	R _{out} = X A _{in}	R _{out} = Y G _{in} AddSub = 1	G _{out} R _{in} = X Done

$$\text{AddSub} = I_3$$

Expressing the 'R0_{in}' signal

	T ₁	T ₂	T ₃
(Load): I ₀	Extern R _{in} = X Done		
(Move): I ₁	R _{in} = X R _{out} = Y Done		
(Add): I ₂	R _{out} = X A _{in}	R _{out} = Y G _{in} AddSub = 0	G _{out} R _{in} = X Done
(Sub): I ₃	R _{out} = X A _{in}	R _{out} = Y G _{in} AddSub = 1	G _{out} R _{in} = X Done

$$R0_{in} = (I_0 + I_1)T_1 X_0 + (I_2 + I_3)T_3 X_0$$

Expressing the 'R_{in}' signal

	T ₁	T ₂	T ₃
(Load): I ₀	Extern R _{in} = X Done		
(Move): I ₁	R _{in} = X R _{out} = Y Done		
(Add): I ₂	R _{out} = X A _{in}	R _{out} = Y G _{in} AddSub = 0	G _{out} R _{in} = X Done
(Sub): I ₃	R _{out} = X A _{in}	R _{out} = Y G _{in} AddSub = 1	G _{out} R _{in} = X Done

$$R_{in} = (I_0 + I_1)T_1 X_1 + (I_2 + I_3)T_3 X_1$$

Expressing the ' R_{in}^2 ' signal

	T_1	T_2	T_3
(Load): I_0	Extern $R_{in} = X$ Done		
(Move): I_1	$R_{in} = X$ $R_{out} = Y$ Done		
(Add): I_2	$R_{out} = X$ A_{in}	$R_{out} = Y$ G_{in} AddSub = 0	G_{out} $R_{in} = X$ Done
(Sub): I_3	$R_{out} = X$ A_{in}	$R_{out} = Y$ G_{in} AddSub = 1	G_{out} $R_{in} = X$ Done

$$R_{in}^2 = (I_0 + I_1)T_1 X_2 + (I_2 + I_3)T_3 X_2$$

Expressing the 'R_{3in}' signal

	T ₁	T ₂	T ₃
(Load): I ₀	Extern R _{in} = X Done		
(Move): I ₁	R _{in} = X R _{out} = Y Done		
(Add): I ₂	R _{out} = X A _{in}	R _{out} = Y G _{in} AddSub = 0	G _{out} R _{in} = X Done
(Sub): I ₃	R _{out} = X A _{in}	R _{out} = Y G _{in} AddSub = 1	G _{out} R _{in} = X Done

$$R_{3in} = (I_0 + I_1)T_1 X_3 + (I_2 + I_3)T_3 X_3$$

Expressing the 'R0_{out}' signal

	T ₁	T ₂	T ₃
(Load): I ₀	Extern R _{in} = X Done		
(Move): I ₁	R _{in} = X R _{out} = Y Done		
(Add): I ₂	R _{out} = X A _{in}	R _{out} = Y G _{in} AddSub = 0	G _{out} R _{in} = X Done
(Sub): I ₃	R _{out} = X A _{in}	R _{out} = Y G _{in} AddSub = 1	G _{out} R _{in} = X Done

$$R0_{out} = I_1 T_1 Y_0 + (I_2 + I_3) (T_1 X_0 + T_2 Y_0)$$

Expressing the 'R₁_{out}' signal

	T ₁	T ₂	T ₃
(Load): I ₀	Extern R _{in} = X Done		
(Move): I ₁	R _{in} = X R _{out} = Y Done		
(Add): I ₂	R _{out} = X A _{in}	R _{out} = Y G _{in} AddSub = 0	G _{out} R _{in} = X Done
(Sub): I ₃	R _{out} = X A _{in}	R _{out} = Y G _{in} AddSub = 1	G _{out} R _{in} = X Done

$$R_{1\text{out}} = I_1 T_1 Y_1 + (I_2 + I_3) (T_1 X_1 + T_2 Y_1)$$

Expressing the 'R₂_{out}' signal

	T ₁	T ₂	T ₃
(Load): I ₀	Extern R _{in} = X Done		
(Move): I ₁	R _{in} = X R _{out} = Y Done		
(Add): I ₂	R _{out} = X A _{in}	R _{out} = Y G _{in} AddSub = 0	G _{out} R _{in} = X Done
(Sub): I ₃	R _{out} = X A _{in}	R _{out} = Y G _{in} AddSub = 1	G _{out} R _{in} = X Done

$$R_{2\text{out}} = I_1 T_1 Y_2 + (I_2 + I_3) (T_1 X_2 + T_2 Y_2)$$

Expressing the 'R₃_{out}' signal

	T ₁	T ₂	T ₃
(Load): I ₀	Extern R _{in} = X Done		
(Move): I ₁	R _{in} = X R _{out} = Y Done		
(Add): I ₂	R _{out} = X A _{in}	R _{out} = Y G _{in} AddSub = 0	G _{out} R _{in} = X Done
(Sub): I ₃	R _{out} = X A _{in}	R _{out} = Y G _{in} AddSub = 1	G _{out} R _{in} = X Done


$$R_{3\text{out}} = I_1 T_1 Y_3 + (I_2 + I_3) (T_1 X_3 + T_2 Y_3)$$

Derivation of the Control Inputs

- For more insights into these derivations see pages 434 and 435 in the textbook

Some Additional Topics

The ALU for the Simple Processor


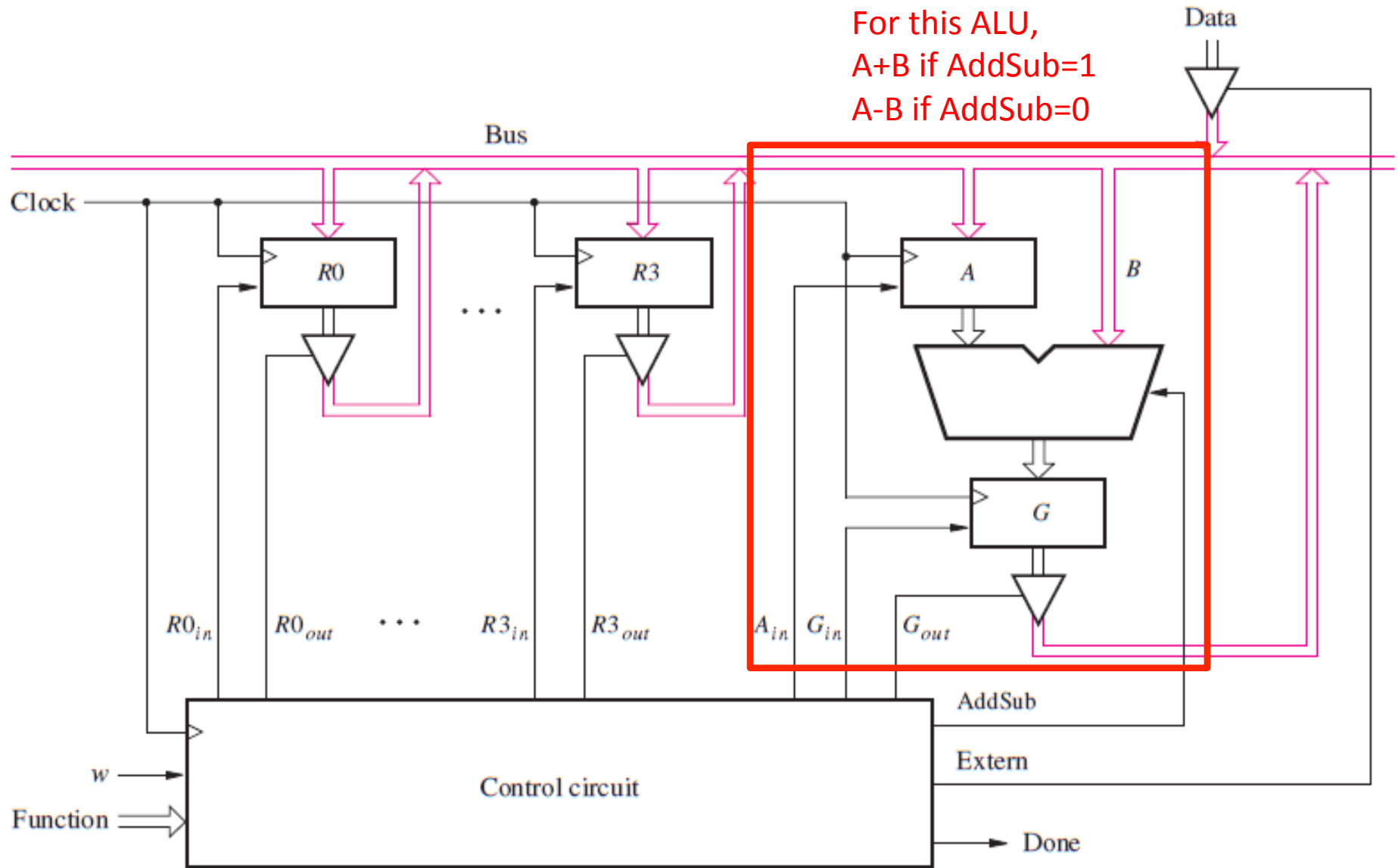


[Figure 7.9 from the textbook]

Another Arithmetic Logic Unit (ALU)


- Arithmetic Logic Unit (ALU) computes arithmetic or logic functions
- Example: A four-function ALU has two selection bits S1 S0 (also called OpCode) to specify the function
 - 00 (ADD), 01 (SUB), 10 (AND), 11 (OR)
- Then the following set up will work

S1	S0	Function
0	0	ADD
0	1	SUB
1	0	AND
1	1	OR

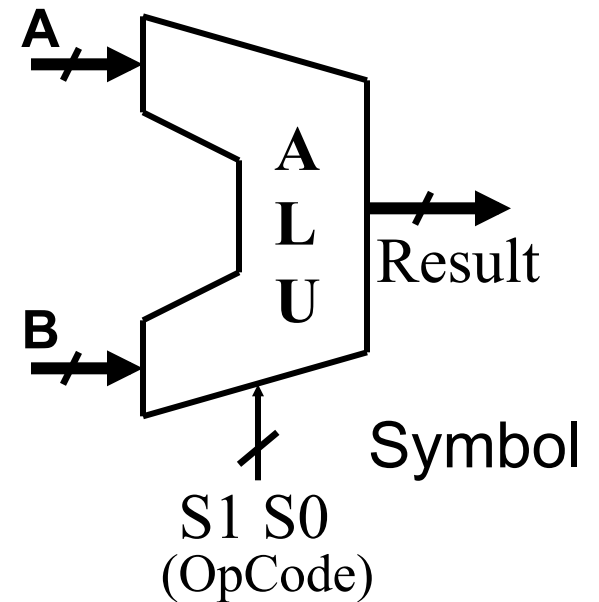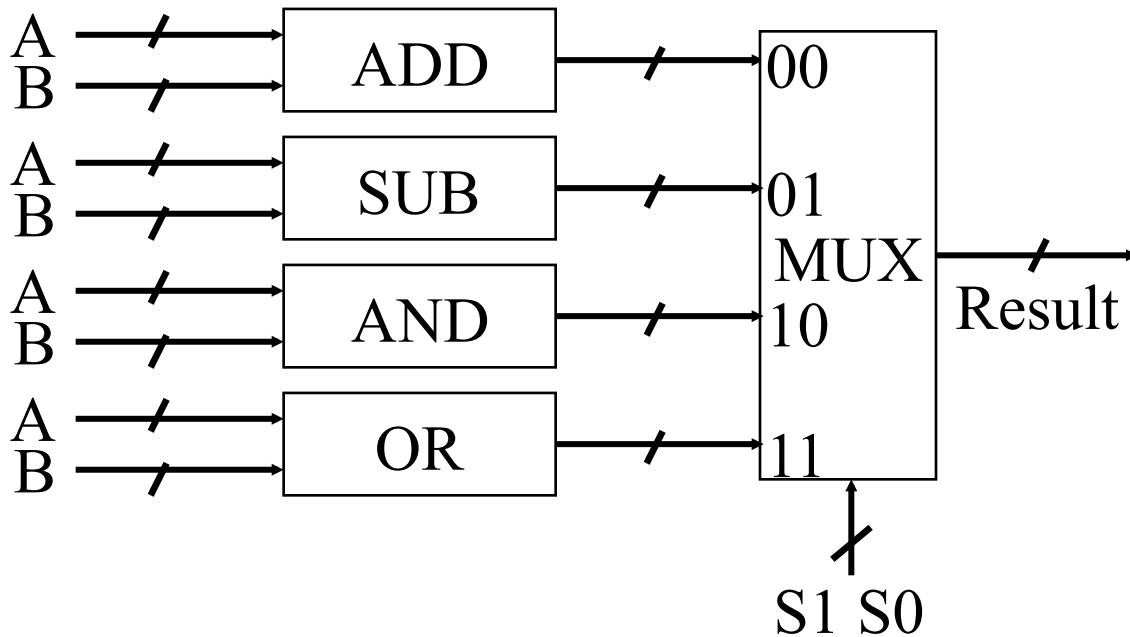

An Alternative Design of Four-Function ALU

 
- The previous design is not very efficient as it uses an adder and a subtractor circuit
- We can design an add/subtract unit as discussed earlier
- Then we can design a logical unit (AND and OR) separately
- Then select appropriate output as result
- What are the control signals, Add/Sub, Select0, and Select1?



S1	S0	Function
0	0	ADD
0	1	SUB
1	0	AND
1	1	OR

Examples of Some Famous Microprocessors

Intel's 4004 Chip

 

[http://en.wikipedia.org/wiki/Intel_4004]


Technical specifications

- **Maximum clock speed was 740 kHz**
- **Instruction cycle time: 10.8 μ s
(8 clock cycles / instruction cycle)**
- **Instruction execution time 1 or 2 instruction cycles
(10.8 or 21.6 μ s), 46300 to 92600 instructions per
second**
- **Built using 2,300 transistors**

Technical specifications

- **Separate program and data storage.**
- **The 4004, with its need to keep pin count down, used a single multiplexed 4-bit bus for transferring:**
 - **12-bit addresses**
 - **8-bit instructions**
 - **4-bit data words**
- **Instruction set contained 46 instructions (of which 41 were 8 bits wide and 5 were 16 bits wide)**
- **Register set contained 16 registers of 4 bits each**
- **Internal subroutine stack, 3 levels deep.**

Intel 4004 Architecture

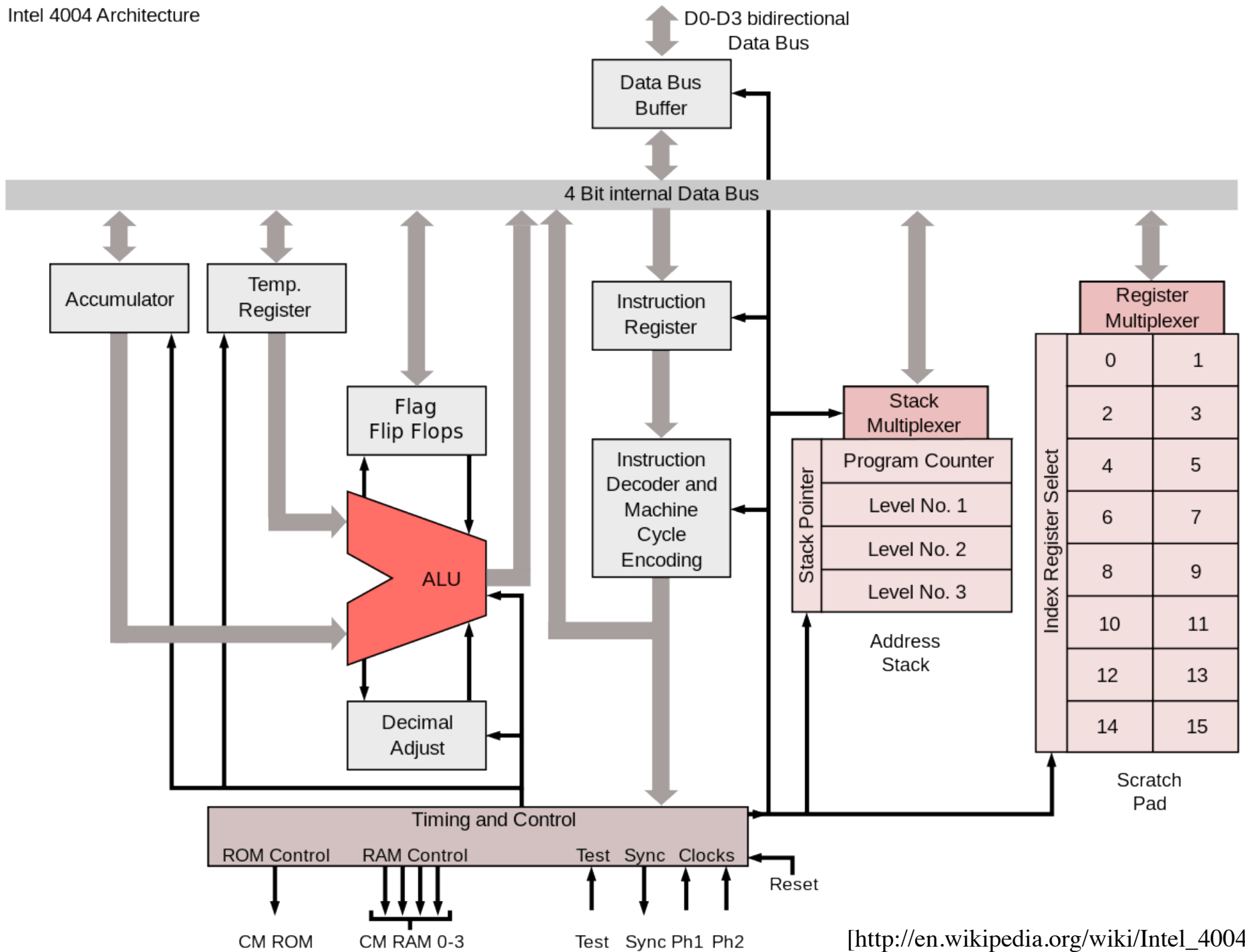

Intel 4004 registers

¹₁ ¹₀ ⁰₉ ⁰₈ ⁰₇ ⁰₆ ⁰₅ ⁰₄ ⁰₃ ⁰₂ ⁰₁ ⁰₀ (bit position)

Main registers

		A	Accumulator
	R0	R1	
	R2	R3	
	R4	R5	
	R6	R7	
	R8	R9	
	R10	R11	
	R12	R13	
	R14	R15	

Program counter

PC	Program Counter
----	-----------------


Push-down address call stack

PC1	Call level 1
PC2	Call level 2
PC3	Call level 3

Status register

C	P	Z	S	Flags
---	---	---	---	-------

Intel's 8086 Chip

 

Intel 8086 registers

¹₉ ¹₈ ¹₇ ¹₆ ¹₅ ¹₄ ¹₃ ¹₂ ¹₁ ⁰₀ ⁰₉ ⁰₈ ⁰₇ ⁰₆ ⁰₅ ⁰₄ ⁰₃ ⁰₂ ⁰₁ ⁰₀ (bit position)

Main registers

	AH	AL	AX (primary accumulator)
	BH	BL	BX (base, accumulator)
	CH	CL	CX (counter, accumulator)
	DH	DL	DX (accumulator, other functions)

Index registers

0 0 0 0	SI	Source Index
0 0 0 0	DI	Destination Index
0 0 0 0	BP	Base Pointer
0 0 0 0	SP	Stack Pointer

Program counter


0 0 0 0	IP	Instruction Pointer
---------	----	----------------------------

Segment registers

CS	0 0 0 0	Code Segment
DS	0 0 0 0	Data Segment
ES	0 0 0 0	ExtraSegment
SS	0 0 0 0	Stack Segment

Status register

- - - - O D I T S Z - A - P - C	Flags
---------------------------------	-------

 

Simplified block diagram of Intel 8088 (a variant of 8086);
 1=main registers;
 2=segment registers and IP;
 3=address adder;
 4=internal address bus;
 5=instruction queue;
 6=control unit (very simplified!);
 7=bus interface;
 8=internal databus;
 9=ALU;
 10/11/12=external address/
 data/control bus.

Questions?

THE END