



# **CprE 281: Digital Logic**

**Instructor: Alexander Stoytchev**

**<http://www.ece.iastate.edu/~alexs/classes/>**

# Review for the Final Exam

*CprE 281: Digital Logic  
Iowa State University, Ames, IA  
Copyright © Alexander Stoytchev*

# **Administrative Stuff**

- **The FINAL exam is scheduled for**
- **Thursday Dec 17 @ 2:15 – 4:15 PM**
- **It will be in this room.**

<http://www.registrar.iastate.edu/students/exams/fallexams>

## Standard Exams by Contact Hour

<u>Time (by first contact)</u>	<u>Exam Day</u>	<u>Exam Date</u>	<u>Exam Time</u>
Mon., 7:30-8:29 a.m.	Mon.	Dec. 14	7:30-9:30 a.m.
Mon., 8:30-9:29 a.m.	Wed.	Dec. 16	7:30-9:30 a.m.
Mon., 9:30-10:29 a.m.	Mon.	Dec. 14	9:45-11:45 a.m.
Mon., 10:30-11:29 a.m.	Tues.	Dec. 15	9:45-11:45 a.m.
Mon., 11:30 a.m.-12:29 p.m.	Thurs.	Dec. 17	12:00-2:00 p.m.
Mon., 12:30-1:29 p.m.	Fri.	Dec. 18	9:45-11:45 a.m.
Mon., 1:30-2:29 p.m.	Mon.	Dec. 14	12:00-2:00 p.m.
Mon., 2:30-3:29 p.m.	Fri.	Dec. 18	12:00-2:00 p.m.
Mon., 3:30-4:29 p.m.	Thurs.	Dec. 17	2:15-4:15 p.m.

# **Final Exam Format**

- **The exam will cover: Chapter 1 to Chapter 6, and Sections 7.1-7.2**
- **Emphasis will be on Chapter 5, 6, and 7**
- **The exam will be open book and open notes (you can bring up to 5 pages of handwritten notes) plus your textbook.**

# Final Exam Format

- The exam will be out of 130 points
- You need 95 points to get an A
- It will be great if you can score more than 100 points.
  - but you can't roll over your extra points 😞

# Topics for the Final Exam

- **K-maps for 2, 3, and 4 variables**
- **Multiplexers (circuits and function)**
- **Synthesis of logic functions using multiplexers**
- **Shannon's Expansion Theorem**
- **1's complement and 2's complement representation**
- **Addition and subtraction of binary numbers**
- **Circuits for adding and subtracting**
- **Serial adder**
- **Latches (circuits, behavior, timing diagrams)**
- **Flip-Flops (circuits, behavior, timing diagrams)**
- **Counters**
- **Registers**
- **Synchronous Sequential Circuits**

# Topics for the Final Exam

- **FSMs**
- **Moore Machine**
- **Mealy Machines**
- **State diagrams, state tables, state-assigned tables**
- **State minimization**
- **Designing a counter**
- **Arbiter Circuits**
- **Reverse engineering a circuit**
- **ASM Charts**
- **Register Machines**
- **Bus structure and Simple Processors**
- **Assembly Language for the Simple Processor**
- **Something from Star Wars**



# **How to Study for the Final Exam**

- **Form a study group**
- **Go over the slides for this class**
- **Go over the homeworks again**
- **Go over the problems at the end of Ch 5 & 6**
- **Exercise**
- **Get some sleep**


# **Administrative Stuff**

- **Please check your grades on BlackBoard**
- **Let me know if something is wrong or missing**

# **Sample Problems**

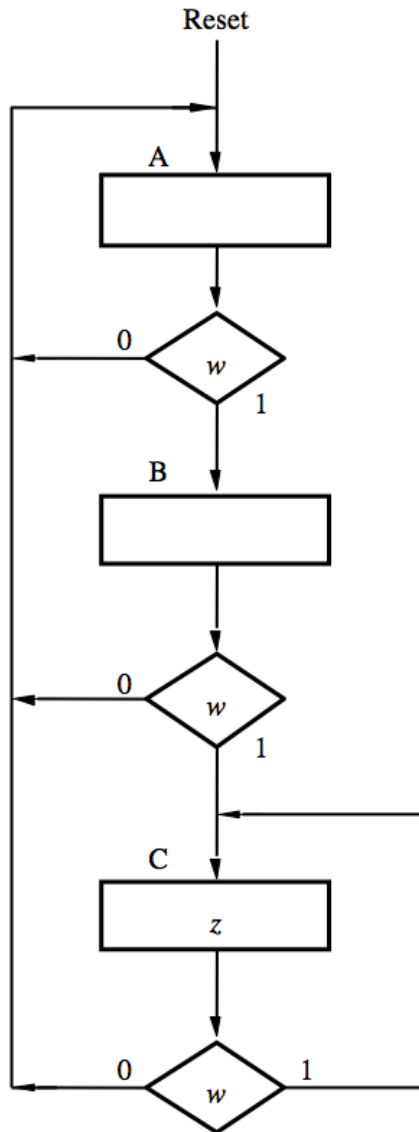
# ASM Charts

Given an ASM chart draw the corresponding FSM




# ASM Charts

Given an ASM chart draw the corresponding FSM

 

[ Figure 6.82 from the textbook ]

 


[ Figure 6.3 from the textbook ]



 
# ASM Charts

Given an FSM draw the corresponding ASM Chart




# ASM Charts

Given an FSM draw the corresponding ASM Chart

 

[ Figure 6.23 from the textbook ]

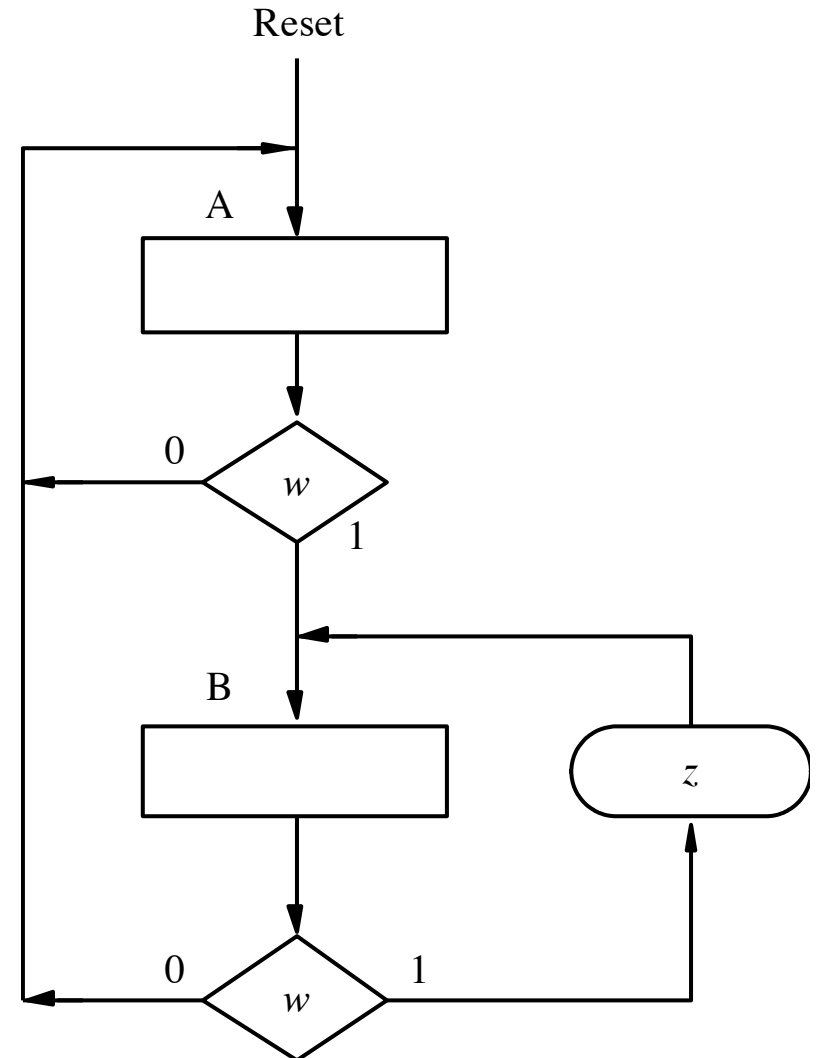

[ Figure 6.83 from the textbook ]





# Circuit Implementation of FSMs

Implement this state-assigned Table using JK flip-flops

	Present state $y_3y_2y_1$	Next state		Output $z$
		$w = 0$	$w = 1$	
		$Y_3Y_2Y_1$	$Y_3Y_2Y_1$	
A	000	100	110	0
B	100	101	110	0
C	101	101	110	1
D	110	100	111	0
E	111	100	111	1

# Circuit Implementation of FSMs

Implement this state-assigned Table using JK flip-flops

$$J_1 = wy_2 + \bar{w}y_3\bar{y}_2$$

$$K_1 = \bar{w}y_2 + wy_1\bar{y}_2$$

$$J_2 = w$$

$$K_2 = \bar{w}$$

$$J_3 = 1$$

$$K_3 = 0$$

$$z = y_1$$

	Present state $y_3y_2y_1$	Next state		Output $z$
		$w = 0$	$w = 1$	
		$Y_3Y_2Y_1$	$Y_3Y_2Y_1$	
A	000	100	110	0
B	100	101	110	0
C	101	101	110	1
D	110	100	111	0
E	111	100	111	1

# Circuit Implementation of FSMs

Implement this state-assigned Table using JK flip-flops

	Present state $y_3y_2y_1$	Flip-flop inputs							Output $z$	
		$w = 0$			$w = 1$					
		$Y_3Y_2Y_1$	$J_3K_3$	$J_2K_2$	$J_1K_1$	$Y_3Y_2Y_1$	$J_3K_3$	$J_2K_2$		$J_1K_1$
A	000	100	$1d$	$0d$	$0d$	110	$1d$	$1d$	$0d$	0
B	100	101	$d0$	$0d$	$1d$	110	$d0$	$1d$	$0d$	0
C	101	101	$d0$	$0d$	$d0$	110	$d0$	$1d$	$d1$	1
D	110	100	$d0$	$d1$	$0d$	111	$d0$	$d0$	$1d$	0
E	111	100	$d0$	$d1$	$d1$	111	$d0$	$d0$	$d0$	1

**Excitation table with JK flip-flops**



# Register Machines:

What does this program do?

How many balls are left in each register at the end of the program?



STEP	INSTRUCTION	REGISTER	GO TO STEP	[BRANCH TO STEP]
1.	Deb	3	1	2
2.	Deb	2	3	4
3.	Inc	3	2	
4.	End			

# Register Machines:


Move the contents of register 2 to register 3



Register 1



Register 2

 

Register 3

STEP	INSTRUCTION	REGISTER	GO TO STEP	[BRANCH TO STEP]
1.	Deb	3	1	2
2.	Deb	2	3	4
3.	Inc	3	2	
4.	End			







# Register Machines:

What does this program do?

How many balls are left in each register at the end of the program?

 

Register 1

 

Register 2




Register 3

STEP	INSTRUCTION	REGISTER	GO TO STEP	[BRANCH TO STEP]
1.	Deb	3	1	2
2.	Deb	2	2	3
3.	Deb	1	4	6
4.	Inc	3	5	
5.	Inc	2	3	
6.	Deb	2	7	8
7.	Inc	1	6	
8.	End			

# Register Machines:

Copy the contents of register 1 to register 3  
using register 2 as a temporary storage

 

Register 1



Register 2




Register 3

STEP	INSTRUCTION	REGISTER	GO TO STEP	[BRANCH TO STEP]
1.	Deb	3	1	2
2.	Deb	2	2	3
3.	Deb	1	4	6
4.	Inc	3	5	
5.	Inc	2	3	
6.	Deb	2	7	8
7.	Inc	1	6	
8.	End			



# What does this circuit do?

 

[ Figure 6.75 from the textbook ]


# Approach

- **Find the flip-flops**
- **Outputs of the flip-flops = present state variables**
- **Inputs of the flip-flops determine the next state variables**
- **Determine the logical expressions for the outputs**
- **Given this info it is easy to do the state-assigned table**
- **Next do the state table**
- **Finally, draw the state diagram.**

# Goal

- **Given a circuit diagram for a synchronous sequential circuit, the goal is to figure out the FSM**
- **Figure out the present state variables, the next state variables, the state-assigned table, the state table, and finally the state diagram.**
- **In other words, the goal is to reverse engineer the circuit.**

# What does this circuit do?

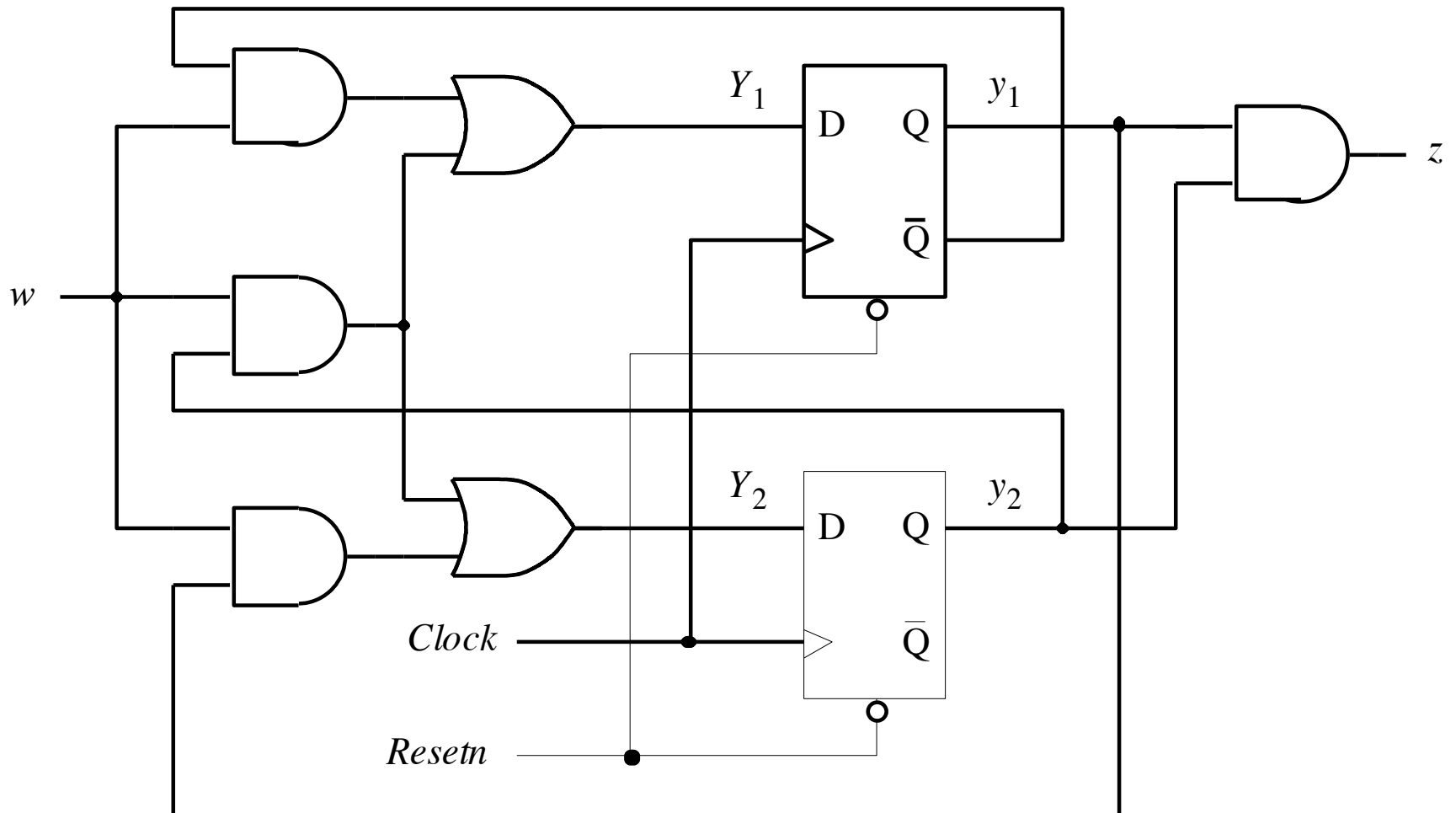


[ Figure 6.75 from the textbook ]

# Approach

- **Find the flip-flops**
- **Outputs of the flip-flops = present state variables**
- **Inputs of the flip-flops determine the next state variables**
- **Determine the logical expressions for the outputs**
- **Given this info it is easy to do the state-assigned table**
- **Next do the state table**
- **Finally, draw the state diagram.**




# Where are the inputs?

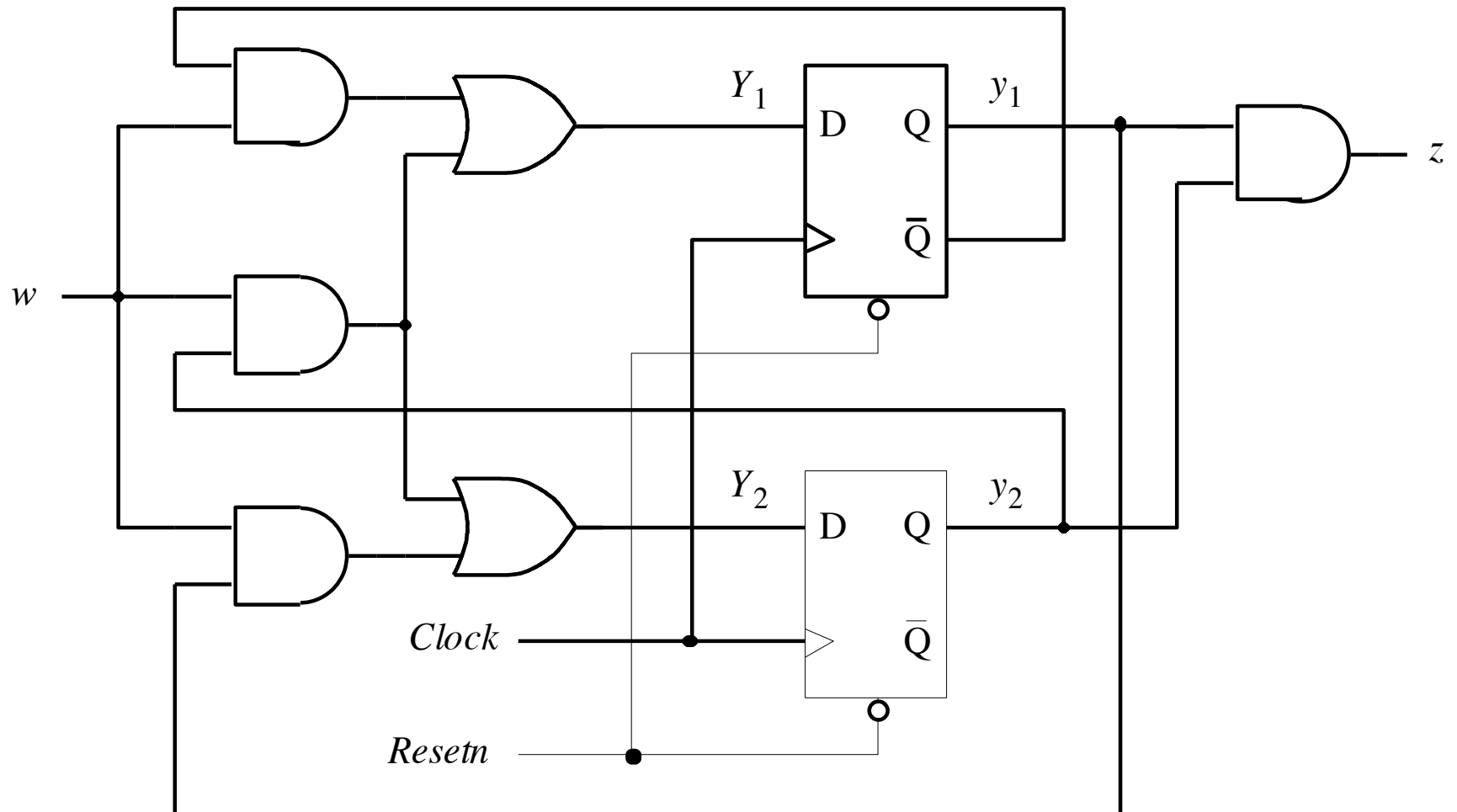


[ Figure 6.75 from the textbook ]

# Where are the inputs?

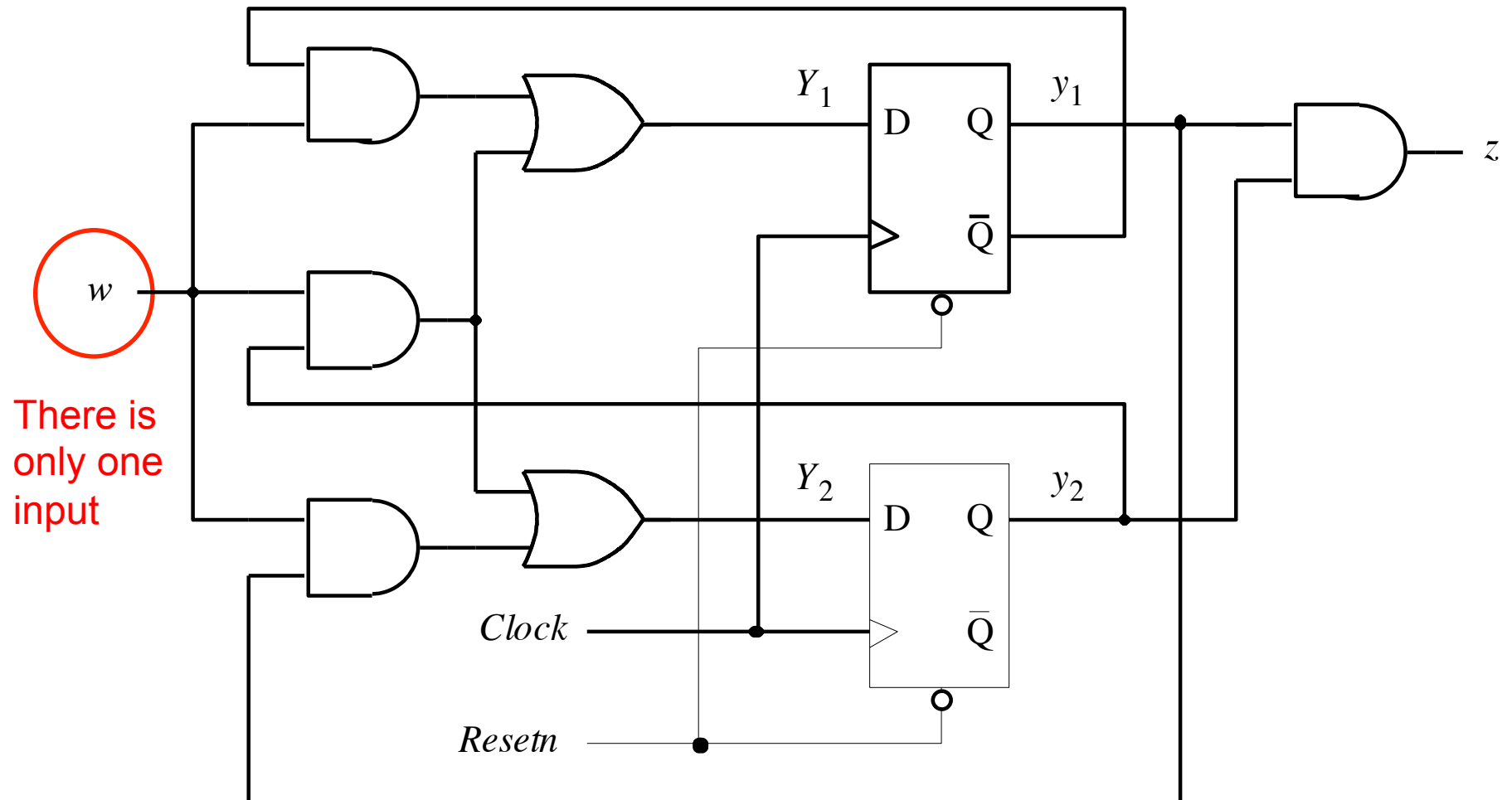


[ Figure 6.75 from the textbook ]

# Where are the outputs?

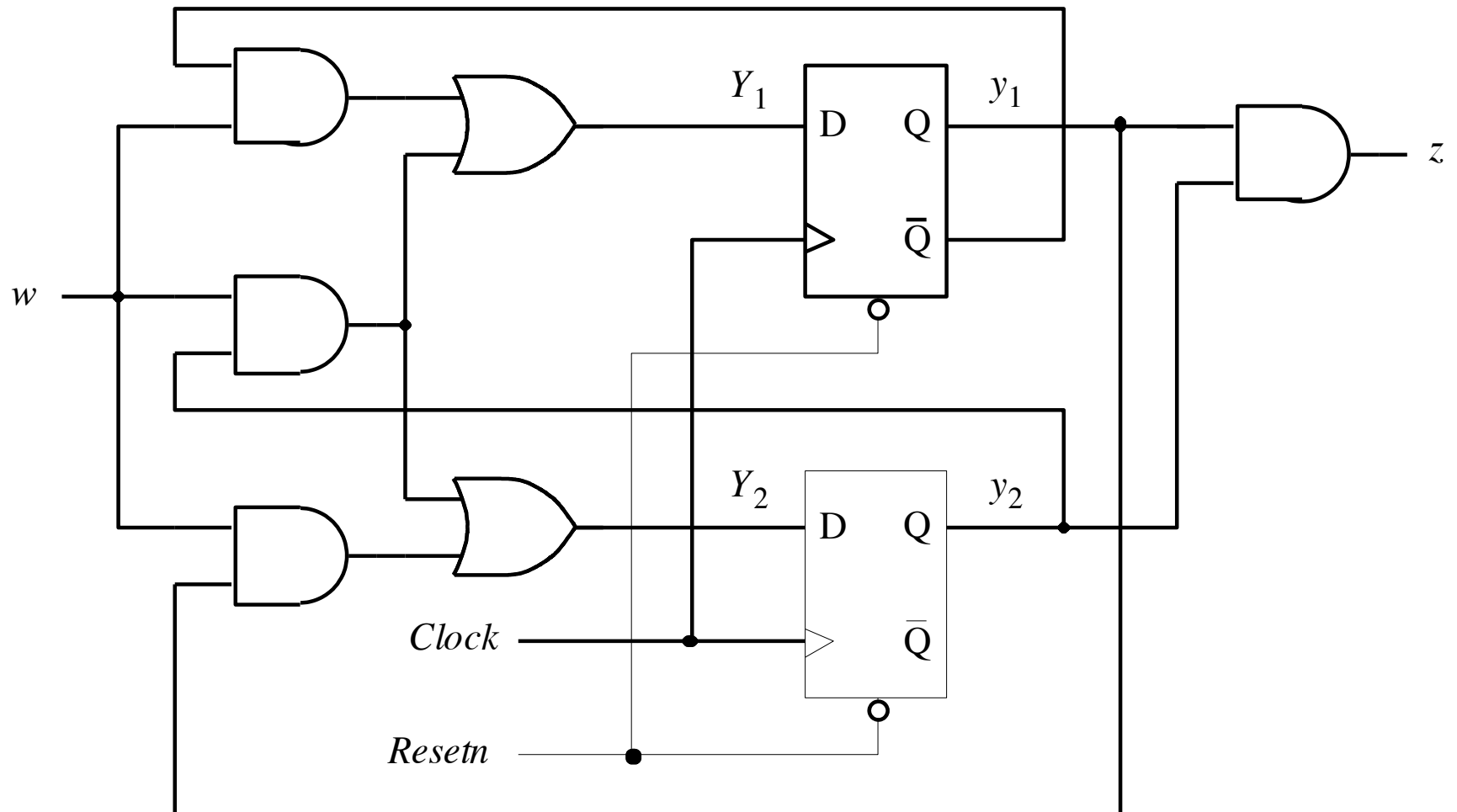

[ Figure 6.75 from the textbook ]


# Where are the outputs?

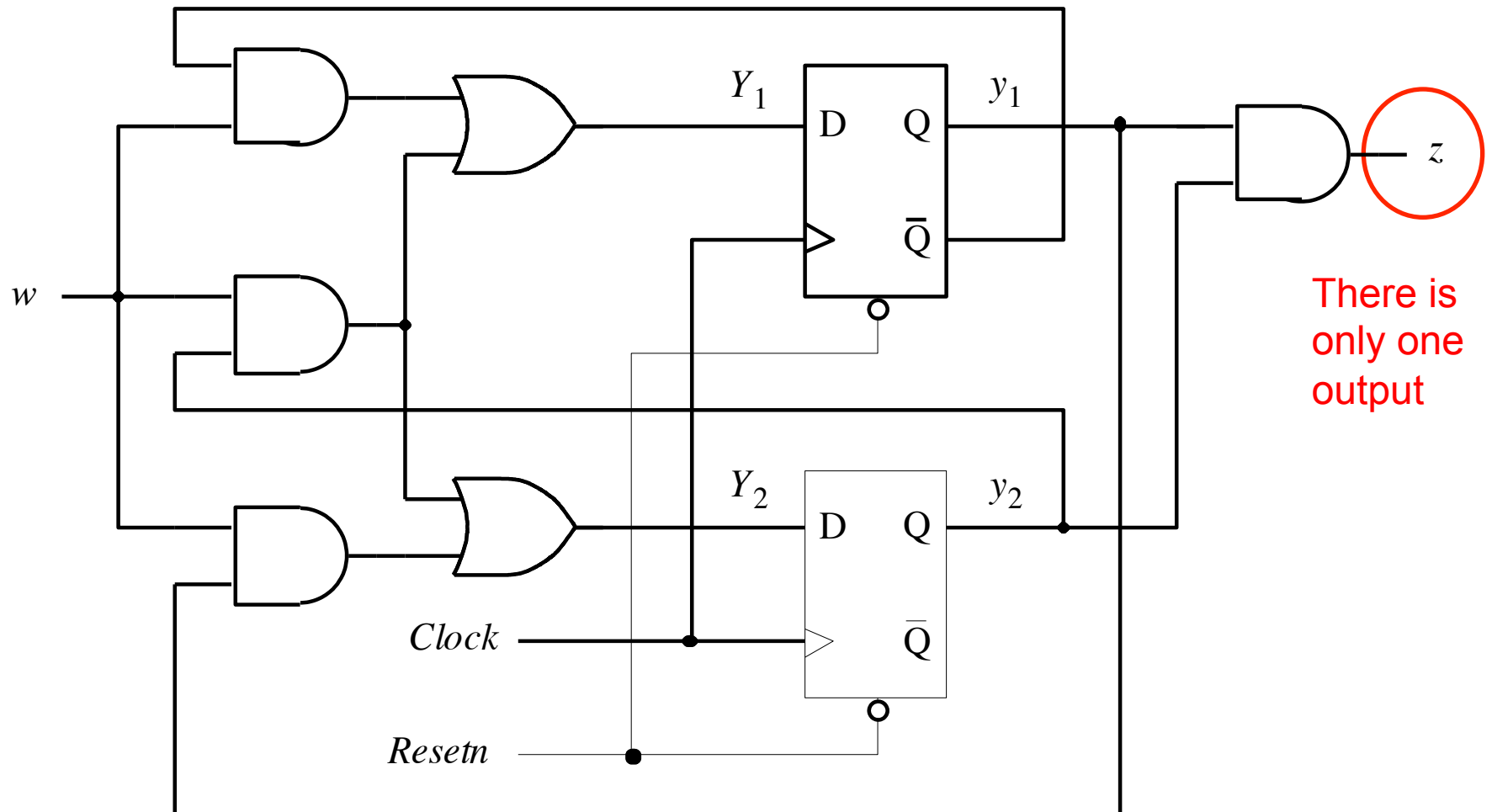

There is only one output


[ Figure 6.75 from the textbook ]
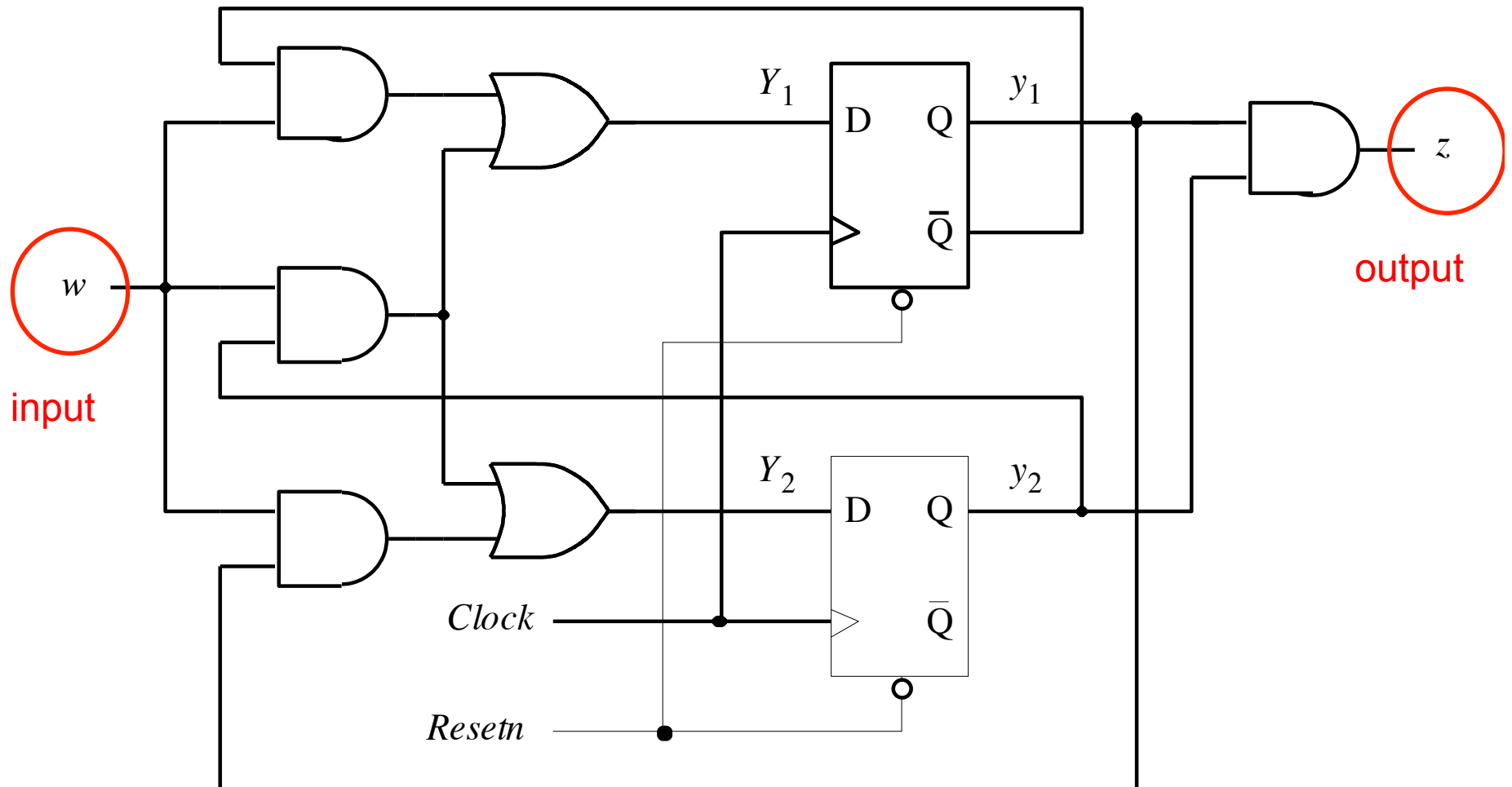
# Where kind of machine is this? Moore or Mealy?






# Where are the memory elements?

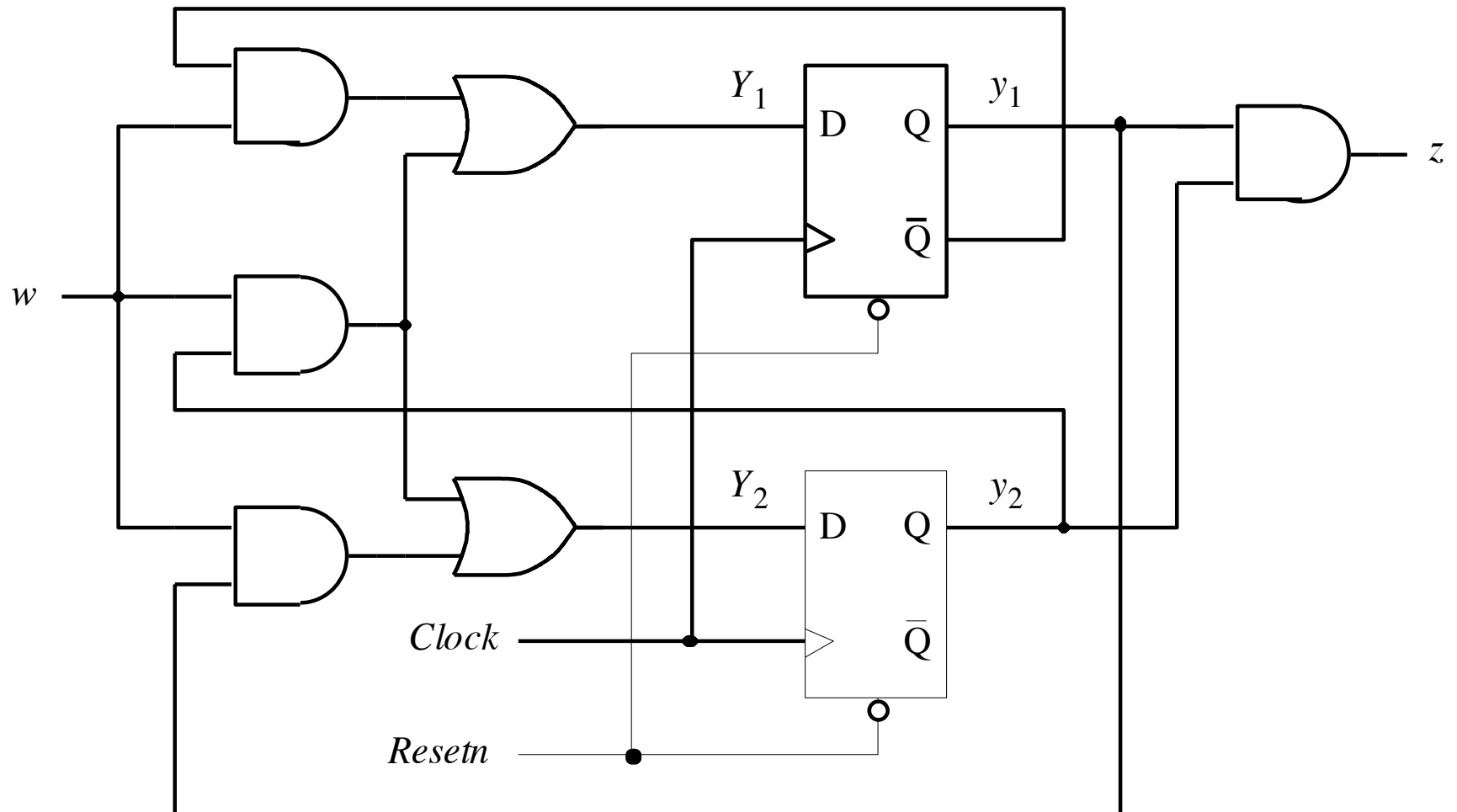


# Where are the memory elements?

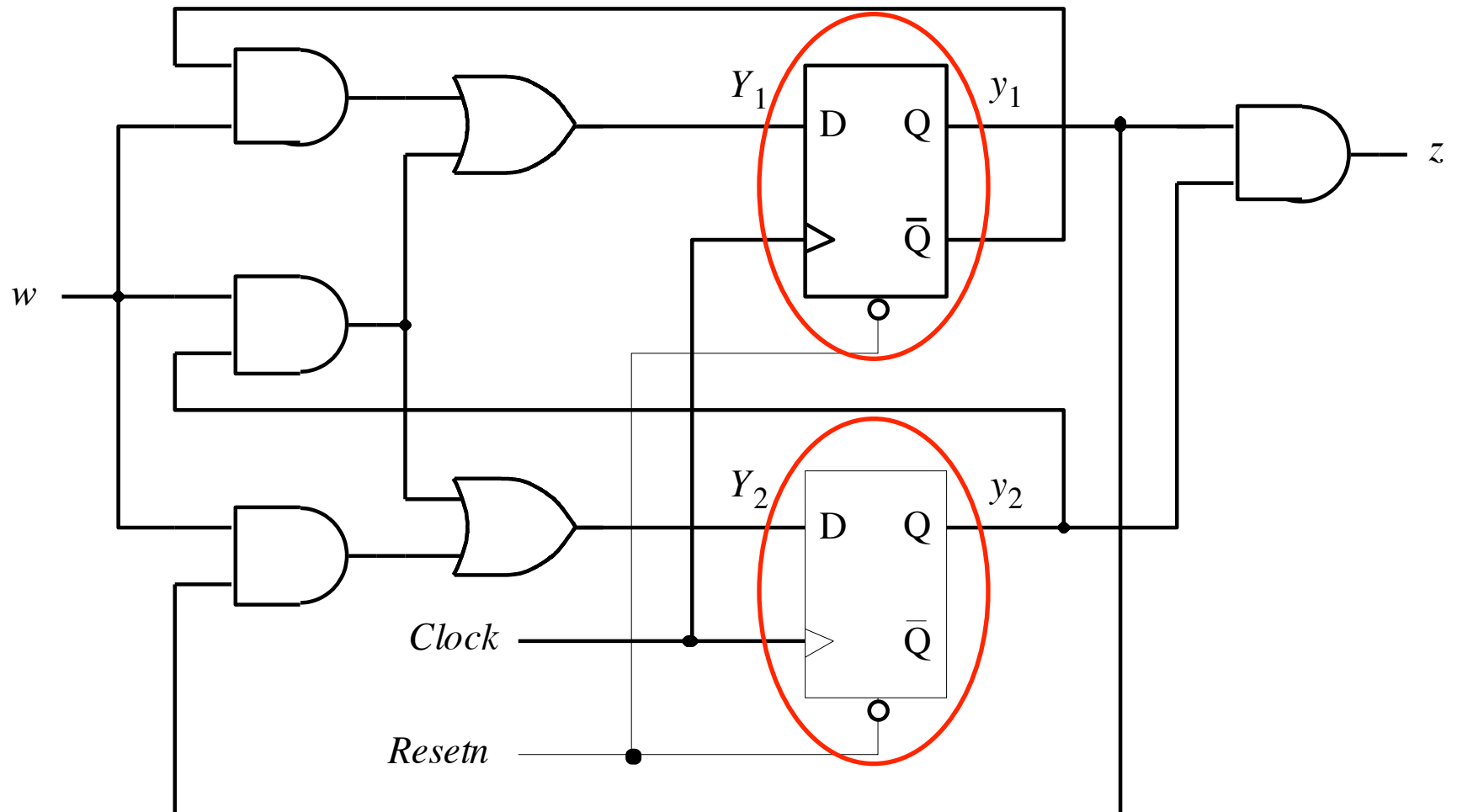




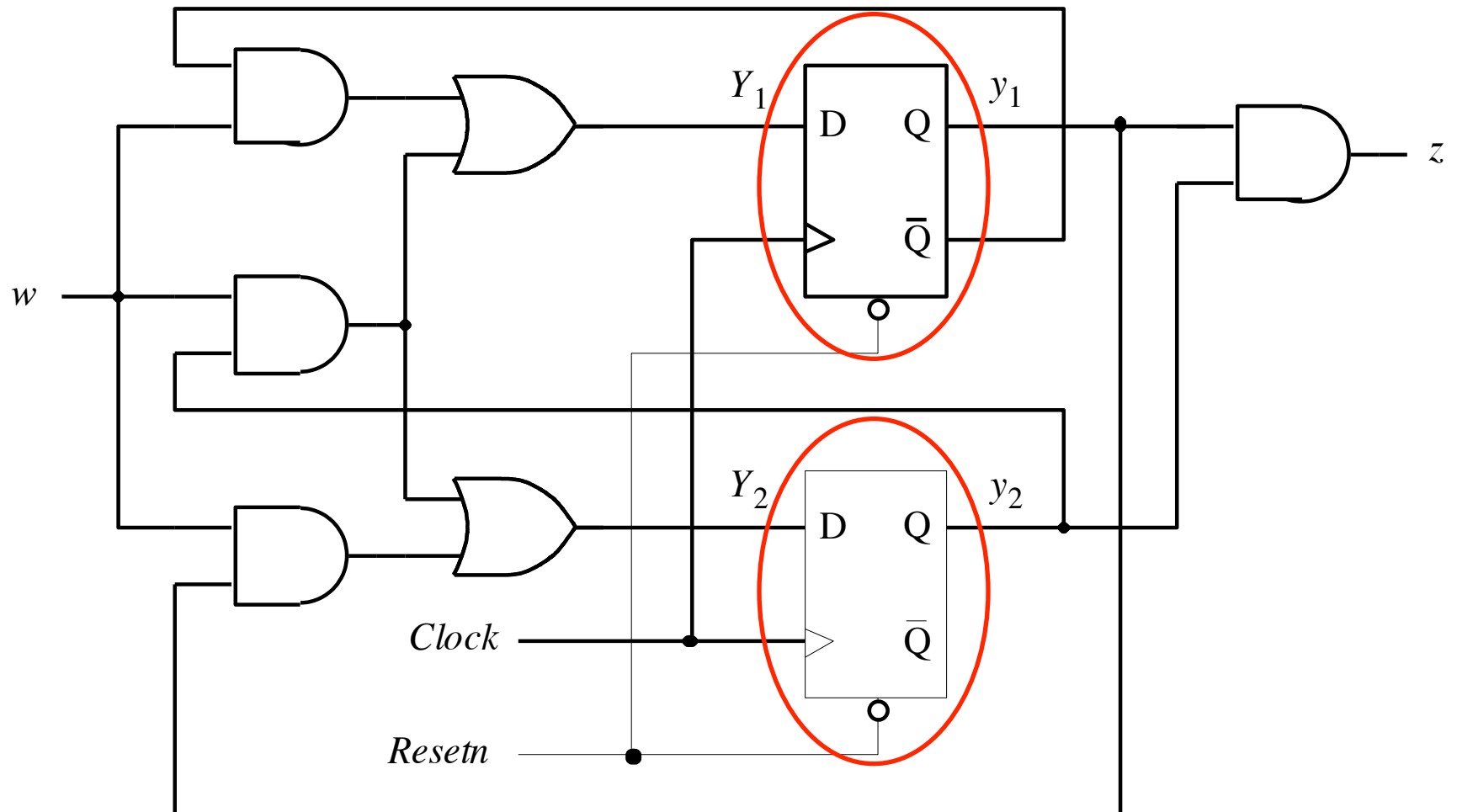
# Where are the outputs of the flip-flops?



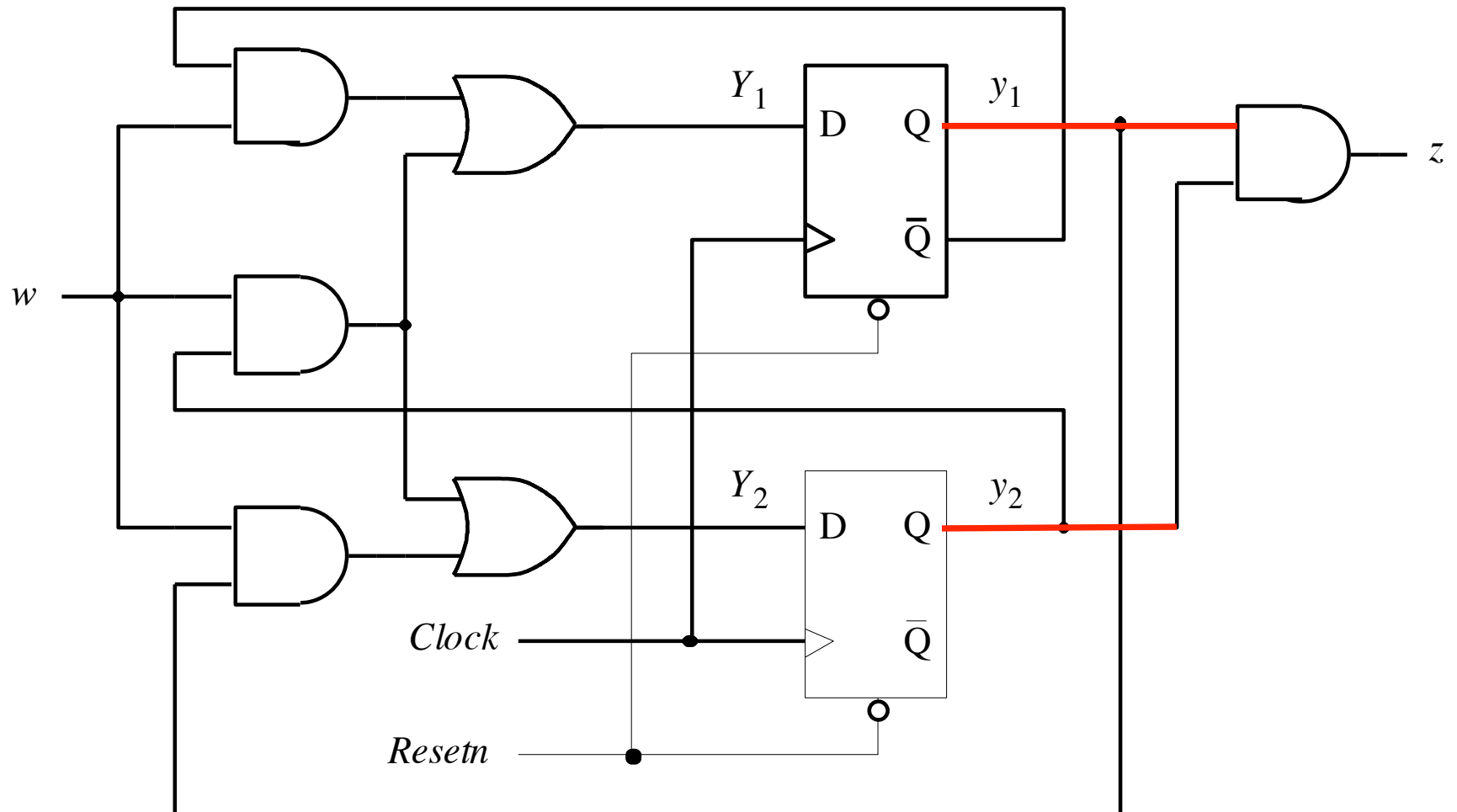
# Where are the outputs of the flip-flops?




# These are the present-state variables

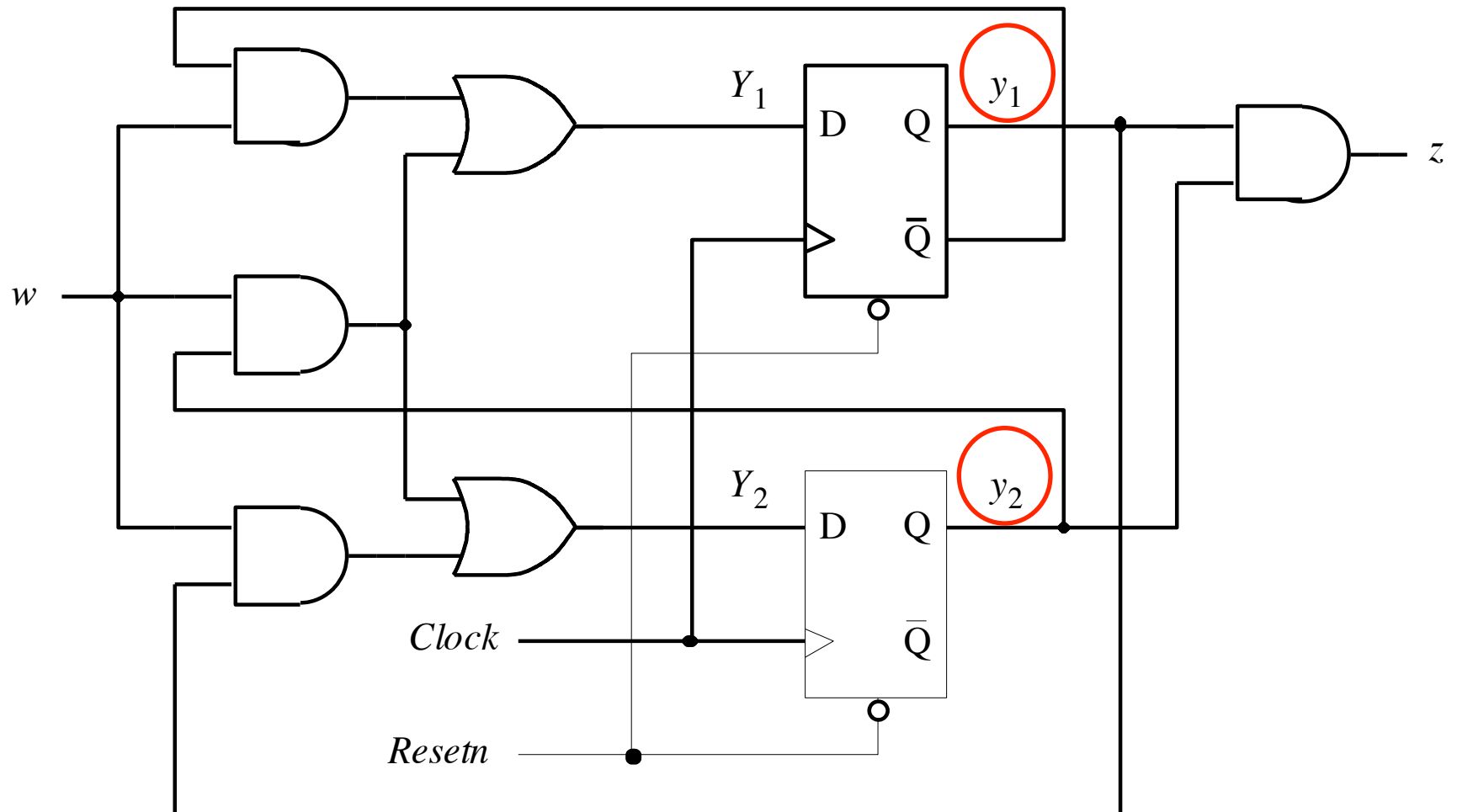

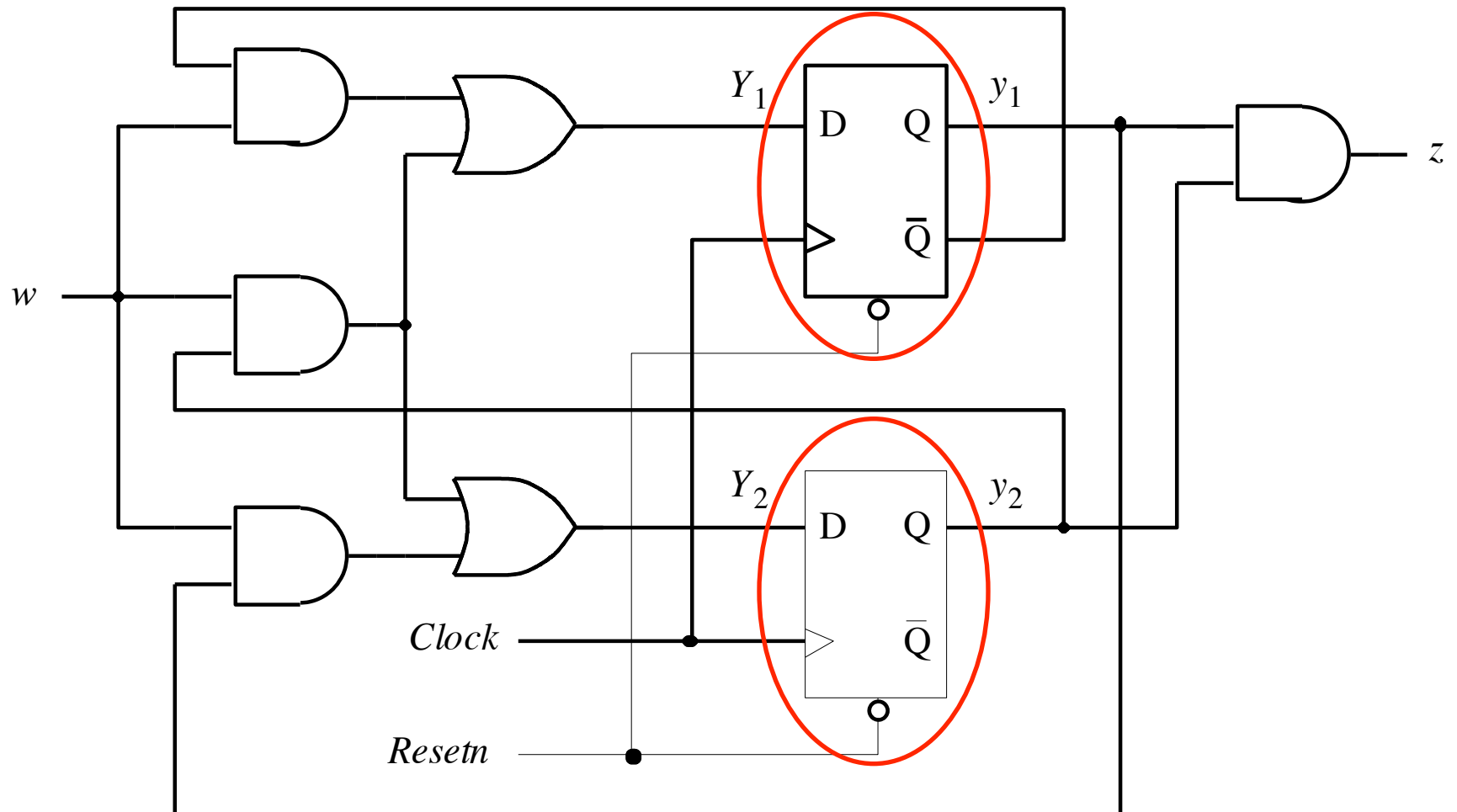
# Where are the inputs of the flip-flops?



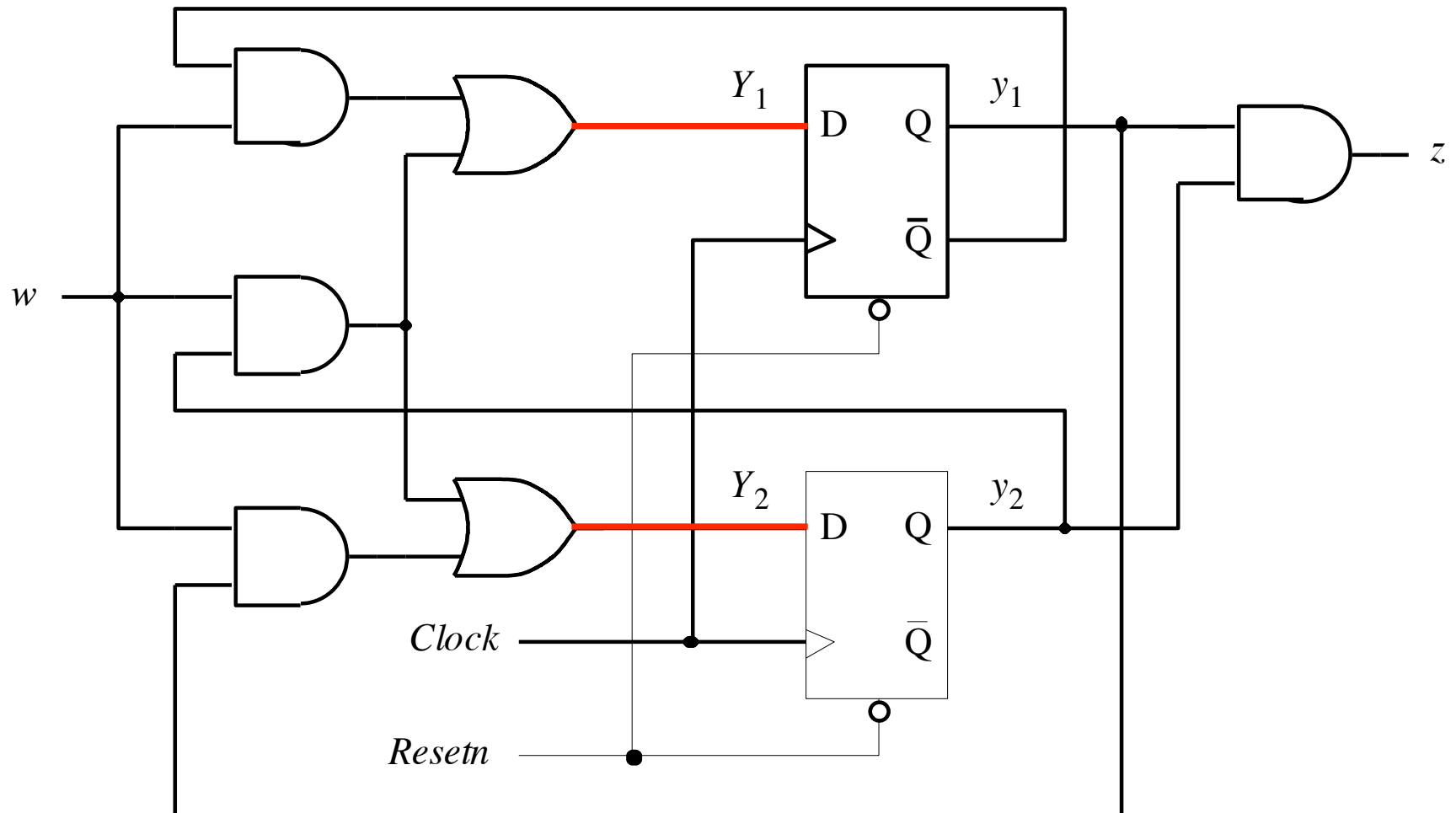
# Where are the inputs of the flip-flops?



# These are the next-state variables

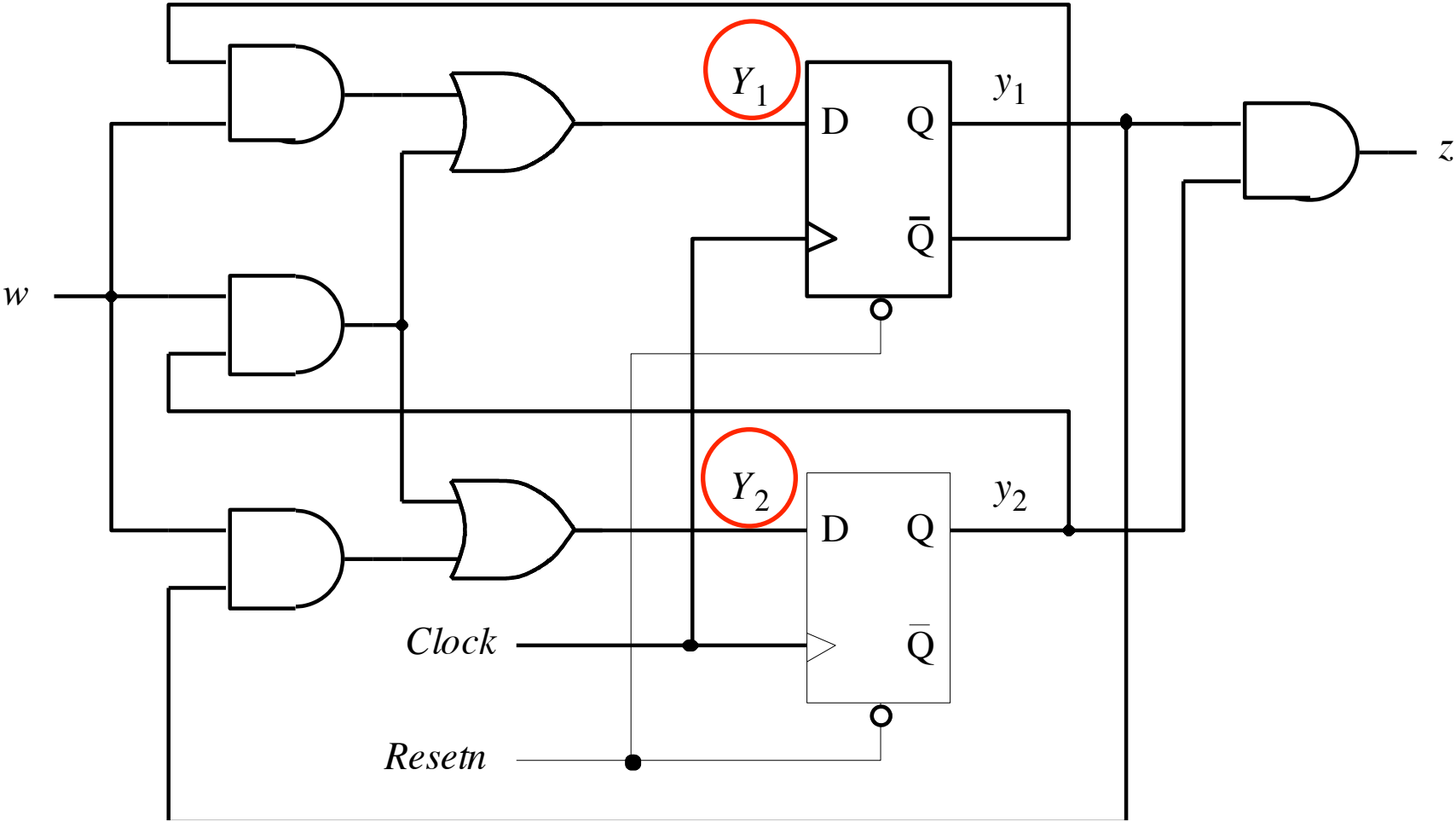


# What are their logic expressions?

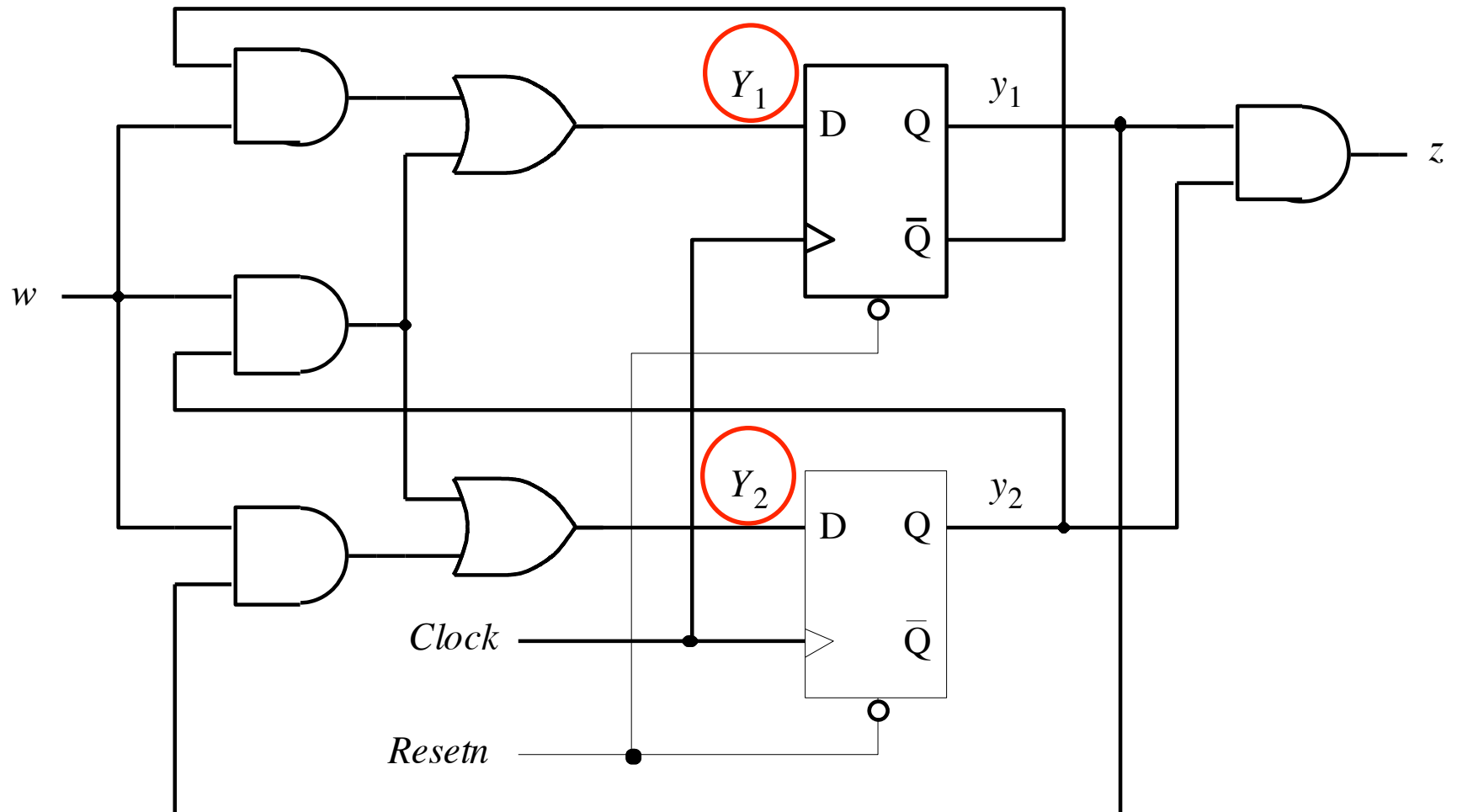

# What are their logic expressions?


$$Y_1 = w\bar{y}_1 + wy_2$$

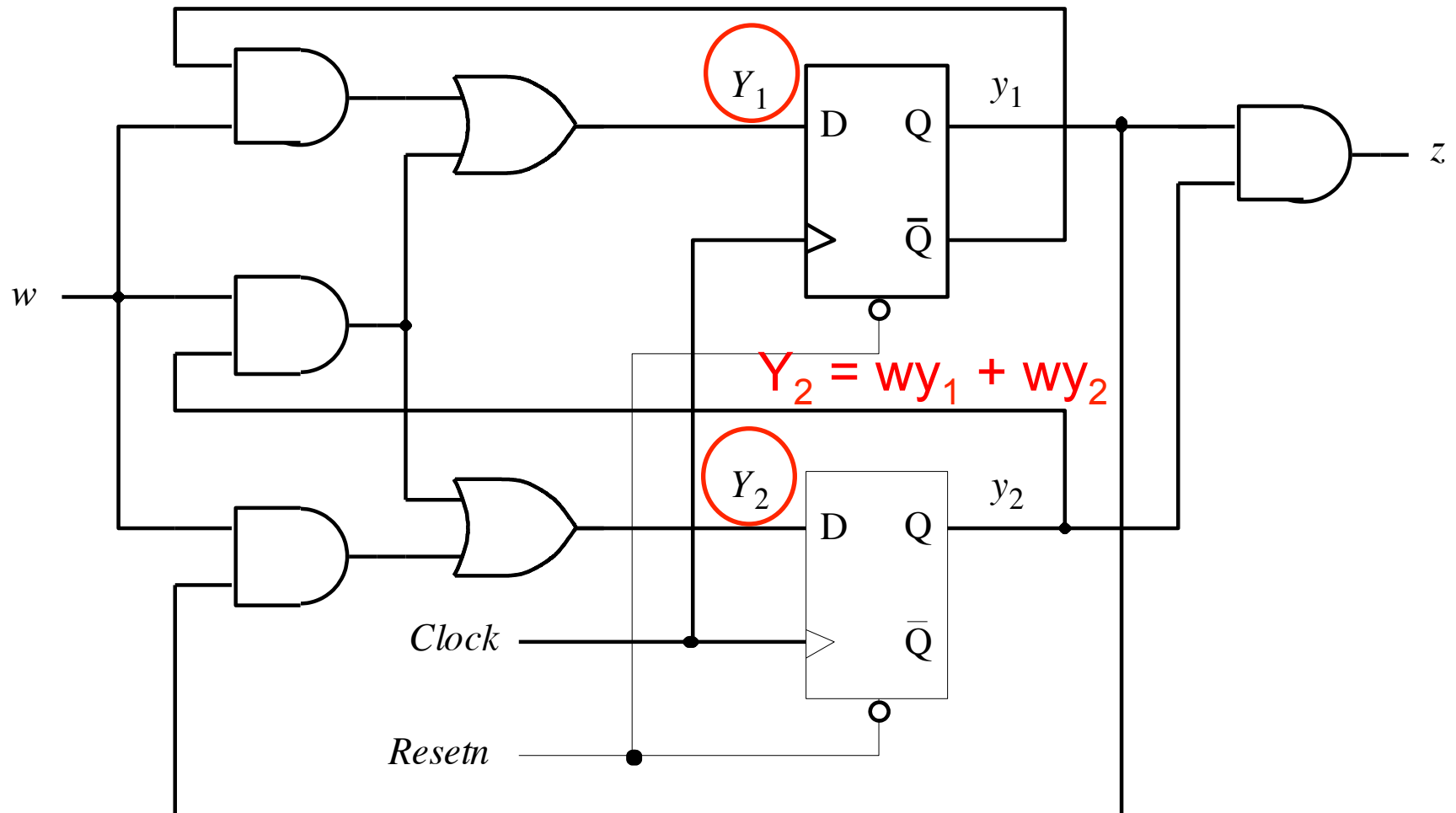


$$Y_2 = wy_1 + wy_2$$




# Where is the output, again?

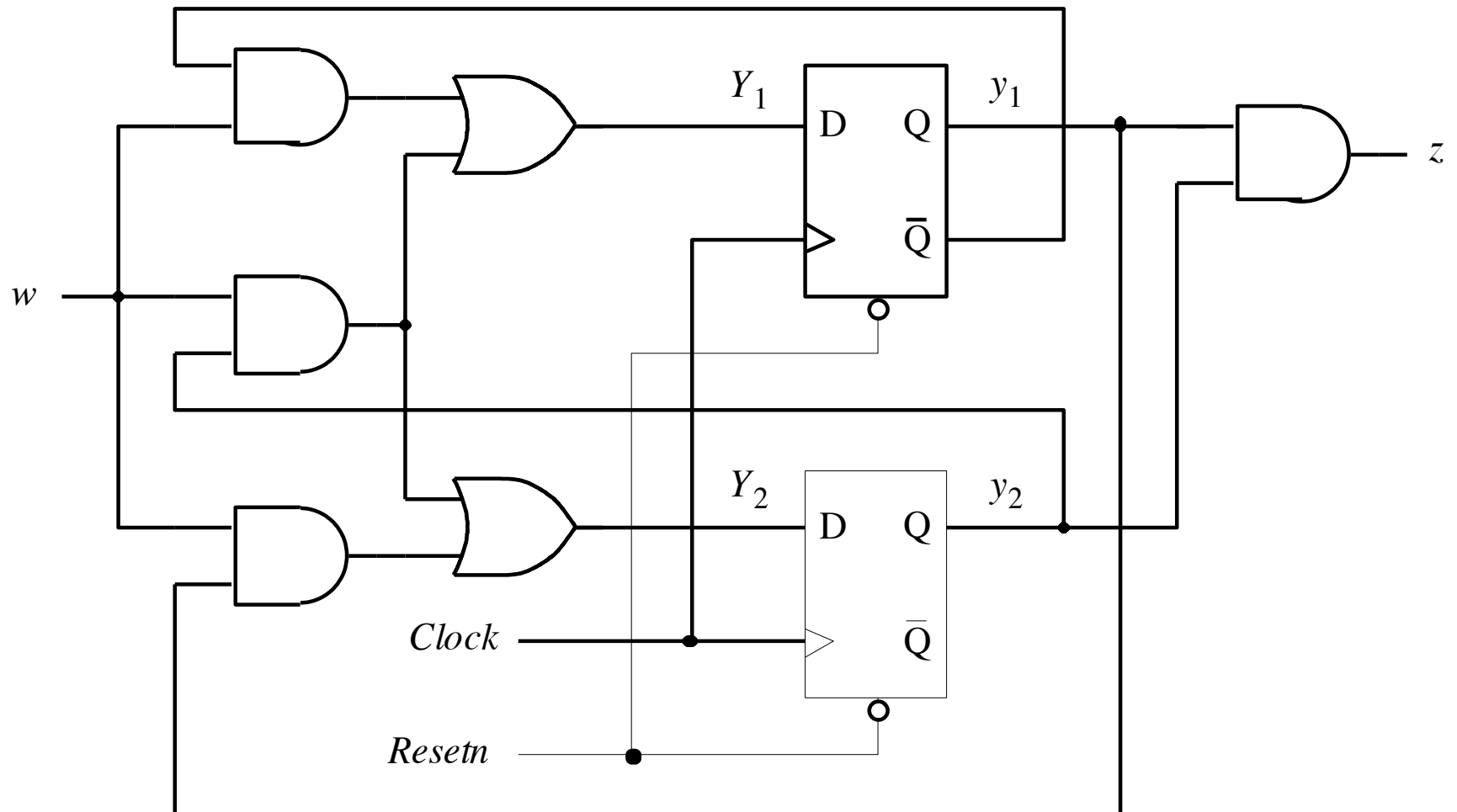


# Where is the output, again?

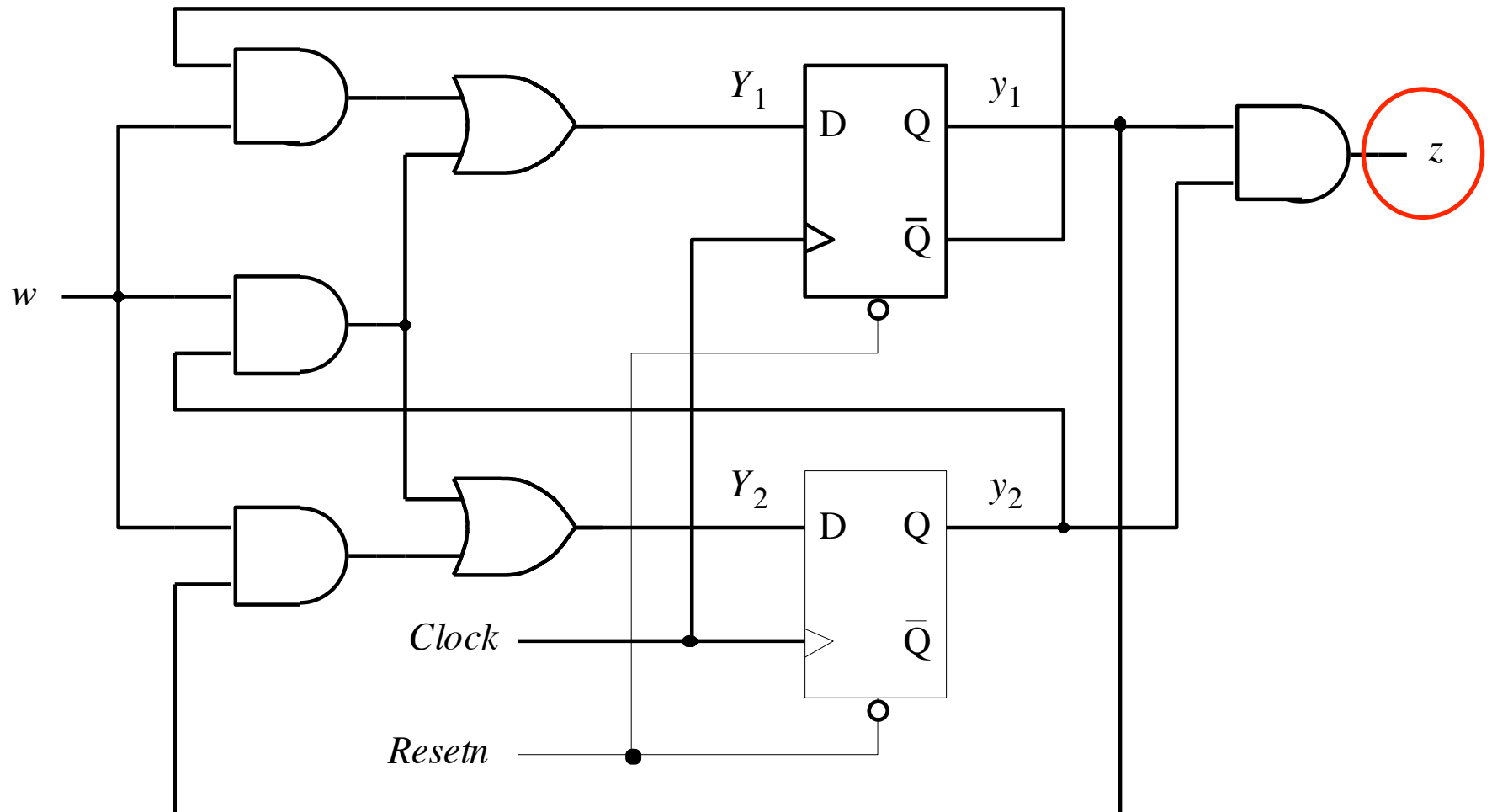

# What is its logic expression?

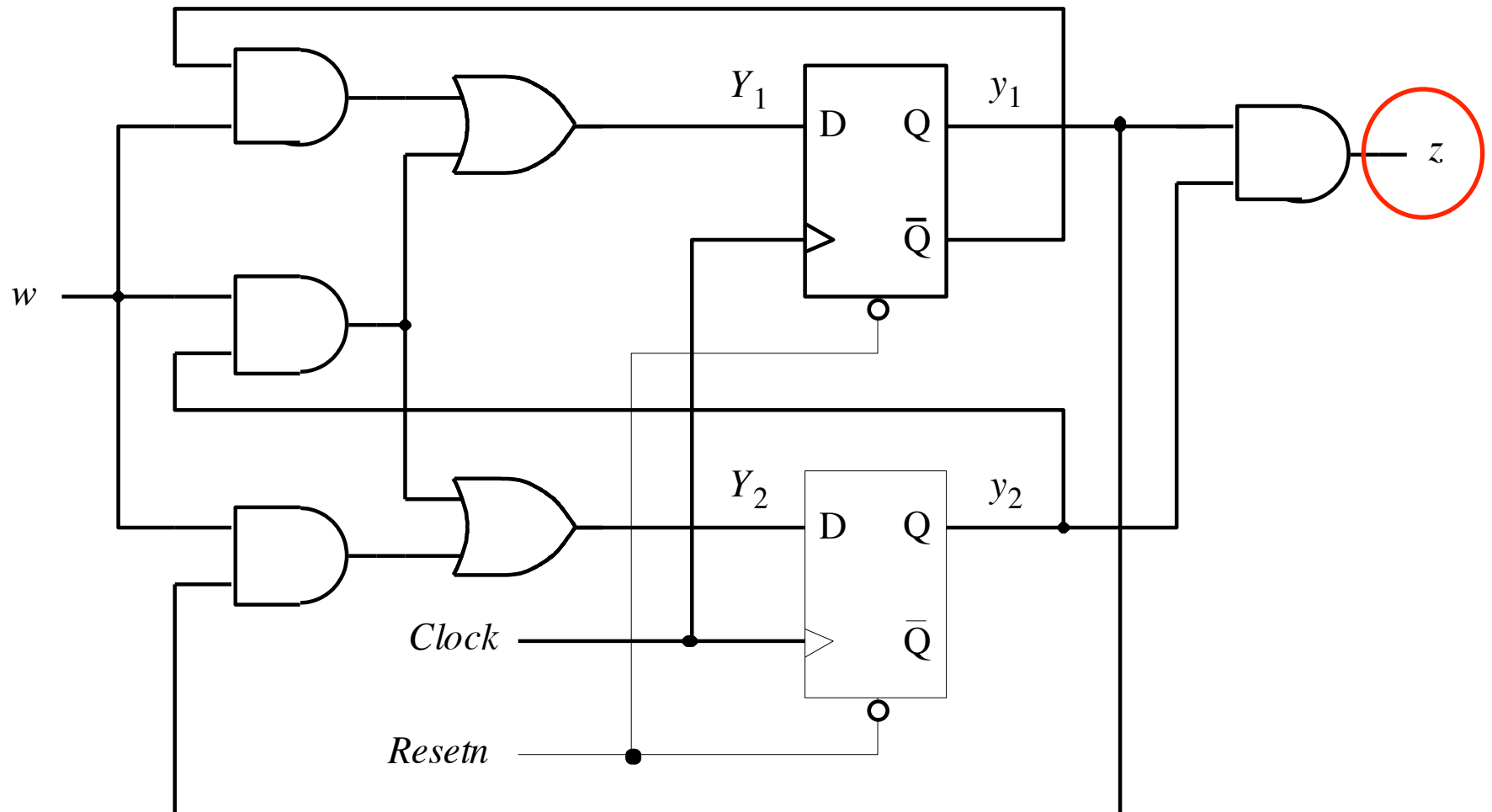

# What is its logic expression?

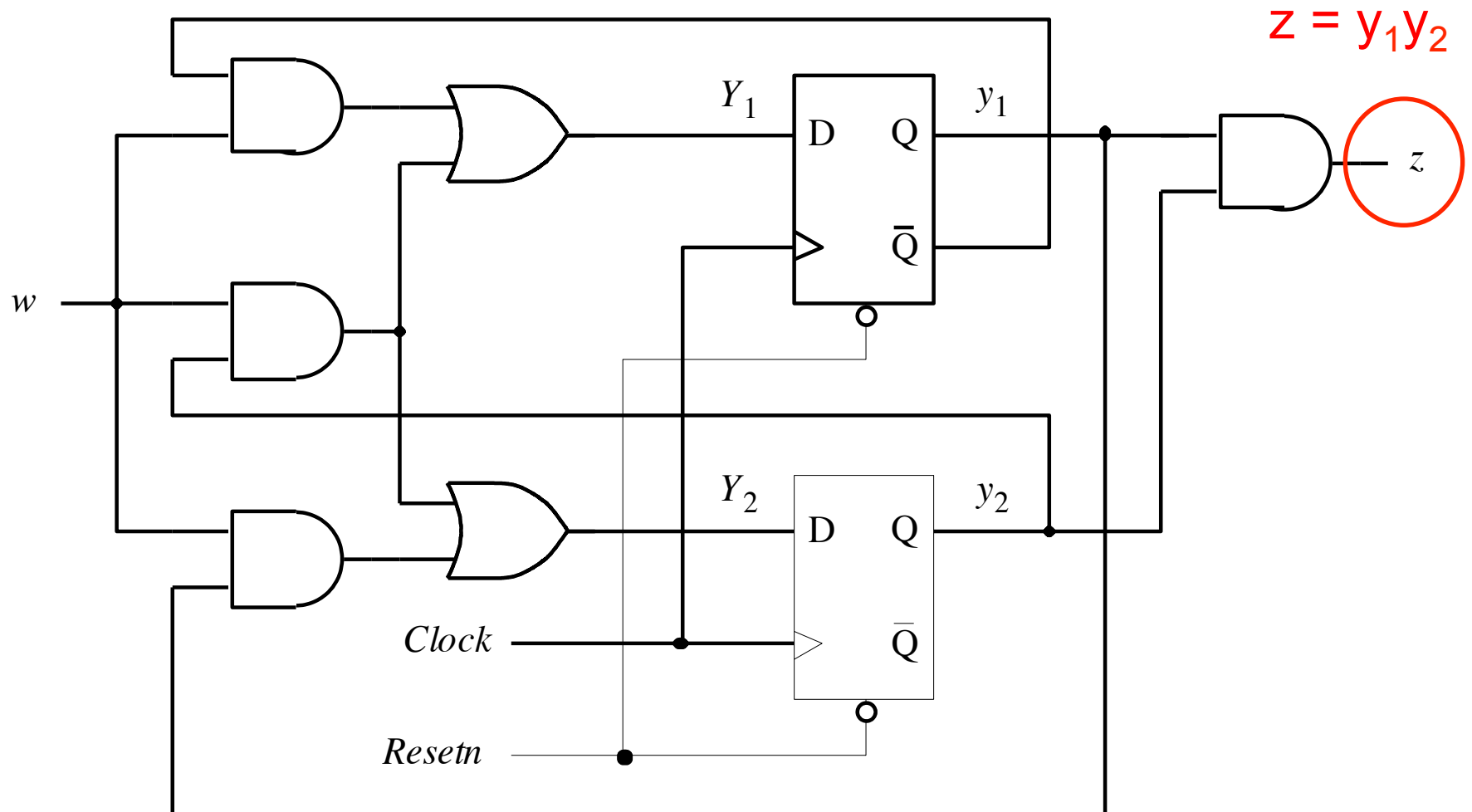

**This is what we have to work with now  
(we don't need the circuit anymore)**

$$Y_1 = w\bar{y}_1 + wy_2$$

$$Y_2 = wy_1 + wy_2$$

$$z = y_1y_2$$

# Let's derive the state-assigned table

$$Y_1 = w\bar{y}_1 + wy_2$$

$$Y_2 = wy_1 + wy_2$$

$$z = y_1y_2$$

Present state $y_2y_1$	Next State		Output $z$
	$w = 0$	$w = 1$	
	$Y_2Y_1$	$Y_2Y_1$	
00			
01			
10			
11			

# Let's derive the state-assigned table

$$Y_1 = w\bar{y}_1 + wy_2$$

$$Y_2 = wy_1 + wy_2$$

$$z = y_1y_2$$

Present state $y_2y_1$	Next State		Output $z$
	$w = 0$	$w = 1$	
00			
01			
10			
11			

# Let's derive the state-assigned table

$$Y_1 = w\bar{y}_1 + wy_2$$

$$Y_2 = wy_1 + wy_2$$

$$z = y_1y_2$$

Present state $y_2y_1$	Next State		Output $z$
	$w = 0$	$w = 1$	
	$Y_2Y_1$	$Y_2Y_1$	
00			0
01			0
10			0
11			1



# Let's derive the state-assigned table

$$Y_1 = w\bar{y}_1 + wy_2$$

$$Y_2 = wy_1 + wy_2$$

$$z = y_1y_2$$

Present state $y_2y_1$	Next State		Output $z$
	$w = 0$	$w = 1$	
	$Y_2Y_1$	$Y_2Y_1$	
00			0
01			0
10			0
11			1

# Let's derive the state-assigned table

$$Y_1 = w\bar{y}_1 + wy_2$$

$$Y_2 = wy_1 + wy_2$$

$$z = y_1y_2$$

Present state $y_2y_1$	Next State		Output $z$
	$w = 0$	$w = 1$	
	$Y_2Y_1$	$Y_2Y_1$	
00	0	1	0
01	0	0	0
10	0	1	0
11	0	1	1

# Let's derive the state-assigned table

$$Y_1 = w\bar{y}_1 + wy_2$$

$$Y_2 = wy_1 + wy_2$$

$$z = y_1y_2$$

Present state $y_2y_1$	Next State		Output $z$
	$w = 0$	$w = 1$	
	$Y_2Y_1$	$Y_2Y_1$	
00	0	1	0
01	0	0	0
10	0	1	0
11	0	1	1

# Let's derive the state-assigned table

$$Y_1 = w\bar{y}_1 + wy_2$$

$$Y_2 = wy_1 + wy_2$$

$$z = y_1y_2$$

Present state $y_2y_1$	Next State		Output $z$
	$w = 0$	$w = 1$	
	$Y_2Y_1$	$Y_2Y_1$	
00	00	01	0
01	00	10	0
10	00	11	0
11	00	11	1

# We don't need the logic expressions anymore

$$Y_1 = w\bar{y}_1 + wy_2$$

$$Y_2 = wy_1 + wy_2$$

$$z = y_1y_2$$

Present state $y_2y_1$	Next State		Output $z$
	$w = 0$	$w = 1$	
	$Y_2Y_1$	$Y_2Y_1$	
00	00	01	0
01	00	10	0
10	00	11	0
11	00	11	1

# We don't need the logic expressions anymore

Present state $y_2y_1$	Next State		Output $z$
	$w = 0$	$w = 1$	
	$Y_2Y_1$	$Y_2Y_1$	
00	00	01	0
01	00	10	0
10	00	11	0
11	00	11	1

# Let's derive the state table

Present state	Next state		Output z
	w = 0	w = 1	

State table

Present state $y_2y_1$	Next State		Output z
	w = 0 $Y_2Y_1$	w = 1 $Y_2Y_1$	
00	00	01	0
01	00	10	0
10	00	11	0
11	00	11	1

State-assigned table

# Let's derive the state table

Present state	Next state		Output z
	w = 0	w = 1	

State table

Present state $y_2y_1$	Next State		Output z
	w = 0	w = 1	
	$Y_2Y_1$	$Y_2Y_1$	
00	00	01	0
01	00	10	0
10	00	11	0
11	00	11	1

State-assigned table




# Let's derive the state table

Present state	Next state		Output z
	w = 0	w = 1	
A			
B			
C			
D			

State table

Present state	Next State		Output z
	w = 0	w = 1	
$y_2y_1$	$Y_2Y_1$	$Y_2Y_1$	
00	00	01	0
01	00	10	0
10	00	11	0
11	00	11	1

State-assigned table

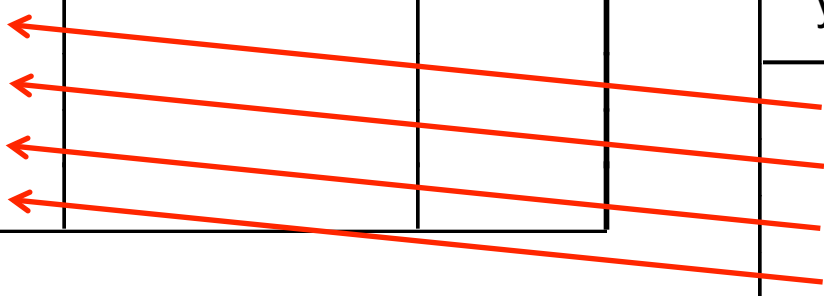

# Let's derive the state table

Present state	Next state		Output z
	w = 0	w = 1	
A			
B			
C			
D			

State table

Present state $y_2y_1$	Next State		Output z
	w = 0 $Y_2Y_1$	w = 1 $Y_2Y_1$	
00	00	01	0
01	00	10	0
10	00	11	0
11	00	11	1

State-assigned table


# Let's derive the state table

Present state	Next state		Output z
	w = 0	w = 1	
A	A		
B	A		
C	A		
D	A		

State table

Present state	Next State		Output z
	w = 0	w = 1	
$y_2y_1$	$Y_2Y_1$	$Y_2Y_1$	
00	00	01	0
01	00	10	0
10	00	11	0
11	00	11	1

State-assigned table

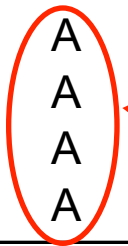

# Let's derive the state table

Present state	Next state		Output z
	w = 0	w = 1	
A	A		
B	A		
C	A		
D	A		

State table

Present state $y_2y_1$	Next State		Output z
	w = 0 $Y_2Y_1$	w = 1 $Y_2Y_1$	
00	00	01	0
01	00	10	0
10	00	11	0
11	00	11	1

State-assigned table


# Let's derive the state table

Present state	Next state		Output z
	w = 0	w = 1	
A	A	B	
B	A	C	
C	A	D	
D	A	D	

State table

Present state	Next State		Output z
	w = 0	w = 1	
$y_2y_1$	$Y_2Y_1$	$Y_2Y_1$	
00	00	01	0
01	00	10	0
10	00	11	0
11	00	11	1

State-assigned table

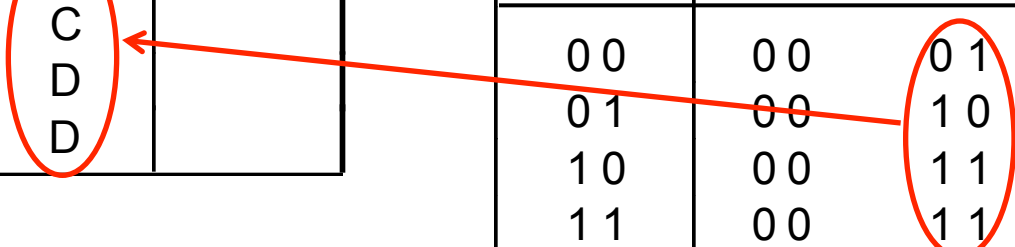

# Let's derive the state table

Present state	Next state		Output z
	w = 0	w = 1	
A	A	B	
B	A	C	
C	A	D	
D	A	D	

State table

Present state $y_2y_1$	Next State		Output z
	w = 0	w = 1	
$Y_2Y_1$	$Y_2Y_1$	$Y_2Y_1$	
00	00	01	0
01	00	10	0
10	00	11	0
11	00	11	1

State-assigned table

# Let's derive the state table

Present state	Next state		Output z
	w = 0	w = 1	
A	A	B	
B	A	C	
C	A	D	
D	A	D	

State table

Present state $y_2y_1$	Next State		Output z
	w = 0	w = 1	
	$Y_2Y_1$	$Y_2Y_1$	
00	00	01	0
01	00	10	0
10	00	11	0
11	00	11	1

State-assigned table

The output is the same in both tables

# The two tables for the initial circuit

Present state	Next state		Output Z
	w = 0	w = 1	
A	A	B	0
B	A	C	0
C	A	D	0
D	A	D	1

State table

Present state $y_2y_1$	Next State		Output Z
	w = 0	w = 1	
	$Y_2Y_1$	$Y_2Y_1$	
00	00	01	0
01	00	10	0
10	00	11	0
11	00	11	1

State-assigned table



# We don't need the state-assigned table anymore

Present state	Next state		Output Z
	w = 0	w = 1	
A	A	B	0
B	A	C	0
C	A	D	0
D	A	D	1

State table

Present state $y_2y_1$	Next State		Output Z
	w = 0	w = 1	
$Y_2Y_1$	$Y_2Y_1$	$Y_2Y_1$	
00	00	01	0
01	00	10	0
10	00	11	0
11	00	11	1

State-assigned table

# We don't need the state-assigned table anymore

Present state	Next state		Output z
	w = 0	w = 1	
A	A	B	0
B	A	C	0
C	A	D	0
D	A	D	1

State table

# Let's Draw the State Diagram

Present state	Next state		Output z
	w = 0	w = 1	
A	A	B	0
B	A	C	0
C	A	D	0
D	A	D	1

# Let's Draw the State Diagram

Present state	Next state		Output z
	w = 0	w = 1	
A	A	B	0
B	A	C	0
C	A	D	0
D	A	D	1

Because this is a Moore machine the output is tied to the state

A / 0

B / 0

C / 0

D / 1

# Let's Draw the State Diagram

Present state	Next state		Output Z
	w = 0	w = 1	
A	A	B	0
B	A	C	0
C	A	D	0
D	A	D	1

A / 0

B / 0

C / 0


D / 1

All transitions when the input w is equal to 1

# Let's Draw the State Diagram


Present state	Next state		Output z
	w = 0	w = 1	
A	A	B	0
B	A	C	0
C	A	D	0
D	A	D	1

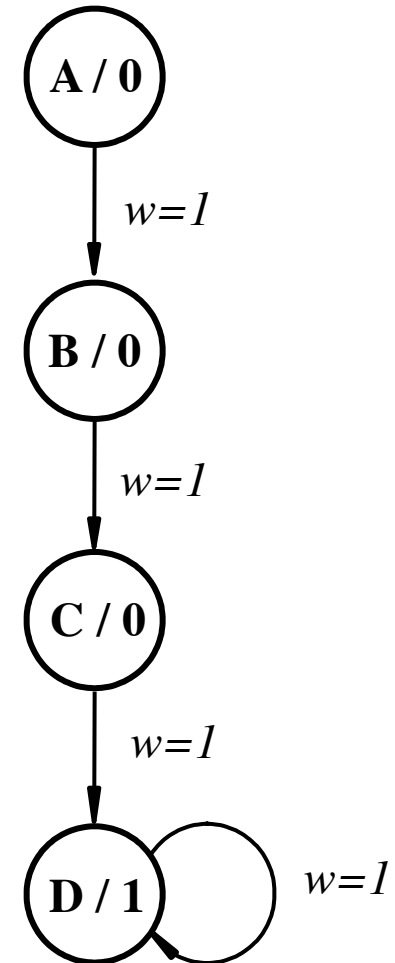All transitions when the input  $w$  is equal to 1



# Let's Draw the State Diagram


Present state	Next state		Output Z
	w = 0	w = 1	
A	A	B	0
B	A	C	0
C	A	D	0
D	A	D	1

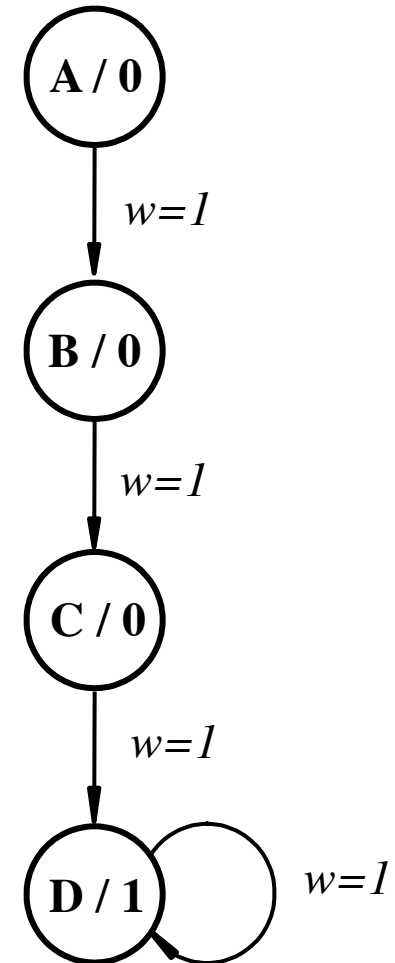

All transitions when the input  $w$  is equal to 0

# Let's Draw the State Diagram

Present state	Next state		Output z
	w = 0	w = 1	
A	A	B	0
B	A	C	0
C	A	D	0
D	A	D	1

 


All transitions when the input  $w$  is equal to 0



# We are done!

Present state	Next state		Output z
	w = 0	w = 1	
A	A	B	0
B	A	C	0
C	A	D	0
D	A	D	1

State table

 


State diagram

# Almost done. What does this FSM do?

Present state	Next state		Output $z$
	$w = 0$	$w = 1$	
A	A	B	0
B	A	C	0
C	A	D	0
D	A	D	1

State table

 


State diagram

# Almost done. What does this FSM do?

It sets the output  $z$  to 1 when three consecutive 1's occur on the input  $w$ . In other words, it is a sequence detector for the input pattern 111.

Present state	Next state		Output $z$
	$w = 0$	$w = 1$	
A	A	B	0
B	A	C	0
C	A	D	0
D	A	D	1


State table

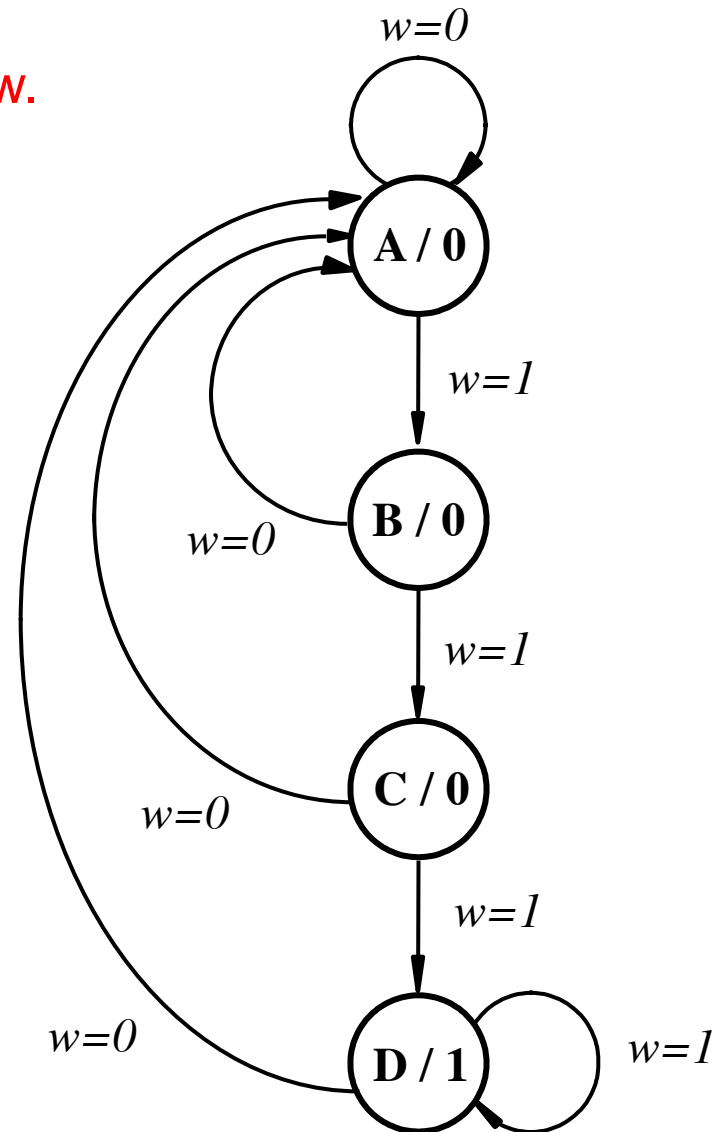

State diagram

# **Another Example (with JK flip-flops)**

# What does this circuit do?

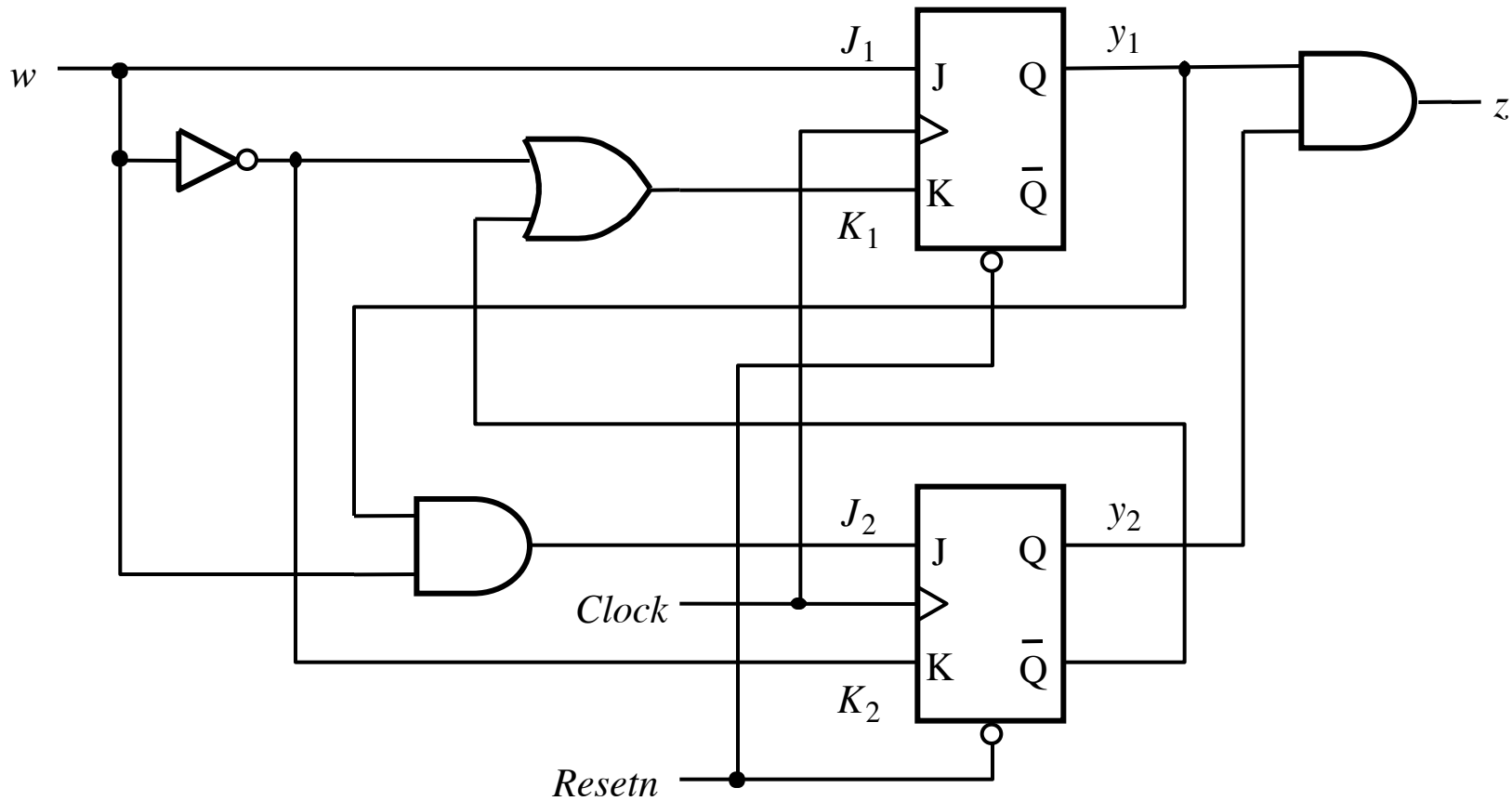


[ Figure 6.77 from the textbook ]

# Approach


- **Find the flip-flops**
- **Outputs of the flip-flops = present state variables**
- **Inputs of the flip-flops determine the next state variables**
- **Determine the logical expressions for the outputs**
- **Given this info it is easy to do the state-assigned table**
- **Next do the state table**
- **Finally, draw the state diagram.**

# Where are the inputs and outputs?

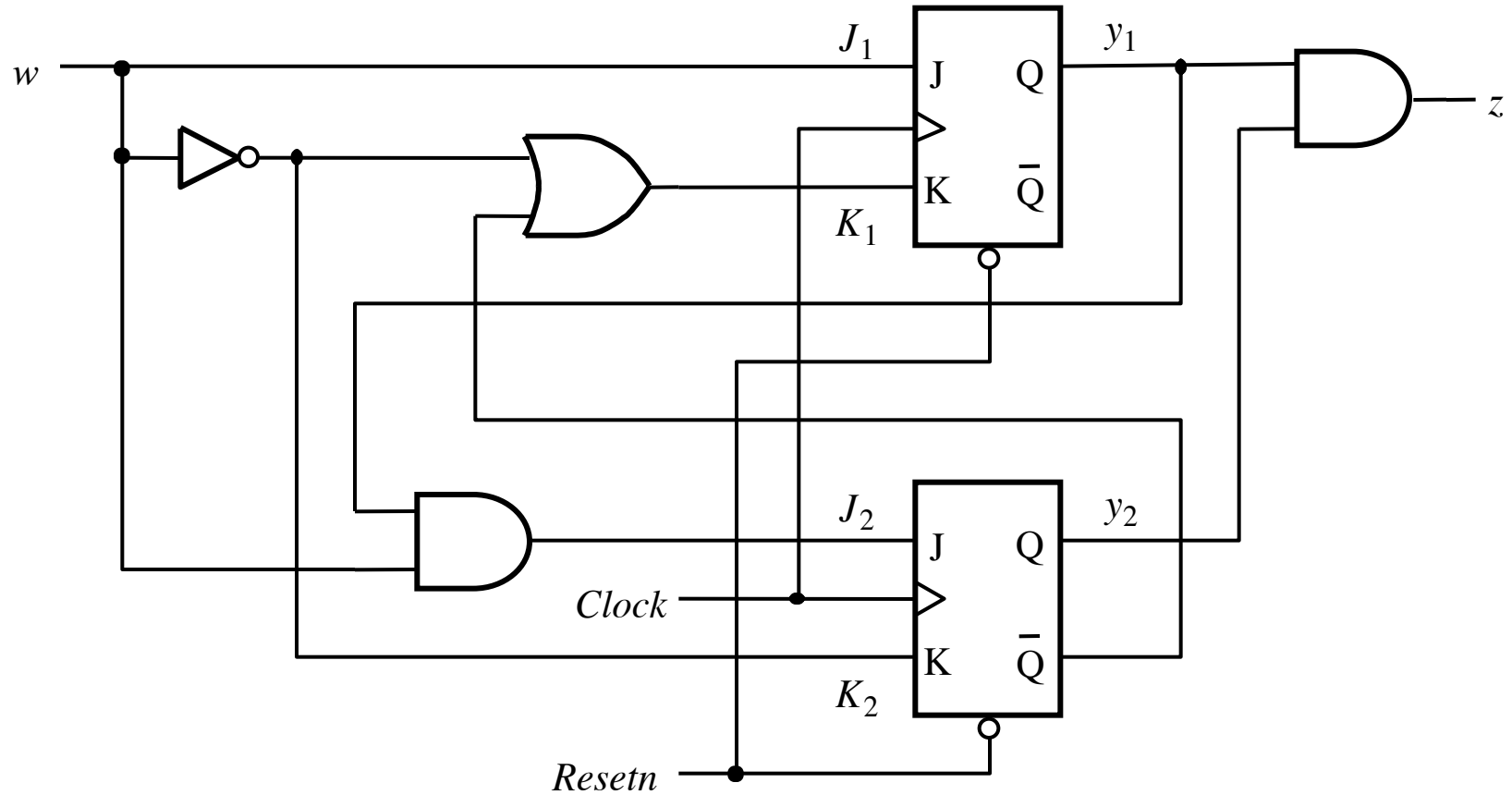


[ Figure 6.77 from the textbook ]

# Where are the inputs and outputs?

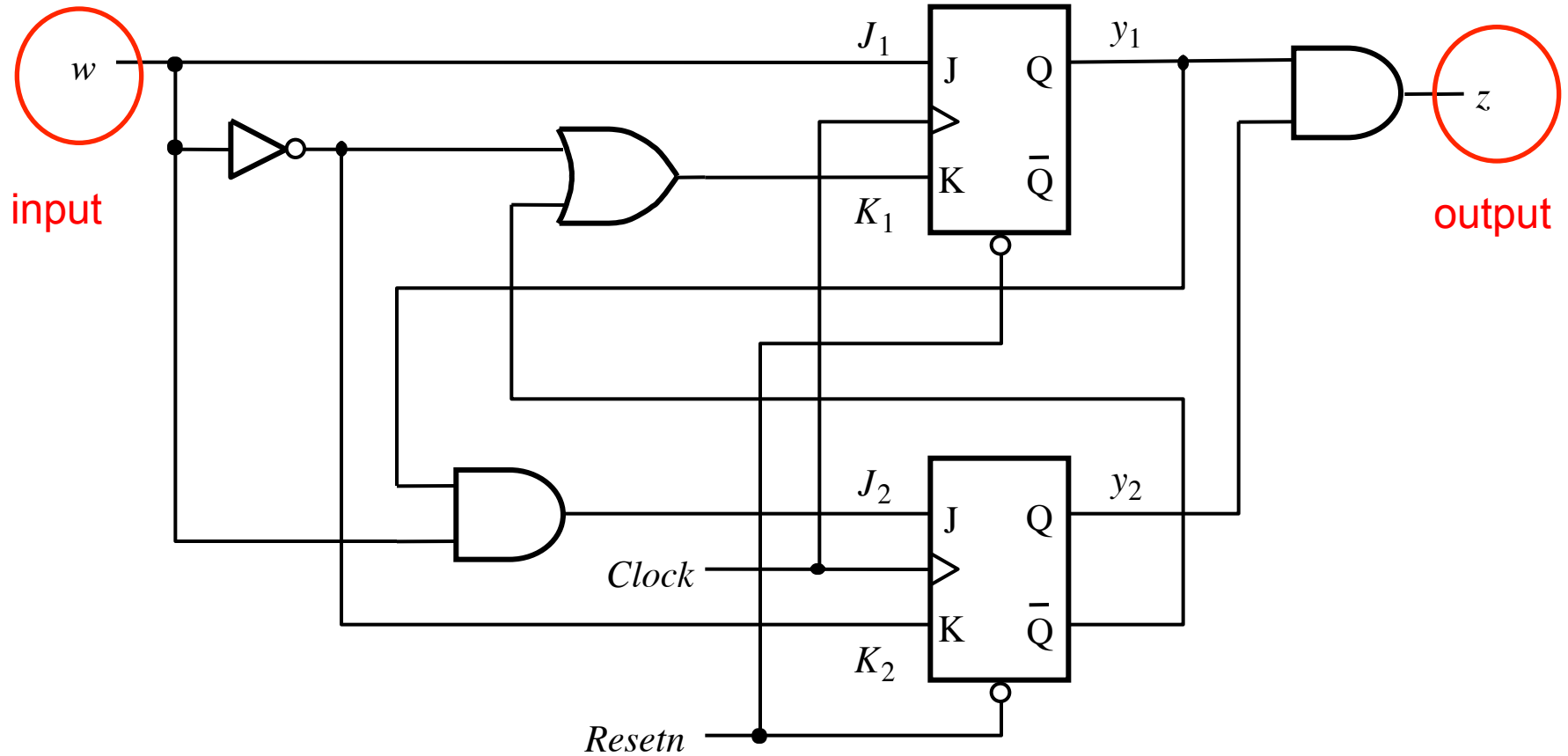





# What kind of machine is this?

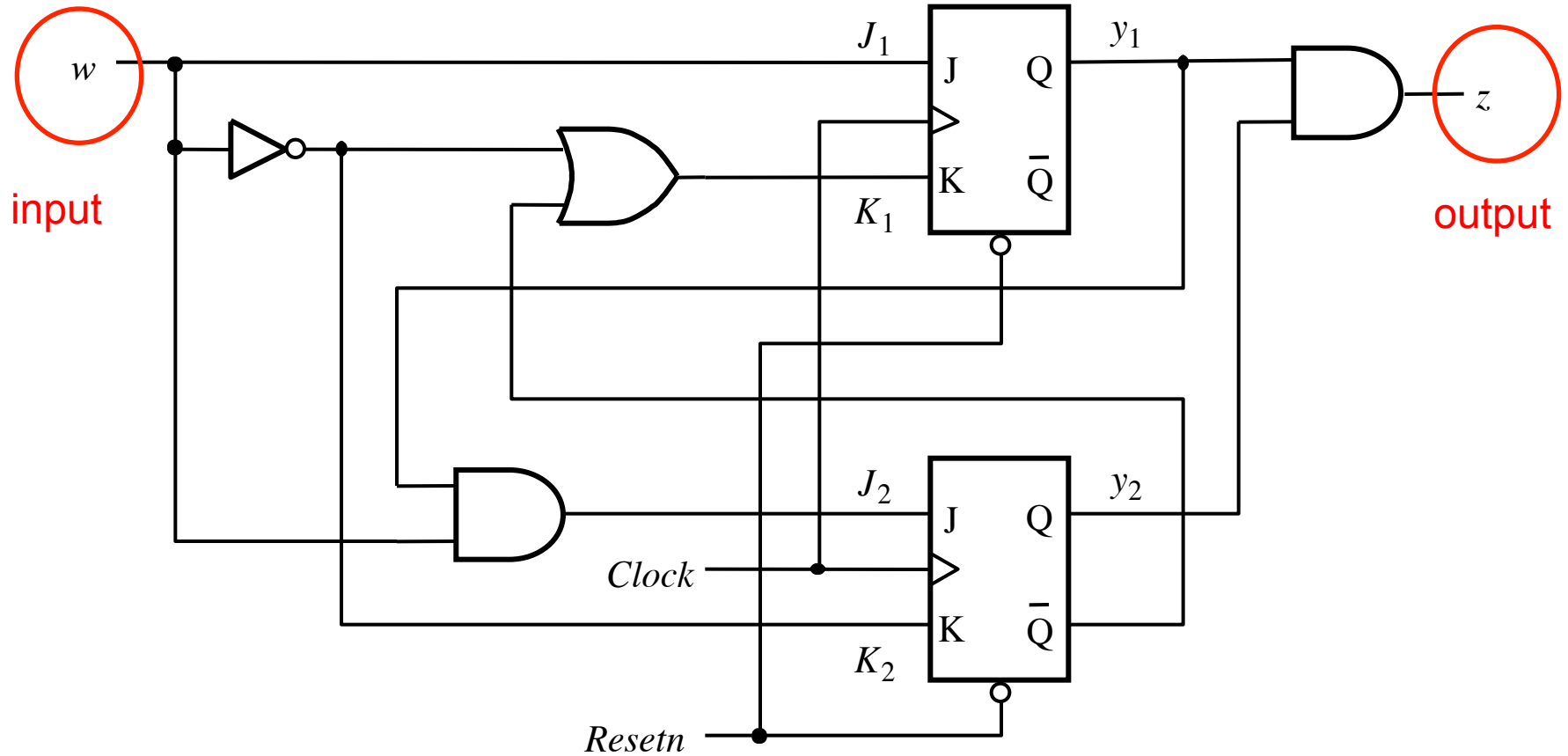


# Where are the flip-flops?

 


# Where are the flip-flops?

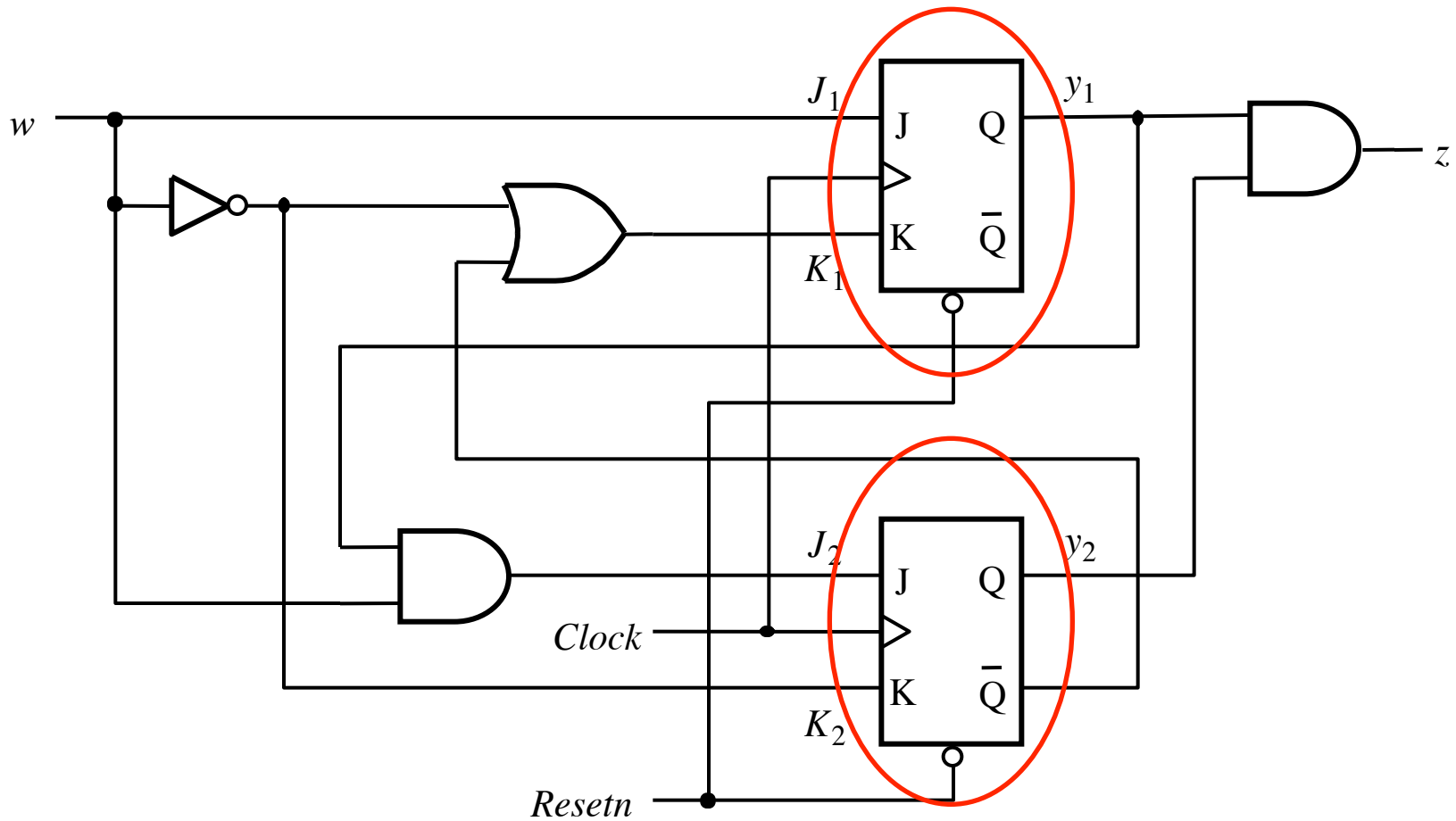

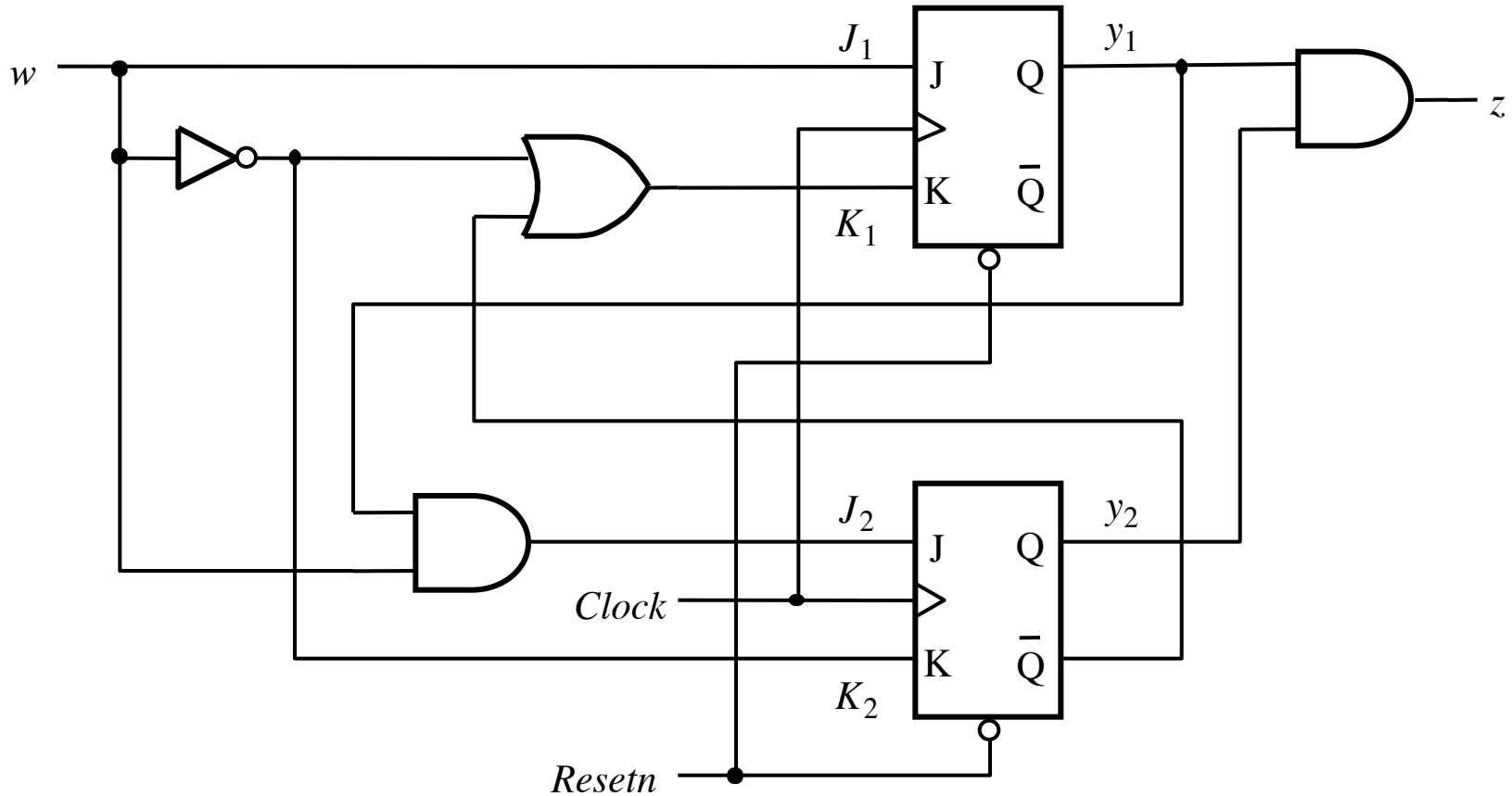
# Where are the outputs of the flip-flops?



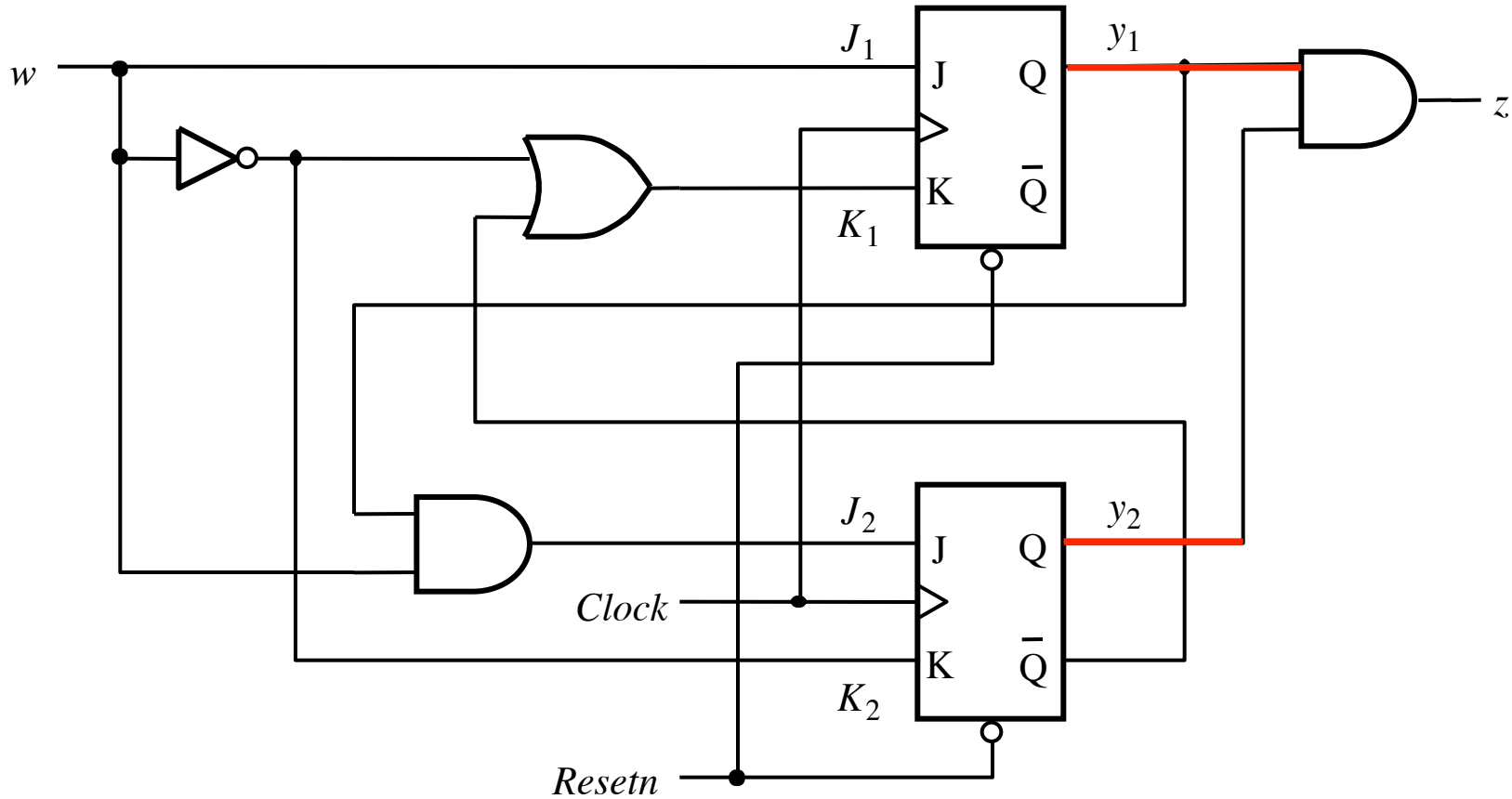
# Where are the outputs of the flip-flops?




# These are the next-state variables

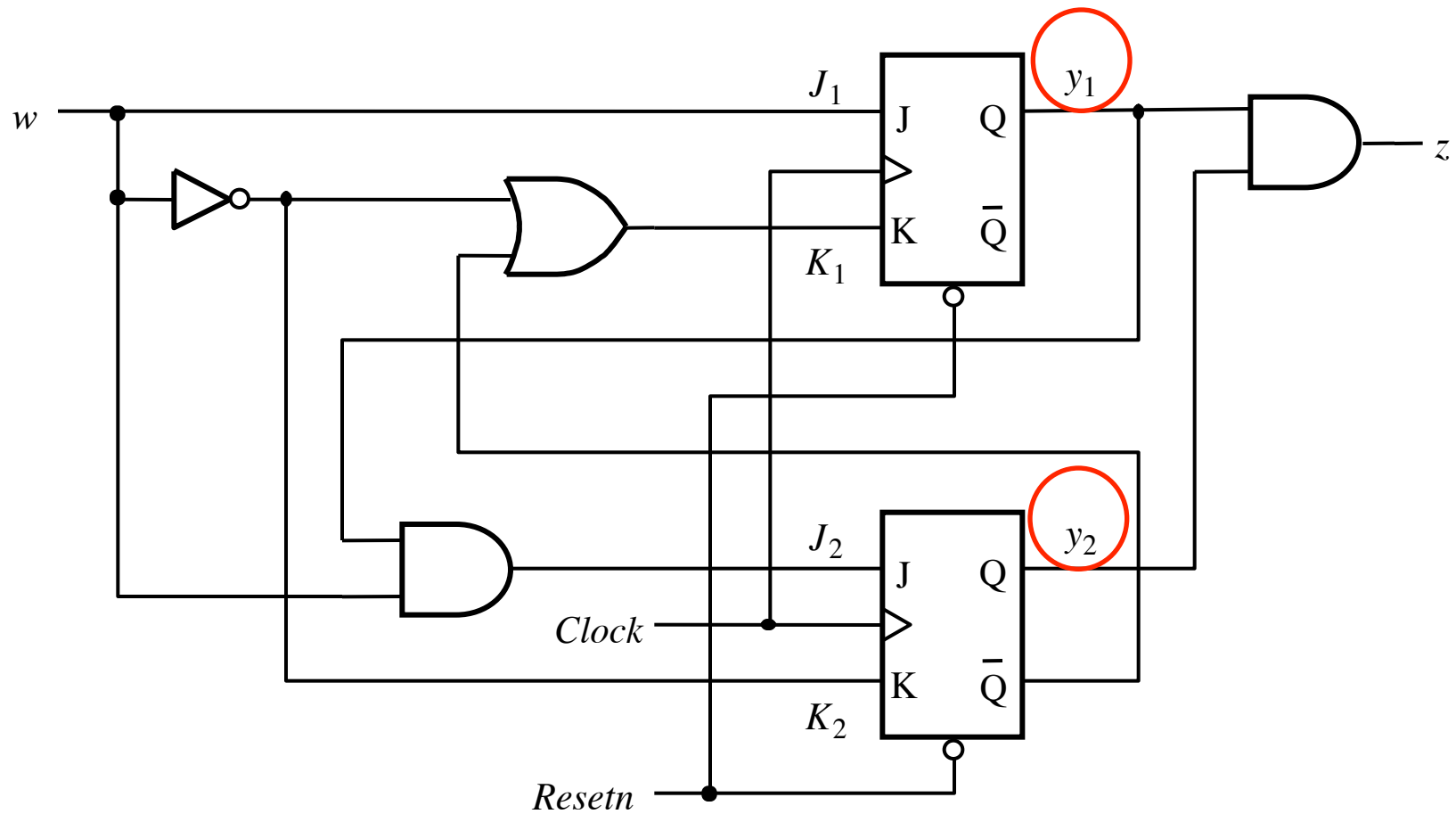
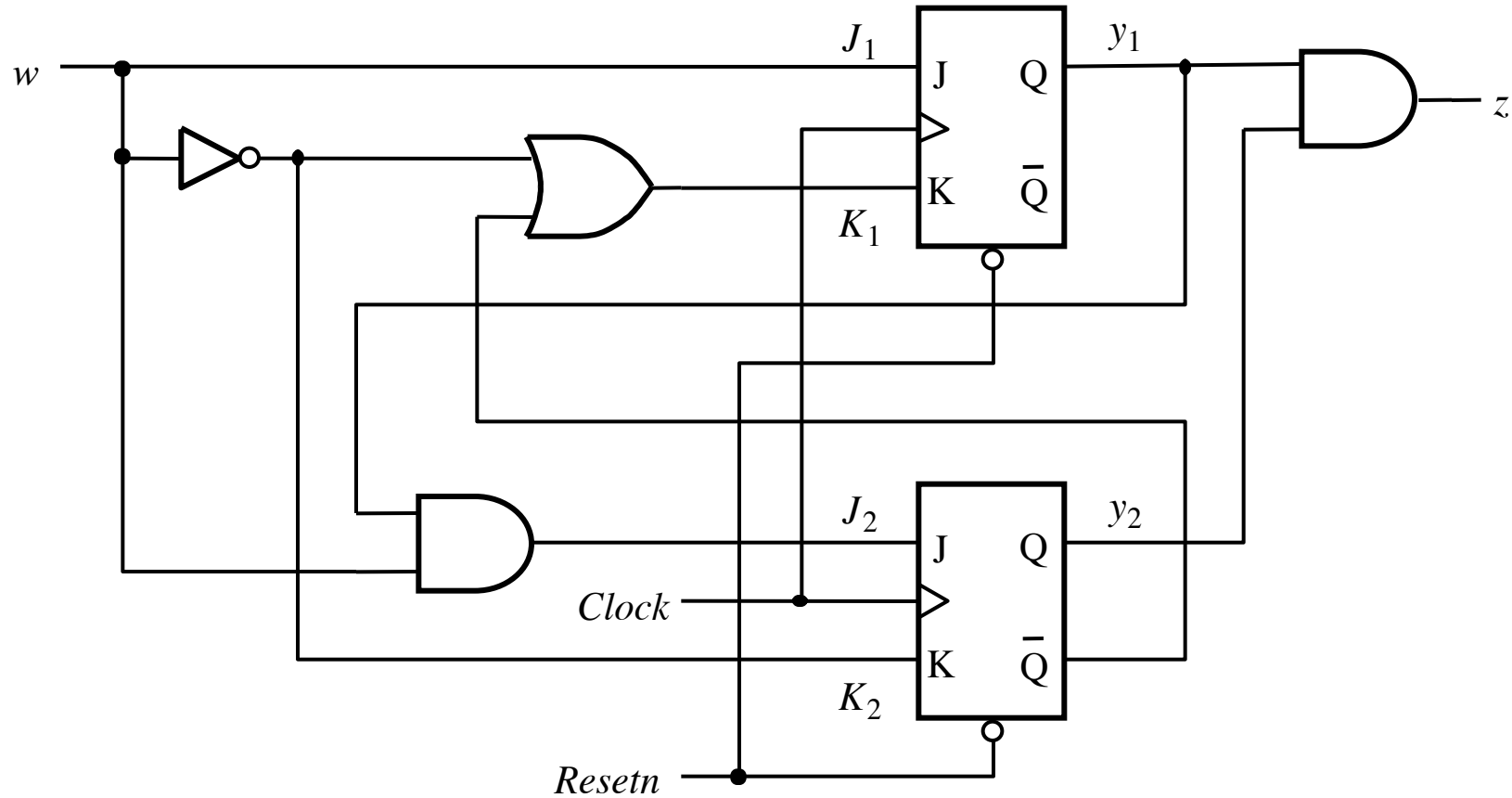
# Where are the inputs of the flip-flops?



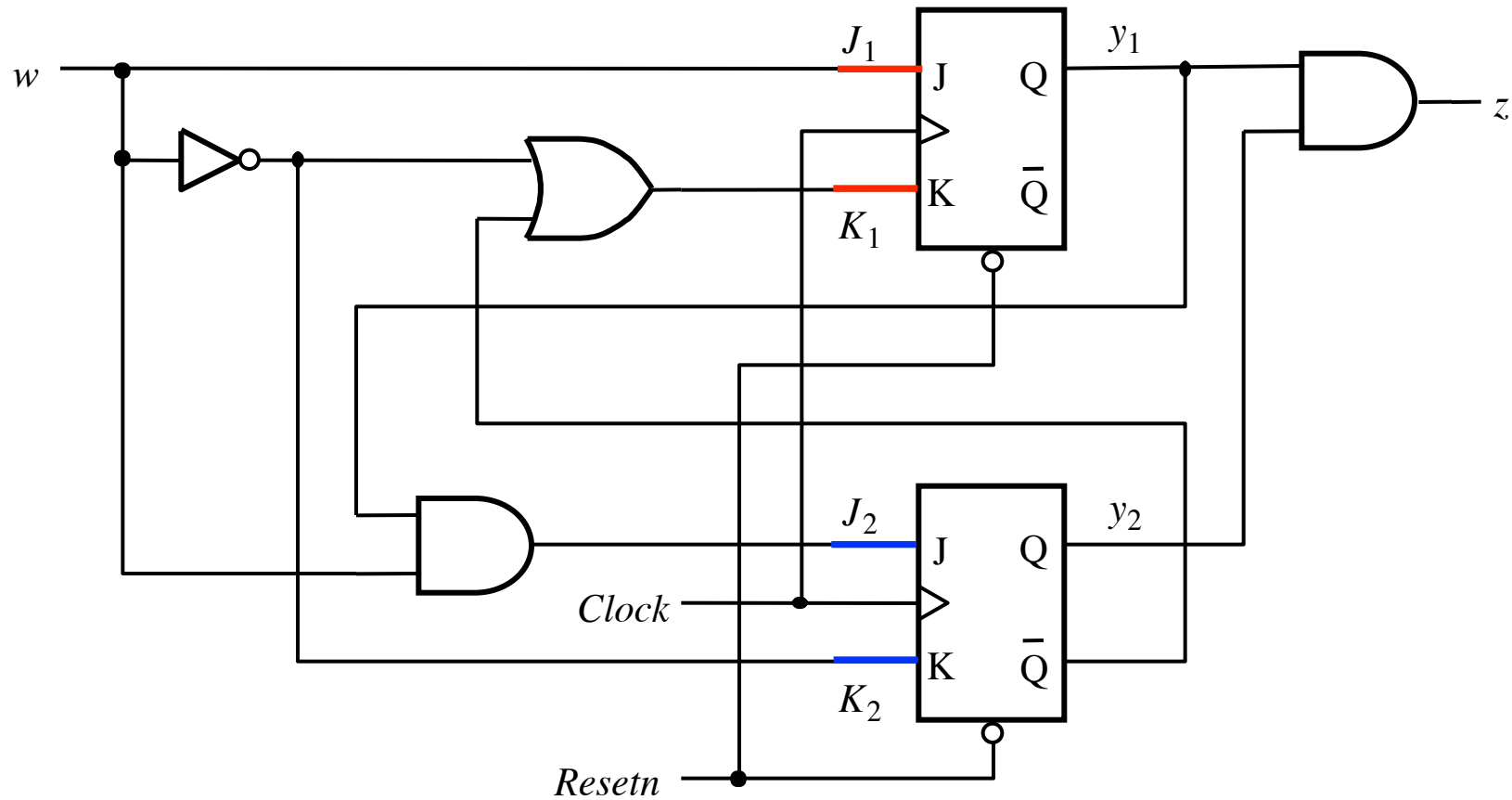
# Where are the inputs of the flip-flops?






# What are their logic expressions?

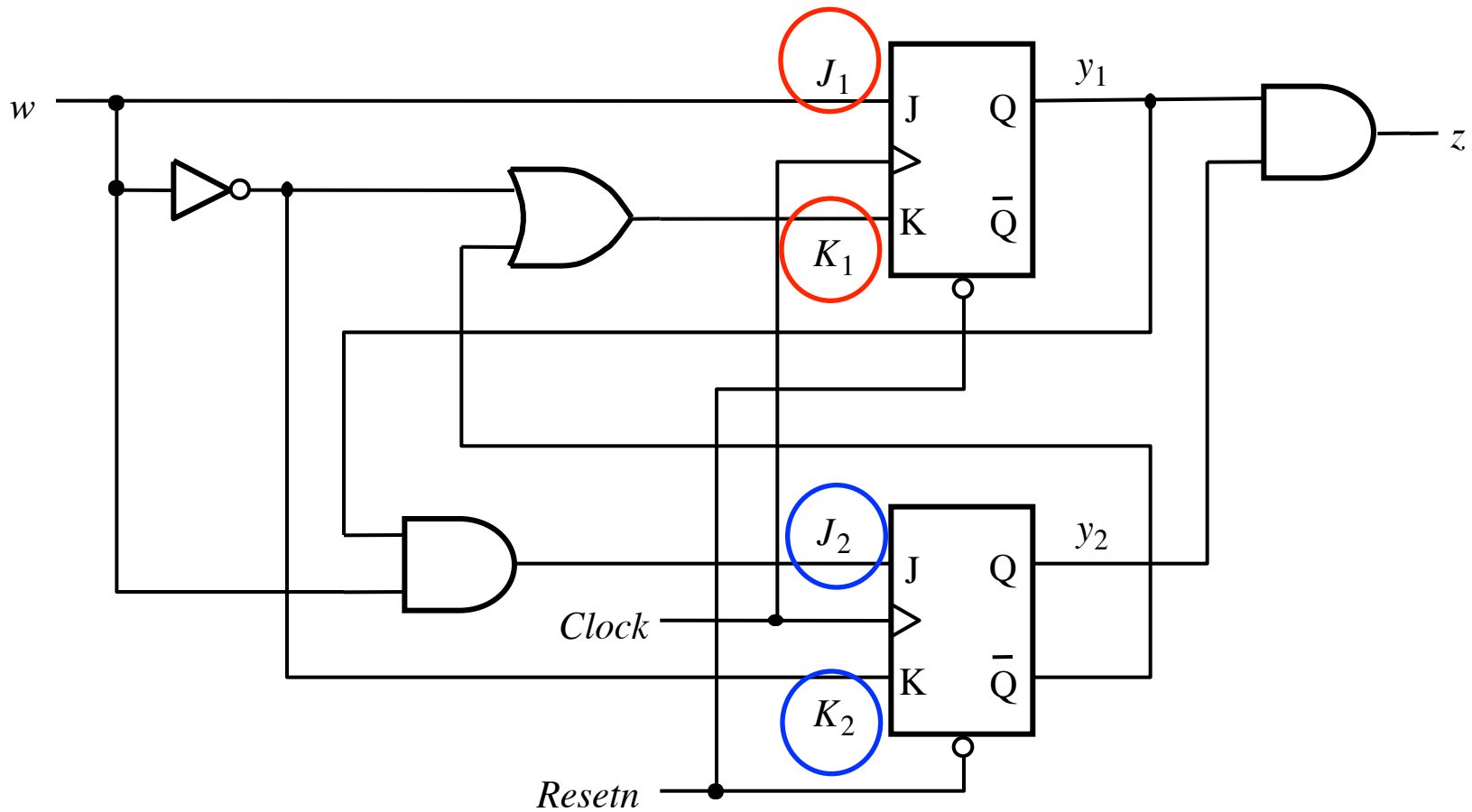

# What are their logic expressions?

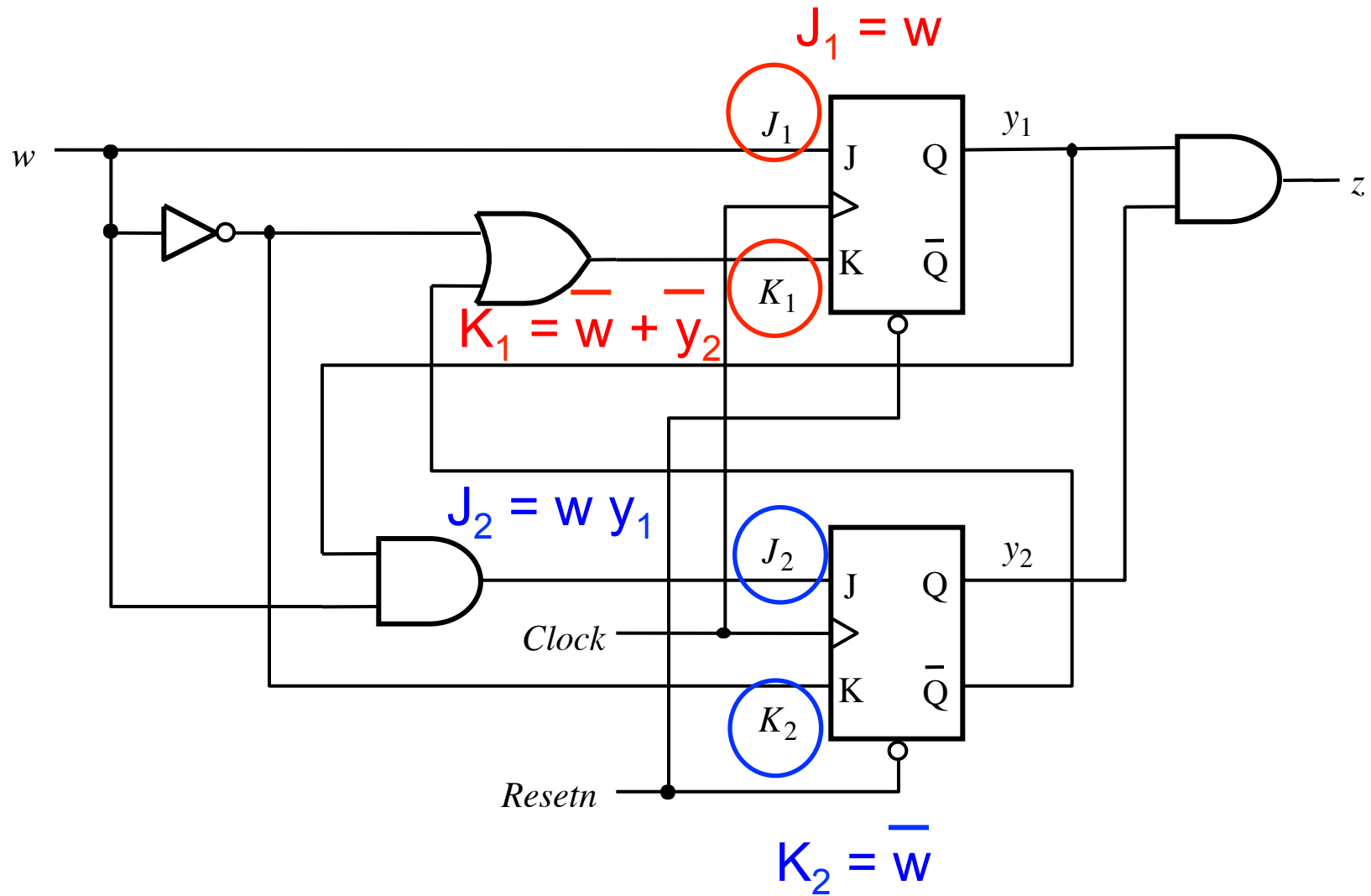





**This is what we have to work with now  
(we don't need the circuit anymore)**

$$J_1 = w$$

$$K_1 = \bar{w} + \bar{y}_2$$

$$J_2 = w y_1$$

$$K_2 = \bar{w}$$

$$z = y_1 y_2$$

# Let's derive the excitation table

$$J_1 = w$$

$$K_1 = \bar{w} + \bar{y}_2$$

$$J_2 = w y_1$$

$$K_2 = \bar{w}$$

$$z = y_1 y_2$$

Present state $y_2 y_1$	Flip-flop inputs				Output $z$
	$w = 0$		$w = 1$		
	$J_2 K_2$	$J_1 K_1$	$J_2 K_2$	$J_1 K_1$	
00					
01					
10					
11					

# Let's derive the excitation table

$$J_1 = w$$

$$K_1 = \bar{w} + \bar{y}_2$$

$$J_2 = w y_1$$

$$K_2 = \bar{w}$$

Present state $y_2y_1$	Flip-flop inputs				Output $z$
	$w = 0$		$w = 1$		
	$J_2K_2$	$J_1K_1$	$J_2K_2$	$J_1K_1$	
00					
01					
10					
11					

$$z = y_1y_2$$

# Let's derive the excitation table

$$J_1 = w$$

$$K_1 = \bar{w} + \bar{y}_2$$

$$J_2 = w y_1$$

$$K_2 = \bar{w}$$

Present state $y_2y_1$	Flip-flop inputs				Output $z$
	$w = 0$		$w = 1$		
	$J_2K_2$	$J_1K_1$	$J_2K_2$	$J_1K_1$	
00					0
01					0
10					0
11					1

$$z = y_1y_2$$



# Let's derive the excitation table

$$J_1 = w$$

$$K_1 = \bar{w} + \bar{y}_2$$

$$J_2 = w y_1$$

$$K_2 = \bar{w}$$

$$z = y_1 y_2$$

Present state $y_2 y_1$	Flip-flop inputs				Output $z$
	$w = 0$		$w = 1$		
	$J_2 K_2$	$J_1 K_1$	$J_2 K_2$	$J_1 K_1$	
00					0
01					0
10					0
11					1

# Let's derive the excitation table

$$J_1 = w$$

$$K_1 = \bar{w} + \bar{y}_2$$

$$J_2 = w y_1$$

$$K_2 = \bar{w}$$

$$z = y_1 y_2$$

Present state $y_2 y_1$	Flip-flop inputs				Output $z$
	$w = 0$		$w = 1$		
	$J_2 K_2$	$J_1 K_1$	$J_2 K_2$	$J_1 K_1$	
00		01		11	0
01		01		11	0
10		01		10	0
11		01		10	1

# Let's derive the excitation table

$$J_1 = w$$

$$K_1 = \bar{w} + \bar{y}_2$$

$$J_2 = w y_1$$

$$K_2 = \bar{w}$$

$$z = y_1 y_2$$

Present state $y_2 y_1$	Flip-flop inputs				Output $z$
	$w = 0$		$w = 1$		
	$J_2 K_2$	$J_1 K_1$	$J_2 K_2$	$J_1 K_1$	
00		01		11	0
01		01		11	0
10		01		10	0
11		01		10	1

# The excitation table

$$J_1 = w$$

$$K_1 = \bar{w} + \bar{y}_2$$

$$J_2 = w y_1$$

$$K_2 = \bar{w}$$

$$z = y_1 y_2$$

Present state $y_2 y_1$	Flip-flop inputs				Output $z$
	$w = 0$		$w = 1$		
	$J_2 K_2$	$J_1 K_1$	$J_2 K_2$	$J_1 K_1$	
00	01	01	00	11	0
01	01	01	10	11	0
10	01	01	00	10	0
11	01	01	10	10	1

# We don't need the logic expressions anymore

$$J_1 = w$$

$$K_1 = \bar{w} + \bar{y}_2$$

$$J_2 = w y_1$$

$$K_2 = \bar{w}$$

$$z = y_1 y_2$$

Present state $y_2 y_1$	Flip-flop inputs				Output $z$
	$w = 0$		$w = 1$		
	$J_2 K_2$	$J_1 K_1$	$J_2 K_2$	$J_1 K_1$	
00	01	01	00	11	0
01	01	01	10	11	0
10	01	01	00	10	0
11	01	01	10	10	1

# We don't need the logic expressions anymore

Present state $y_2y_1$	Flip-flop inputs				Output $z$
	$w = 0$		$w = 1$		
	$J_2K_2$	$J_1K_1$	$J_2K_2$	$J_1K_1$	
00	01	01	00	11	0
01	01	01	10	11	0
10	01	01	00	10	0
11	01	01	10	10	1

# Let's derive the state table

Present state	Next state		Output z
	w = 0	w = 1	

State table

Present state $y_2y_1$	Flip-flop inputs				Output z
	w = 0		w = 1		
	$J_2K_2$	$J_1K_1$	$J_2K_2$	$J_1K_1$	
00	01	01	00	11	0
01	01	01	10	11	0
10	01	01	00	10	0
11	01	01	10	10	1

Excitation table

# Let's derive the state table

Present state	Next state		Output z
	w = 0	w = 1	
A			
B			
C			
D			

Present state $y_2y_1$	Flip-flop inputs				Output z
	w = 0		w = 1		
	$J_2K_2$	$J_1K_1$	$J_2K_2$	$J_1K_1$	
00	01	01	00	11	0
01	01	01	10	11	0
10	01	01	00	10	0
11	01	01	10	10	1

State table

Excitation table

This step is easy  
(map 2-bit numbers to 4 letters)



# Let's derive the state table

Present state	Next state		Output z
	w = 0	w = 1	
A			0
B			0
C			0
D			1

Present state $y_2y_1$	Flip-flop inputs				Output z
	w = 0		w = 1		
	$J_2K_2$	$J_1K_1$	$J_2K_2$	$J_1K_1$	
00	01	01	00	11	0
01	01	01	10	11	0
10	01	01	00	10	0
11	01	01	10	10	1

State table

Excitation table

This step is easy too  
(the outputs are the same in both tables)

# Let's derive the state table

Present state	Next state		Output z
	w = 0	w = 1	
A	?		0
B			0
C			0
D			1


State table

Present state $y_2y_1$	Flip-flop inputs				Output z
	w = 0		w = 1		
	$J_2K_2$	$J_1K_1$	$J_2K_2$	$J_1K_1$	
00	01	01	00	11	0
01	01	01	10	11	0
10	01	01	00	10	0
11	01	01	10	10	1

Excitation table


How should we do this?

# JK Flip-Flop Refresher

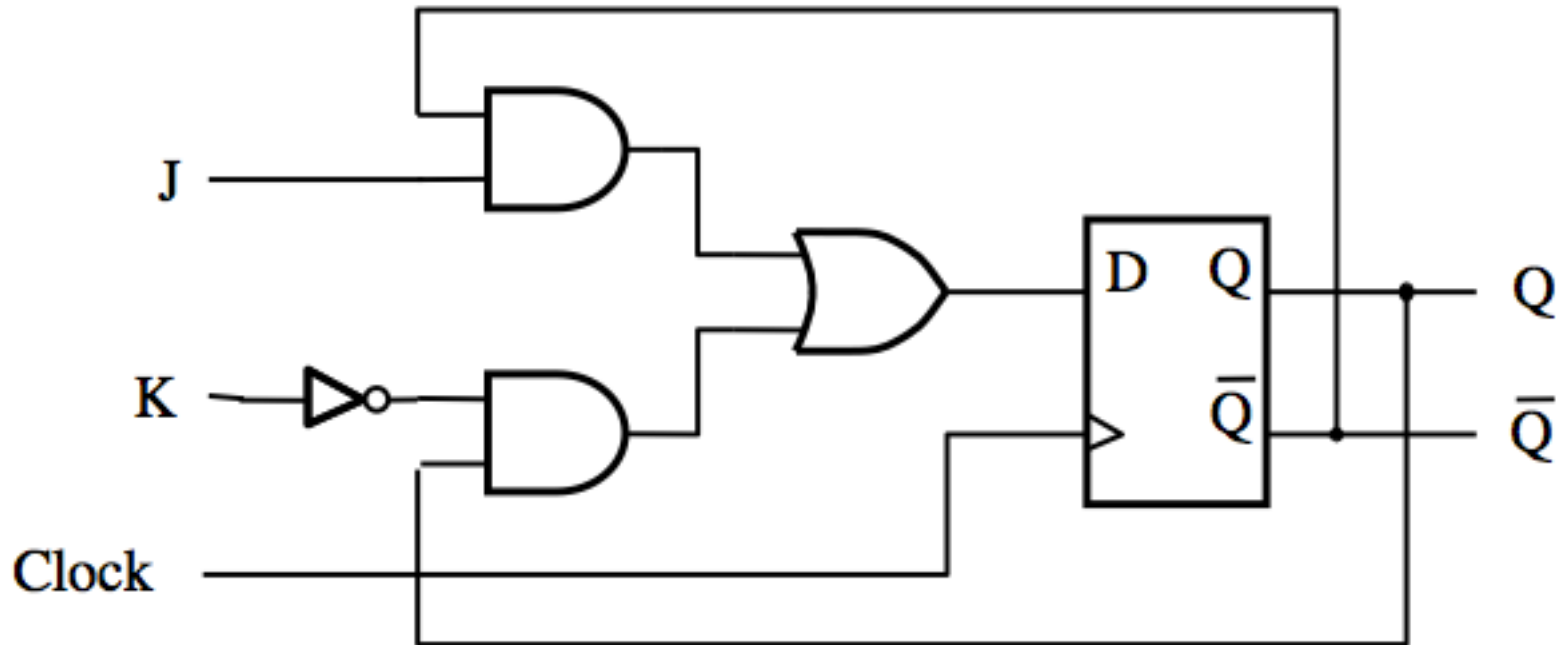

$$D = \overline{JQ} + \overline{KQ}$$


# JK Flip-Flop Refresher

 

(a) Circuit

J	K	$Q(t+1)$
0	0	$Q(t)$
0	1	0
1	0	1
1	1	$\bar{Q}(t)$

(b) Truth table

 

(c) Graphical symbol

# Let's derive the state table

Present state	Next state		Output z
	w = 0	w = 1	
A	?		0
B			0
C			0
D			1

State table

Present state $y_2y_1$	Flip-flop inputs				Output z
	w = 0		w = 1		
	$J_2K_2$	$J_1K_1$	$J_2K_2$	$J_1K_1$	
00	01	01	00	11	0
01	01	01	10	11	0
10	01	01	00	10	0
11	01	01	10	10	1

Excitation table

How should we do this?

# Let's derive the state table

Present state	Next state		Output z
	w = 0	w = 1	
A			0
B			0
C			0
D			1

Present state $y_2y_1$	Flip-flop inputs				Output z
	w = 0		w = 1		
	$J_2K_2$	$J_1K_1$	$J_2K_2$	$J_1K_1$	
00	01	01	00	11	0
01	01	01	10	11	0
10	01	01	00	10	0
11	01	01	10	10	1

J	K	Q(t+1)
0	0	Q(t)
0	1	0
1	0	1
1	1	$\bar{Q}(t)$

# Let's derive the state table

Present state	Next state		Output z
	w = 0	w = 1	
A			0
B			0
C			0
D			1

Present state $y_2y_1$	Flip-flop inputs				Output z
	w = 0		w = 1		
	$J_2K_2$	$J_1K_1$	$J_2K_2$	$J_1K_1$	
00	01	01	00	11	0
01	01	01	10	11	0
10	01	01	00	10	0
11	01	01	10	10	1

J	K	$Q(t+1)$	J	K	$Q(t+1)$
0	0	$Q(t)$	0	0	$Q(t)$
0	1	0	0	1	0
1	0	1	1	0	1
1	1	$\bar{Q}(t)$	1	1	$\bar{Q}(t)$

# Let's derive the state table

Present state	Next state		Output z
	w = 0	w = 1	
A	A		0
B			0
C			0
D			1

Present state $y_2y_1$	Flip-flop inputs				Output z
	w = 0		w = 1		
	$J_2K_2$	$J_1K_1$	$J_2K_2$	$J_1K_1$	
00	01	01	00	11	0
01	01	01	10	11	0
10	01	01	00	10	0
11	01	01	10	10	1

Note that A = 00

J	K	$Q(t+1)$	J	K	$Q(t+1)$
0	0	$Q(t)$	0	0	$Q(t)$
0	1	0	0	1	0
1	0	1	1	0	1
1	1	$\bar{Q}(t)$	1	1	$\bar{Q}(t)$



# Let's derive the state table

Present state	Next state		Output z
	w = 0	w = 1	
A	A	<span style="border: 1px solid red; padding: 2px;">?</span>	0
B			0
C			0
D			1

Present state $y_2y_1$	Flip-flop inputs				Output z
	w = 0		w = 1		
	$J_2K_2$	$J_1K_1$	$J_2K_2$	$J_1K_1$	
00	01	01	00	11	0
01	01	01	10	11	0
10	01	01	00	10	0
11	01	01	10	10	1

J	K	$Q(t+1)$
0	0	$Q(t)$
0	1	0
1	0	1
1	1	$\bar{Q}(t)$

J	K	$Q(t+1)$
0	0	$Q(t)$
0	1	0
1	0	1
1	1	$\bar{Q}(t)$

# Let's derive the state table

Present state	Next state		Output z
	w = 0	w = 1	
A	A		0
B			0
C			0
D			1

Present state $y_2y_1$	Flip-flop inputs				Output z
	w = 0		w = 1		
	$J_2K_2$	$J_1K_1$	$J_2K_2$	$J_1K_1$	
00	01	01	00	11	0
01	01	01	10	11	0
10	01	01	00	10	0
11	01	01	10	10	1

J	K	$Q(t+1)$	J	K	$Q(t+1)$
0	0	$Q(t)$	0	0	$Q(t)$
0	1	0	0	1	0
1	0	1	1	0	1
1	1	$\bar{Q}(t)$	1	1	$\bar{Q}(t)$

# Let's derive the state table

Present state	Next state		Output z
	w = 0	w = 1	
A	A		0
B			0
C			0
D			1

Present state $y_2y_1$	Flip-flop inputs				Output z
	w = 0		w = 1		
	$J_2K_2$	$J_1K_1$	$J_2K_2$	$J_1K_1$	
00	01	01	00	11	0
01	01	01	10	11	0
10	01	01	00	10	0
11	01	01	10	10	1


J	K	$Q(t+1)$	J	K	$Q(t+1)$
0	0	$Q(t)$	0	0	$Q(t)$
0	1	0	0	1	0
1	0	1	1	0	1
1	1	$\bar{Q}(t)$	1	1	$\bar{Q}(t)$

# Let's derive the state table

Present state	Next state		Output z
	w = 0	w = 1	
A	A		0
B			0
C			0
D			1

Present state $y_2y_1$	Flip-flop inputs				Output z
	w = 0		w = 1		
	$J_2K_2$	$J_1K_1$	$J_2K_2$	$J_1K_1$	
00	01	01	00	11	0
01	01	01	10	11	0
10	01	01	00	10	0
11	01	01	10	10	1

J	K	$Q(t+1)$	J	K	$Q(t+1)$
0	0	$Q(t)$	0	0	$Q(t)$
0	1	0	0	1	0
1	0	1	1	0	1
1	1	$\bar{Q}(t)$	1	1	$\bar{Q}(t)$

 

# Let's derive the state table

Present state	Next state		Output z
	w = 0	w = 1	
A	A		0
B	A		0
C	A		0
D	A		1

Present state $y_2y_1$	Flip-flop inputs				Output z
	w = 0		w = 1		
	$J_2K_2$	$J_1K_1$	$J_2K_2$	$J_1K_1$	
00	01	01	00	11	0
01	01	01	10	11	0
10	01	01	00	10	0
11	01	01	10	10	1

J	K	$Q(t+1)$	J	K	$Q(t+1)$
0	0	$Q(t)$	0	0	$Q(t)$
0	1	0	0	1	0
1	0	1	1	0	1
1	1	$\bar{Q}(t)$	1	1	$\bar{Q}(t)$

$\bar{1} = 0$

# Let's derive the state table

Present state	Next state		Output z
	w = 0	w = 1	
A	A		0
B		C	0
C			0
D			1

Present state $y_2y_1$	Flip-flop inputs				Output z
	w = 0		w = 1		
	$J_2K_2$	$J_1K_1$	$J_2K_2$	$J_1K_1$	
00	01	01	00	11	0
01	01	01	10	11	0
10	01	01	00	10	0
11	01	01	10	10	1

Note that C = 10

J	K	$Q(t+1)$	J	K	$Q(t+1)$
0	0	$Q(t)$	0	0	$Q(t)$
0	1	0	0	1	0
1	0	1	1	0	1
1	1	$\bar{Q}(t)$	1	1	$\bar{Q}(t)$ = 0

# The two tables for the initial circuit

Present state	Next state		Output z
	w = 0	w = 1	
A	A	B	0
B	A	C	0
C	A	D	0
D	A	D	1

State table


Present state $y_2y_1$	Flip-flop inputs				Output z
	w = 0		w = 1		
	$J_2K_2$	$J_1K_1$	$J_2K_2$	$J_1K_1$	
00	01	01	00	11	0
01	01	01	10	11	0
10	01	01	00	10	0
11	01	01	10	10	1

Excitation table

# The state diagram

Present state	Next state		Output z
	w = 0	w = 1	
A	A	B	0
B	A	C	0
C	A	D	0
D	A	D	1

State table

 

State diagram




# The state diagram

Thus, this FSM is identical to the one in the previous example, even though the circuit uses JK flip-flops.

Present state	Next state		Output z
	w = 0	w = 1	
A	A	B	0
B	A	C	0
C	A	D	0
D	A	D	1


State table

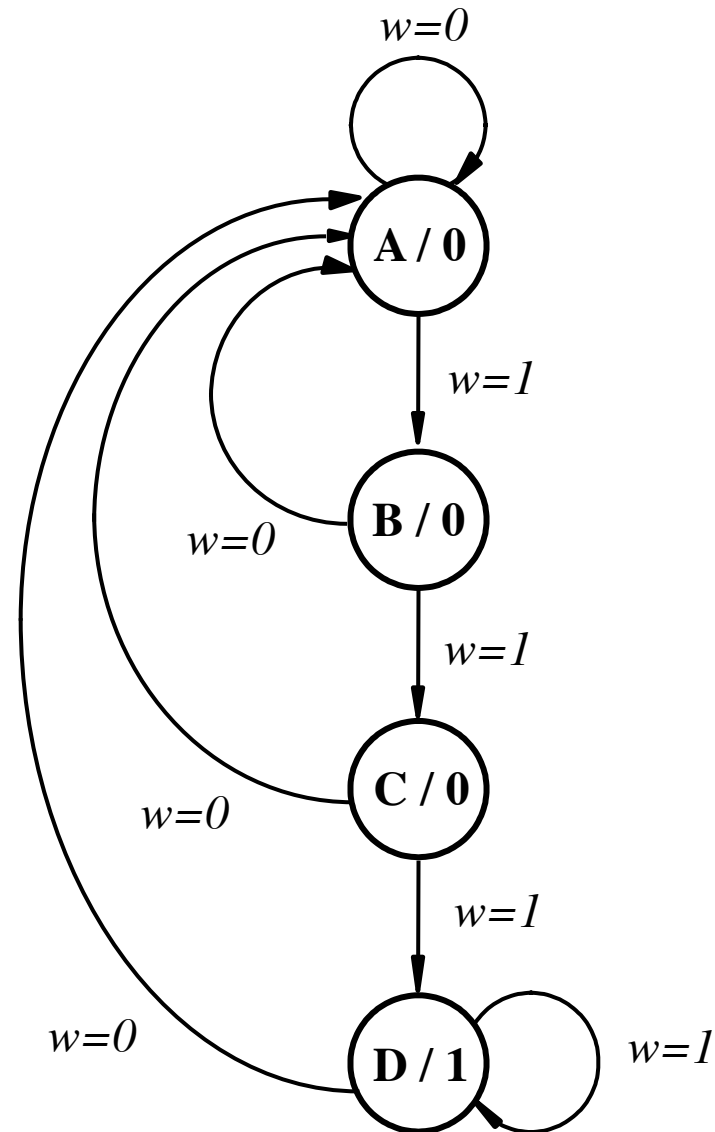

State diagram

# **Yet Another Example (with mixed flip-flops)**

# What does this circuit do?

 

[ Figure 6.79 from the textbook ]


# Approach

- **Find the flip-flops**
- **Outputs of the flip-flops = present state variables**
- **Inputs of the flip-flops determine the next state variables**
- **Determine the logical expressions for the outputs**
- **Given this info it is easy to do the state-assigned table**
- **Next do the state table**
- **Finally, draw the state diagram.**





# What are the logic expressions?

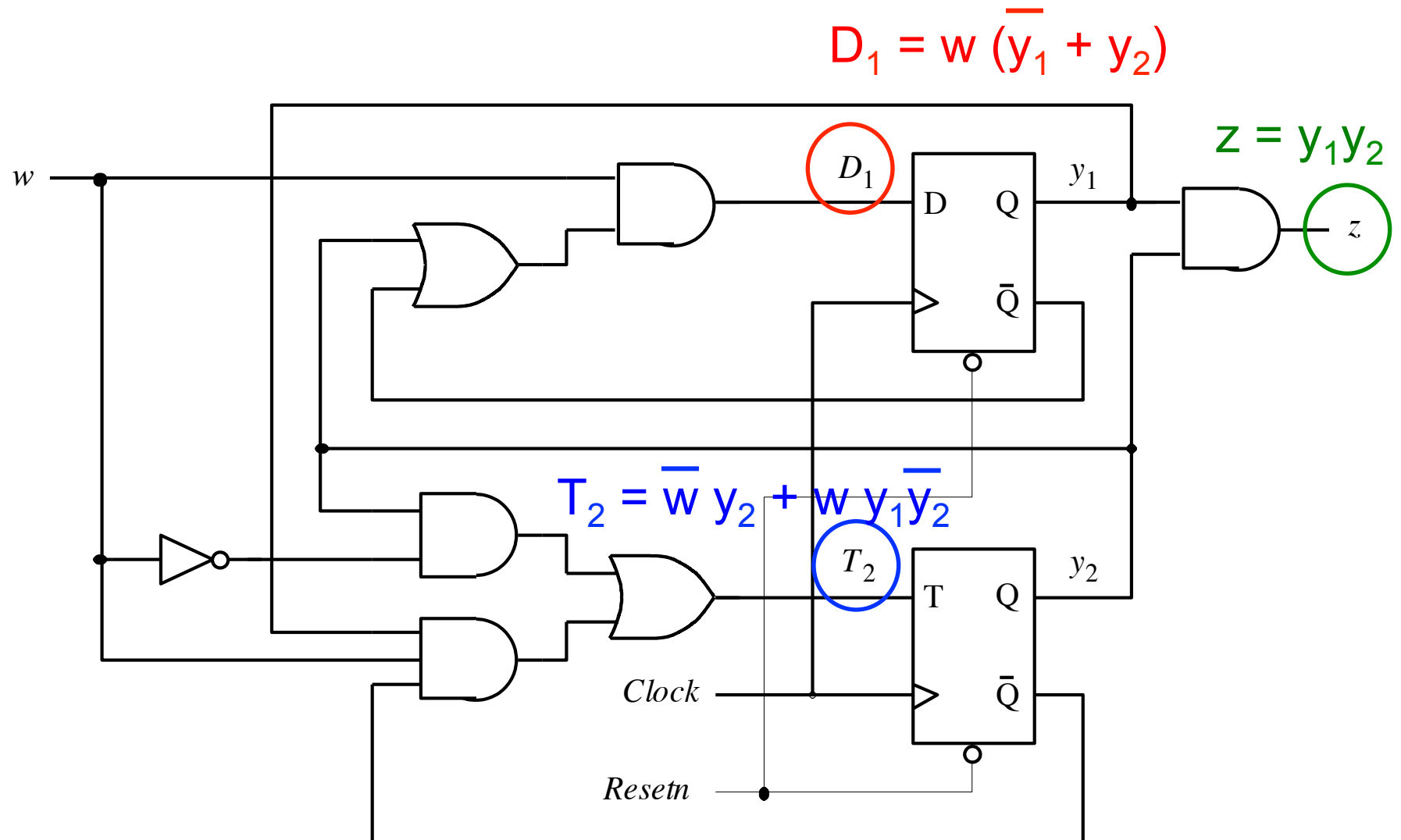

# The Excitation Table

$$D_1 = w (\bar{y}_1 + y_2)$$

$$T_2 = \bar{w} y_2 + w y_1 \bar{y}_2$$

$$z = y_1 y_2$$

Present state $y_2 y_1$	Flip-flop inputs		Output $z$
	$w = 0$	$w = 1$	
	$T_2 D_1$	$T_2 D_1$	
00	00	01	0
01	00	10	0
10	10	01	0
11	10	01	1

Excitation table



# Let's derive the state table

Present state	Next state		Output z
	w = 0	w = 1	

Present state $y_2y_1$	Flip-flop inputs		Output z
	w = 0	w = 1	
	$T_2D_1$	$T_2D_1$	
00	00	01	0
01	00	10	0
10	10	01	0
11	10	01	1

# Let's derive the state table

Present state	Next state		Output z
	w = 0	w = 1	
A			
B			
C			
D			

Present state $y_2y_1$	Flip-flop inputs		Output z
	w = 0	w = 1	
	$T_2D_1$	$T_2D_1$	
00	00	01	0
01	00	10	0
10	10	01	0
11	10	01	1

This step is easy  
(map 2-bit numbers to 4 letters)

# Let's derive the state table

Present state	Next state		Output z
	w = 0	w = 1	
A			0
B			0
C			0
D			1

Present state $y_2y_1$	Flip-flop inputs		Output z
	w = 0	w = 1	
	$T_2D_1$	$T_2D_1$	
00	00	01	0
01	00	10	0
10	10	01	0
11	10	01	1

This step is easy too  
(the outputs are the same in both tables)

# Let's derive the state table

Present state	Next state		Output z
	w = 0	w = 1	
A	?		0
B			0
C			0
D			1

Present state $y_2y_1$	Flip-flop inputs		Output z
	w = 0	w = 1	
	$T_2D_1$	$T_2D_1$	
00	00	01	0
01	00	10	0
10	10	01	0
11	10	01	1

What should we do here?

# Let's derive the state table

Present state	Next state		Output z
	w = 0	w = 1	
A	?		0
B			0
C			0
D			1

Present state $y_2y_1$	Flip-flop inputs		Output z
	w = 0	w = 1	
	$T_2D_1$	$T_2D_1$	
00	00	01	0
01	00	10	0
10	10	01	0
11	10	01	1

What should we do here?

T	$Q(t+1)$	D	$Q(t+1)$
0	$Q(t)$	0	0
1	$\overline{Q(t)}$	1	1

# Let's derive the state table

Present state	Next state		Output z
	w = 0	w = 1	
A			0
B			0
C			0
D			1

Present state $y_2y_1$	Flip-flop inputs		Output z
	w = 0	w = 1	
	$T_2D_1$	$T_2D_1$	
00	00	01	0
01	00	10	0
10	10	01	0
11	10	01	1

T	$Q(t+1)$	D	$Q(t+1)$
0	$Q(t)$	0	0
1	$\overline{Q(t)}$	1	1

# Let's derive the state table

Present state	Next state		Output z
	w = 0	w = 1	
A			0
B			0
C			0
D			1

Present state $y_2y_1$	Flip-flop inputs		Output z
	w = 0	w = 1	
	$T_2D_1$	$T_2D_1$	
00	00	01	0
01	00	10	0
10	10	01	0
11	10	01	1

T	$Q(t+1)$	D	$Q(t+1)$
0	$Q(t)$	0	0
1	$\overline{Q(t)}$	1	1

# Let's derive the state table

Present state	Next state		Output z
	w = 0	w = 1	
A			0
B			0
C			0
D			1

Present state $y_2y_1$	Flip-flop inputs		Output z
	w = 0	w = 1	
	$T_2D_1$	$T_2D_1$	
00	00	01	0
01	00	10	0
10	10	01	0
11	10	01	1

T	$Q(t+1)$	D	$Q(t+1)$
0	$Q(t)$	0	0
1	$\overline{Q(t)}$	1	1



# Let's derive the state table

Present state	Next state		Output z
	w = 0	w = 1	
A			0
B			0
C			0
D			1

Present state $y_2y_1$	Flip-flop inputs		Output z
	w = 0	w = 1	
	$T_2D_1$	$T_2D_1$	
00	00	01	0
01	00	10	0
10	10	01	0
11	10	01	1

T	$Q(t+1)$	D	$Q(t+1)$
0	0	0	0
1	$\overline{Q(t)}$	1	1

# Let's derive the state table

Present state	Next state		Output z
	w = 0	w = 1	
A			0
B			0
C			0
D			1

Present state $y_2y_1$	Flip-flop inputs		Output z
	w = 0	w = 1	
	$T_2D_1$	$T_2D_1$	
00	00	01	0
01	00	10	0
10	10	01	0
11	10	01	1

T	$Q(t+1)$	D	$Q(t+1)$
0	0	0	0
1	$\overline{Q(t)}$	1	1

# Let's derive the state table

Present state	Next state		Output z
	w = 0	w = 1	
A			0
B			0
C			0
D			1

Present state $y_2y_1$	Flip-flop inputs		Output z
	w = 0	w = 1	
	$T_2D_1$	$T_2D_1$	
00	00	01	0
01	00	10	0
10	10	01	0
11	10	01	1

T	$Q(t+1)$	D	$Q(t+1)$
0	0	0	0
1	$\overline{Q(t)}$	1	1

# Let's derive the state table

Present state	Next state		Output z
	w = 0	w = 1	
A	A		0
B			0
C			0
D			1

Present state $y_2y_1$	Flip-flop inputs		Output z
	w = 0	w = 1	
	$T_2D_1$	$T_2D_1$	
00	00	01	0
01	00	10	0
10	10	01	0
11	10	01	1

Note that A = 00

T	$Q(t+1)$	D	$Q(t+1)$
0	0	0	0
1	$\overline{Q(t)}$	1	1

# Let's derive the state table

Present state	Next state		Output z
	w = 0	w = 1	
A	A		0
B	A		0
C	?		0
D	A		1

Present state $y_2y_1$	Flip-flop inputs		Output z
	w = 0	w = 1	
	$T_2D_1$	$T_2D_1$	
00	00	01	0
01	00	10	0
10	10	01	0
11	10	01	1

What should we do here?

T	$Q(t+1)$	D	$Q(t+1)$
0	$Q(t)$	0	0
1	$\overline{Q(t)}$	1	1

# Let's derive the state table

Present state	Next state		Output z
	w = 0	w = 1	
A	A		0
B	A		0
C	A		0
D	A		1

Present state $y_2y_1$	Flip-flop inputs		Output z
	w = 0	w = 1	
	$T_2D_1$	$T_2D_1$	
00	00	01	0
01	00	10	0
10	10	01	0
11	10	01	1

T	$Q(t+1)$	D	$Q(t+1)$
0	$Q(t)$	0	0
1	$\overline{Q(t)}$	1	1

# Let's derive the state table

Present state	Next state		Output z
	w = 0	w = 1	
A	A		0
B	A		0
C	A		0
D	A		1

Present state $y_2y_1$	Flip-flop inputs		Output z
	w = 0	w = 1	
	$T_2D_1$	$T_2D_1$	
00	00	01	0
01	00	10	0
10	10	01	0
11	10	01	1

T	$Q(t+1)$	D	$Q(t+1)$
0	$Q(t)$	0	0
1	$\overline{Q(t)}$	1	1

# Let's derive the state table

Present state	Next state		Output z
	w = 0	w = 1	
A	A		0
B			0
C			0
D			1

Present state $y_2y_1$	Flip-flop inputs		Output z
	w = 0	w = 1	
	$T_2D_1$	$T_2D_1$	
00	00	01	0
01	00	10	0
10	10	01	0
11	10	01	1

T	$Q(t+1)$	D	$Q(t+1)$
0	$Q(t)$	0	0
1	$\overline{Q(t)}$	1	1



# Let's derive the state table

Present state	Next state		Output z
	w = 0	w = 1	
A	A		0
B	A		0
C	A		0
D	A		1

Present state $y_2y_1$	Flip-flop inputs		Output z
	w = 0	w = 1	
	$T_2D_1$	$T_2D_1$	
00	00	01	0
01	00	10	0
10	10	01	0
11	10	01	1

T	$Q(t+1)$	D	$Q(t+1)$
0	1	0	0
1	$\overline{Q(t)}$	1	1

# Let's derive the state table

Present state	Next state		Output z
	w = 0	w = 1	
A	A		0
B	A		0
C	A		0
D	A		1

Present state $y_2y_1$	Flip-flop inputs		Output z
	w = 0	w = 1	
	$T_2D_1$	$T_2D_1$	
00	00	01	0
01	00	10	0
10	10	01	0
11	10	01	1

T	$Q(t+1)$	D	$Q(t+1)$
0	1	0	0
1	$\overline{Q(t)}$	1	1

# Let's derive the state table

Present state	Next state		Output z
	w = 0	w = 1	
A	A		0
B	A		0
C	A		0
D	A		1

Present state $y_2y_1$	Flip-flop inputs		Output z
	w = 0	w = 1	
	$T_2D_1$	$T_2D_1$	
00	00	01	0
01	00	10	0
10	10	01	0
11	10	01	1

T	$Q(t+1)$	D	$Q(t+1)$
0	1	0	0
1	$\overline{Q}(t)$	1	1

# Let's derive the state table

Present state	Next state		Output z
	w = 0	w = 1	
A	A		0
B			0
C		D	0
D			1

Present state $y_2y_1$	Flip-flop inputs		Output z
	w = 0	w = 1	
	$T_2D_1$	$T_2D_1$	
00	00	01	0
01	00	10	0
10	10	01	0
11	10	01	1

Note that D = 11

T	$Q(t+1)$	D	$Q(t+1)$
0	1	0	0
1	$\bar{Q}(t)$	1	1

# Let's derive the state table

Present state	Next state		Output z
	w = 0	w = 1	
A	A	B	0
B	A	C	0
C	A	D	0
D	A	D	1

Present state $y_2y_1$	Flip-flop inputs		Output z
	w = 0	w = 1	
	$T_2D_1$	$T_2D_1$	
00	00	01	0
01	00	10	0
10	10	01	0
11	10	01	1

T	$Q(t+1)$		D	$Q(t+1)$
0	$Q(t)$		0	0
1	$\overline{Q(t)}$		1	1

# The two tables for the initial circuit

Present state	Next state		Output z
	w = 0	w = 1	
A	A	B	0
B	A	C	0
C	A	D	0
D	A	D	1

State table

Present state $y_2y_1$	Flip-flop inputs		Output z
	w = 0	w = 1	
	$T_2D_1$	$T_2D_1$	
00	00	01	0
01	00	10	0
10	10	01	0
11	10	01	1

Excitation table


[ Figure 6.75b from the textbook ]

[ Figure 6.80 from the textbook ]

# The state diagram

Present state	Next state		Output z
	w = 0	w = 1	
A	A	B	0
B	A	C	0
C	A	D	0
D	A	D	1

State table

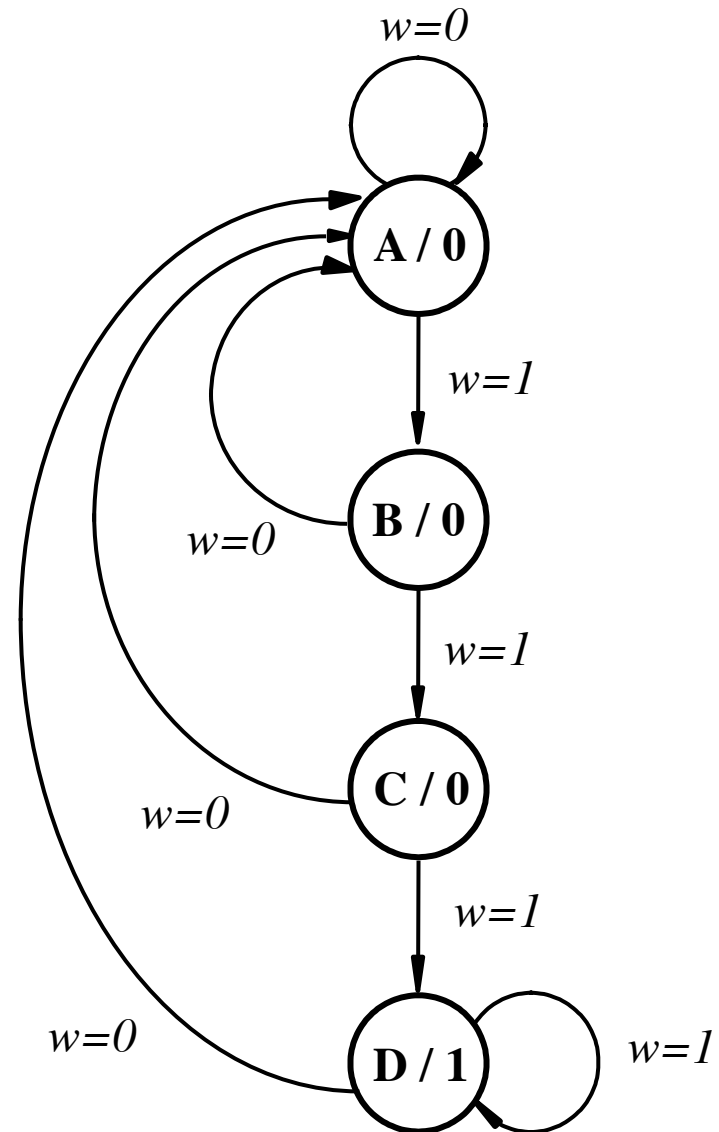


State diagram

# The state diagram

Thus, this FSM is identical to the ones in the previous examples, even though the circuit uses JK flip-flops.

Present state	Next state		Output z
	w = 0	w = 1	
A	A	B	0
B	A	C	0
C	A	D	0
D	A	D	1

State table

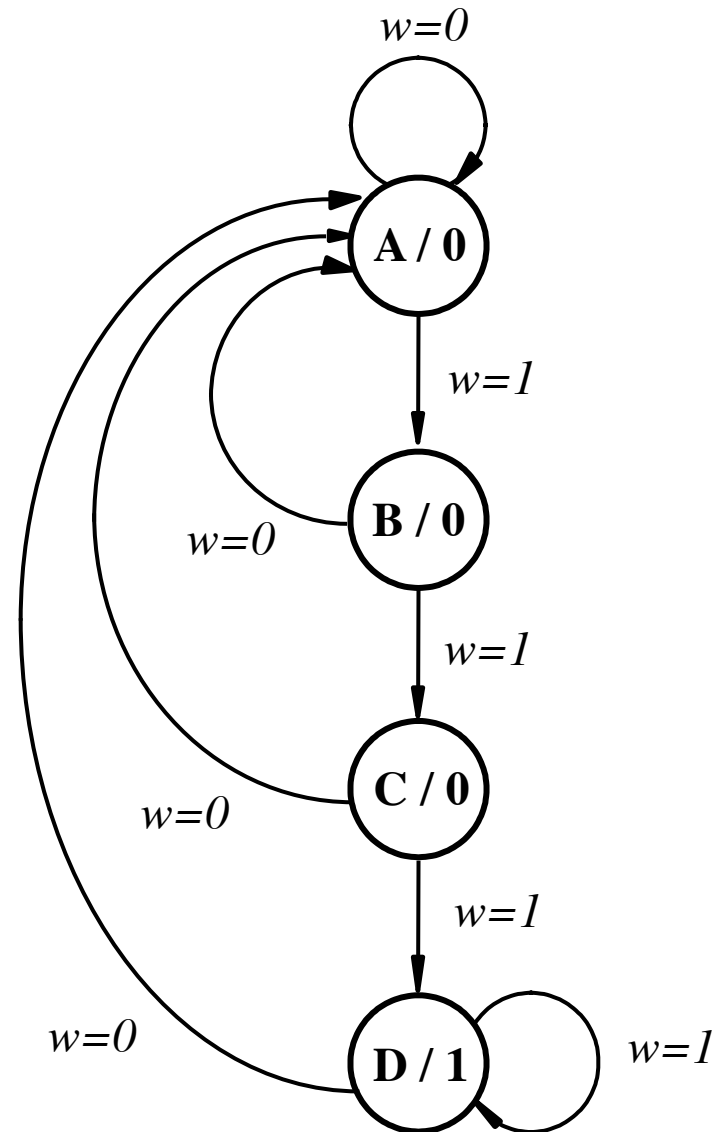

State diagram






# State Minimization

# State Table for This Example

Present state	Next state		Output $z$
	$w = 0$	$w = 1$	
A	B	C	1
B	D	F	1
C	F	E	0
D	B	G	1
E	F	C	0
F	E	D	0
G	F	G	0


# State Diagram (just the states)

Present state	Next state		Output $z$
	$w = 0$	$w = 1$	
A	B	C	1
B	D	F	1
C	F	E	0
D	B	G	1
E	F	C	0
F	E	D	0
G	F	G	0

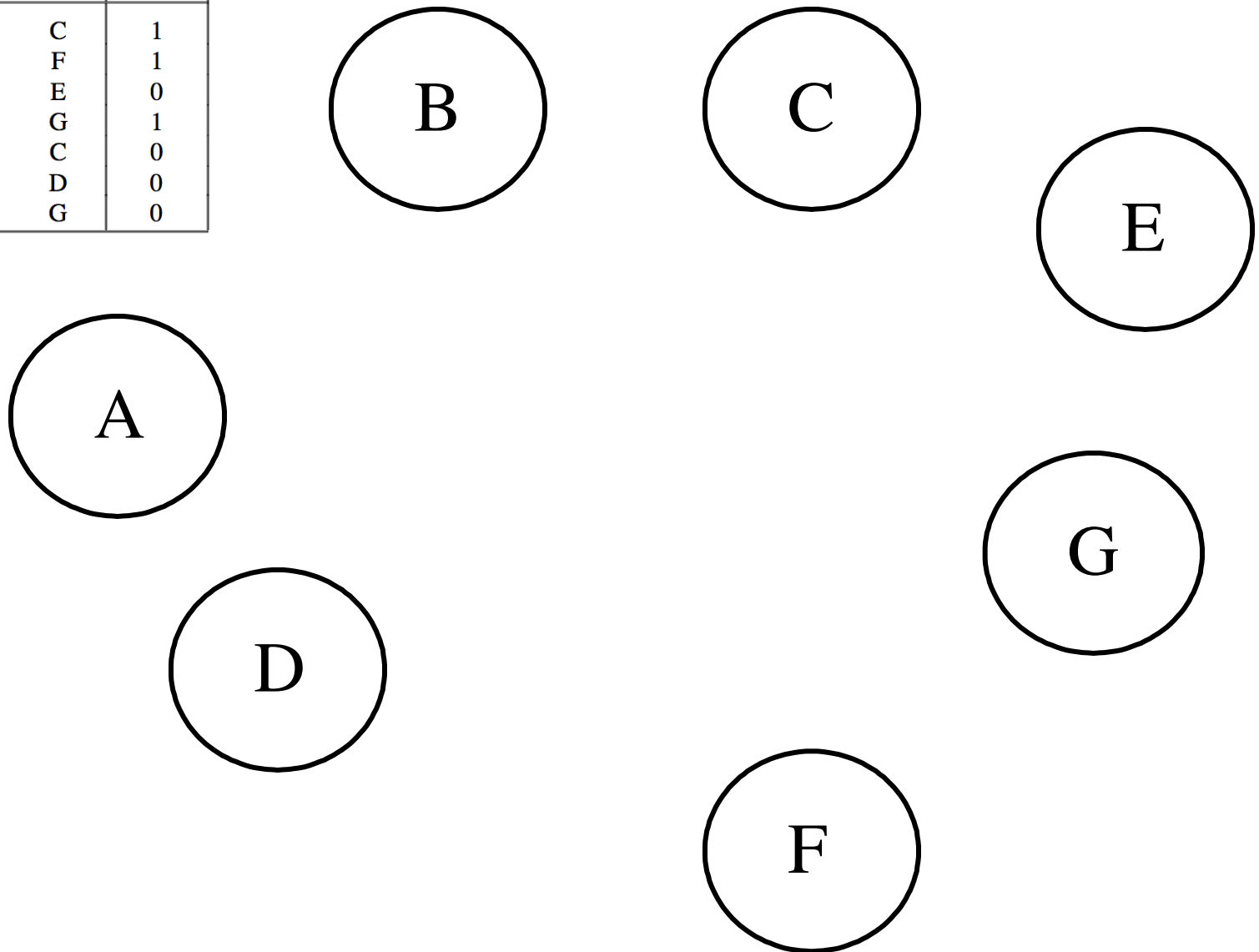


# State Diagram (transitions when $w=0$ )

Present state	Next state		Output $z$
	$w = 0$	$w = 1$	
A	B	C	1
B	D	F	1
C	F	E	0
D	B	G	1
E	F	C	0
F	E	D	0
G	F	G	0

 


# State Diagram (transitions when $w=1$ )

Present state	Next state		Output $z$
	$w = 0$	$w = 1$	
A	B	C	1
B	D	F	1
C	F	E	0
D	B	G	1
E	F	C	0
F	E	D	0
G	F	G	0

 


# Outputs

Present state	Next state		Output
	$w = 0$	$w = 1$	$z$
A	B	C	1
B	D	F	1
C	F	E	0
D	B	G	1
E	F	C	0
F	E	D	0
G	F	G	0

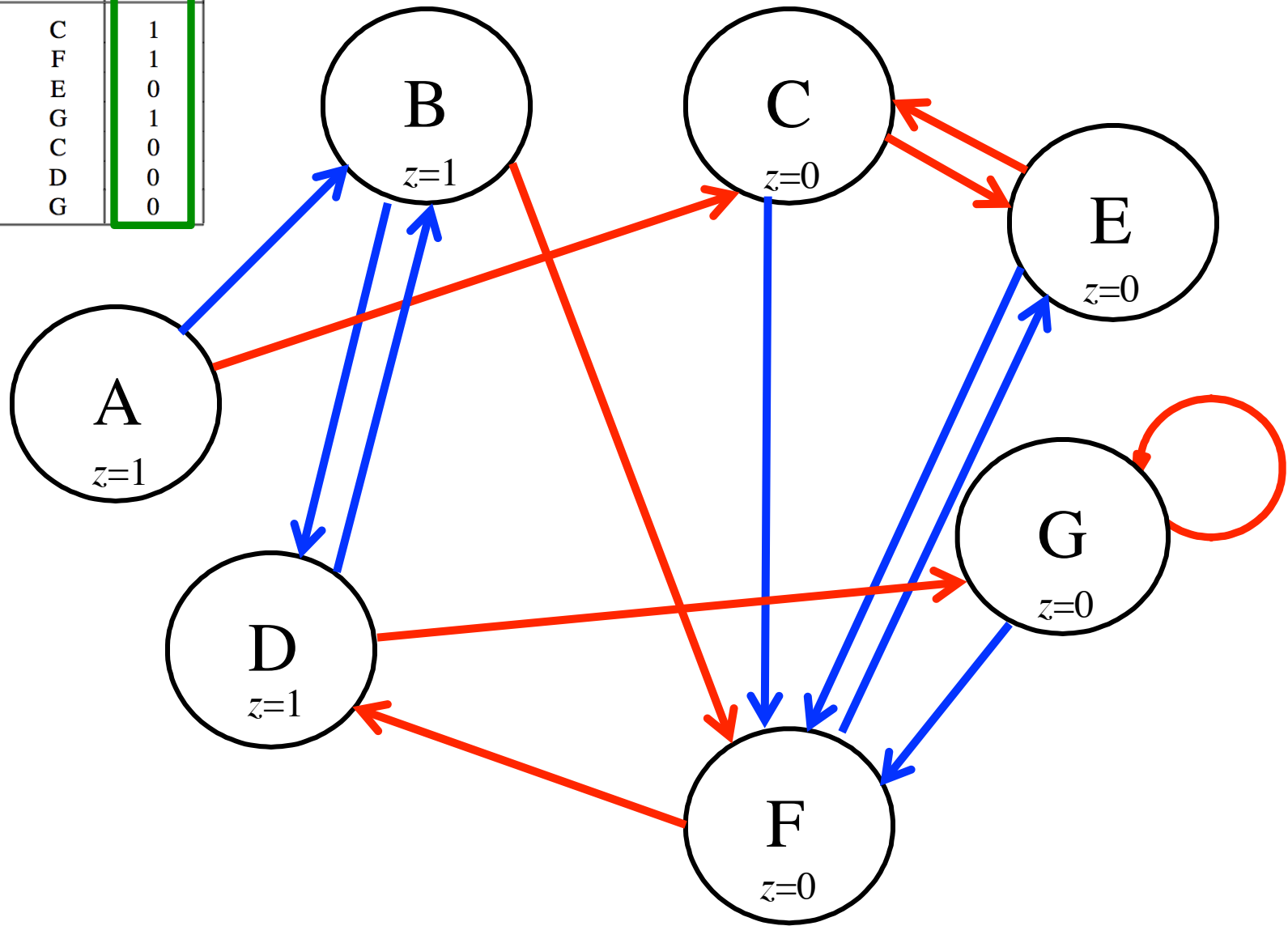

# Partition #1


(All states in the same partition)

 




# Partition #1

(ABCDEFGG)

 


# Partition #2

(based on outputs)

 


# Partition #2

(ABD)(CEFG)

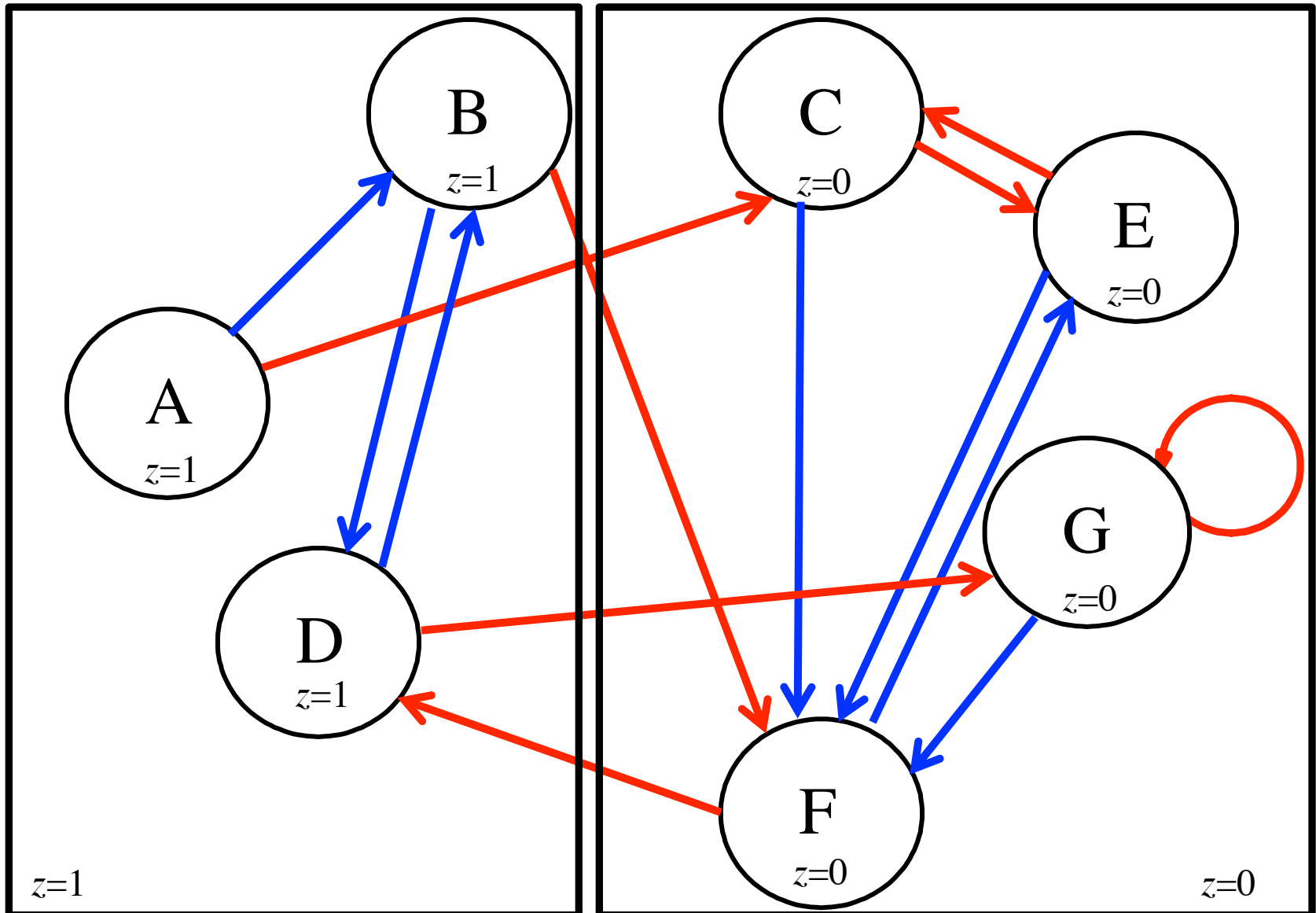


# Partition #3.1

(Examine the 0-successors of ABD)

 


# Partition #3.1

(Examine the 1-successors of ABD)

 


# Partition #3.2

(Examine the 0-successors of CCFG)

 


# Partition #3.2

(Examine the 1-successors of CEFG)

 

# Partition #3.2


(Examine the 1-successors of CCFG)

 




# Partition #3

(ABD)(CEG)(F)

 


# Partition #3

(ABD)(CEG)(F)

 


# Partition #4.1

(Examine the 0-successors of ABD)

 

# Partition #4.1


(Examine the 1-successors of ABD)

 

# Partition #4.1


(Examine the 1-successors of ABD)

This needs to be  
in a new block

 


# Partition #4

(AD)(B)(CEG)(F)

 


# Partition #4

(AD)(B)(CEG)(F)

 

# Partition #5.1


(Examine the 0-successors of AD)

 




# Partition #5.1

(Examine the 1-successors of AD)

 


# Partition #5.2

(Examine the 0-successors of B)

 


# Partition #5.2

(Examine the 1-successors of B)

 


# Partition #5.3

(Examine the 0-successors of CEG)

 


# Partition #5.3

(Examine the 1-successors of CEG)

 


# Partition #5.4

(Examine the 0-successors of F)

 


# Partition #5.4

(Examine the 1-successors of F)

 

# Partition #5


(AD)(B)(CEG)(F)

 




# Partition #4

(AD)(B)(CEG)(F)

 
 
# Partition #5

(This is the same as #4 so we can stop here)



# Minimized state table


Present state	Nextstate		Output z
	w = 0	w = 1	
A	B	C	1
B	A	F	1
C	F	C	0
F	C	A	0

# **Multiplexers**

# 4-1 Multiplexer (Definition)

- Has four inputs:  $w_0$ ,  $w_1$ ,  $w_2$ ,  $w_3$
- Also has two select lines:  $s_1$  and  $s_0$
- If  $s_1=0$  and  $s_0=0$ , then the output  $f$  is equal to  $w_0$
- If  $s_1=0$  and  $s_0=1$ , then the output  $f$  is equal to  $w_1$
- If  $s_1=1$  and  $s_0=0$ , then the output  $f$  is equal to  $w_2$
- If  $s_1=1$  and  $s_0=1$ , then the output  $f$  is equal to  $w_3$

# Graphical Symbol and Truth Table

 


(a) Graphic symbol

$s_1$	$s_0$	$f$
0	0	$w_0$
0	1	$w_1$
1	0	$w_2$
1	1	$w_3$


(b) Truth table

# Using three 2-to-1 multiplexers to build one 4-to-1 multiplexer

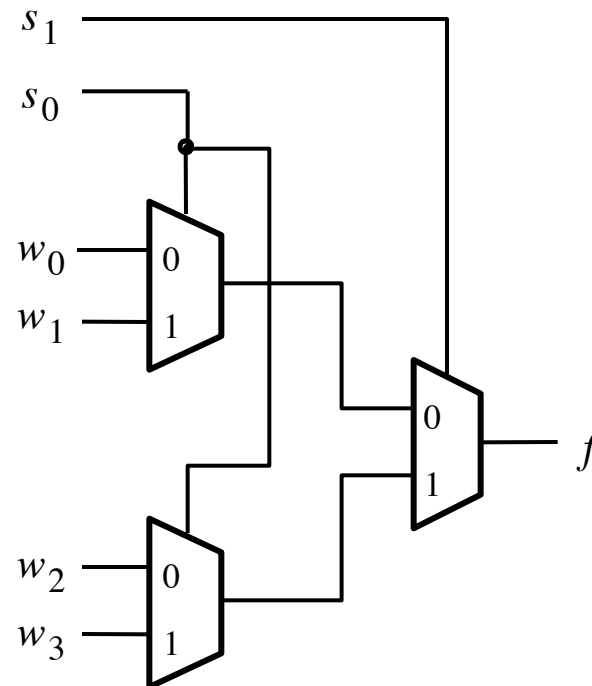


[ Figure 4.3 from the textbook ]

# Implementation of a logic function

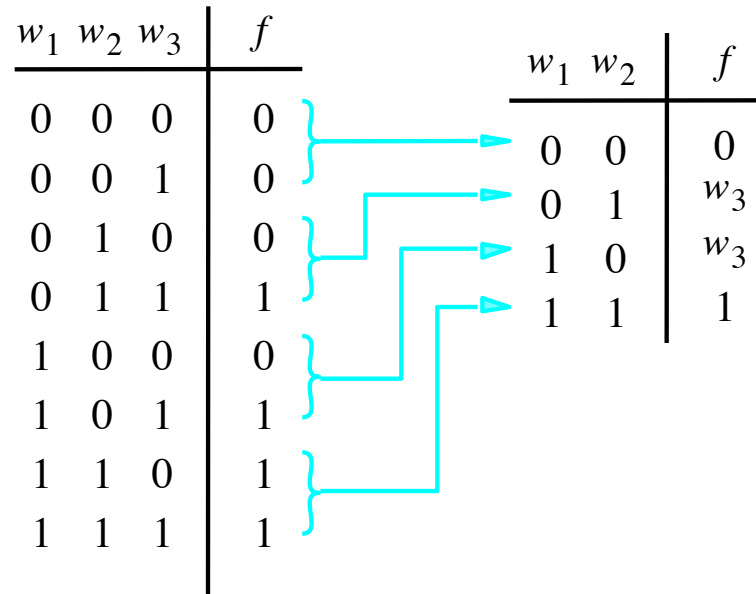

(a) Modified truth table

 

(b) Circuit

[ Figure 4.7 from the textbook ]




# Implementation of 3-input XOR with a 4-to-1 Multiplexer

$w_1$	$w_2$	$w_3$	$f$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

# Implementation of 3-input XOR with a 4-to-1 Multiplexer

$w_1$	$w_2$	$w_3$	$f$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1


(a) Truth table

 

(b) Circuit

# **Gated D Latch**


# Circuit Diagram for the Gated D Latch

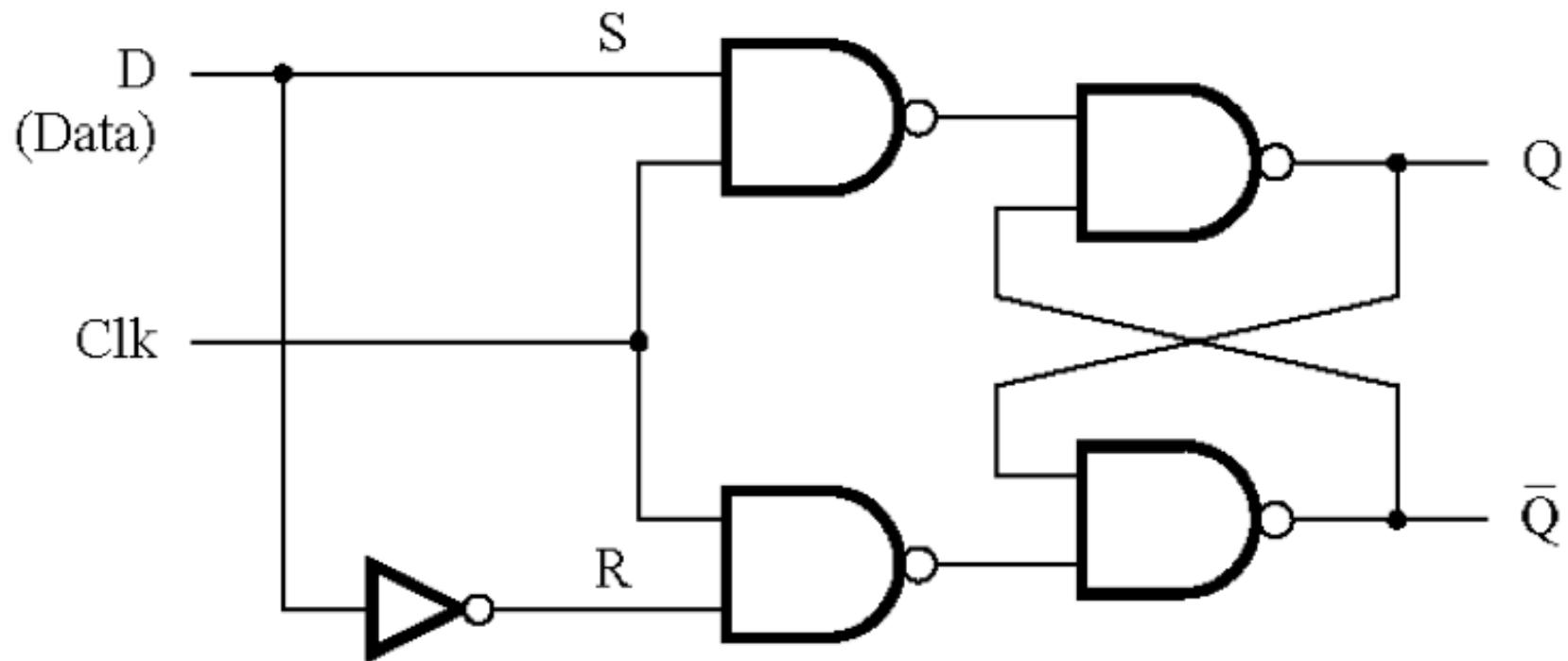

[ Figure 5.7a from the textbook ]


# **Edge-Triggered D Flip-Flops**

# Master-Slave D Flip-Flop

 


(a) Circuit

 
# Negative-Edge-Triggered Master-Slave D Flip-Flop


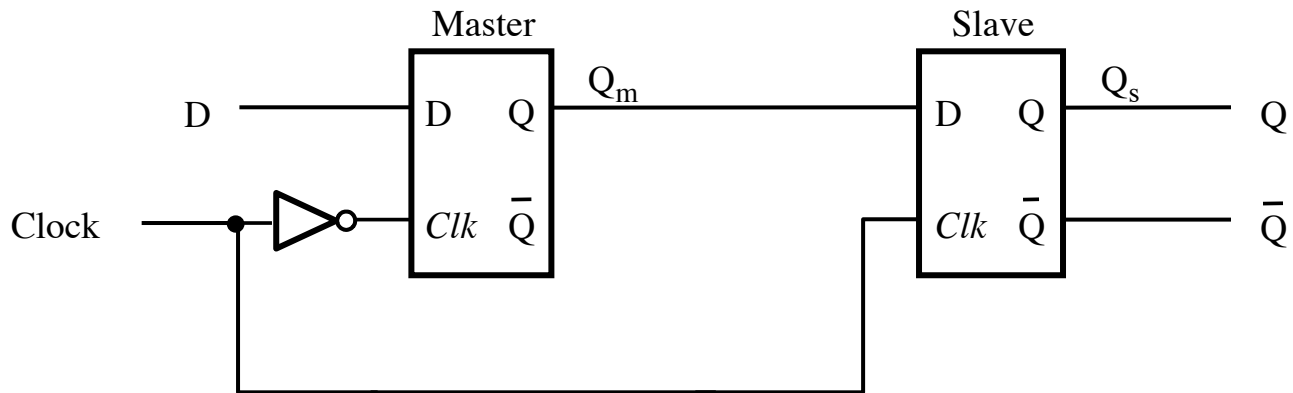
# Positive-Edge-Triggered Master-Slave D Flip-Flop





# Circuit Diagram for the Gated D Latch

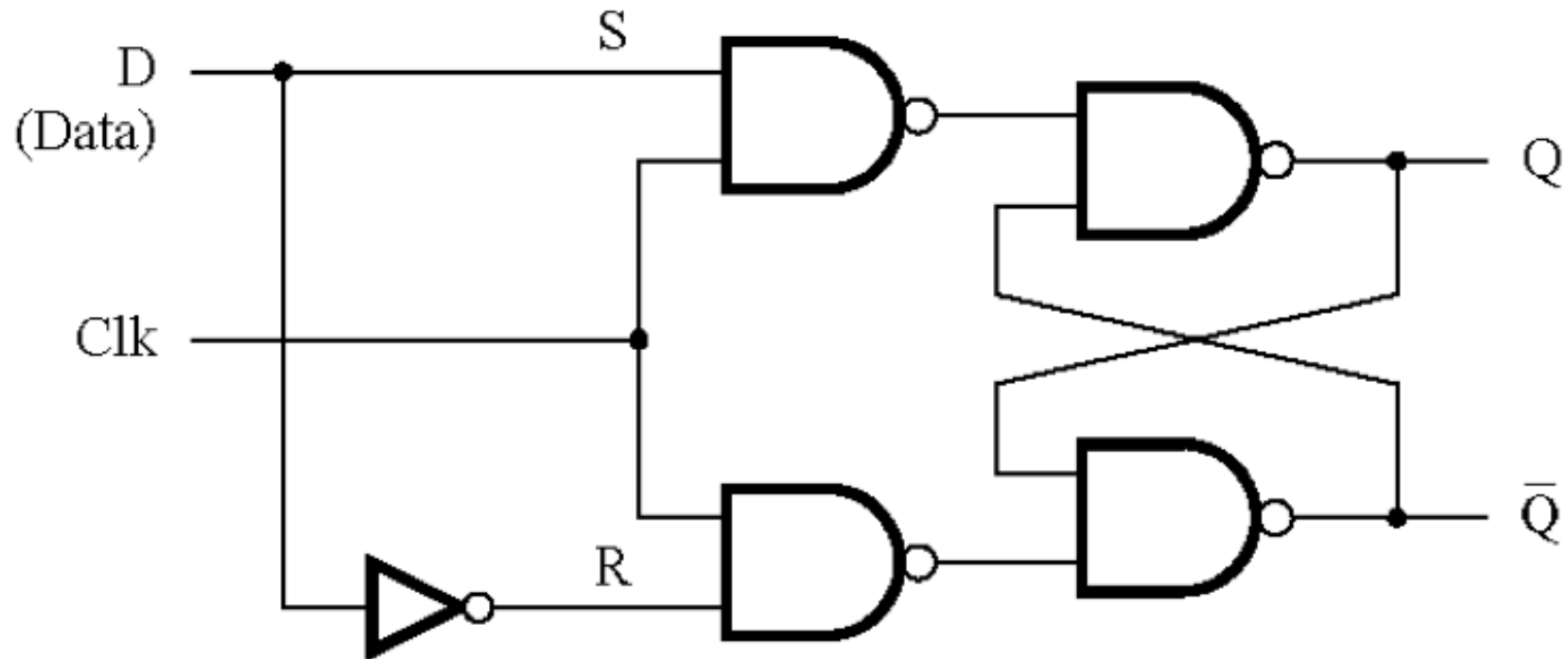


[ Figure 5.7a from the textbook ]





# Constructing a D Flip-Flop

  


# Constructing a D Flip-Flop

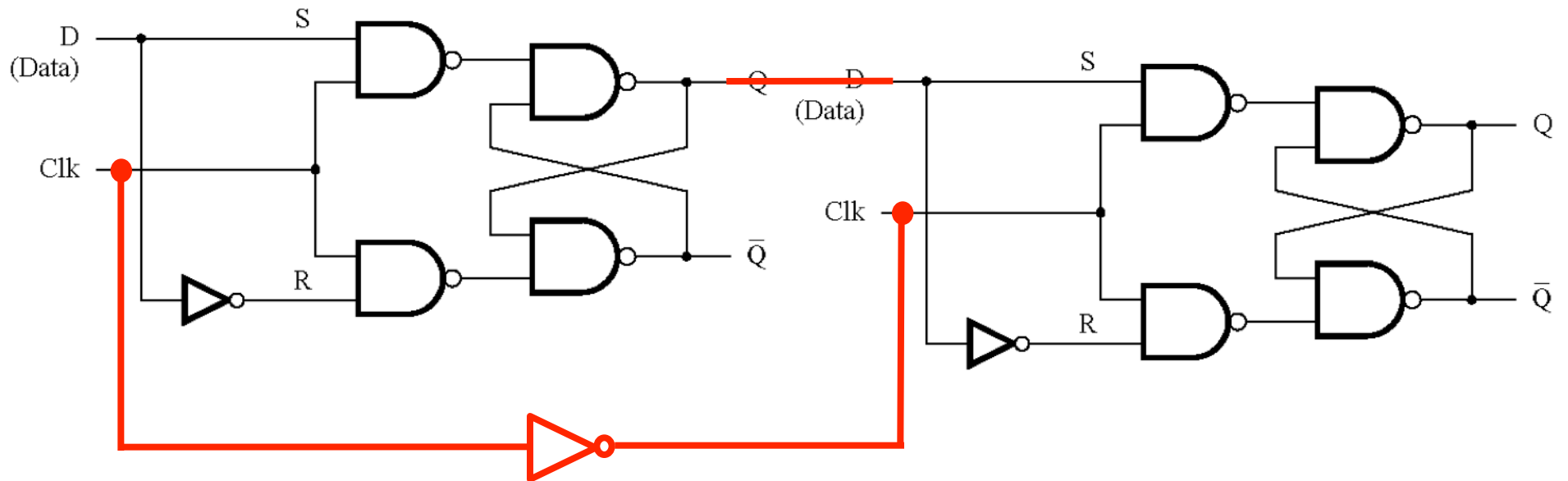
  
# Constructing a D Flip-Flop (with one less NOT gate)



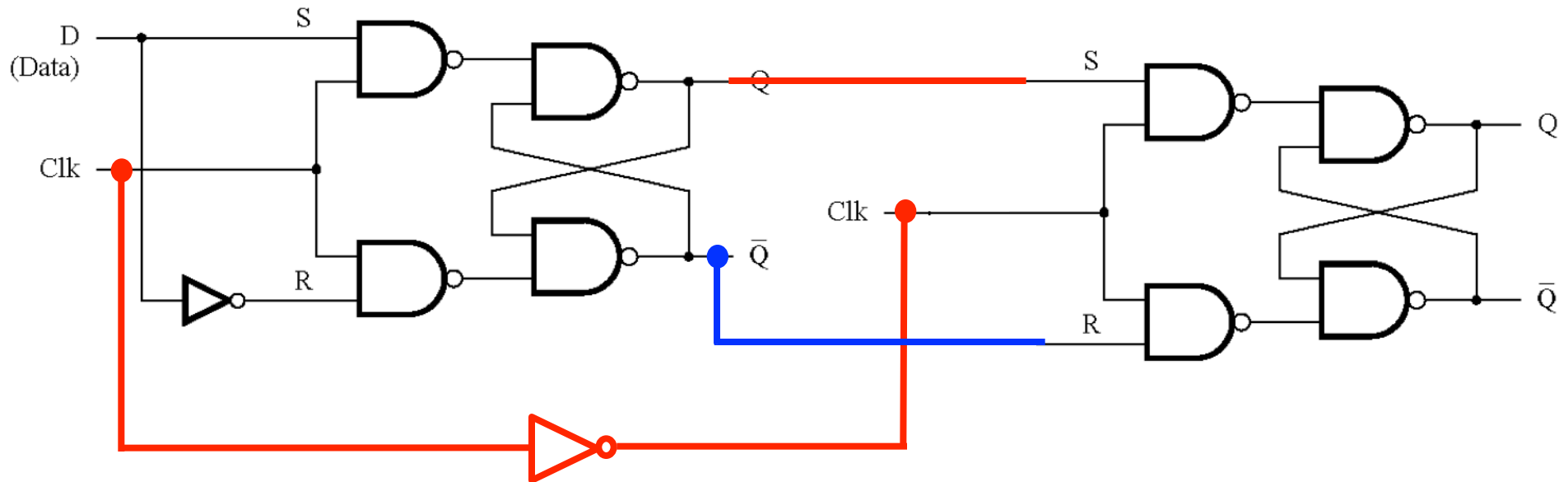
# Constructing a D Flip-Flop (with one less NOT gate)




# T Flip-Flop

# T Flip-Flop

 

[ Figure 5.15a from the textbook ]


# T Flip-Flop

 

Positive-edge-triggered  
D Flip-Flop

[ Figure 5.15a from the textbook ]

# T Flip-Flop

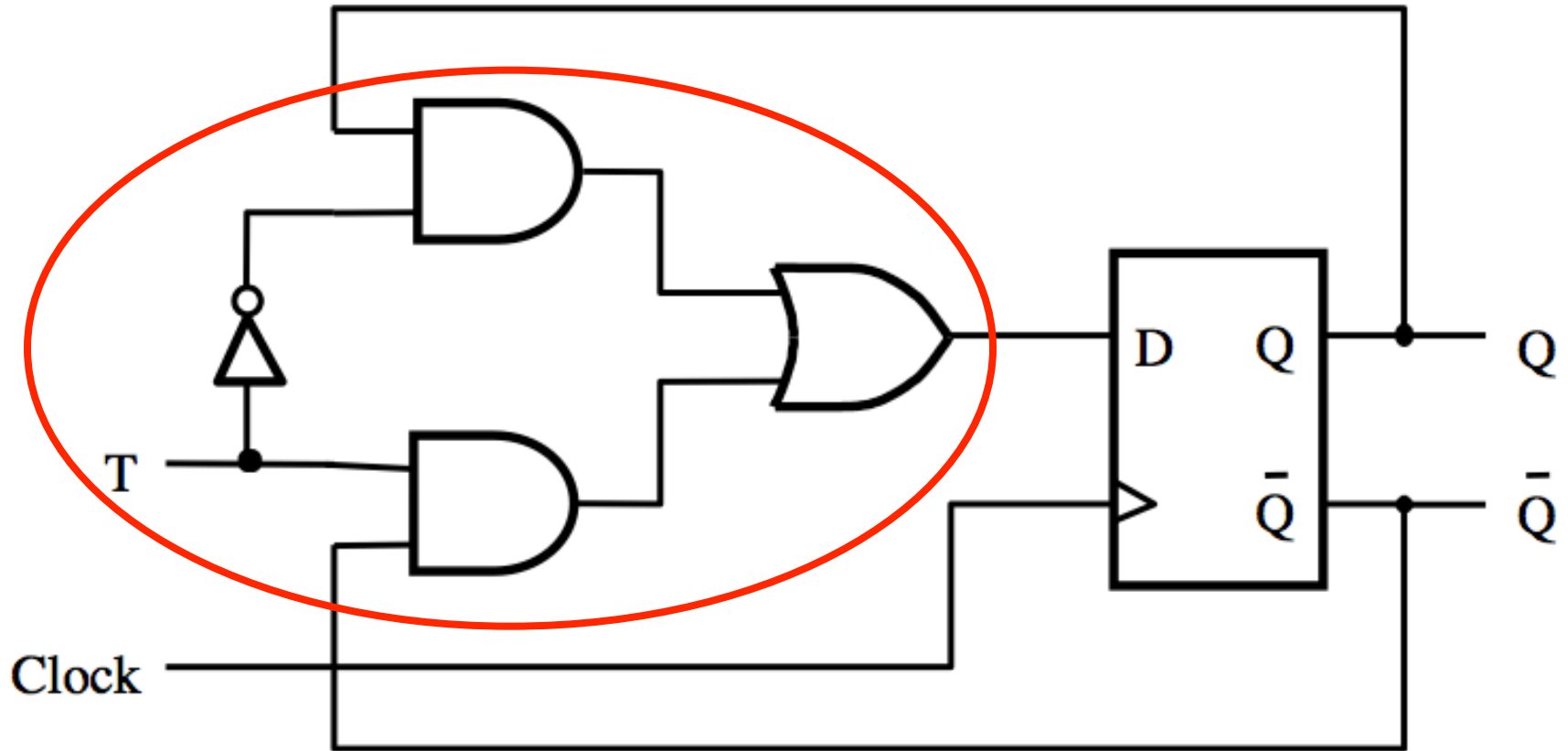


What is this?


[ Figure 5.15a from the textbook ]




**What is this?**

 

# What is this?

 

# T Flip-Flop

 


# What is this?




+

Clock

 


= ?

# T Flip-Flop

 


# **JK Flip-Flop**

# JK Flip-Flop

 

$$D = \overline{JQ} + \overline{KQ}$$


# JK Flip-Flop

 

(a) Circuit

J	K	$Q(t+1)$
0	0	$Q(t)$
0	1	0
1	0	1
1	1	$\bar{Q}(t)$

(b) Truth table

 

(c) Graphical symbol



# **JK Flip-Flop (How it Works)**

**A versatile circuit that can be used both as a SR flip-flop and as a T flip flop**

**If  $J=0$  and  $S=0$  it stays in the same state**

**Just like SR It can be set and reset**

**$J=S$  and  $K=R$**


**If  $J=K=1$  then it behaves as a T flip-flop**

# Registers

# **Register (Definition)**

**An n-bit structure consisting of flip-flops**

# A simple shift register

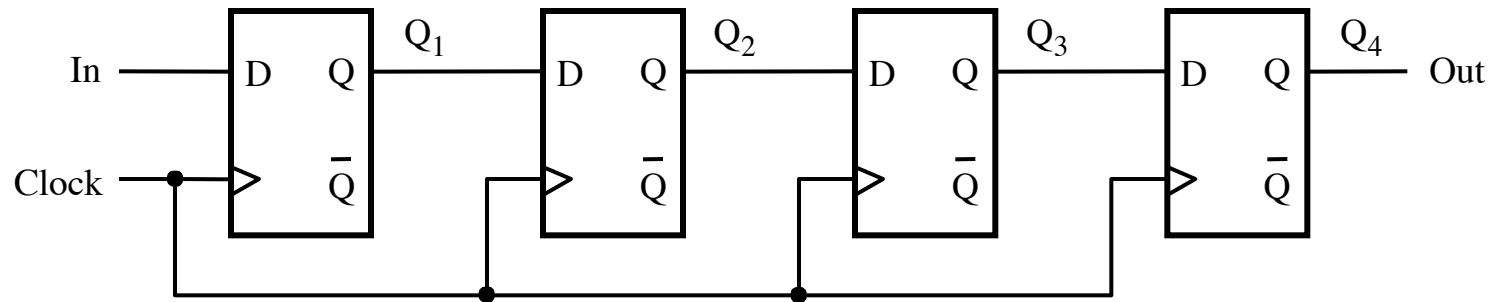


(a) Circuit

	In	Q <sub>1</sub>	Q <sub>2</sub>	Q <sub>3</sub>	Q <sub>4</sub> = Out
$t_0$	1	0	0	0	0
$t_1$	0	1	0	0	0
$t_2$	1	0	1	0	0
$t_3$	1	1	0	1	0
$t_4$	1	1	1	0	1
$t_5$	0	1	1	1	0
$t_6$	0	0	1	1	1
$t_7$	0	0	0	1	1

(b) A sample sequence

[ Figure 5.17 from the textbook ]


# Parallel-access shift register

 


[ Figure 5.18 from the textbook ]

# Counters


# A three-bit up-counter

 

# A three-bit up-counter

 


(a) Circuit

 

(b) Timing diagram




# A three-bit down-counter

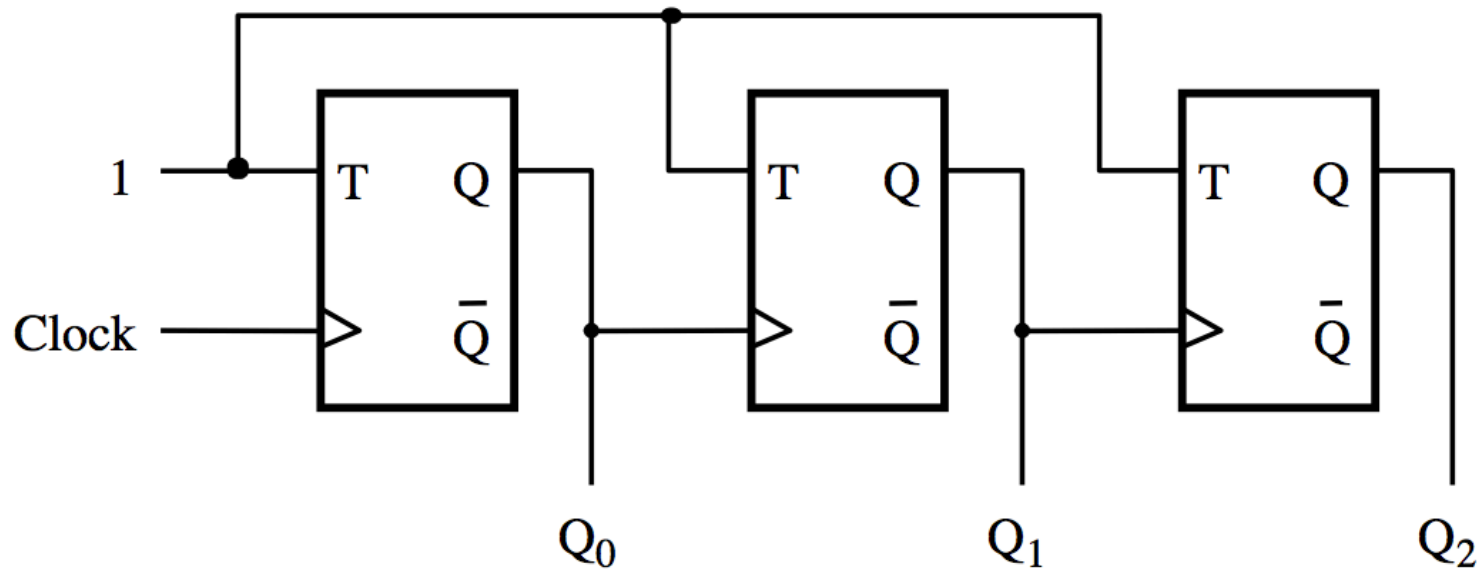


[ Figure 5.20 from the textbook ]

# A three-bit down-counter

 

(a) Circuit

 


(b) Timing diagram

[ Figure 5.20 from the textbook ]

# **Synchronous Counters**


# A four-bit synchronous up-counter

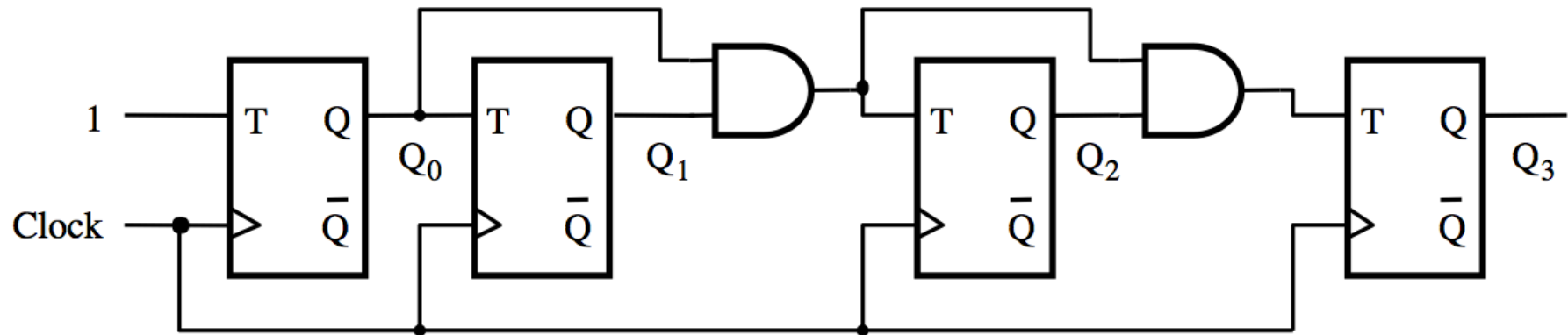

[ Figure 5.21 from the textbook ]

# **Synchronous Counter with D Flip-Flops**


# A four-bit counter with D flip-flops

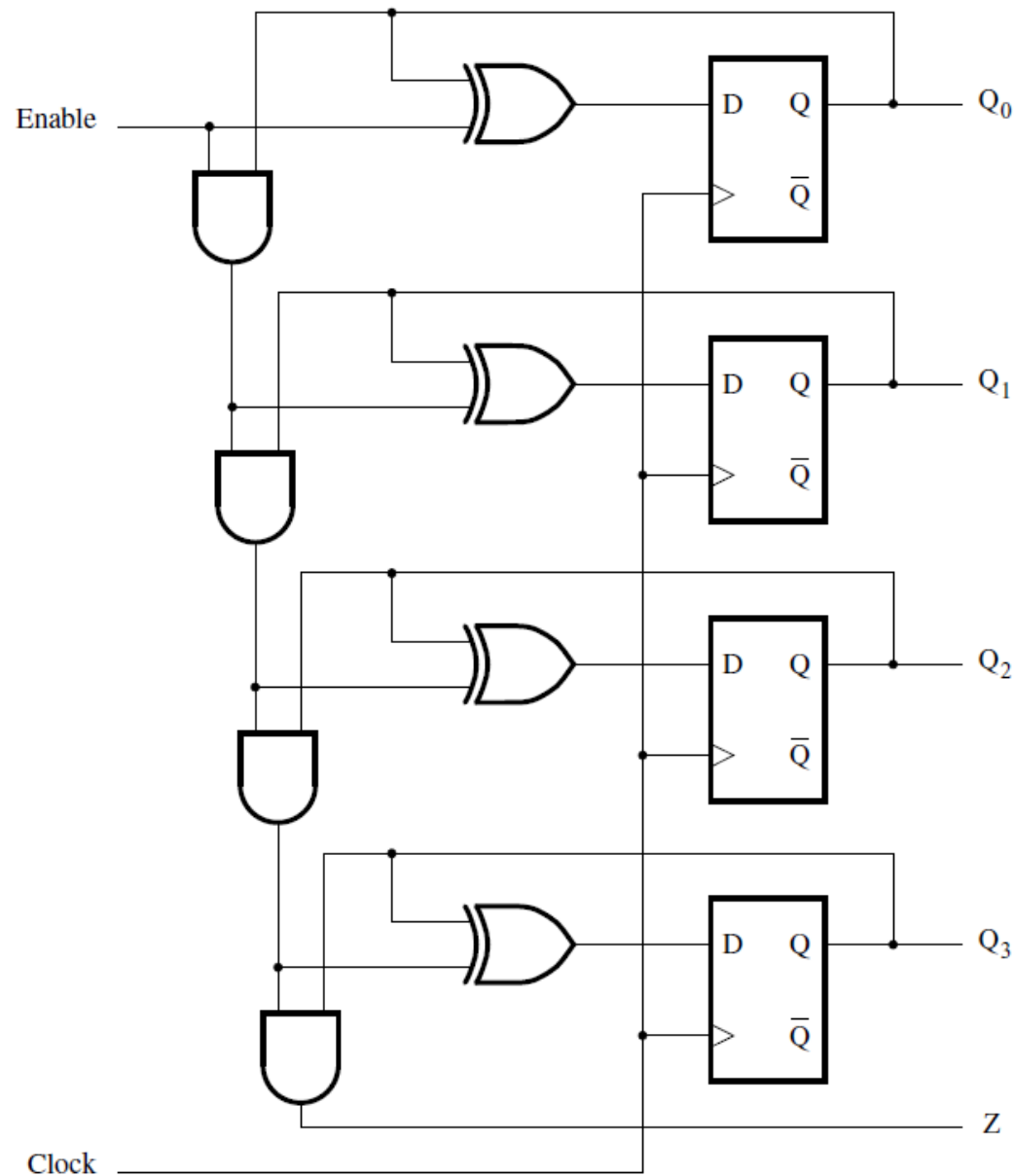

[ Figure 5.23 from the textbook ]

# **Counters with Parallel Load**


# A counter with parallel-load capability

 

[ Figure 5.24 from the textbook ]




# A shift register with parallel load and enable control inputs

 


[ Figure 5.59 from the textbook ]

# What does this circuit do?

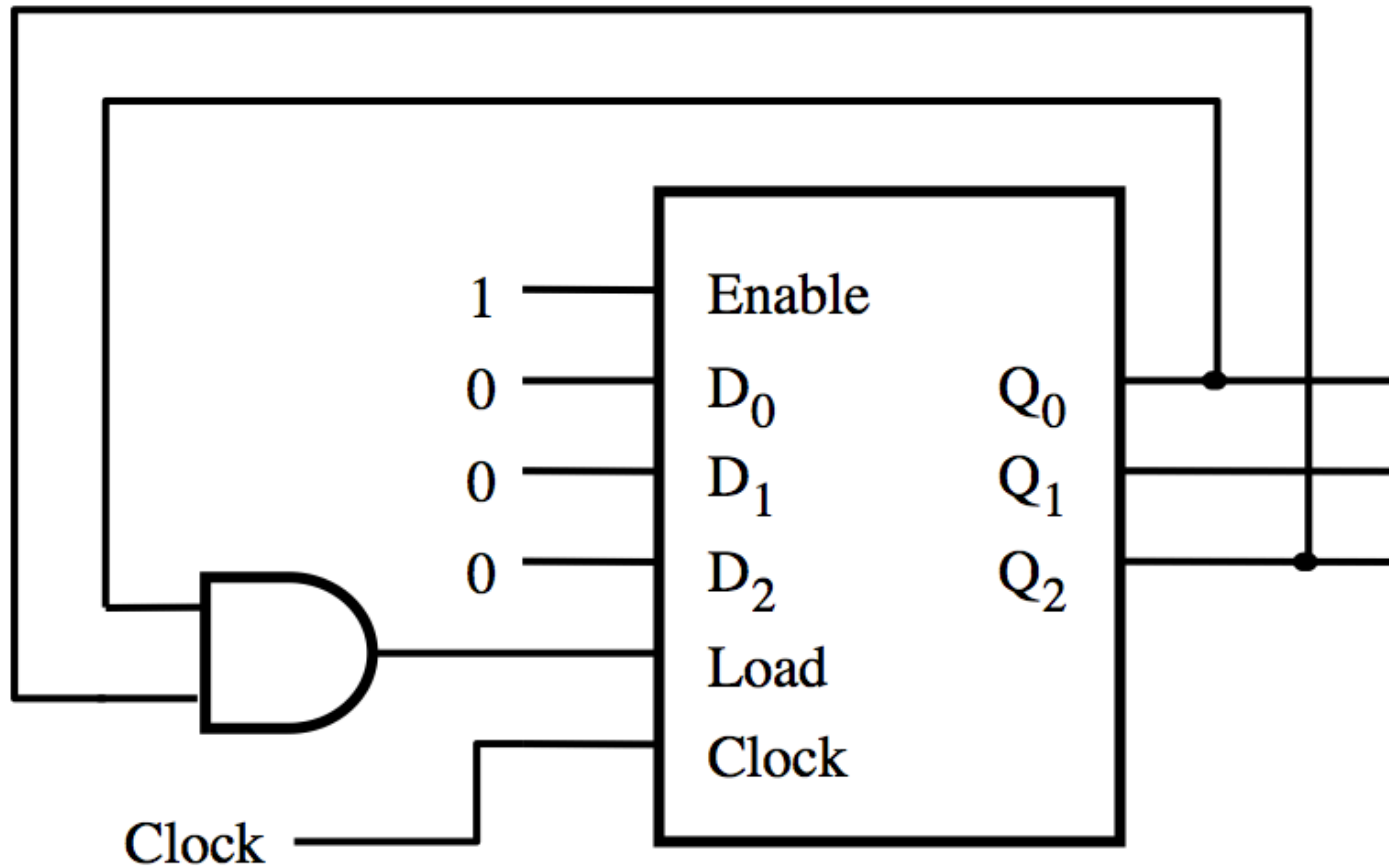


# **Designing The Control Circuit**

# A Simple Processor

 


[ Figure 7.9 from the textbook ]

# The function register and decoders

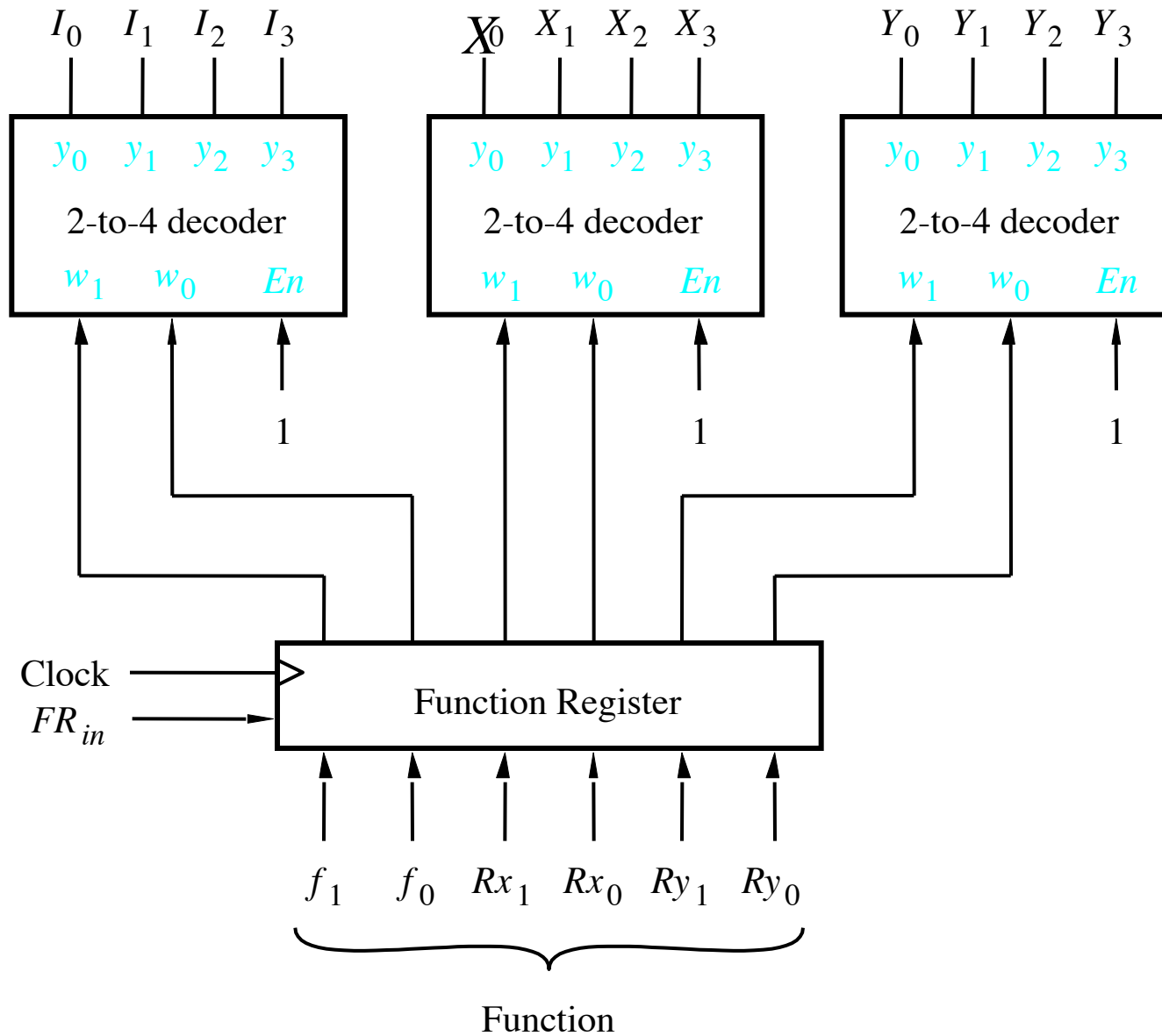

[ Figure 7.11 from the textbook ]
 
# A part of the control circuit for the processor



# Control signals asserted in each time step

	T <sub>1</sub>	T <sub>2</sub>	T <sub>3</sub>
(Load): I <sub>0</sub>	Extern R <sub>in</sub> = X Done		
(Move): I <sub>1</sub>	R <sub>in</sub> = X R <sub>out</sub> = Y Done		
(Add): I <sub>2</sub>	R <sub>out</sub> = X A <sub>in</sub>	R <sub>out</sub> = Y G <sub>in</sub> AddSub = 0	G <sub>out</sub> R <sub>in</sub> = X Done
(Sub): I <sub>3</sub>	R <sub>out</sub> = X A <sub>in</sub>	R <sub>out</sub> = Y G <sub>in</sub> AddSub = 1	G <sub>out</sub> R <sub>in</sub> = X Done

# Operations performed by this processor

Operation	Function Performed
<b>Load</b> Rx, Data	Rx ← Data
<b>Move</b> Rx, Ry	Rx ← [Ry]
<b>Add</b> Rx, Ry	Rx ← [Rx] + [Ry]
<b>Sub</b> Rx, Ry	Rx ← [Rx] - [Ry]




# Operations performed by this processor

Operation	Function Performed
<b>Load</b> Rx, Data	Rx ← Data
<b>Move</b> Rx, Ry	Rx ← [Ry]
<b>Add</b> Rx, Ry	Rx ← [Rx] + [Ry]
<b>Sub</b> Rx, Ry	Rx ← [Rx] - [Ry]

Where Rx and Ry can be one of four possible options: R0, R1, R2, and R3

# Operations performed by this processor

 


$f_1$	$f_0$	Function
0	0	Load
0	1	Move
1	0	Add
1	1	Sub

$Rx_1$	$Rx_0$	Register
0	0	R0
0	1	R1
1	0	R2
1	1	R3

$Ry_1$	$Ry_0$	Register
0	0	R0
0	1	R1
1	0	R2
1	1	R3

# Operations performed by this processor

 


$f_1$	$f_0$	Function
0	0	Load
<b>0</b>	<b>1</b>	<b>Move</b>
1	0	Add
1	1	Sub

$Rx_1$	$Rx_0$	Register
0	0	R0
0	1	R1
1	0	R2
<b>1</b>	<b>1</b>	<b>R3</b>

$Ry_1$	$Ry_0$	Register
<b>0</b>	<b>0</b>	<b>R0</b>
0	1	R1
1	0	R2
1	1	R3

# Operations performed by this processor

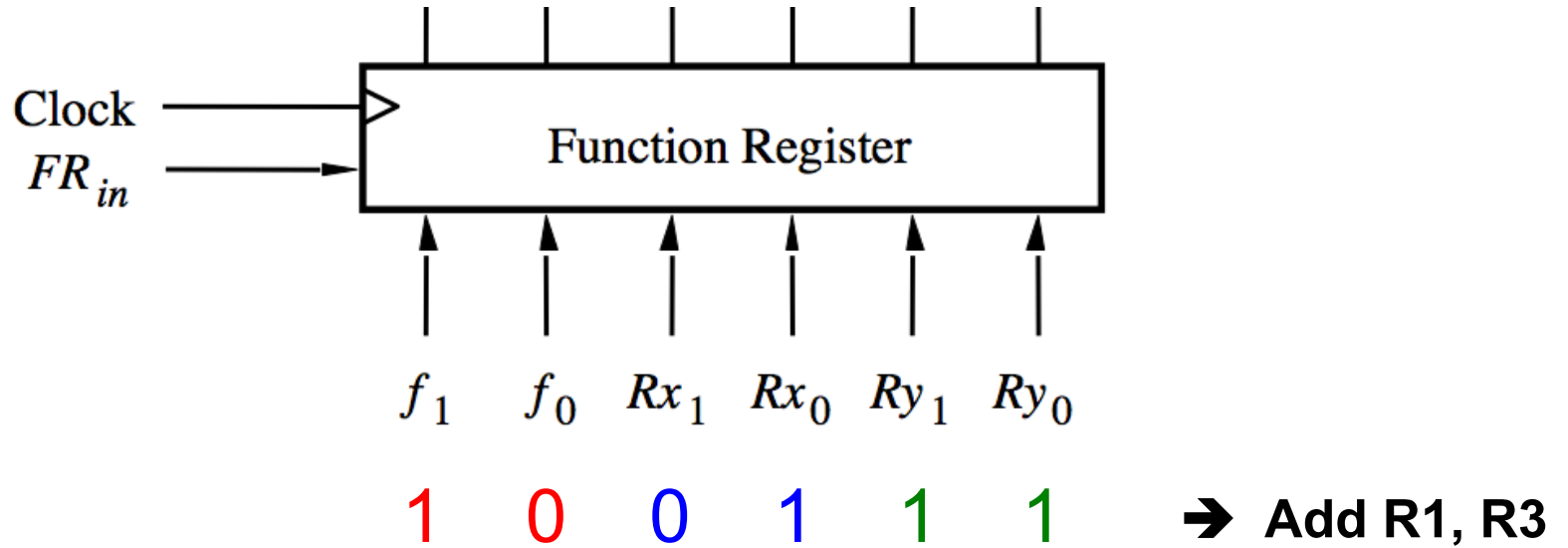


$f_1$	$f_0$	Function
0	0	Load
0	1	Move
1	0	Add
1	1	Sub

$Rx_1$	$Rx_0$	Register
0	0	R0
0	1	R1
1	0	R2
1	1	R3

$Ry_1$	$Ry_0$	Register
0	0	R0
0	1	R1
1	0	R2
1	1	R3

# Operations performed by this processor

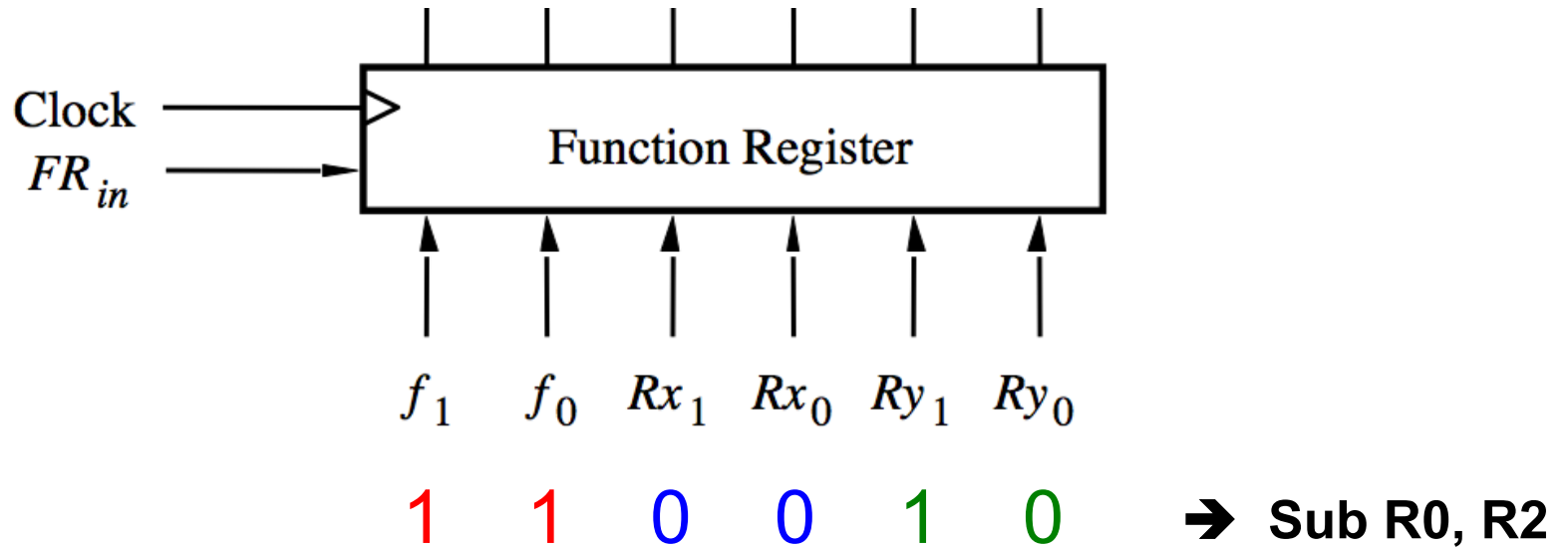


$f_1$	$f_0$	Function
0	0	Load
0	1	Move
1	0	Add
<b>1</b>	<b>1</b>	<b>Sub</b>

$Rx_1$	$Rx_0$	Register
<b>0</b>	<b>0</b>	<b>R0</b>
0	1	R1
1	0	R2
1	1	R3

$Ry_1$	$Ry_0$	Register
0	0	R0
0	1	R1
<b>1</b>	<b>0</b>	<b>R2</b>
1	1	R3

# Operations performed by this processor

 


$f_1$	$f_0$	Function
<b>0</b>	<b>0</b>	<b>Load</b>
0	1	Move
1	0	Add
1	1	Sub

$Rx_1$	$Rx_0$	Register
0	0	R0
0	1	R1
<b>1</b>	<b>0</b>	<b>R2</b>
1	1	R3

$Ry_1$	$Ry_0$	Register
0	0	R0
0	1	R1
1	0	R2
1	1	R3

# Similar Encoding is Used by Modern Chips

## MIPS32 Add Immediate Instruction

 

Equivalent mnemonic:

**addi** \$r1, \$r2, 350

# Sample Assembly Language Program For This Processor

```
Move   R3 , R0
Add    R1 , R3
Sub    R0 , R2
Load   R2 , Data
```



# Machine Language vs Assembly Language

Machine Language	Assembly Language	Meaning / Interpretation
011100	Move R3, R0	R3 ← [R0]
100111	Add R1, R3	R1 ← [R1] + [R3]
110010	Sub R0, R2	R0 ← [R0] - [R2]
001000	Load R2, Data	R2 ← Data

# Machine Language vs Assembly Language

Machine Language	Assembly Language	Meaning / Interpretation
011100	Move R3, R0	R3 ← [R0]
100111	Add R1, R3	R1 ← [R1] + [R3]
110010	Sub R0, R2	R0 ← [R0] - [R2]
001000	Load R2, Data	R2 ← Data

# Machine Language vs Assembly Language

Machine Language	Assembly Language	Meaning / Interpretation
011100	Move R3, R0	R3 ← [R0]
100111	Add R1, R3	R1 ← [R1] + [R3]
110010	Sub R0, R2	R0 ← [R0] - [R2]
001000	Load R2, Data	R2 ← Data

For short, each line  
can be expressed as a  
hexadecimal number

# Machine Language vs Assembly Language

Machine Language	Assembly Language	Meaning / Interpretation
1C	Move R3, R0	R3 ← [R0]
27	Add R1, R3	R1 ← [R1] + [R3]
32	Sub R0, R2	R0 ← [R0] - [R2]
08	Load R2, Data	R2 ← Data

**Questions?**

**THE END**