

P1. (10 points)

Briefly explain the major difference between a Moore state machine and a Mealy state machine.

P2. (25 points)

A FSM with an input w and an output z has the following state table.

Present State	Next State		Output z	
	$w=0$	$w=1$	$w=0$	$w=1$
A	A	B	0	1
B	C	B	1	0
C	B	A	0	0


- (5 points) Draw the state diagram based on the state table.
- (5 points) Complete the state-assigned table based on the state table.

	Present State y_1y_0	Next State Y_1Y_0		Output z	
		$w=0$	$w=1$	$w=0$	$w=1$
A	0 0				
B	0 1				
C	1 0				

- (5 points) Find the simplified SOP expressions for Y_1 , Y_0 , and z .
- (5 points) Draw the circuit diagram using D flip-flops and any other required gates.
- (5 points) Is this a Moore machine or a Mealy machine? Why?

P3. (15 points)

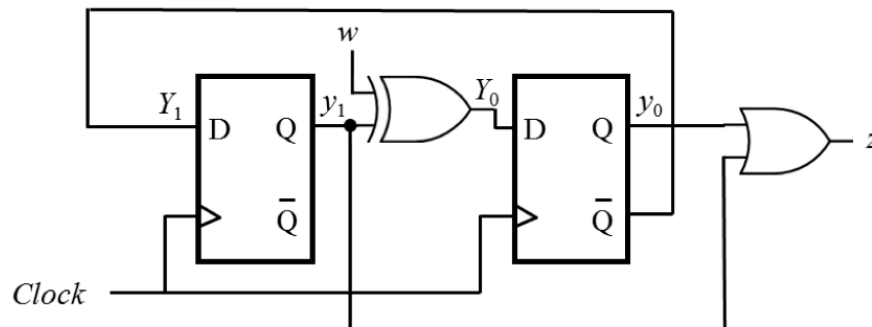
A FSM has two D flip-flops, an input w , and an output z . The circuit diagram is shown below.



- (5 points) Find the logic expressions of Y_1 , Y_0 , and the output z .
- (5 points) Show the state-assigned table of the FSM.
- (5 points) Draw the state diagram of the FSM.

P4. (10 points)

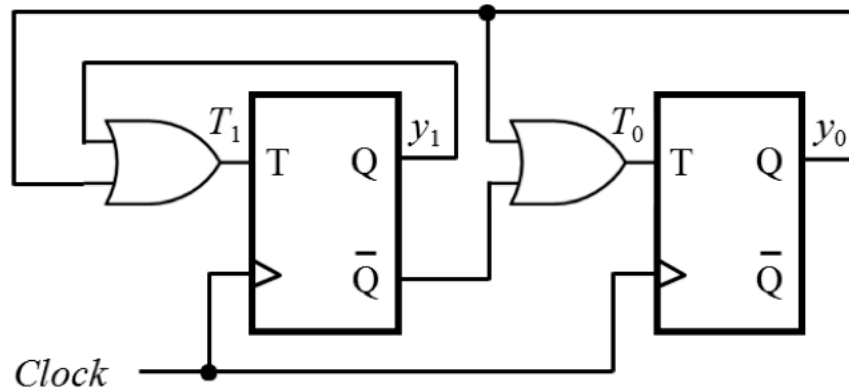A two-bit counter has the following circuit diagram. The output is $z_1z_0 = y_1y_0$.



- (5 points) Draw the state diagram of the counter.
- (5 points) What is the repeated counting sequence of this counter?

P5. (30 points)

Consider the following state table for a FSM.

Present State	Next State		Output z
	$w=0$	$w=1$	
A	A	B	0
B	B	C	1
C	C	D	0
D	D	A	1

- (5 points) Draw the state diagram of the FSM.
- (5 points) Draw the circuit diagram of FSM using D flip-flops.
- (5 points) Perform state minimization to minimize the number of states. Show your partitions in the procedure.
- (5 points) Draw the new state diagram of the minimized FSM.
- (5 points) Draw the circuit diagram of the minimized FSM using D flip-flops.
- (5 points) Compare the circuits in (b) and (e), what is the benefit of state minimization?

P6. (10 points)

Bob needs to use a 3-bit up-counter. However, he only has a 4-bit synchronous down-counter and several NOT gates. He is NOT allowed to modify the internal structure of the down-counter. How can he construct the 3-bit up-counter using only the devices that he has?