 


- T1. Answer any general questions about the materials covered in the second midterm exam.  
 T2. Answer any general questions about Lab 08.  
 T3. Solve the following problems.

1. Consider a T flip flop. Let Clk be a periodical signal (switches from 1 to 0 or from 0 to 1) every 1 micro second. Let  $T=1$ . Describe the waveform of the output Q.
2. Draw waveforms for signals D, Clk, S, R, SS, RR, Q and Q' for the gated D-latch circuit below (same as Fig. 5.7(a) in textbook) for 16 time steps. Assume  $Q=0$  and  $Q'=1$  initially. Assume  $D = 0$  from time steps 0 to 6 and then  $D=1$ . Clk is 0 from time steps 0 to 7 and then Clk = 1. Assume each gate has a delay of one time step.



3. A TD flip flop has two inputs, C and I. When  $C=0$ , the TD FF acts as a D FF, where  $D=I$ . When  $C=1$ , the TD FF acts as a T FF, where  $T=I$ . Design a TD FF using one JK flip flop and several other simple gates like AND, OR, NOT, and XOR. Please make your design as minimal as possible.
4. The universal flip-flop has two operation select lines  $S_2$  and  $S_1$ , and two inputs  $I_2$  and  $I_1$ . It can work as the SR, D, JK or T flip-flops depending on the values of  $S_2$  and  $S_1$ , and the inputs  $I_2$  and  $I_1$  act as the flip-flop inputs as given below. For example, according to the table below, when  $S_2 = 0$  and  $S_1 = 1$ , the flip-flop works as a D flip-flop.  $I_1$  is equal to D if  $I_2 = 0$ , while  $I_1$  is equal to  $D'$  if  $I_2 = 1$ . Convert a JK flip-flop to a universal flip-flop using two 2-to-1 multiplexers at the input of J and K terminals and  $S_1$  as their select. Identify inputs of the muxes.

$S_2$	$S_1$	Operation	$I_2$	$I_1$
0	0	SR flip-flop	S	R
0	1	D flip-flop	0	D
0	1	D flip-flop	1	$D'$
1	0	JK flip-flop	J	K
1	1	T flip-flop	0	T
1	1	T flip-flop	1	$T'$