
 


## Recitation #9 Solutions

1. The circuit is given below:

 

2. (a) 3-bit up synchronous up-counter with enable:



All clear and preset signals should be set to 1, i.e.,  $C2=C1=C0=P2=P1=P0=1$ .

(b) Clear and preset signals should be set as follows:

q2	q1	q0	C2	C1	C0	P2	P1	P0
0	0	0	1	1	1	1	1	1
0	0	1	1	1	1	1	1	1
0	1	0	1	1	1	1	1	1
0	1	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	1
1	0	1	0	0	0	1	1	1
1	1	0	d	d	d	d	d	d
1	1	1	d	d	d	d	d	d

$$C2=C1=C0=(q2'+q0')$$

$$P2=P1=P0=1$$

(c) Clear and preset signals should be set as follows:

q2	q1	q0	C2	C1	C0	P2	P1	P0
0	0	0	1	1	1	1	1	1
0	0	1	1	1	1	1	1	1
0	1	0	1	1	1	1	1	1
0	1	1	1	0	1	0	1	0
1	0	0	d	d	d	d	d	d
1	0	1	0	0	0	1	1	1
1	1	0	d	d	d	d	d	d
1	1	1	d	d	d	d	d	d

$$C2=C0=q2', C1=q2'(q1'+q0')$$

$$P2=P0=(q1'+q0'), P1=1$$

3. (a) Clear and preset signals should be set as follows:

q2	q1	q0	C2	C1	C0	P2	P1	P0
0	0	0	1	1	1	1	1	1
0	0	1	1	1	1	1	1	1
0	1	0	1	1	1	1	1	1
0	1	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	1
1	0	1	1	1	1	1	1	1
1	1	0	0	0	0	1	1	1
1	1	1	d	d	d	d	d	d

$$C2=C1=C0=(q2'+q1')$$

$$P2=P1=P0=1$$

- (b) Ideally, all flip-flops will be forced to 0 at the same time when  $q2=1$ ,  $q1=1$  and  $q0=0$  (or 1). However, if the flip-flops switch at different speeds, one of  $q2$  and  $q1$  may be changed to 0 while the other may still be 1. Then the C signals may be changed to 1 before all flip-flops are cleared.
4. The idea of a 4-bit ring counter is described in Ch. 5.11.2 and Fig. 5.28 in textbook. The following modification is needed to make it a 6-bit ring counter. First, the 3-bit counter should be converted to a modulo-6 counter by clearing it after 101 is detected. Second, only  $Q0$ ,  $Q1$ , ...,  $Q5$  of the 3-to-8 decoder are treated as outputs of the 6-bit ring counter.  $Q6$  and  $Q7$  are ignored.