



# **CprE 281: Digital Logic**

**Instructor: Alexander Stoytchev**

**<http://www.ece.iastate.edu/~alexs/classes/>**

# Fast Adders

*CprE 281: Digital Logic  
Iowa State University, Ames, IA  
Copyright © Alexander Stoytchev*

# **Administrative Stuff**

- **HW5 is out**
- **It is due on Monday Oct 2 @ 4pm.**
- **Please write clearly on the first page (in block capital letters) the following three things:**
  - **Your First and Last Name**
  - **Your Student ID Number**
  - **Your Lab Section Letter**
- **Also, please staple all of your pages together.**

# Administrative Stuff

- **Labs Next Week**
- **Mini-Project**
- **This one is worth 3% of your grade.**
- **Make sure to get all the points.**
- **[http://www.ece.iastate.edu/~alexs/classes/2017\\_Fall\\_281/labs/Project-Mini/](http://www.ece.iastate.edu/~alexs/classes/2017_Fall_281/labs/Project-Mini/)**

# **Quick Review**

**The problems in which row are easier to calculate?**

$$\begin{array}{r} \text{—} \quad 82 \\ \quad 61 \\ \hline ?? \end{array}$$

$$\begin{array}{r} \text{—} \quad 48 \\ \quad 26 \\ \hline ?? \end{array}$$

$$\begin{array}{r} \text{—} \quad 32 \\ \quad 11 \\ \hline ?? \end{array}$$

$$\begin{array}{r} \text{—} \quad 82 \\ \quad 64 \\ \hline ?? \end{array}$$

$$\begin{array}{r} \text{—} \quad 48 \\ \quad 29 \\ \hline ?? \end{array}$$

$$\begin{array}{r} \text{—} \quad 32 \\ \quad 13 \\ \hline ?? \end{array}$$

The problems in which row are easier to calculate?

$$\begin{array}{r} \phantom{-} 82 \\ - 61 \\ \hline 21 \end{array}$$

$$\begin{array}{r} \phantom{-} 48 \\ - 26 \\ \hline 22 \end{array}$$

$$\begin{array}{r} \phantom{-} 32 \\ - 11 \\ \hline 21 \end{array}$$

Why?

$$\begin{array}{r} \phantom{-} 82 \\ - 64 \\ \hline 18 \end{array}$$

$$\begin{array}{r} \phantom{-} 48 \\ - 29 \\ \hline 19 \end{array}$$

$$\begin{array}{r} \phantom{-} 32 \\ - 13 \\ \hline 19 \end{array}$$

# Another Way to Do Subtraction

$$82 - 64 = 82 + 100 - 100 - 64$$



# Another Way to Do Subtraction

$$\begin{aligned}82 - 64 &= 82 + 100 - 100 - 64 \\ &= 82 + (100 - 64) - 100\end{aligned}$$

# Another Way to Do Subtraction

$$82 - 64 = 82 + 100 - 100 - 64$$

$$= 82 + (100 - 64) - 100$$

$$= 82 + (99 + 1 - 64) - 100$$

# Another Way to Do Subtraction

$$\begin{aligned}82 - 64 &= 82 + 100 - 100 - 64 \\ &= 82 + (100 - 64) - 100 \\ &= 82 + (99 + 1 - 64) - 100 \\ &= 82 + (99 - 64) + 1 - 100\end{aligned}$$

# Another Way to Do Subtraction

$$82 - 64 = 82 + 100 - 100 - 64$$

$$= 82 + (100 - 64) - 100$$

$$= 82 + (99 + 1 - 64) - 100$$

Does not require borrows

$$= 82 + (99 - 64) + 1 - 100$$

# 9's Complement (subtract each digit from 9)

$$\begin{array}{r} 99 \\ - 64 \\ \hline 35 \end{array}$$

# 10's Complement

(subtract each digit from 9 and add 1 to the result)

$$\begin{array}{r} \phantom{-} 99 \\ - 64 \\ \hline 35 + 1 = 36 \end{array}$$

# Another Way to Do Subtraction

$$82 - 64 = 82 + (99 - 64) + 1 - 100$$

# Another Way to Do Subtraction

9's complement

$$82 - 64 = 82 + (99 - 64) + 1 - 100$$



# Another Way to Do Subtraction

9's complement

$$\begin{aligned} 82 - 64 &= 82 + (99 - 64) + 1 - 100 \\ &= 82 + 35 + 1 - 100 \end{aligned}$$

# Another Way to Do Subtraction

9's complement

$$82 - 64 = 82 + (99 - 64) + 1 - 100$$

10's complement

$$= 82 + (35 + 1) - 100$$

# Another Way to Do Subtraction

9's complement

$$82 - 64 = 82 + (99 - 64) + 1 - 100$$

10's complement

$$= 82 + (35 + 1) - 100$$

$$= 82 + 36 - 100$$

# Another Way to Do Subtraction

9's complement

$$82 - 64 = 82 + (99 - 64) + 1 - 100$$

10's complement

$$= 82 + (35 + 1) - 100$$

$$= (82 + 36) - 100 \quad // \text{ Add the first two.}$$

$$= 118 - 100$$

# Another Way to Do Subtraction

9's complement

$$82 - 64 = 82 + (99 - 64) + 1 - 100$$

10's complement

$$= 82 + (35 + 1) - 100$$

$$= (82 + 36) - 100 \quad // \text{ Add the first two.}$$

$$= 118 - 100 \quad // \text{ Just delete the leading 1.}$$

// No need to subtract 100.

$$= 18$$



# 2' s complement

Let  $K$  be the negative equivalent of an  $n$ -bit positive number  $P$ .

Then, in 2' s complement representation  $K$  is obtained by subtracting  $P$  from  $2^n$  , namely

$$K = 2^n - P$$

# Deriving 2' s complement

For a positive n-bit number P, let  $K_1$  and  $K_2$  denote its 1' s and 2' s complements, respectively.

$$K_1 = (2^n - 1) - P$$

$$K_2 = 2^n - P$$

Since  $K_2 = K_1 + 1$ , it is evident that in a logic circuit the 2' s complement can be computed by inverting all bits of P and then adding 1 to the resulting 1' s-complement number.



**Find the 2' s complement of ...**

0 1 0 1

0 0 1 0

0 1 0 0

0 1 1 1

# Find the 2's complement of ...

0 1 0 1

1 0 1 0

0 0 1 0

1 1 0 1

0 1 0 0

1 0 1 1

0 1 1 1

1 0 0 0

Invert all bits.

# Find the 2's complement of ...

$$\begin{array}{r} 0101 \\ + 1010 \\ \hline 1011 \end{array}$$

$$\begin{array}{r} 0010 \\ + 1101 \\ \hline 1110 \end{array}$$

$$\begin{array}{r} 0100 \\ + 1011 \\ \hline 1100 \end{array}$$

$$\begin{array}{r} 0111 \\ + 1000 \\ \hline 1001 \end{array}$$

Then add 1.

# Interpretation of four-bit signed integers

$b_3b_2b_1b_0$	Sign and magnitude	1's complement	2's complement
0111	+7	+7	+7
0110	+6	+6	+6
0101	+5	+5	+5
0100	+4	+4	+4
0011	+3	+3	+3
0010	+2	+2	+2
0001	+1	+1	+1
0000	+0	+0	+0
1000	-0	-7	-8
1001	-1	-6	-7
1010	-2	-5	-6
1011	-3	-4	-5
1100	-4	-3	-4
1101	-5	-2	-3
1110	-6	-1	-2
1111	-7	-0	-1

# Interpretation of four-bit signed integers

$b_3b_2b_1b_0$	Sign and magnitude	1's complement	2's complement
0111	+7	+7	+7
0110	+6	+6	+6
0101	+5	+5	+5
0100	+4	+4	+4
0011	+3	+3	+3
0010	+2	+2	+2
0001	+1	+1	+1
0000	+0	+0	+0
1000	-0	-7	-8
1001	-1	-6	-7
1010	-2	-5	-6
1011	-3	-4	-5
1100	-4	-3	-4
1101	-5	-2	-3
1110	-6	-1	-2
1111	-7	-0	-1

The top half is the same in all three representations.  
It corresponds to the positive integers.

# Interpretation of four-bit signed integers

$b_3b_2b_1b_0$	Sign and magnitude	1's complement	2's complement
0111	+7	+7	+7
0110	+6	+6	+6
0101	+5	+5	+5
0100	+4	+4	+4
0011	+3	+3	+3
0010	+2	+2	+2
0001	+1	+1	+1
0000	+0	+0	+0
1000	-0	-7	-8
1001	-1	-6	-7
1010	-2	-5	-6
1011	-3	-4	-5
1100	-4	-3	-4
1101	-5	-2	-3
1110	-6	-1	-2
1111	-7	-0	-1

In all three representations the first bit represents the sign.  
If that bit is 1, then the number is negative.

# Interpretation of four-bit signed integers

$b_3b_2b_1b_0$	Sign and magnitude	1's complement	2's complement
0111	+7	+7	+7
0110	+6	+6	+6
0101	+5	+5	+5
0100	+4	+4	+4
0011	+3	+3	+3
0010	+2	+2	+2
0001	+1	+1	+1
0000	+0	+0	+0
1000	-0	-7	-8
1001	-1	-6	-7
1010	-2	-5	-6
1011	-3	-4	-5
1100	-4	-3	-4
1101	-5	-2	-3
1110	-6	-1	-2
1111	-7	-0	-1

Notice that in this representation there are two zeros!

# Interpretation of four-bit signed integers

$b_3b_2b_1b_0$	Sign and magnitude	1's complement	2's complement
0111	+7	+7	+7
0110	+6	+6	+6
0101	+5	+5	+5
0100	+4	+4	+4
0011	+3	+3	+3
0010	+2	+2	+2
0001	+1	+1	+1
0000	+0	+0	+0
1000	-0	-7	-8
1001	-1	-6	-7
1010	-2	-5	-6
1011	-3	-4	-5
1100	-4	-3	-4
1101	-5	-2	-3
1110	-6	-1	-2
1111	-7	-0	-1

There are two zeros in this representation as well!


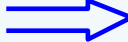
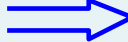
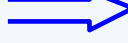

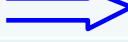
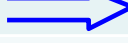
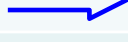



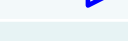
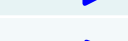
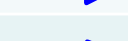




# Interpretation of four-bit signed integers

$b_3b_2b_1b_0$	Sign and magnitude	1's complement	2's complement
0111	+7	+7	+7
0110	+6	+6	+6
0101	+5	+5	+5
0100	+4	+4	+4
0011	+3	+3	+3
0010	+2	+2	+2
0001	+1	+1	+1
0000	+0	+0	+0
1000	-0	-7	-8
1001	-1	-6	-7
1010	-2	-5	-6
1011	-3	-4	-5
1100	-4	-3	-4
1101	-5	-2	-3
1110	-6	-1	-2
1111	-7	-0	-1

In this representation there is one more negative number.

# Taking the 2's complement negates the number


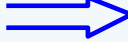
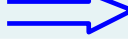
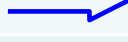

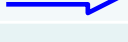
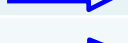






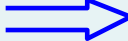
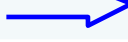

decimal	$b_3 b_2 b_1 b_0$	take the 2's complement	$b_3 b_2 b_1 b_0$	decimal
+7	0111		1001	-7
+6	0110		1010	-6
+5	0101		1011	-5
+4	0100		1100	-4
+3	0011		1101	-3
+2	0010		1110	-2
+1	0001		1111	-1
+0	0000		0000	+0
-8	1000		1000	-8
-7	1001		0111	+7
-6	1010		0110	+6
-5	1011		0101	+5
-4	1100		0100	+4
-3	1101		0011	+3
-2	1110		0010	+2
-1	1111		0001	+1

# Taking the 2's complement negates the number

decimal	b <sub>3</sub> b <sub>2</sub> b <sub>1</sub> b <sub>0</sub>	take the 2's complement	b <sub>3</sub> b <sub>2</sub> b <sub>1</sub> b <sub>0</sub>	decimal
+7	0111	⇒	1001	-7
+6	0110	⇒	1010	-6
+5	0101	⇒	1011	-5
+4	0100	⇒	1100	-4
+3	0011	⇒	1101	-3
+2	0010	⇒	1110	-2
+1	0001	⇒	1111	-1
+0	0000	⇒	0000	+0
-8	1000	⇒	1000	-8
-7	1001	⇒	0111	+7
-6	1010	⇒	0110	+6
-5	1011	⇒	0101	+5
-4	1100	⇒	0100	+4
-3	1101	⇒	0011	+3
-2	1110	⇒	0010	+2
-1	1111	⇒	0001	+1


This is the only exception

# Taking the 2's complement negates the number

decimal	$b_3 b_2 b_1 b_0$	take the 2's complement	$b_3 b_2 b_1 b_0$	decimal
+7	0111		1001	-7
+6	0110		1010	-6
+5	0101		1011	-5
+4	0100		1100	-4
+3	0011		1101	-3
+2	0010		1110	-2
+1	0001		1111	-1
+0	0000		0000	+0
-8	1000		1000	-8
-7	1001		0111	+7
-6	1010		0110	+6
-5	1011		0101	+5
-4	1100		0100	+4
-3	1101		0011	+3
-2	1110		0010	+2
-1	1111		0001	+1

And this one too.

# The number circle for 2's complement

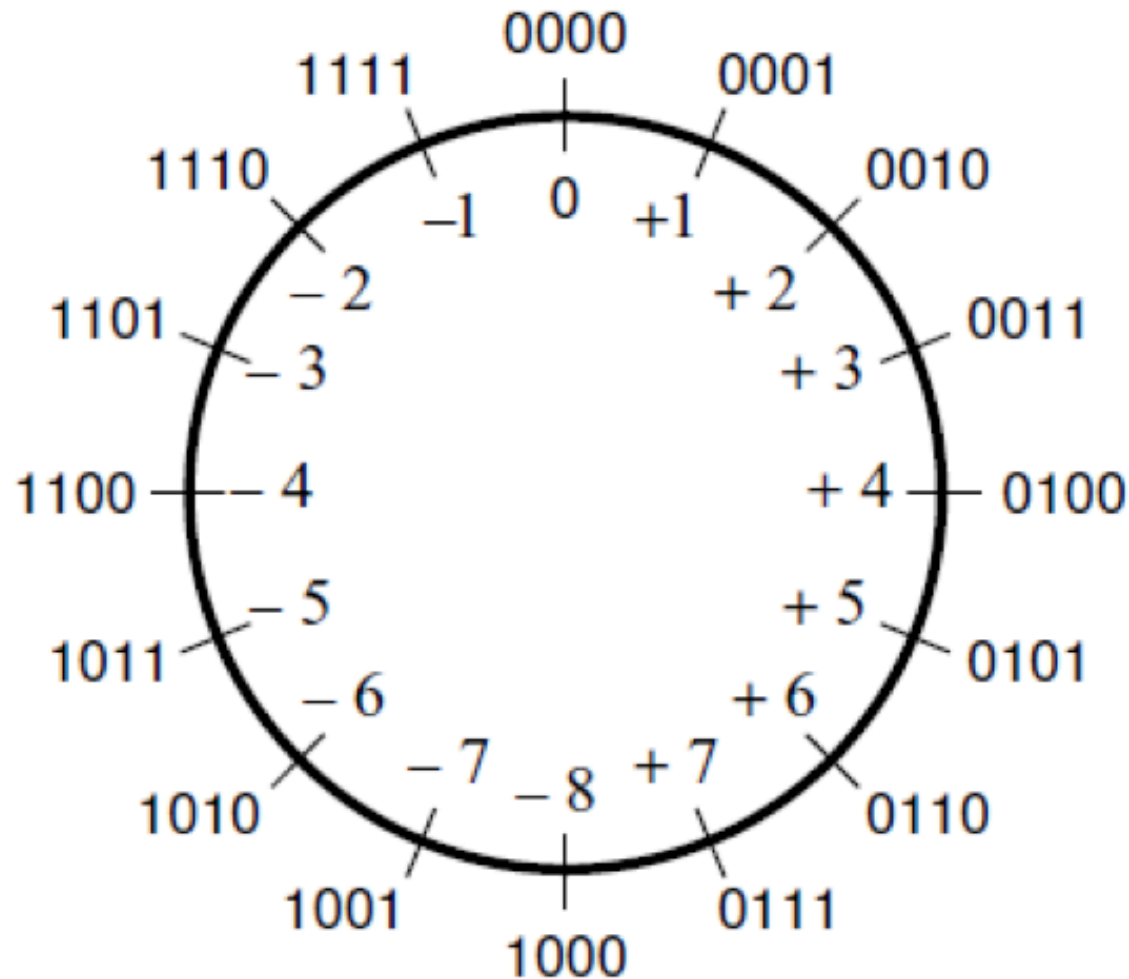

[ Figure 3.11a from the textbook ]

# A) Example of 2's complement addition

$$\begin{array}{r}
 (+5) \\
 + (+2) \\
 \hline
 (+7)
 \end{array}
 \qquad
 \begin{array}{r}
 0101 \\
 + 0010 \\
 \hline
 0111
 \end{array}$$

$b_3b_2b_1b_0$	2's complement
0111	+7
0110	+6
0101	+5
0100	+4
0011	+3
0010	+2
0001	+1
0000	+0
1000	-8
1001	-7
1010	-6
1011	-5
1100	-4
1101	-3
1110	-2
1111	-1


## B) Example of 2's complement addition

$$\begin{array}{r}
 (-5) \\
 + (+2) \\
 \hline
 (-3)
 \end{array}
 \qquad
 \begin{array}{r}
 \color{red}{1011} \\
 + \color{green}{0010} \\
 \hline
 \color{blue}{1101}
 \end{array}$$

$b_3b_2b_1b_0$	2's complement
0111	+7
0110	+6
0101	+5
0100	+4
0011	+3
<b>0010</b>	<b>+2</b>
0001	+1
0000	+0
1000	-8
1001	-7
1010	-6
<b>1011</b>	<b>-5</b>
1100	-4
<b>1101</b>	<b>-3</b>
1110	-2
1111	-1

# C) Example of 2's complement addition

$$\begin{array}{r}
 (+5) \quad \quad \quad 0101 \\
 + (-2) \quad \quad 1110 \\
 \hline
 (+3) \quad \quad 10011
 \end{array}$$



  
 ignore

$b_3b_2b_1b_0$	2's complement
0111	+7
0110	+6
0101	+5
0100	+4
0011	+3
0010	+2
0001	+1
0000	+0
1000	-8
1001	-7
1010	-6
1011	-5
1100	-4
1101	-3
1110	-2
1111	-1



# D) Example of 2's complement addition

$$\begin{array}{r}
 (-5) \\
 + (-2) \\
 \hline
 (-7)
 \end{array}
 \qquad
 \begin{array}{r}
 1011 \\
 + 1110 \\
 \hline
 11001
 \end{array}$$


  
 ignore

$b_3b_2b_1b_0$	2's complement
0111	+7
0110	+6
0101	+5
0100	+4
0011	+3
0010	+2
0001	+1
0000	+0
1000	-8
1001	-7
1010	-6
1011	-5
1100	-4
1101	-3
1110	-2
1111	-1



# **Naming Ambiguity: 2's Complement**

**2's complement has two different meanings:**

- **representation for signed integer numbers**
- **algorithm for computing the 2's complement (regardless of the representation of the number)**

# Naming Ambiguity: 2's Complement

2's complement has two different meanings:

- representation for signed integer numbers  
**in 2's complement**
- algorithm for computing the 2's complement  
(regardless of the representation of the number)  
**take the 2's complement**

# Example of 2's complement subtraction

$$\begin{array}{r} (+5) \\ - (+2) \\ \hline (+3) \end{array} \quad \begin{array}{r} 0101 \\ - 0010 \\ \hline \end{array} \quad \Rightarrow \quad \begin{array}{r} 0101 \\ + 1110 \\ \hline 10011 \\ \uparrow \\ \text{ignore} \end{array}$$

$\Rightarrow$  means take the 2's complement

# Example of 2's complement subtraction

$$\begin{array}{r} (+5) \\ \textcircled{-} (+2) \\ \hline (+3) \end{array} \quad \begin{array}{r} 0101 \\ - 0010 \\ \hline \end{array} \quad \Rightarrow \quad \begin{array}{r} 0101 \\ \textcircled{+} 1110 \\ \hline 10011 \\ \uparrow \\ \text{ignore} \end{array}$$

Notice that the minus changes to a plus.

$\Rightarrow$  means take the 2's complement


# Example of 2's complement subtraction

$$\begin{array}{r}
 (+5) \\
 - (+2) \\
 \hline
 (+3)
 \end{array}
 \quad
 \begin{array}{r}
 \underline{0101} \\
 - \underline{0010} \\
 \hline
 \end{array}
 \Rightarrow
 \begin{array}{r}
 \phantom{+} 0101 \\
 + 1110 \\
 \hline
 10011 \\
 \uparrow \\
 \text{ignore}
 \end{array}$$

$b_3b_2b_1b_0$	2's complement
0111	+7
0110	+6
<b>0101</b>	<b>+5</b>
0100	+4
0011	+3
<b>0010</b>	<b>+2</b>
0001	+1
0000	+0
1000	-8
1001	-7
1010	-6
1011	-5
1100	-4
1101	-3
1110	-2
1111	-1

[ Figure 3.10 from the textbook ]

# Example of 2's complement subtraction

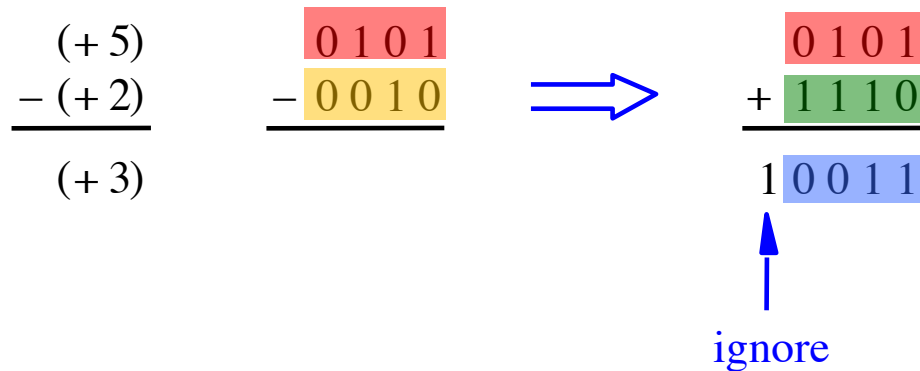


$b_3b_2b_1b_0$	2's complement
0111	+7
0110	+6
0101	+5
0100	+4
0011	+3
0010	+2
0001	+1
0000	+0
1000	-8
1001	-7
1010	-6
1011	-5
1100	-4
1101	-3
1110	-2
1111	-1


[ Figure 3.10 from the textbook ]


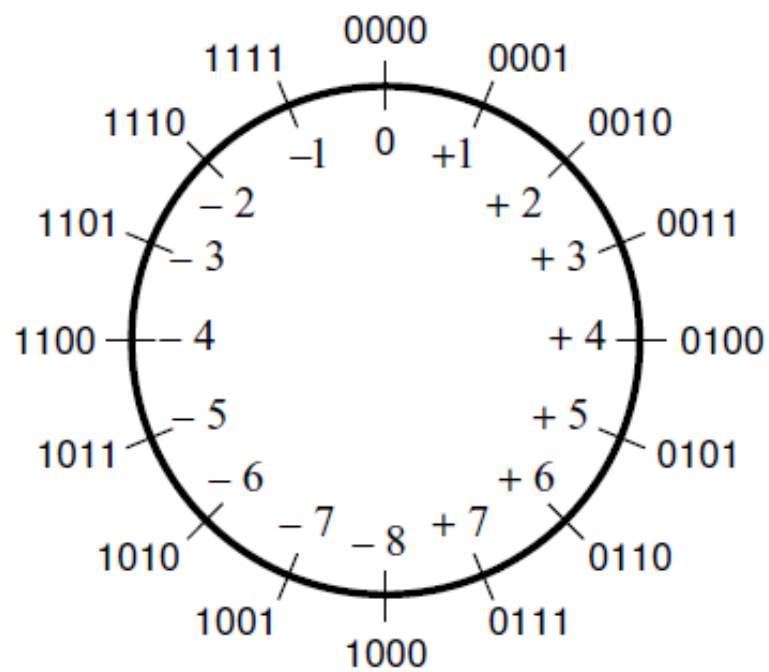
# Graphical interpretation of four-bit 2's complement numbers




(a) The number circle

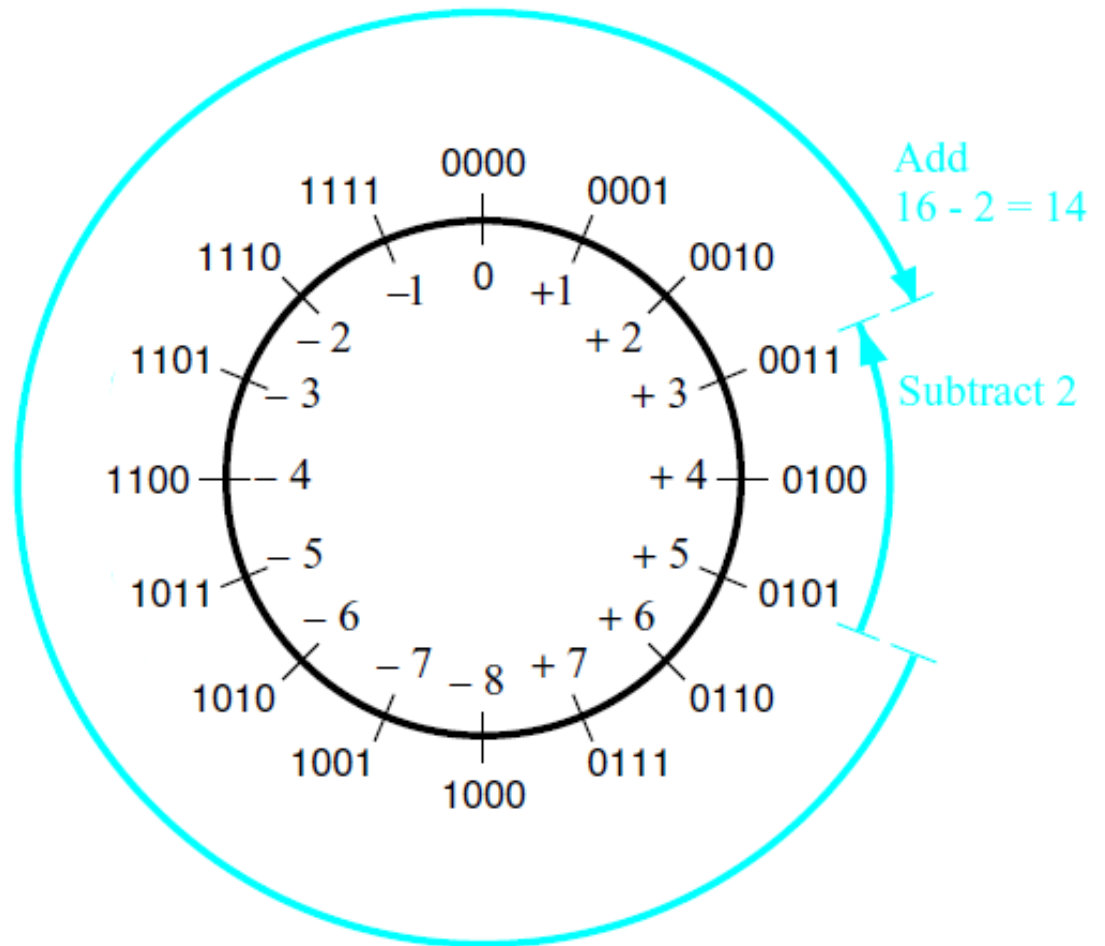

(b) Subtracting 2 by adding its 2's complement

# Example of 2's complement subtraction

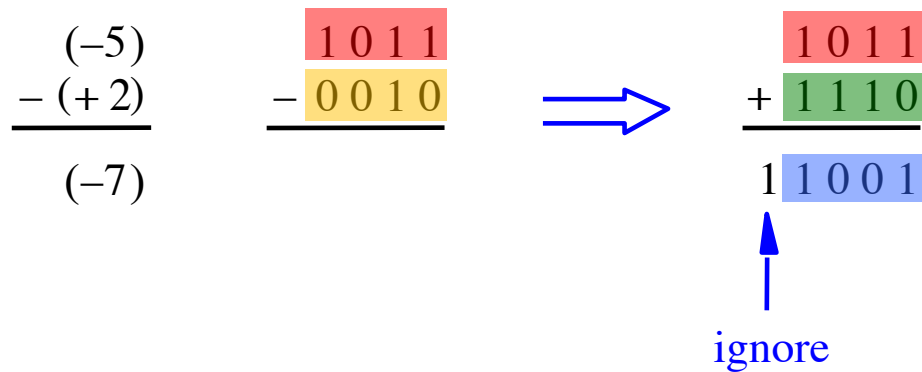

$b_3b_2b_1b_0$	2's complement
0111	+7
0110	+6
0101	+5
0100	+4
0011	+3
0010	+2
0001	+1
0000	+0
1000	-8
1001	-7
1010	-6
1011	-5
1100	-4
1101	-3
1110	-2
1111	-1

[ Figure 3.10 from the textbook ]

# Example of 2's complement subtraction

$$\begin{array}{r}
 (+5) \quad \quad \quad 0101 \\
 - (-2) \quad \quad \quad 1110 \\
 \hline
 (+7)
 \end{array}
 \quad \Rightarrow \quad
 \begin{array}{r}
 \quad \quad \quad 0101 \\
 + \quad \quad \quad 0010 \\
 \hline
 \quad \quad \quad 0111
 \end{array}$$

$b_3b_2b_1b_0$	2's complement
0111	+7
0110	+6
0101	+5
0100	+4
0011	+3
0010	+2
0001	+1
0000	+0
1000	-8
1001	-7
1010	-6
1011	-5
1100	-4
1101	-3
1110	-2
1111	-1

[ Figure 3.10 from the textbook ]

# Example of 2's complement subtraction

$$\begin{array}{r}
 (-5) \\
 - (-2) \\
 \hline
 (-3)
 \end{array}
 \quad
 \begin{array}{r}
 \color{red}{1011} \\
 - \color{yellow}{1110} \\
 \hline
 \end{array}
 \quad
 \Rightarrow
 \quad
 \begin{array}{r}
 \color{red}{1011} \\
 + \color{green}{0010} \\
 \hline
 \color{blue}{1101}
 \end{array}$$


$b_3b_2b_1b_0$	2's complement
0111	+7
0110	+6
0101	+5
0100	+4
0011	+3
0010	+2
0001	+1
0000	+0
1000	-8
1001	-7
1010	-6
1011	-5
1100	-4
1101	-3
1110	-2
1111	-1

[ Figure 3.10 from the textbook ]

# Take Home Message

- **Subtraction can be performed by simply adding the 2's complement of the second number, regardless of the signs of the two numbers.**
- **Thus, the same adder circuit can be used to perform both addition and subtraction !!!**


# Adder/subtractor unit

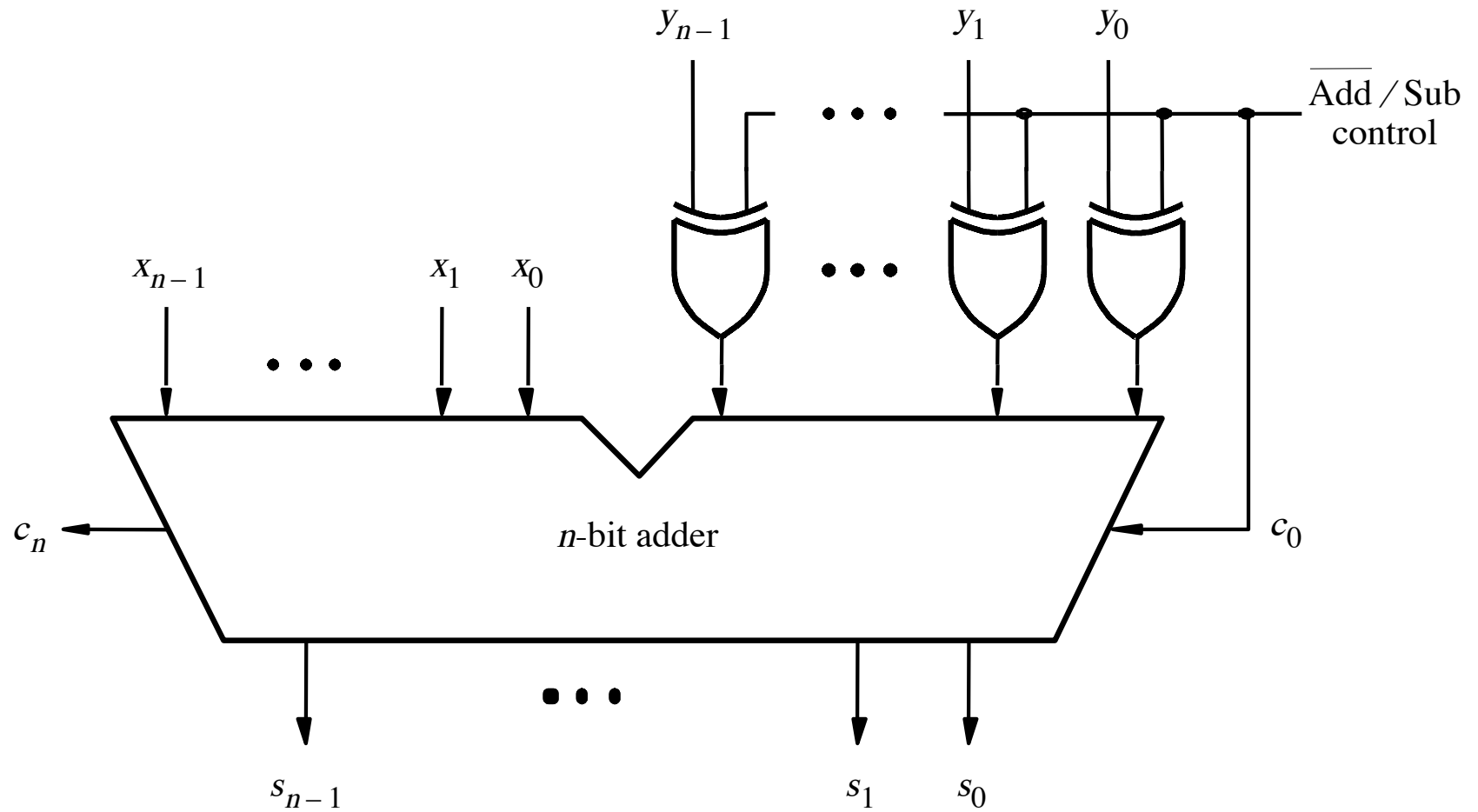

[ Figure 3.12 from the textbook ]



# XOR Tricks

control	$y$	out
0	0	0
0	1	1
1	0	1
1	1	0

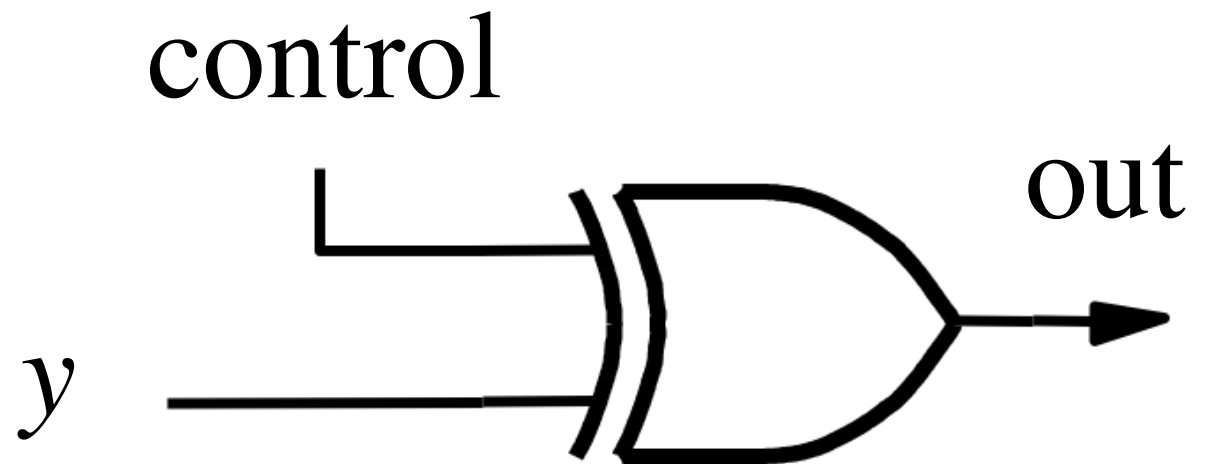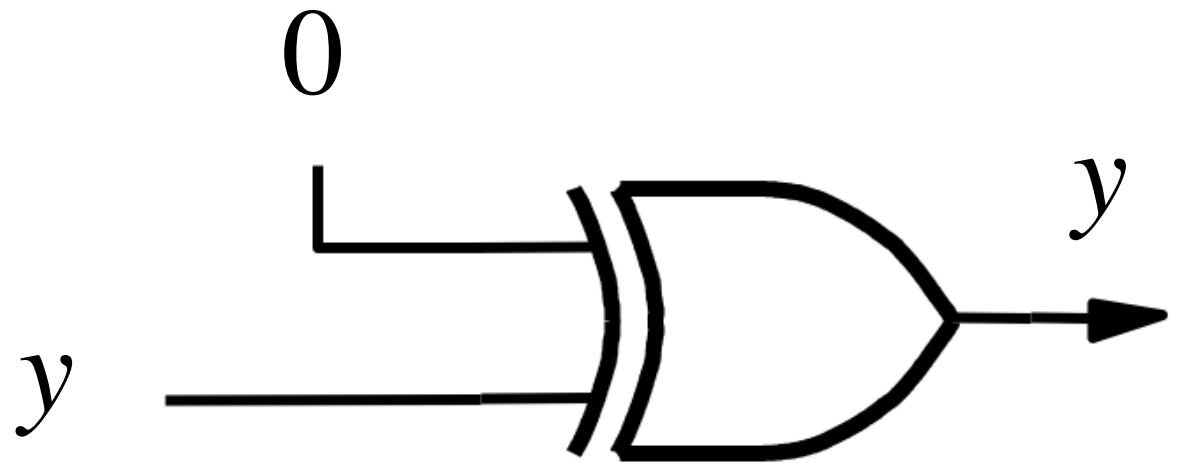

# XOR as a repeater


control	$y$	out
0	0	0
0	1	1






# XOR as an inverter

control	$y$	out
1	0	1
1	1	0

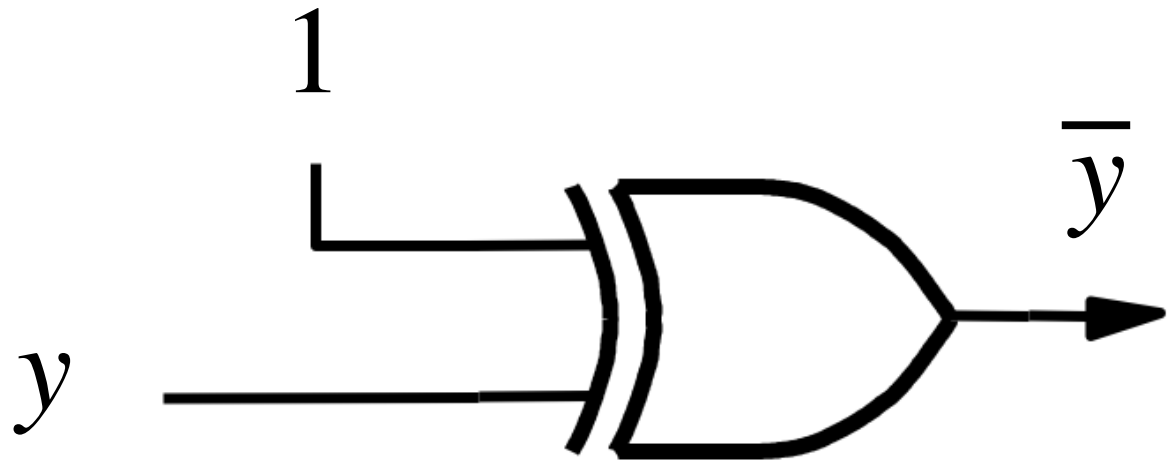


# Addition: when control = 0

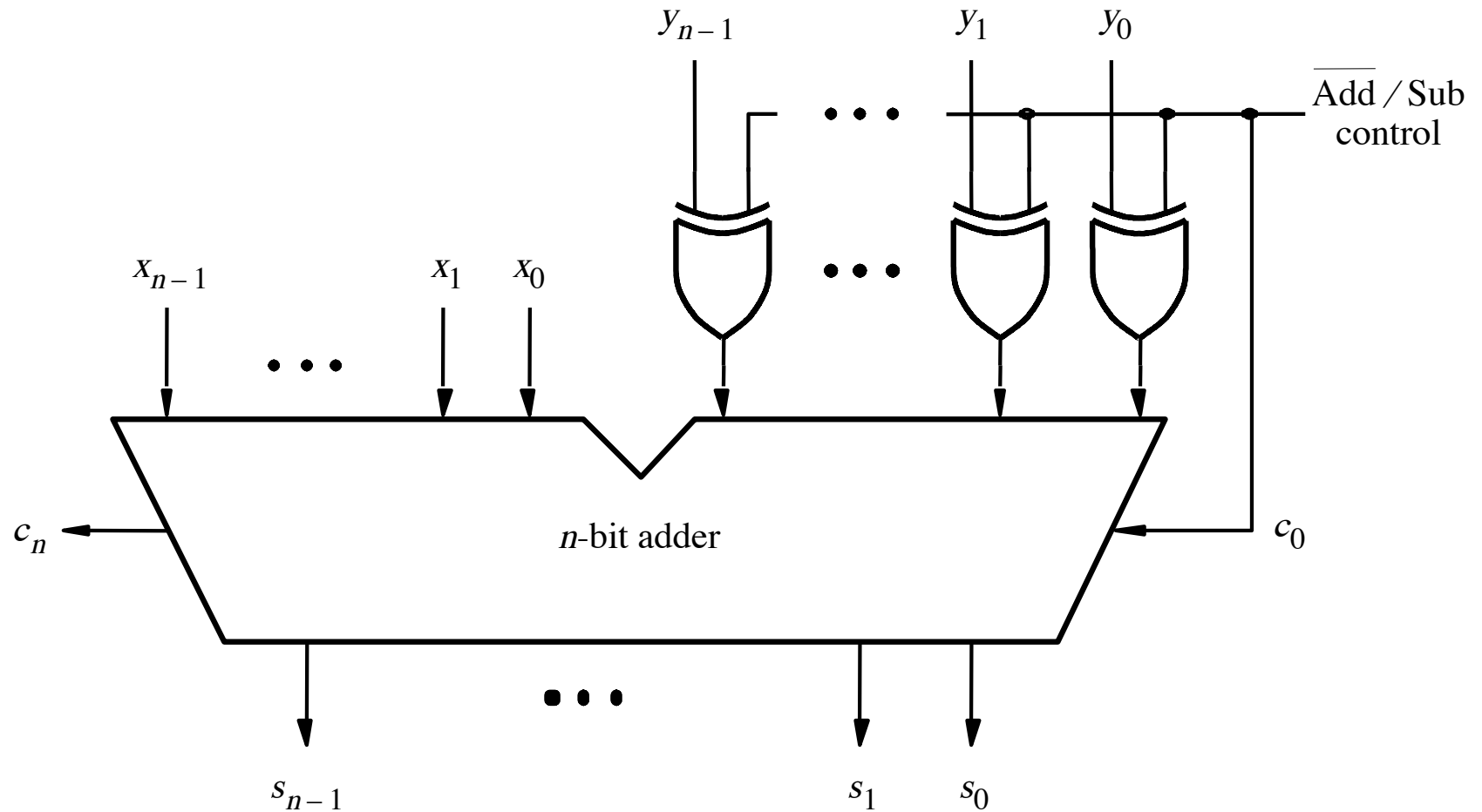


[ Figure 3.12 from the textbook ]

# Addition: when control = 0

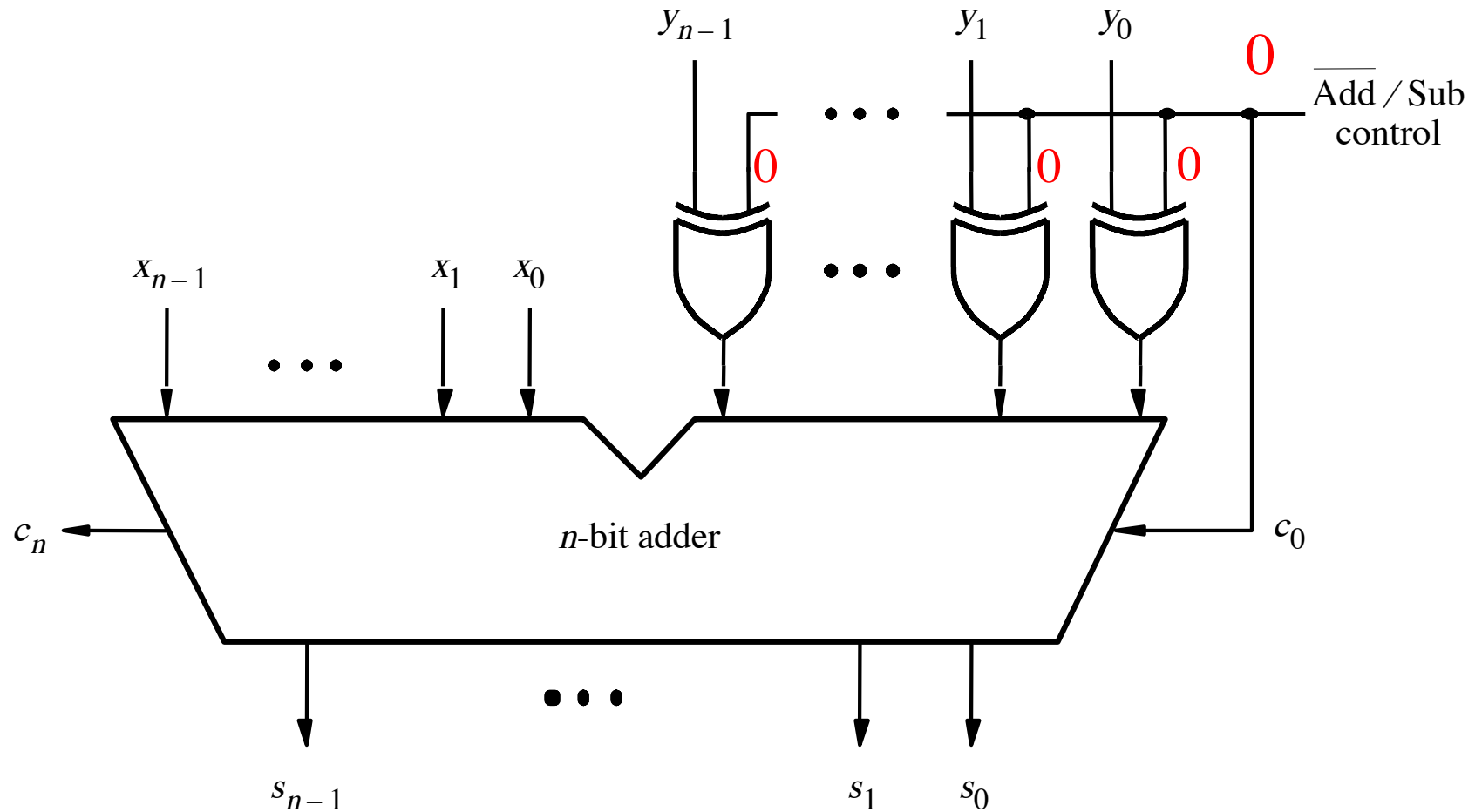


[ Figure 3.12 from the textbook ]

# Addition: when control = 0

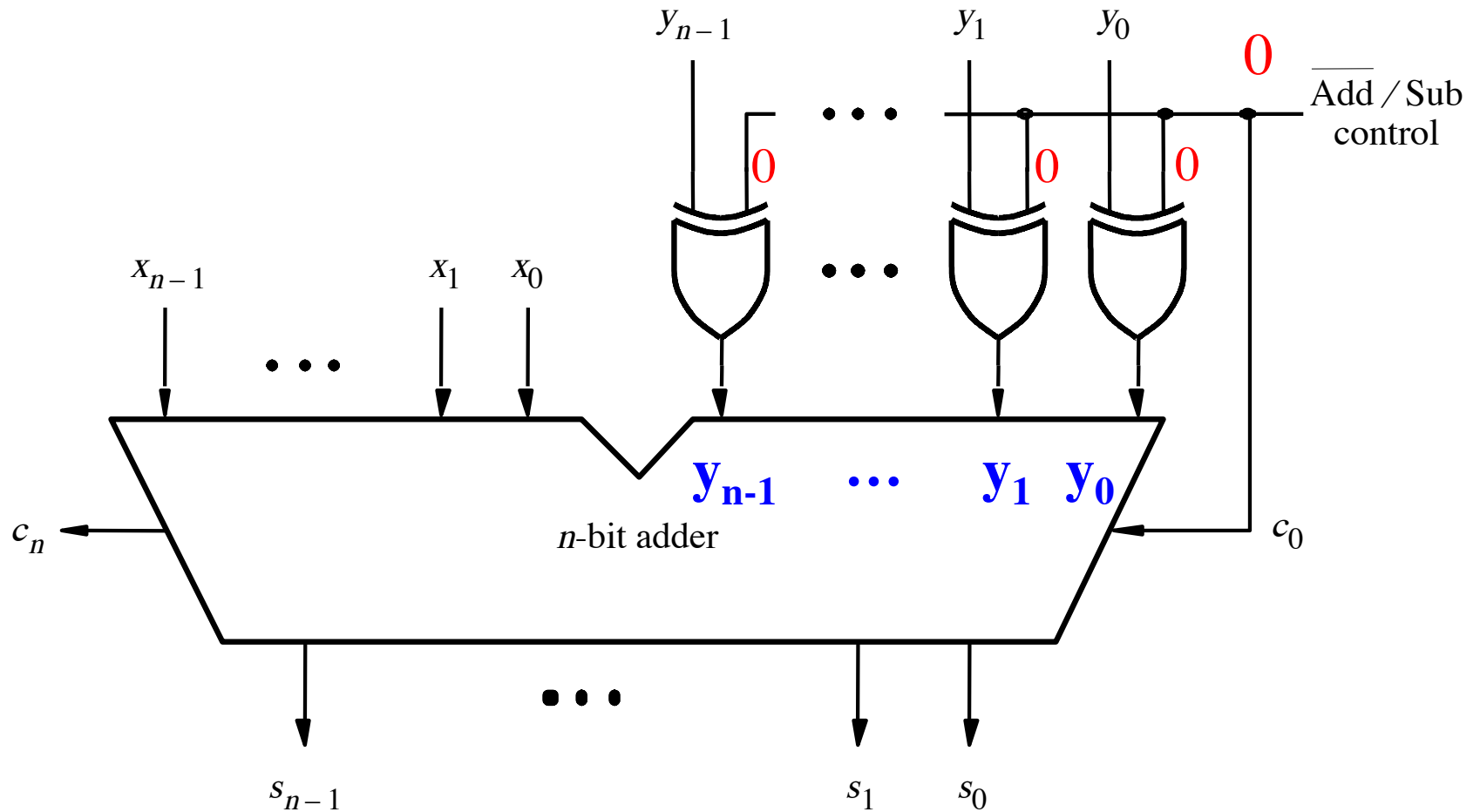


[ Figure 3.12 from the textbook ]

# Subtraction: when control = 1

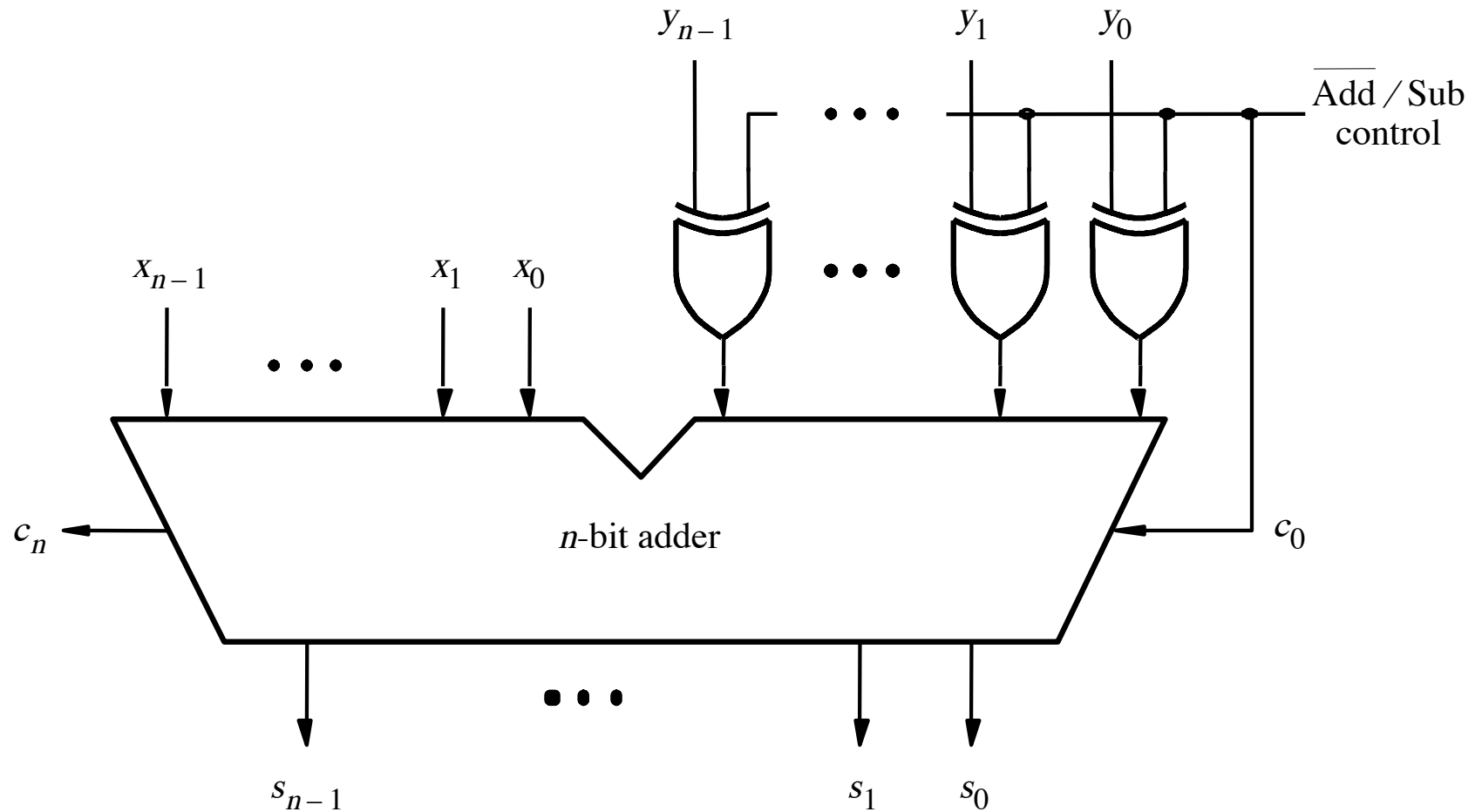


[ Figure 3.12 from the textbook ]

# Subtraction: when control = 1

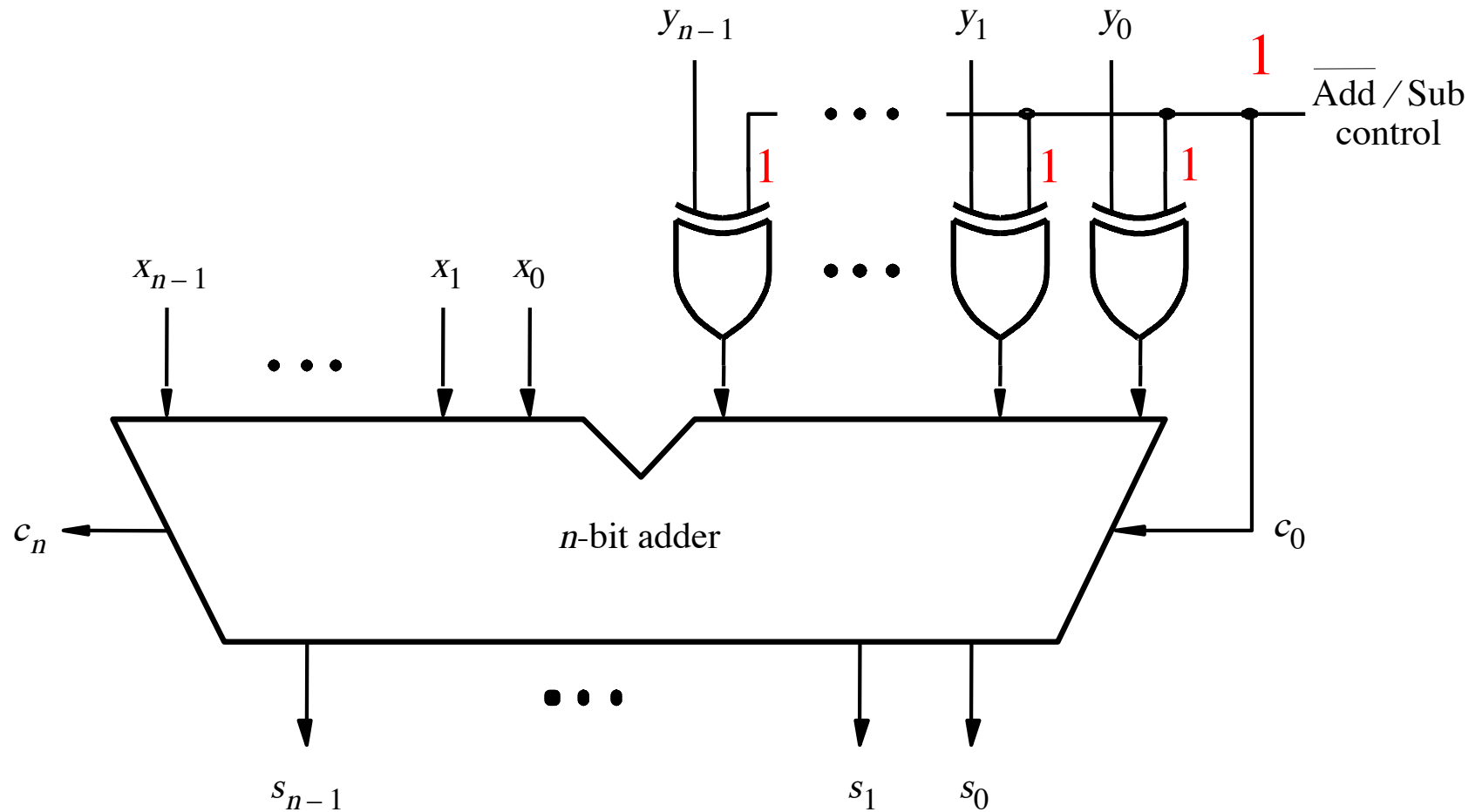


[ Figure 3.12 from the textbook ]

# Subtraction: when control = 1

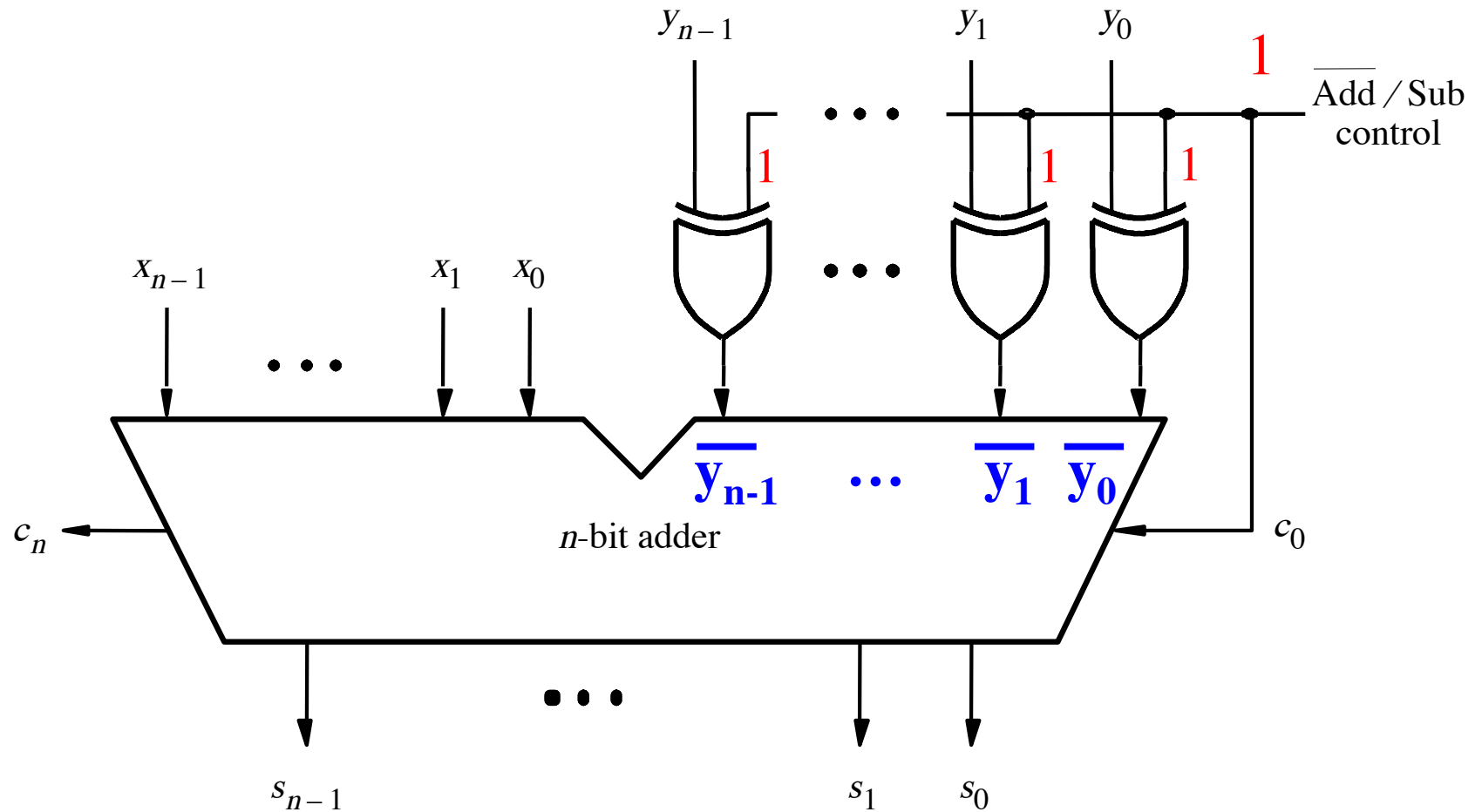

[ Figure 3.12 from the textbook ]

# Subtraction: when control = 1

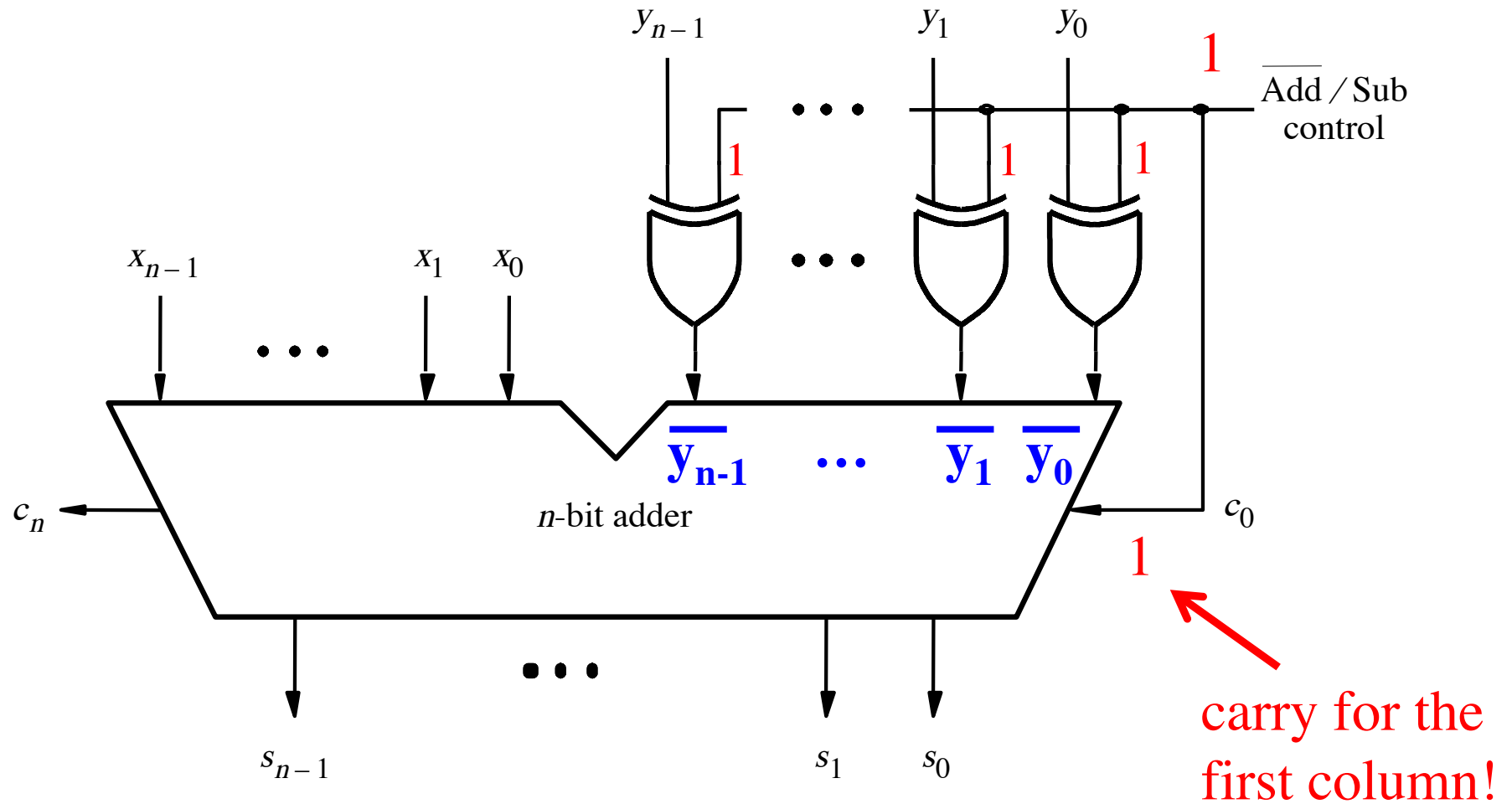

[ Figure 3.12 from the textbook ]



# Examples of determination of overflow

$$\begin{array}{r} (+7) \\ + (+2) \\ \hline (+9) \end{array} \quad + \quad \begin{array}{r} 0111 \\ 0010 \\ \hline 1001 \end{array}$$

$$\begin{array}{r} (-7) \\ + (+2) \\ \hline (-5) \end{array} \quad + \quad \begin{array}{r} 1001 \\ 0010 \\ \hline 1011 \end{array}$$

$$\begin{array}{r} (+7) \\ + (-2) \\ \hline (+5) \end{array} \quad + \quad \begin{array}{r} 0111 \\ 1110 \\ \hline 10101 \end{array}$$

$$\begin{array}{r} (-7) \\ + (-2) \\ \hline (-9) \end{array} \quad + \quad \begin{array}{r} 1001 \\ 1110 \\ \hline 10111 \end{array}$$

# Examples of determination of overflow

$$\begin{array}{r} (+7) \\ + (+2) \\ \hline (+9) \end{array} \quad \begin{array}{r} 01100 \\ + 0111 \\ \hline 0010 \\ + 1001 \end{array}$$

$$\begin{array}{r} (-7) \\ + (+2) \\ \hline (-5) \end{array} \quad \begin{array}{r} 00000 \\ + 1001 \\ \hline 0010 \\ + 1011 \end{array}$$

$$\begin{array}{r} (+7) \\ + (-2) \\ \hline (+5) \end{array} \quad \begin{array}{r} 11100 \\ + 0111 \\ \hline 1110 \\ + 10101 \end{array}$$

$$\begin{array}{r} (-7) \\ + (-2) \\ \hline (-9) \end{array} \quad \begin{array}{r} 10000 \\ + 1001 \\ \hline 1110 \\ + 10111 \end{array}$$

Include the carry bits:  $c_4 c_3 c_2 c_1 c_0$

# Examples of determination of overflow

(+ 7)	+	<span style="border: 1px solid green; padding: 2px;">0 1</span> 1 0 0	(- 7)	+	<span style="border: 1px solid green; padding: 2px;">0 0</span> 0 0 0
+ (+ 2)		0 1 1 1	+ (+ 2)		1 0 0 1
(+ 9)		0 0 1 0	(- 5)		0 0 1 0
		1 0 0 1			1 0 1 1

(+ 7)	+	<span style="border: 1px solid green; padding: 2px;">1 1</span> 1 0 0	(- 7)	+	<span style="border: 1px solid green; padding: 2px;">1 0</span> 0 0 0
+ (- 2)		0 1 1 1	+ (- 2)		1 0 0 1
(+ 5)		1 1 1 0	(- 9)		1 1 1 0
		1 0 1 0 1			1 0 1 1 1

Include the carry bits: c<sub>4</sub> c<sub>3</sub> c<sub>2</sub> c<sub>1</sub> c<sub>0</sub>

# Examples of determination of overflow

$$c_4 = 0$$

$$c_3 = 1$$

$$\begin{array}{r}
 (+7) \\
 + (+2) \\
 \hline
 (+9)
 \end{array}
 \quad
 \begin{array}{r}
 \boxed{01}100 \\
 + \quad 0111 \\
 \hline
 1001
 \end{array}$$

$$\begin{array}{r}
 (-7) \\
 + (+2) \\
 \hline
 (-5)
 \end{array}
 \quad
 \begin{array}{r}
 \boxed{00}000 \\
 + \quad 1001 \\
 \hline
 1011
 \end{array}
 \quad
 \begin{array}{r}
 c_4 = 0 \\
 c_3 = 0
 \end{array}$$

$$c_4 = 1$$

$$c_3 = 1$$

$$\begin{array}{r}
 (+7) \\
 + (-2) \\
 \hline
 (+5)
 \end{array}
 \quad
 \begin{array}{r}
 \boxed{11}100 \\
 + \quad 0111 \\
 \hline
 10101
 \end{array}$$

$$\begin{array}{r}
 (-7) \\
 + (-2) \\
 \hline
 (-9)
 \end{array}
 \quad
 \begin{array}{r}
 \boxed{10}000 \\
 + \quad 1001 \\
 \hline
 10111
 \end{array}
 \quad
 \begin{array}{r}
 c_4 = 1 \\
 c_3 = 0
 \end{array}$$

Include the carry bits:  $\boxed{c_4 c_3} c_2 c_1 c_0$

# Examples of determination of overflow

$$c_4 = 0$$

$$c_3 = 1$$

$$\begin{array}{r} (+7) \\ + (+2) \\ \hline (+9) \end{array}$$

$$\begin{array}{r} \boxed{01}100 \\ + \quad 0111 \\ \hline 0010 \\ \hline 1001 \end{array}$$

$$\begin{array}{r} (-7) \\ + (+2) \\ \hline (-5) \end{array}$$

$$\begin{array}{r} \boxed{00}000 \\ + \quad 1001 \\ \hline 0010 \\ \hline 1011 \end{array}$$

$$c_4 = 0$$

$$c_3 = 0$$

$$c_4 = 1$$

$$c_3 = 1$$

$$\begin{array}{r} (+7) \\ + (-2) \\ \hline (+5) \end{array}$$

$$\begin{array}{r} \boxed{11}100 \\ + \quad 0111 \\ \hline 1110 \\ \hline 10101 \end{array}$$

$$\begin{array}{r} (-7) \\ + (-2) \\ \hline (-9) \end{array}$$

$$\begin{array}{r} \boxed{10}000 \\ + \quad 1001 \\ \hline 1110 \\ \hline 10111 \end{array}$$

$$c_4 = 1$$

$$c_3 = 0$$

Overflow occurs only in these two cases.

# Examples of determination of overflow

$$c_4 = 0$$

$$c_3 = 1$$

$$\begin{array}{r} (+7) \\ + (+2) \\ \hline (+9) \end{array}$$

$$\begin{array}{r} \boxed{01}100 \\ + \quad 0111 \\ \hline 0010 \\ + \quad 0010 \\ \hline 1001 \end{array}$$

$$\begin{array}{r} (-7) \\ + (+2) \\ \hline (-5) \end{array}$$

$$\begin{array}{r} \boxed{00}000 \\ + \quad 1001 \\ \hline 0010 \\ + \quad 0010 \\ \hline 1011 \end{array}$$

$$c_4 = 0$$

$$c_3 = 0$$

$$c_4 = 1$$

$$c_3 = 1$$

$$\begin{array}{r} (+7) \\ + (-2) \\ \hline (+5) \end{array}$$

$$\begin{array}{r} \boxed{11}100 \\ + \quad 0111 \\ \hline 1110 \\ + \quad 1110 \\ \hline 10101 \end{array}$$

$$\begin{array}{r} (-7) \\ + (-2) \\ \hline (-9) \end{array}$$

$$\begin{array}{r} \boxed{10}000 \\ + \quad 1001 \\ \hline 1110 \\ + \quad 1110 \\ \hline 10111 \end{array}$$

$$c_4 = 1$$

$$c_3 = 0$$

$$\text{Overflow} = c_3 \bar{c}_4 + \bar{c}_3 c_4$$

# Examples of determination of overflow

$$c_4 = 0$$

$$c_3 = 1$$

$$\begin{array}{r} (+7) \\ + (+2) \\ \hline (+9) \end{array}$$

$$\begin{array}{r} \boxed{01}100 \\ + \quad 0111 \\ \hline 0010 \\ + \quad 0010 \\ \hline 1001 \end{array}$$

$$\begin{array}{r} (-7) \\ + (+2) \\ \hline (-5) \end{array}$$

$$\begin{array}{r} \boxed{00}000 \\ + \quad 1001 \\ \hline 0010 \\ + \quad 0010 \\ \hline 1011 \end{array}$$

$$c_4 = 0$$

$$c_3 = 0$$

$$c_4 = 1$$

$$c_3 = 1$$

$$\begin{array}{r} (+7) \\ + (-2) \\ \hline (+5) \end{array}$$

$$\begin{array}{r} \boxed{11}100 \\ + \quad 0111 \\ \hline 1110 \\ + \quad 1110 \\ \hline 10101 \end{array}$$

$$\begin{array}{r} (-7) \\ + (-2) \\ \hline (-9) \end{array}$$

$$\begin{array}{r} \boxed{10}000 \\ + \quad 1001 \\ \hline 1110 \\ + \quad 1110 \\ \hline 10111 \end{array}$$

$$c_4 = 1$$

$$c_3 = 0$$

$$\text{Overflow} = \underbrace{c_3 \bar{c}_4 + \bar{c}_3 c_4}_{\text{XOR}}$$

# Calculating overflow for 4-bit numbers with only three significant bits


$$\begin{aligned}\text{Overflow} &= c_3 \bar{c}_4 + \bar{c}_3 c_4 \\ &= c_3 \oplus c_4\end{aligned}$$




# Calculating overflow for n-bit numbers with only n-1 significant bits

$$\text{Overflow} = c_{n-1} \oplus c_n$$

# Detecting Overflow

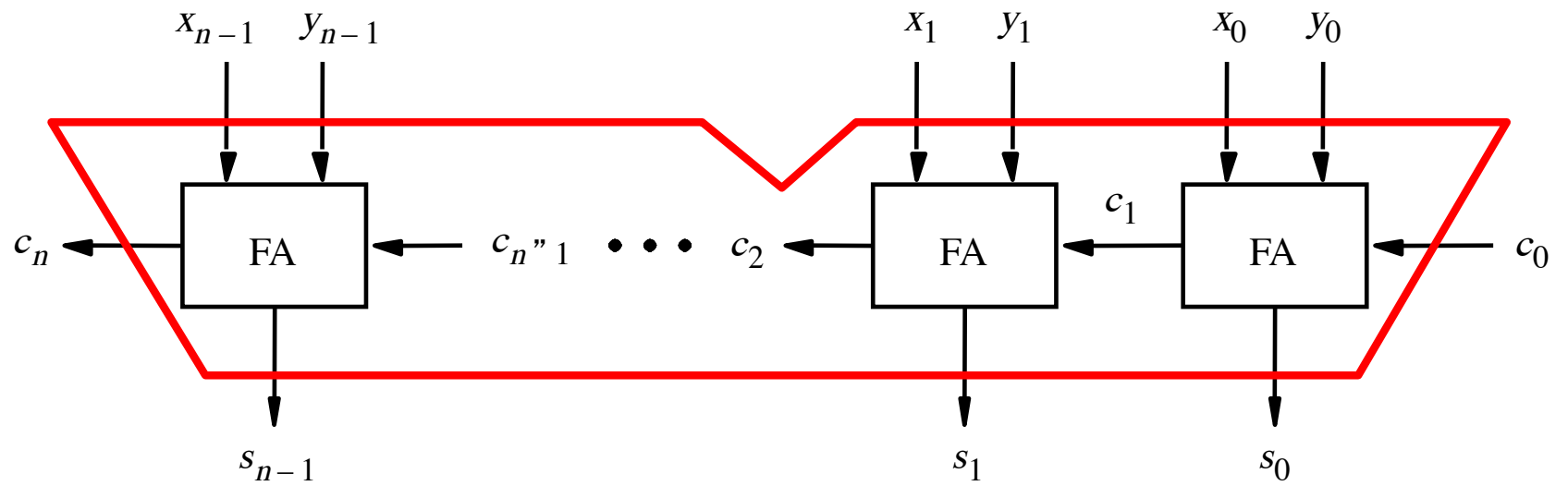
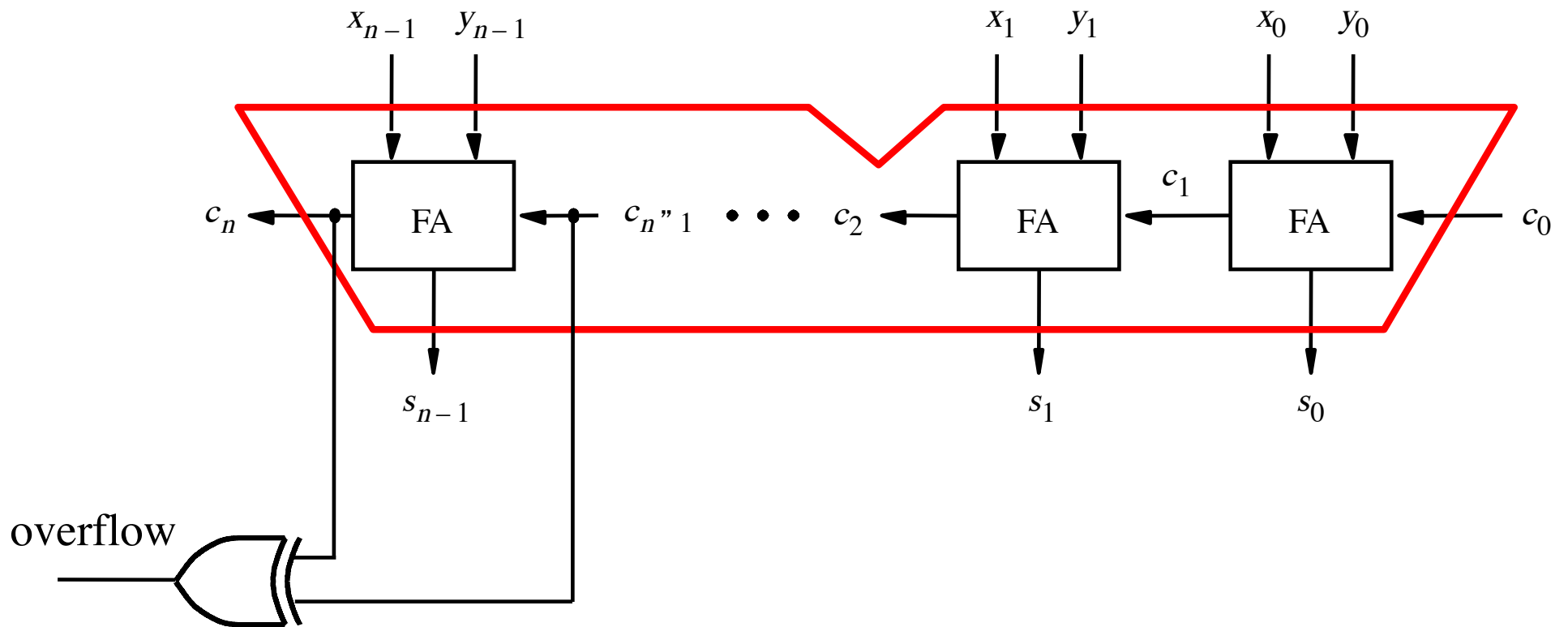
# Detecting Overflow (with one extra XOR)



# Another way to look at the overflow issue

$$\begin{array}{r} + \\ X = x_3 \ x_2 \ x_1 \ x_0 \\ Y = y_3 \ y_2 \ y_1 \ y_0 \end{array}$$

---

$$S = s_3 \ s_2 \ s_1 \ s_0$$

# Another way to look at the overflow issue

$$\begin{array}{rcccc} + & X = & x_3 & x_2 & x_1 & x_0 \\ & Y = & y_3 & y_2 & y_1 & y_0 \\ \hline & S = & s_3 & s_2 & s_1 & s_0 \end{array}$$

If both numbers that we are adding have the same sign but the sum does not, then we have an overflow.

# Examples of determination of overflow

$$\begin{array}{r} (+7) \\ + (+2) \\ \hline (+9) \end{array} \quad + \quad \begin{array}{r} 0111 \\ 0010 \\ \hline 1001 \end{array}$$

$$\begin{array}{r} (-7) \\ + (+2) \\ \hline (-5) \end{array} \quad + \quad \begin{array}{r} 1001 \\ 0010 \\ \hline 1011 \end{array}$$

$$\begin{array}{r} (+7) \\ + (-2) \\ \hline (+5) \end{array} \quad + \quad \begin{array}{r} 0111 \\ 1110 \\ \hline 10101 \end{array}$$

$$\begin{array}{r} (-7) \\ + (-2) \\ \hline (-9) \end{array} \quad + \quad \begin{array}{r} 1001 \\ 1110 \\ \hline 10111 \end{array}$$

# Examples of determination of overflow

$$\begin{array}{r} (+7) \\ + (+2) \\ \hline (+9) \end{array} \quad + \quad \begin{array}{r} \boxed{0}111 \\ 0010 \\ \hline \boxed{1}001 \end{array}$$

$$\begin{array}{r} (-7) \\ + (+2) \\ \hline (-5) \end{array} \quad + \quad \begin{array}{r} \boxed{1}001 \\ 0010 \\ \hline \boxed{1}011 \end{array}$$

$$\begin{array}{r} (+7) \\ + (-2) \\ \hline (+5) \end{array} \quad + \quad \begin{array}{r} \boxed{0}111 \\ 1110 \\ \hline 1\boxed{0}101 \end{array}$$

$$\begin{array}{r} (-7) \\ + (-2) \\ \hline (-9) \end{array} \quad + \quad \begin{array}{r} \boxed{1}001 \\ 1110 \\ \hline 1\boxed{0}111 \end{array}$$

# Examples of determination of overflow

$$\begin{aligned} x_3 &= 0 \\ y_3 &= 0 \\ s_3 &= 1 \end{aligned}$$

$$\begin{array}{r} (+7) \\ + (+2) \\ \hline (+9) \end{array} \quad + \quad \begin{array}{r} \boxed{0}111 \\ 0010 \\ \hline \boxed{1}001 \end{array}$$

$$\begin{array}{r} (-7) \\ + (+2) \\ \hline (-5) \end{array}$$

$$\begin{array}{r} \boxed{1}001 \\ 0010 \\ \hline \boxed{1}011 \end{array}$$

$$\begin{aligned} x_3 &= 1 \\ y_3 &= 0 \\ s_3 &= 1 \end{aligned}$$

$$\begin{aligned} x_3 &= 0 \\ y_3 &= 1 \\ s_3 &= 0 \end{aligned}$$

$$\begin{array}{r} (+7) \\ + (-2) \\ \hline (+5) \end{array} \quad + \quad \begin{array}{r} \boxed{0}111 \\ 1110 \\ \hline \boxed{1}0101 \end{array}$$

$$\begin{array}{r} (-7) \\ + (-2) \\ \hline (-9) \end{array}$$

$$\begin{array}{r} \boxed{1}001 \\ 1110 \\ \hline \boxed{1}0111 \end{array}$$

$$\begin{aligned} x_3 &= 1 \\ y_3 &= 1 \\ s_3 &= 0 \end{aligned}$$



# Examples of determination of overflow

$$\begin{aligned} x_3 &= 0 \\ y_3 &= 0 \\ s_3 &= 1 \end{aligned}$$

$$\begin{array}{r} (+7) \\ + (+2) \\ \hline (+9) \end{array} \quad + \quad \begin{array}{r} \boxed{0}111 \\ \boxed{0}010 \\ \hline \boxed{1}001 \end{array}$$

$$\begin{array}{r} (-7) \\ + (+2) \\ \hline (-5) \end{array}$$

$$\begin{array}{r} \boxed{1}001 \\ \boxed{0}010 \\ \hline \boxed{1}011 \end{array}$$

$$\begin{aligned} x_3 &= 1 \\ y_3 &= 0 \\ s_3 &= 1 \end{aligned}$$

$$\begin{aligned} x_3 &= 0 \\ y_3 &= 1 \\ s_3 &= 0 \end{aligned}$$

$$\begin{array}{r} (+7) \\ + (-2) \\ \hline (+5) \end{array} \quad + \quad \begin{array}{r} \boxed{0}111 \\ \boxed{1}110 \\ \hline \boxed{1}0101 \end{array}$$

$$\begin{array}{r} (-7) \\ + (-2) \\ \hline (-9) \end{array}$$

$$\begin{array}{r} \boxed{1}001 \\ \boxed{1}110 \\ \hline \boxed{1}0111 \end{array}$$

$$\begin{aligned} x_3 &= 1 \\ y_3 &= 1 \\ s_3 &= 0 \end{aligned}$$

In 2's complement, both +9 and -9 are not representable with 4 bits.

# Examples of determination of overflow

$$\begin{array}{l} x_3 = 0 \\ y_3 = 0 \\ s_3 = 1 \end{array}$$

$$\begin{array}{r} (+7) \\ + (+2) \\ \hline (+9) \end{array}$$

$$+ \begin{array}{r} 0111 \\ 0010 \\ \hline 1001 \end{array}$$

$$\begin{array}{r} (-7) \\ + (+2) \\ \hline (-5) \end{array}$$

$$+ \begin{array}{r} 1001 \\ 0010 \\ \hline 1011 \end{array}$$

$$\begin{array}{l} x_3 = 1 \\ y_3 = 0 \\ s_3 = 1 \end{array}$$

$$\begin{array}{l} x_3 = 0 \\ y_3 = 1 \\ s_3 = 0 \end{array}$$

$$\begin{array}{r} (+7) \\ + (-2) \\ \hline (+5) \end{array}$$

$$+ \begin{array}{r} 0111 \\ 1110 \\ \hline 10101 \end{array}$$

$$\begin{array}{r} (-7) \\ + (-2) \\ \hline (-9) \end{array}$$

$$+ \begin{array}{r} 1001 \\ 1110 \\ \hline 10111 \end{array}$$

$$\begin{array}{l} x_3 = 1 \\ y_3 = 1 \\ s_3 = 0 \end{array}$$

Overflow occurs only in these two cases.

# Examples of determination of overflow

$$\begin{aligned} x_3 &= 0 \\ y_3 &= 0 \\ s_3 &= 1 \end{aligned}$$

$$\begin{array}{r} (+7) \\ + (+2) \\ \hline (+9) \end{array}$$

$$+ \begin{array}{r} 0111 \\ 0010 \\ \hline 1001 \end{array}$$

$$\begin{array}{r} (-7) \\ + (+2) \\ \hline (-5) \end{array}$$

$$+ \begin{array}{r} 1001 \\ 0010 \\ \hline 1011 \end{array}$$

$$\begin{aligned} x_3 &= 1 \\ y_3 &= 0 \\ s_3 &= 1 \end{aligned}$$

$$\begin{aligned} x_3 &= 0 \\ y_3 &= 1 \\ s_3 &= 0 \end{aligned}$$

$$\begin{array}{r} (+7) \\ + (-2) \\ \hline (+5) \end{array}$$

$$+ \begin{array}{r} 0111 \\ 1110 \\ \hline 10101 \end{array}$$

$$\begin{array}{r} (-7) \\ + (-2) \\ \hline (-9) \end{array}$$

$$+ \begin{array}{r} 1001 \\ 1110 \\ \hline 10111 \end{array}$$

$$\begin{aligned} x_3 &= 1 \\ y_3 &= 1 \\ s_3 &= 0 \end{aligned}$$

$$\text{Overflow} = \bar{x}_3 \bar{y}_3 s_3 + x_3 y_3 \bar{s}_3$$

# Another way to look at the overflow issue


$$\begin{array}{rcccc} + & X = & x_3 & x_2 & x_1 & x_0 \\ & Y = & y_3 & y_2 & y_1 & y_0 \\ \hline & S = & s_3 & s_2 & s_1 & s_0 \end{array}$$

If both numbers that we are adding have the same sign but the sum does not, then we have an overflow.

$$\text{Overflow} = \bar{x}_3 \bar{y}_3 s_3 + x_3 y_3 \bar{s}_3$$



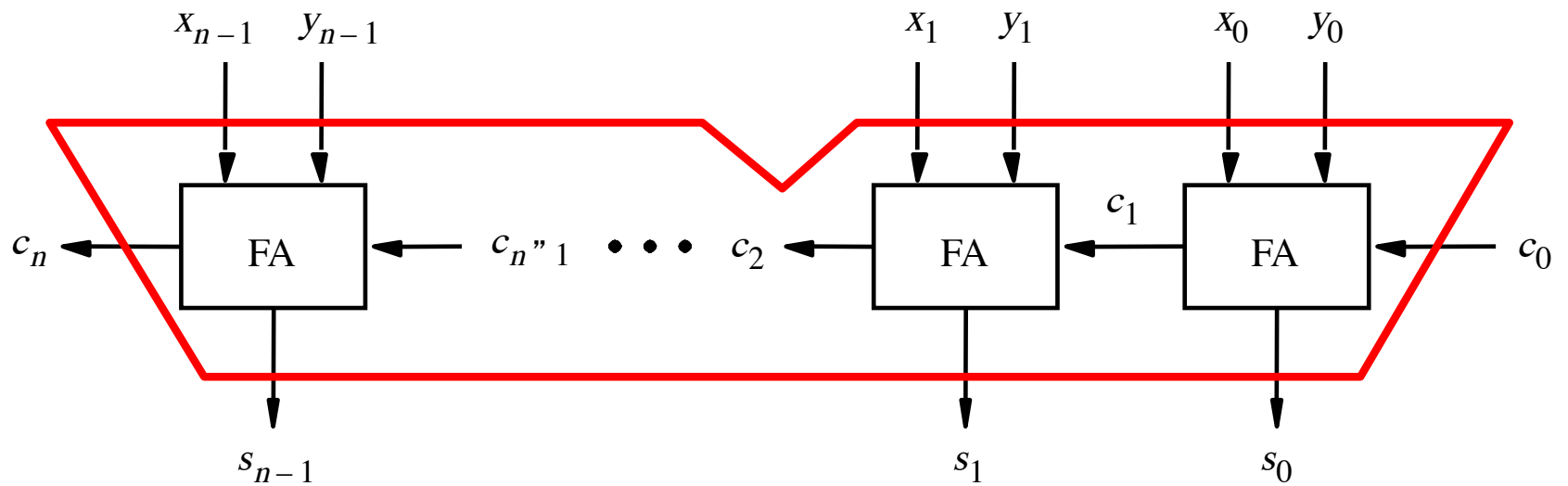
# How long does it take to compute all sum bits and all carry bits?



# **Can we perform addition even faster?**

**The goal is to evaluate very fast if the carry from the previous stage will be equal to 0 or 1.**


# The Full-Adder Circuit

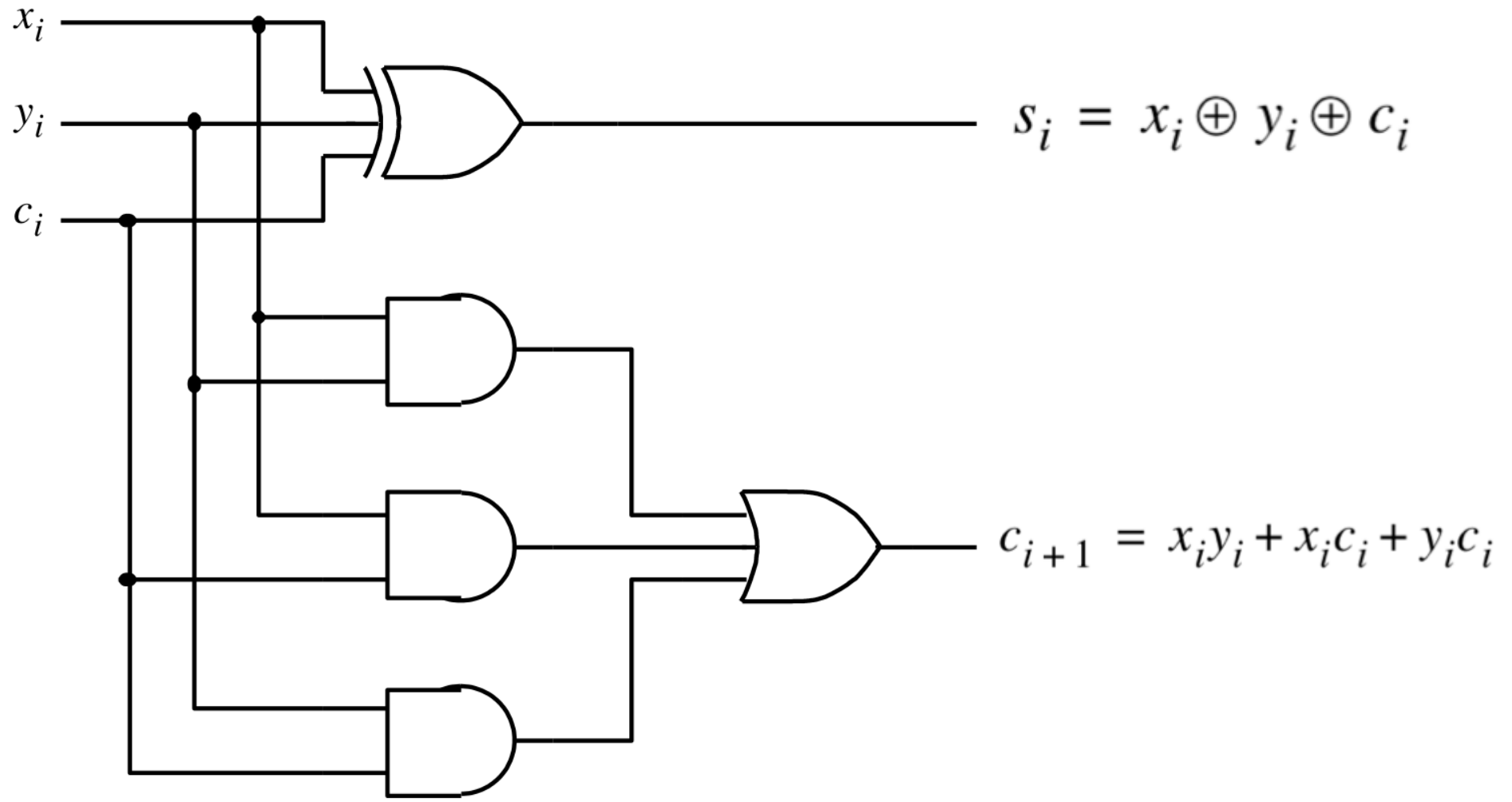

[ Figure 3.3c from the textbook ]



# The Full-Adder Circuit

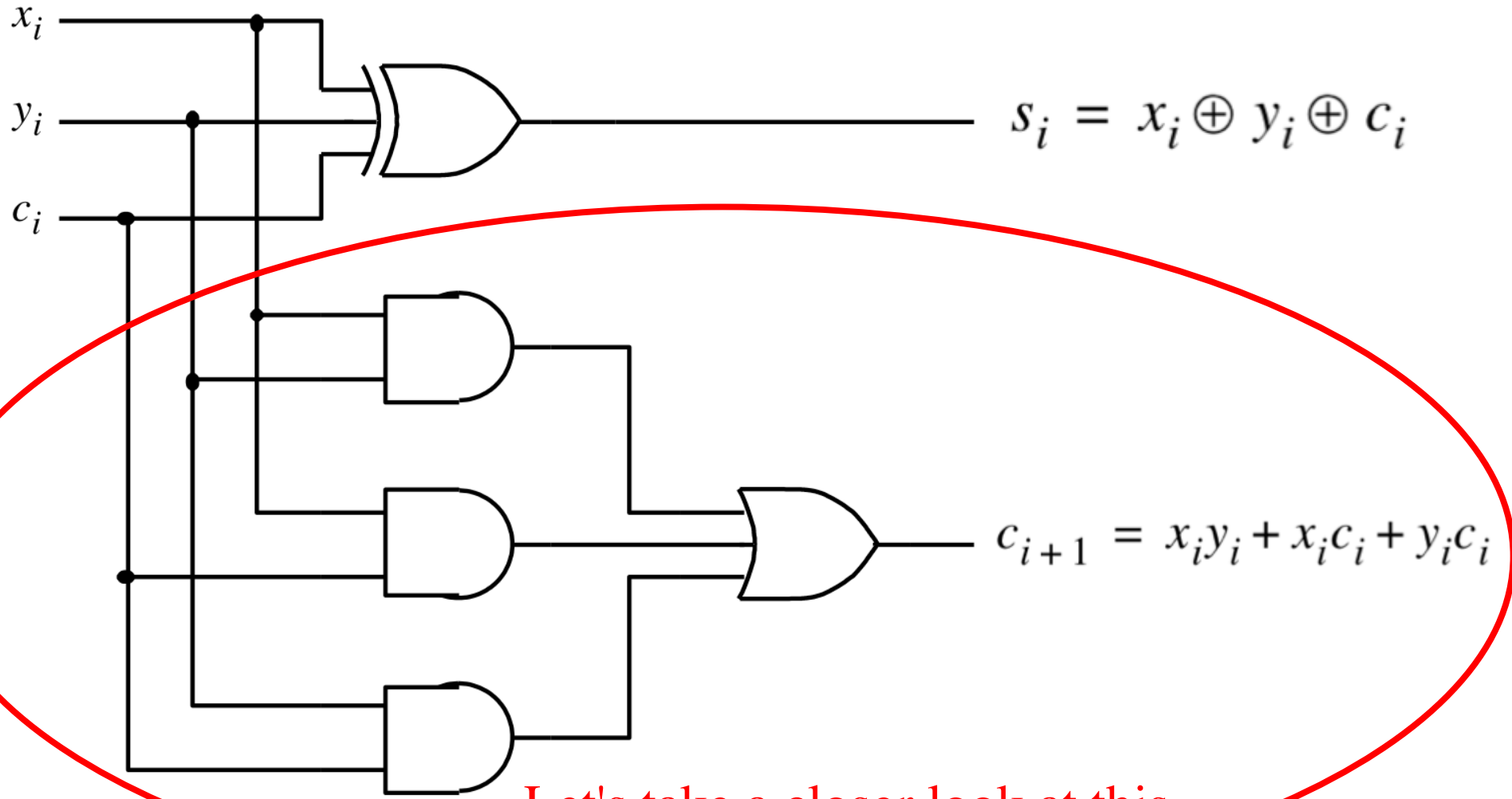

Let's take a closer look at this.

# Decomposing the Carry Expression

$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

# Decomposing the Carry Expression


$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

$$c_{i+1} = x_i y_i + (x_i + y_i) c_i$$

# Decomposing the Carry Expression

$$C_{i+1} = x_i y_i + x_i c_i + y_i c_i$$


$$C_{i+1} = x_i y_i + (x_i + y_i) c_i$$

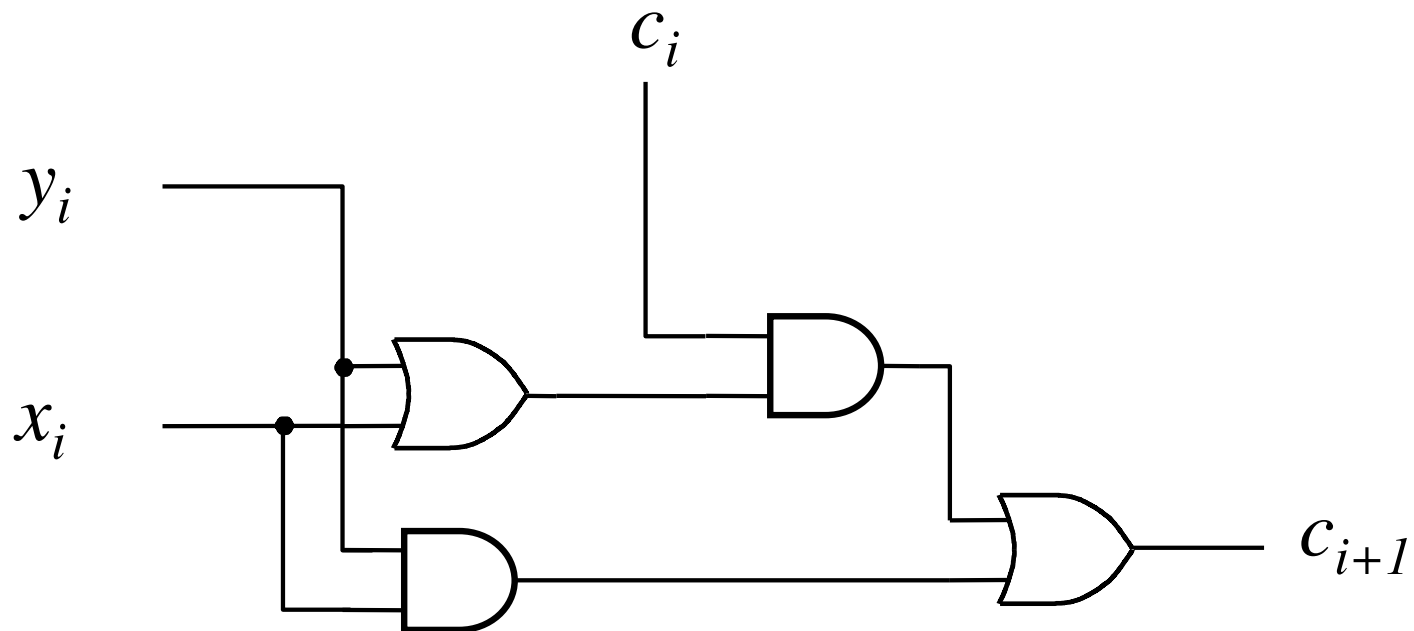

# Another Way to Draw the Full-Adder Circuit


$$C_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

$$C_{i+1} = x_i y_i + (x_i + y_i) c_i$$

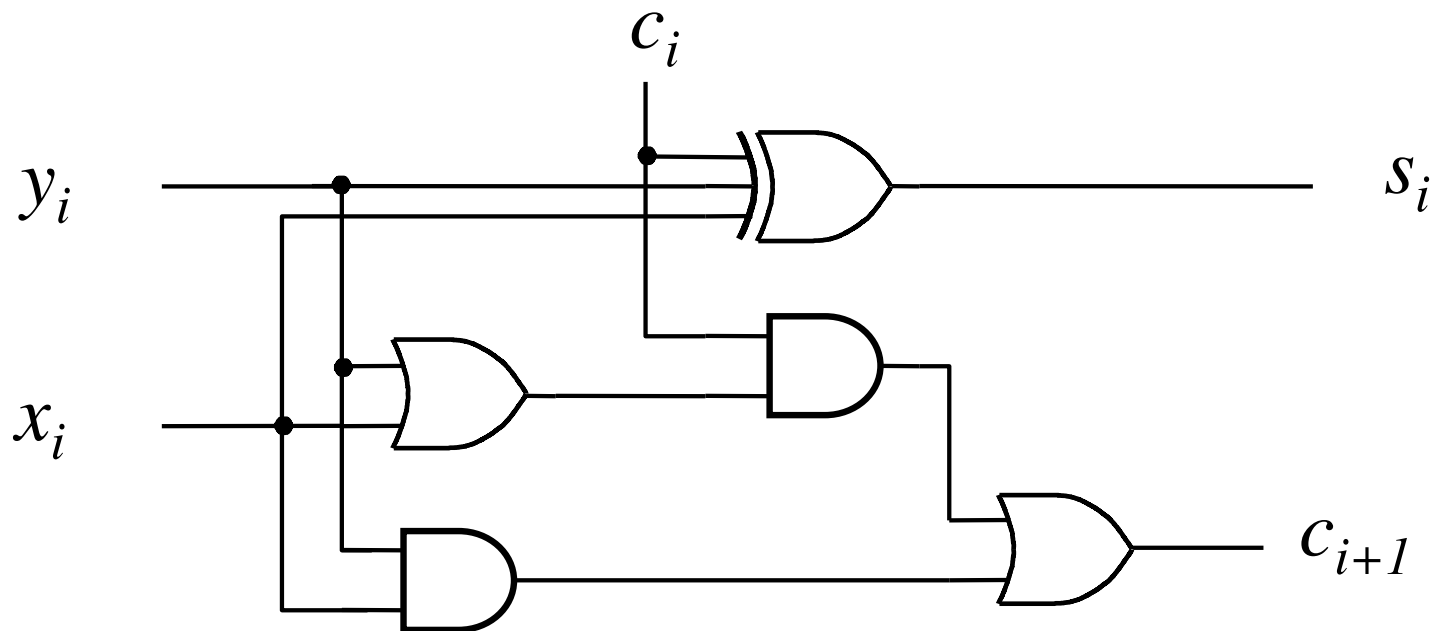


# Another Way to Draw the Full-Adder Circuit

$$C_{i+1} = x_i y_i + (x_i + y_i)c_i$$

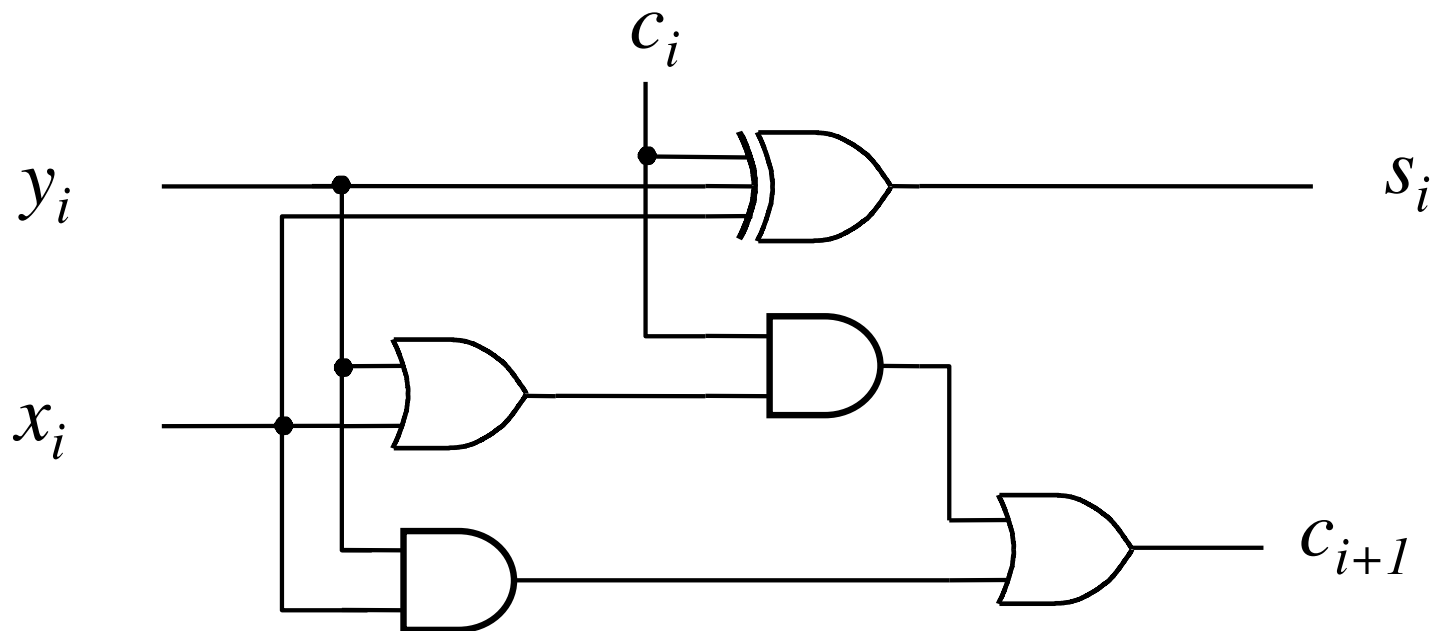
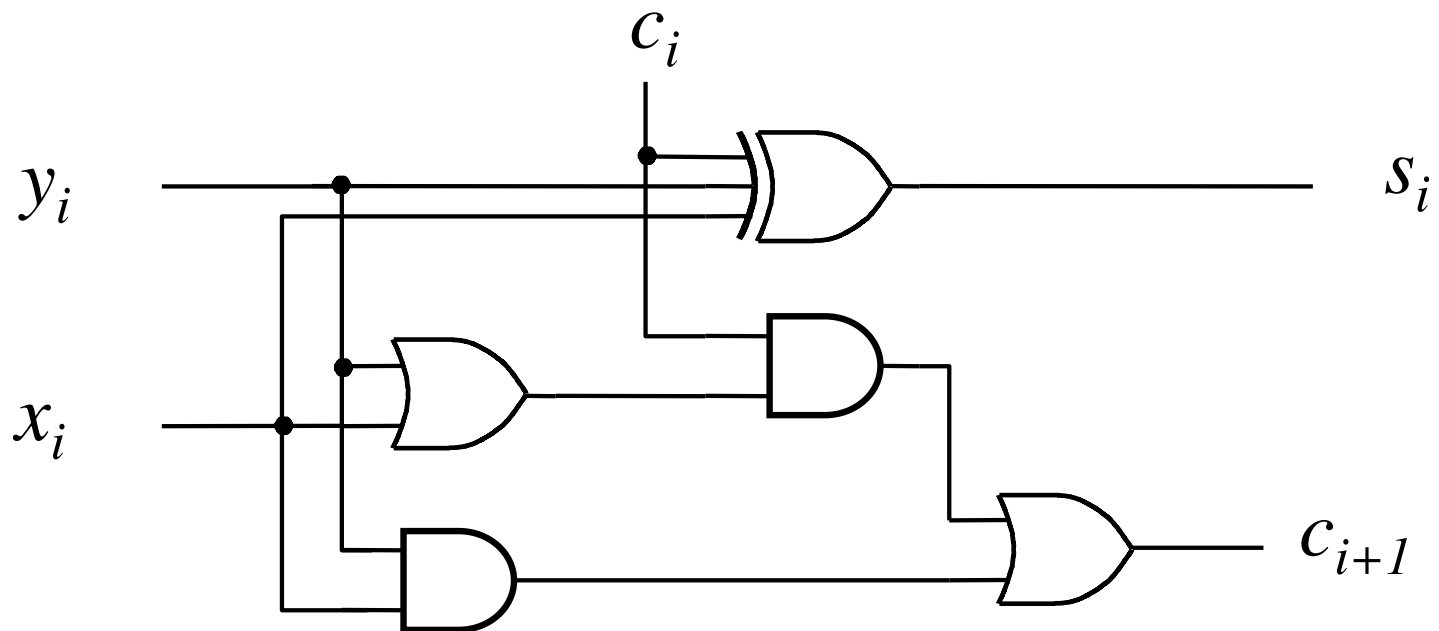
# Another Way to Draw the Full-Adder Circuit

$$C_{i+1} = \underbrace{x_i y_i}_{g_i} + \underbrace{(x_i + y_i)}_{p_i} c_i$$




# Another Way to Draw the Full-Adder Circuit

g - generate


p - propagate
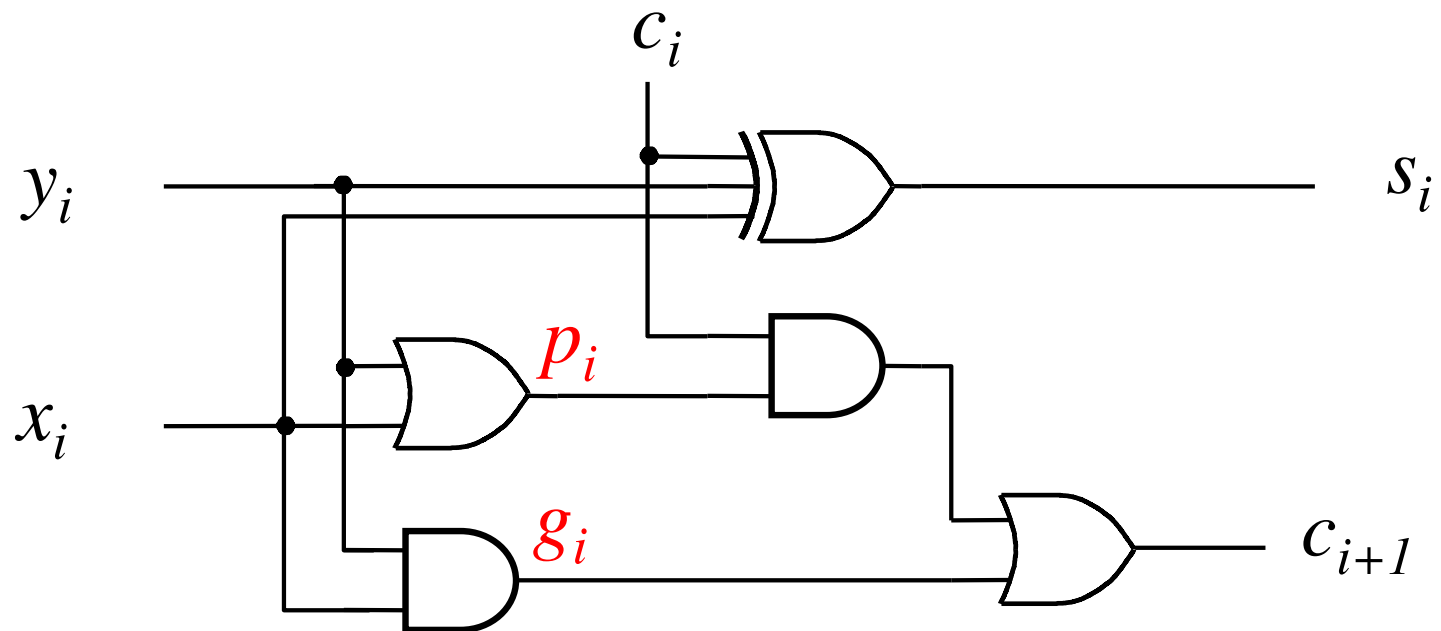
$$C_{i+1} = \underbrace{x_i y_i}_{g_i} + \underbrace{(x_i + y_i)}_{p_i} C_i$$





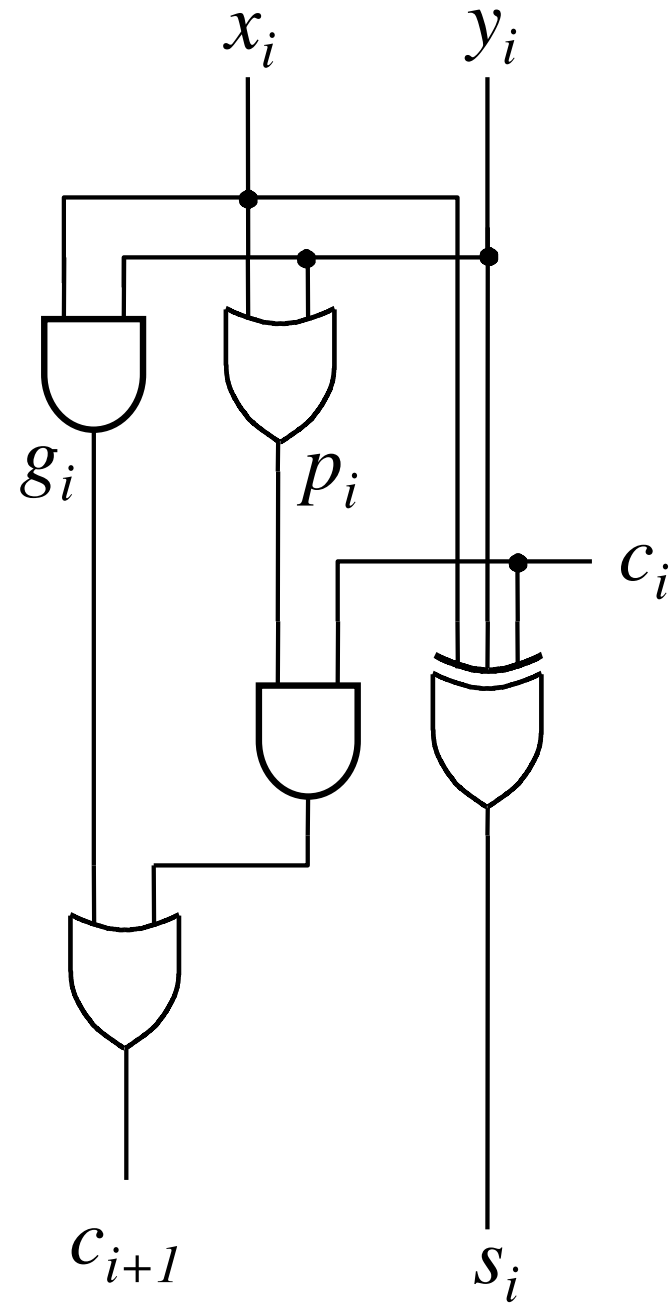
# Yet Another Way to Draw It (Just Rotate It)



# Now we can Build a Ripple-Carry Adder

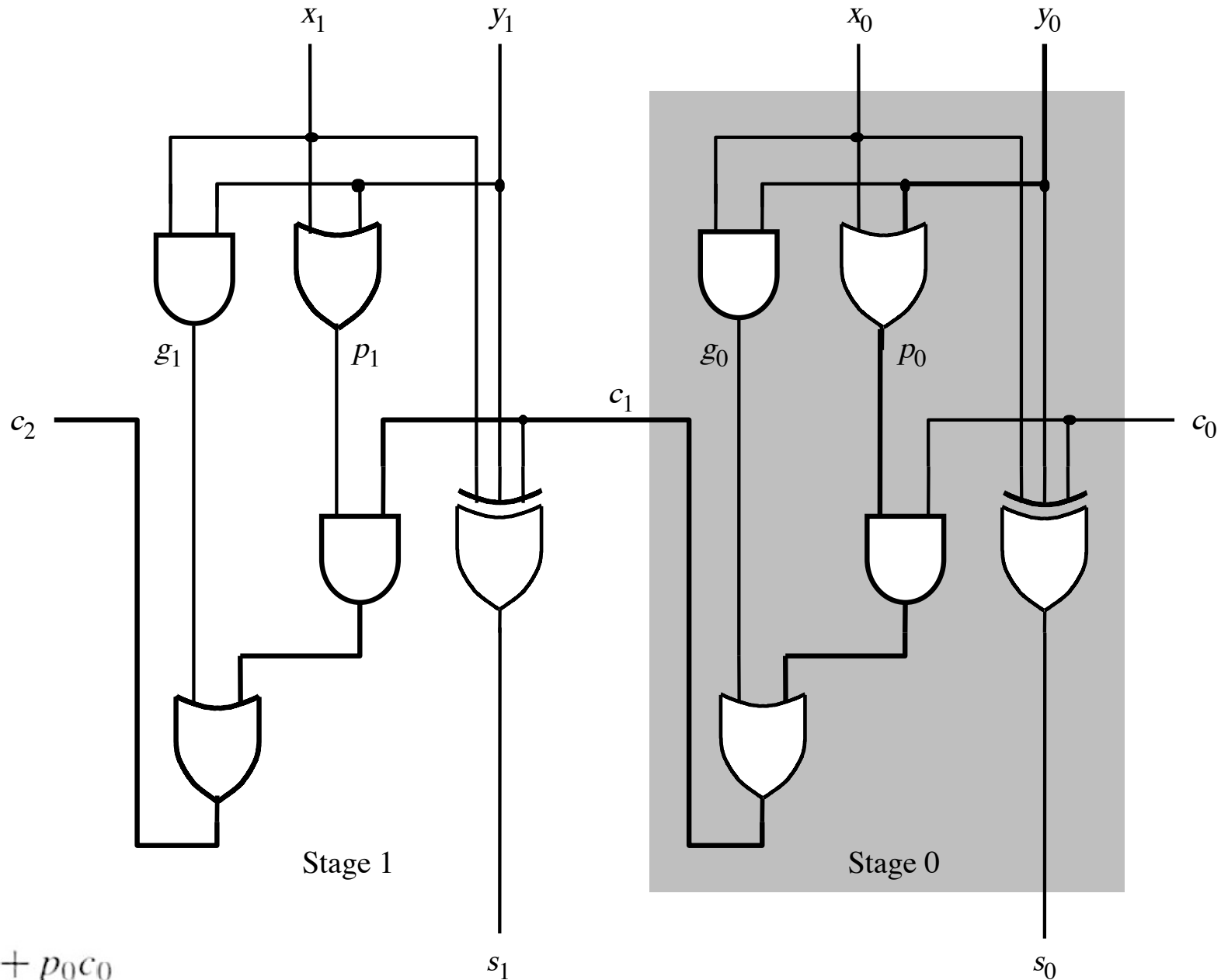


$$c_1 = g_0 + p_0 c_0$$

$$c_2 = g_1 + p_1 g_0 + p_1 p_0 c_0$$

[ Figure 3.14 from the textbook ]

# Now we can Build a Ripple-Carry Adder

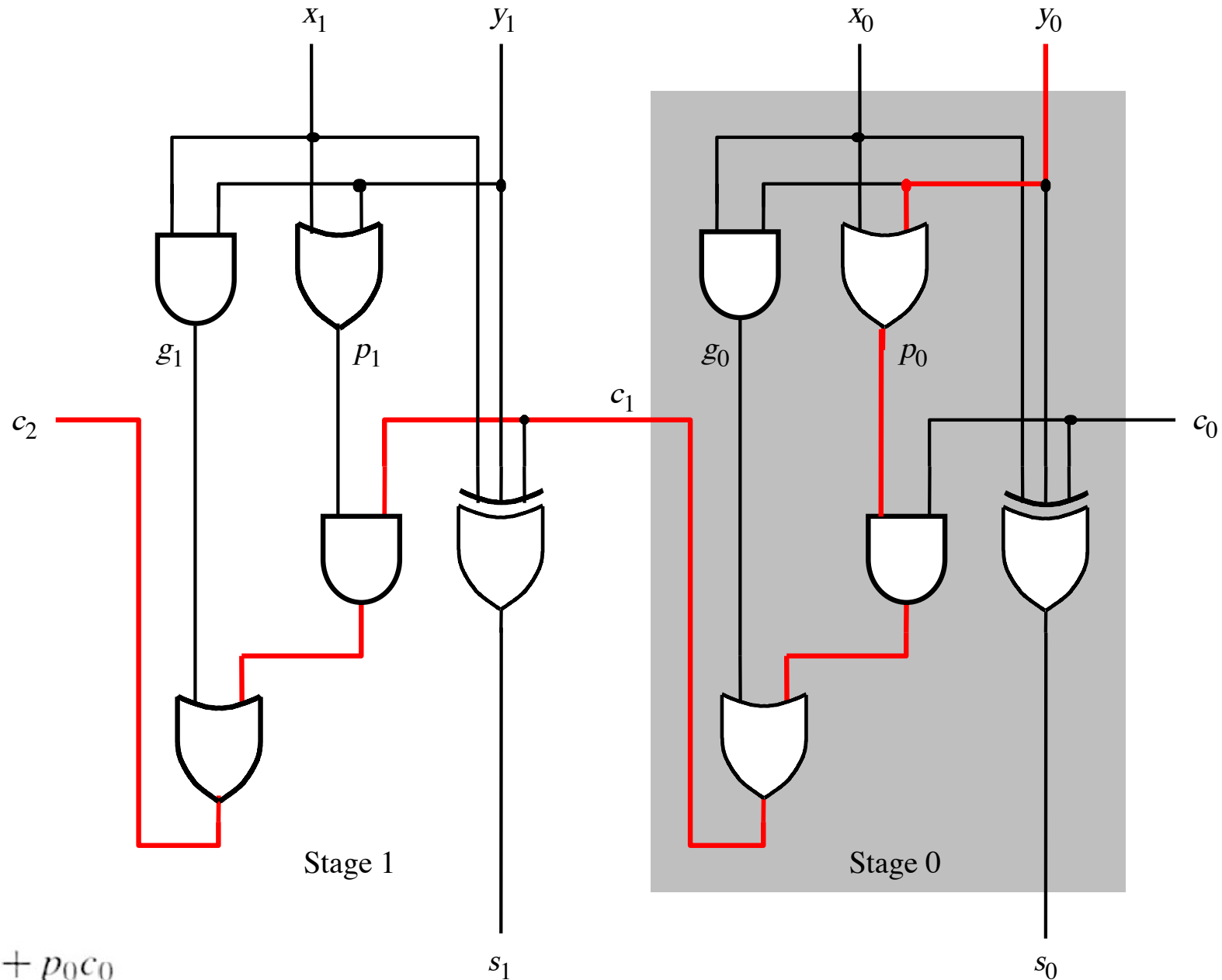


$$c_1 = g_0 + p_0 c_0$$


$$c_2 = g_1 + p_1 g_0 + p_1 p_0 c_0$$

[ Figure 3.14 from the textbook ]

# The delay is 5 gates (1+2+2)

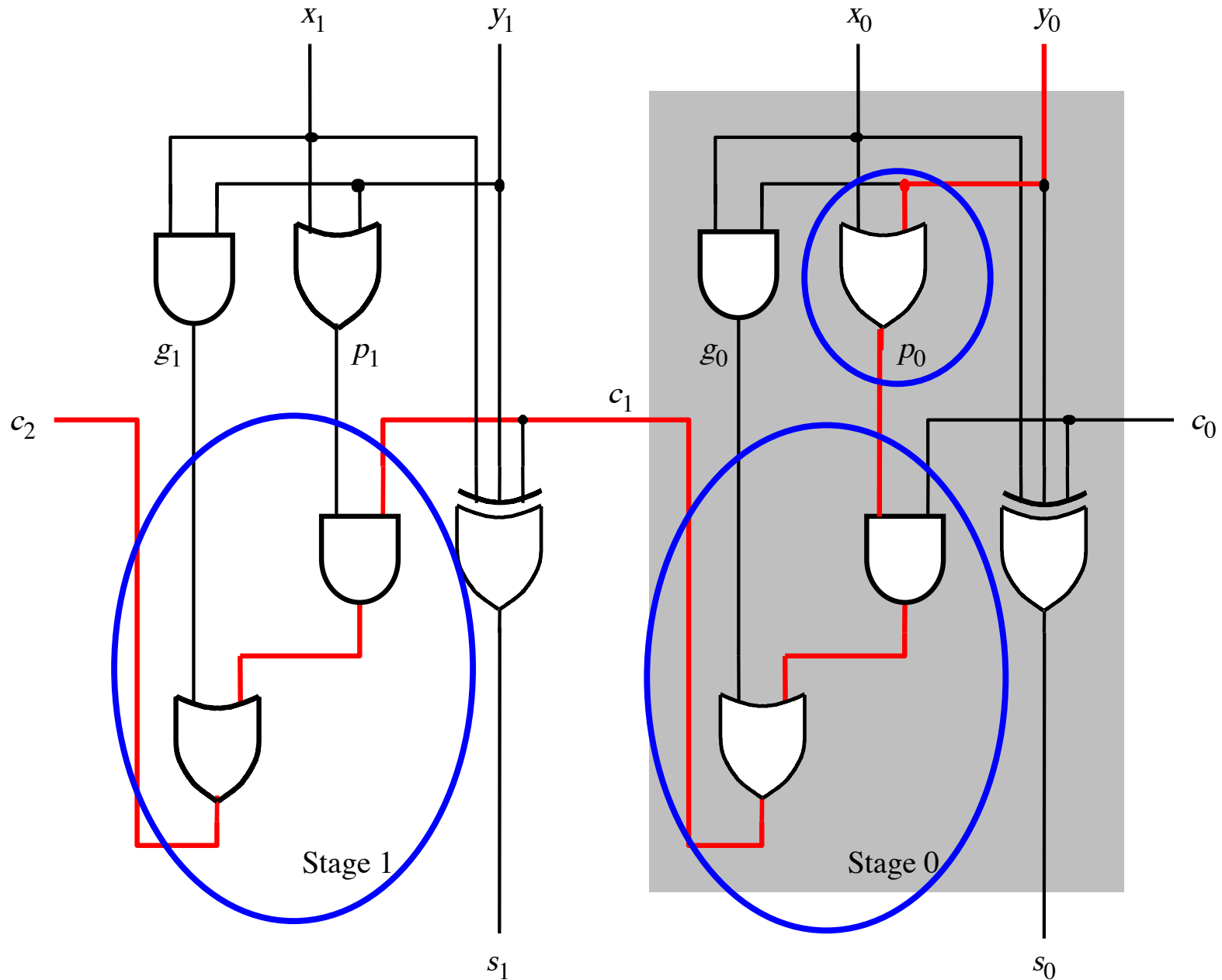
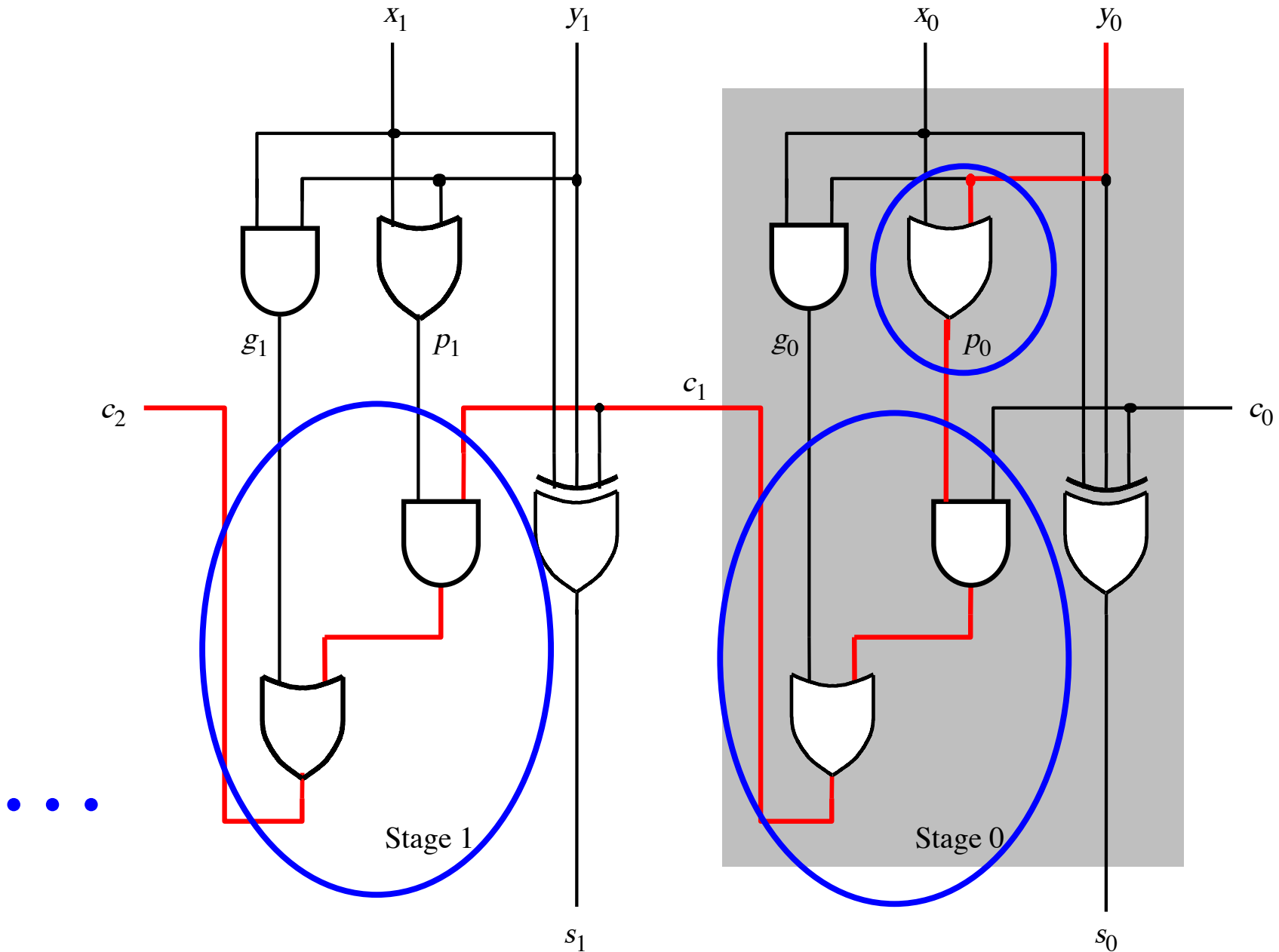
# n-bit ripple-carry adder: $2n+1$ gate delays



# Decomposing the Carry Expression

$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

$$c_{i+1} = \underbrace{x_i y_i}_{g_i} + \underbrace{(x_i + y_i)}_{p_i} c_i$$

$$c_{i+1} = g_i + p_i c_i$$

$$c_{i+1} = g_i + p_i (g_{i-1} + p_{i-1} c_{i-1})$$


$$= g_i + p_i g_{i-1} + p_i p_{i-1} c_{i-1}$$

# Carry for the first two stages

$$c_1 = g_0 + p_0 c_0$$

$$c_2 = g_1 + p_1 g_0 + p_1 p_0 c_0$$
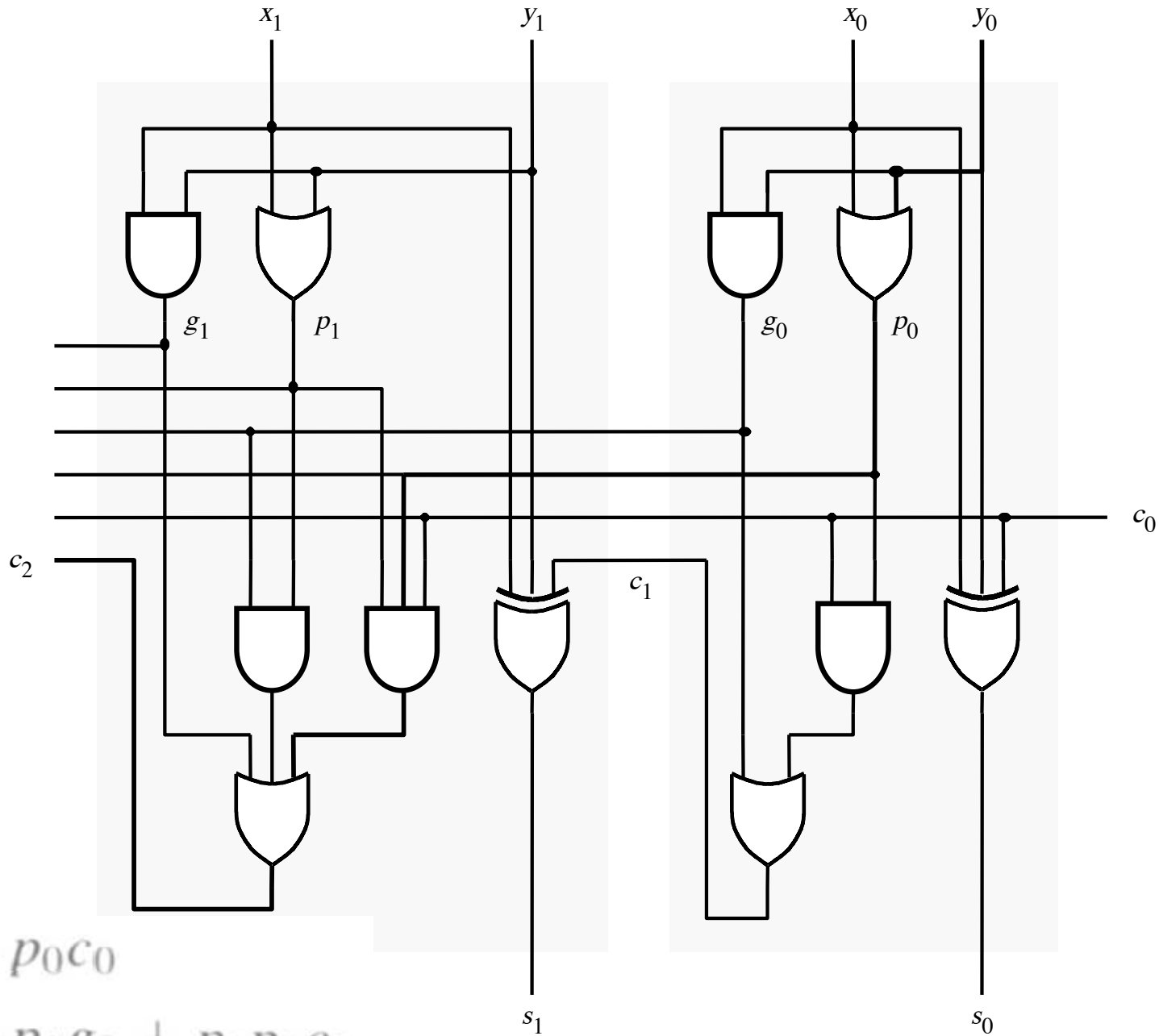
# The first two stages of a carry-lookahead adder




$$c_1 = g_0 + p_0 c_0$$

$$c_2 = g_1 + p_1 g_0 + p_1 p_0 c_0$$

[ Figure 3.15 from the textbook ]



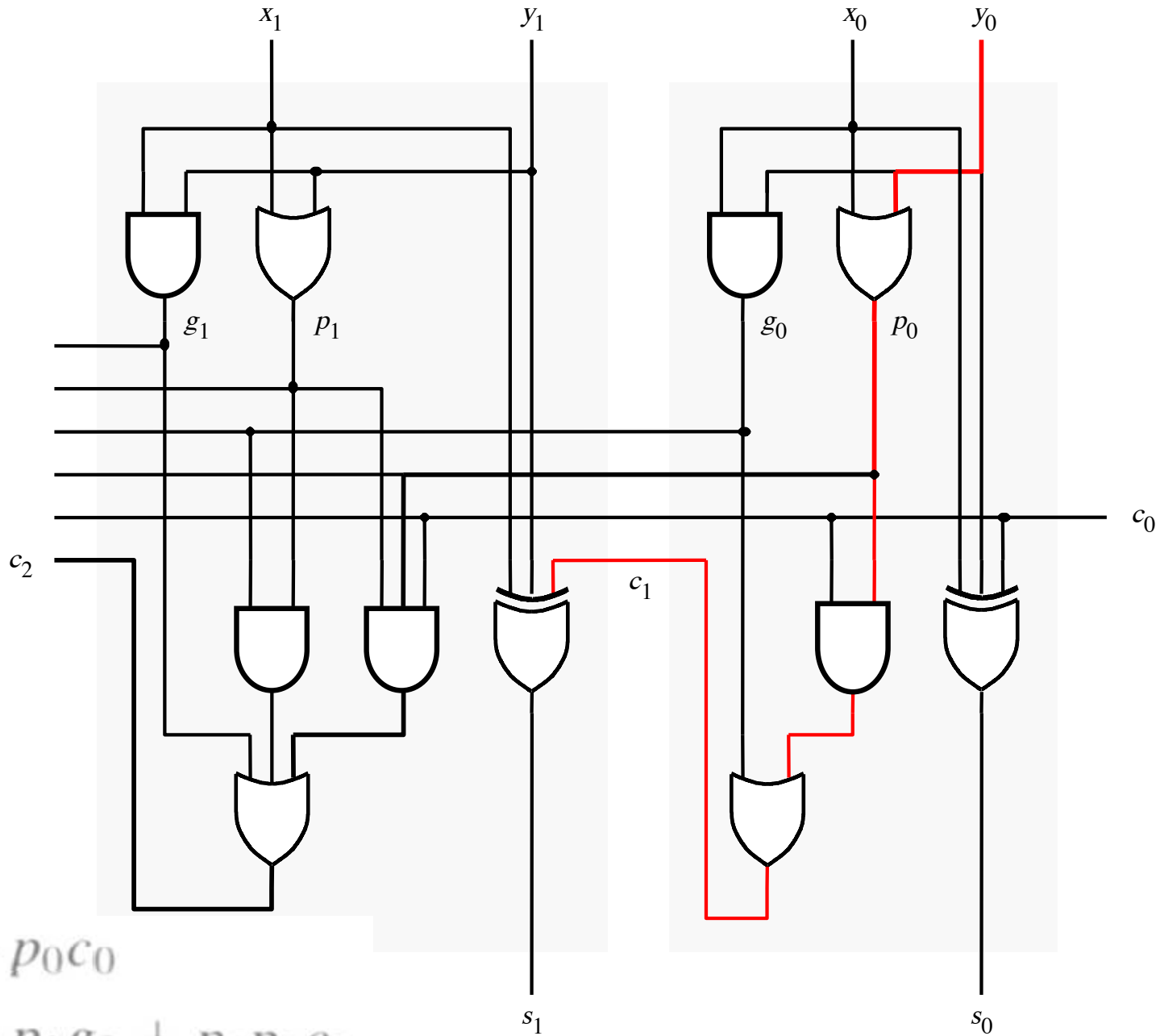
# It takes 3 gate delays to generate $c_1$



$$c_1 = g_0 + p_0 c_0$$

$$c_2 = g_1 + p_1 g_0 + p_1 p_0 c_0$$

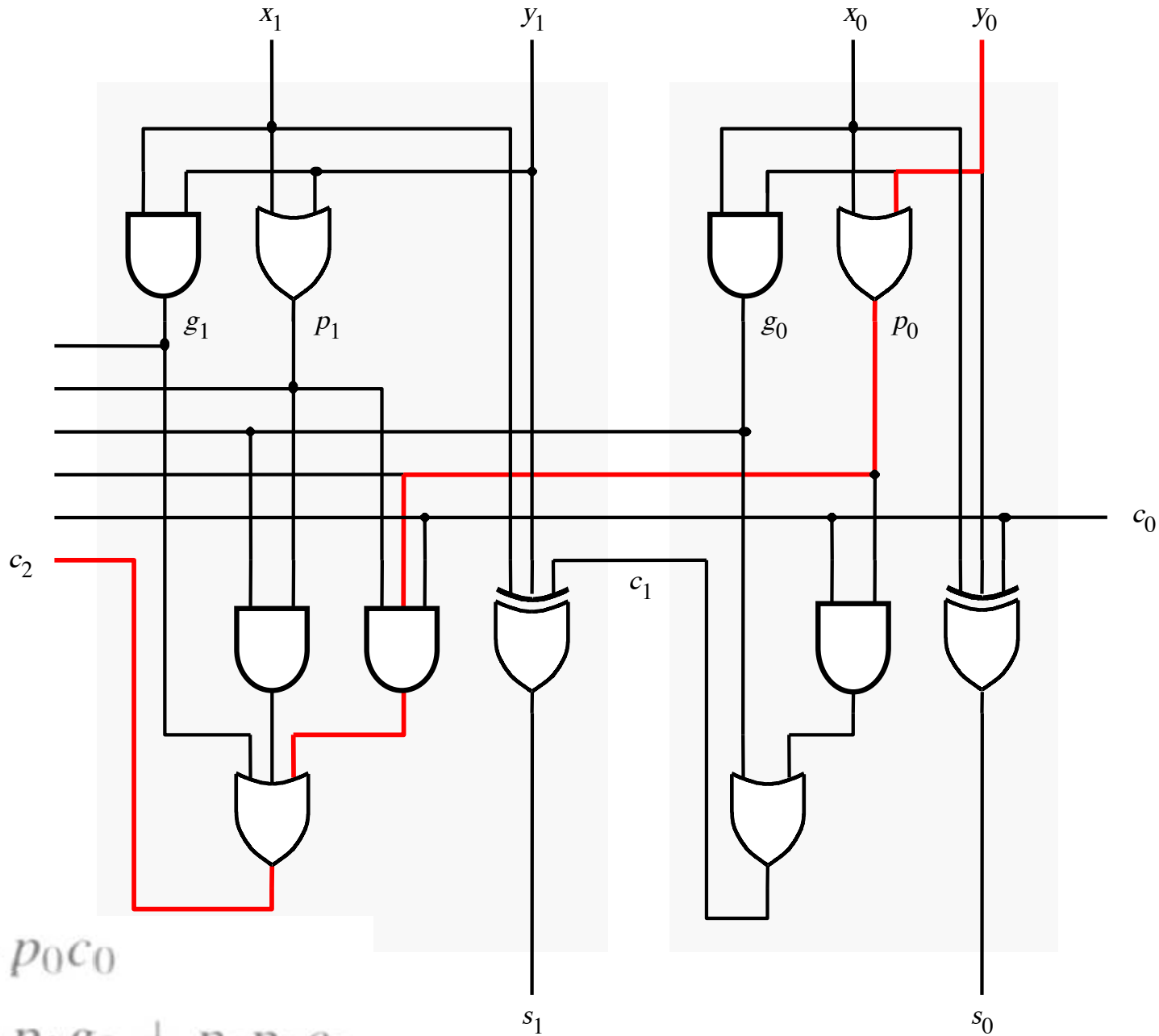
# It takes 3 gate delays to generate $c_2$




$$c_1 = g_0 + p_0 c_0$$

$$c_2 = g_1 + p_1 g_0 + p_1 p_0 c_0$$

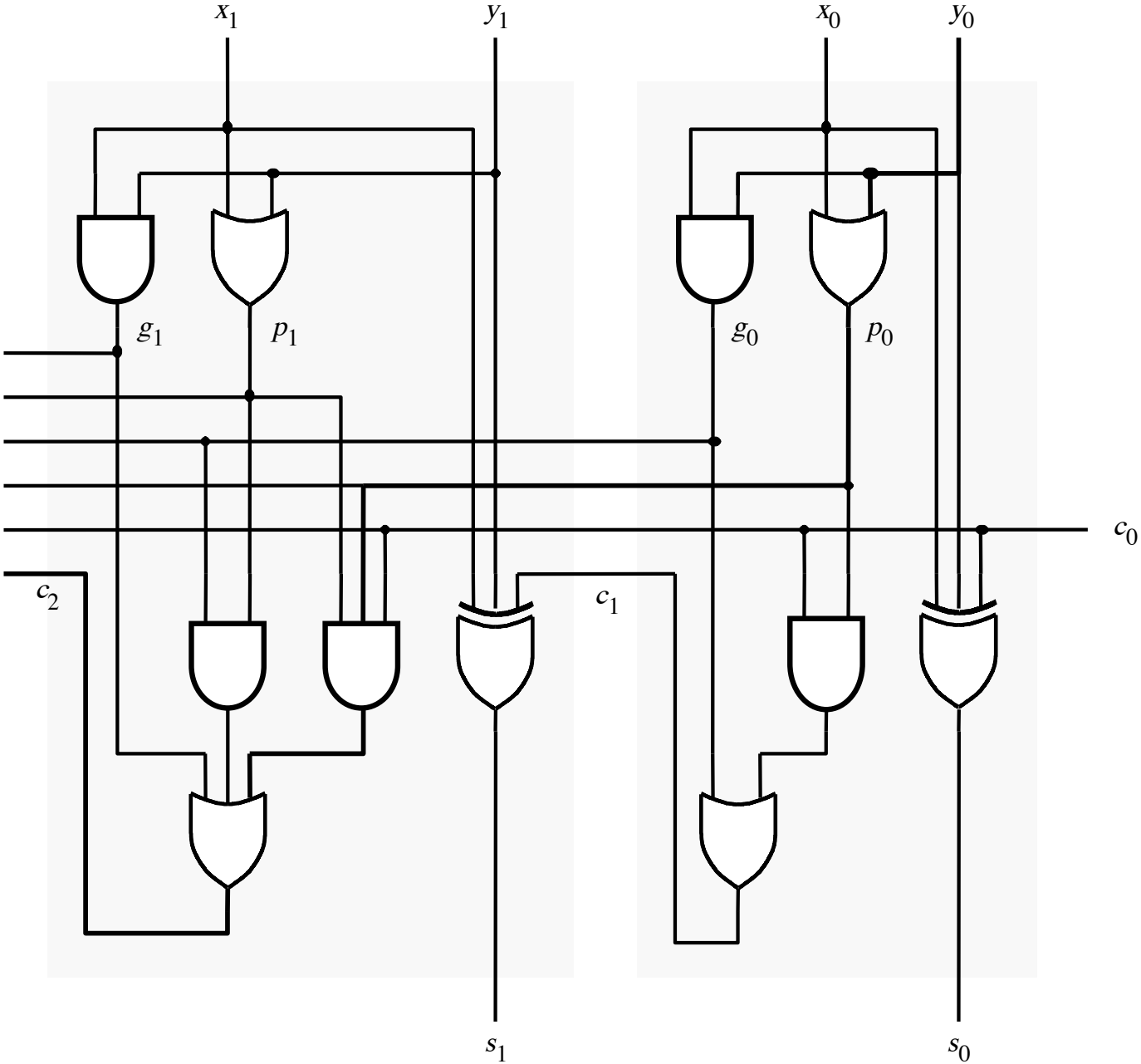
# The first two stages of a carry-lookahead adder



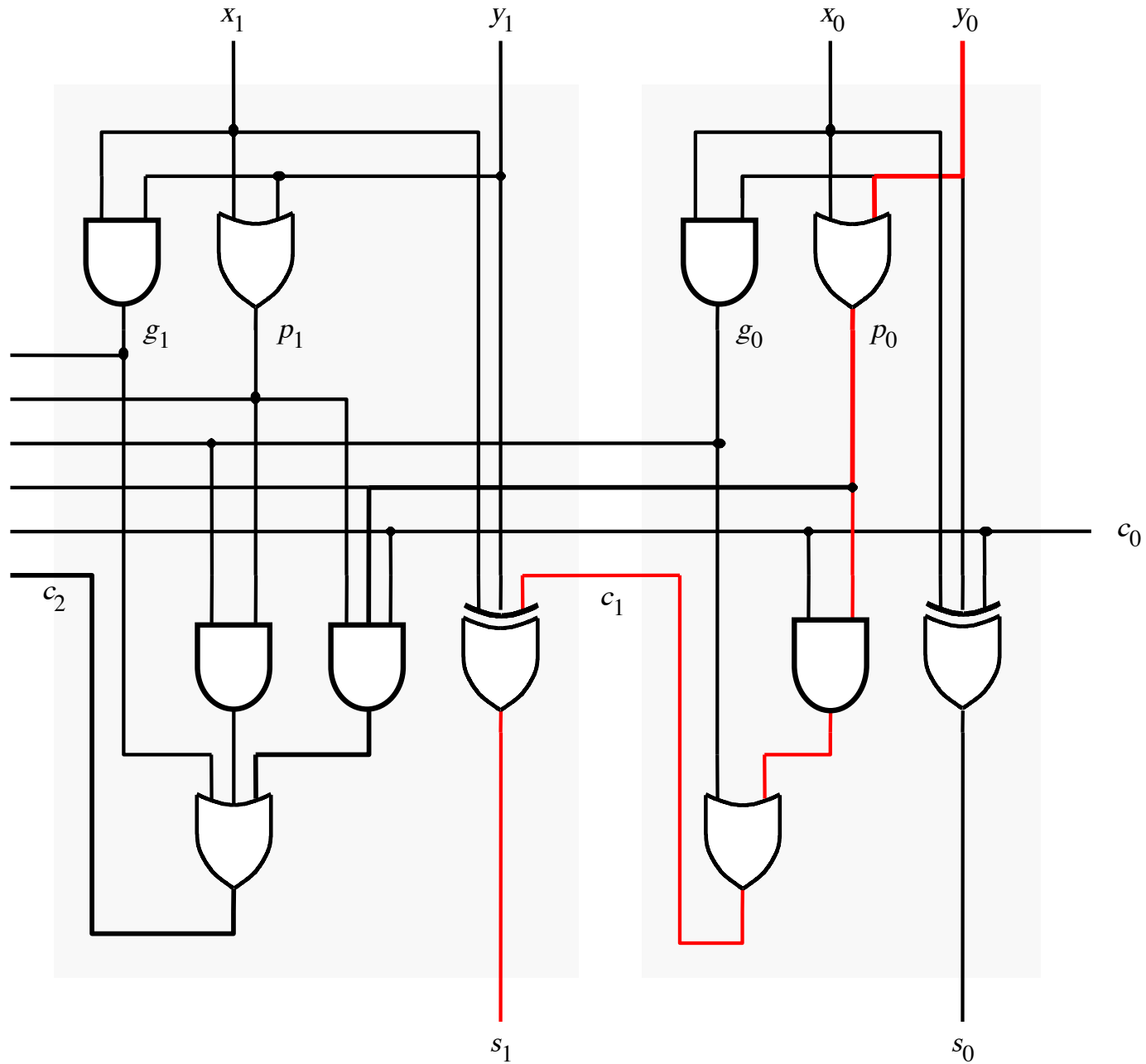**It takes 4 gate delays to generate  $s_1$**



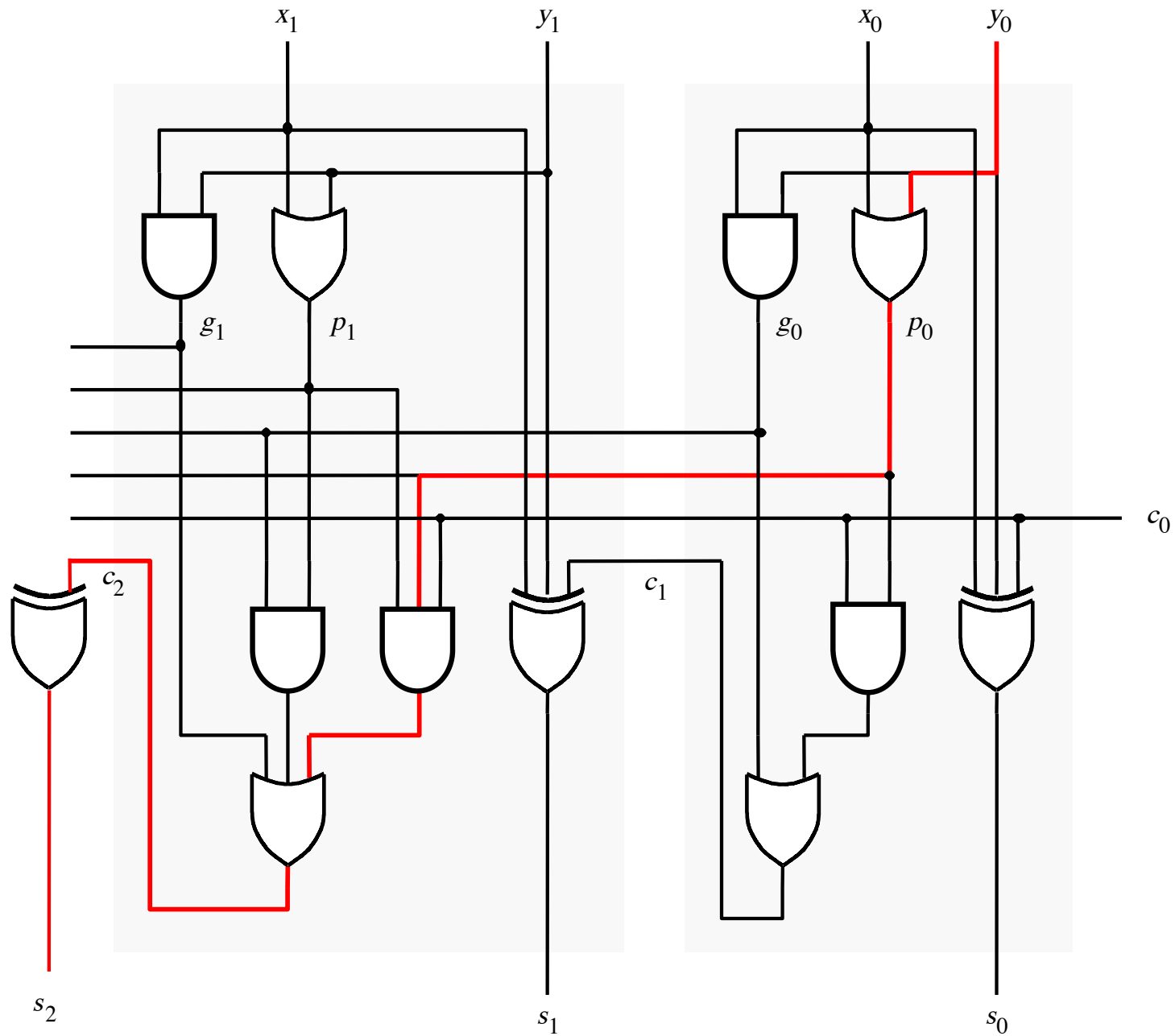**It takes 4 gate delays to generate  $s_2$**



# **N-bit Carry-Lookahead Adder**

- **It takes 3 gate delays to generate all carry signals**
- **It takes 1 more gate delay to generate all sum bits**
- **Thus, the total delay through an n-bit carry-lookahead adder is only 4 gate delays!**

# Expanding the Carry Expression

$$c_{i+1} = g_i + p_i c_i$$

$$c_1 = g_0 + p_0 c_0$$

$$c_2 = g_1 + p_1 g_0 + p_1 p_0 c_0$$

$$c_3 = g_2 + p_2 g_1 + p_2 p_1 g_0 + p_2 p_1 p_0 c_0$$

...

$$\begin{aligned} c_8 = & g_7 + p_7 g_6 + p_7 p_6 g_5 + p_7 p_6 p_5 g_4 \\ & + p_7 p_6 p_5 p_4 g_3 + p_7 p_6 p_5 p_4 p_3 g_2 \\ & + p_7 p_6 p_5 p_4 p_3 p_2 g_1 + p_7 p_6 p_5 p_4 p_3 p_2 p_1 g_0 \\ & + p_7 p_6 p_5 p_4 p_3 p_2 p_1 p_0 c_0 \end{aligned}$$

# Expanding the Carry Expression

$$c_{i+1} = g_i + p_i c_i$$

$$c_1 = g_0 + p_0 c_0$$

$$c_2 = g_1 + p_1 g_0 + p_1 p_0 c_0$$

$$c_3 = g_2 + p_2 g_1 + p_2 p_1 g_0 + p_2 p_1 p_0 c_0$$

...

$$c_8 = g_7 + p_7 g_6 + p_7 p_6 g_5 + p_7 p_6 p_5 g_4$$

Even this takes  
only 3 gate delays


$$+ p_7 p_6 p_5 p_4 g_3 + p_7 p_6 p_5 p_4 p_3 g_2$$

$$+ p_7 p_6 p_5 p_4 p_3 p_2 g_1 + p_7 p_6 p_5 p_4 p_3 p_2 p_1 g_0$$


$$+ p_7 p_6 p_5 p_4 p_3 p_2 p_1 p_0 c_0$$



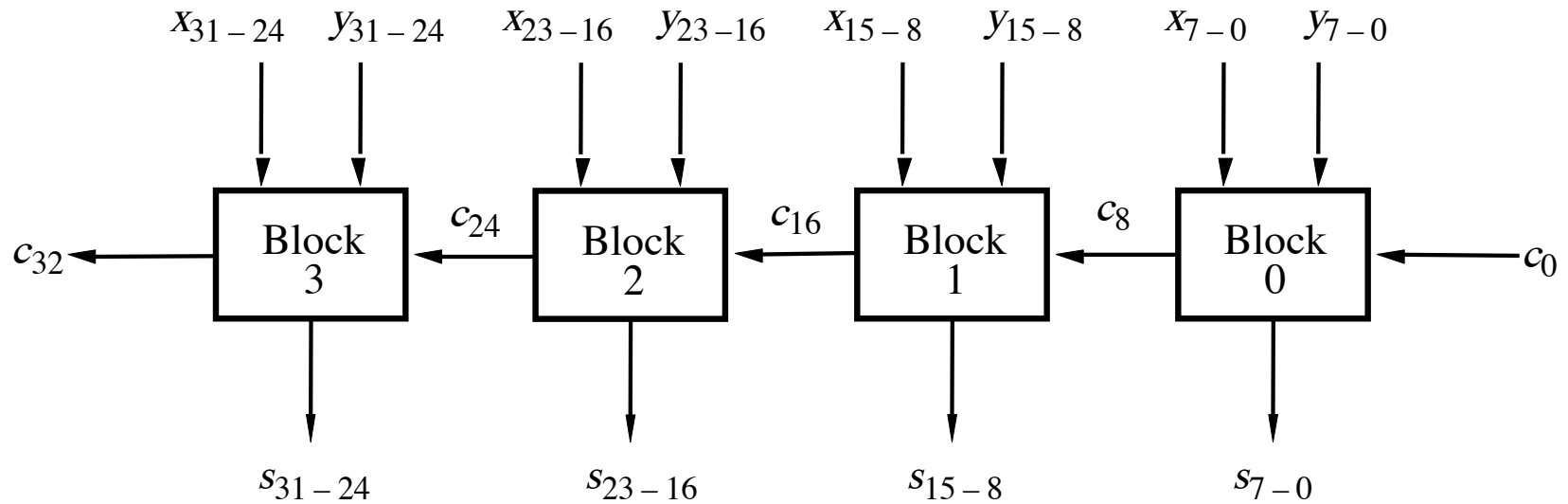
# A hierarchical carry-lookahead adder with ripple-carry between blocks



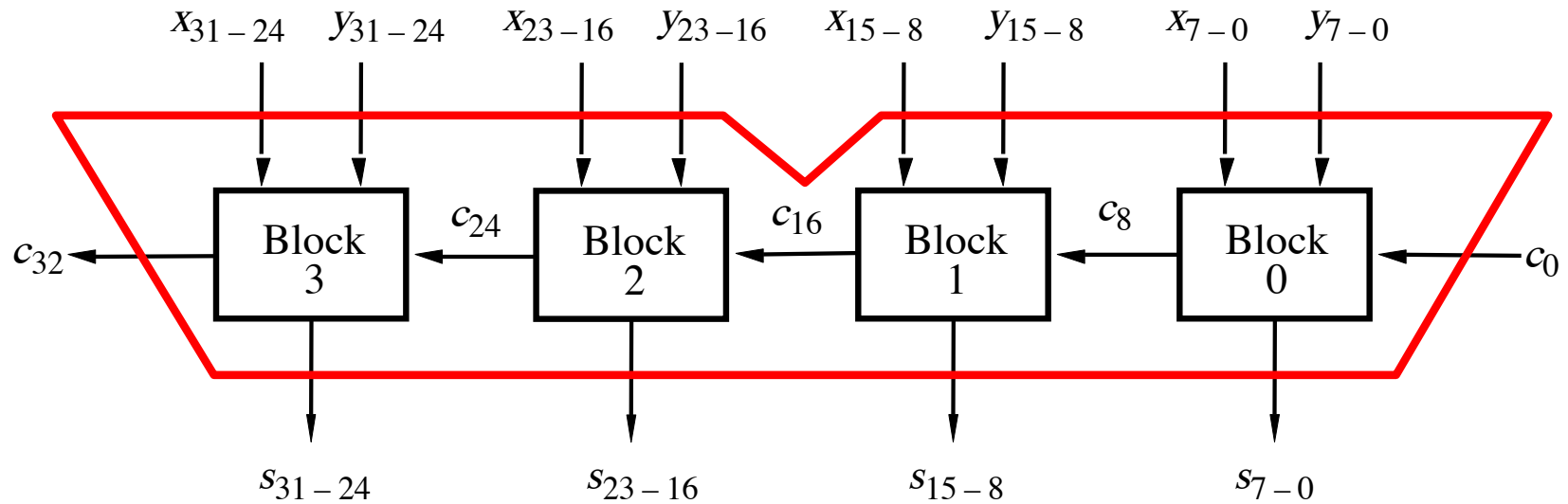
# A hierarchical carry-lookahead adder with ripple-carry between blocks



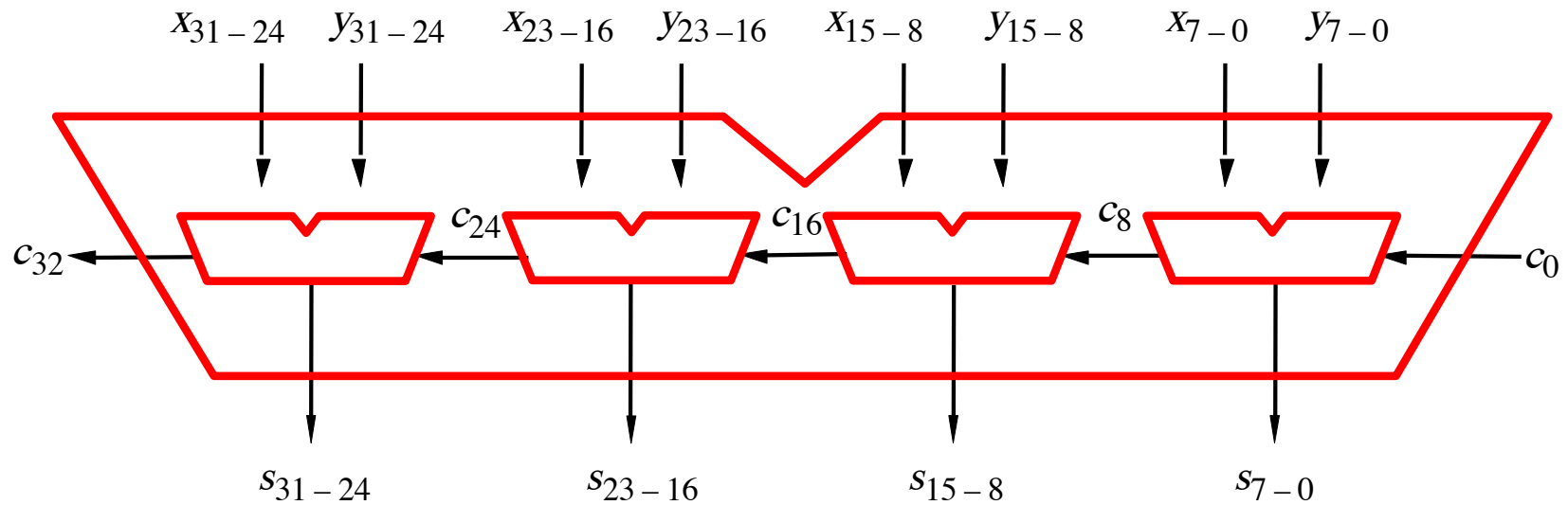
# A hierarchical carry-lookahead adder with ripple-carry between blocks


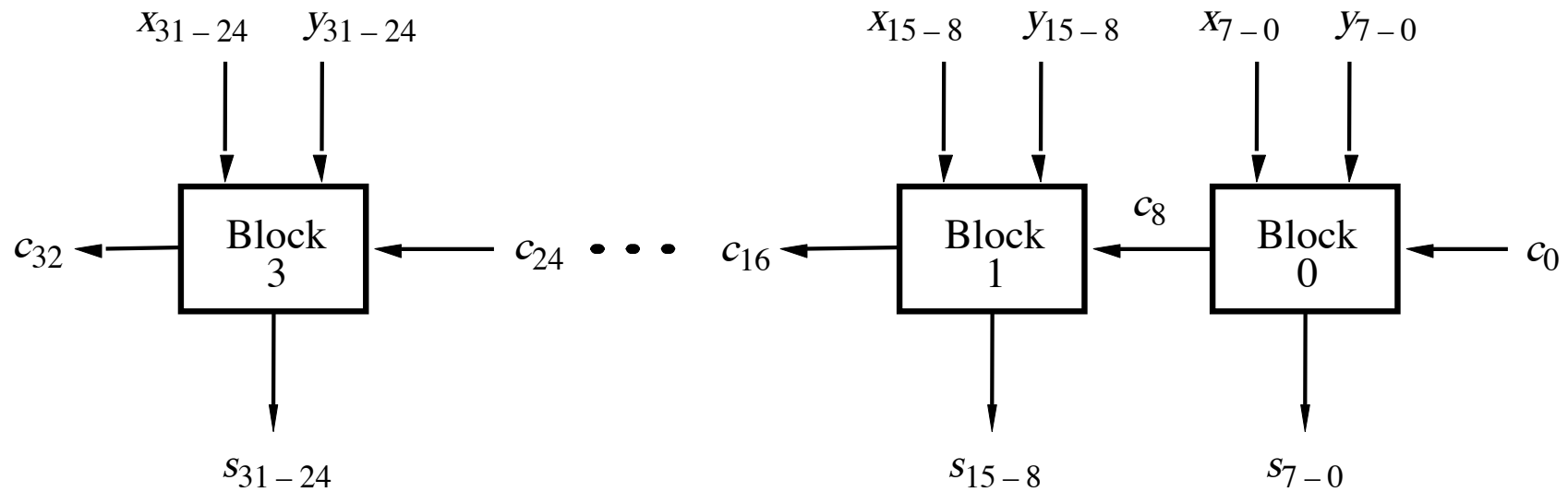
# A hierarchical carry-lookahead adder with ripple-carry between blocks




# A hierarchical carry-lookahead adder

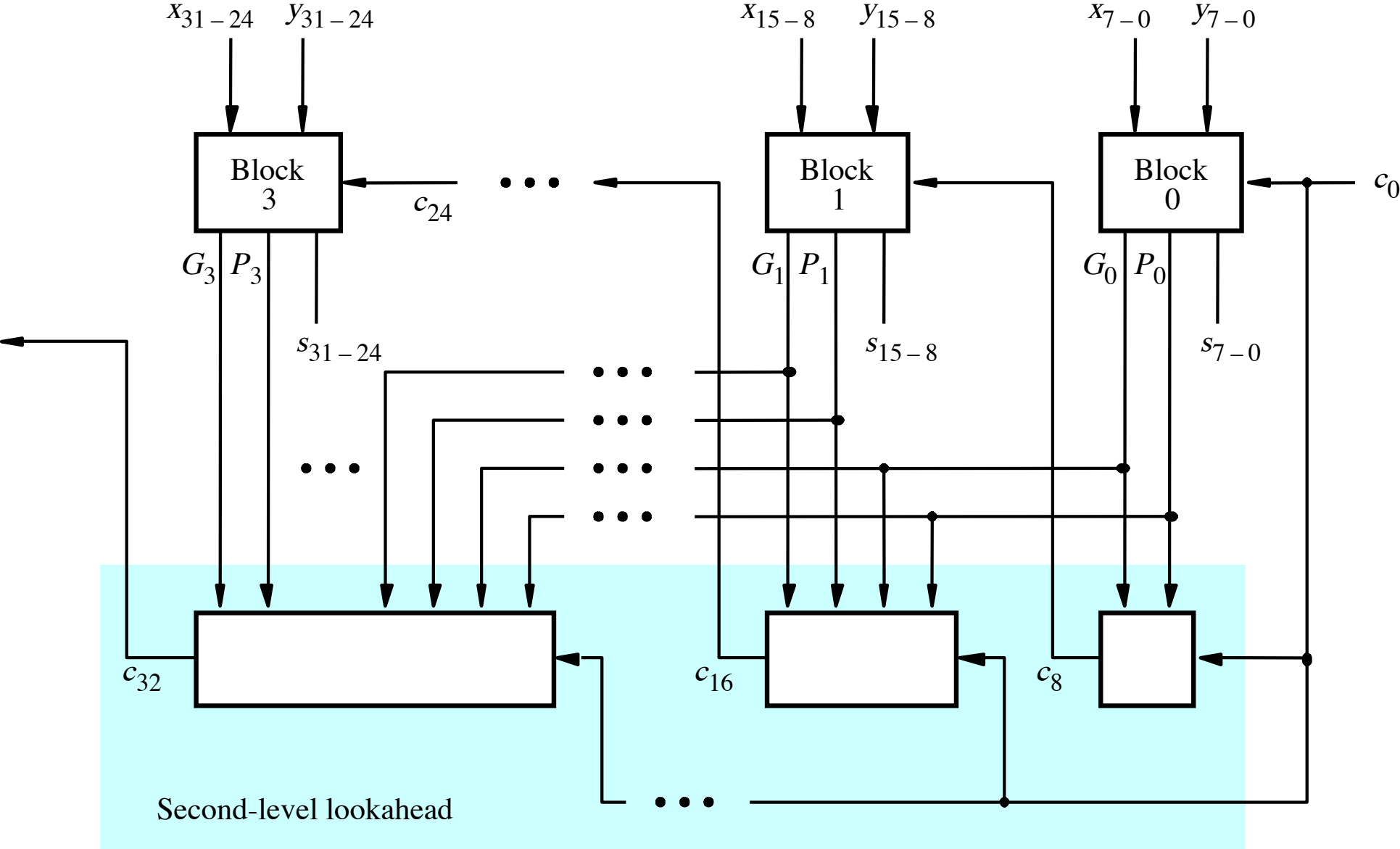


[ Figure 3.17 from the textbook ]


# A hierarchical carry-lookahead adder

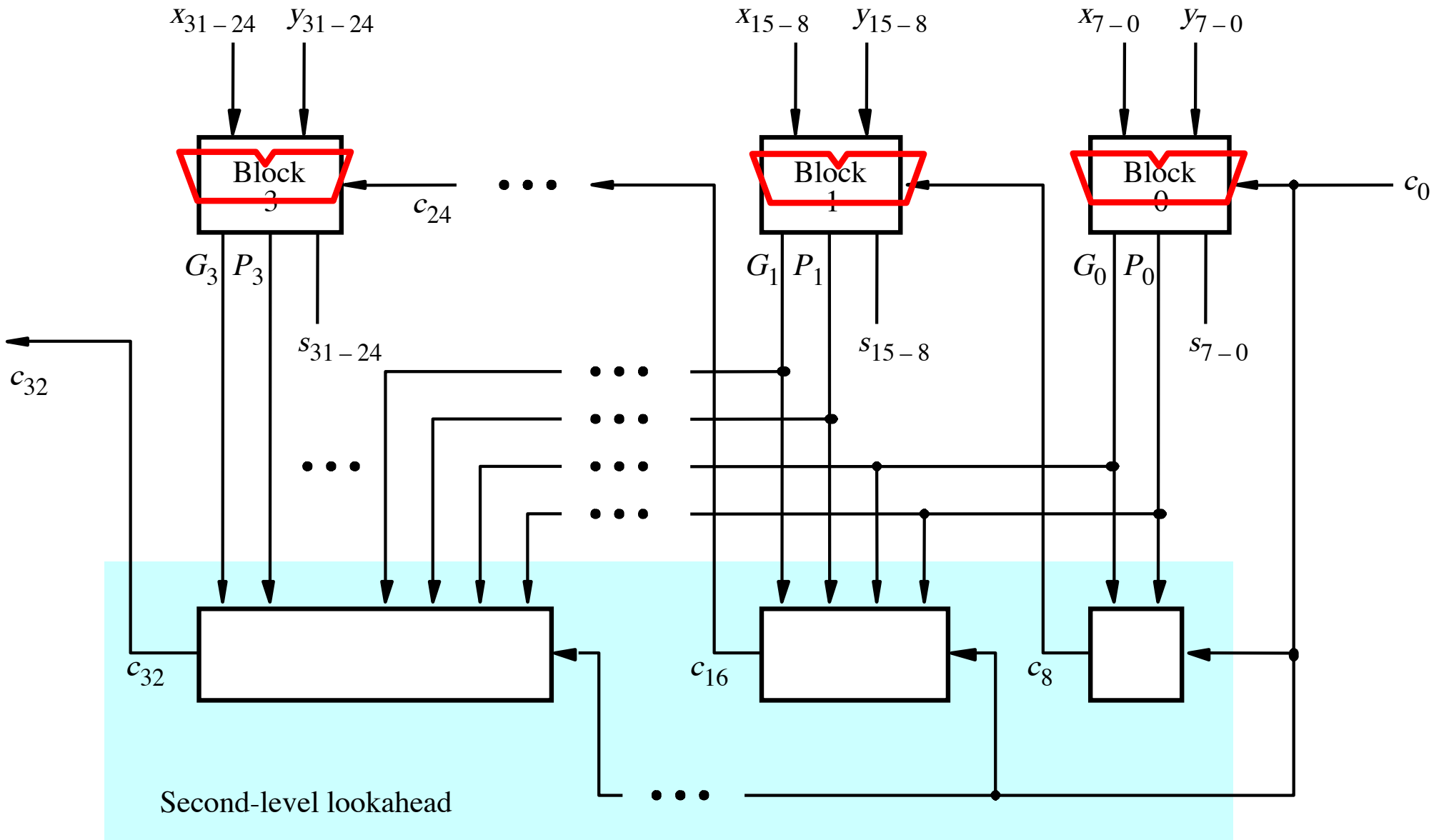

# A hierarchical carry-lookahead adder

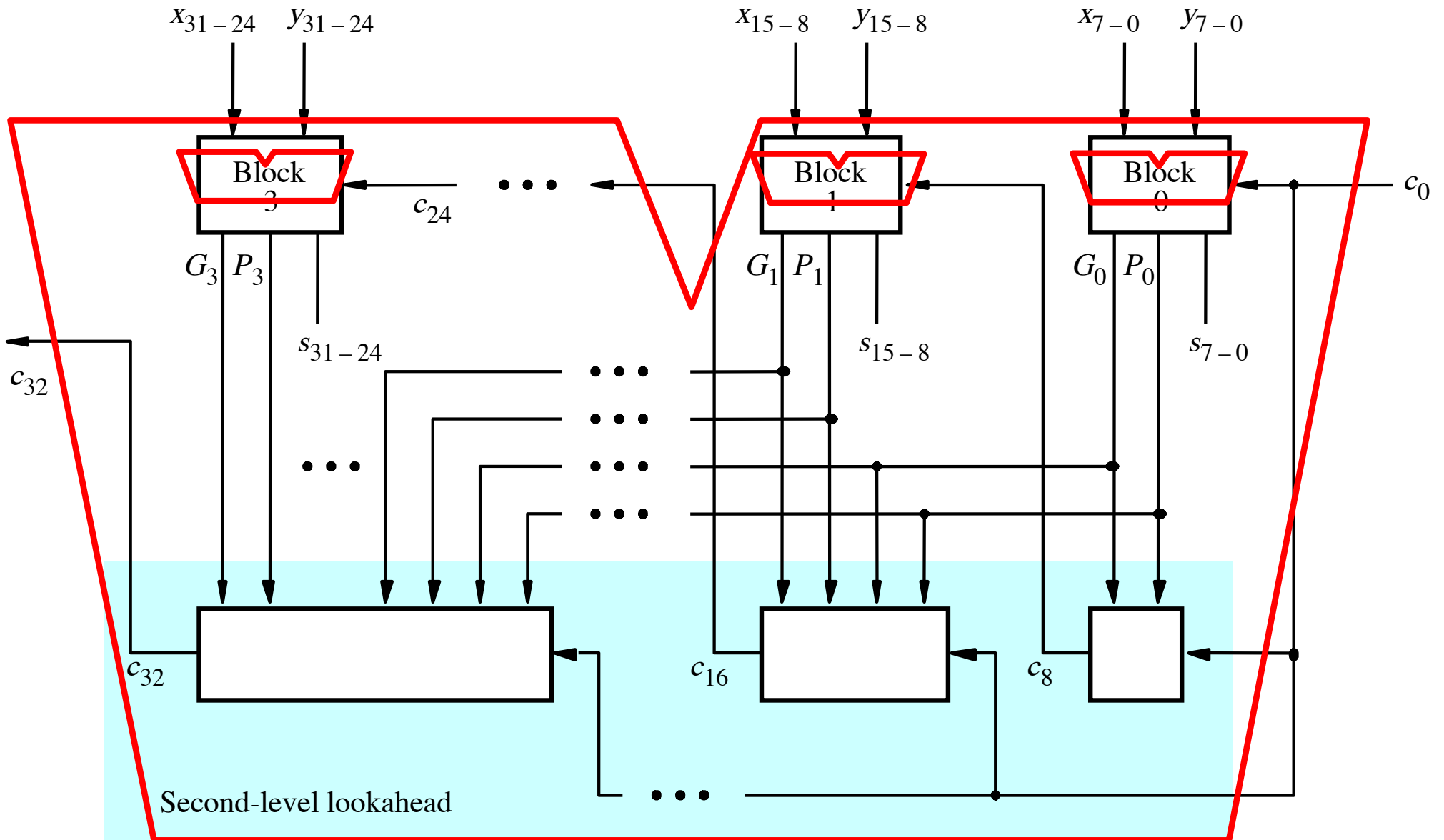

# A hierarchical carry-lookahead adder

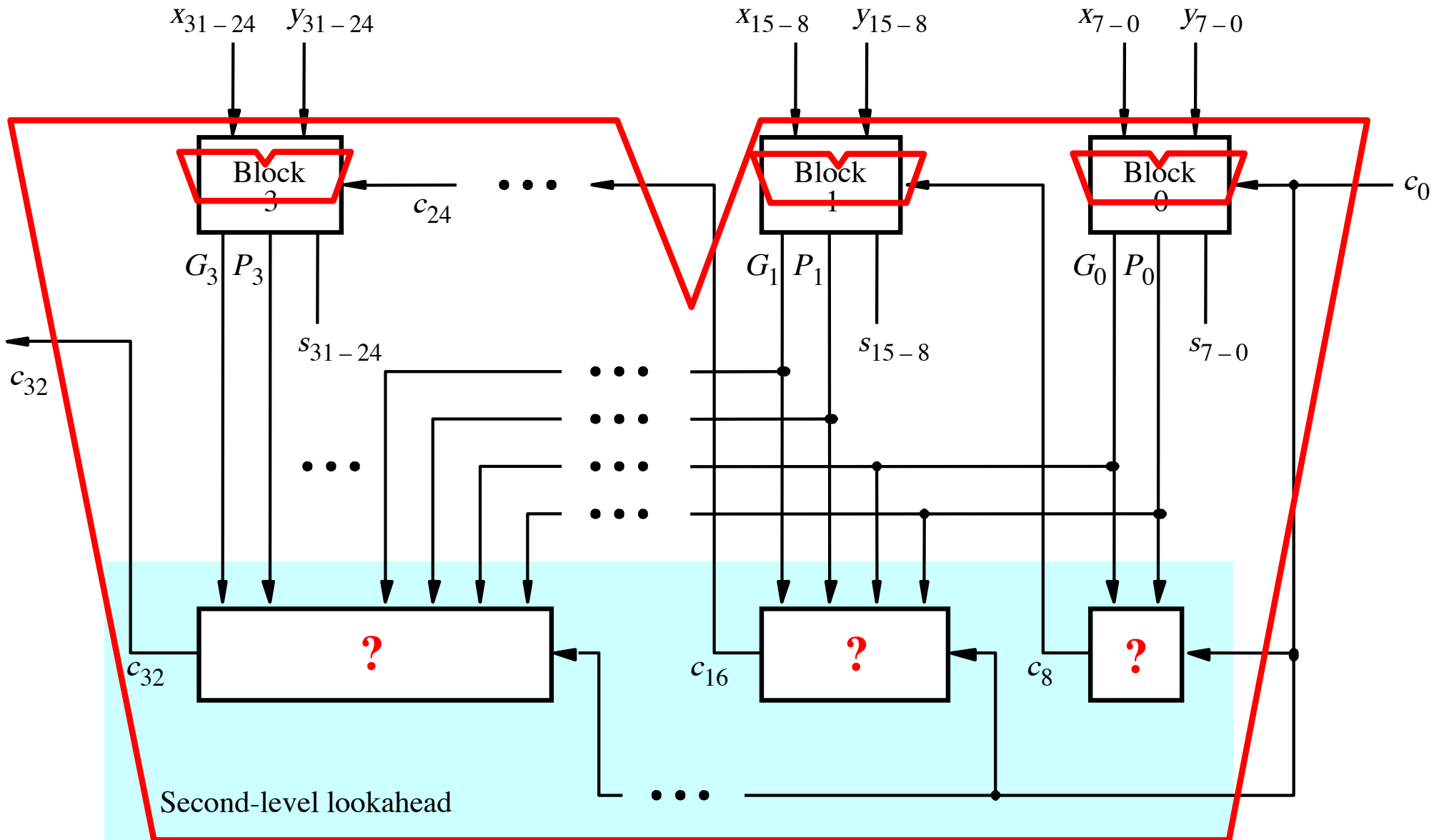



# The Hierarchical Carry Expression

$$\begin{aligned}c_8 = & g_7 + p_7g_6 + p_7p_6g_5 + p_7p_6p_5g_4 \\ & + p_7p_6p_5p_4g_3 + p_7p_6p_5p_4p_3g_2 \\ & + p_7p_6p_5p_4p_3p_2g_1 + p_7p_6p_5p_4p_3p_2p_1g_0 \\ & + p_7p_6p_5p_4p_3p_2p_1p_0c_0\end{aligned}$$

# The Hierarchical Carry Expression

$$\begin{aligned} c_8 = & g_7 + p_7g_6 + p_7p_6g_5 + p_7p_6p_5g_4 \\ & + p_7p_6p_5p_4g_3 + p_7p_6p_5p_4p_3g_2 \\ & + p_7p_6p_5p_4p_3p_2g_1 + p_7p_6p_5p_4p_3p_2p_1g_0 \\ & + p_7p_6p_5p_4p_3p_2p_1p_0c_0 \end{aligned}$$

# The Hierarchical Carry Expression

$$c_8 = g_7 + p_7g_6 + p_7p_6g_5 + p_7p_6p_5g_4$$
$$+ p_7p_6p_5p_4g_3 + p_7p_6p_5p_4p_3g_2$$
$$+ p_7p_6p_5p_4p_3p_2g_1 + p_7p_6p_5p_4p_3p_2p_1g_0$$
$$+ p_7p_6p_5p_4p_3p_2p_1p_0c_0$$

$G_0$  →

$P_0$  →

# The Hierarchical Carry Expression

$$c_8 = g_7 + p_7g_6 + p_7p_6g_5 + p_7p_6p_5g_4$$
$$+ p_7p_6p_5p_4g_3 + p_7p_6p_5p_4p_3g_2$$
$$+ p_7p_6p_5p_4p_3p_2g_1 + p_7p_6p_5p_4p_3p_2p_1g_0$$
$$+ p_7p_6p_5p_4p_3p_2p_1p_0c_0$$

$G_0$  →

$P_0$  →

$$c_8 = G_0 + P_0c_0$$

# The Hierarchical Carry Expression


$$c_8 = G_0 + P_0 c_0$$

$$\begin{aligned} c_{16} &= G_1 + P_1 c_8 \\ &= G_1 + P_1 G_0 + P_1 P_0 c_0 \end{aligned}$$

$$c_{24} = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 c_0$$


$$c_{32} = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 c_0$$

# A hierarchical carry-lookahead adder

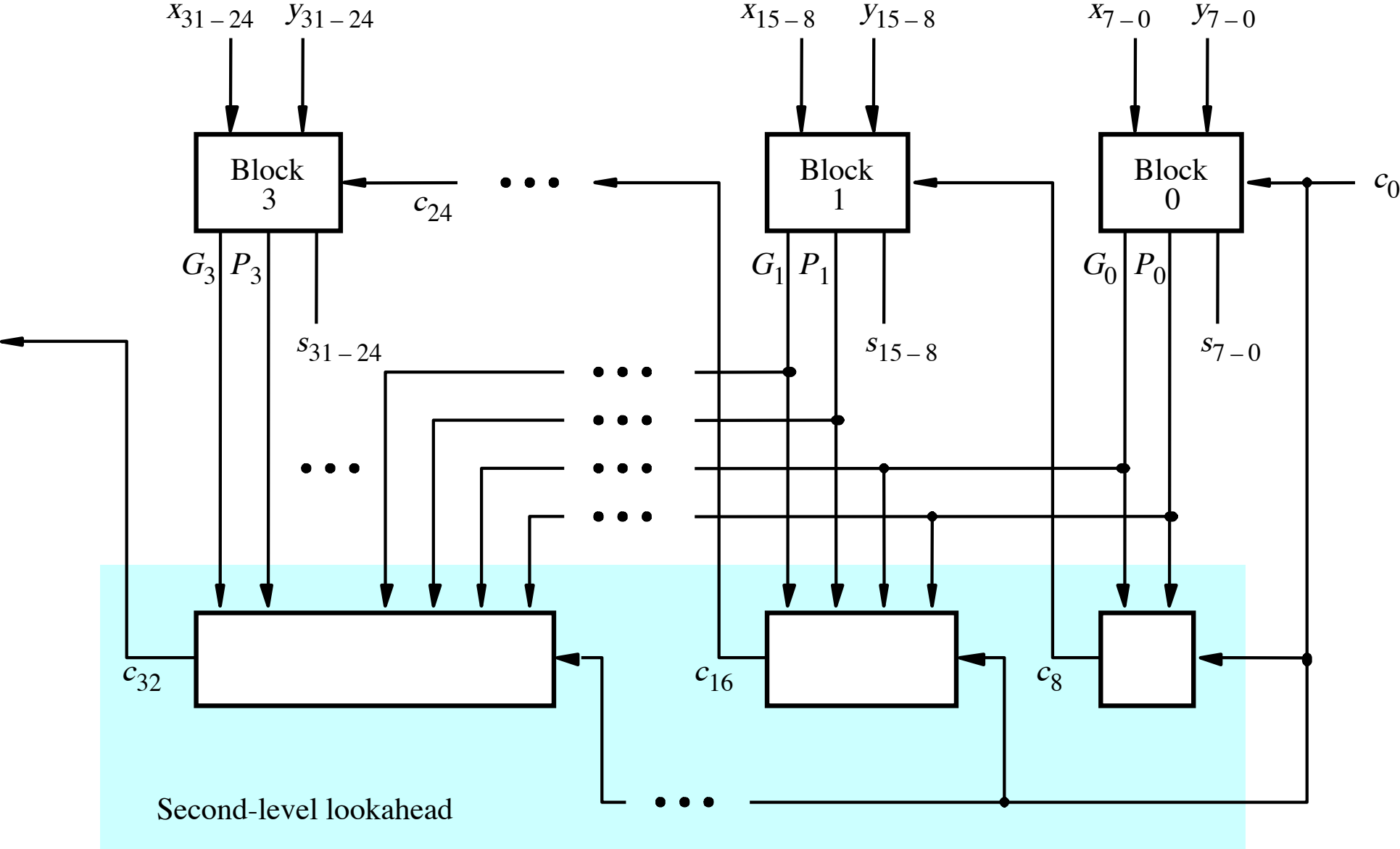

[ Figure 3.17 from the textbook ]

# A hierarchical carry-lookahead adder


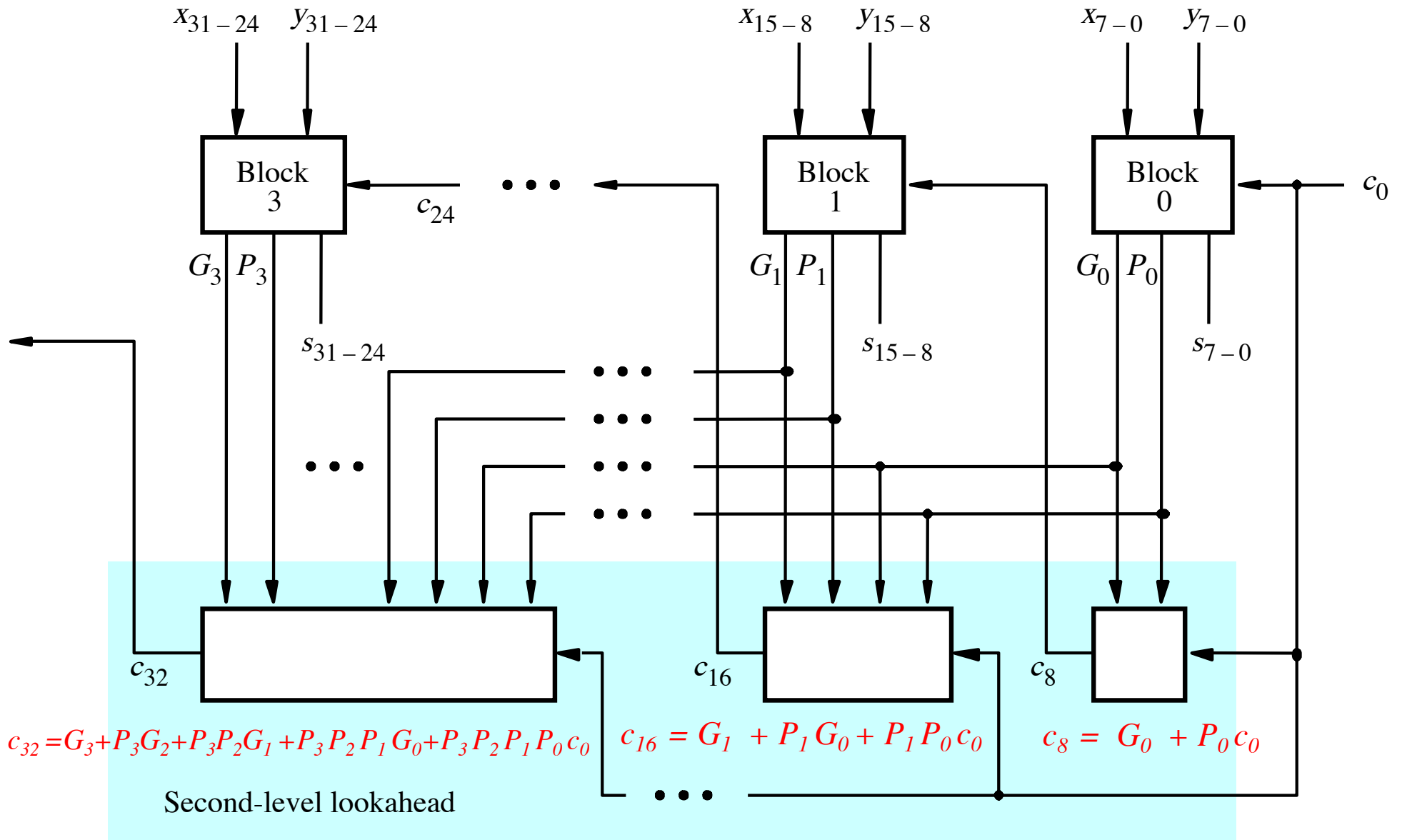


[ Figure 3.17 from the textbook ]
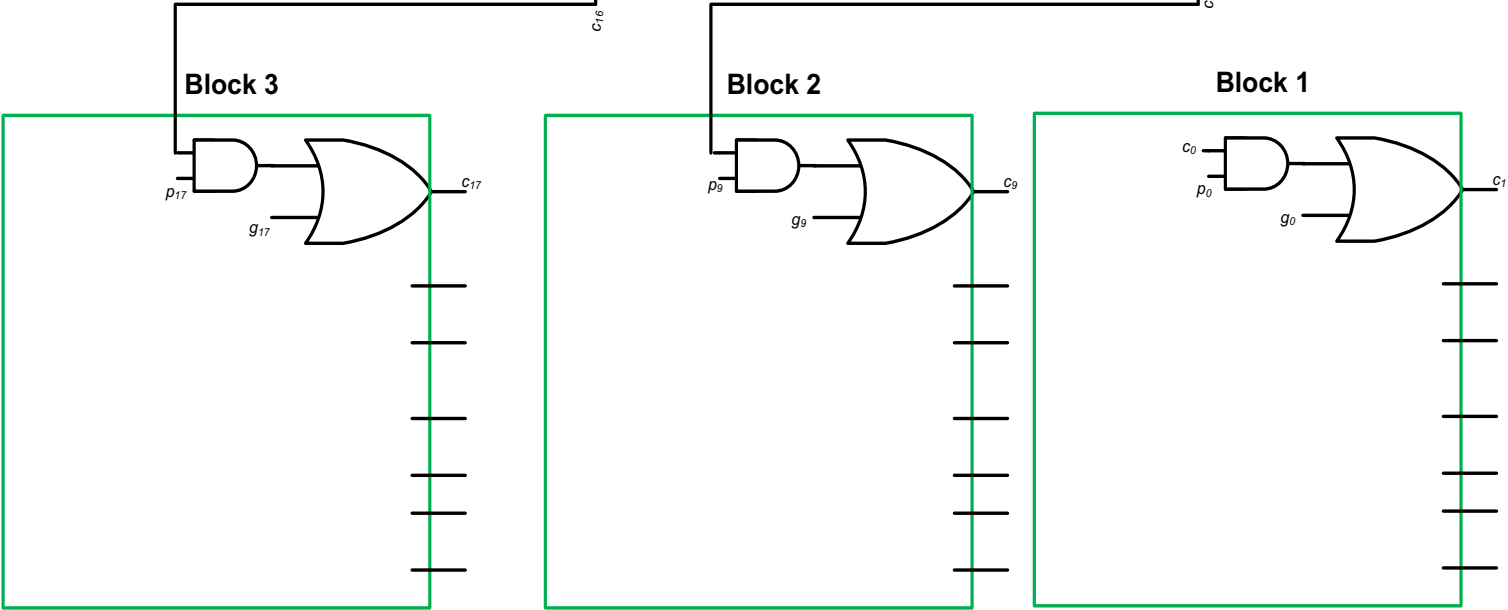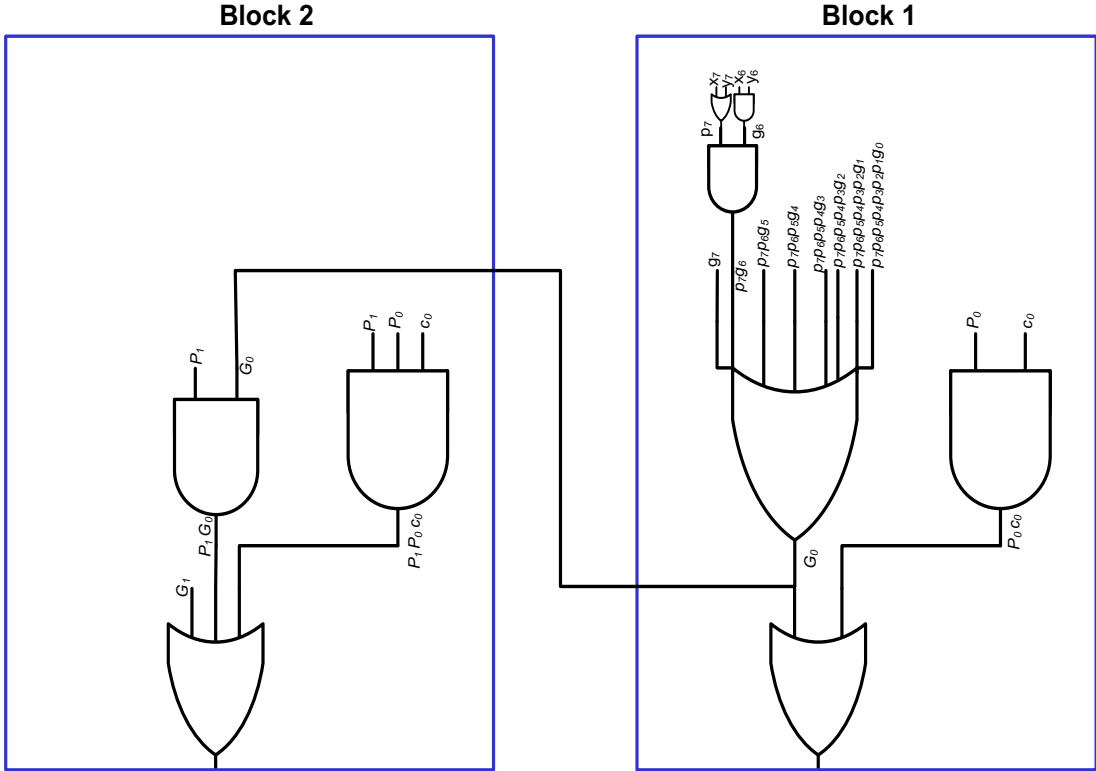
# Hierarchical CLA Adder Carry Logic

SECOND  
LEVEL  
HIERARCHY

- C8 – 5 gate delays
- C16 – 5 gate delays
- C24 – 5 Gate delays
- C32 – 5 Gate delays



FIRST LEVEL HIERARCHY




# Hierarchical CLA Critical Path

SECOND  
LEVEL  
HIERARCHY

C9 – 7 gate delays

C17 – 7 gate delays

C25 – 7 Gate delays

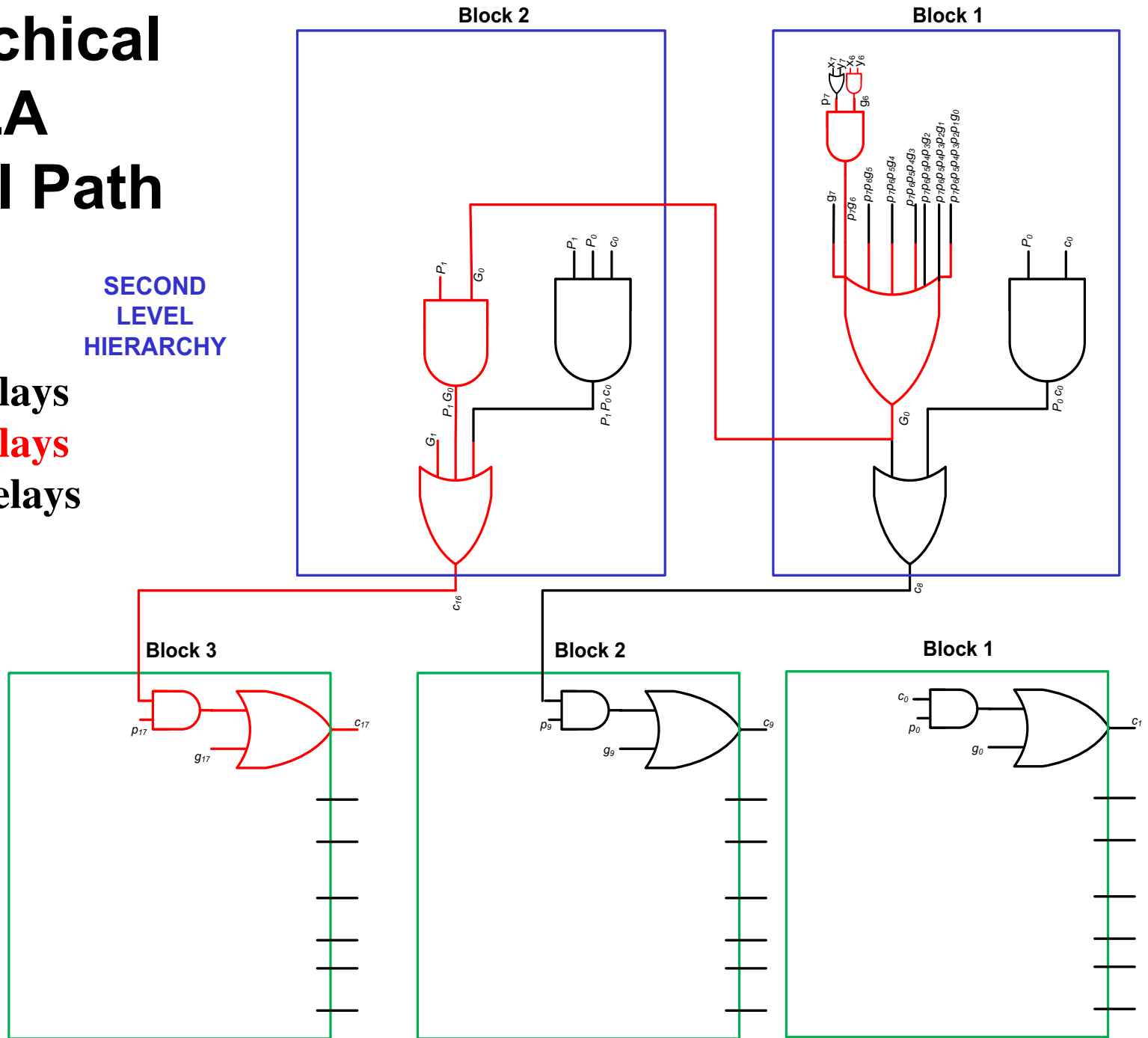

FIRST LEVEL HIERARCHY

# Total Gate Delay Through a Hierarchical Carry-Lookahead Adder

- Is 8 gates
  - 3 to generate all  $G_j$  and  $P_j$
  - +2 to generate  $c_8$ ,  $c_{16}$ ,  $c_{24}$ , and  $c_{32}$
  - +2 to generate internal carries in the blocks
  - +1 to generate the sum bits (one extra XOR)

**Questions?**

**THE END**