



# **CprE 281: Digital Logic**

**Instructor: Alexander Stoytchev**

**<http://www.ece.iastate.edu/~alexs/classes/>**

# Decoders and Encoders

*CprE 281: Digital Logic  
Iowa State University, Ames, IA  
Copyright © Alexander Stoytchev*

# **Administrative Stuff**

- **HW 6 is due today**

# **Administrative Stuff**


- **HW 7 is out**
- **It is due next Monday (Oct 16)**

# **Administrative Stuff**


- **Midterm Grades are Due this Friday**
- **only grades of C-, D, F have to be submitted to the registrar's office**

# **Quick Review**


# Graphical Symbol for a 2-1 Multiplexer

 

# Circuit for 2-1 Multiplexer

 

(b) Circuit

 


(c) Graphical symbol


$$f(s, x_1, x_2) = \bar{s}x_1 + sx_2$$




# The Three Basic Logic Gates

 

NOT gate

 


AND gate

 


OR gate

# Building an AND Gate with 2-to-1 Mux

 


$x_1$	$x_2$	$x_1 \cdot x_2$
0	0	0
0	1	0
1	0	0
1	1	1

 Red annotations: A vertical red line is drawn between the  $x_1$  and  $x_2$  columns. A horizontal red line is drawn between the second and third rows. Red curly braces group the output values: the first two rows are grouped as 0, and the last two rows are grouped as  $x_2$ .




# Building an OR Gate with 2-to-1 Mux

 


$x_1$	$x_2$	$x_1 + x_2$
0	0	0
0	1	1
1	0	1
1	1	1

 
Red annotations: A vertical red line is drawn between the  $x_1$  and  $x_2$  columns. A horizontal red line is drawn between the second and third rows. Red curly braces on the right group the output values: the first two rows (0, 1) are grouped and labeled  $x_2$ , and the last two rows (1, 1) are grouped and labeled 1.



# Building a NOT Gate with 2-to-1 Mux

 


$x$	$\bar{x}$
0	1
1	0

 

# Implications

**Any Boolean function can be implemented  
using only 2-to-1 multiplexers!**
 
# 4-to-1 Multiplexer: Graphical Symbol and Truth Table




(a) Graphic symbol


$s_1$	$s_0$	$f$
0	0	$w_0$
0	1	$w_1$
1	0	$w_2$
1	1	$w_3$

(b) Truth table


# The Three Basic Logic Gates

 

NOT gate

 


AND gate

 


OR gate

# Building an AND Gate with 4-to-1 Mux

 


$x_1$	$x_2$	$x_1 \cdot x_2$
0	0	0
0	1	0
1	0	0
1	1	1

 





# Building an OR Gate with 4-to-1 Mux

 



$x_1$	$x_2$	$x_1 + x_2$
0	0	0
0	1	1
1	0	1
1	1	1

 

# Building a NOT Gate with 4-to-1 Mux

 

$x$	$\bar{x}$
0	1
1	0

  


Two alternative solutions.


# Implications

**Any Boolean function can be implemented  
using only 4-to-1 multiplexers!**
 
# Using three 2-to-1 multiplexers to build one 4-to-1 multiplexer



# 16-1 Multiplexer

 


[ Figure 4.4 from the textbook ]

# **Synthesis of Logic Circuits Using Multiplexers**

# Implementation of a logic function with a 4x1 multiplexer

$w_1$	$w_2$	$f$
0	0	0
0	1	1
1	0	1
1	1	0

 


# Implementation of the same logic function with a 2x1 multiplexer

$w_1$	$w_2$	$f$
0	0	0
0	1	1
1	0	1
1	1	0

$w_1$	$f$
0	$w_2$
1	$\bar{w}_2$


(b) Modified truth table

 

(c) Circuit



# The XOR Logic Gate

 


(a) Two switches that control a light

$x$	$y$	$L$
0	0	0
0	1	1
1	0	1
1	1	0

(b) Truth table


# The XOR Logic Gate

 

(a) Two switches that control a light

$x$	$y$	$L$
0	0	0
0	1	1
1	0	1
1	1	0

(b) Truth table

 


(c) Logic network




(d) XOR gate symbol

 
# Implementation of the XOR Logic Gate with a 2-to-1 multiplexer and one NOT



 
# Implementation of the XOR Logic Gate with a 2-to-1 multiplexer and one NOT





 
# Implementation of the XOR Logic Gate with a 2-to-1 multiplexer and one NOT



 These two circuits are equivalent  
(the wires of the bottom AND gate are flipped)



   **In other words,  
all four of these are equivalent!**



# **Another Example (3-input XOR)**

# Implementation of 3-input XOR with 2-to-1 Multiplexers

$w_1$	$w_2$	$w_3$	$f$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1



# Implementation of 3-input XOR with 2-to-1 Multiplexers

$w_1$	$w_2$	$w_3$	$f$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1


Red annotations in the original image: A vertical red line is drawn between the  $w_1$  column and the  $w_2$  column. A horizontal red line is drawn between the  $w_3$  column and the  $f$  column. Red curly braces group the rows where  $w_1=0$  and  $w_1=1$ . The top brace is labeled  $w_2 \oplus w_3$ . The bottom brace is labeled  $\overline{w_2 \oplus w_3}$ .

# Implementation of 3-input XOR with 2-to-1 Multiplexers

$w_1$	$w_2$	$w_3$	$f$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

The truth table is divided into two groups by a horizontal red line. The top group (rows 1-4) has a red bracket on the right labeled  $w_2 \oplus w_3$ . The bottom group (rows 5-8) has a red bracket on the right labeled  $\overline{w_2 \oplus w_3}$ .

(a) Truth table

 

(b) Circuit


# Implementation of 3-input XOR with 2-to-1 Multiplexers

$w_1$	$w_2$	$w_3$	$f$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Blue annotations in the table:
 

- A blue bracket on the right side groups the first two rows (0,0) and (0,1) under the label  $w_3$ .
- A blue bracket on the right side groups the last two rows (0,1) and (1,0) under the label  $\overline{w_3}$ .

(a) Truth table

 

(b) Circuit

# Implementation of 3-input XOR with a 4-to-1 Multiplexer

$w_1$	$w_2$	$w_3$	$f$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

# Implementation of 3-input XOR with a 4-to-1 Multiplexer

$w_1$	$w_2$	$w_3$	$f$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1


# Implementation of 3-input XOR with a 4-to-1 Multiplexer

$w_1$	$w_2$	$w_3$	$f$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

# Implementation of 3-input XOR with a 4-to-1 Multiplexer

$w_1$	$w_2$	$w_3$	$f$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

(a) Truth table

 

(b) Circuit

# **Multiplexor Synthesis Using Shannon's Expansion**



# Three-input majority function

$w_1$	$w_2$	$w_3$	$f$
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

# Three-input majority function

$w_1$	$w_2$	$w_3$	$f$
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

$w_1$	$f$
0	0
1	1

# Three-input majority function

$w_1$	$w_2$	$w_3$	$f$
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

$w_1$	$f$
0	$w_2 w_3$
1	$w_2 + w_3$


# Three-input majority function

$w_1$	$w_2$	$w_3$	$f$
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

$w_1$	$f$
0	$w_2 w_3$
1	$w_2 + w_3$

(b) Truth table

 


(b) Circuit
 
# Three-input majority function

$$f = \bar{w}_1 w_2 w_3 + w_1 \bar{w}_2 w_3 + w_1 w_2 \bar{w}_3 + w_1 w_2 w_3$$

$$\begin{aligned} f &= \bar{w}_1 (w_2 w_3) + w_1 (\bar{w}_2 w_3 + w_2 \bar{w}_3 + w_2 w_3) \\ &= \bar{w}_1 (w_2 w_3) + w_1 (w_2 + w_3) \end{aligned}$$



# Shannon's Expansion Theorem

Any Boolean function  $f(w_1, \dots, w_n)$  can be rewritten in the form:

$$f(w_1, w_2, \dots, w_n) = \bar{w}_1 \cdot f(0, w_2, \dots, w_n) + w_1 \cdot f(1, w_2, \dots, w_n)$$

# Shannon's Expansion Theorem

Any Boolean function  $f(w_1, \dots, w_n)$  can be rewritten in the form:

$$f(w_1, w_2, \dots, w_n) = \bar{w}_1 \cdot f(0, w_2, \dots, w_n) + w_1 \cdot f(1, w_2, \dots, w_n)$$

$$f = \bar{w}_1 f_{\bar{w}_1} + w_1 f_{w_1}$$

# Shannon's Expansion Theorem

Any Boolean function  $f(w_1, \dots, w_n)$  can be rewritten in the form:

$$f(w_1, w_2, \dots, w_n) = \bar{w}_1 \cdot f(0, w_2, \dots, w_n) + w_1 \cdot f(1, w_2, \dots, w_n)$$

$$f = \bar{w}_1 f_{\bar{w}_1} + w_1 f_{w_1}$$

cofactor

cofactor



# Shannon's Expansion Theorem (Example)

$$f(w_1, w_2, w_3) = w_1w_2 + w_1w_3 + w_2w_3$$

# Shannon's Expansion Theorem (Example)

$$f(w_1, w_2, w_3) = w_1w_2 + w_1w_3 + w_2w_3$$

$$f(w_1, w_2, w_3) = w_1w_2 + w_1w_3 + w_2w_3 (\overline{w_1} + w_1)$$

# Shannon's Expansion Theorem (Example)

$$f(w_1, w_2, w_3) = w_1w_2 + w_1w_3 + w_2w_3$$

$$f(w_1, w_2, w_3) = w_1w_2 + w_1w_3 + w_2w_3 (\bar{w}_1 + w_1)$$

$$\begin{aligned} f &= \bar{w}_1(0 \cdot w_2 + 0 \cdot w_3 + w_2w_3) + w_1(1 \cdot w_2 + 1 \cdot w_3 + w_2w_3) \\ &= \bar{w}_1(w_2w_3) + w_1(w_2 + w_3) \end{aligned}$$

# Shannon's Expansion Theorem (In terms of more than one variable)

$$f(w_1, \dots, w_n) = \bar{w}_1 \bar{w}_2 \cdot f(0, 0, w_3, \dots, w_n) + \bar{w}_1 w_2 \cdot f(0, 1, w_3, \dots, w_n) \\ + w_1 \bar{w}_2 \cdot f(1, 0, w_3, \dots, w_n) + w_1 w_2 \cdot f(1, 1, w_3, \dots, w_n)$$

This form is suitable for implementation with a 4x1 multiplexer.

# **Another Example**

**Factor and implement the following function with a 2x1 multiplexer**


$$f = \bar{w}_1 \bar{w}_3 + w_1 w_2 + w_1 w_3$$

# Factor and implement the following function with a 2x1 multiplexer

$$f = \bar{w}_1 \bar{w}_3 + w_1 w_2 + w_1 w_3$$

$$\begin{aligned} f &= \bar{w}_1 f_{\bar{w}_1} + w_1 f_{w_1} \\ &= \bar{w}_1 (\bar{w}_3) + w_1 (w_2 + w_3) \end{aligned}$$
 
# Factor and implement the following function with a 2x1 multiplexer



$$\begin{aligned} f &= \bar{w}_1 f_{\bar{w}_1} + w_1 f_{w_1} \\ &= \bar{w}_1 (\bar{w}_3) + w_1 (w_2 + w_3) \end{aligned}$$



**Factor and implement the following function with a 4x1 multiplexer**


$$f = \bar{w}_1 \bar{w}_3 + w_1 w_2 + w_1 w_3$$

# Factor and implement the following function with a 4x1 multiplexer

$$f = \bar{w}_1 \bar{w}_3 + w_1 w_2 + w_1 w_3$$

$$\begin{aligned} f &= \bar{w}_1 \bar{w}_2 f_{\bar{w}_1 \bar{w}_2} + \bar{w}_1 w_2 f_{\bar{w}_1 w_2} + w_1 \bar{w}_2 f_{w_1 \bar{w}_2} + w_1 w_2 f_{w_1 w_2} \\ &= \bar{w}_1 \bar{w}_2 (\bar{w}_3) + \bar{w}_1 w_2 (\bar{w}_3) + w_1 \bar{w}_2 (w_3) + w_1 w_2 (1) \end{aligned}$$
 
# Factor and implement the following function with a 4x1 multiplexer



$$\begin{aligned} f &= \bar{w}_1 \bar{w}_2 f_{\bar{w}_1 \bar{w}_2} + \bar{w}_1 w_2 f_{\bar{w}_1 w_2} + w_1 \bar{w}_2 f_{w_1 \bar{w}_2} + w_1 w_2 f_{w_1 w_2} \\ &= \bar{w}_1 \bar{w}_2 (\bar{w}_3) + \bar{w}_1 w_2 (\bar{w}_3) + w_1 \bar{w}_2 (w_3) + w_1 w_2 (1) \end{aligned}$$

# **Yet Another Example**

**Factor and implement the following function using only 2x1 multiplexers**

$$f = w_1w_2 + w_1w_3 + w_2w_3$$

**Factor and implement the following function using only 2x1 multiplexers**

$$f = w_1w_2 + w_1w_3 + w_2w_3$$

$$\begin{aligned} f &= \bar{w}_1(w_2w_3) + w_1(w_2 + w_3 + w_2w_3) \\ &= \bar{w}_1(w_2w_3) + w_1(w_2 + w_3) \end{aligned}$$

**Factor and implement the following function using only 2x1 multiplexers**


$$f = w_1w_2 + w_1w_3 + w_2w_3$$

$$f = \bar{w}_1(w_2w_3) + w_1(w_2 + w_3 + w_2w_3)$$

$$= \bar{w}_1(\underbrace{w_2w_3}) + w_1(\underbrace{w_2 + w_3})$$

$$g = w_2w_3 \quad h = w_2 + w_3$$

 **Factor and implement the following function using only 2x1 multiplexers**



$$f = \bar{w}_1(w_2w_3) + w_1(w_2 + w_3 + w_2w_3)$$

$$= \bar{w}_1(\underbrace{w_2w_3}) + w_1(\underbrace{w_2 + w_3})$$

$$g = w_2w_3 \quad h = w_2 + w_3$$



**Factor and implement the following function using only 2x1 multiplexers**

$$g = w_2 w_3$$

$$h = w_2 + w_3$$

**Factor and implement the following function using only 2x1 multiplexers**

$$g = w_2 w_3$$





$$g = \bar{w}_2(0) + w_2(w_3)$$

$$h = w_2 + w_3$$



$$h = \bar{w}_2(w_3) + w_2(1)$$

  
# Factor and implement the following function using only 2x1 multiplexers




$$g = \bar{w}_2(0) + w_2(w_3)$$

$$h = \bar{w}_2(w_3) + w_2(1)$$

 
# Finally, we are ready to draw the circuit


 
# Finally, we are ready to draw the circuit


 
# Finally, we are ready to draw the circuit



# Decoders

# 2-to-4 Decoder (Definition)


- Has two inputs:  $w_1$  and  $w_0$
- Has four outputs:  $y_0$  ,  $y_1$  ,  $y_2$  , and  $y_3$
- If  $w_1=0$  and  $w_0=0$ , then the output  $y_0$  is set to 1
- If  $w_1=0$  and  $w_0=1$ , then the output  $y_1$  is set to 1
- If  $w_1=1$  and  $w_0=0$ , then the output  $y_2$  is set to 1
- If  $w_1=1$  and  $w_0=1$ , then the output  $y_3$  is set to 1
- Only one output is set to 1. All others are set to 0.



# Truth Table and Graphical Symbol for a 2-to-4 Decoder

$w_1$	$w_0$	$y_0$	$y_1$	$y_2$	$y_3$
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

(a) Truth table

 


(b) Graphical symbol

# Truth Table and Graphical Symbol for a 2-to-4 Decoder

$w_1$	$w_0$	$y_0$	$y_1$	$y_2$	$y_3$
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1


The outputs are “one-hot” encoded

(a) Truth table

 


(b) Graphical symbol

# The Logic Circuit for a 2-to-4 Decoder

 


[ Figure 4.13c from the textbook ]

# The Logic Circuit for a 2-to-4 Decoder

 


[ Figure 4.13c from the textbook ]

# The Logic Circuit for a 2-to-4 Decoder

 


[ Figure 4.13c from the textbook ]

# The Logic Circuit for a 2-to-4 Decoder

 


[ Figure 4.13c from the textbook ]

# The Logic Circuit for a 2-to-4 Decoder

 

[ Figure 4.13c from the textbook ]


# The Logic Circuit for a 2-to-4 Decoder

 

[ Figure 4.13c from the textbook ]




# The Logic Circuit for a 2-to-4 Decoder

 


[ Figure 4.13c from the textbook ]

# Adding an Enable Input

 


[ Figure 4.13c from the textbook ]

# Adding an Enable Input

 


[ Figure 4.13c from the textbook ]

# Adding an Enable Input

 

When  $En=1$  this circuit behaves like the one without enable.

# Adding an Enable Input

 


When  $En=0$  all outputs are set to 0 and the decoder is disabled.

# Truth Table and Graphical Symbol for a 2-to-4 Decoder with an Enable Input

$En$	$w_1$	$w_0$	$y_0$	$y_1$	$y_2$	$y_3$
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1
0	x	x	0	0	0	0

(a) Truth table

 


(b) Graphical symbol

# Truth Table and Graphical Symbol for a 2-to-4 Decoder with an Enable Input

$En$	$w_1$	$w_0$	$y_0$	$y_1$	$y_2$	$y_3$
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1
0	x	x	0	0	0	0


(a) Truth table

 

(b) Graphical symbol

x indicates that it does not matter what the value of this variable is for this row of the truth table
 
# Graphical Symbol for a Binary $n$ -to- $2^n$ Decoder with an Enable Input



(d) An  $n$ -to- $2^n$  decoder

A binary decoder with  $n$  inputs has  $2^n$  outputs


The outputs of an enabled binary decoder are “one-hot” encoded, meaning that only a single bit is set to 1, i.e., it is *hot*.



# How can we build larger decoders?


- 3-to-8 ?
- 4-to-16?
- 5-to-??

# Hint: How did we build a 16-1 Multiplexer

 


[ Figure 4.4 from the textbook ]
 
# A 3-to-8 decoder using two 2-to-4 decoders



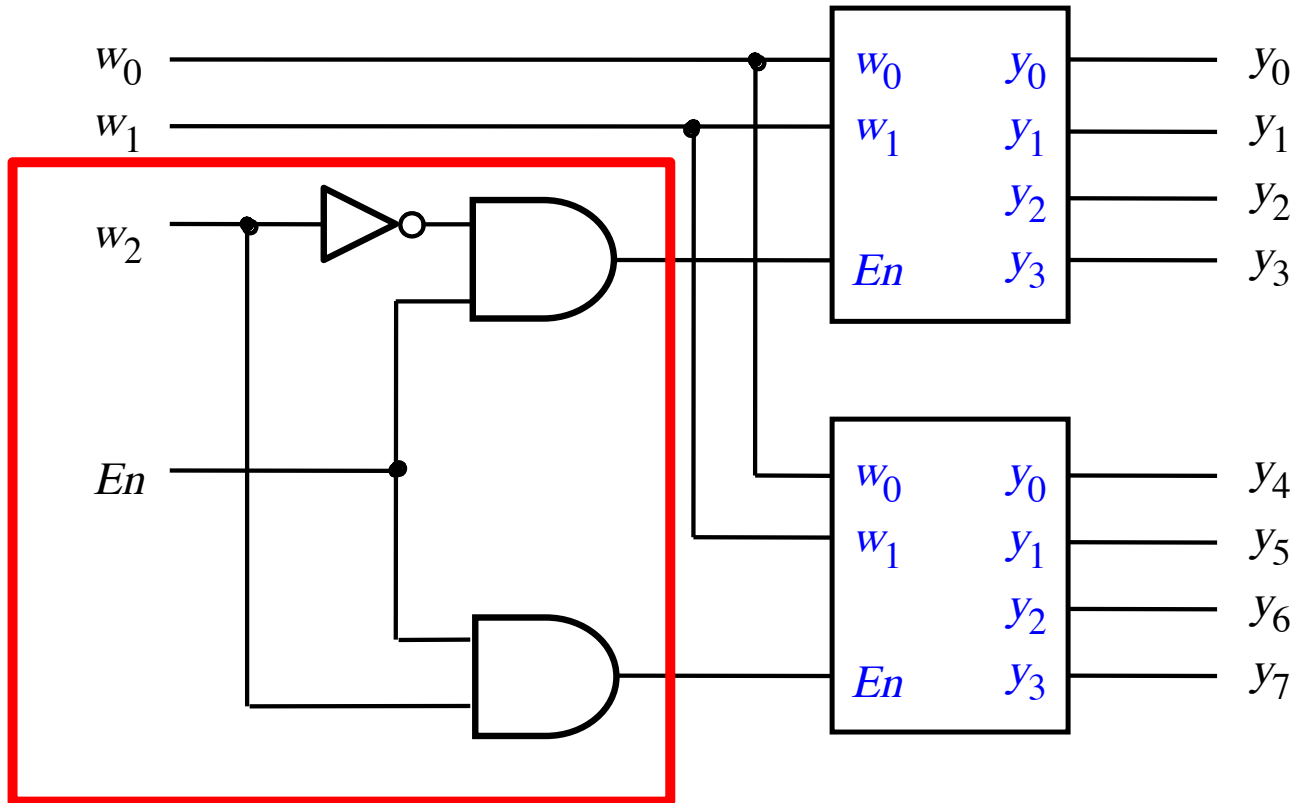
# A 3-to-8 decoder using two 2-to-4 decoders




What is this?

# What is this?

 


# What is this?

 


This is a 1-to-2 decoder with an enable input.
 
# A 3-to-8 decoder using two 2-to-4 decoders



 
# A 3-to-8 decoder using two 2-to-4 decoders






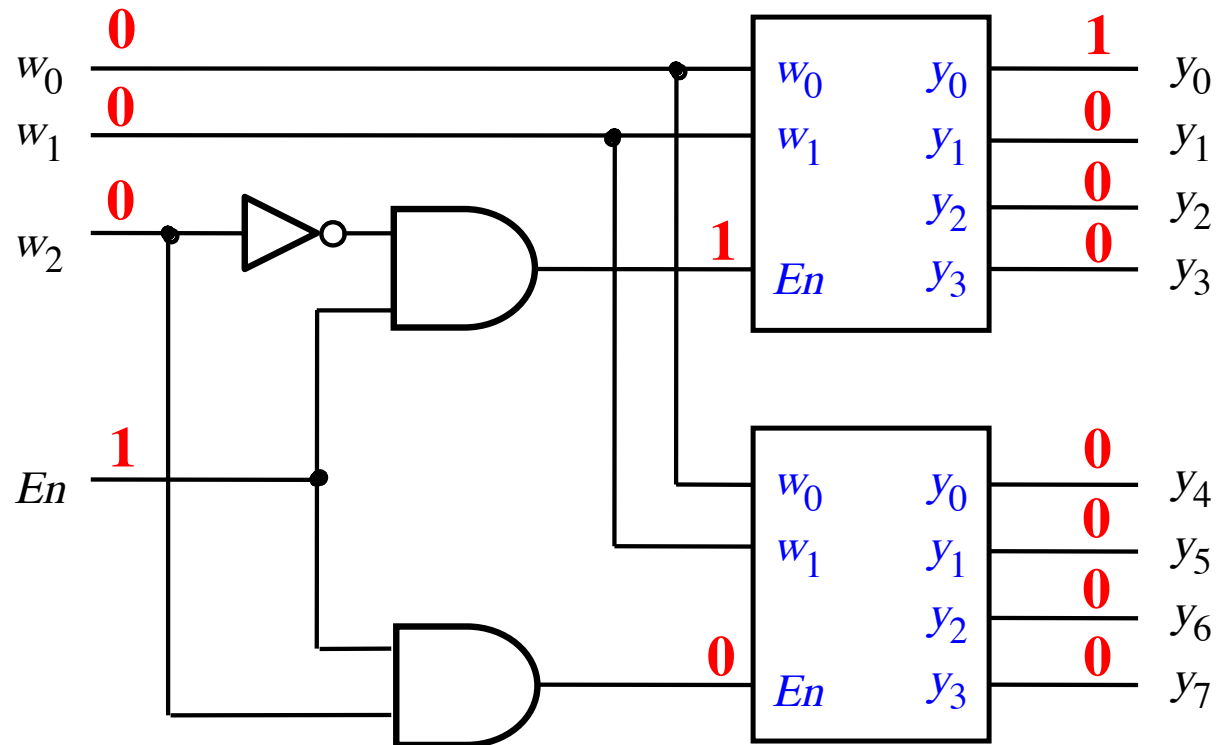
# A 3-to-8 decoder using two 2-to-4 decoders



 
# A 3-to-8 decoder using two 2-to-4 decoders



 
# A 3-to-8 decoder using two 2-to-4 decoders



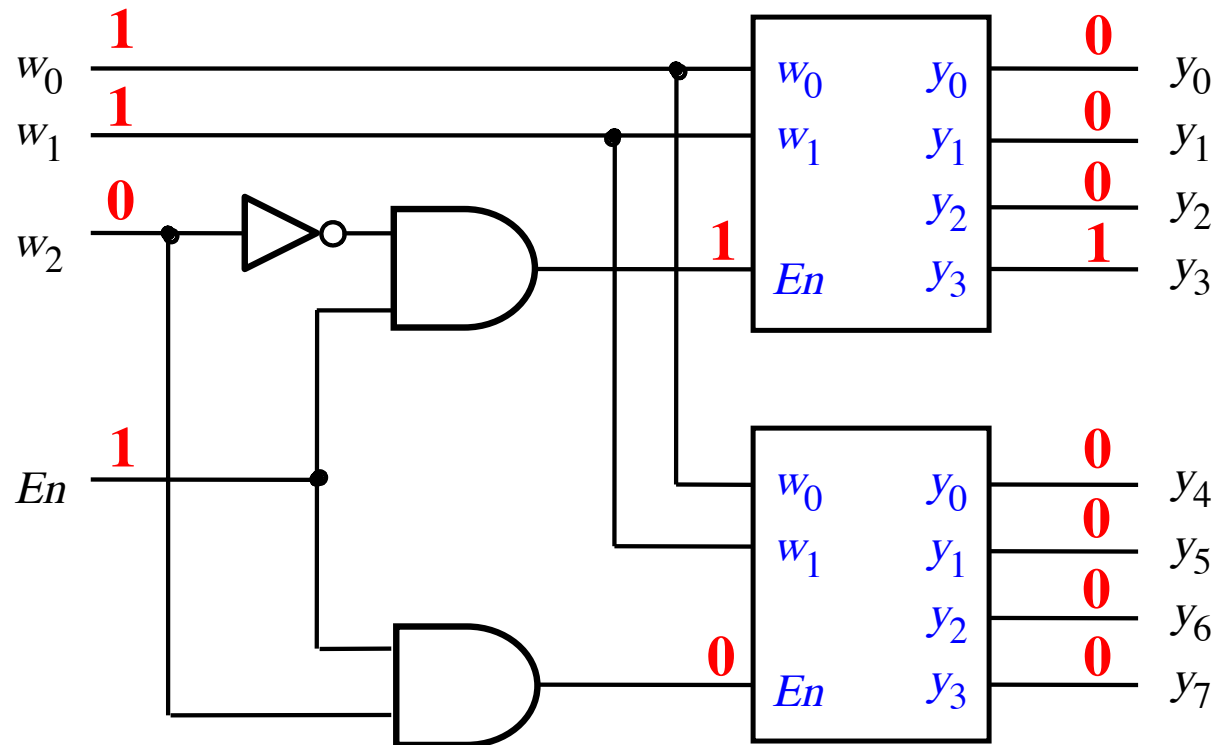
# A 3-to-8 decoder using two 2-to-4 decoders



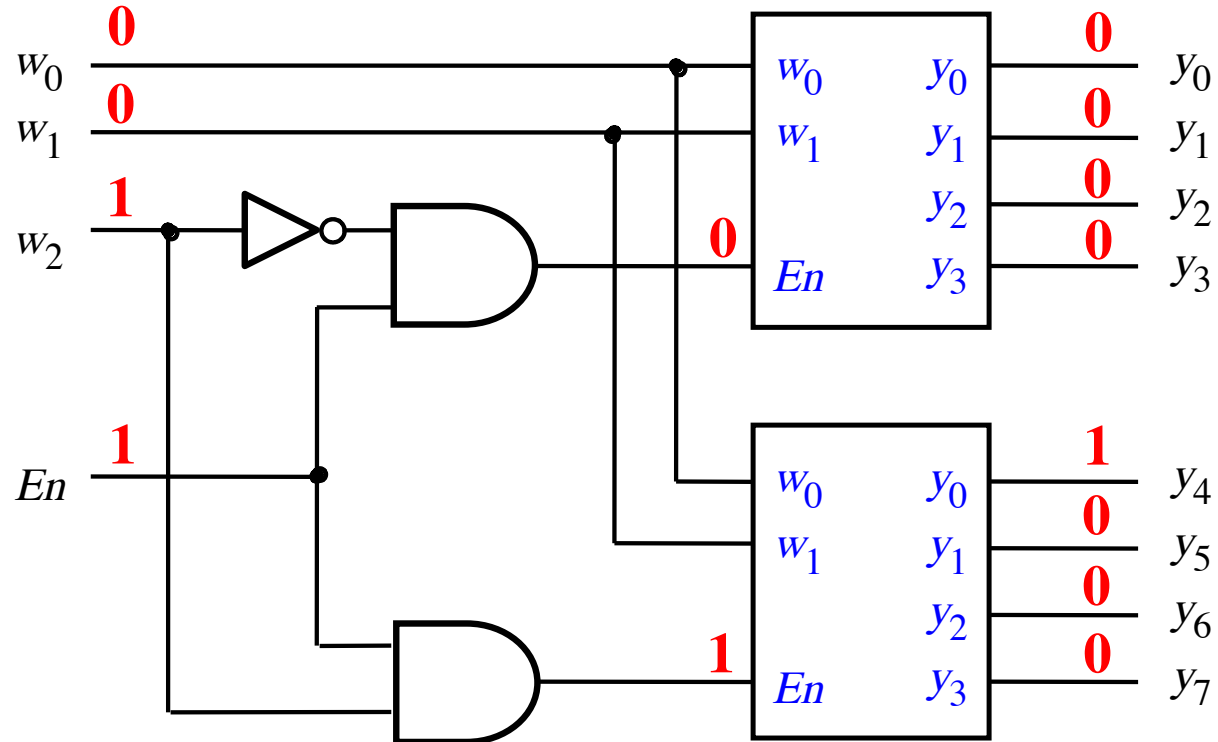
# A 3-to-8 decoder using two 2-to-4 decoders



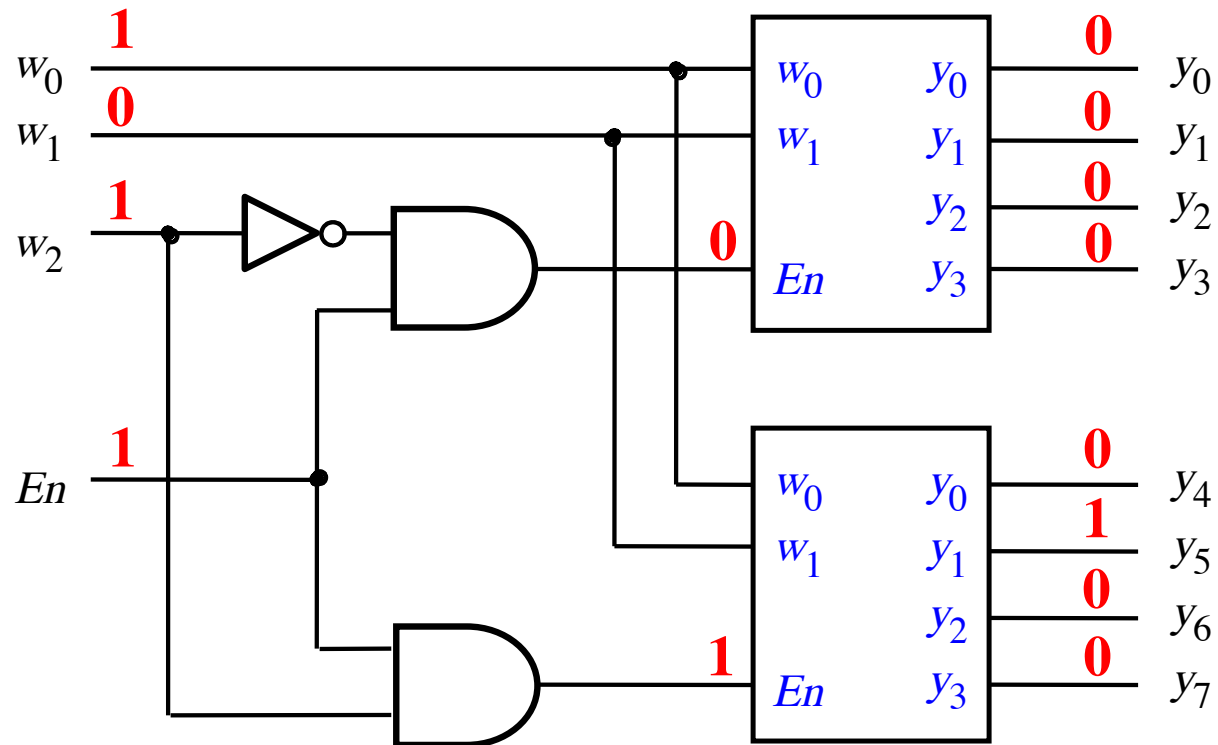
# A 3-to-8 decoder using two 2-to-4 decoders


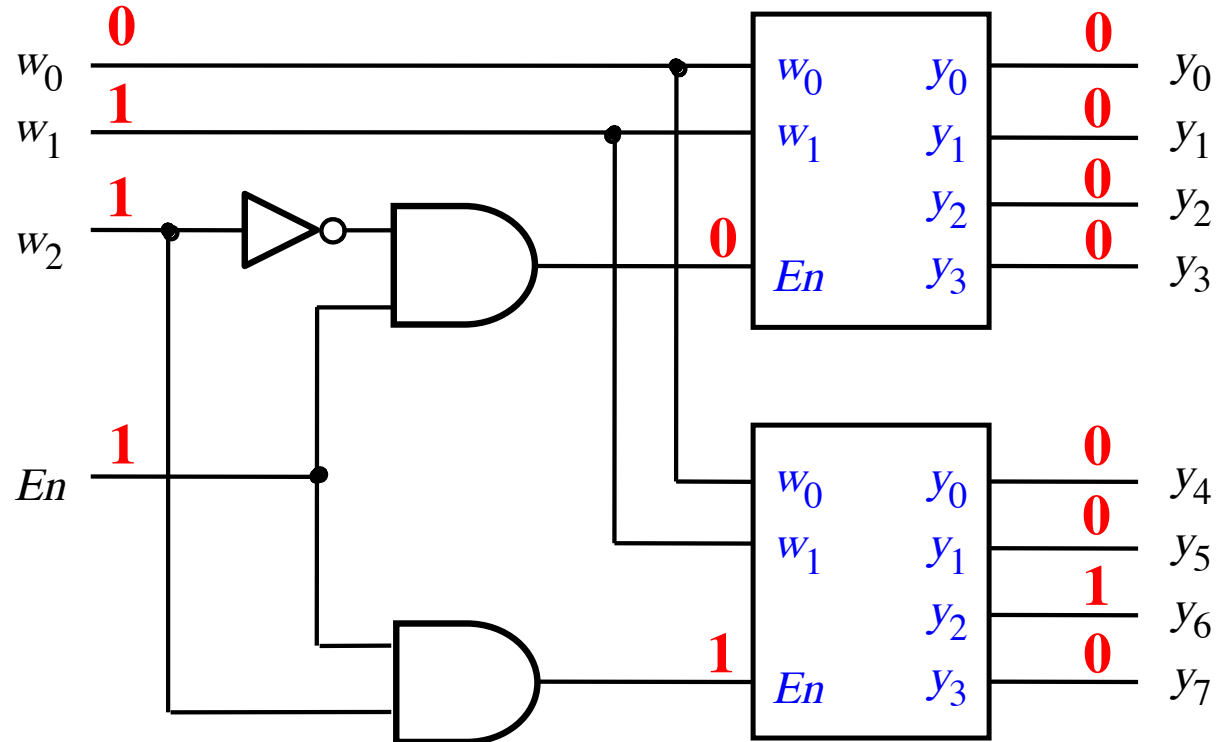
# A 3-to-8 decoder using two 2-to-4 decoders



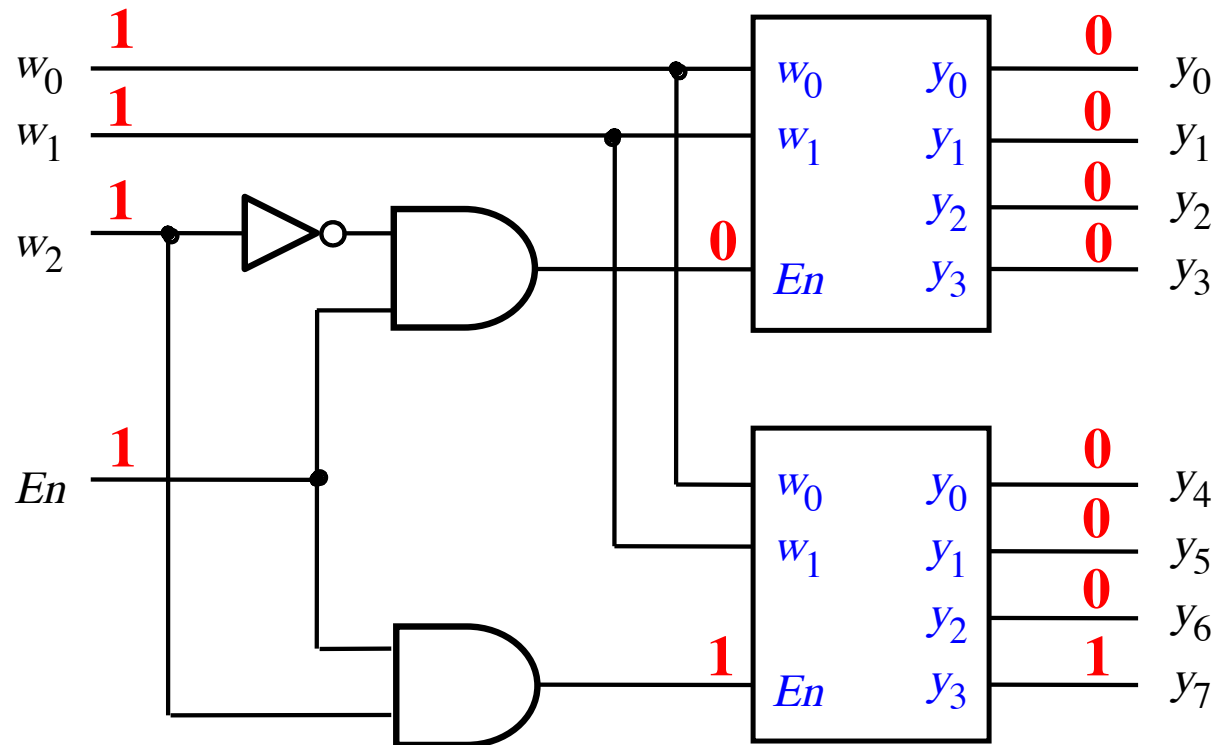
# A 3-to-8 decoder using two 2-to-4 decoders







# A 4-to-16 decoder built using a decoder tree

 


[ Figure 4.16 from the textbook ]


# Let's build a 5-to-32 decoder

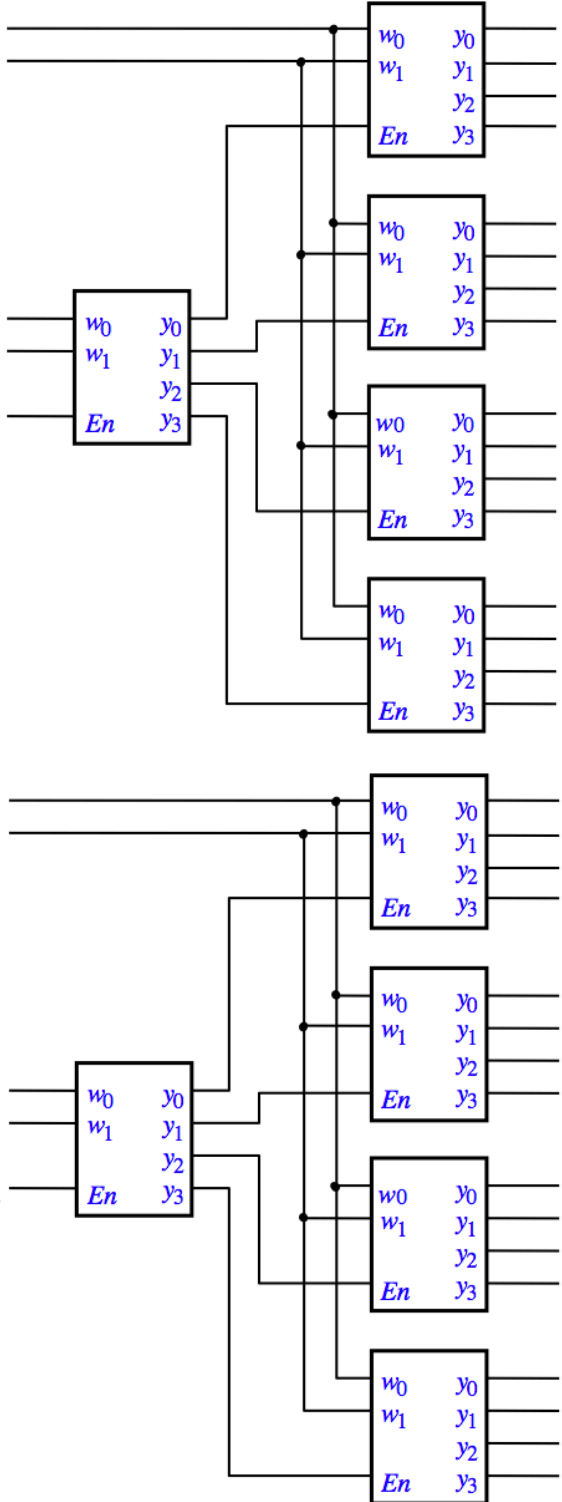 

# Let's build a 5-to-32 decoder

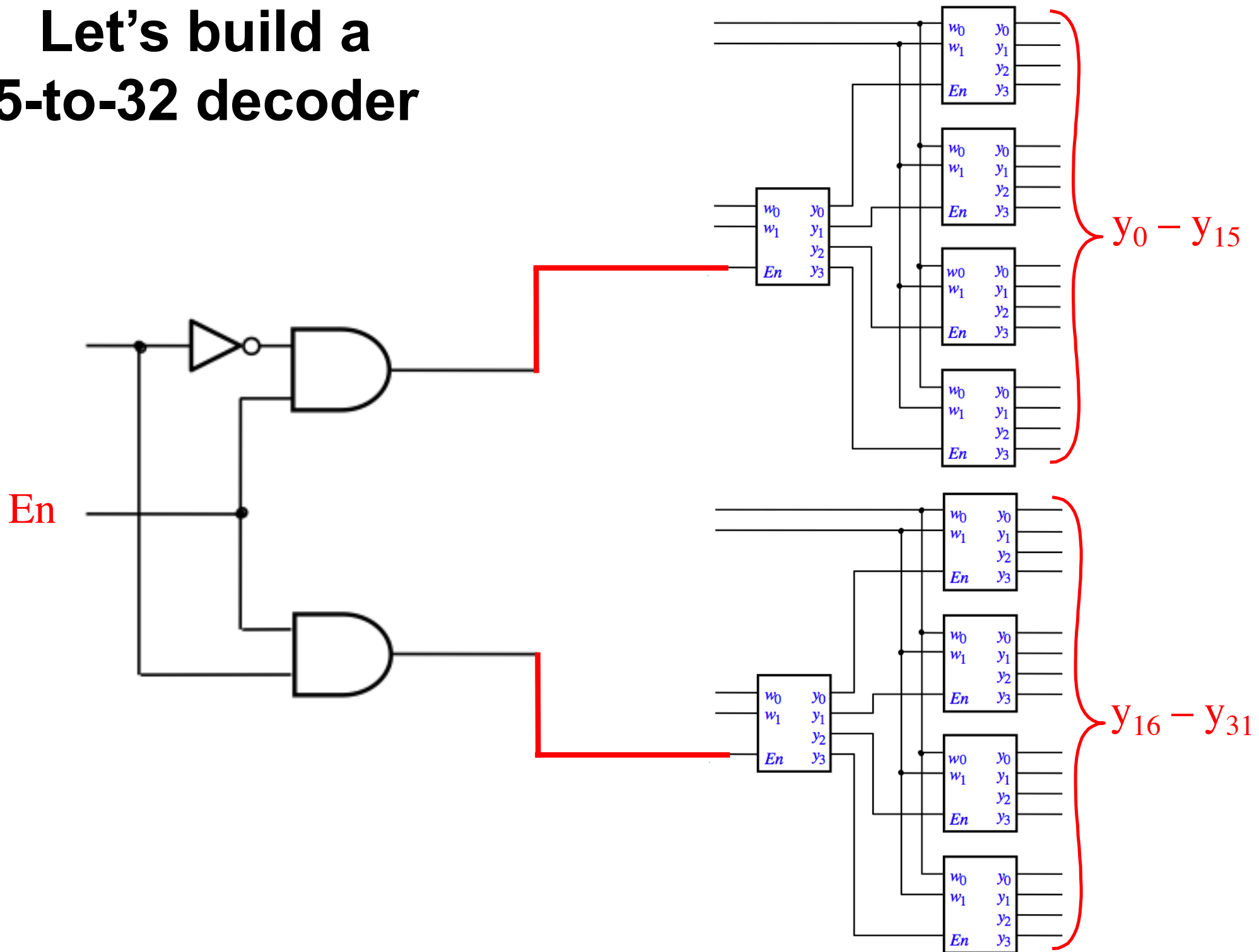

# Let's build a 5-to-32 decoder

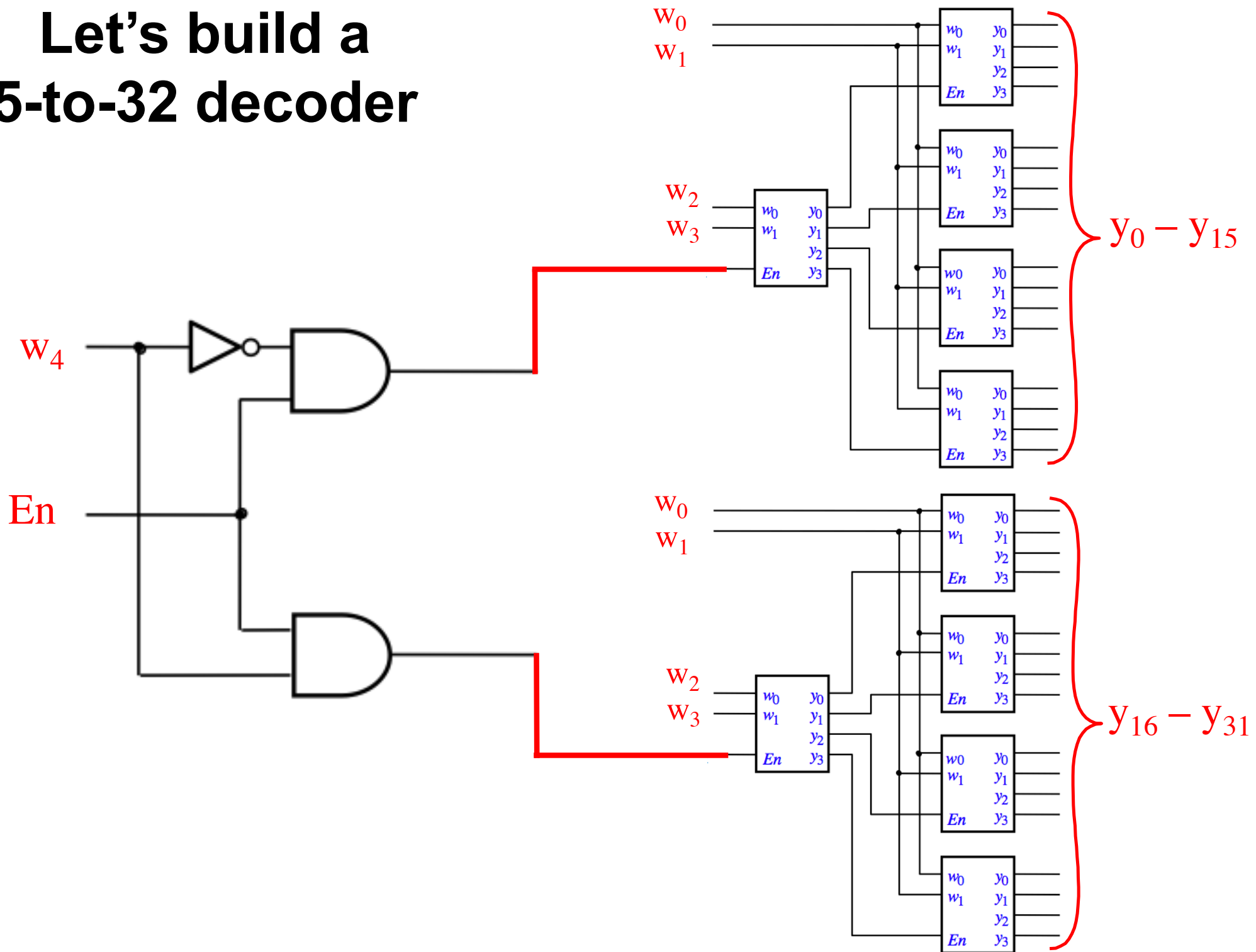


# Demultiplexers

# 1-to-4 Demultiplexer (Definition)


- Has one data input line:  $D$
- Has two output select lines:  $w_1$  and  $w_0$
- Has four outputs:  $y_0$ ,  $y_1$ ,  $y_2$ , and  $y_3$
- If  $w_1=0$  and  $w_0=0$ , then the output  $y_0$  is set to  $D$
- If  $w_1=0$  and  $w_0=1$ , then the output  $y_1$  is set to  $D$
- If  $w_1=1$  and  $w_0=0$ , then the output  $y_2$  is set to  $D$
- If  $w_1=1$  and  $w_0=1$ , then the output  $y_3$  is set to  $D$
- Only one output is set to  $D$ . All others are set to 0.
 
# A 1-to-4 demultiplexer built with a 2-to-4 decoder



# A 1-to-4 demultiplexer built with a 2-to-4 decoder

output  
select  
lines

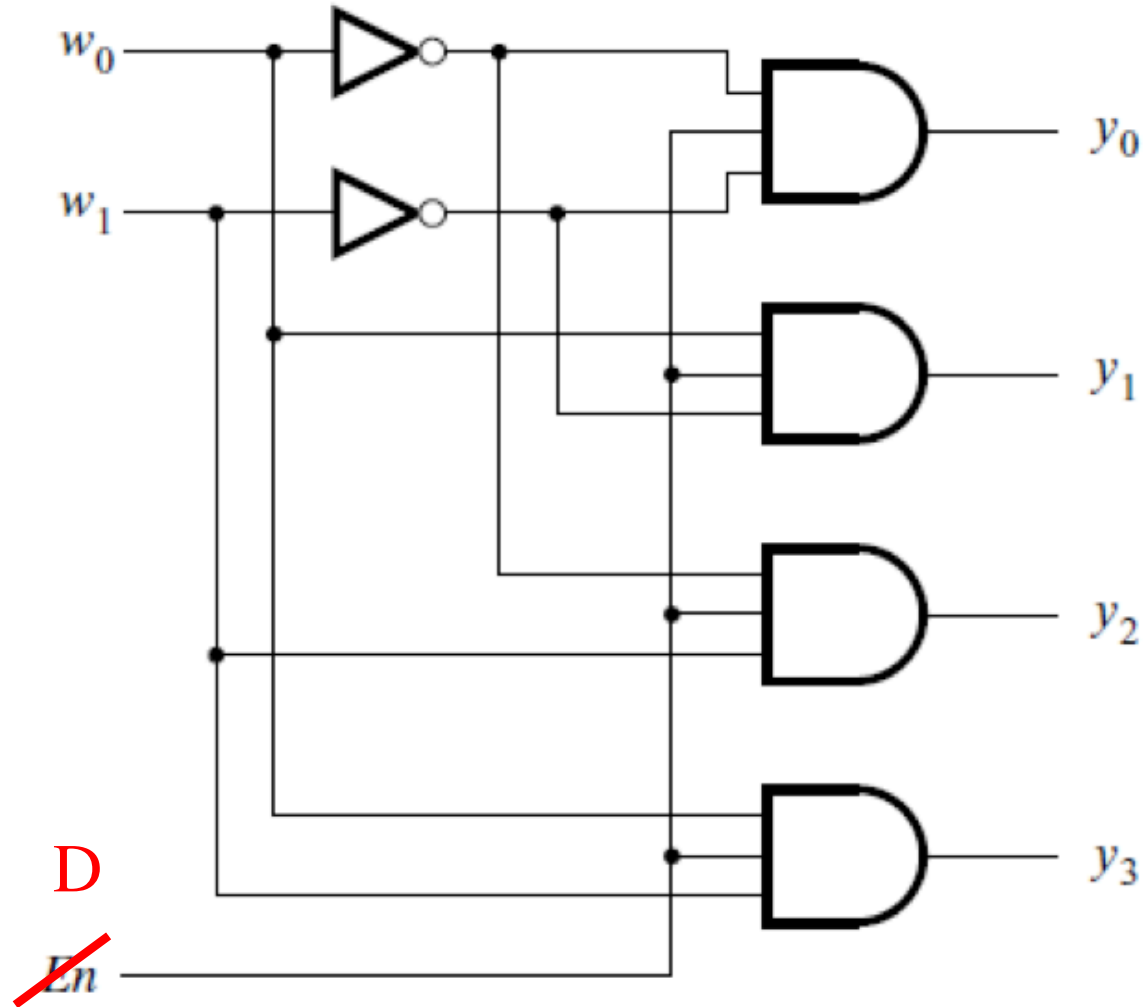

the  
four  
output  
lines


data  
input  
line




# **Multiplexers**

## **(Implemented with Decoders)**

 
# A 4-to-1 multiplexer built using a 2-to-4 decoder



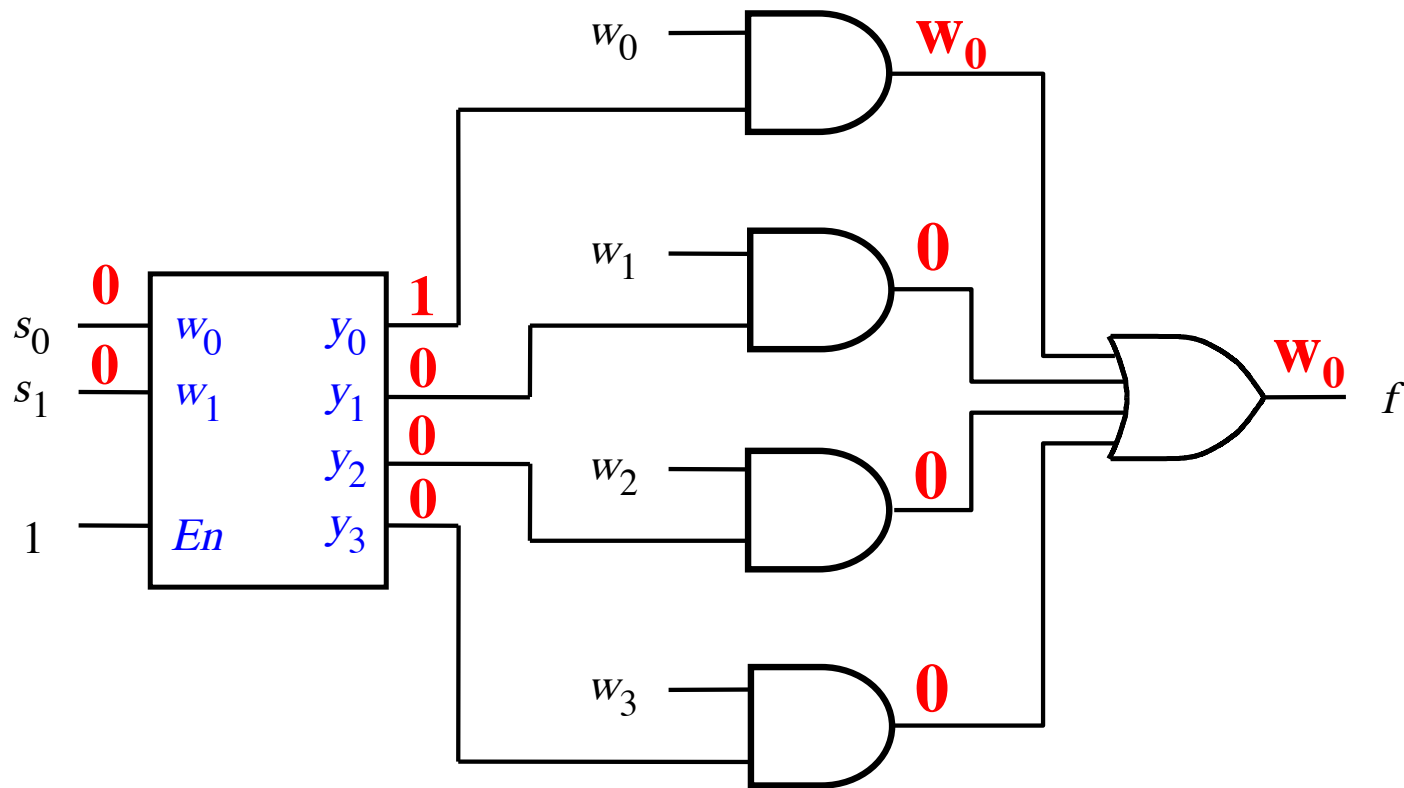
# A 4-to-1 multiplexer built using a 2-to-4 decoder



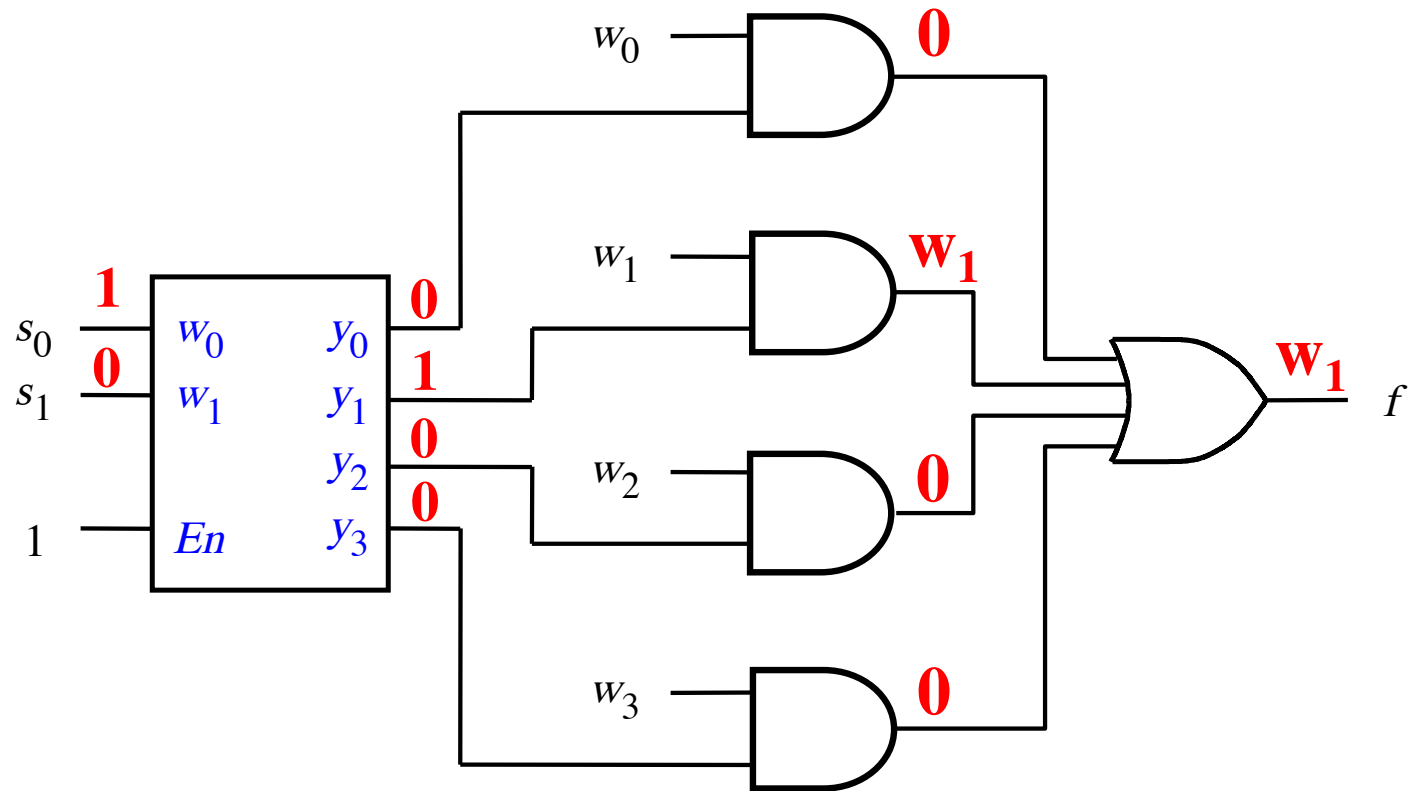
# A 4-to-1 multiplexer built using a 2-to-4 decoder


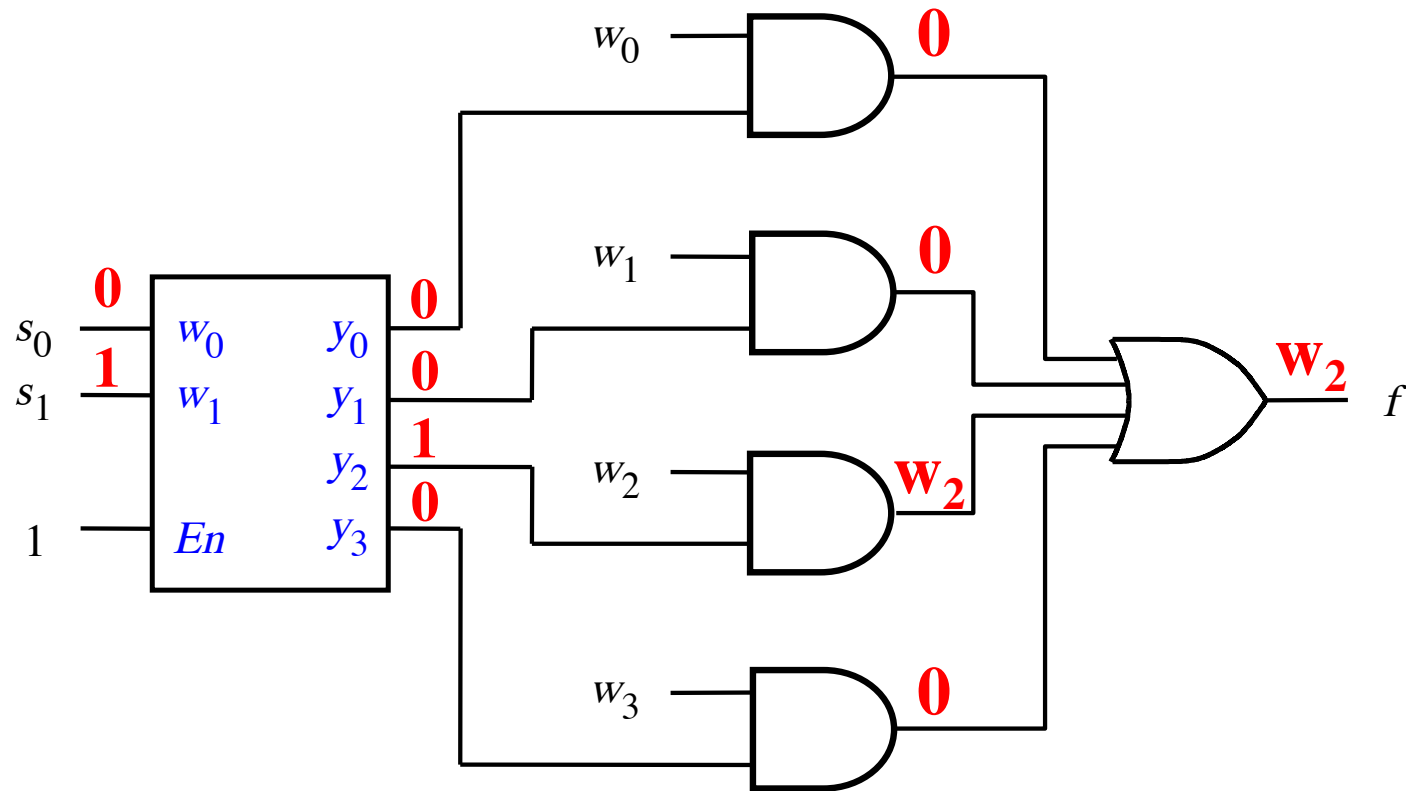
# A 4-to-1 multiplexer built using a 2-to-4 decoder


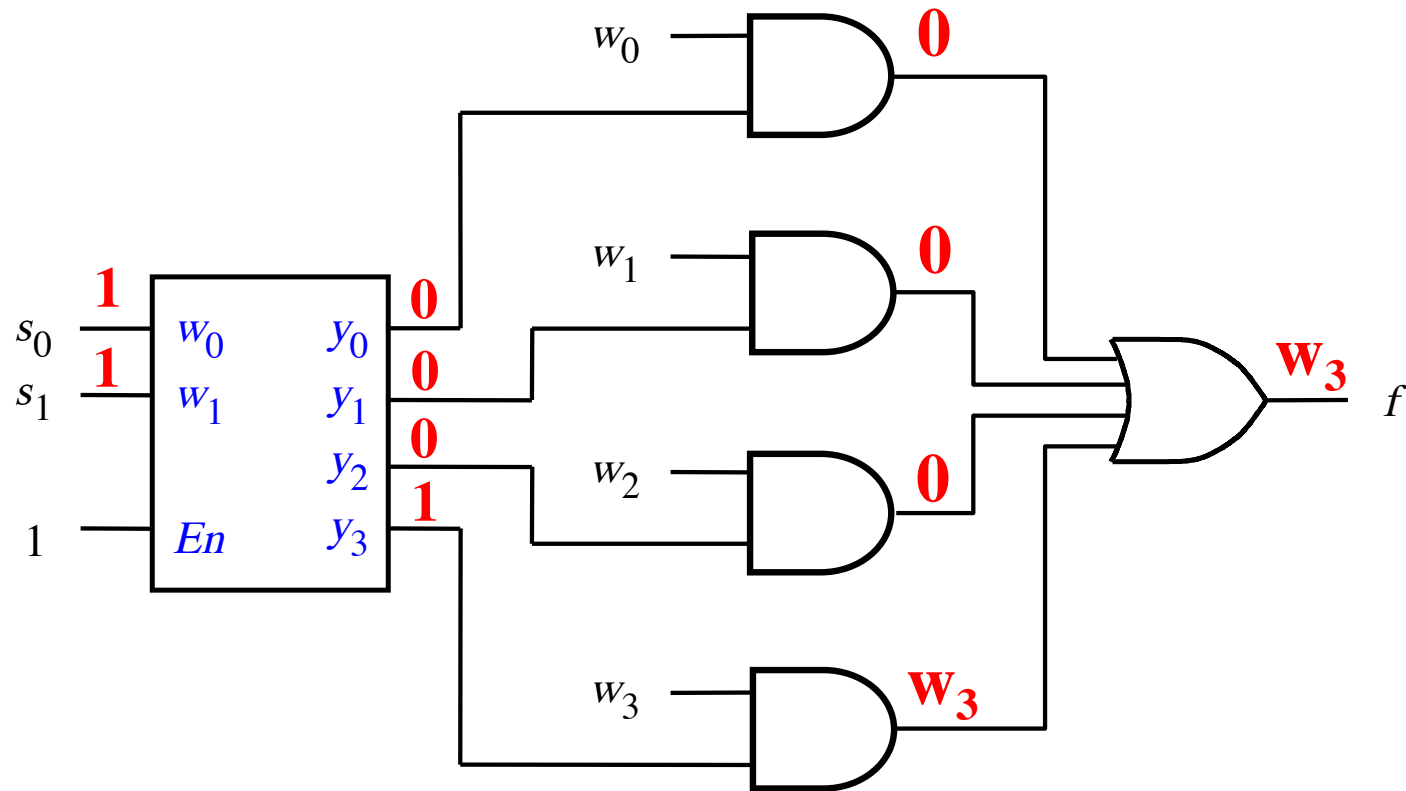
# A 4-to-1 multiplexer built using a 2-to-4 decoder



# Encoders

# Binary Encoders



# 4-to-2 Binary Encoder (Definition)

- Has four inputs:  $w_3$  ,  $w_2$  ,  $w_1$  , and  $w_0$
- Has two outputs:  $y_1$  and  $y_0$
- Only one input is set to 1 (“one-hot” encoded). All others are set to 0.
- If  $w_0=1$  then  $y_1=0$  and  $y_0=0$
- If  $w_1=1$  then  $y_1=0$  and  $y_0=1$
- If  $w_2=1$  then  $y_1=1$  and  $y_0=0$
- If  $w_3=1$  then  $y_1=1$  and  $y_0=1$

# Truth table for a 4-to-2 binary encoder

$w_3$	$w_2$	$w_1$	$w_0$	$y_1$	$y_0$
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1


# Truth table for a 4-to-2 binary encoder

$w_3$	$w_2$	$w_1$	$w_0$	$y_1$	$y_0$
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

The inputs are “one-hot” encoded


# Circuit for a 4-to-2 binary encoder

$w_3$	$w_2$	$w_1$	$w_0$	$y_1$	$y_0$
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

 


# Circuit for a 4-to-2 binary encoder

$w_3$	$w_2$	$w_1$	$w_0$	$y_1$	$y_0$
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

 


# Circuit for a 4-to-2 binary encoder

$w_3$	$w_2$	$w_1$	$w_0$	$y_1$	$y_0$
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

 


# Circuit for a 4-to-2 binary encoder

$w_3$	$w_2$	$w_1$	$w_0$	$y_1$	$y_0$
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

 

# Circuit for a 4-to-2 binary encoder


$w_3$	$w_2$	$w_1$	$w_0$	$y_1$	$y_0$
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

 




# Circuit for a 4-to-2 binary encoder

$w_3$	$w_2$	$w_1$	$w_0$	$y_1$	$y_0$
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

 


# Circuit for a 4-to-2 binary encoder

$w_3$	$w_2$	$w_1$	$w_0$	$y_1$	$y_0$
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

 

# A $2^n$ -to- $n$ binary encoder

 

# Priority Encoders

# Truth table for a 4-to-2 priority encoder (abbreviated version)

$w_3$	$w_2$	$w_1$	$w_0$	$y_1$	$y_0$	$z$
0	0	0	0	d	d	0
0	0	0	1	0	0	1
0	0	1	x	0	1	1
0	1	x	x	1	0	1
1	x	x	x	1	1	1

# Truth table for a 4-to-2 priority encoder (abbreviated version)

$w_3$	$w_2$	$w_1$	$w_0$	$y_1$	$y_0$	$z$
0	0	0	0	d	d	0
0	0	0	1	0	0	1
0	0	1	x	0	1	1
0	1	x	x	1	0	1
1	x	x	x	1	1	1

# Truth table for a 4-to-2 priority encoder

	$w_3$	$w_2$	$w_1$	$w_0$	$y_1$	$y_0$	$z$
0 0 0 0	0	0	0	0	d	d	0
0 0 0 1	0	0	0	1	0	0	1
0 0 1 x	0	0	1	0	0	1	1
	0	0	1	1	0	1	1
0 1 x x	0	1	0	0	1	0	1
	0	1	0	1	1	0	1
	0	1	1	0	1	0	1
	0	1	1	1	1	0	1
1 x x x	1	0	0	0	1	1	1
	1	0	0	1	1	1	1
	1	0	1	0	1	1	1
	1	0	1	1	1	1	1
	1	1	0	0	1	1	1
	1	1	0	1	1	1	1
	1	1	1	0	1	1	1
	1	1	1	1	1	1	1

# Expressions for 4-to-2 priority encoder

$w_3$	$w_2$	$w_1$	$w_0$	$y_1$	$y_0$	$z$
0	0	0	0	d	d	0
0	0	0	1	0	0	1
0	0	1	0	0	1	1
0	0	1	1	0	1	1
0	1	0	0	1	0	1
0	1	0	1	1	0	1
0	1	1	0	1	0	1
0	1	1	1	1	0	1
1	0	0	0	1	1	1
1	0	0	1	1	1	1
1	0	1	0	1	1	1
1	0	1	1	1	1	1
1	1	0	0	1	1	1
1	1	0	1	1	1	1
1	1	1	0	1	1	1
1	1	1	1	1	1	1

		$w_3 w_2$			
		00	01	11	10
$w_1 w_0$	00	d	1	1	1
	01	0	1	1	1
	11	0	1	1	1
	10	0	1	1	1

$$y_1 = w_3 + w_2$$



# Expressions for 4-to-2 priority encoder

$w_3$	$w_2$	$w_1$	$w_0$	$y_1$	$y_0$	$z$
0	0	0	0	d	d	0
0	0	0	1	0	0	1
0	0	1	0	0	1	1
0	0	1	1	0	1	1
0	1	0	0	1	0	1
0	1	0	1	1	0	1
0	1	1	0	1	0	1
0	1	1	1	1	0	1
1	0	0	0	1	1	1
1	0	0	1	1	1	1
1	0	1	0	1	1	1
1	0	1	1	1	1	1
1	1	0	0	1	1	1
1	1	0	1	1	1	1
1	1	1	0	1	1	1
1	1	1	1	1	1	1

$w_3 \ w_2$	$w_1 \ w_0$	00	01	11	10
00	00	d	0	1	1
00	01	0	0	1	1
00	11	1	0	1	1
00	10	1	0	1	1

$$y_0 = w_3 + w_1 \overline{w_2}$$


# Expressions for 4-to-2 priority encoder

$w_3$	$w_2$	$w_1$	$w_0$	$y_1$	$y_0$	$z$
0	0	0	0	d	d	0
0	0	0	1	0	0	1
0	0	1	0	0	1	1
0	0	1	1	0	1	1
0	1	0	0	1	0	1
0	1	0	1	1	0	1
0	1	1	0	1	0	1
0	1	1	1	1	0	1
1	0	0	0	1	1	1
1	0	0	1	1	1	1
1	0	1	0	1	1	1
1	0	1	1	1	1	1
1	1	0	0	1	1	1
1	1	0	1	1	1	1
1	1	1	0	1	1	1
1	1	1	1	1	1	1

		$w_3 w_2$			
		00	01	11	10
$w_1 w_0$	00	0	1	1	1
	01	1	1	1	1
	11	1	1	1	1
	10	1	1	1	1

$$Z = w_3 + w_2 + w_1 + w_0$$
 
# Circuit for the 4-to-2 priority encoder



# The textbook derives a different circuit for the 4-to-2 priority encoder using a 4-to-2 binary encoder

$w_3$	$w_2$	$w_1$	$w_0$	$y_1$	$y_0$	$z$
0	0	0	0	d	d	0
0	0	0	1	0	0	1
0	0	1	x	0	1	1
0	1	x	x	1	0	1
1	x	x	x	1	1	1

$$i_0 = \bar{w}_3 \bar{w}_2 \bar{w}_1 w_0$$

$$i_1 = \bar{w}_3 \bar{w}_2 w_1$$

$$i_2 = \bar{w}_3 w_2$$

$$i_3 = w_3$$

$$y_0 = i_1 + i_3$$

$$y_1 = i_2 + i_3$$

$$z = i_0 + i_1 + i_2 + i_3$$

# The textbook derives a different circuit for the 4-to-2 priority encoder using a 4-to-2 binary encoder

$w_3$	$w_2$	$w_1$	$w_0$	$y_1$	$y_0$	$z$
0	0	0	0	d	d	0
0	0	0	1	0	0	1
0	0	1	x	0	1	1
0	1	x	x	1	0	1
1	x	x	x	1	1	1

$$i_0 = \bar{w}_3 \bar{w}_2 \bar{w}_1 w_0$$

$$i_1 = \bar{w}_3 \bar{w}_2 w_1$$


$$i_2 = \bar{w}_3 w_2$$

$$i_3 = w_3$$

$$y_0 = i_1 + i_3$$

$$y_1 = i_2 + i_3$$

$$z = i_0 + i_1 + i_2 + i_3$$

 

# The textbook derives a different circuit for the 4-to-2 priority encoder using a 4-to-2 binary encoder

$w_3$	$w_2$	$w_1$	$w_0$	$y_1$	$y_0$	$z$
0	0	0	0	d	d	0
0	0	0	1	0	0	1
0	0	1	x	0	1	1
0	1	x	x	1	0	1
1	x	x	x	1	1	1

$$i_0 = \bar{w}_3 \bar{w}_2 \bar{w}_1 w_0$$

$$i_1 = \bar{w}_3 \bar{w}_2 w_1$$


$$i_2 = \bar{w}_3 w_2$$

$$i_3 = w_3$$

$$y_0 = i_1 + i_3$$

$$y_1 = i_2 + i_3$$

$$z = i_0 + i_1 + i_2 + i_3$$

 

# The textbook derives a different circuit for the 4-to-2 priority encoder using a 4-to-2 binary encoder

$w_3$	$w_2$	$w_1$	$w_0$	$y_1$	$y_0$	$z$
0	0	0	0	d	d	0
0	0	0	1	0	0	1
0	0	1	x	0	1	1
0	1	x	x	1	0	1
1	x	x	x	1	1	1

$$i_0 = \bar{w}_3 \bar{w}_2 \bar{w}_1 w_0$$

$$i_1 = \bar{w}_3 \bar{w}_2 w_1$$


$$i_2 = \bar{w}_3 w_2$$

$$i_3 = w_3$$

$$y_0 = i_1 + i_3$$

$$y_1 = i_2 + i_3$$

$$z = i_0 + i_1 + i_2 + i_3$$

 

Try to prove that this is equivalent to the circuit that was derived above.

**Questions?**



**THE END**