



CprE 281: Digital Logic

Instructor: Alexander Stoytchev

<http://www.ece.iastate.edu/~alexs/classes/>

Registers and Counters

CprE 281: Digital Logic
Iowa State University, Ames, IA
Copyright © Alexander Stoytchev

Administrative Stuff

- **The second midterm is this Friday.**
- **Homework 8 is due today.**
- **Homework 9 is out. It is due on Mon Nov 6.**
- **No HW due next Monday**

Administrative Stuff

- **Midterm Exam #2**
- **When: Friday October 27 @ 4pm.**
- **Where: This classroom**
- **What: Chapters 1, 2, 3, 4 and 5.1-5.8**
- **The exam will be open book and open notes (you can bring up to 3 pages of handwritten notes).**


Registers

Register (Definition)


An n-bit structure consisting of flip-flops

Parallel-Access Register

1-Bit Parallel-Access Register

 


1-Bit Parallel-Access Register

 

The 2-to-1 multiplexer is used to select whether to load a new value into the D flip-flop or to retain the old value.

The output of this circuit is the Q output of the flip-flop.


1-Bit Parallel-Access Register

 


If Load = 0, then retain the old value.

If Load = 1, then load the new value from In.


2-Bit Parallel-Access Register

 

2-Bit Parallel-Access Register

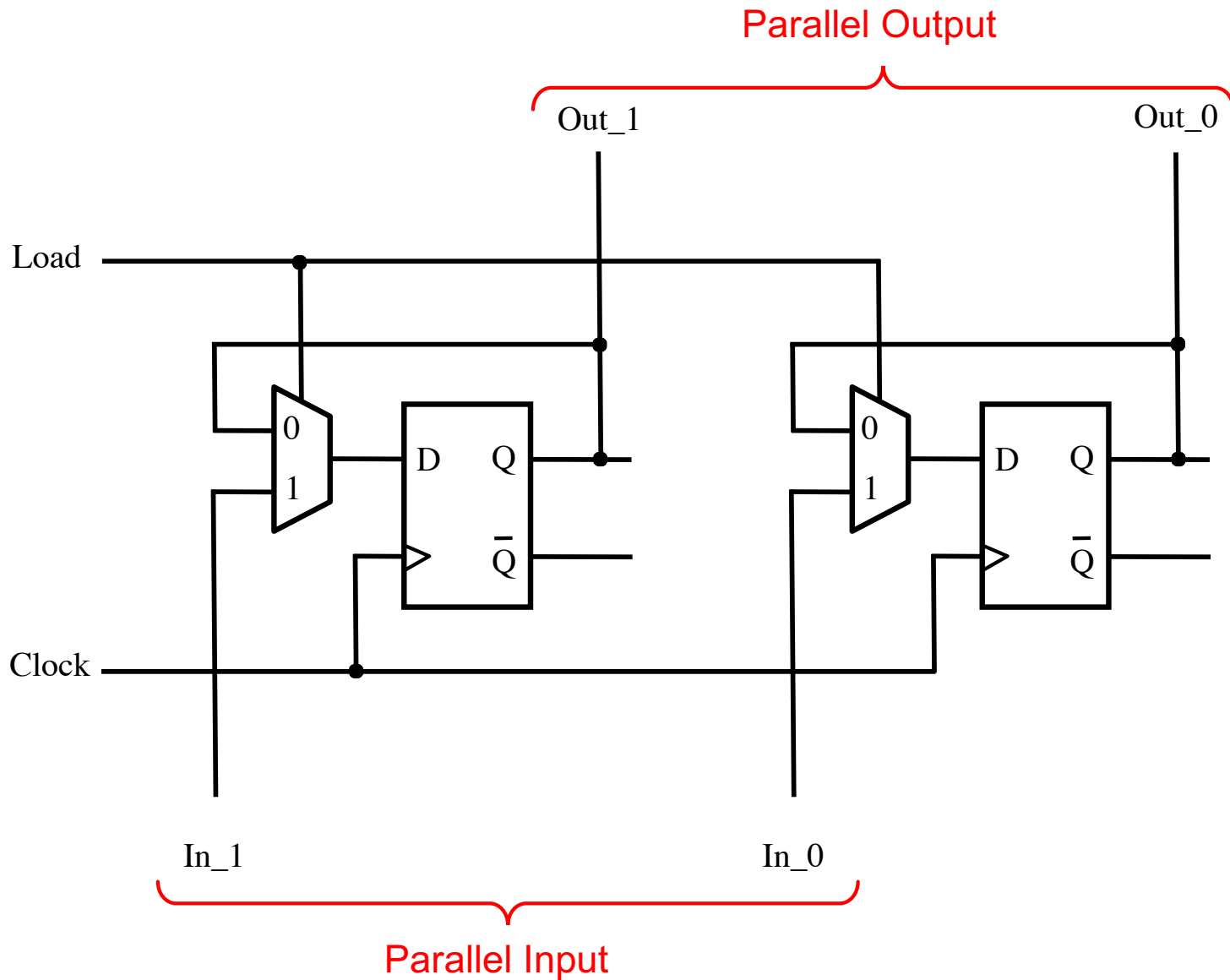


3-Bit Parallel-Access Register

 


Notice that all flip-flops are on the same clock cycle.


3-Bit Parallel-Access Register

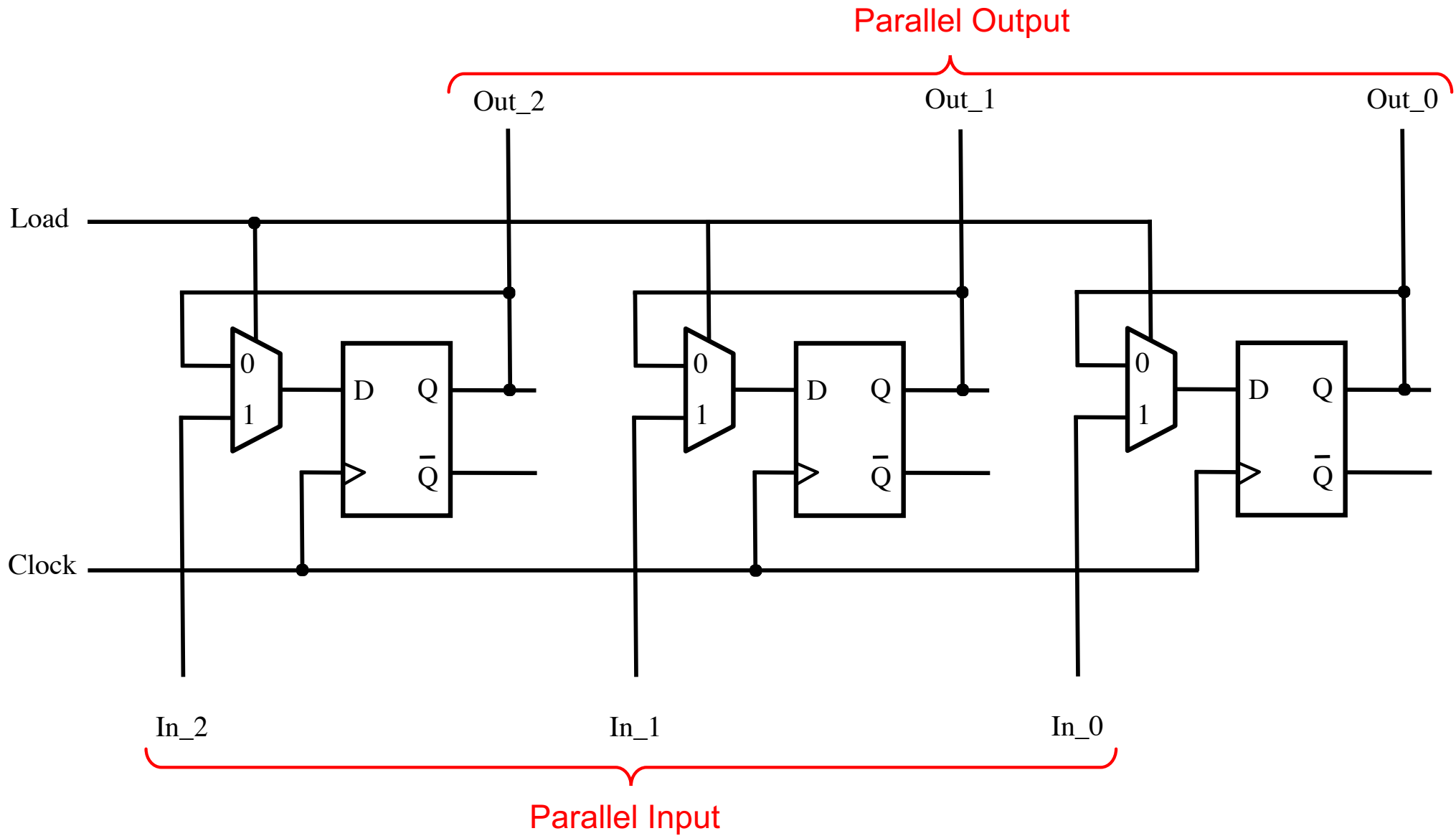

4-Bit Parallel-Access Register

 


4-Bit Parallel-Access Register

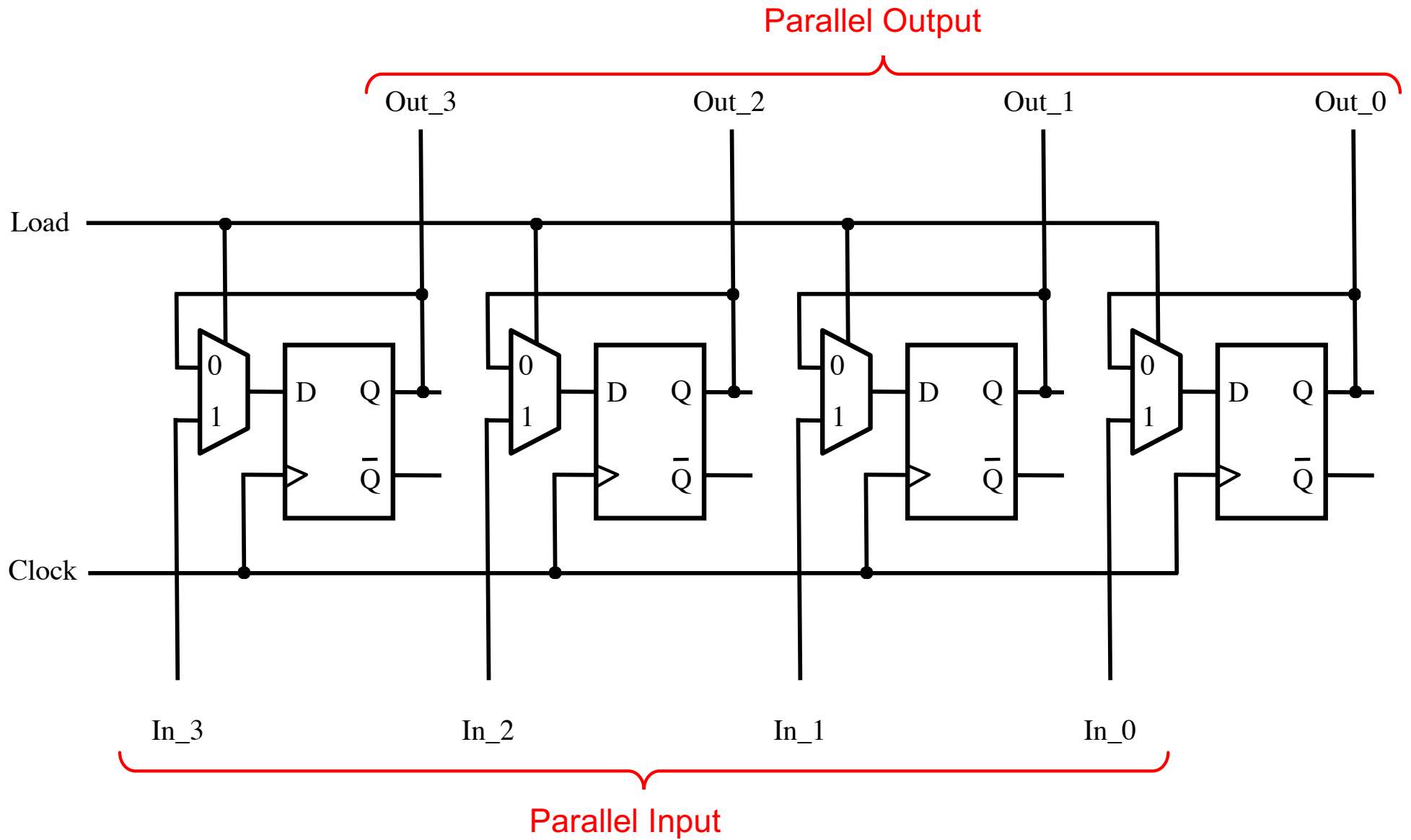


Shift Register

A simple shift register


 


A simple shift register


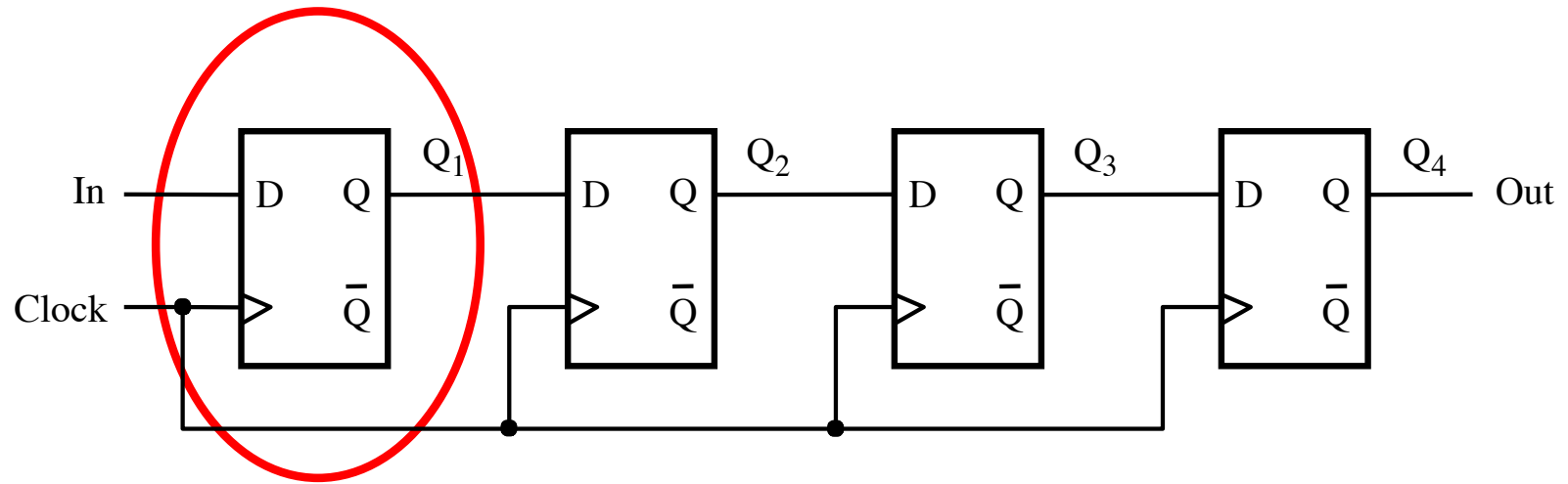


Positive-edge-triggered
D Flip-Flop


A simple shift register

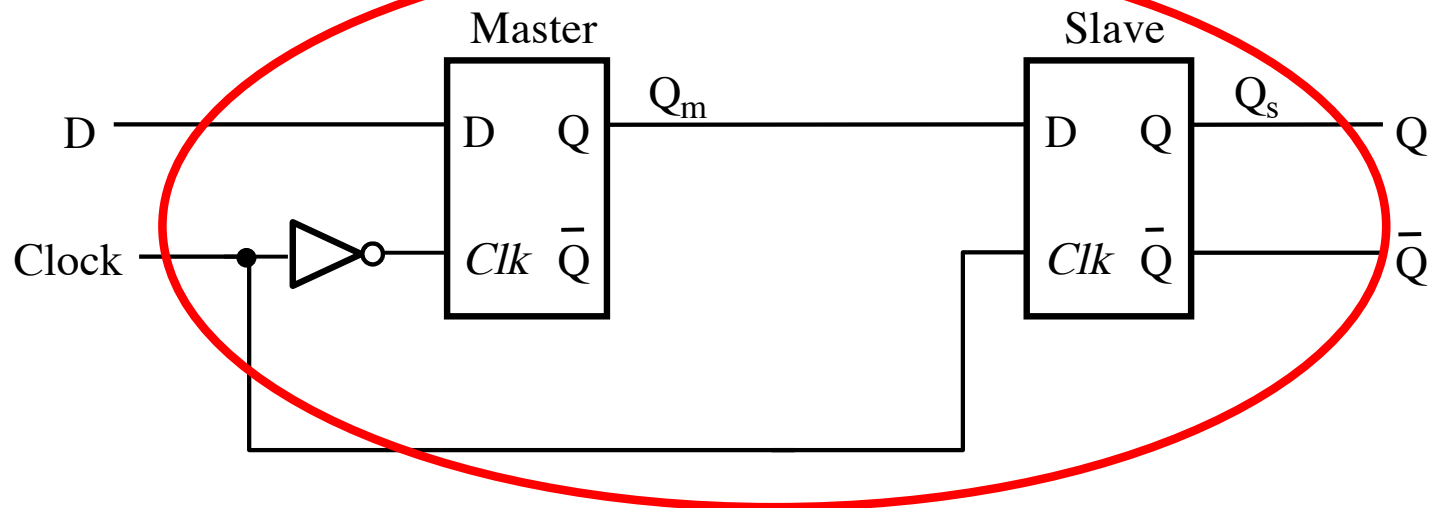 



A simple shift register

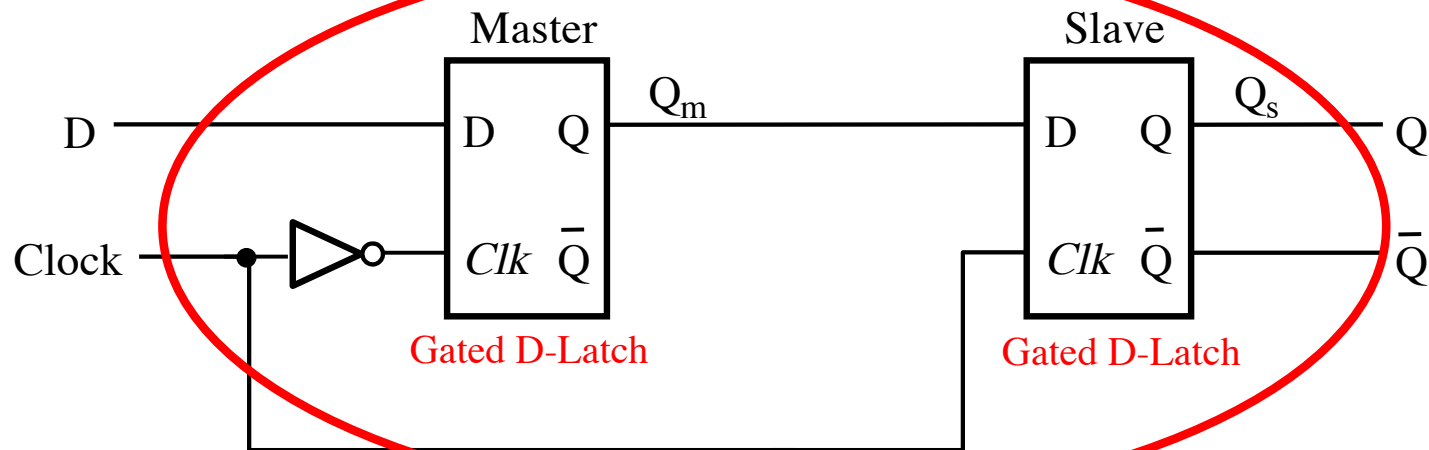 



A simple shift register

 



A simple shift register

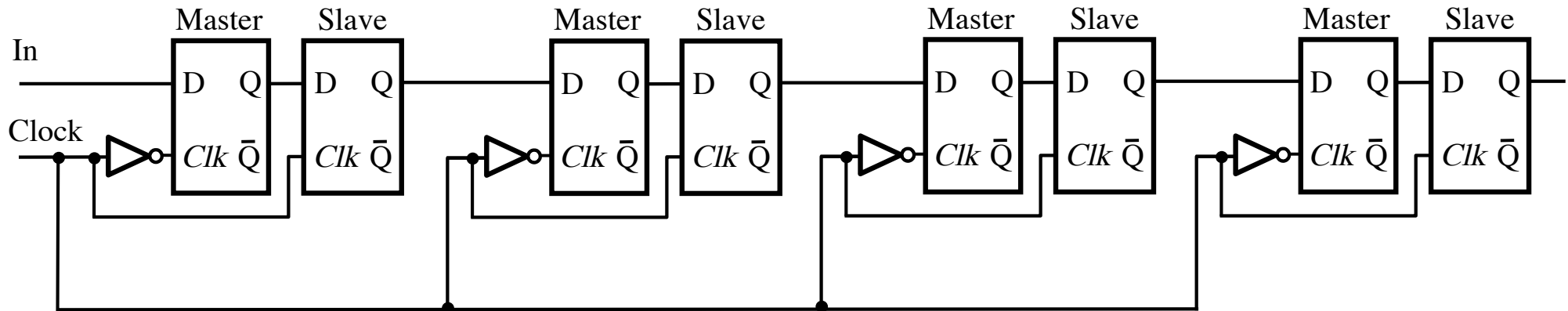 



A simple shift register

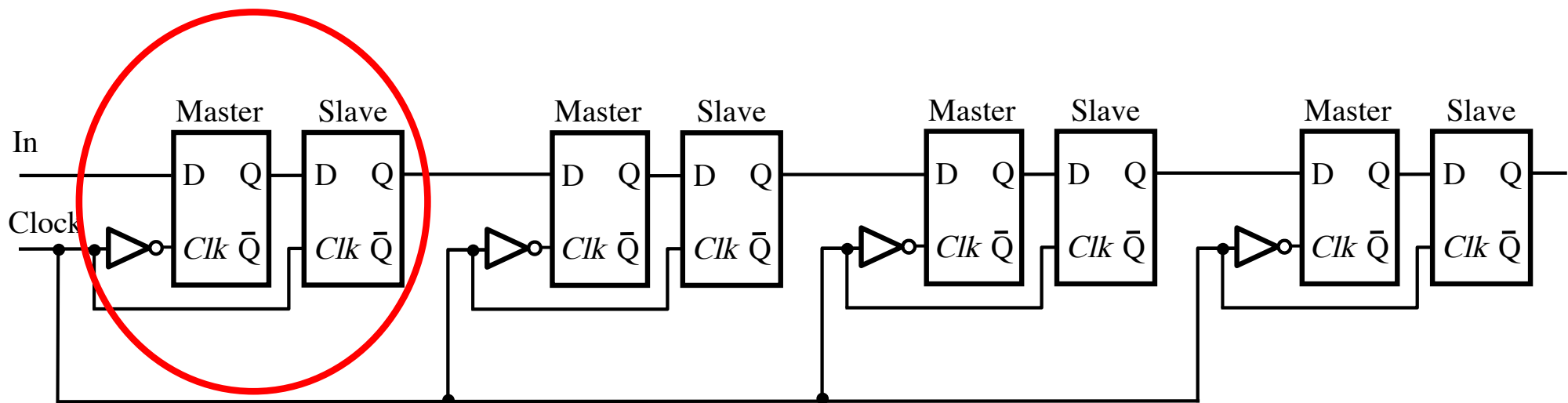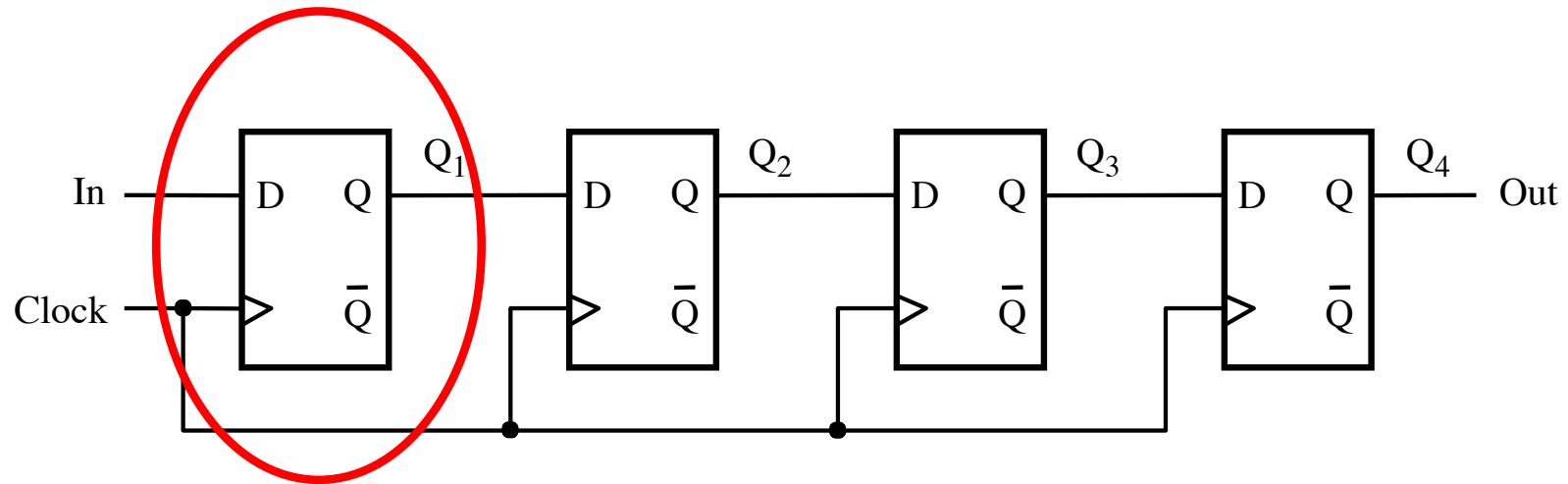



A simple shift register

 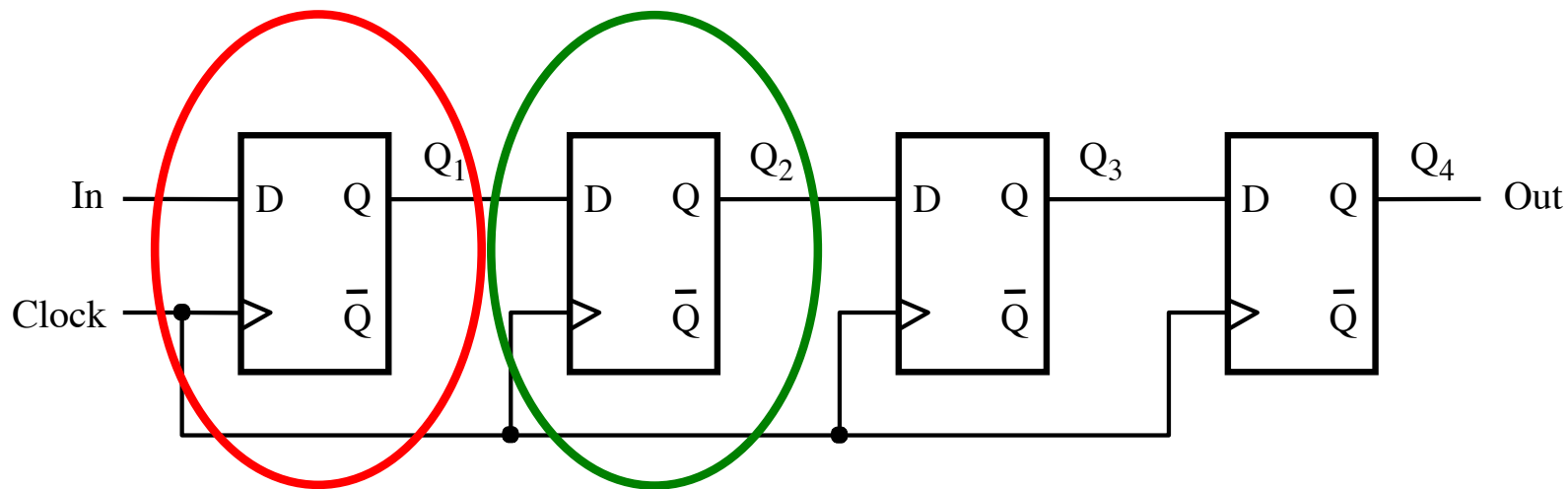


A simple shift register

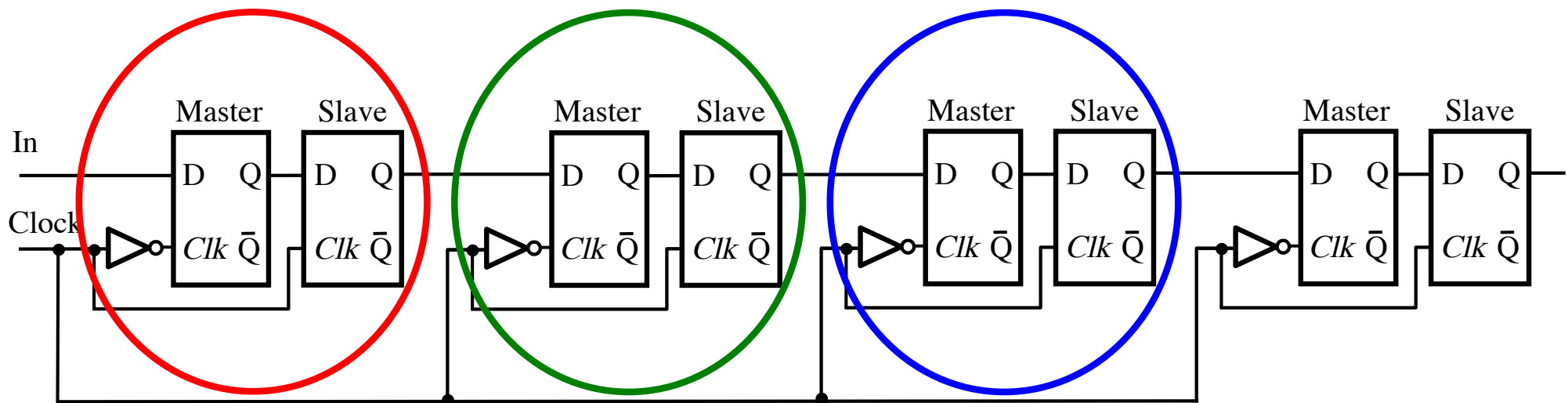 


A simple shift register

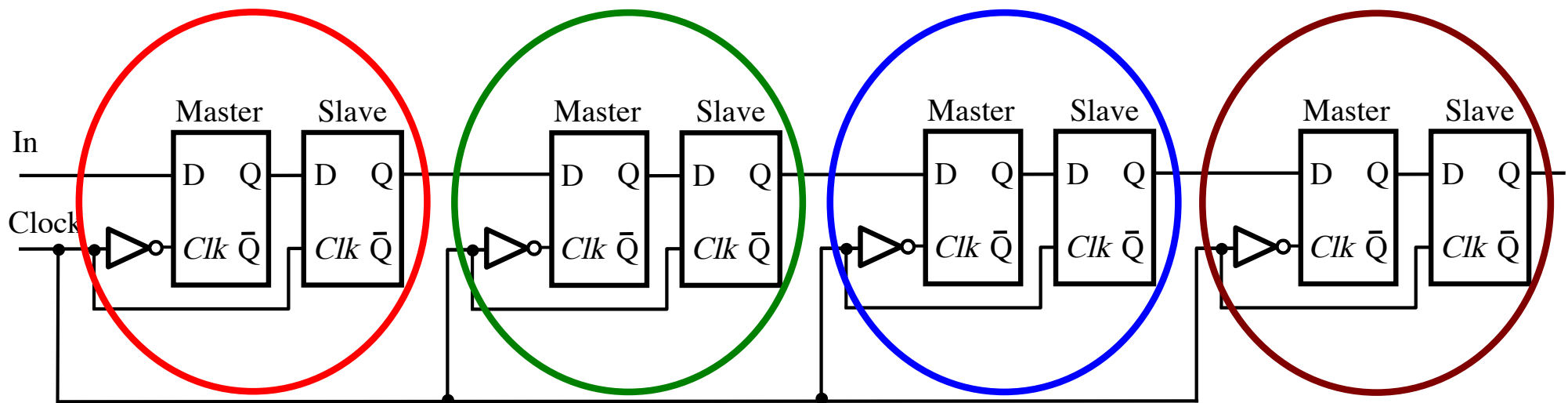 

A simple shift register

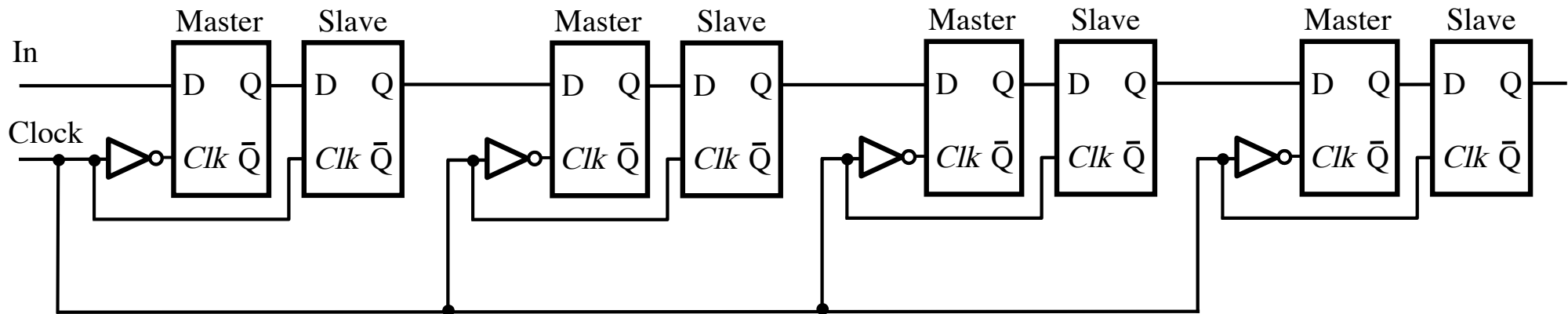


A simple shift register

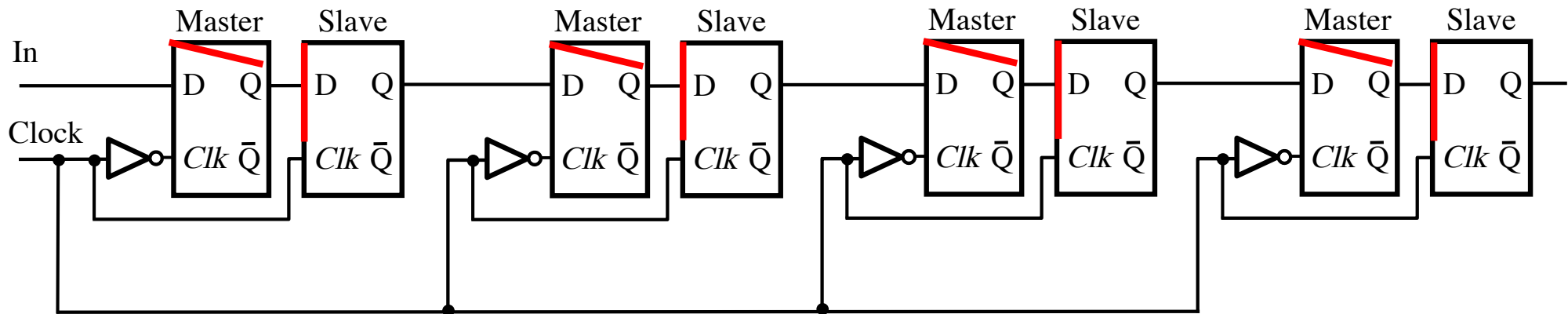


Clock



A simple shift register

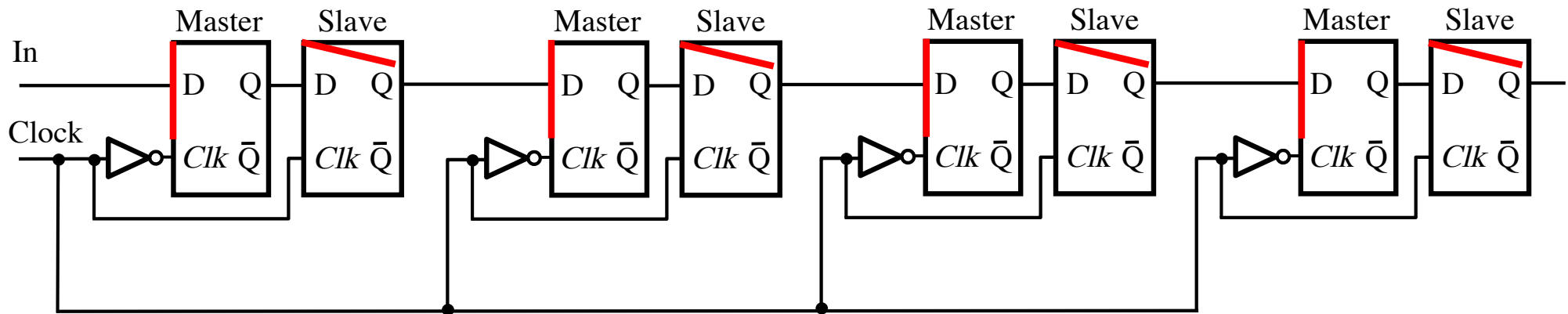


A simple shift register

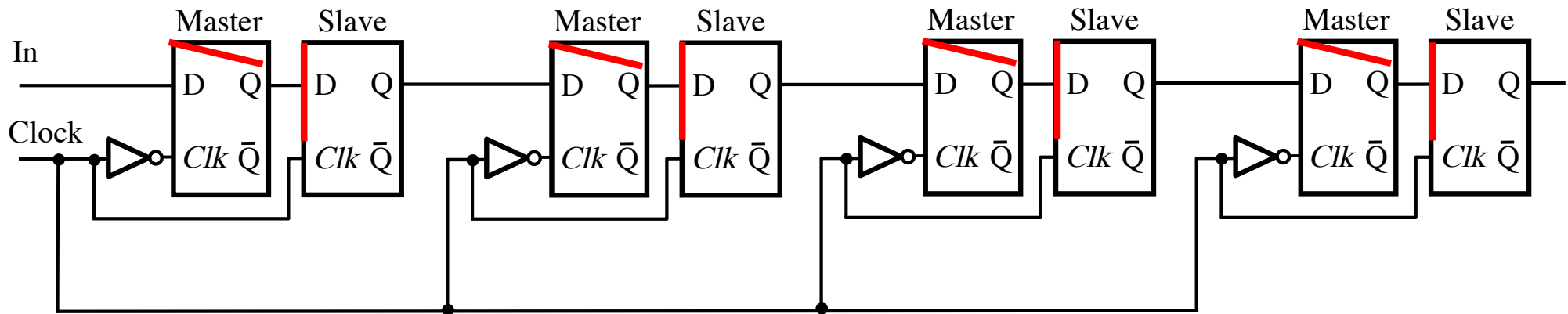


Clock



A simple shift register

 

A simple shift register

 


(a) Circuit

	In	Q ₁	Q ₂	Q ₃	Q ₄ = Out
t_0	1	0	0	0	0
t_1	0	1	0	0	0
t_2	1	0	1	0	0
t_3	1	1	0	1	0
t_4	1	1	1	0	1
t_5	0	1	1	1	0
t_6	0	0	1	1	1
t_7	0	0	0	1	1


(b) A sample sequence

Parallel-Access Shift Register

Parallel-access shift register

 


Parallel-access shift register

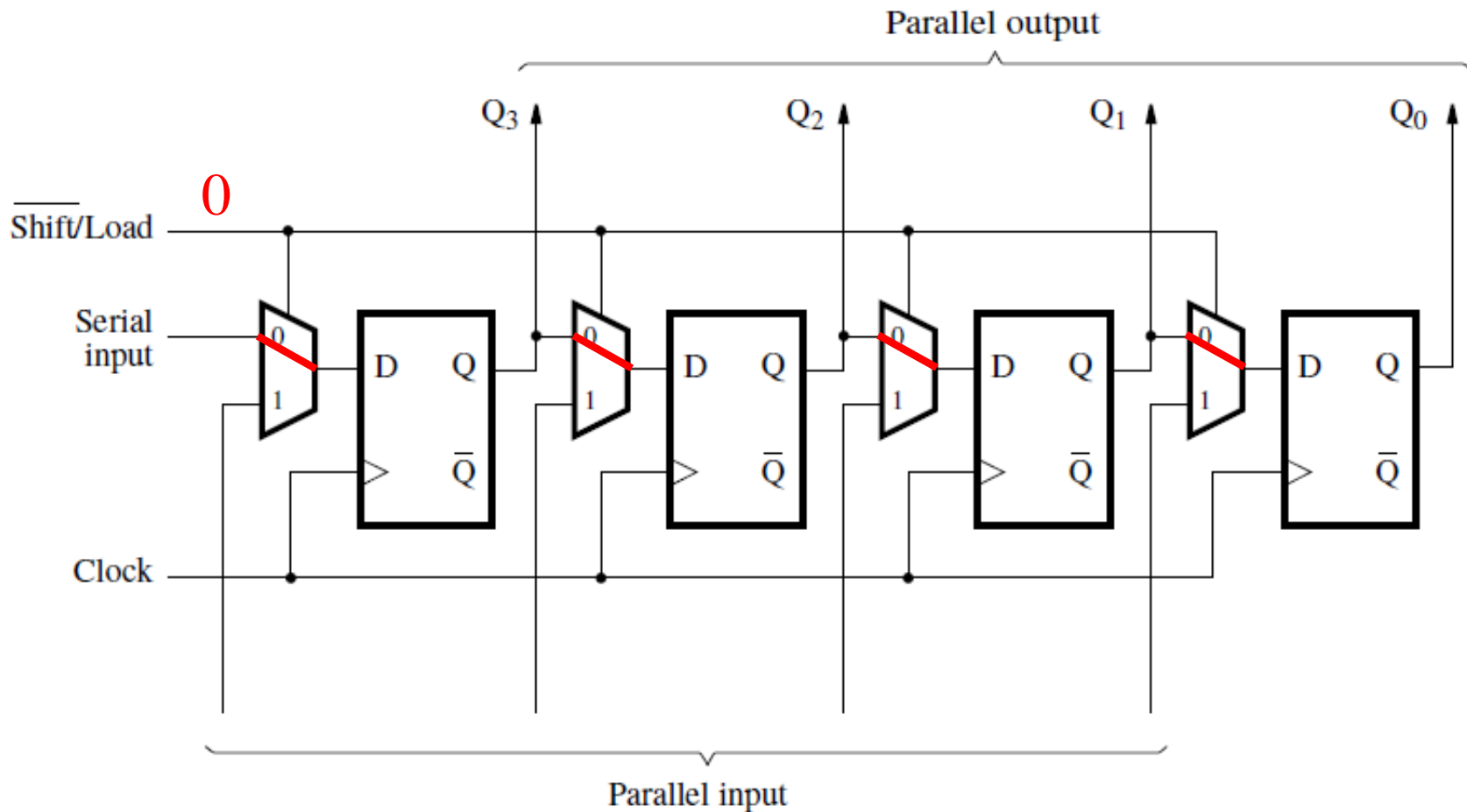

When Load=0, this behaves like a shift register.


Parallel-access shift register

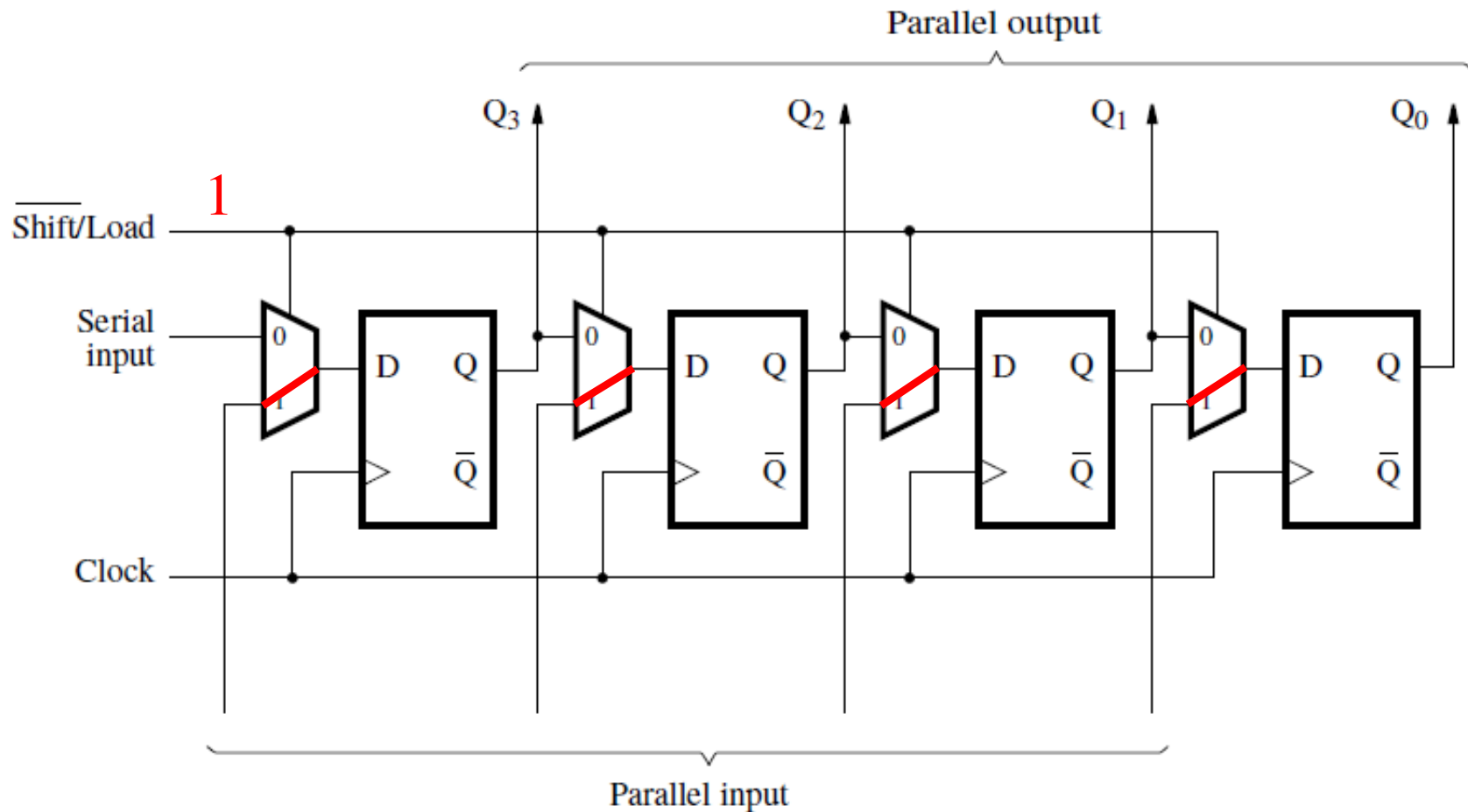

When Load=1, this behaves like a parallel-access register.


Shift Register With Parallel Load and Enable

A shift register with parallel load and enable control inputs

 


[Figure 5.59 from the textbook]

 A shift register with parallel load and enable control inputs




The directions of the input and output lines are switched relative to the previous slides.

A shift register with parallel load and enable control inputs

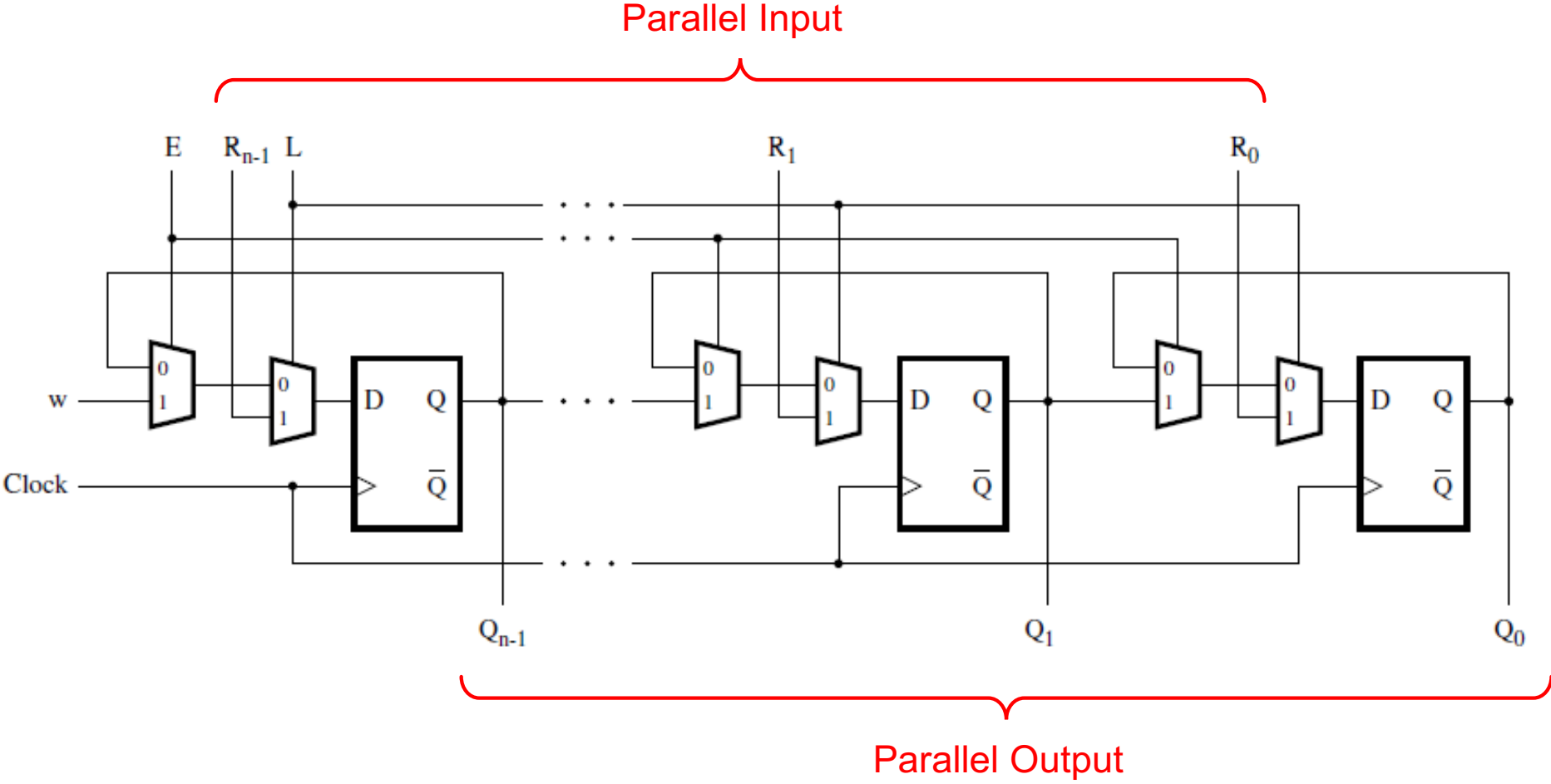


[Figure 5.59 from the textbook]

A shift register with parallel load and enable control inputs

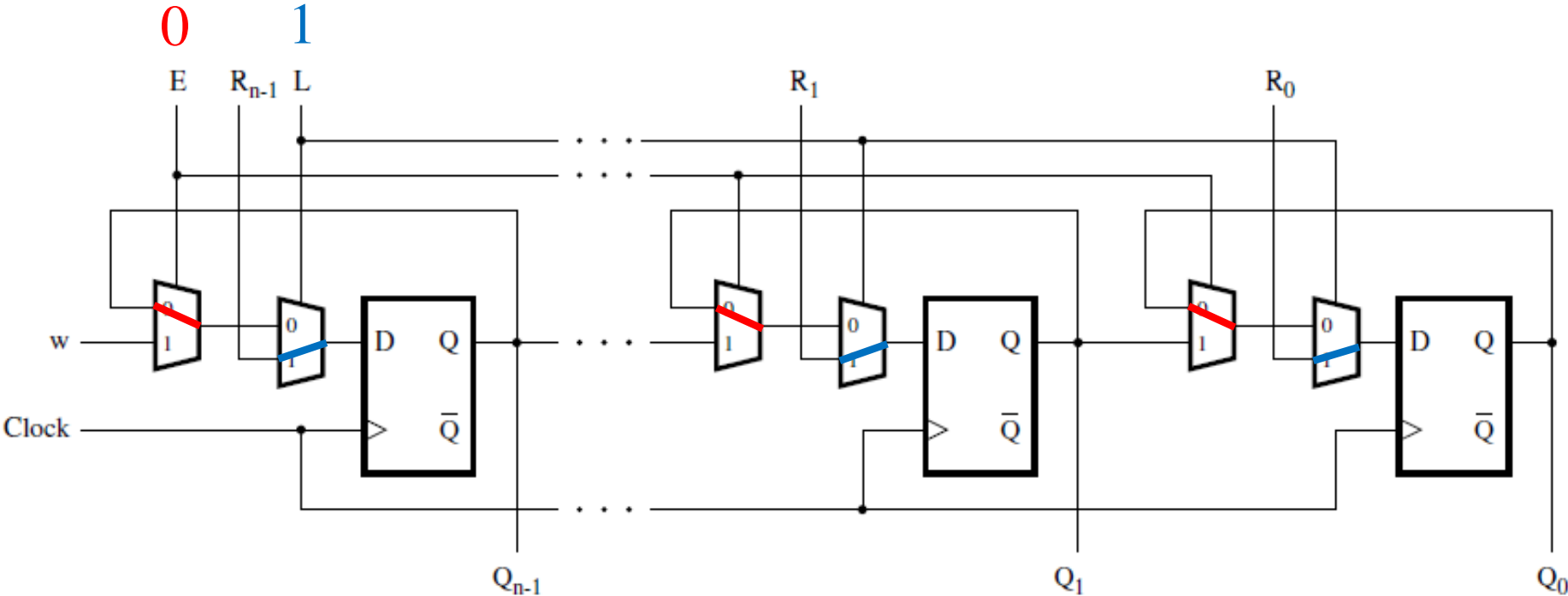

[Figure 5.59 from the textbook]

A shift register with parallel load and enable control inputs

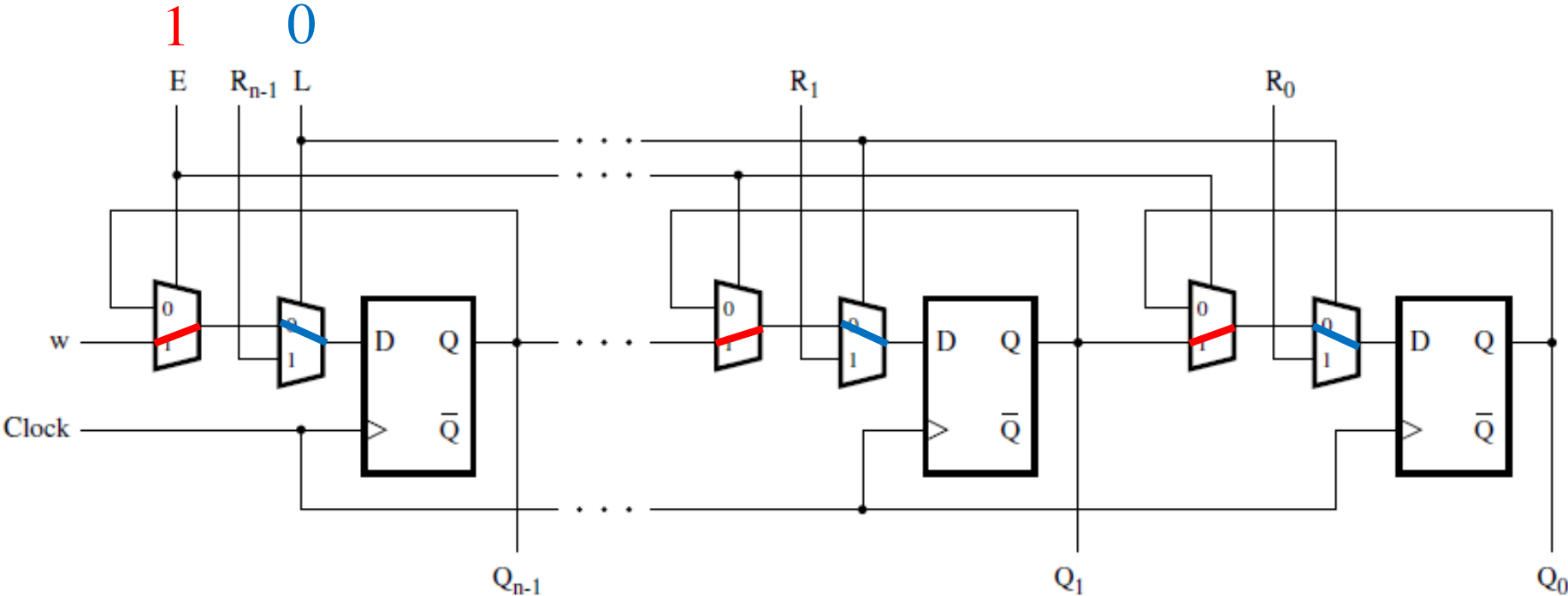


[Figure 5.59 from the textbook]


Multiplexer Tricks

(select one of two 2-bit numbers)


Select Either $A=A_1A_0$ or $B=B_1B_0$

 

Select Either $A=A_1A_0$ or $B=B_1B_0$

 


Select Either $A=A_1A_0$ or $B=B_1B_0$

 


Multiplexer Tricks

(select one of four 2-bit numbers)

 
Select $A=A_1A_0$ or $B=B_1B_0$ or $C=C_1C_0$ or $D=D_1D_0$



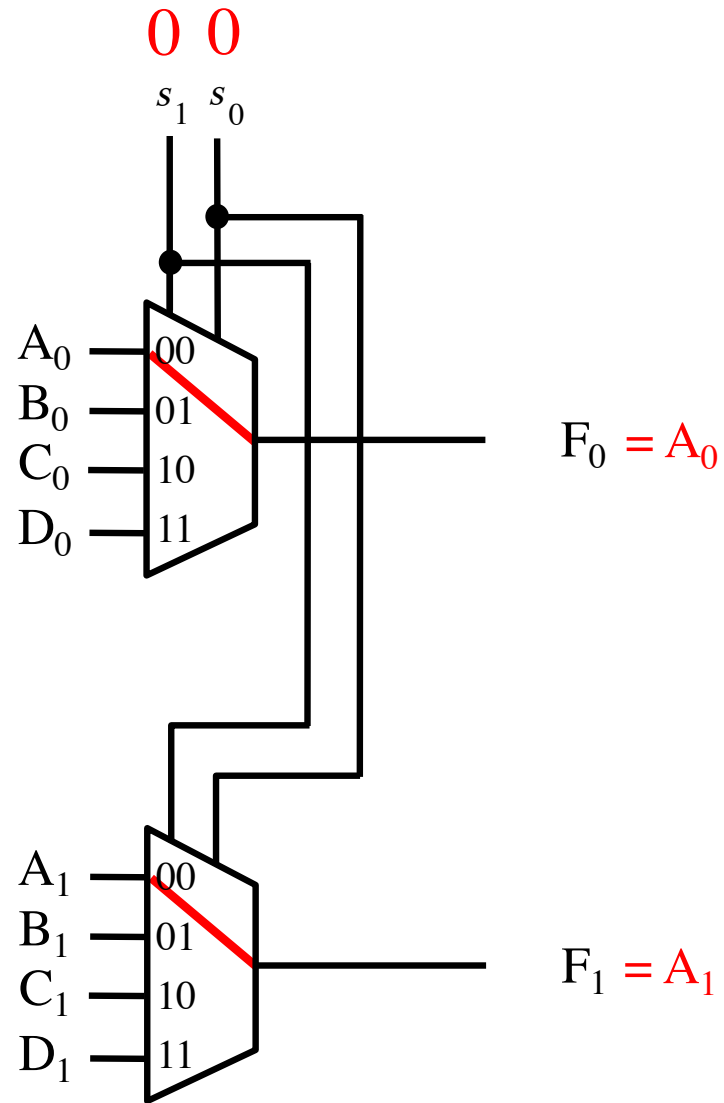
Select $A=A_1A_0$ or $B=B_1B_0$ or $C=C_1C_0$ or $D=D_1D_0$



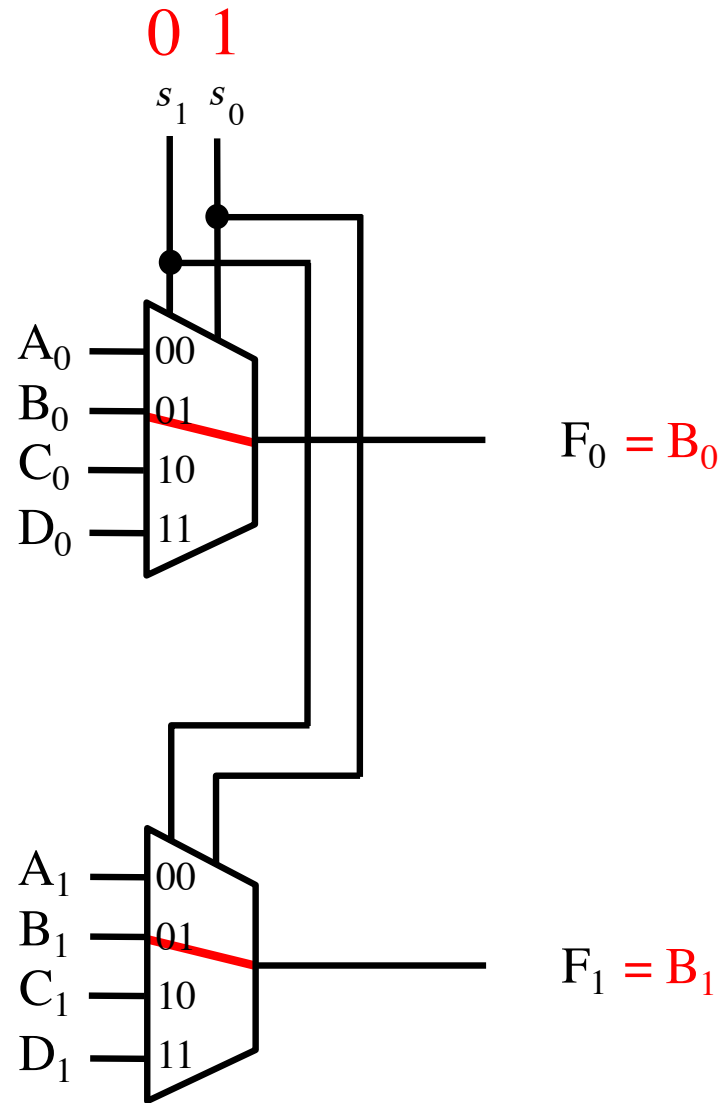
Select $A=A_1A_0$ or $B=B_1B_0$ or $C=C_1C_0$ or $D=D_1D_0$



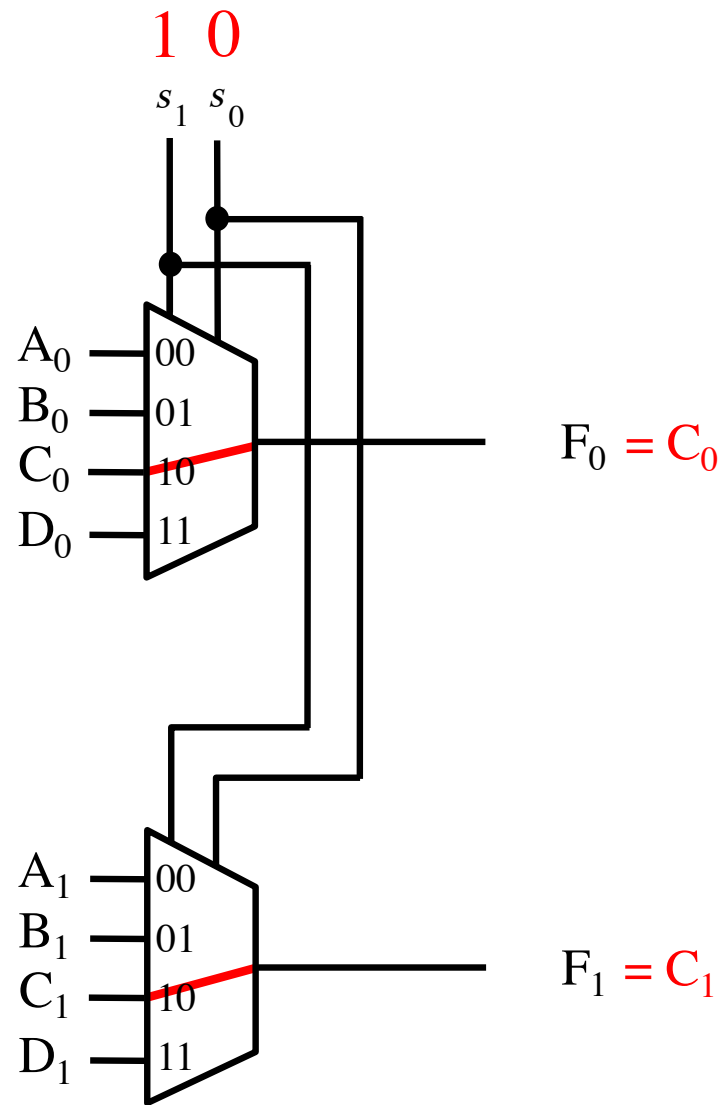Select $A=A_1A_0$ or $B=B_1B_0$ or $C=C_1C_0$ or $D=D_1D_0$
























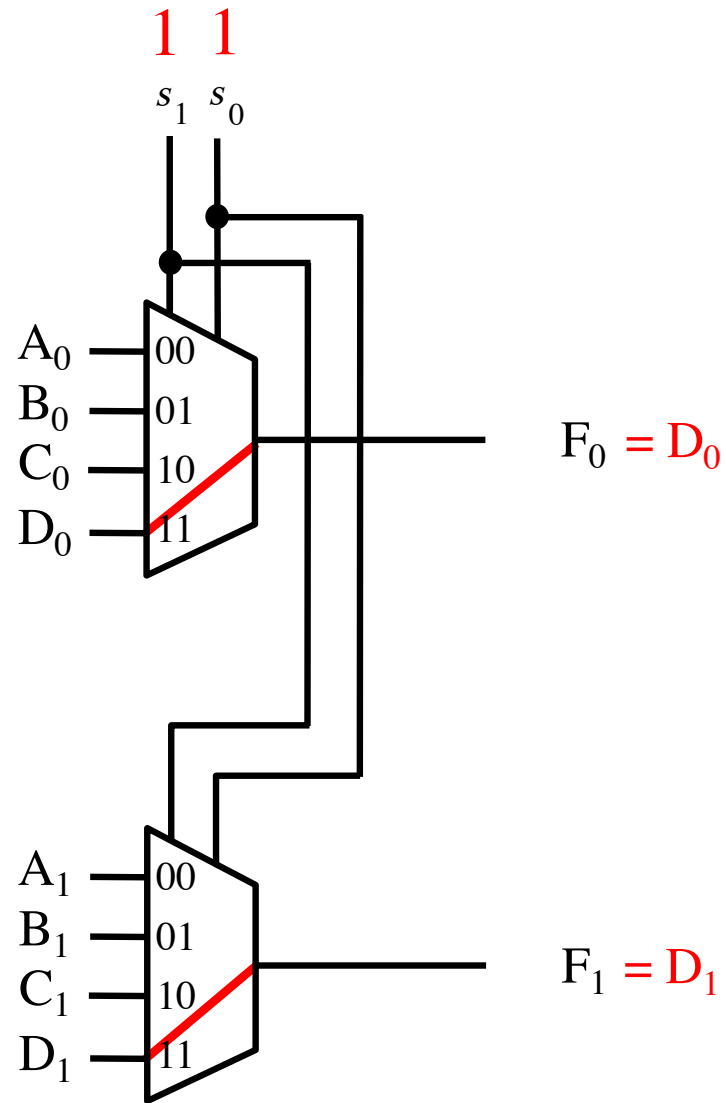
Select $A=A_1A_0$ or $B=B_1B_0$ or $C=C_1C_0$ or $D=D_1D_0$




Register File


Complete the following circuit diagram to implement a register file with four 2-bit registers, one write port, one read port, and one write enable line.

           

           


 


Register 0

 




Register 1

 


Register 2

 


Register 3

   


 


Register A

 




Register B

 


Register C

 


Register D

   


 


Register A

 




Register B




 


Register C

 


Register D

   

   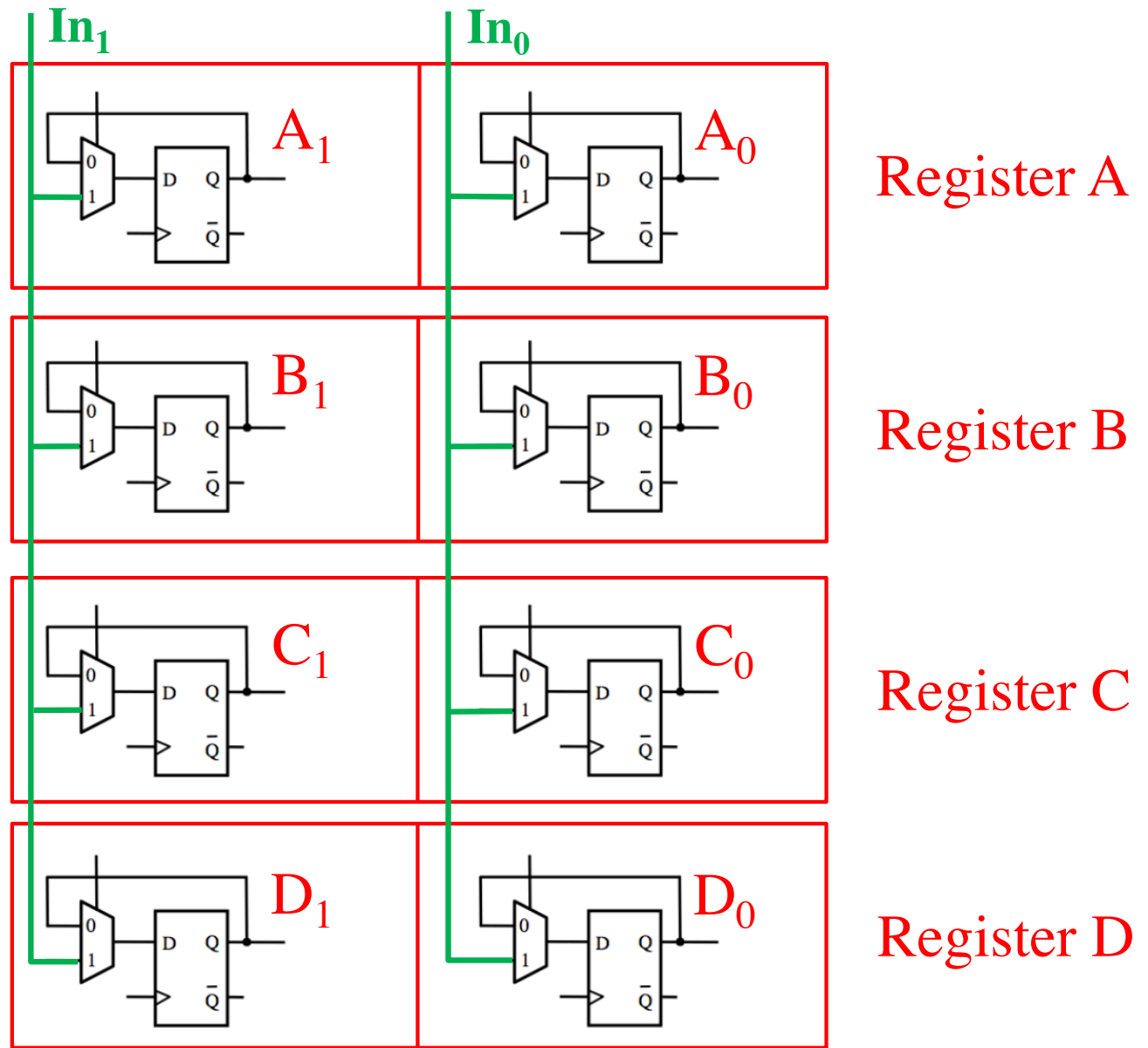

In_1

In_0



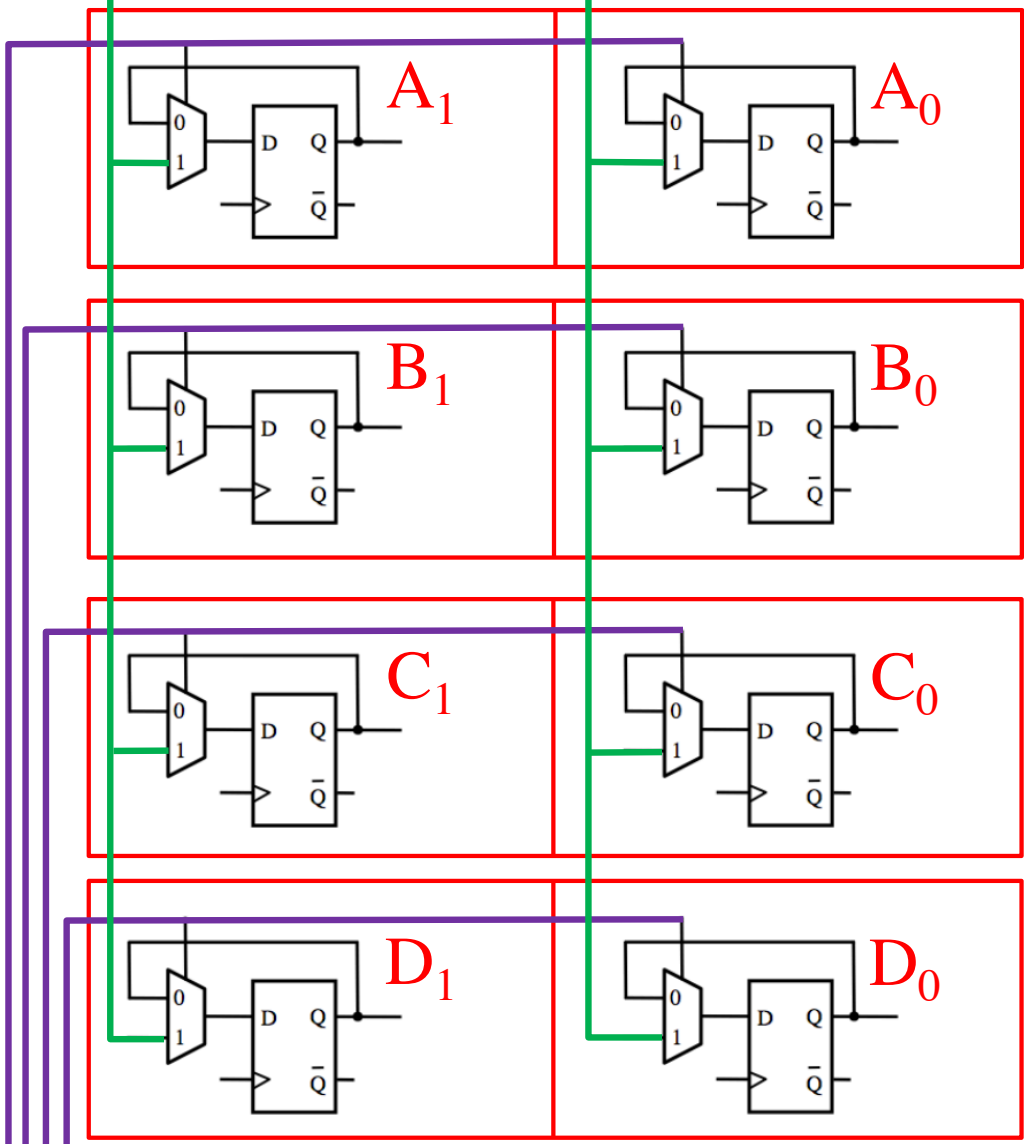



Register A

Register B



Register C

Register D

   

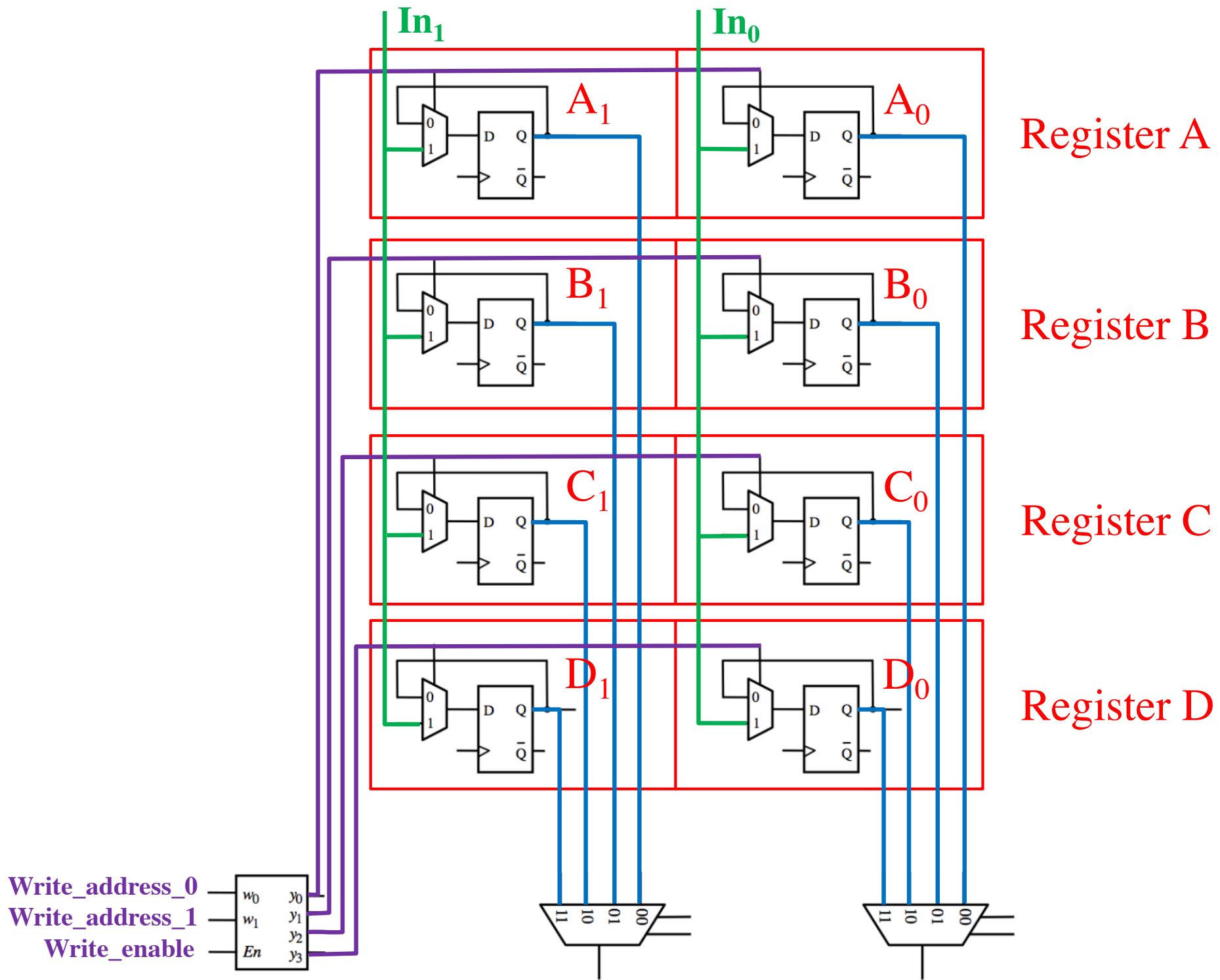

  Write_address_0
 Write_address_1
 Write_enable



Register A

Register B

Register C

Register D

A_1

A_0

B_1


B_0


C_1


C_0

D_1

D_0

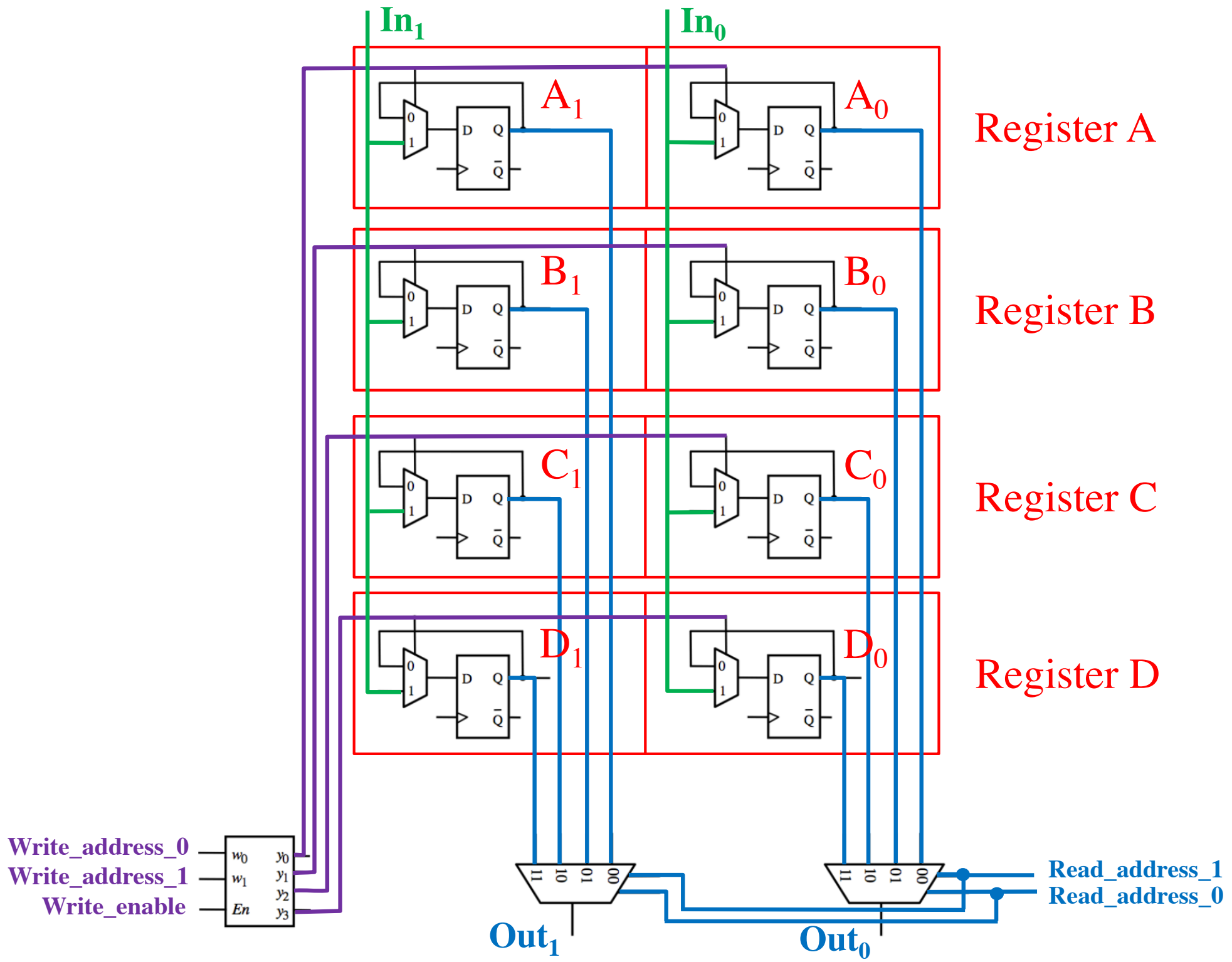

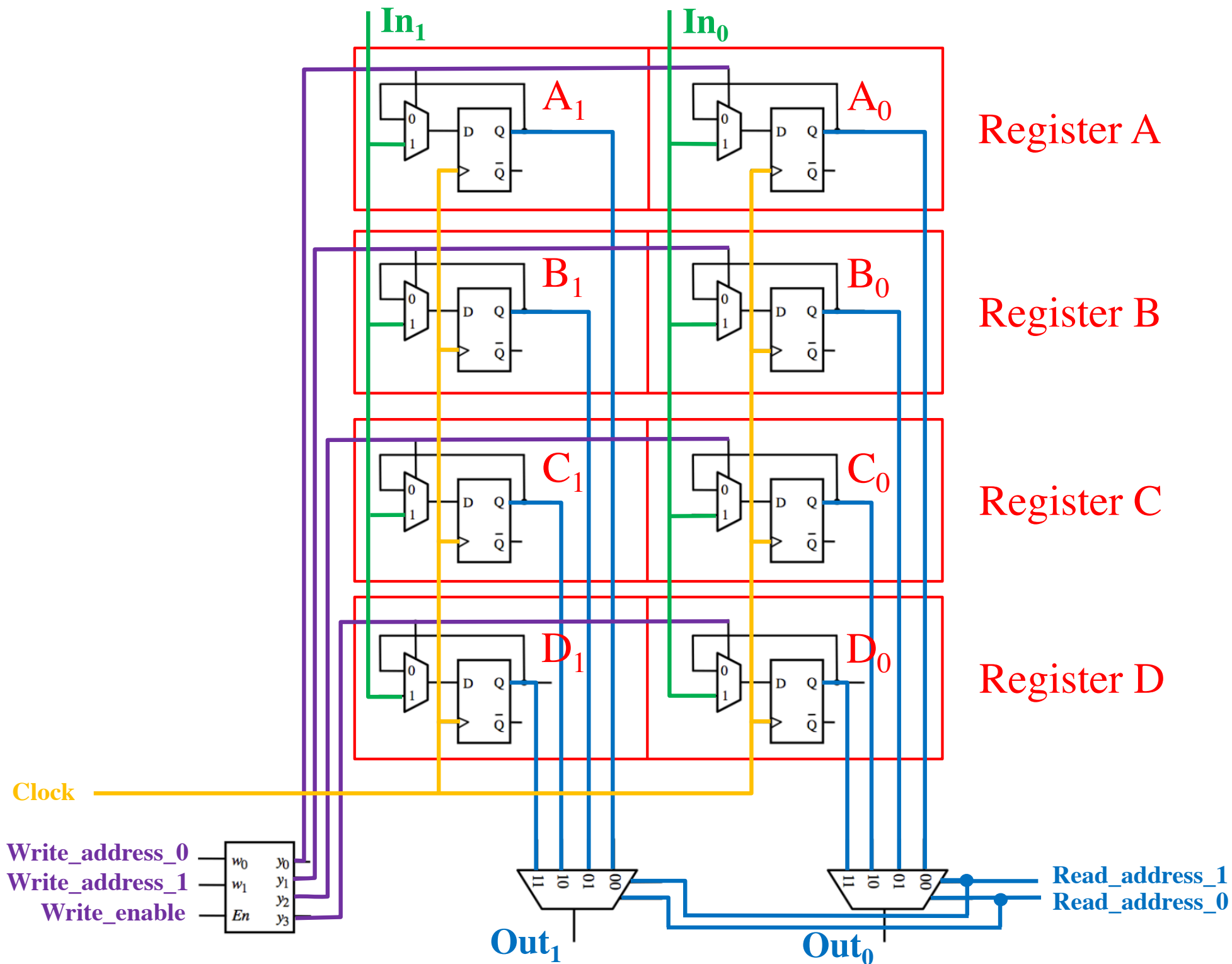


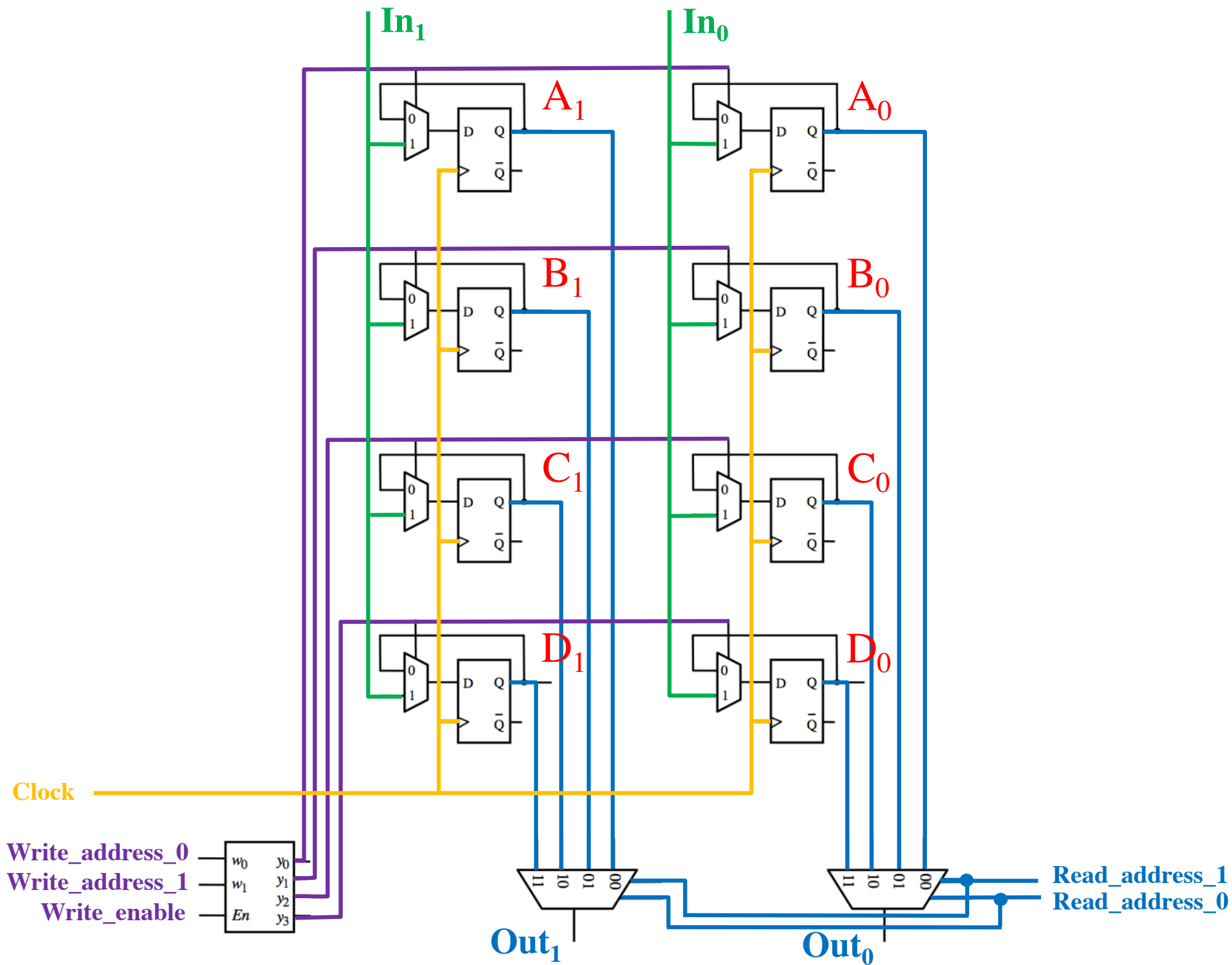

Another Register File

Register File

- **Register file is a unit containing r registers**
 - r can be 4, 8, 16, 32, etc.
- **Each register has n bits**
 - n can be 4, 8, 16, 32, etc.
 - n defines the data path width
- **Output ports (DATA1 and DATA2) are used for reading the register file**
 - Any register can be read from any of the ports
 - Each port needs a $\log_2 r$ bits to specify the read address (RA1 and RA2)
- **Input port (LD_DATA) is used for writing data to the register file**
 - Write address is also specified by $\log_2 r$ bits (WA)
 - Writing is enabled by a 1-bit signal (WR)

 


Register File: Exercise

- Suppose that a register file
 - contains 32 registers
 - width of data path is 16 bits (i.e., each register has 16 bits)


- How many bits are there for each of the signals?

 - RA1 5
- RA2 5
- DATA1 16
- DATA2 16
- WA 5
- LD_DATA 16
- WR 1




Register file design

 - We will design an eight-register file with 4-bit wide registers
- A single 4-bit register and its abstraction are shown below



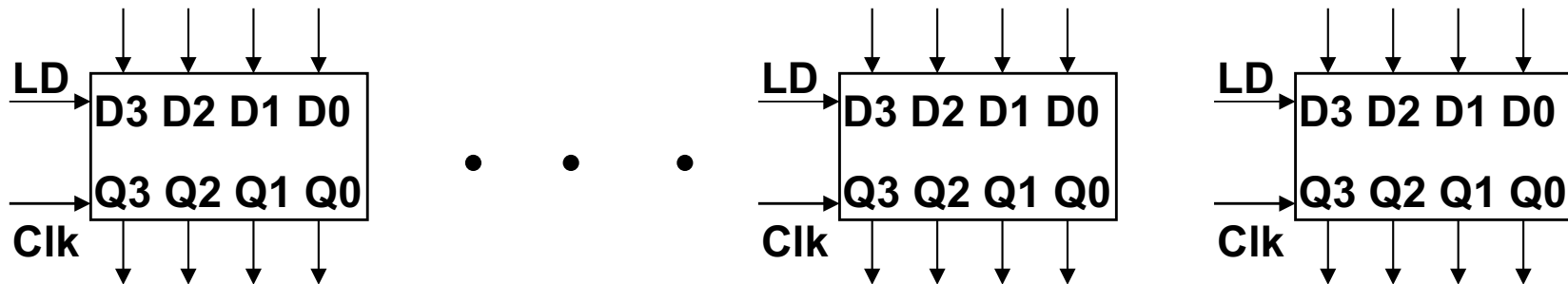
- We have to use eight such registers to make an eight register file



- How many bits are required to specify a register address?


Adding write control to register file

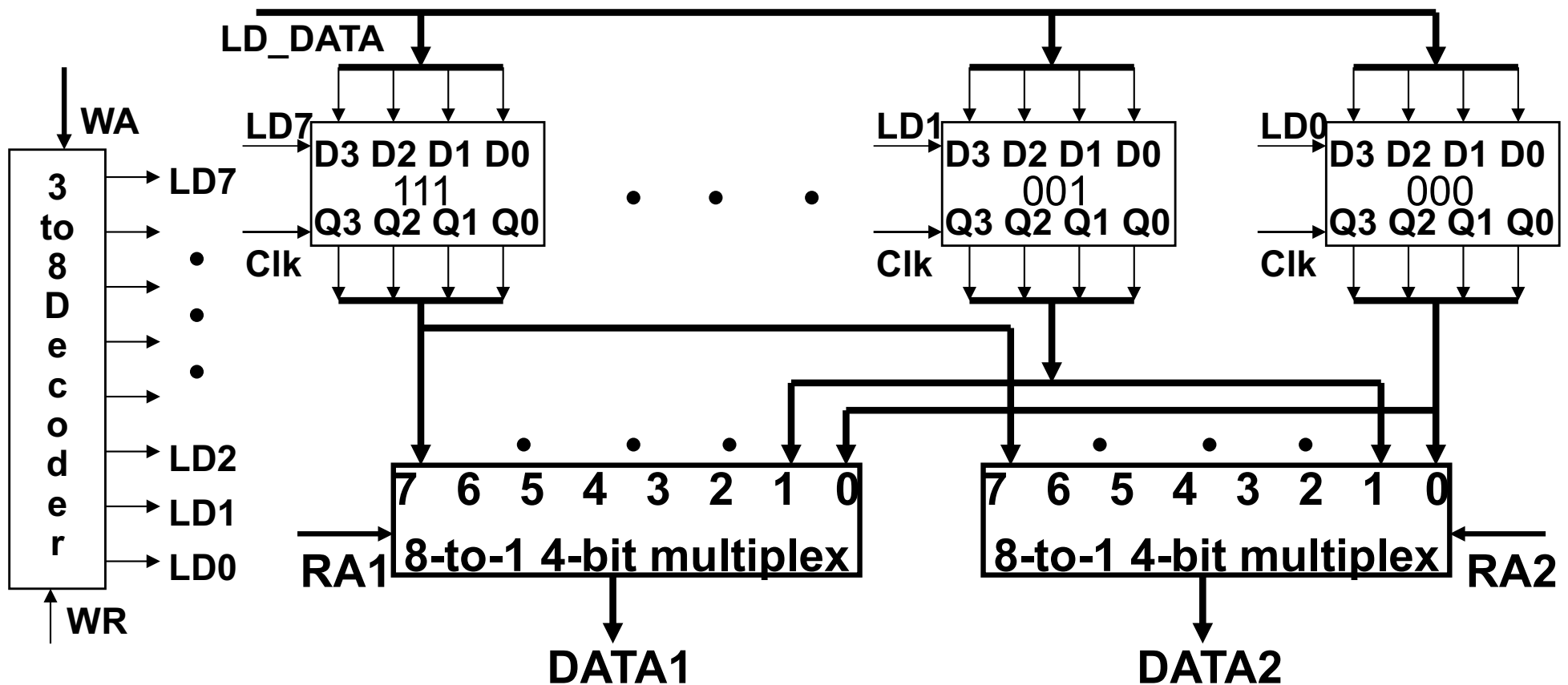
- To write to any register, we need the register's address (WA) and a write register signal (WR)
- A 3-bit write address is decoded if write register signal is present
- One of the eight registers gets a LD signal from the decoder





Register File (More Examples)

Register File

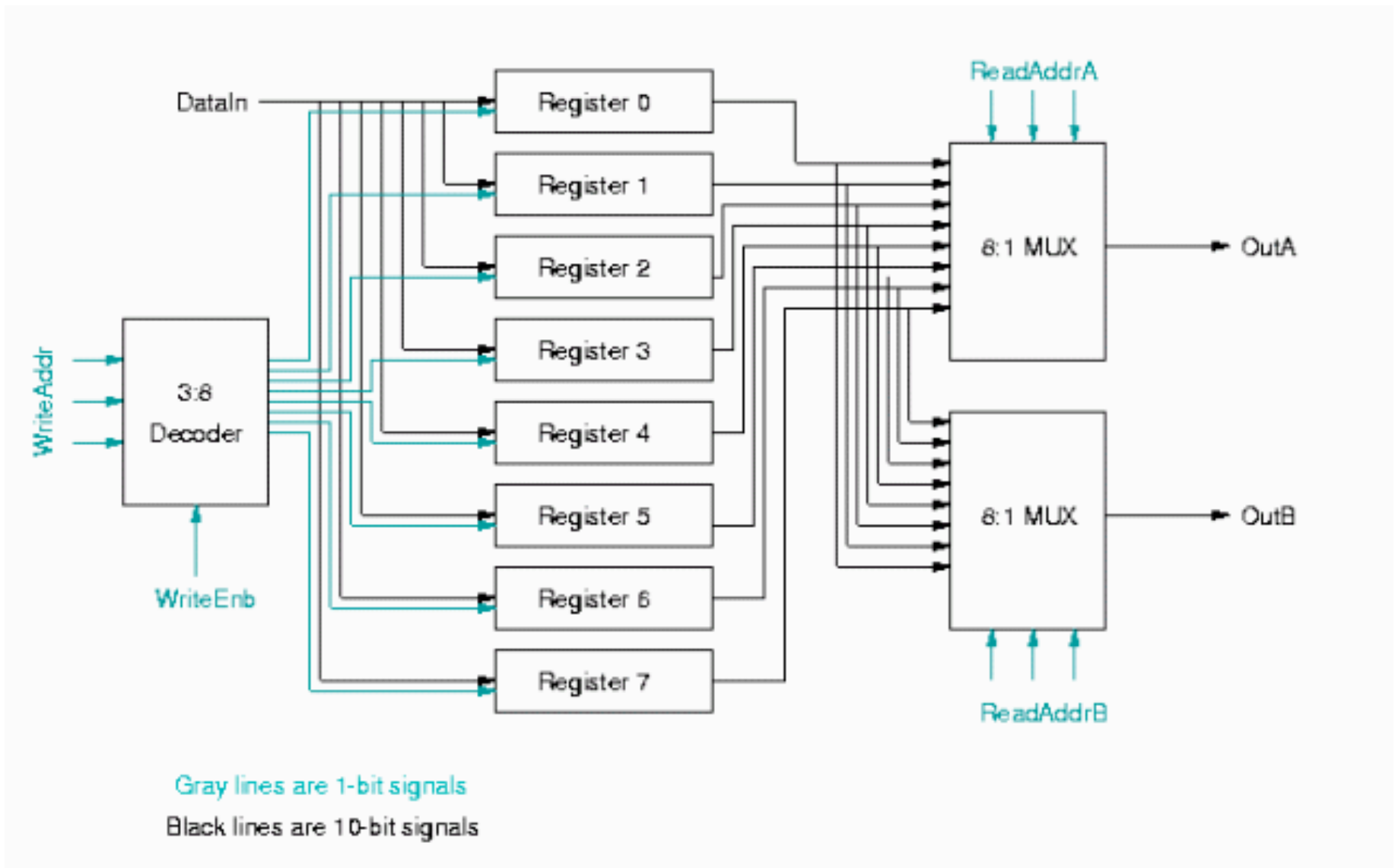

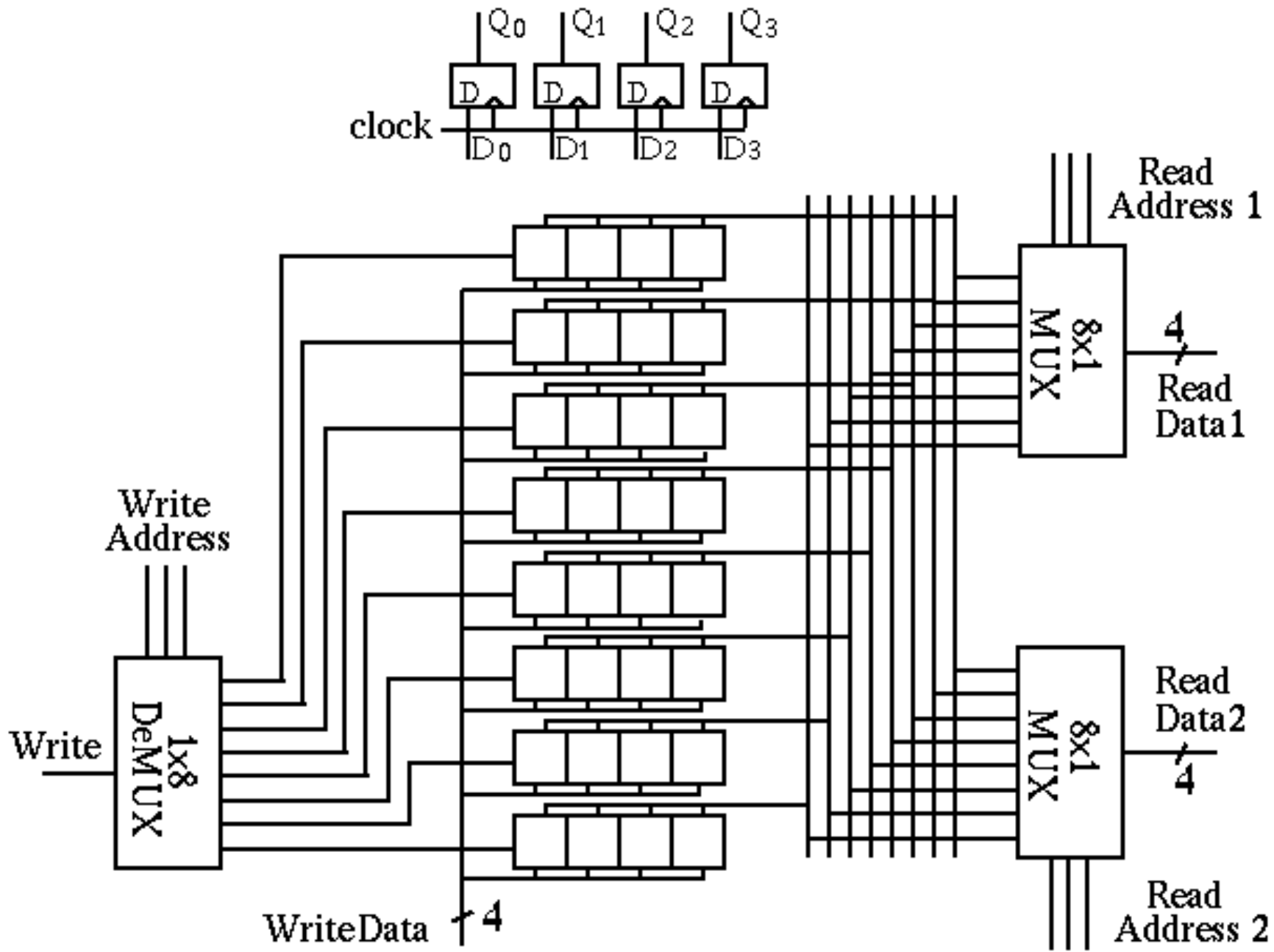


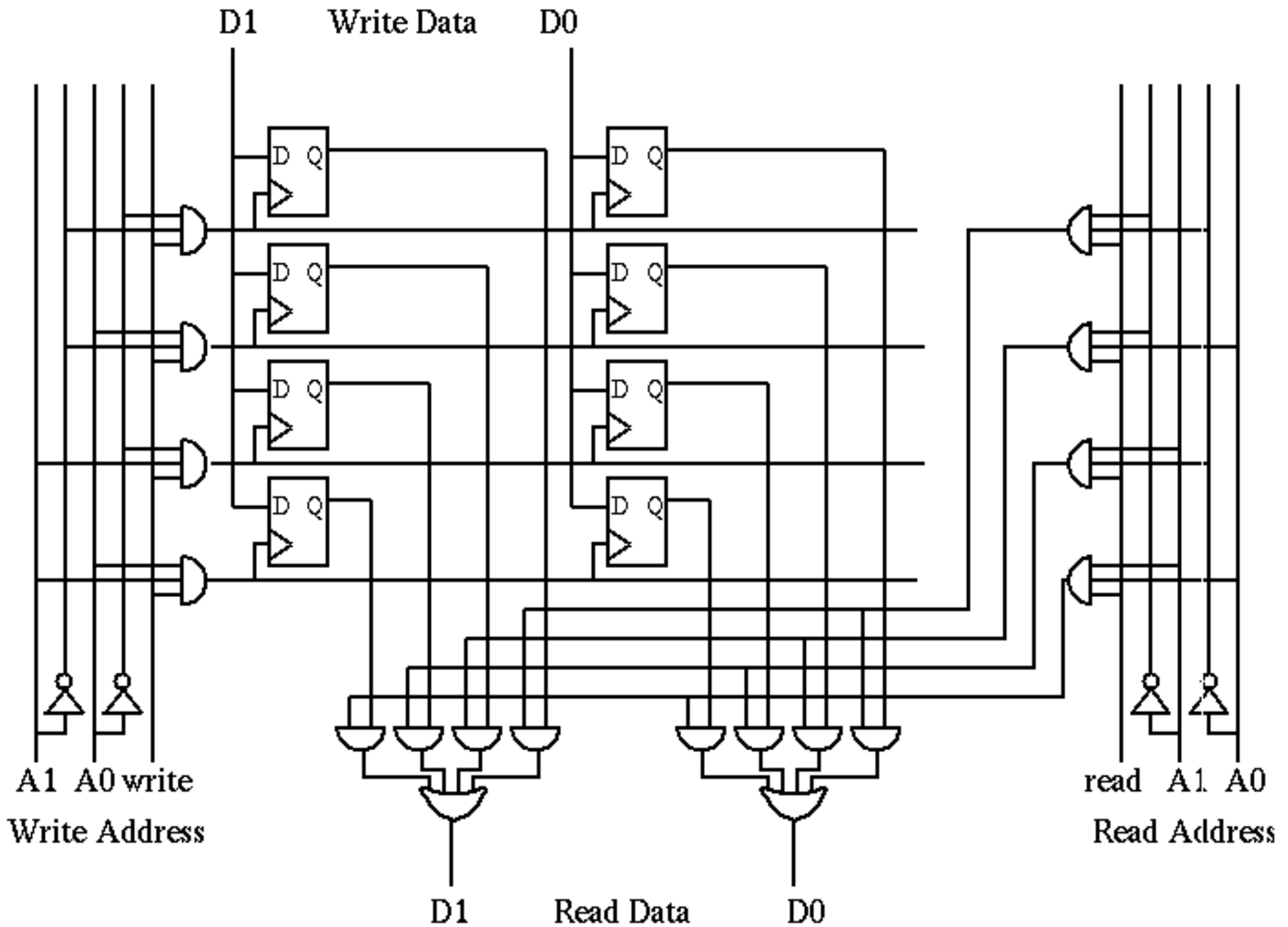

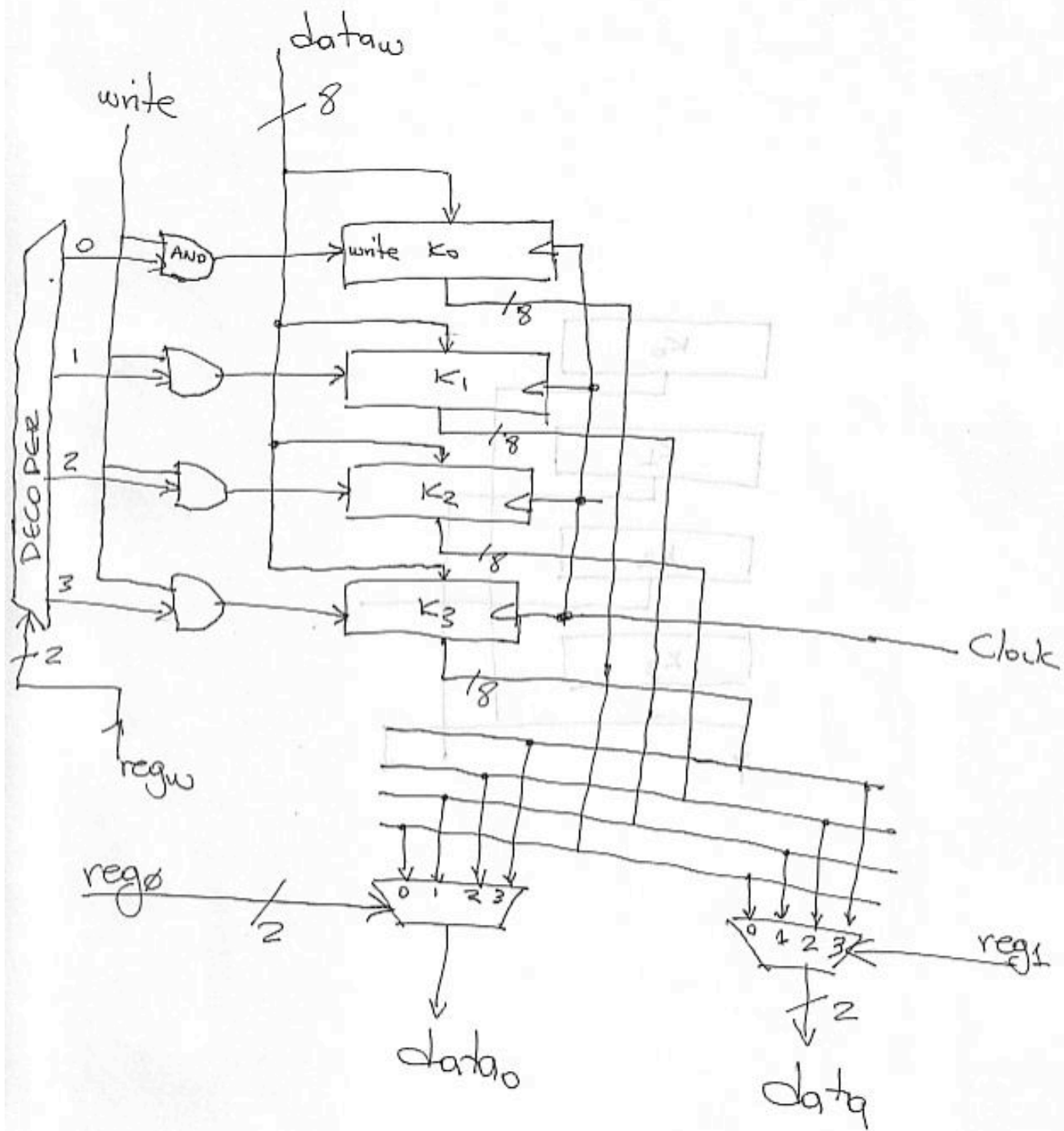


Counters

 
**The output of the T Flip-Flop
divides the frequency of the clock by 2**



 
**The output of the T Flip-Flop
divides the frequency of the clock by 2**



A three-bit down-counter

 


A three-bit down-counter

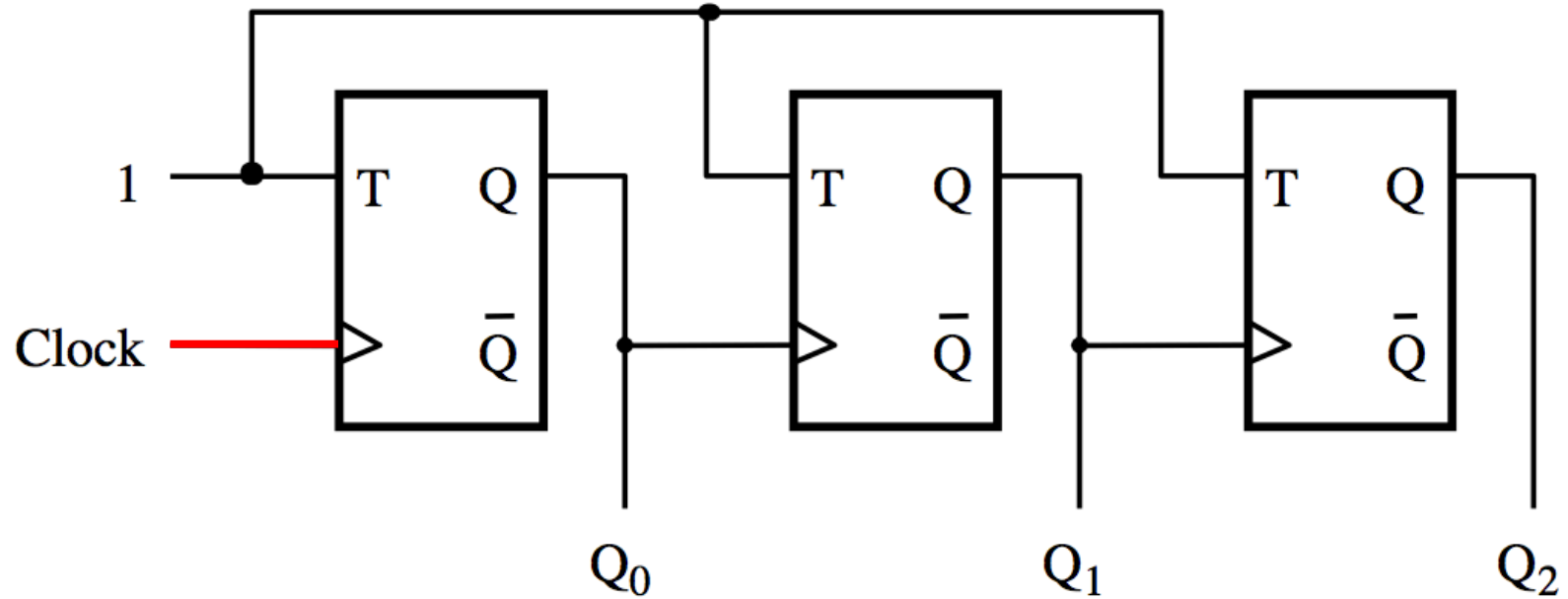

The first flip-flop changes
on the positive edge of the clock


A three-bit down-counter

 

The first flip-flop changes
on the positive edge of the clock

The second flip-flop changes
on the positive edge of Q_0

A three-bit down-counter

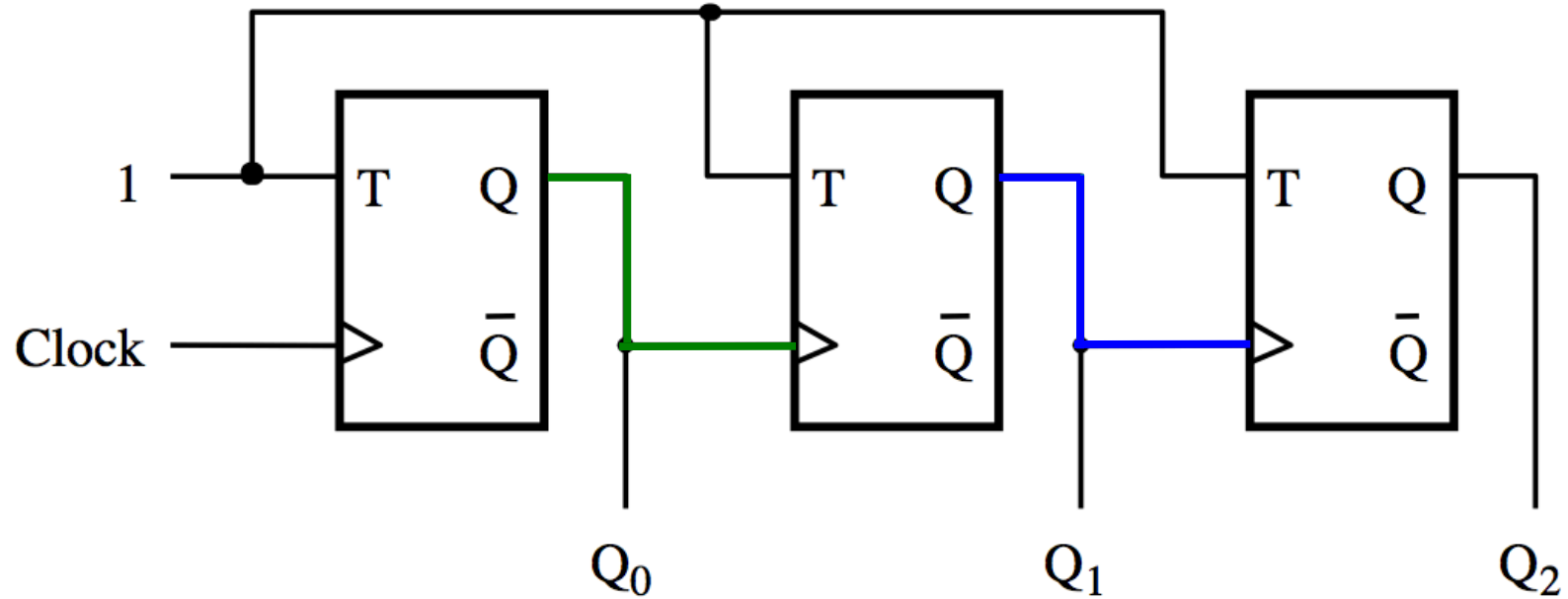


The first flip-flop changes
on the positive edge of the clock


The second flip-flop changes
on the positive edge of Q_0

The third flip-flop changes
on the positive edge of Q_1

A three-bit down-counter

 


(a) Circuit

 


(b) Timing diagram

A three-bit down-counter

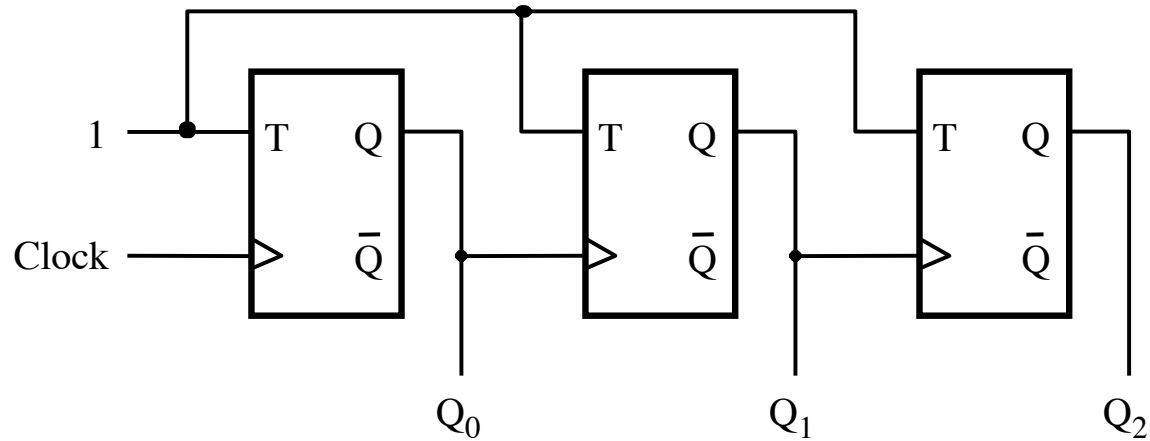


(a) Circuit

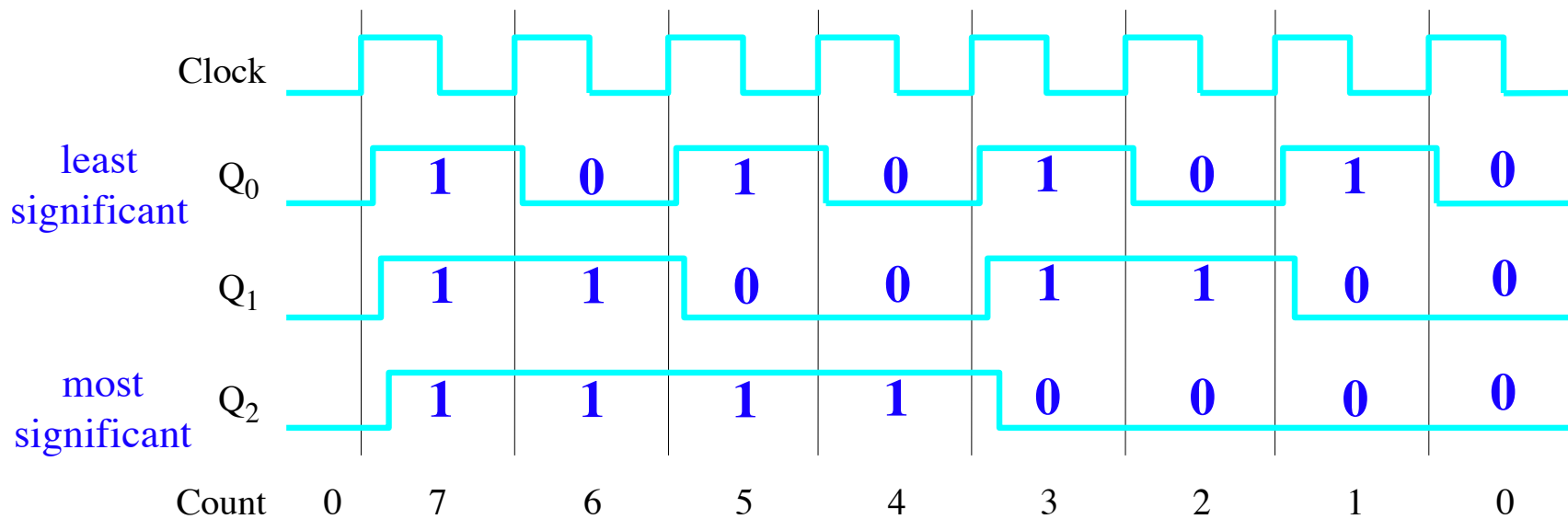


(b) Timing diagram

A three-bit down-counter

 


(a) Circuit

 


(b) Timing diagram

A three-bit down-counter

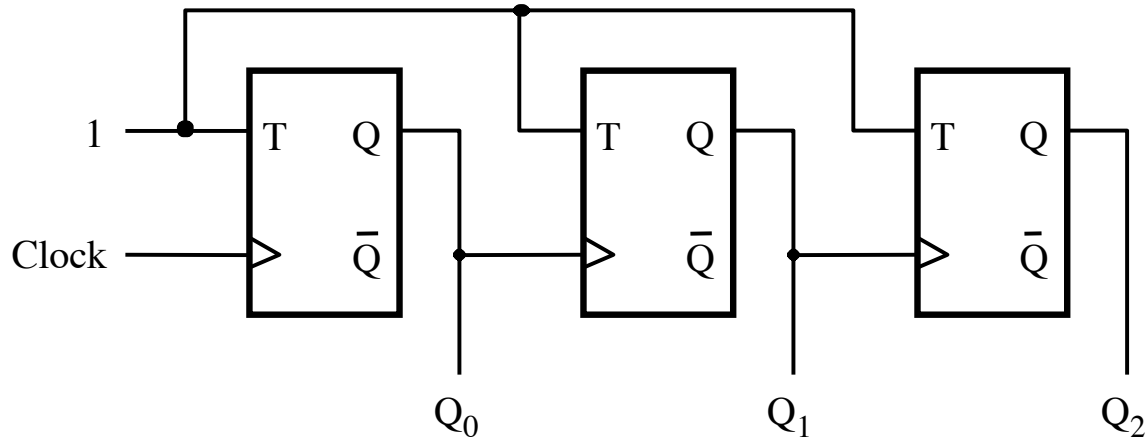


(a) Circuit

 


(b) Timing diagram

A three-bit down-counter

 


(a) Circuit

 


(b) Timing diagram

A three-bit down-counter

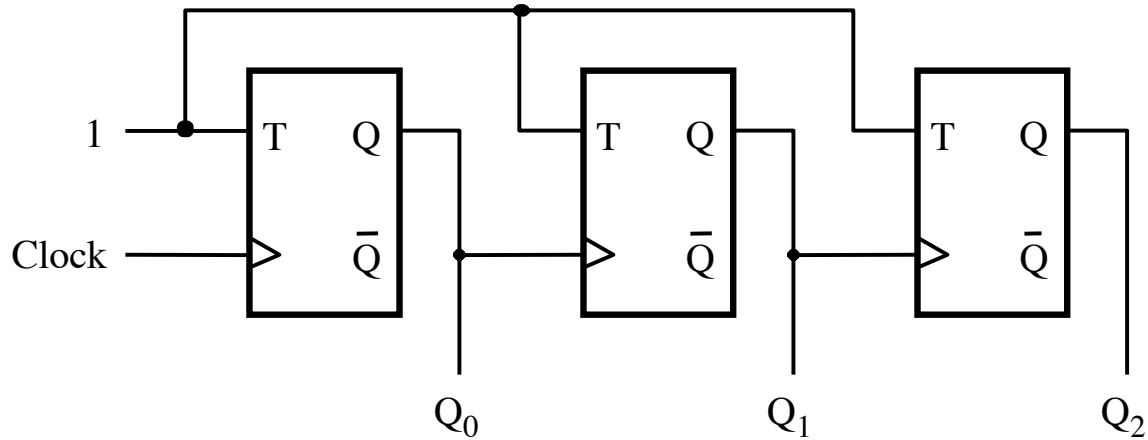


(a) Circuit

The propagation delays get longer

 


(b) Timing diagram

A three-bit up-counter

 


A three-bit up-counter

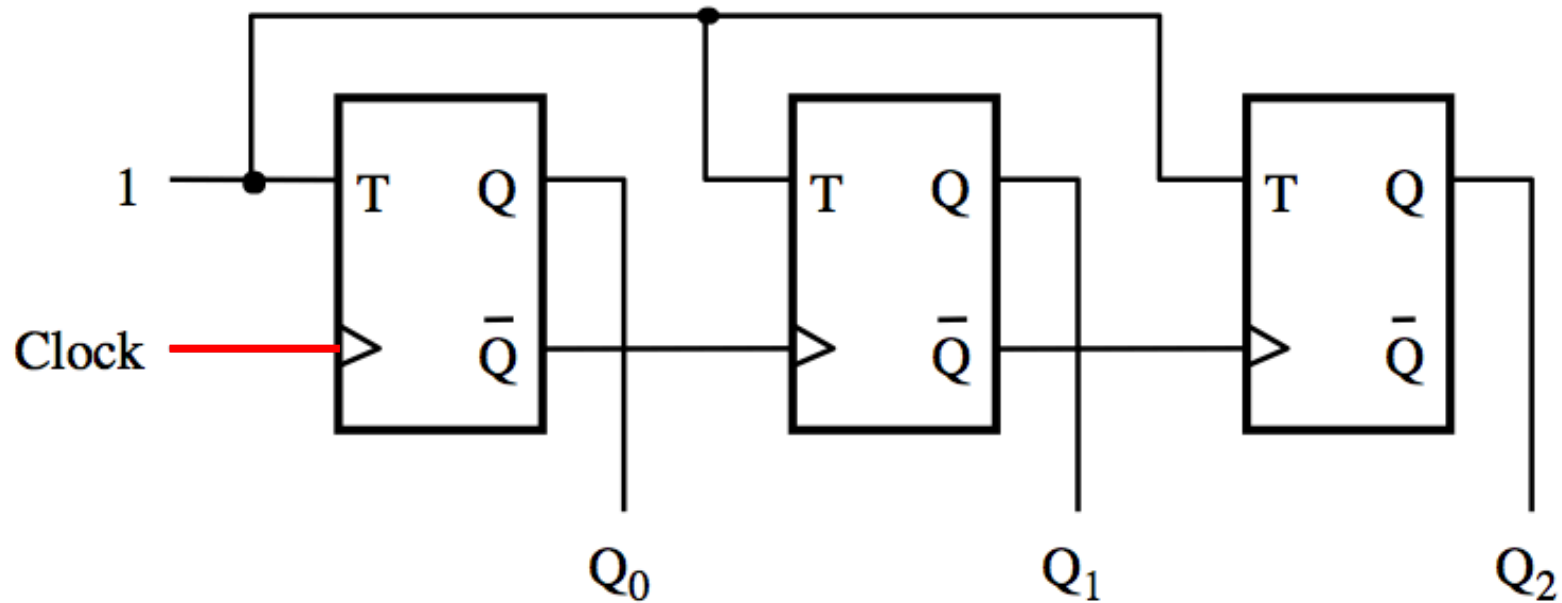

The first flip-flop changes
on the positive edge of the clock


A three-bit up-counter

 

The first flip-flop changes
on the positive edge of the clock

The second flip-flop changes
on the positive edge of \bar{Q}_0

A three-bit up-counter

 


The first flip-flop changes on the positive edge of the clock


The second flip-flop changes on the positive edge of \bar{Q}_0

The third flip-flop changes on the positive edge of \bar{Q}_1

A three-bit up-counter

 


(a) Circuit

 


(b) Timing diagram

A three-bit up-counter

 


(a) Circuit

 


(b) Timing diagram

A three-bit up-counter

 


(a) Circuit

 


(b) Timing diagram

A three-bit up-counter

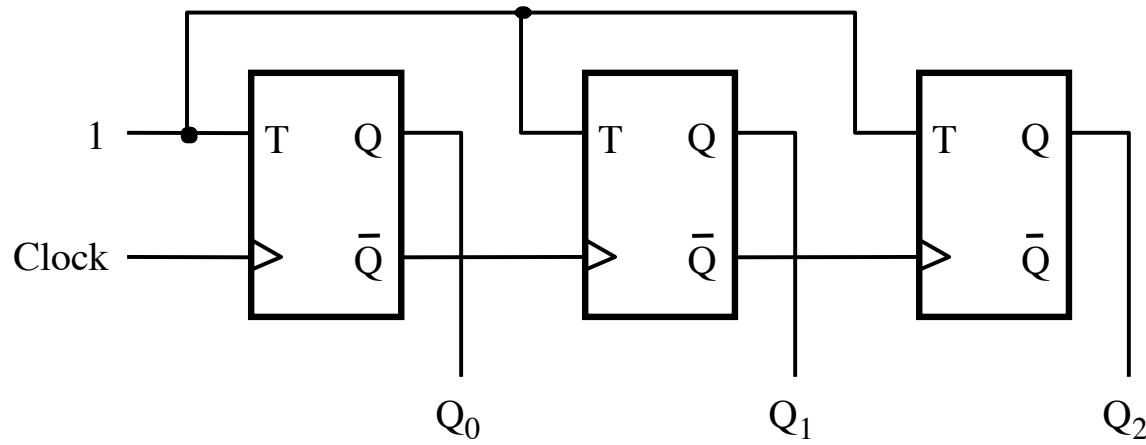


(a) Circuit

 


(b) Timing diagram

A three-bit up-counter

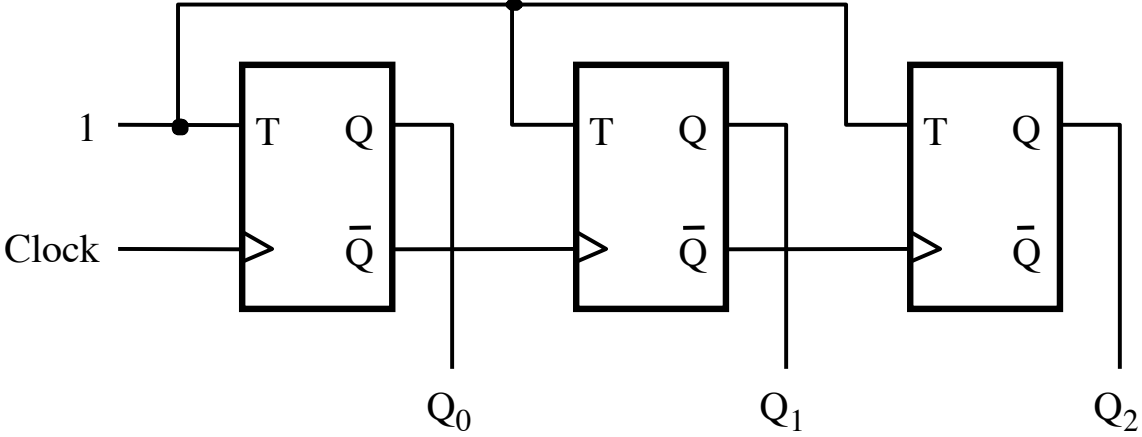


(a) Circuit

 


(b) Timing diagram

A three-bit up-counter

 


(a) Circuit

 


(b) Timing diagram

A three-bit up-counter

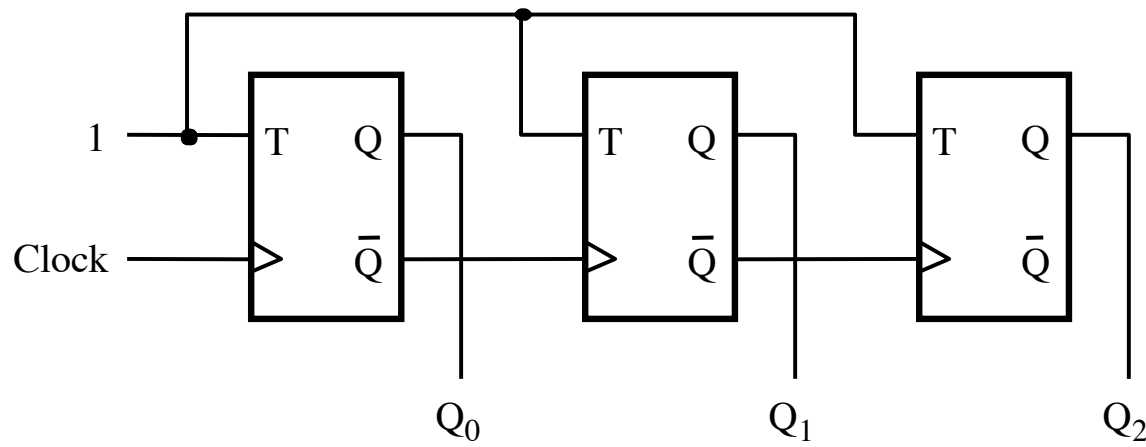


(a) Circuit

 


(b) Timing diagram

A three-bit up-counter

 


 (a) Circuit **The propagation delays get longer**




(b) Timing diagram

A three-bit up-counter

 

(a) Circuit


The propagation delays get longer

 


(b) Timing diagram

Synchronous Counters

A four-bit synchronous up-counter

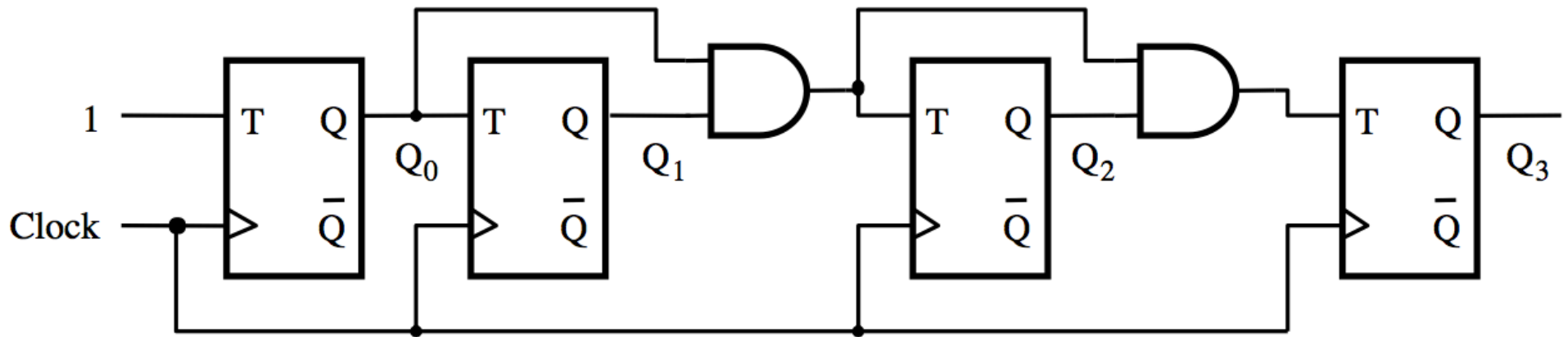


A four-bit synchronous up-counter

 


The propagation delay through all AND gates combined must not exceed the clock period minus the setup time for the flip-flops

A four-bit synchronous up-counter

 

(a) Circuit

 

(b) Timing diagram

Derivation of the synchronous up-counter

Clock cycle	Q ₂	Q ₁	Q ₀
0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1
8	0	0	0

Q₁ changes

Q₂ changes

Derivation of the synchronous up-counter

Clock cycle	Q ₂	Q ₁	Q ₀
0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1
8	0	0	0

Q₁ changes


Q₂ changes

$$T_0 = 1$$

$$T_1 = Q_0$$

$$T_2 = Q_0 Q_1$$

A four-bit synchronous up-counter

 

$$T_0 = 1$$

$$T_1 = Q_0$$

$$T_2 = Q_0 Q_1$$

In general we have

$$T_0 = 1$$

$$T_1 = Q_0$$

$$T_2 = Q_0 Q_1$$


$$T_3 = Q_0 Q_1 Q_2$$

...


$$T_n = Q_0 Q_1 Q_2 \cdots Q_{n-1}$$

Synchronous v.s. Asynchronous Clear

 
2-Bit Synchronous Up-Counter (without clear capability)



 2-Bit Synchronous Up-Counter (with asynchronous clear)




 2-Bit Synchronous Up-Counter (with asynchronous clear)



This is the same circuit but uses D Flip-Flops.

 
2-Bit Synchronous Up-Counter (with synchronous clear)




This counter can be cleared only on the positive clock edge.

Adding Enable Capability

A four-bit synchronous up-counter

 


Inclusion of Enable and Clear Capability

 


[Figure 5.22 from the textbook]

Inclusion of Enable and Clear Capability

 
This is the new thing relative to the previous figure, plus the clear_n line



 Providing an enable input for a D flip-flop




(a) Using a multiplexer

 

(b) Clock gating

Synchronous Counter (with D Flip-Flops)


A four-bit counter with D flip-flops

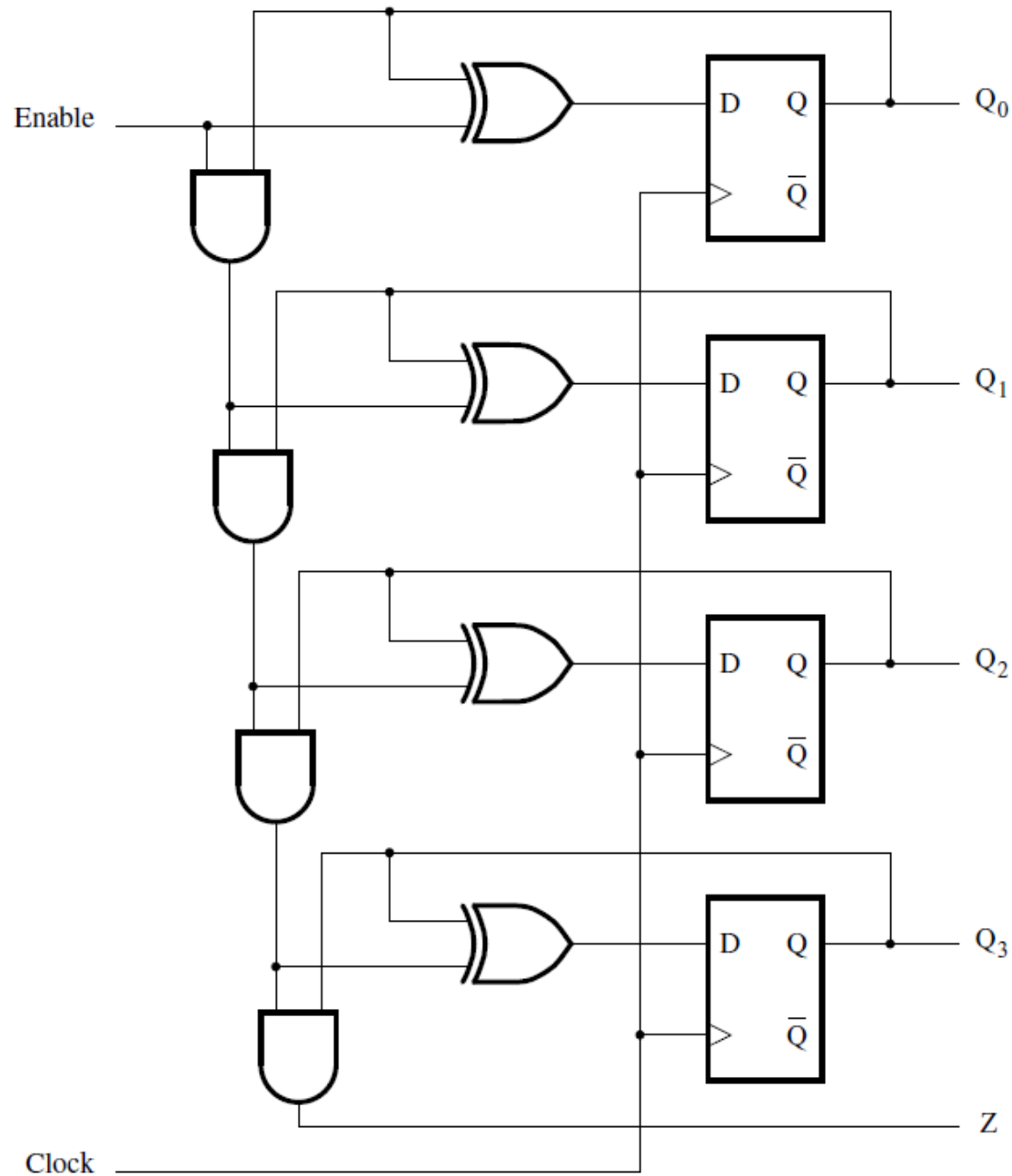

[Figure 5.23 from the textbook]


Counters with Parallel Load

A 4-bit up-counter with D flip-flops

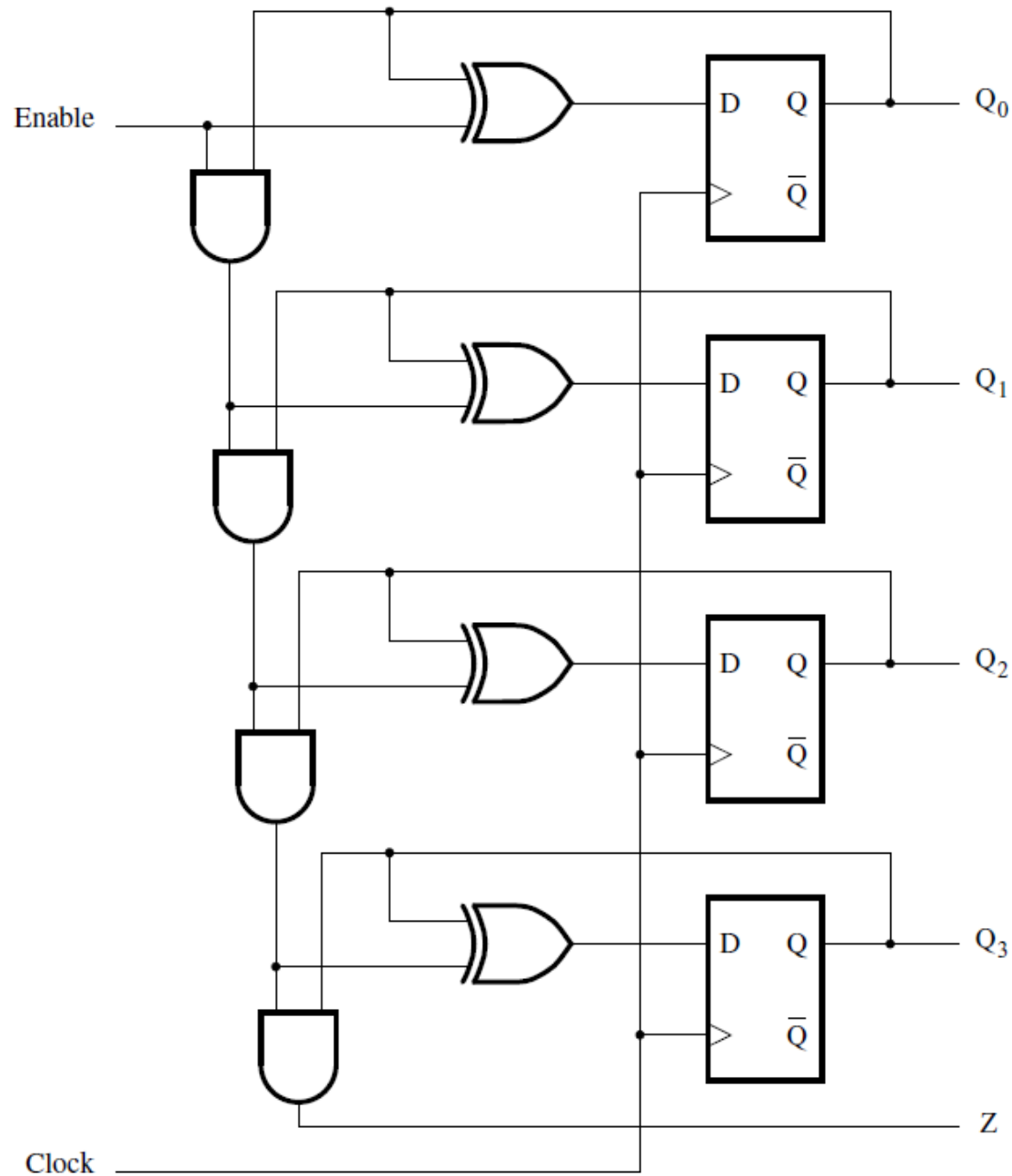


[Figure 5.23 from the textbook]

A 4-bit up-counter with D flip-flops

 


[Figure 5.23 from the textbook]

 Equivalent to this circuit with T flip-flops



 Equivalent to this circuit with T flip-flops




But has one extra output called Z, which can be used to connect two 4-bit counters to make an 8-bit counter.

When $Z=1$ the counter will go 0000 on the next clock edge, i.e., the outputs of all flip-flops are currently 1 (maximum count value).


Counters with Parallel Load

A counter with parallel-load capability

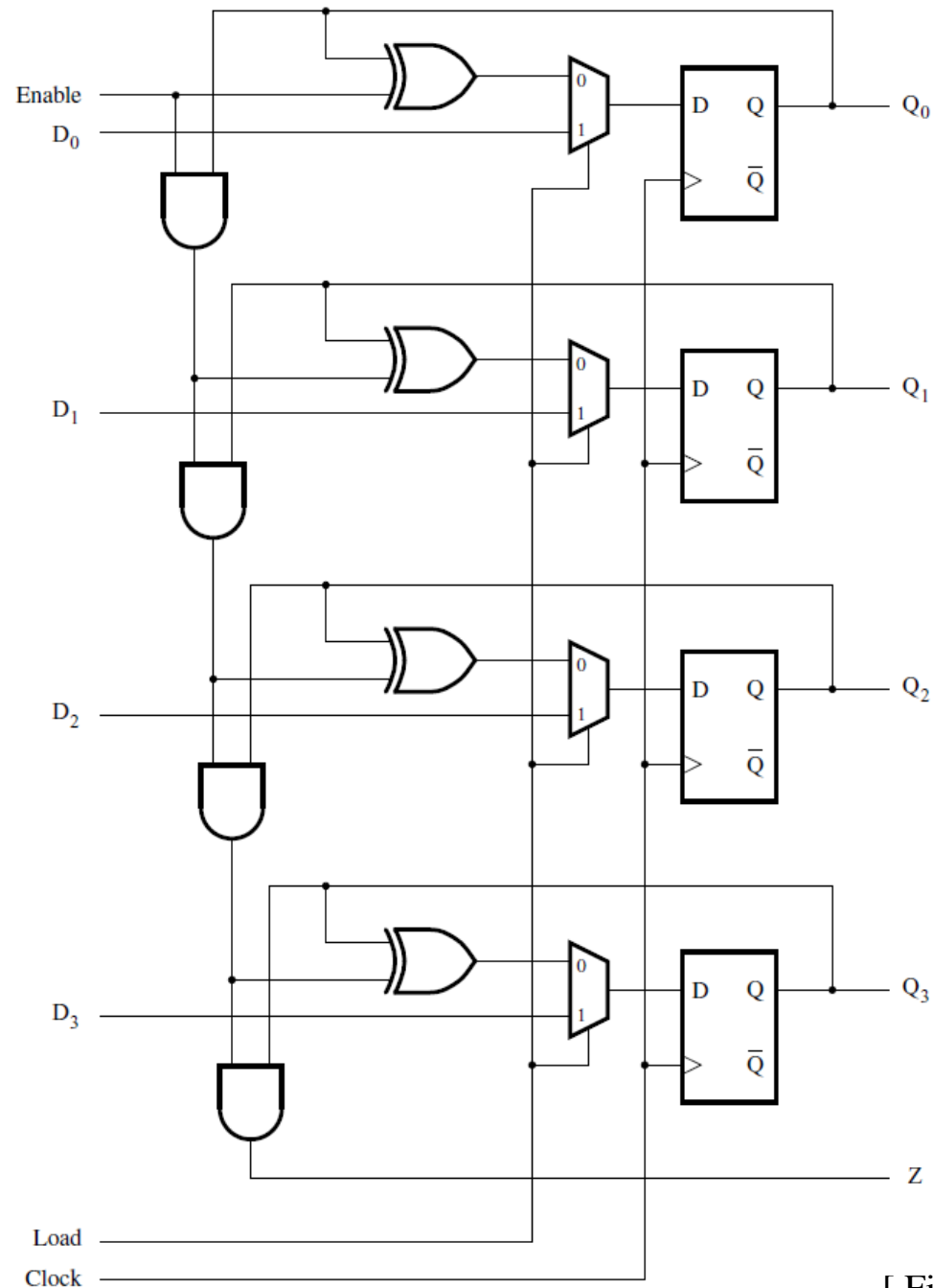


[Figure 5.24 from the textbook]

How to load the initial count value

 


Set the initial count on
the parallel load lines
(in this case 5).

How to zero a counter

 

Set "Load" to 1, to open the "1" line of the multiplexers.

How to zero a counter

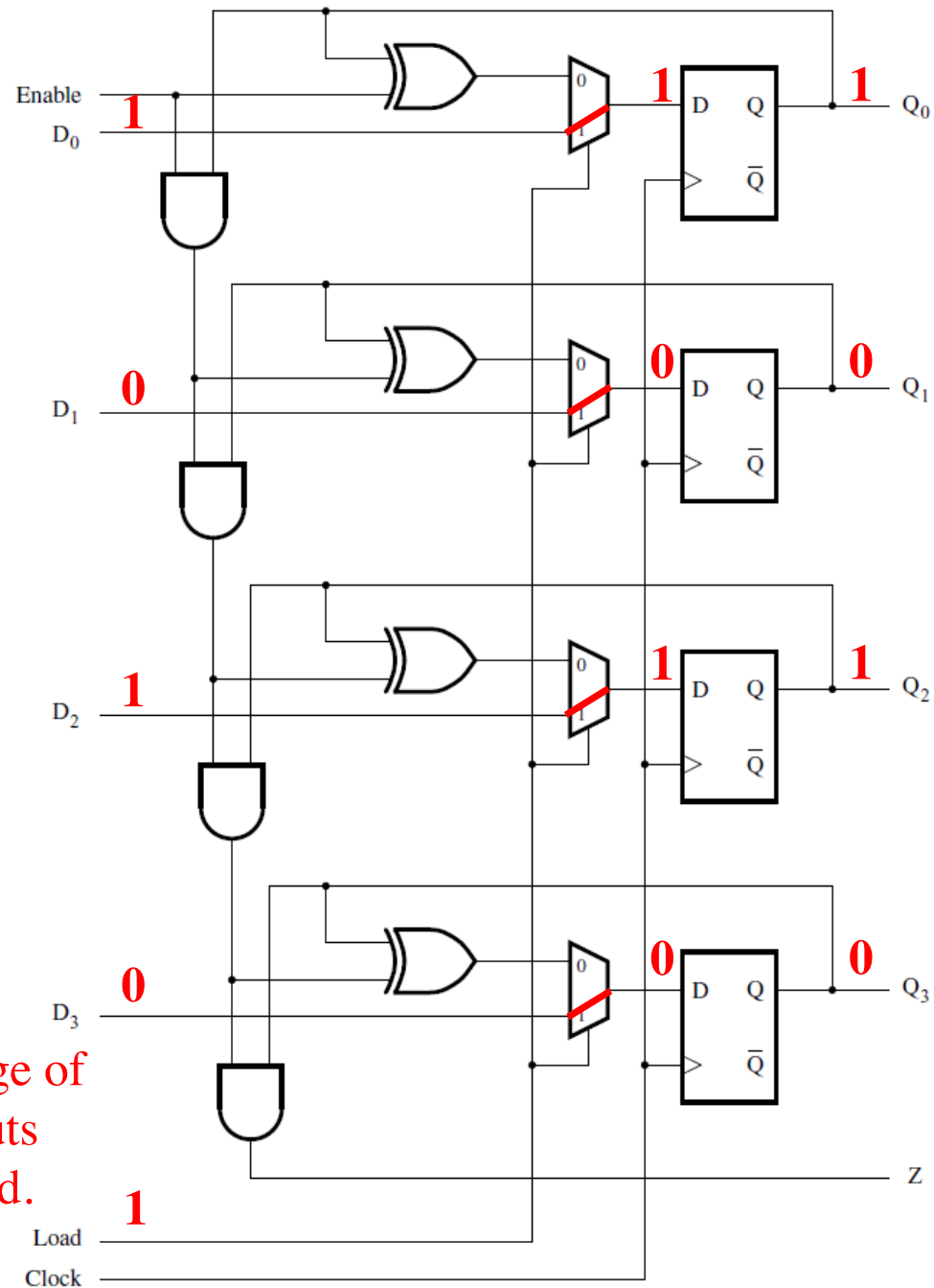


When the next positive edge of the clock arrives, the outputs of the flip-flops are updated.

Reset Synchronization


Motivation

- **An n-bit counter counts from 0, 1, ..., 2^n-1**
- **For example a 3-bit counter counts up as follow**
 - **0, 1, 2, 3, 4, 5, 6, 7, 0, 1, 2, ...**
- **What if we want it to count like this**
 - **0, 1, 2, 3, 4, 5, 0, 1, 2, 3, 4, 5, 0, 1, ...**
- **In other words, what is the cycle is not a power of 2?**


What does this circuit do?

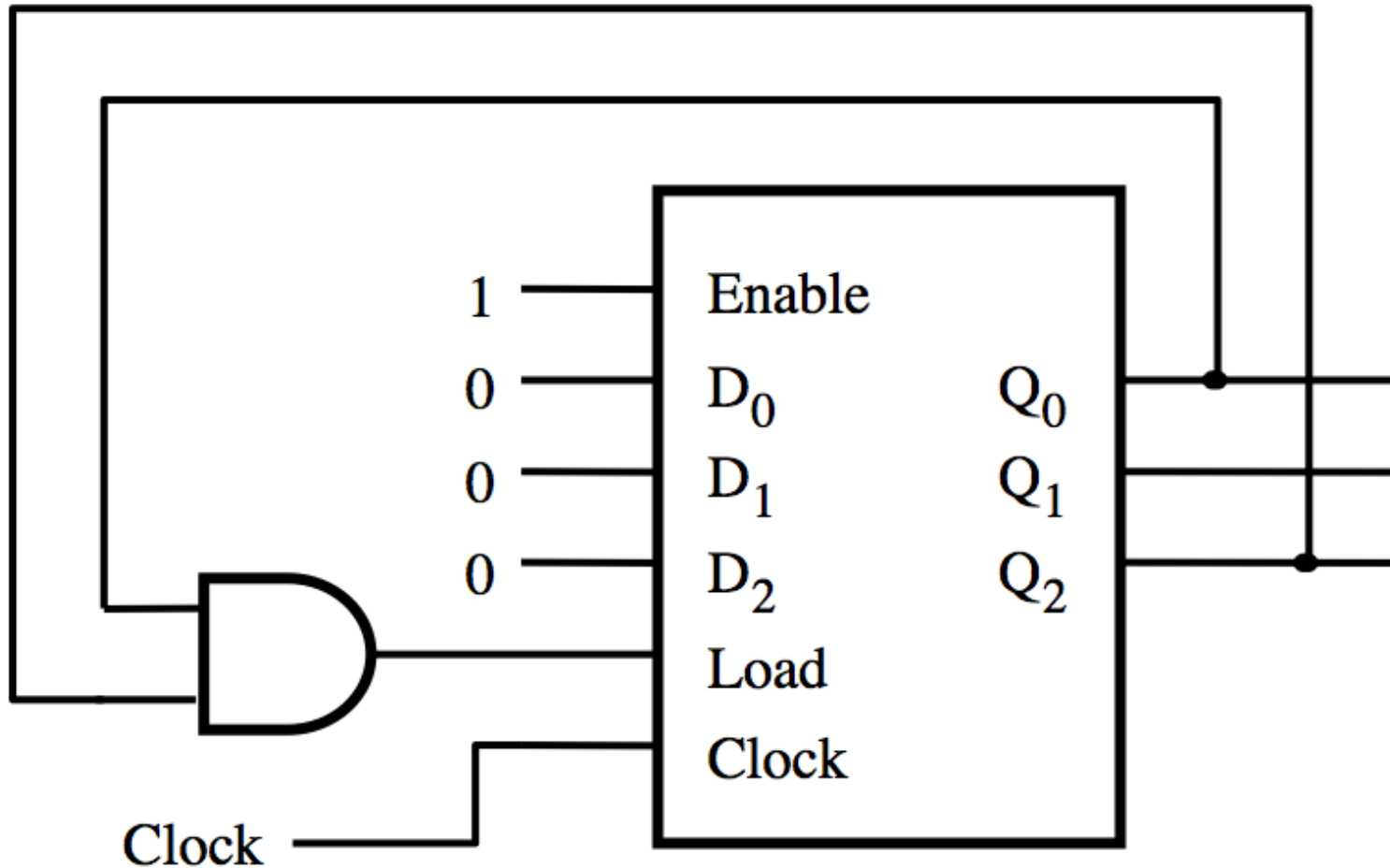

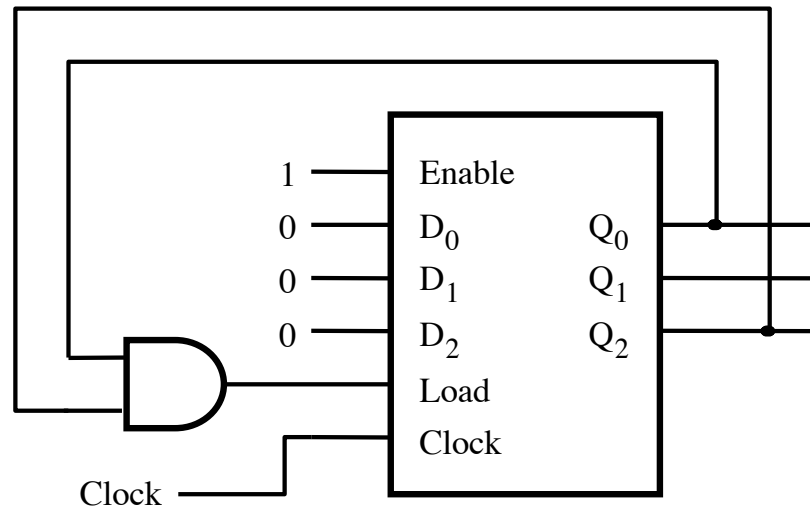A modulo-6 counter with synchronous reset




(a) Circuit

 


 (b) Timing diagram

A modulo-6 counter with asynchronous reset




(a) Circuit

 

 
(b) Timing diagram

A modulo-6 counter with asynchronous reset



 (a) Circuit

The number 5 is displayed for a very short amount of time



(b) Timing diagram

Questions?

THE END