



CprE 281: Digital Logic

Instructor: Alexander Stoytchev

<http://www.ece.iastate.edu/~alexs/classes/>

Synthesis

Using AND, OR, and NOT Gates

Administrative Stuff

- **HW2 is due on Wednesday Sep 5 @ 4pm**
- **Please write clearly on the first page (in block capital letters) the following three things:**
 - **Your First and Last Name**
 - **Your Student ID Number**
 - **Your Lab Section Letter**
 - **Staple all of your pages**
- **If any of these are missing, then you will lose 10% of your grade for that homework.**

Administrative Stuff

- **Next week we will start with Lab2**
- **It will be graded!**
- **Print the answer sheet for that lab and do the prelab at home. Otherwise you'll lose 20% of your grade for that lab.**

Labs Next Week


- **If your lab is on Mondays, i.e.,**
- **Section P: Mondays, 12:10 - 3:00 pm (Coover Hall, room 1318)**
- **You will have 2 labs in one on September 10.**
- **That is, Lab #2 and Lab #3.**

Labs Next Week


- **If your recitation is on Mondays (Sections N & P), please go to one of the other 11 recitations next week:**
- **Section U: Tuesday 11:00 AM - 1:50 PM (Coover Hall, room 2050)**
- **Section M: Tuesday 2:10 PM - 5:00 PM (Coover Hall, room 2050)**
- **Section Z: Tuesday 2:10 PM - 5:00 PM (Coover Hall, room 1318)**
- **Section J: Wednesday 8:00 AM - 10:50 AM (Coover Hall, room 1318)**
- **Section W: Wednesday 11:00 AM - 1:50 PM (Coover Hall, room 1318)**
- **Section T: Wednesday 6:10 PM - 9:00 PM (Coover Hall, room 1318)**
- **Section Q: Thursday 11:00 AM - 1:50 PM (Coover Hall, room 2050)**
- **Section V: Thursday 11:00 AM - 1:50 PM (Coover Hall, room 1318)**
- **Section L: Thursday 2:10 PM - 5:00 PM (Coover Hall, room 1318)**
- **Section K: Thursday 5:10 PM - 8:00 PM (Coover Hall, room 1318)**
- **Section G: Friday 11:00 AM - 1:50 PM (Coover Hall, room 2050)**
- **This is only for next week. And only for the recitation (first hour). You won't be able to stay for the lab as the sections are full.**

Quick Review


The Three Basic Logic Gates

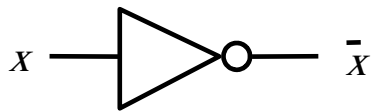

NOT gate

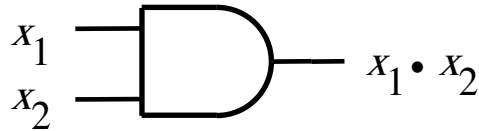


AND gate

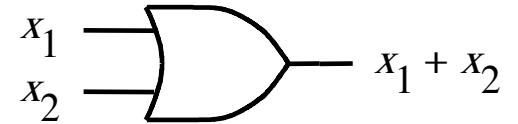


OR gate

Truth Table for NOT

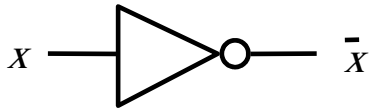


x	\bar{x}
0	1
1	0

Truth Table for AND

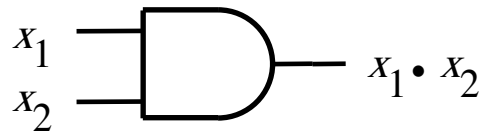

x_1	x_2	$x_1 \cdot x_2$
0	0	0
0	1	0
1	0	0
1	1	1

Truth Table for OR

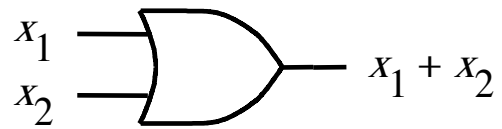

x_1	x_2	$x_1 + x_2$
0	0	0
0	1	1
1	0	1
1	1	1

Truth Tables for AND and OR

x_1	x_2	$x_1 \cdot x_2$	$x_1 + x_2$
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	1

AND

OR

Operator Precedence

- **In regular arithmetic and algebra, multiplication takes precedence over addition**
- **This is also true in Boolean algebra**

Operator Precedence

(three different ways to write the same)

$$x_1 \cdot x_2 + \bar{x}_1 \cdot \bar{x}_2$$

$$(x_1 \cdot x_2) + ((\bar{x}_1) \cdot (\bar{x}_2))$$

$$x_1x_2 + \bar{x}_1\bar{x}_2$$

DeMorgan's Theorem

$$15a. \quad \overline{x \cdot y} = \bar{x} + \bar{y}$$

$$15b. \quad \overline{x + y} = \bar{x} \cdot \bar{y}$$

Function Synthesis

Synthesize the Following Function

x_1	x_2	$f(x_1, x_2)$
0	0	1
0	1	1
1	0	0
1	1	1

1) Split the function into a sum of 4 functions

x_1	x_2	$f(x_1, x_2)$		$f_{00}(x_1, x_2)$	$f_{01}(x_1, x_2)$	$f_{10}(x_1, x_2)$	$f_{11}(x_1, x_2)$
0	0	1		1	0	0	0
0	1	1		0	1	0	0
1	0	0		0	0	1	0
1	1	1		0	0	0	1

1) Split the function into a sum of 4 functions

x_1	x_2	$f(x_1, x_2)$	$f_{00}(x_1, x_2)$	$f_{01}(x_1, x_2)$	$f_{10}(x_1, x_2)$	$f_{11}(x_1, x_2)$
0	0	1	1	0	0	0
0	1	1	0	1	0	0
1	0	0	0	0	1	0
1	1	1	0	0	0	1

$$f(x_1, x_2) = 1 \cdot f_{00} + 1 \cdot f_{01} + 0 \cdot f_{10} + 1 \cdot f_{11}$$

2) Write the expressions for all four

x_1	x_2	$f(x_1, x_2)$	$f_{00}(x_1, x_2)$	$f_{01}(x_1, x_2)$	$f_{10}(x_1, x_2)$	$f_{11}(x_1, x_2)$
0	0	1	1	0	0	0
0	1	1	0	1	0	0
1	0	0	0	0	1	0
1	1	1	0	0	0	1

$$f(x_1, x_2) = \underbrace{1 \cdot f_{00}} + \underbrace{1 \cdot f_{01}} + \underbrace{0 \cdot f_{10}} + \underbrace{1 \cdot f_{11}}$$

2) Write the expressions for all four

x_1	x_2	$f(x_1, x_2)$	$f_{00}(x_1, x_2)$	$f_{01}(x_1, x_2)$	$f_{10}(x_1, x_2)$	$f_{11}(x_1, x_2)$
0	0	1	1	0	0	0
0	1	1	0	1	0	0
1	0	0	0	0	1	0
1	1	1	0	0	0	1

$$f(x_1, x_2) = \underbrace{1 \cdot f_{00}}_{\bar{x}_1 \bar{x}_2} + \underbrace{1 \cdot f_{01}}_{\bar{x}_1 x_2} + \underbrace{0 \cdot f_{10}}_0 + \underbrace{1 \cdot f_{11}}_{x_1 x_2}$$

3) Then just add them together

x_1	x_2	$f(x_1, x_2)$	$f_{00}(x_1, x_2)$	$f_{01}(x_1, x_2)$	$f_{10}(x_1, x_2)$	$f_{11}(x_1, x_2)$
0	0	1	1	0	0	0
0	1	1	0	1	0	0
1	0	0	0	0	1	0
1	1	1	0	0	0	1

$$f(x_1, x_2) = \underbrace{1 \cdot f_{00}} + \underbrace{1 \cdot f_{01}} + \underbrace{0 \cdot f_{10}} + \underbrace{1 \cdot f_{11}}$$

$$f(x_1, x_2) = \bar{x}_1 \bar{x}_2 + \bar{x}_1 x_2 + 0 + x_1 x_2$$

3) Then just add them together

x_1	x_2	$f(x_1, x_2)$		$f_{00}(x_1, x_2)$	$f_{01}(x_1, x_2)$	$f_{10}(x_1, x_2)$	$f_{11}(x_1, x_2)$
0	0	1		1	0	0	0
0	1	1		0	1	0	0
1	0	0		0	0	1	0
1	1	1		0	0	0	1

$$f(x_1, x_2) = \bar{x}_1\bar{x}_2 + \bar{x}_1x_2 + 0 + x_1x_2$$

A function to be synthesized

x_1	x_2	$f(x_1, x_2)$
0	0	1
0	1	1
1	0	0
1	1	1

**Let's look at it row by row.
How can we express the last row?**

x_1	x_2	$f(x_1, x_2)$
0	0	1
0	1	1
1	0	0
1	1	1



**Let's look at it row by row.
How can we express the last row?**

x_1	x_2	$f(x_1, x_2)$
0	0	1
0	1	1
1	0	0
1	1	1

x_1x_2


**Let's look at it row by row.
How can we express the last row?**

x_1	x_2	$f(x_1, x_2)$
0	0	1
0	1	1
1	0	0
1	1	1

What about this row?


x_1	x_2	$f(x_1, x_2)$
0	0	1
0	1	1
1	0	0
1	1	1

 x_1
 x_2

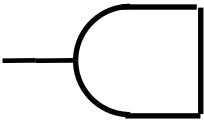What about this row?

x_1	x_2	$f(x_1, x_2)$
0	0	1
0	1	1
1	0	0
1	1	1

$\bar{x}_1 x_2$

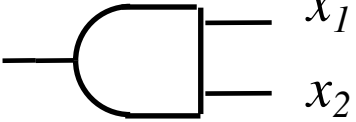

The diagram shows an AND gate with two inputs labeled x_1 and x_2 . The output of the gate is connected to the output column of the truth table.

What about this row?

x_1	x_2	$f(x_1, x_2)$
0	0	1
0	1	1
1	0	0
1	1	1

The table shows a function $f(x_1, x_2)$ with four rows. The second row, where $x_1=0$ and $x_2=1$, has a value of 1 highlighted in green. To the right of the table, two logic diagrams are shown. The top diagram is an AND gate with inputs x_1 and x_2 , followed by a NOT gate, representing the expression $\neg(x_1 \wedge x_2)$. The bottom diagram is a simple AND gate with inputs x_1 and x_2 , representing the expression $x_1 \wedge x_2$.

What about the first row?

x_1	x_2	$f(x_1, x_2)$
0	0	1
0	1	1
1	0	0
1	1	1


Logic circuit diagrams illustrating the function $f(x_1, x_2)$:

- The first row (0, 0, 1) is highlighted in green, indicating the focus of the question.
- The second row (0, 1, 1) is implemented by an AND gate followed by a NOT gate (inverter). The output is labeled x_1 .
- The fourth row (1, 1, 1) is implemented by an AND gate. The output is labeled x_2 .


What about the first row?

x_1	x_2	$f(x_1, x_2)$
0	0	1
0	1	1
1	0	0
1	1	1

$\bar{x}_1\bar{x}_2$

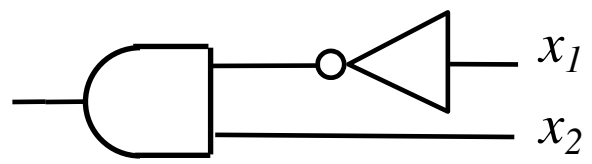

x_1
 x_2

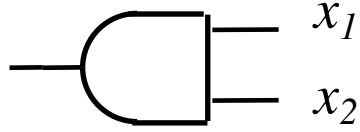

x_1
 x_2

What about the first row?

x_1	x_2	$f(x_1, x_2)$
0	0	1
0	1	1
1	0	0
1	1	1

Logic diagrams illustrating the implementation of the function $f(x_1, x_2)$ for the first row (0, 0):

- The first diagram shows an AND gate with inputs x_1 and x_2 . The output is inverted by a NOT gate, resulting in $\neg(x_1 \wedge x_2)$.
- The second diagram shows an AND gate with inputs x_1 and x_2 . The output of the AND gate is inverted by a NOT gate, resulting in $\neg(x_1 \wedge x_2)$.
- The third diagram shows an AND gate with inputs x_1 and x_2 , resulting in $x_1 \wedge x_2$.


Finally, what about the zero?

x_1	x_2	$f(x_1, x_2)$
0	0	1
0	1	1
1	0	0
1	1	1


The table is accompanied by logic diagrams for each row:

- Row 1 (0, 0): A logic diagram with two inputs, x_1 and x_2 . Both inputs pass through inverters (NOT gates) and are then connected to the inputs of an AND gate. The output of this AND gate is the value 1.
- Row 2 (0, 1): A logic diagram with two inputs, x_1 and x_2 . Input x_1 passes through an inverter and is connected to the top input of an AND gate. Input x_2 is connected directly to the bottom input of the AND gate. The output of this AND gate is the value 1.
- Row 3 (1, 0): A logic diagram with two inputs, x_1 and x_2 . Input x_1 is connected directly to the top input of an AND gate. Input x_2 passes through an inverter and is connected to the bottom input of the AND gate. The output of this AND gate is the value 0, which is highlighted in a green box.
- Row 4 (1, 1): A logic diagram with two inputs, x_1 and x_2 . Both inputs are connected directly to the inputs of an AND gate. The output of this AND gate is the value 1.


Putting it all together

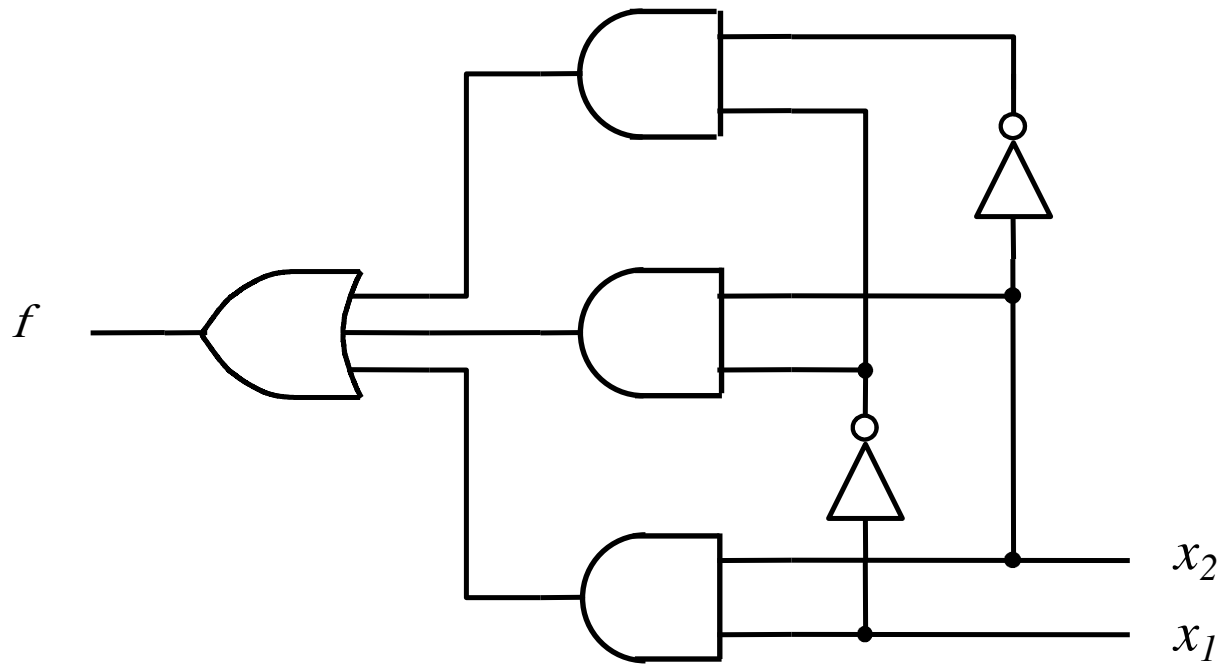

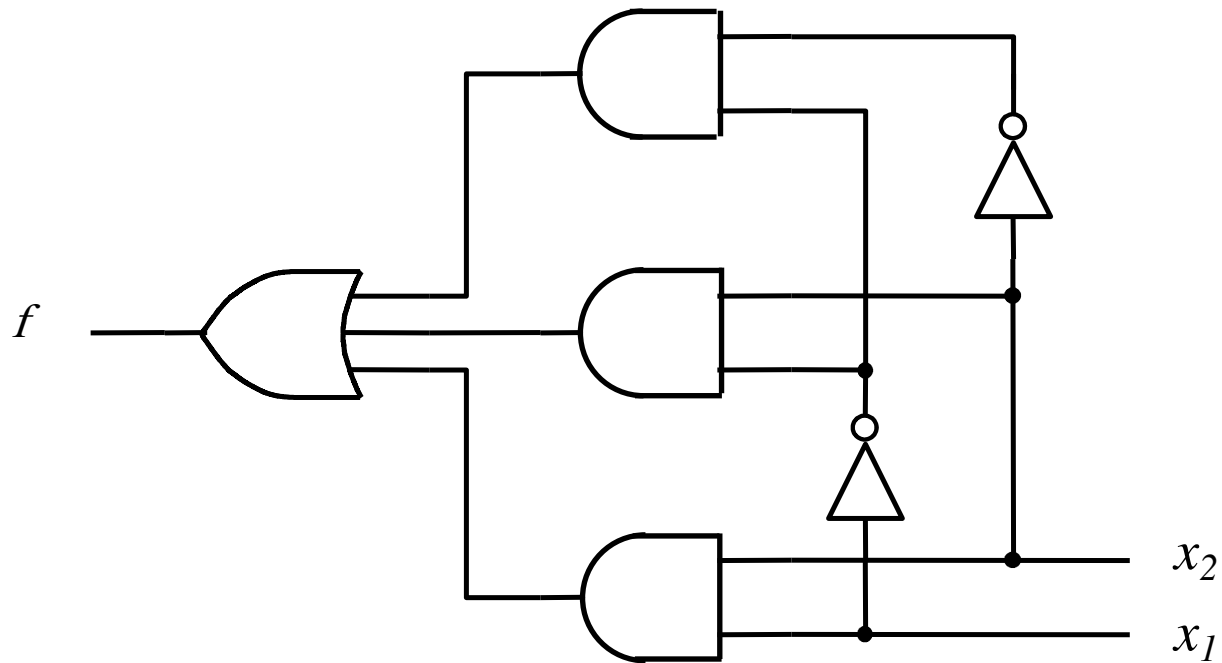
Let's verify that this circuit implements correctly the target truth table




Putting it all together

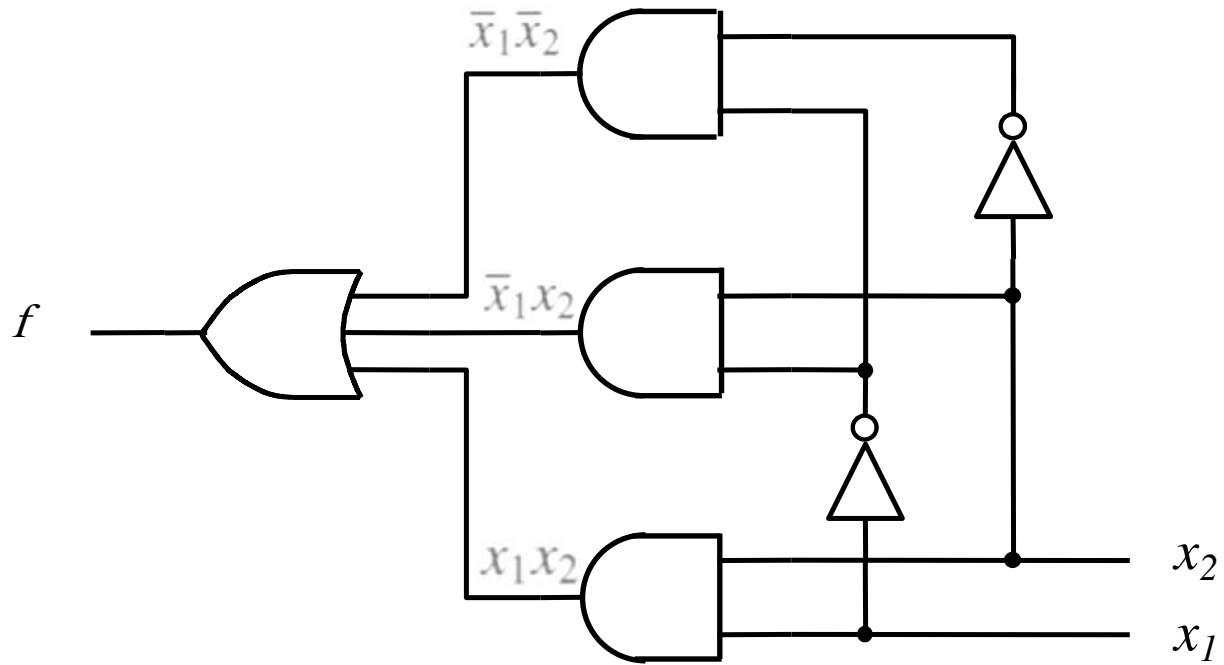

Putting it all together

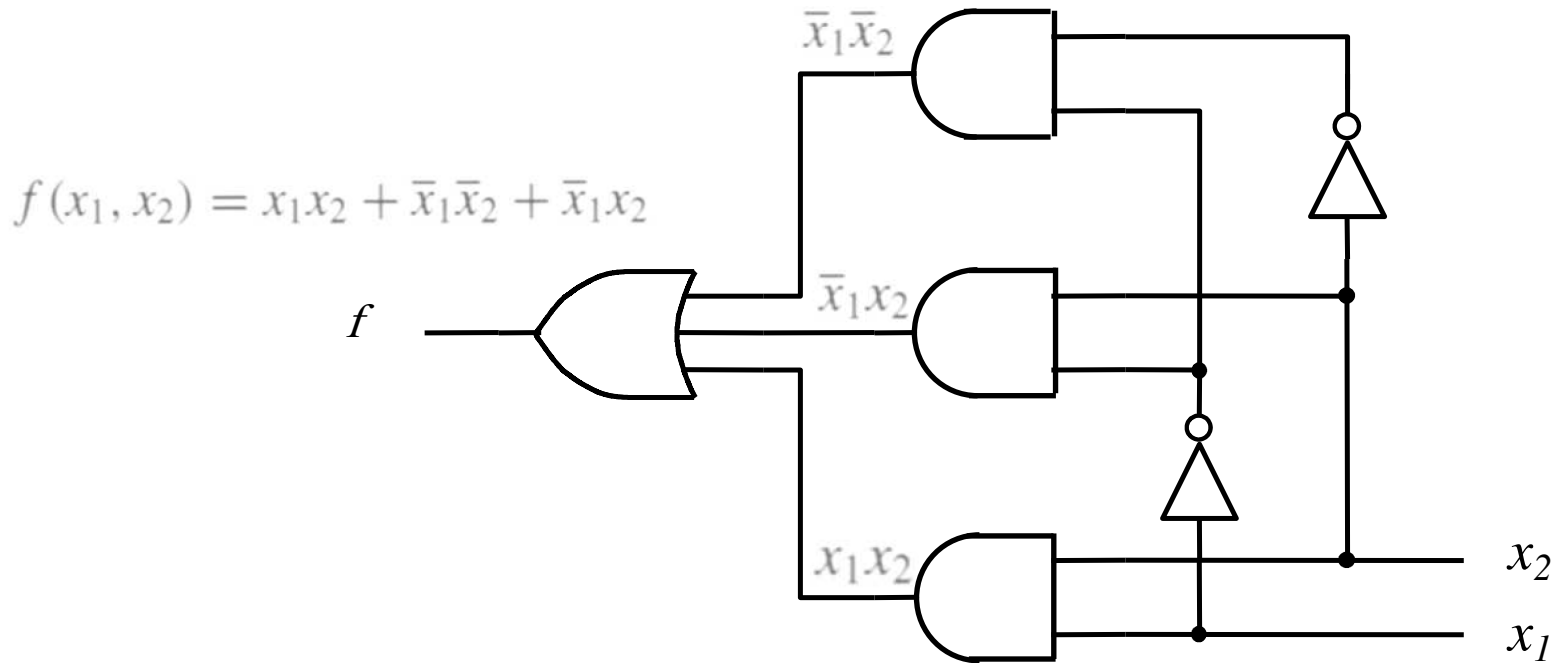

Canonical Sum-Of-Products (SOP)

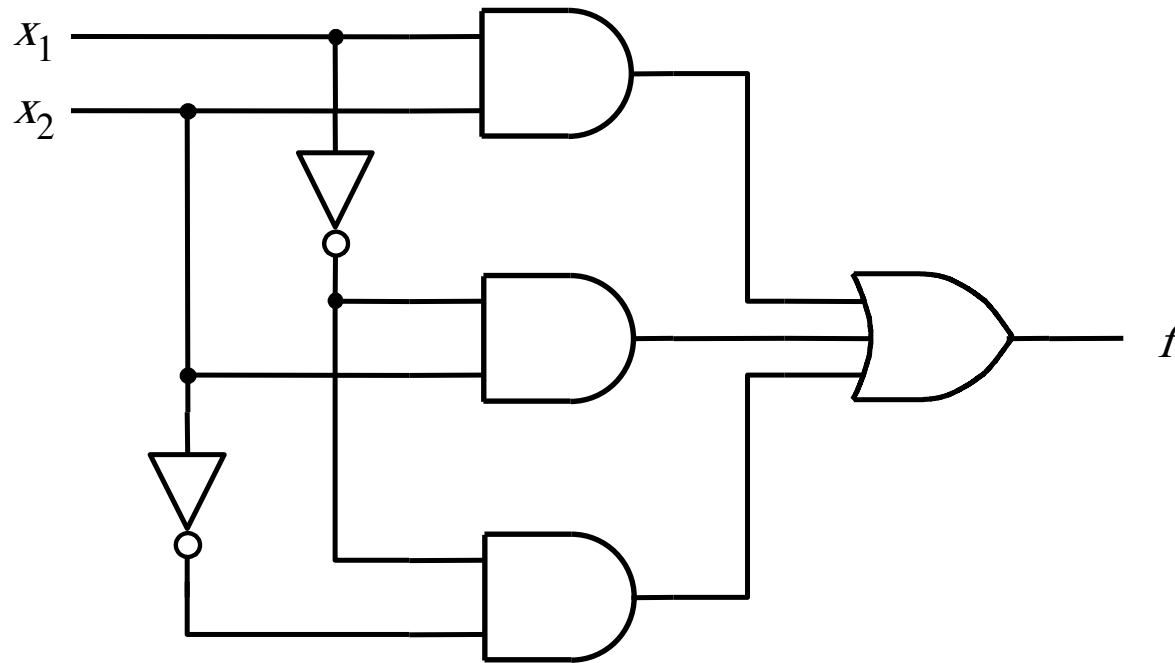


$$f(x_1, x_2) = x_1x_2 + \bar{x}_1\bar{x}_2 + \bar{x}_1x_2$$

Summary of This Procedure

- **Get the truth table of the function**
- **Form a product term (AND gate) for each row of the table for which the function is 1**
- **Each product term contains all input variables**
- **In each row, if $x_i = 1$ enter it as x_i , otherwise use $\overline{x_i}$**
- **Sum all of these products (OR gate) to get the function**

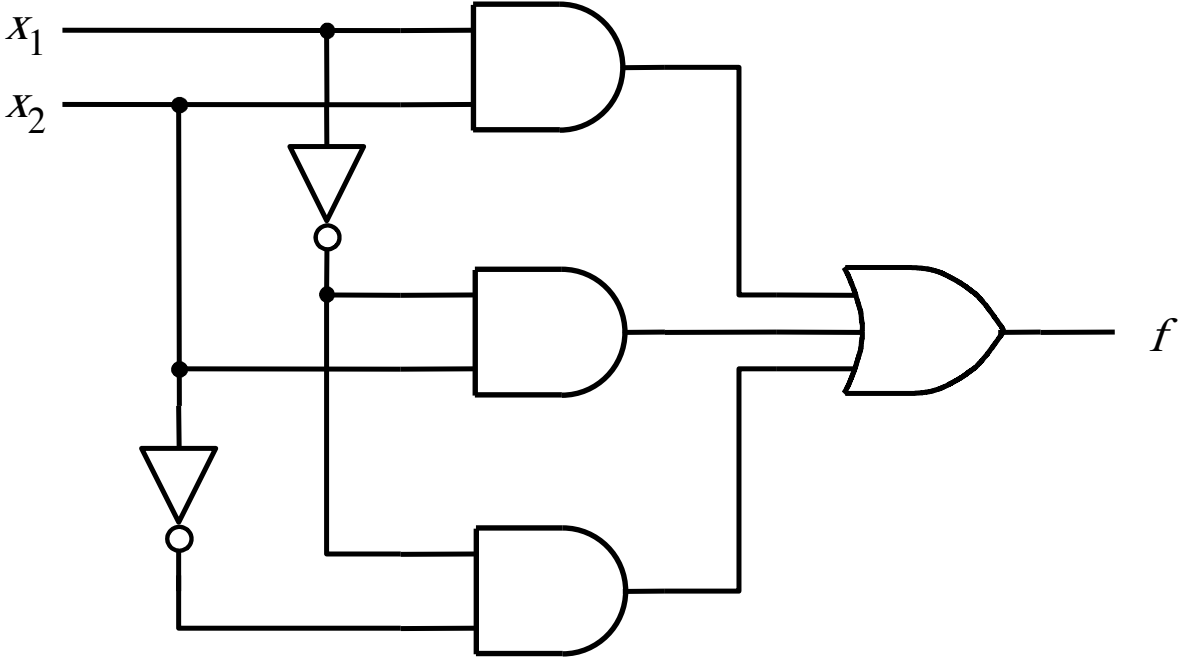Two implementations for the same function



(a) Canonical sum-of-products



(b) Minimal-cost realization

[Figure 2.20 from the textbook]

Simplification Steps

$$f(x_1, x_2) = x_1x_2 + \bar{x}_1\bar{x}_2 + \bar{x}_1x_2$$

Simplification Steps

$$f(x_1, x_2) = x_1x_2 + \bar{x}_1\bar{x}_2 + \bar{x}_1x_2$$

replicate
this term

$$f(x_1, x_2) = x_1x_2 + \bar{x}_1\bar{x}_2 + \bar{x}_1x_2 + \bar{x}_1x_2$$

Simplification Steps

$$f(x_1, x_2) = x_1x_2 + \bar{x}_1\bar{x}_2 + \bar{x}_1x_2$$

group
these terms

$$f(x_1, x_2) = x_1x_2 + \bar{x}_1\bar{x}_2 + \bar{x}_1x_2 + \bar{x}_1x_2$$

$$f(x_1, x_2) = (x_1 + \bar{x}_1)x_2 + \bar{x}_1(\bar{x}_2 + x_2)$$

Simplification Steps

$$f(x_1, x_2) = x_1x_2 + \bar{x}_1\bar{x}_2 + \bar{x}_1x_2$$

$$f(x_1, x_2) = x_1x_2 + \bar{x}_1\bar{x}_2 + \bar{x}_1x_2 + \bar{x}_1x_2$$

These two terms are trivially equal to 1

$$f(x_1, x_2) = (x_1 + \bar{x}_1)x_2 + \bar{x}_1(\bar{x}_2 + x_2)$$

$$f(x_1, x_2) = 1 \cdot x_2 + \bar{x}_1 \cdot 1$$

Simplification Steps

$$f(x_1, x_2) = x_1x_2 + \bar{x}_1\bar{x}_2 + \bar{x}_1x_2$$

$$f(x_1, x_2) = x_1x_2 + \bar{x}_1\bar{x}_2 + \bar{x}_1x_2 + \bar{x}_1x_2$$

$$f(x_1, x_2) = (x_1 + \bar{x}_1)x_2 + \bar{x}_1(\bar{x}_2 + x_2)$$


$$f(x_1, x_2) = \boxed{1} \cdot x_2 + \bar{x}_1 \cdot \boxed{1}$$

Drop the 1's


$$f(x_1, x_2) = x_2 + \bar{x}_1$$

Minimal-cost realization

$$f(x_1, x_2) = x_2 + \bar{x}_1$$

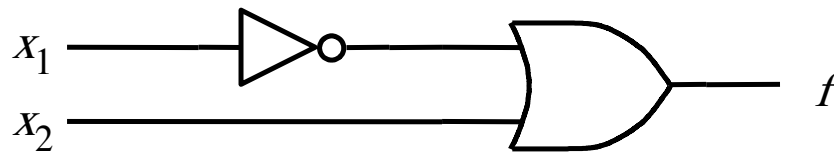

Let's look at another problem

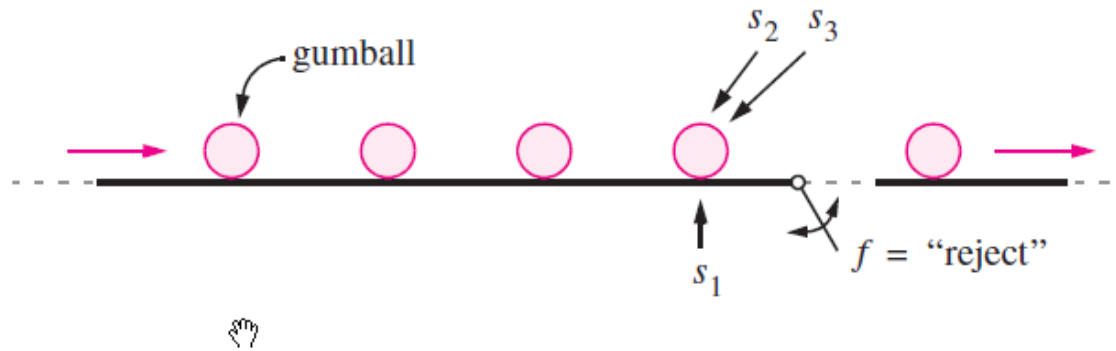

(a) Conveyor and sensors

s_1	s_2	s_3	f
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

(b) Truth table

Let's look at another problem

s_1	s_2	s_3	f
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Let's look at another problem

s_1	s_2	s_3	f
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Let's look at another problem

s_1	s_2	s_3	f	
0	0	0	0	
0	0	1	1	$\bar{s}_1 \bar{s}_2 s_3$
0	1	0	0	
0	1	1	1	$\bar{s}_1 s_2 s_3$
1	0	0	0	
1	0	1	1	$s_1 \bar{s}_2 s_3$
1	1	0	1	$s_1 s_2 \bar{s}_3$
1	1	1	1	$s_1 s_2 s_3$

Let's look at another problem

s_1	s_2	s_3	f	
0	0	0	0	
0	0	1	1	$\bar{s}_1\bar{s}_2s_3$
0	1	0	0	
0	1	1	1	$\bar{s}_1s_2s_3$
1	0	0	0	
1	0	1	1	$s_1\bar{s}_2s_3$
1	1	0	1	$s_1s_2\bar{s}_3$
1	1	1	1	$s_1s_2s_3$


$$f = \bar{s}_1\bar{s}_2s_3 + \bar{s}_1s_2s_3 + s_1\bar{s}_2s_3 + s_1s_2\bar{s}_3 + s_1s_2s_3$$

Let's look at another problem (minimization)

$$\begin{aligned} f &= \bar{s}_1 \bar{s}_2 s_3 + \bar{s}_1 s_2 s_3 + s_1 \bar{s}_2 s_3 + s_1 s_2 s_3 + s_1 s_2 \bar{s}_3 + s_1 s_2 s_3 \\ &= \bar{s}_1 s_3 (\bar{s}_2 + s_2) + s_1 s_3 (\bar{s}_2 + s_2) + s_1 s_2 (\bar{s}_3 + s_3) \\ &= \bar{s}_1 s_3 + s_1 s_3 + s_1 s_2 \\ &= s_3 + s_1 s_2 \end{aligned}$$

Let's look at another problem (minimization)
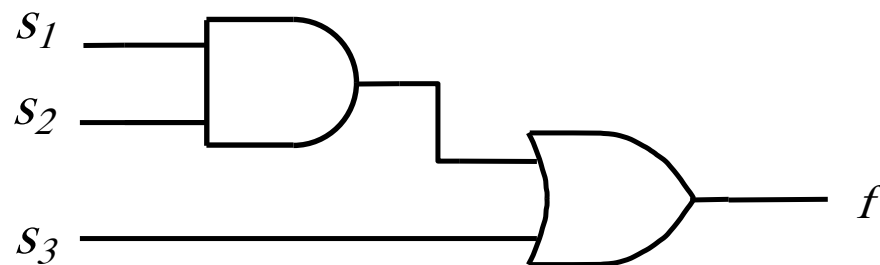
$$\begin{aligned} f &= \bar{s}_1\bar{s}_2s_3 + \bar{s}_1s_2s_3 + s_1\bar{s}_2s_3 + s_1s_2s_3 + s_1s_2\bar{s}_3 + s_1s_2s_3 \\ &= \bar{s}_1s_3(\bar{s}_2 + s_2) + s_1s_3(\bar{s}_2 + s_2) + s_1s_2(\bar{s}_3 + s_3) \\ &= \bar{s}_1s_3 + s_1s_3 + s_1s_2 \\ &= s_3 + s_1s_2 \end{aligned}$$



Minterms and Maxterms

Row number	x_1	x_2	Minterm	Maxterm
0	0	0	$m_0 = \bar{x}_1\bar{x}_2$	$M_0 = x_1 + x_2$
1	0	1	$m_1 = \bar{x}_1x_2$	$M_1 = x_1 + \bar{x}_2$
2	1	0	$m_2 = x_1\bar{x}_2$	$M_2 = \bar{x}_1 + x_2$
3	1	1	$m_3 = x_1x_2$	$M_3 = \bar{x}_1 + \bar{x}_2$

Minterms and Maxterms

Row number	x_1	x_2	Minterm	Maxterm
0	0	0	$m_0 = \bar{x}_1 \bar{x}_2$	$M_0 = x_1 + x_2$
1	0	1	$m_1 = \bar{x}_1 x_2$	$M_1 = x_1 + \bar{x}_2$
2	1	0	$m_2 = x_1 \bar{x}_2$	$M_2 = \bar{x}_1 + x_2$
3	1	1	$m_3 = x_1 x_2$	$M_3 = \bar{x}_1 + \bar{x}_2$

Use these for
Sum-of-Products
Minimization
(1's of the function)

Use these for
Product-of-Sums
Minimization
(0's of the function)

Sum-of-Products Form

(uses the **ones** of the function)

Sum-of-Products Form

(for the AND logic function)

Row number	x_1	x_2	Minterm	$f(x_1, x_2)$
0	0	0	$m_0 = \bar{x}_1\bar{x}_2$	0
1	0	1	$m_1 = \bar{x}_1x_2$	0
2	1	0	$m_2 = x_1\bar{x}_2$	0
3	1	1	$m_3 = x_1x_2$	1

Sum-of-Products Form

(for the AND logic function)

Row number	x_1	x_2	Minterm	$f(x_1, x_2)$
0	0	0	$m_0 = \bar{x}_1\bar{x}_2$	0
1	0	1	$m_1 = \bar{x}_1x_2$	0
2	1	0	$m_2 = x_1\bar{x}_2$	0
3	1	1	$m_3 = x_1x_2$	1

Sum-of-Products Form

(for the AND logic function)

Row number	x_1	x_2	Minterm	$f(x_1, x_2)$
0	0	0	$m_0 = \bar{x}_1 \bar{x}_2$	0
1	0	1	$m_1 = \bar{x}_1 x_2$	0
2	1	0	$m_2 = x_1 \bar{x}_2$	0
3	1	1	$m_3 = x_1 x_2$	1

$$f(x_1, x_2) = m_3 = x_1 x_2$$

(In this case there is just one product and there is no need for a sum)

Another Example

Sum-of-Products Form

Row number	x_1	x_2	Minterm	$f(x_1, x_2)$
0	0	0	$m_0 = \bar{x}_1\bar{x}_2$	1
1	0	1	$m_1 = \bar{x}_1x_2$	1
2	1	0	$m_2 = x_1\bar{x}_2$	0
3	1	1	$m_3 = x_1x_2$	1

Sum-of-Products Form

Row number	x_1	x_2	Minterm	$f(x_1, x_2)$
0	0	0	$m_0 = \bar{x}_1\bar{x}_2$	1
1	0	1	$m_1 = \bar{x}_1x_2$	1
2	1	0	$m_2 = x_1\bar{x}_2$	0
3	1	1	$m_3 = x_1x_2$	1

Sum-of-Products Form

Row number	x_1	x_2	Minterm	$f(x_1, x_2)$
0	0	0	$m_0 = \bar{x}_1\bar{x}_2$	1
1	0	1	$m_1 = \bar{x}_1x_2$	1
2	1	0	$m_2 = x_1\bar{x}_2$	0
3	1	1	$m_3 = x_1x_2$	1

$$\begin{aligned}f &= m_0 \cdot 1 + m_1 \cdot 1 + m_2 \cdot 0 + m_3 \cdot 1 \\&= m_0 + m_1 + m_3 \\&= \bar{x}_1\bar{x}_2 + \bar{x}_1x_2 + x_1x_2\end{aligned}$$

Product-of-Sums Form

(uses the **zeros** of the function)

Product-of-Sums Form (for the OR logic function)

Row number	x_1	x_2	Maxterm	$f(x_1, x_2)$
0	0	0	$M_0 = x_1 + x_2$	0
1	0	1	$M_1 = x_1 + \bar{x}_2$	1
2	1	0	$M_2 = \bar{x}_1 + x_2$	1
3	1	1	$M_3 = \bar{x}_1 + \bar{x}_2$	1

Product-of-Sums Form (for the OR logic function)

Row number	x_1	x_2	Maxterm	$f(x_1, x_2)$
0	0	0	$M_0 = x_1 + x_2$	0
1	0	1	$M_1 = x_1 + \bar{x}_2$	1
2	1	0	$M_2 = \bar{x}_1 + x_2$	1
3	1	1	$M_3 = \bar{x}_1 + \bar{x}_2$	1

Product-of-Sums Form (for the OR logic function)

Row number	x_1	x_2	Maxterm	$f(x_1, x_2)$
0	0	0	$M_0 = x_1 + x_2$	0
1	0	1	$M_1 = x_1 + \bar{x}_2$	1
2	1	0	$M_2 = \bar{x}_1 + x_2$	1
3	1	1	$M_3 = \bar{x}_1 + \bar{x}_2$	1

$$f(x_1, x_2) = M_0 = x_1 + x_2$$

(In this case there is just one sum and there is no need for a product)

Another Example

Product-of-Sums Form

Row number	x_1	x_2	Maxterm	$f(x_1, x_2)$
0	0	0	$M_0 = x_1 + x_2$	1
1	0	1	$M_1 = x_1 + \bar{x}_2$	1
2	1	0	$M_2 = \bar{x}_1 + x_2$	0
3	1	1	$M_3 = \bar{x}_1 + \bar{x}_2$	1

We need to minimize using the zeros of the function f .
 But let's first minimize the inverse of f , i.e., \bar{f} .

Product-of-Sums Form

Row number	x_1	x_2	Maxterm	$f(x_1, x_2)$	$\overline{f}(x_1, x_2)$
0	0	0	$M_0 = x_1 + x_2$	1	0
1	0	1	$M_1 = x_1 + \overline{x_2}$	1	0
2	1	0	$M_2 = \overline{x_1} + x_2$	0	1
3	1	1	$M_3 = \overline{x_1} + \overline{x_2}$	1	0

Product-of-Sums Form

Row number	x_1	x_2	Maxterm	$f(x_1, x_2)$	$\overline{f}(x_1, x_2)$
0	0	0	$M_0 = x_1 + x_2$	1	0
1	0	1	$M_1 = x_1 + \overline{x}_2$	1	0
2	1	0	$M_2 = \overline{x}_1 + x_2$	0	1
3	1	1	$M_3 = \overline{x}_1 + \overline{x}_2$	1	0

$$\begin{aligned}\overline{f}(x_1, x_2) &= m_2 \\ &= x_1 \overline{x}_2\end{aligned}$$

Product-of-Sums Form

Row number	x_1	x_2	Maxterm	$f(x_1, x_2)$	$\overline{f}(x_1, x_2)$
0	0	0	$M_0 = x_1 + x_2$	1	0
1	0	1	$M_1 = x_1 + \overline{x}_2$	1	0
2	1	0	$M_2 = \overline{x}_1 + x_2$	0	1
3	1	1	$M_3 = \overline{x}_1 + \overline{x}_2$	1	0

$$\begin{aligned} \overline{\overline{f}} &= f = \overline{x_1 \overline{x}_2} & \overline{f}(x_1, x_2) &= m_2 \\ &= \overline{x}_1 + x_2 & &= x_1 \overline{x}_2 \end{aligned}$$

Product-of-Sums Form

Row number	x_1	x_2	Maxterm	$f(x_1, x_2)$	$\overline{f}(x_1, x_2)$
0	0	0	$M_0 = x_1 + x_2$	1	0
1	0	1	$M_1 = x_1 + \overline{x}_2$	1	0
2	1	0	$M_2 = \overline{x}_1 + x_2$	0	1
3	1	1	$M_3 = \overline{x}_1 + \overline{x}_2$	1	0

$$\begin{aligned} \overline{\overline{f}} &= f = \overline{\overline{x_1 \overline{x}_2}} & \overline{f}(x_1, x_2) &= m_2 \\ &= \overline{\overline{x}_1 + x_2} & &= x_1 \overline{x}_2 \end{aligned}$$

$$f = \overline{m}_2 = M_2$$

Minterms and Maxterms (with three variables)

Row number	x_1	x_2	x_3	Minterm	Maxterm
0	0	0	0	$m_0 = \bar{x}_1\bar{x}_2\bar{x}_3$	$M_0 = x_1 + x_2 + x_3$
1	0	0	1	$m_1 = \bar{x}_1\bar{x}_2x_3$	$M_1 = x_1 + x_2 + \bar{x}_3$
2	0	1	0	$m_2 = \bar{x}_1x_2\bar{x}_3$	$M_2 = x_1 + \bar{x}_2 + x_3$
3	0	1	1	$m_3 = \bar{x}_1x_2x_3$	$M_3 = x_1 + \bar{x}_2 + \bar{x}_3$
4	1	0	0	$m_4 = x_1\bar{x}_2\bar{x}_3$	$M_4 = \bar{x}_1 + x_2 + x_3$
5	1	0	1	$m_5 = x_1\bar{x}_2x_3$	$M_5 = \bar{x}_1 + x_2 + \bar{x}_3$
6	1	1	0	$m_6 = x_1x_2\bar{x}_3$	$M_6 = \bar{x}_1 + \bar{x}_2 + x_3$
7	1	1	1	$m_7 = x_1x_2x_3$	$M_7 = \bar{x}_1 + \bar{x}_2 + \bar{x}_3$

A three-variable function

Row number	x_1	x_2	x_3	$f(x_1, x_2, x_3)$
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	0
4	1	0	0	1
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

Sum-of-Products Form

Row number	x_1	x_2	x_3	$f(x_1, x_2, x_3)$
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	0
4	1	0	0	1
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

Sum-of-Products Form

Row number	x_1	x_2	x_3	$f(x_1, x_2, x_3)$
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	0
4	1	0	0	1
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

$$f(x_1, x_2, x_3) = \bar{x}_1\bar{x}_2x_3 + x_1\bar{x}_2\bar{x}_3 + x_1\bar{x}_2x_3 + x_1x_2\bar{x}_3$$

Sum-of-Products Form

Row number	x_1	x_2	x_3	$f(x_1, x_2, x_3)$
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	0
4	1	0	0	1
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

$$f(x_1, x_2, x_3) = \bar{x}_1\bar{x}_2x_3 + x_1\bar{x}_2\bar{x}_3 + x_1\bar{x}_2x_3 + x_1x_2\bar{x}_3$$

$$\begin{aligned} f &= (\bar{x}_1 + x_1)\bar{x}_2x_3 + x_1(\bar{x}_2 + x_2)\bar{x}_3 \\ &= 1 \cdot \bar{x}_2x_3 + x_1 \cdot 1 \cdot \bar{x}_3 \\ &= \bar{x}_2x_3 + x_1\bar{x}_3 \end{aligned}$$

A three-variable function

Row number	x_1	x_2	x_3	$f(x_1, x_2, x_3)$
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	0
4	1	0	0	1
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

Product-of-Sums Form

Row number	x_1	x_2	x_3	$f(x_1, x_2, x_3)$
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	0
4	1	0	0	1
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

Product-of-Sums Form

Row number	x_1	x_2	x_3	$f(x_1, x_2, x_3)$
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	0
4	1	0	0	1
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

$$f = \overline{m_0 + m_2 + m_3 + m_7}$$

$$= \overline{m_0} \cdot \overline{m_2} \cdot \overline{m_3} \cdot \overline{m_7}$$

$$= M_0 \cdot M_2 \cdot M_3 \cdot M_7$$

$$= (x_1 + x_2 + x_3)(x_1 + \bar{x}_2 + x_3)(x_1 + \bar{x}_2 + \bar{x}_3)(\bar{x}_1 + \bar{x}_2 + \bar{x}_3)$$

Product-of-Sums Form

Row number	x_1	x_2	x_3	$f(x_1, x_2, x_3)$
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	0
4	1	0	0	1
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

$$f = ((x_1 + x_3) + x_2)((x_1 + x_3) + \bar{x}_2)(x_1 + (\bar{x}_2 + \bar{x}_3))(\bar{x}_1 + (\bar{x}_2 + \bar{x}_3))$$

$$f = (x_1 + x_3)(\bar{x}_2 + \bar{x}_3)$$

Shorthand Notation

- **Sum-of-Products**

$$f(x_1, x_2, x_3) = \sum (m_1, m_4, m_5, m_6)$$

or

$$f(x_1, x_2, x_3) = \sum m(1, 4, 5, 6)$$


- **Product-of-sums**

$$f(x_1, x_2, x_3) = \Pi (M_0, M_2, M_3, M_7)$$


or

$$f(x_1, x_2, x_3) = \Pi M (0, 2, 3, 7)$$

Two realizations of that function

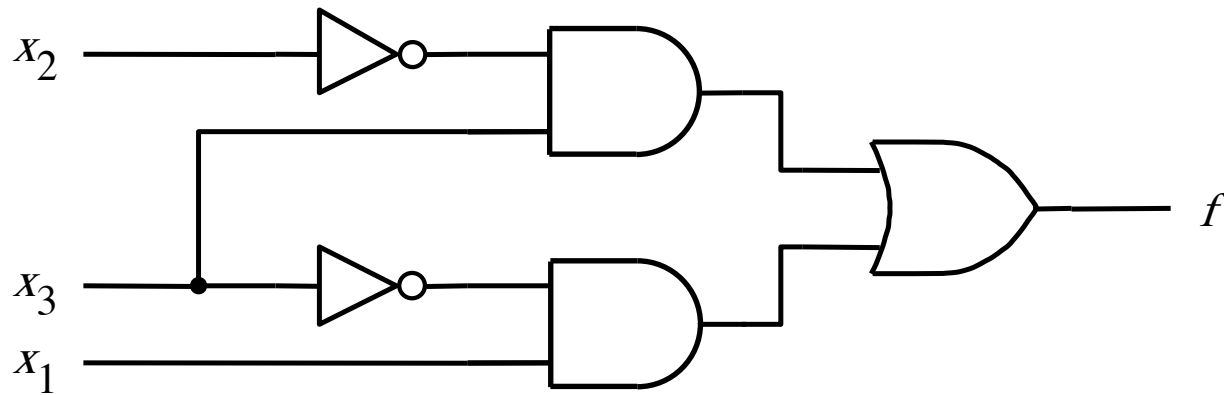

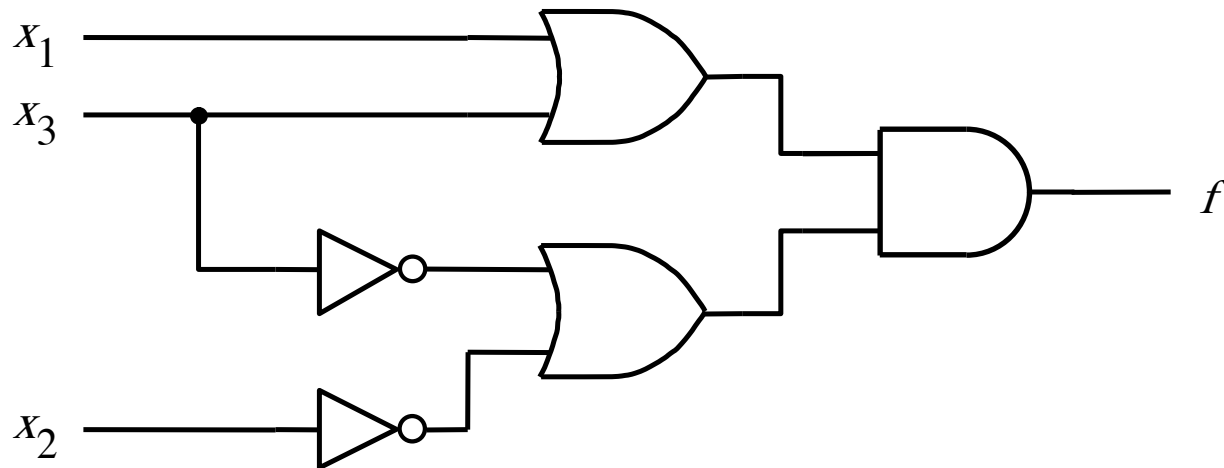(a) A minimal sum-of-products realization




(b) A minimal product-of-sums realization

[Figure 2.24 from the textbook]


The Cost of a Circuit

- **Count all gates**
- **Count all inputs/wires to the gates**

What is the cost of each circuit?

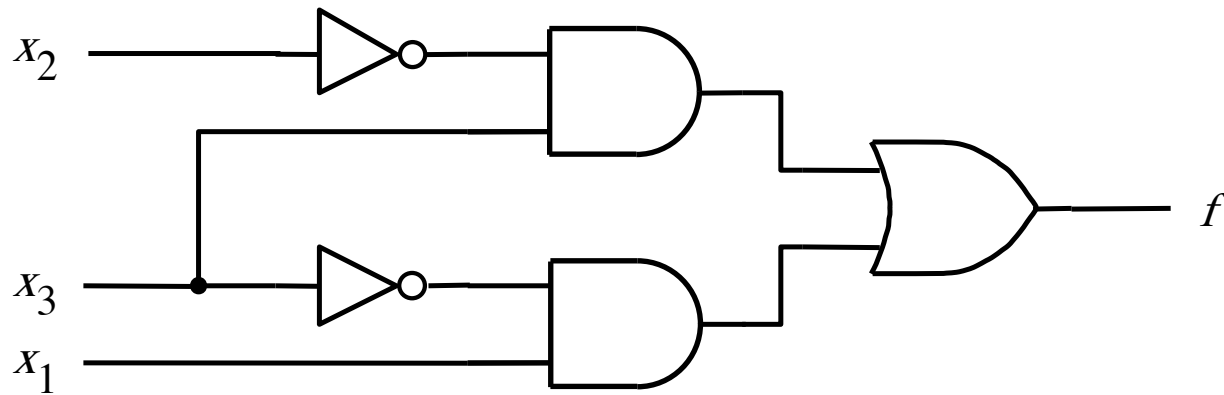

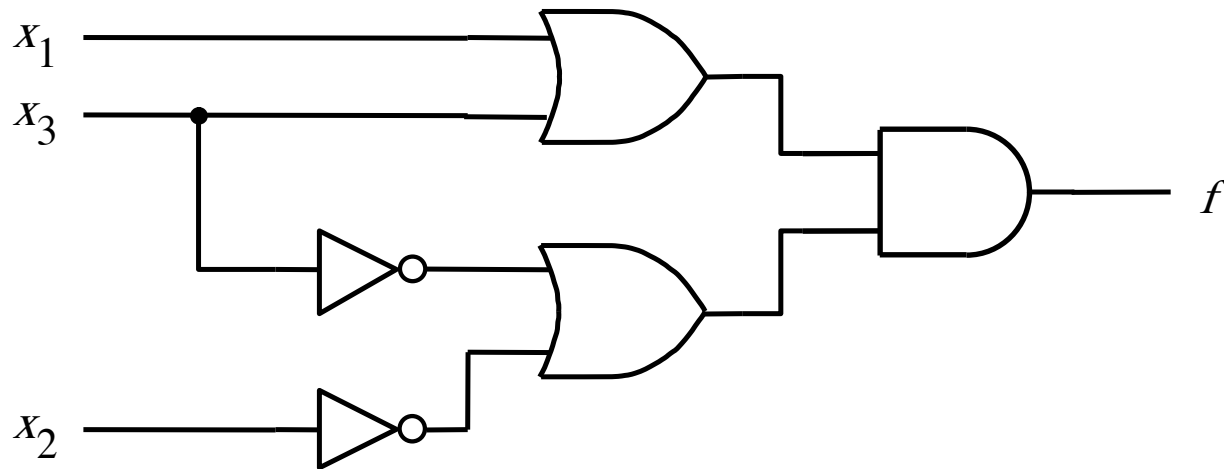
(a) A minimal sum-of-products realization



(b) A minimal product-of-sums realization

[Figure 2.24 from the textbook]

What is the cost of this circuit?

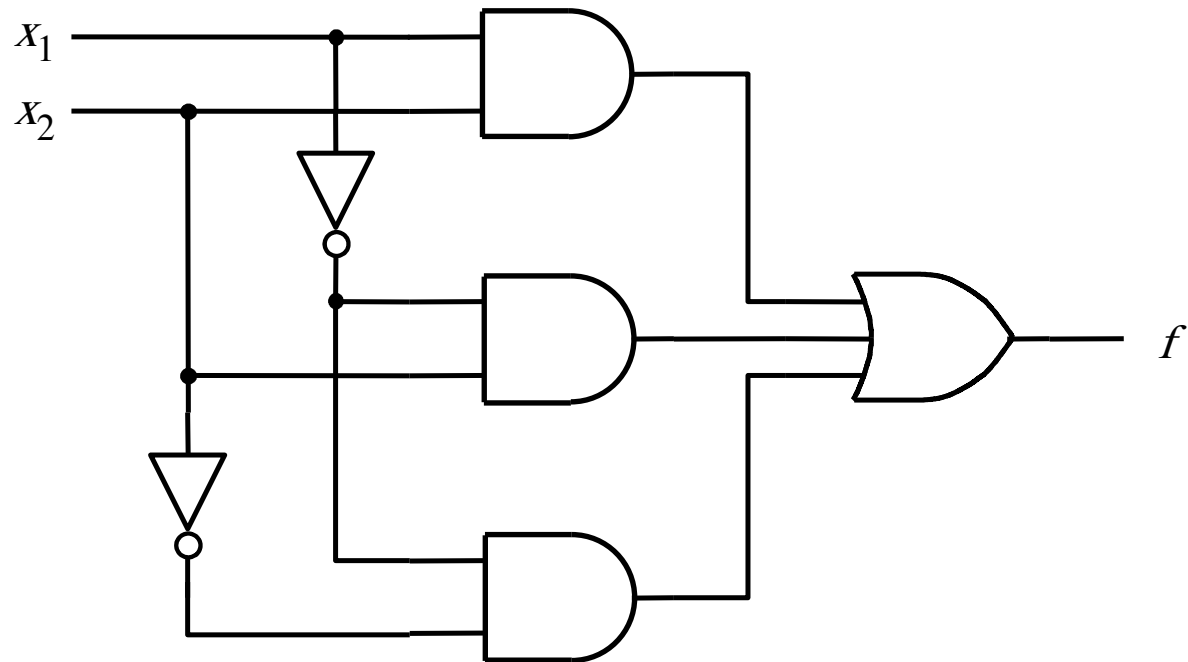

Questions?

THE END