

CprE 281: Digital Logic

Instructor: Alexander Stoytchev

<http://www.ece.iastate.edu/~alexs/classes/>

Intro to Verilog

*CprE 281: Digital Logic
Iowa State University, Ames, IA
Copyright © Alexander Stoytchev*

Administrative Stuff

- HW3 is due on Monday Sep 10 @ 4p**

Administrative Stuff

- HW4 is out
- It is due on Monday Sep 17 @ 4pm.
- Please write clearly on the first page (in BLOCK CAPITAL letters) the following three things:
 - Your First and Last Name
 - Your Student ID Number
 - Your Lab Section Letter
- Also, please
 - Staple your pages

Administrative Stuff


- **Midterm Exam #1**
- **When: Friday Sep 21.**
- **Where: This classroom**
- **What: Chapter 1 and Chapter 2 plus number systems**
- **The exam will be open book and open notes (you can bring up to 3 pages of handwritten notes).**
- **More details to follow.**

Quick Review

2-1 Multiplexer (Definition)

- Has two inputs: x_1 and x_2
- Also has another input line s
- If $s=0$, then the output is equal to x_1
- If $s=1$, then the output is equal to x_2

Graphical Symbol for a 2-1 Multiplexer

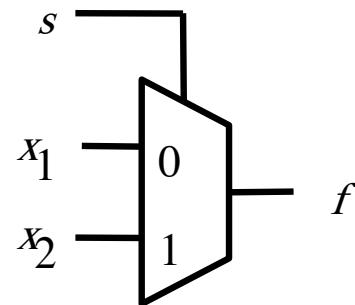

[Figure 2.33c from the textbook]

Let's Derive the SOP form

$s \ x_1 \ x_2$	$f(s, x_1, x_2)$	
0 0 0	0	
0 0 1	0	
0 1 0	1	$\bar{s} \ x_1 \ \bar{x}_2$
0 1 1	1	$\bar{s} \ x_1 \ x_2$
1 0 0	0	
1 0 1	1	$s \ \bar{x}_1 \ x_2$
1 1 0	0	
1 1 1	1	$s \ x_1 \ x_2$

$$f(s, x_1, x_2) = \bar{s}x_1\bar{x}_2 + \bar{s}x_1x_2 + s\bar{x}_1x_2 + sx_1x_2$$


Let's simplify this expression

$$f(s, x_1, x_2) = \bar{s}x_1\bar{x}_2 + \bar{s}x_1x_2 + s\bar{x}_1x_2 + s x_1x_2$$


$$f(s, x_1, x_2) = \bar{s}x_1(\bar{x}_2 + x_2) + s(\bar{x}_1 + x_1)x_2$$

$$f(s, x_1, x_2) = \bar{s}x_1 + s x_2$$

Circuit for 2-1 Multiplexer

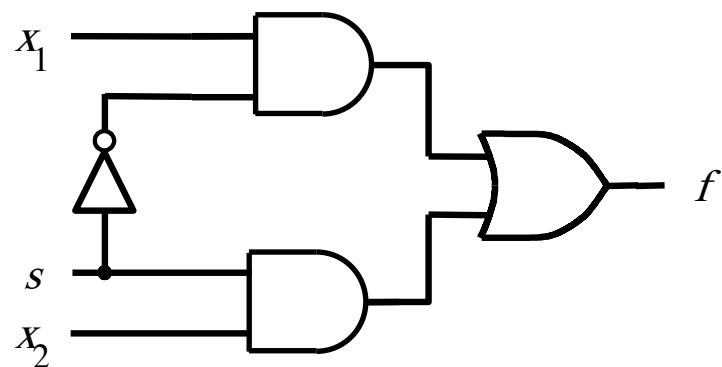

(b) Circuit

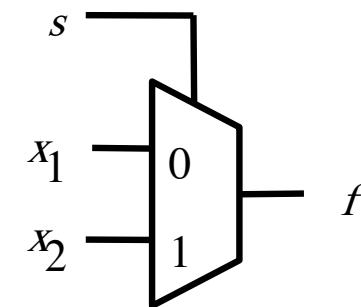


(c) Graphical symbol


$$f(s, x_1, x_2) = \bar{s}x_1 + s x_2$$

[Figure 2.33b-c from the textbook]


Analogy: Railroad Switch

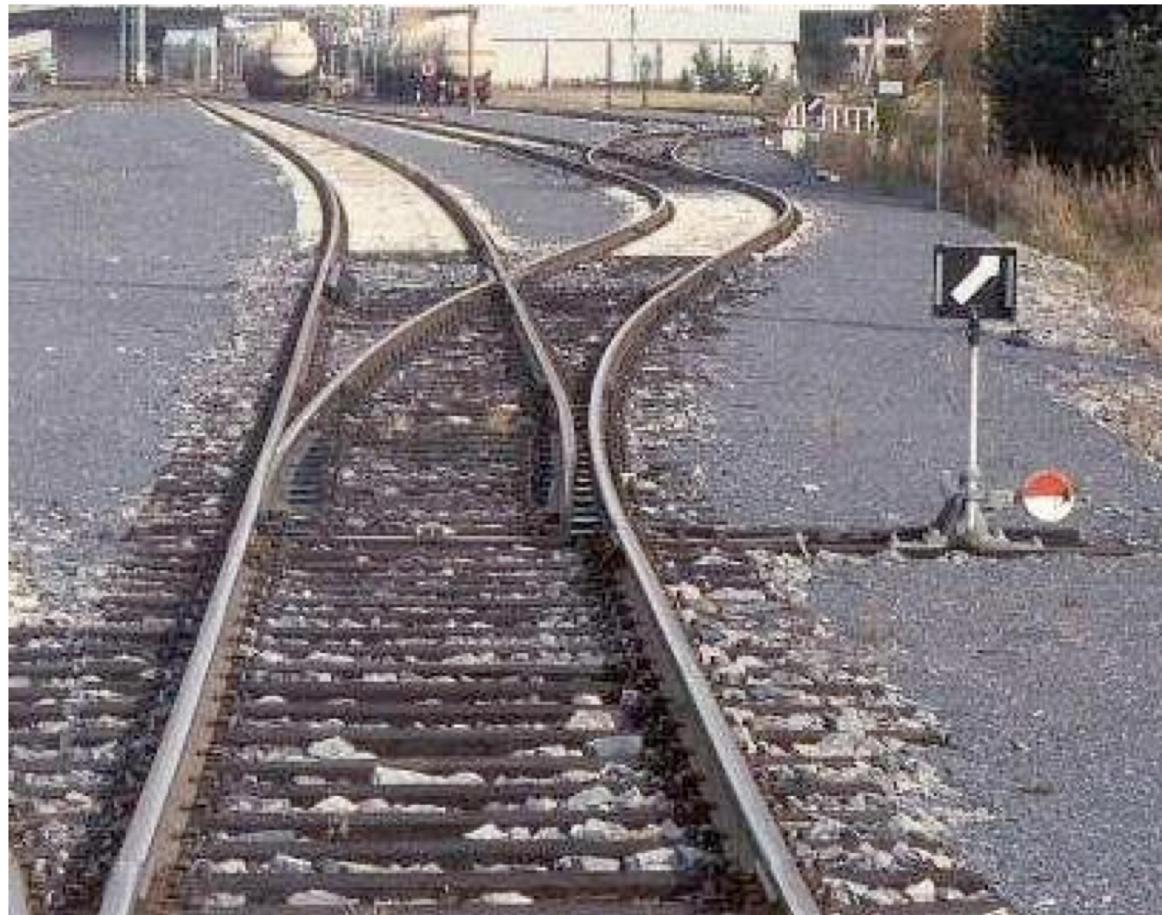

Analogy: Railroad Switch

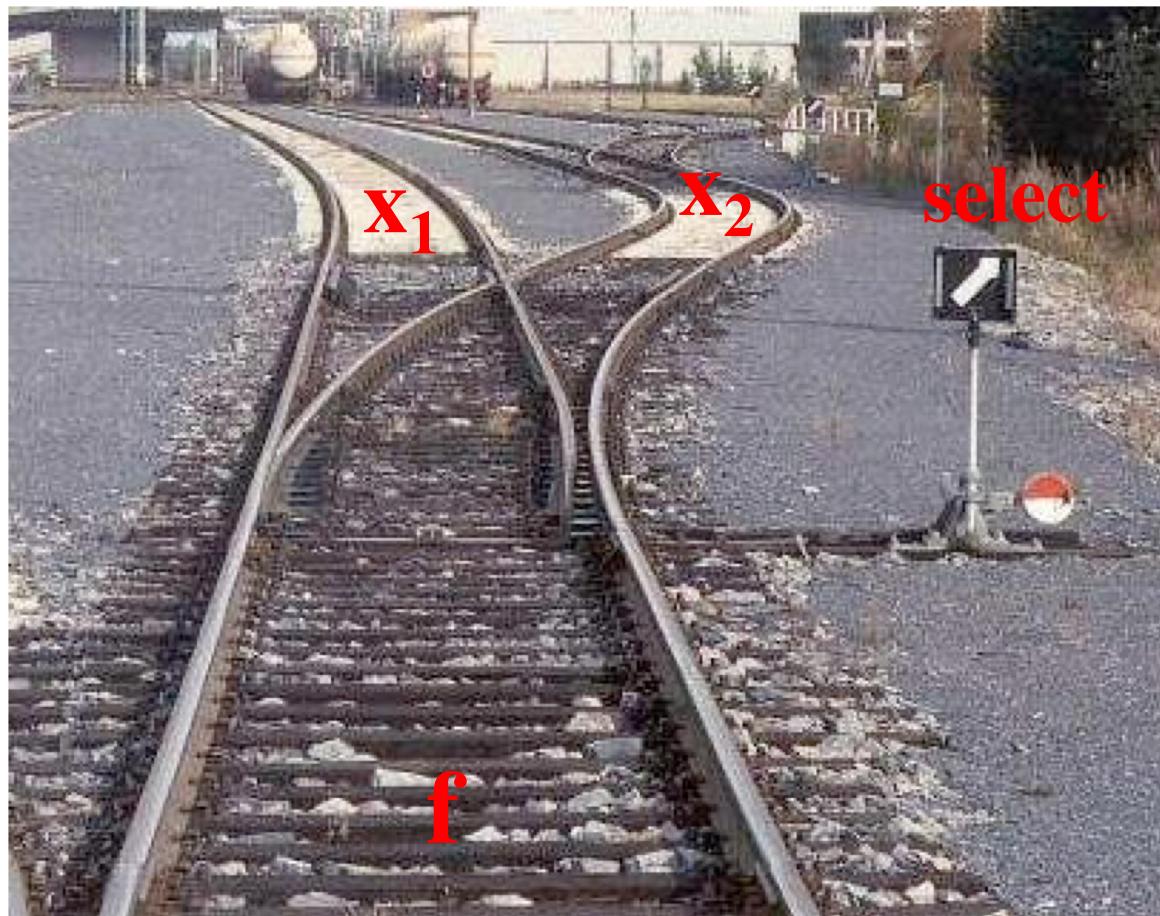

Analogy: Railroad Switch

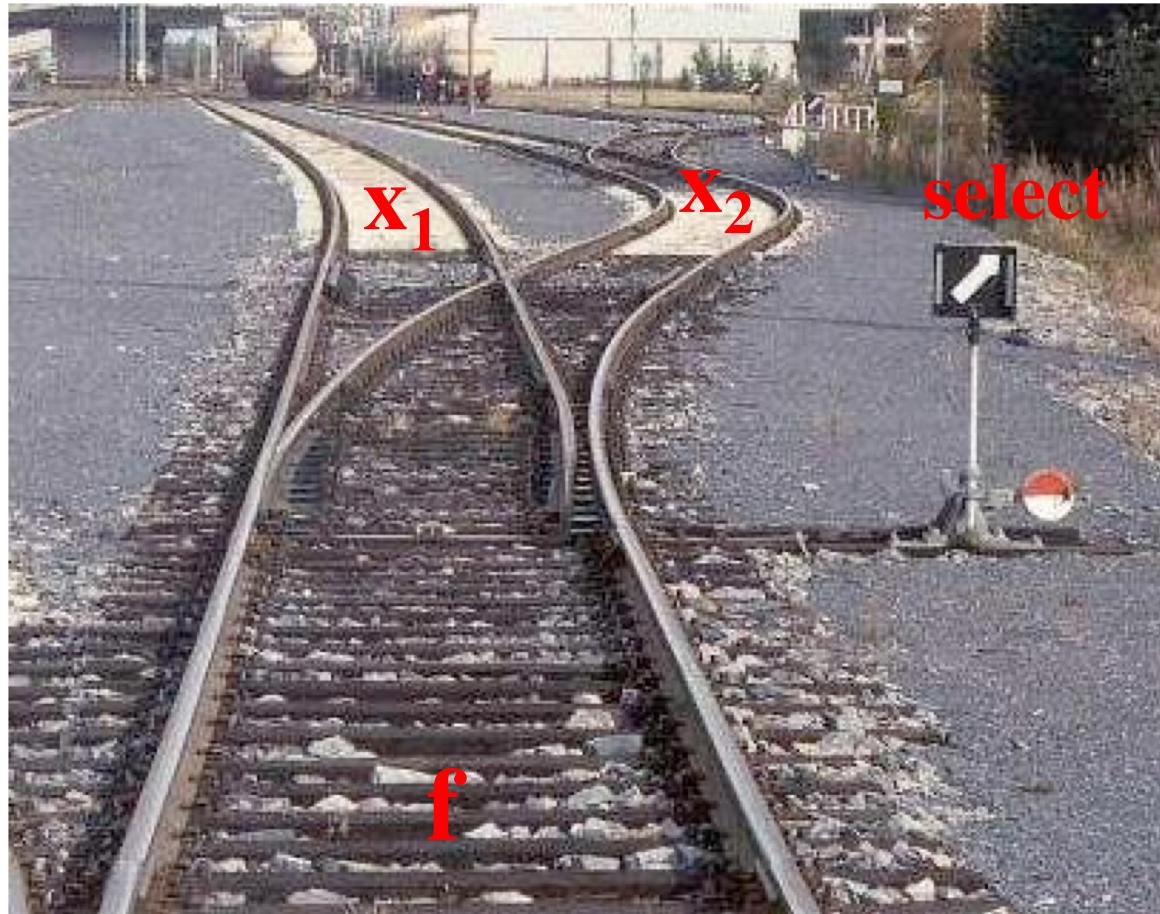

This is not a perfect analogy because the trains can go in either direction, while the multiplexer would only allow them to go from top to bottom.

More Compact Truth-Table Representation

s	x_1	x_2	$f(s, x_1, x_2)$
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

(a) Truth table

s	$f(s, x_1, x_2)$
0	x_1
1	x_2


[Figure 2.33 from the textbook]

4-1 Multiplexer (Definition)

- Has four inputs: w_0 , w_1 , w_2 , w_3
- Also has two select lines: s_1 and s_0
- If $s_1=0$ and $s_0=0$, then the output f is equal to w_0
- If $s_1=0$ and $s_0=1$, then the output f is equal to w_1
- If $s_1=1$ and $s_0=0$, then the output f is equal to w_2
- If $s_1=1$ and $s_0=1$, then the output f is equal to w_3

We'll talk more about this when we get to chapter 4, but here is a quick preview.

Graphical Symbol and Truth Table

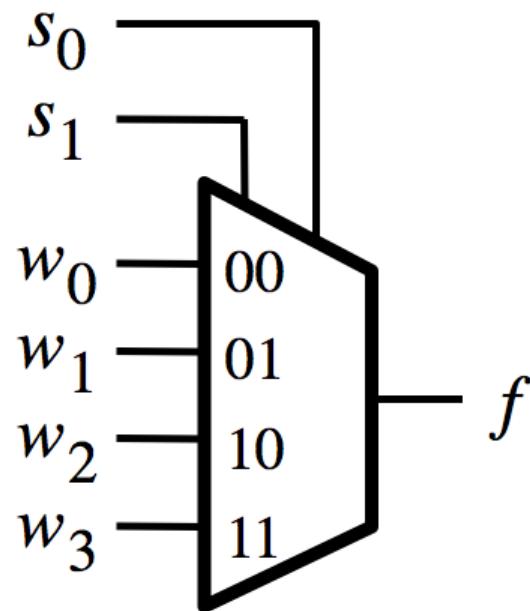

(a) Graphic symbol

s_1	s_0	f
0	0	w_0
0	1	w_1
1	0	w_2
1	1	w_3


(b) Truth table

[Figure 4.2a-b from the textbook]

The long-form truth table


$S_1 S_0$	I ₃	I ₂	I ₁	I ₀	F	$S_1 S_0$	I ₃	I ₂	I ₁	I ₀	F	$S_1 S_0$	I ₃	I ₂	I ₁	I ₀	F	$S_1 S_0$	I ₃	I ₂	I ₁	I ₀	F
0 0	0	0	0	0	0	0 1	0	0	0	0	0	1 0	0	0	0	0	0	1 1	0	0	0	0	0
	0	0	0	1	1		0	0	0	1	0		0	0	0	1	0		0	0	0	1	0
	0	0	1	0	0		0	0	1	0	1		0	0	1	0	0		0	0	1	0	0
	0	0	1	1	1		0	0	1	1	1		0	0	1	1	0		0	0	1	1	0
	0	1	0	0	0		0	1	0	0	0		0	1	0	0	1		0	1	0	0	0
	0	1	0	1	1		0	1	0	1	0		0	1	0	1	1		0	1	0	1	0
	0	1	1	0	0		0	1	1	0	1		0	1	1	0	1		0	1	1	0	0
	0	1	1	1	1		0	1	1	1	1		0	1	1	1	1		0	1	1	1	0
	1	0	0	0	0		1	0	0	0	0		1	0	0	0	0		1	0	0	0	1
	1	0	0	1	1		1	0	0	1	0		1	0	0	1	0		1	0	0	1	1
	1	0	1	0	0		1	0	1	0	1		1	0	1	0	0		1	0	1	0	1
	1	0	1	1	1		1	0	1	1	1		1	0	1	1	0		1	0	1	1	1
	1	1	0	0	0		1	1	0	0	0		1	1	0	0	1		1	1	0	0	1
	1	1	0	1	1		1	1	0	1	0		1	1	0	1	1		1	1	0	1	1
	1	1	1	0	0		1	1	1	0	1		1	1	1	0	1		1	1	1	0	1
	1	1	1	1	1		1	1	1	1	1		1	1	1	1	1		1	1	1	1	1

4-1 Multiplexer (SOP circuit)

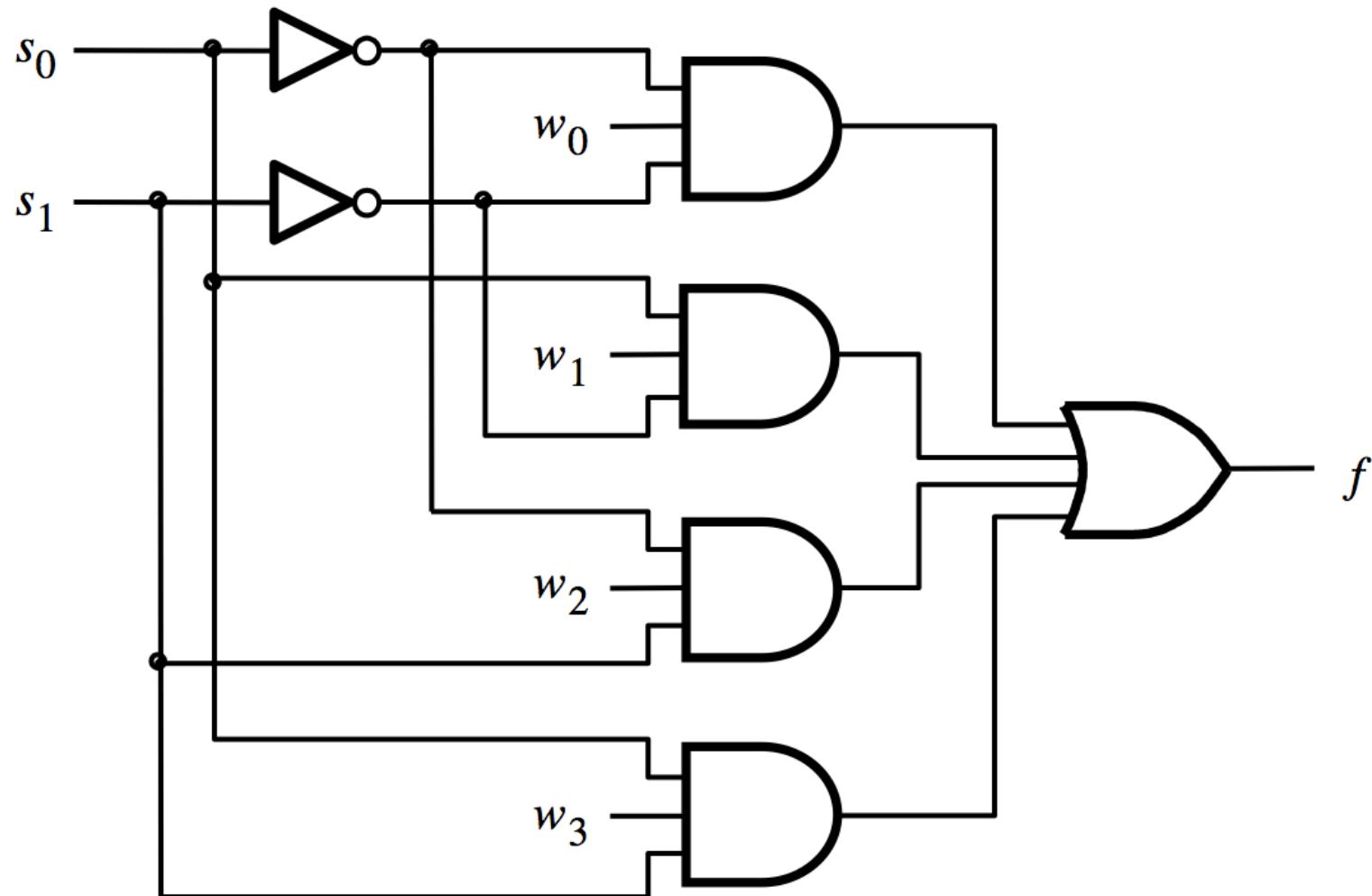




[Figure 4.2c from the textbook]

Using three 2-to-1 multiplexers to build one 4-to-1 multiplexer

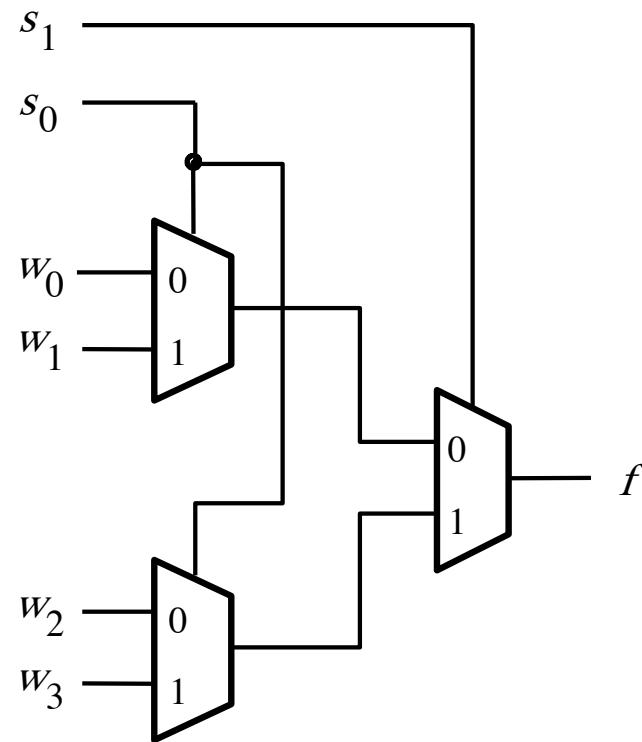




[Figure 4.3 from the textbook]

Analogy: Railroad Switches

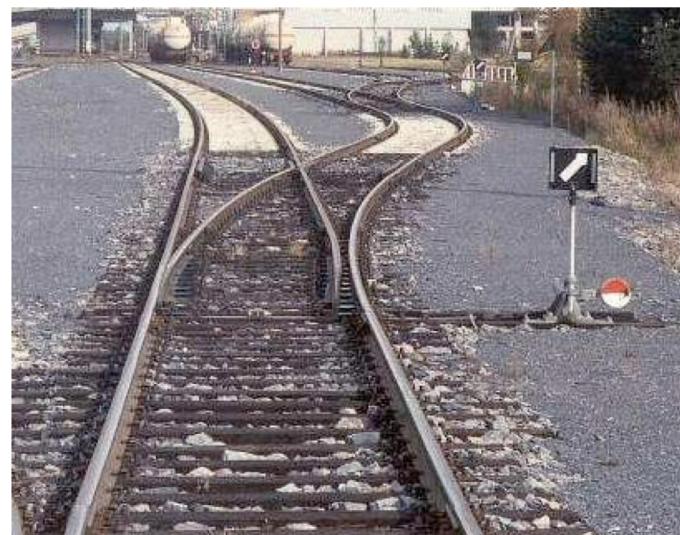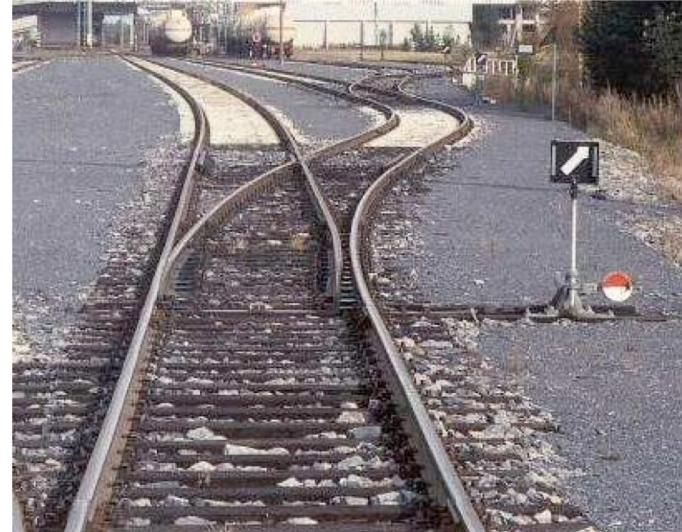
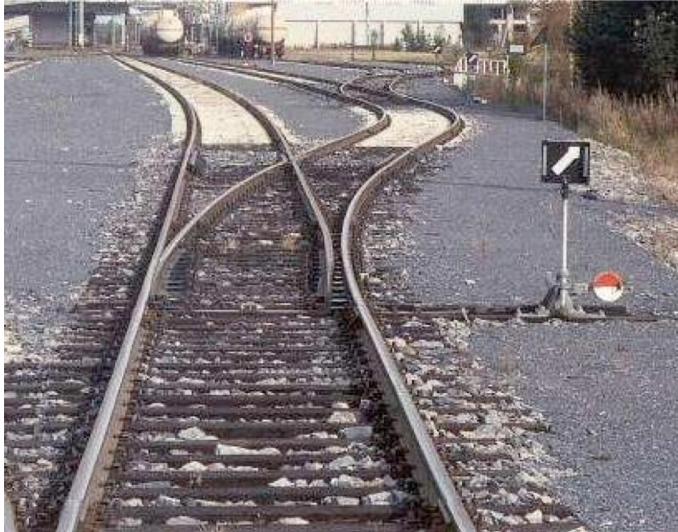


[http://en.wikipedia.org/wiki/Railroad_switch\]](http://en.wikipedia.org/wiki/Railroad_switch)

Analogy: Railroad Switches

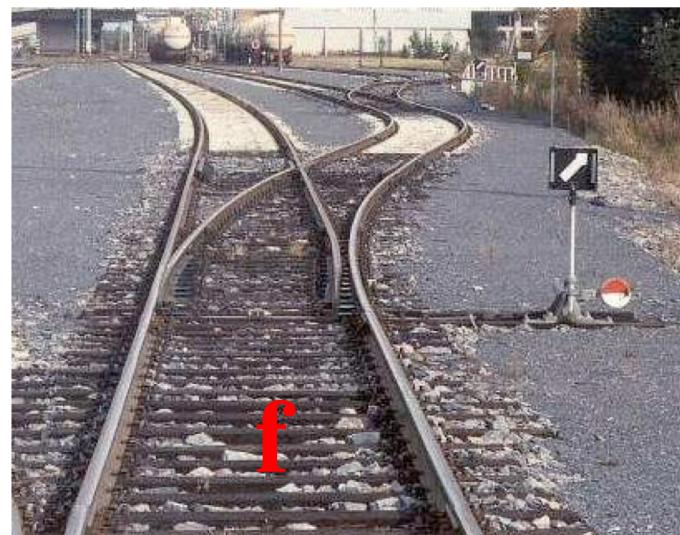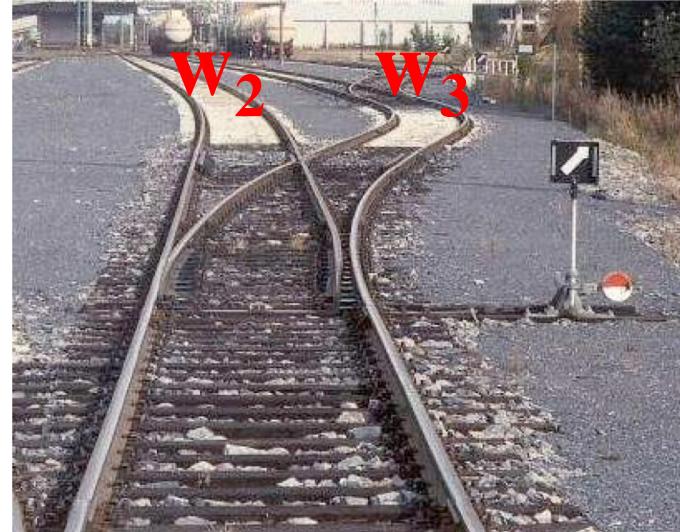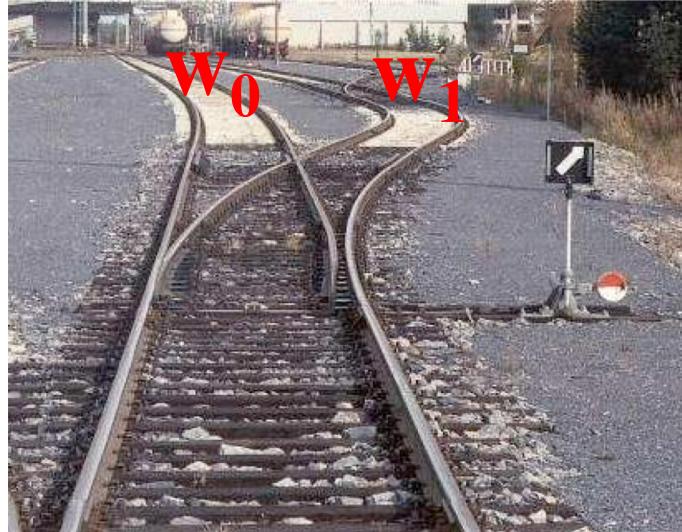


Analogy: Railroad Switches

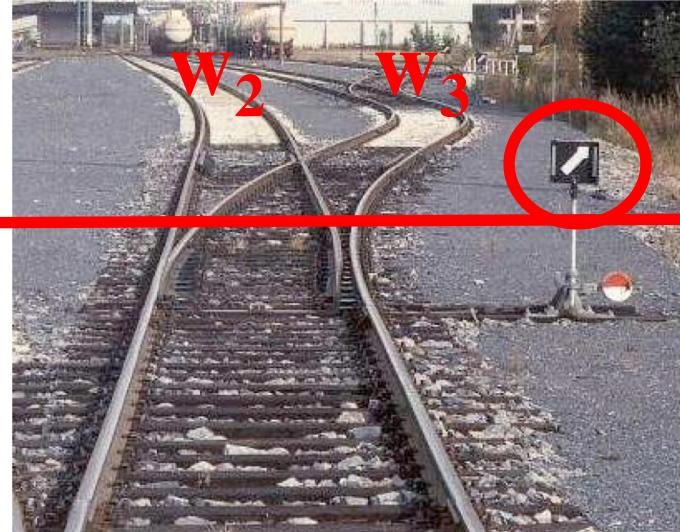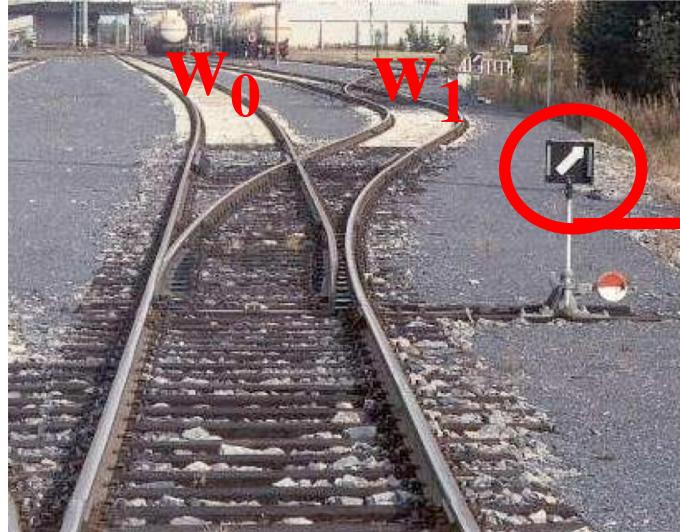




s_0

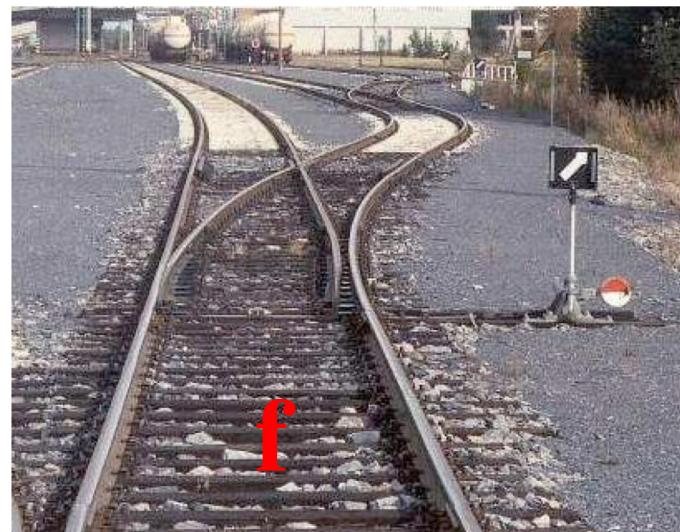these two
switches are
controlled
together




s_1

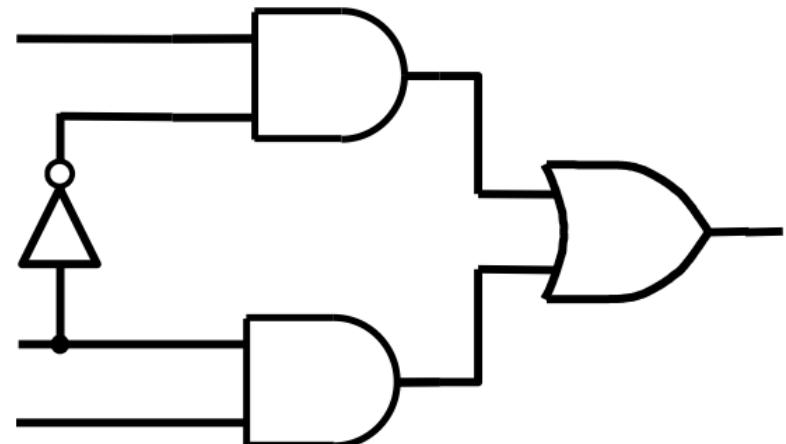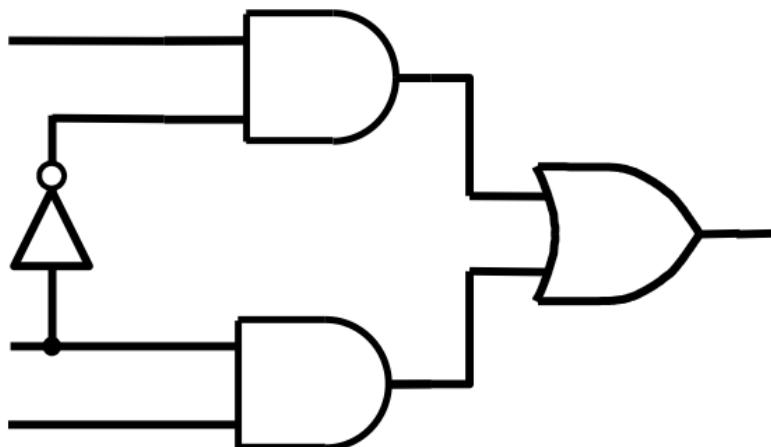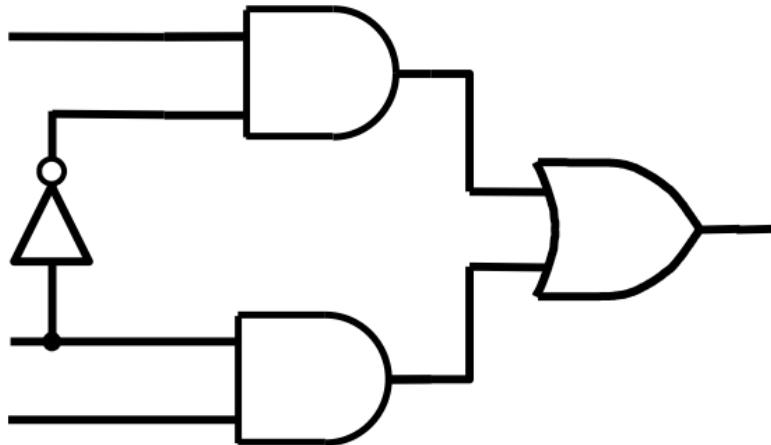
Using three 2-to-1 multiplexers to build one 4-to-1 multiplexer



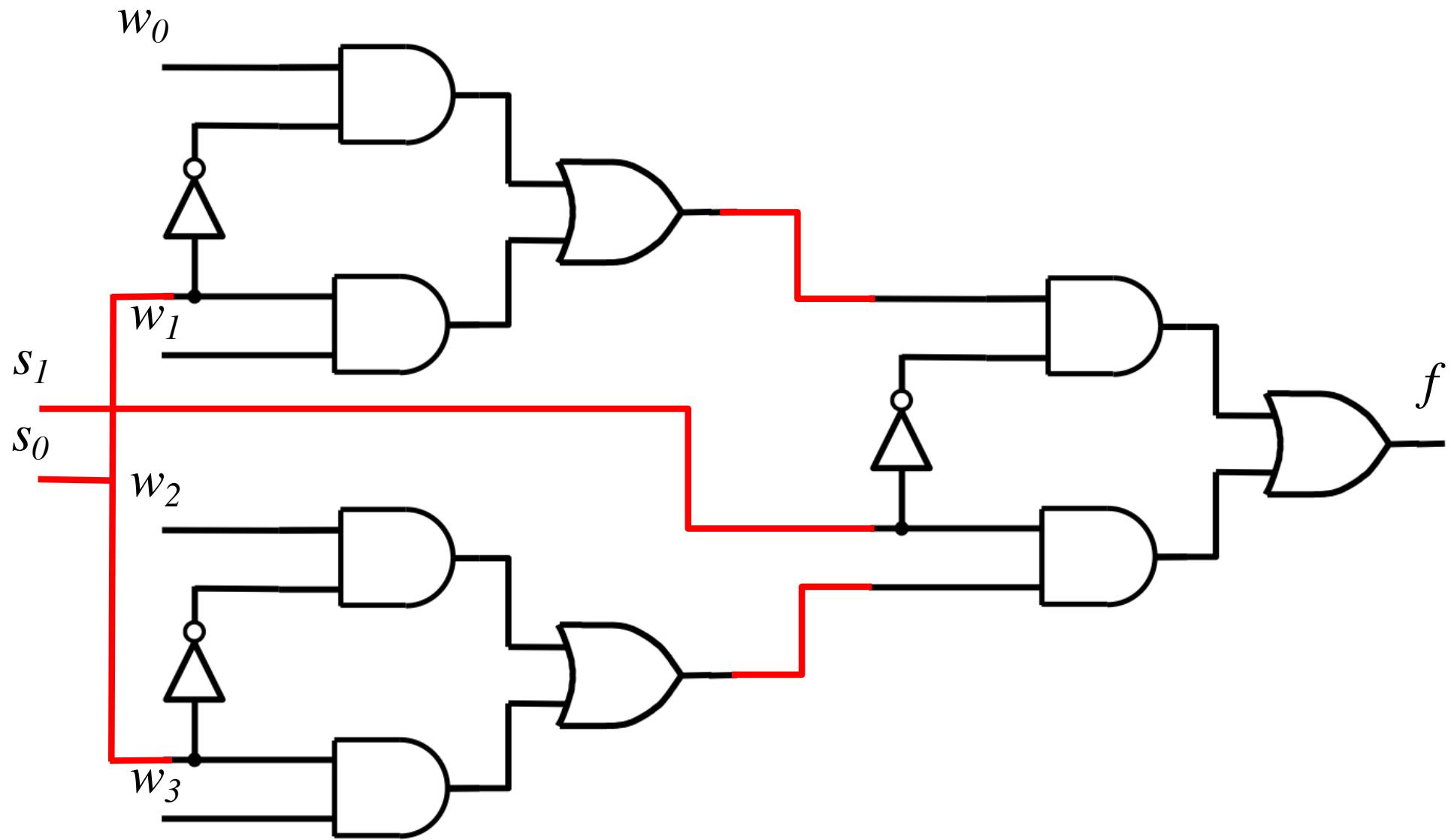
Using three 2-to-1 multiplexers to build one 4-to-1 multiplexer



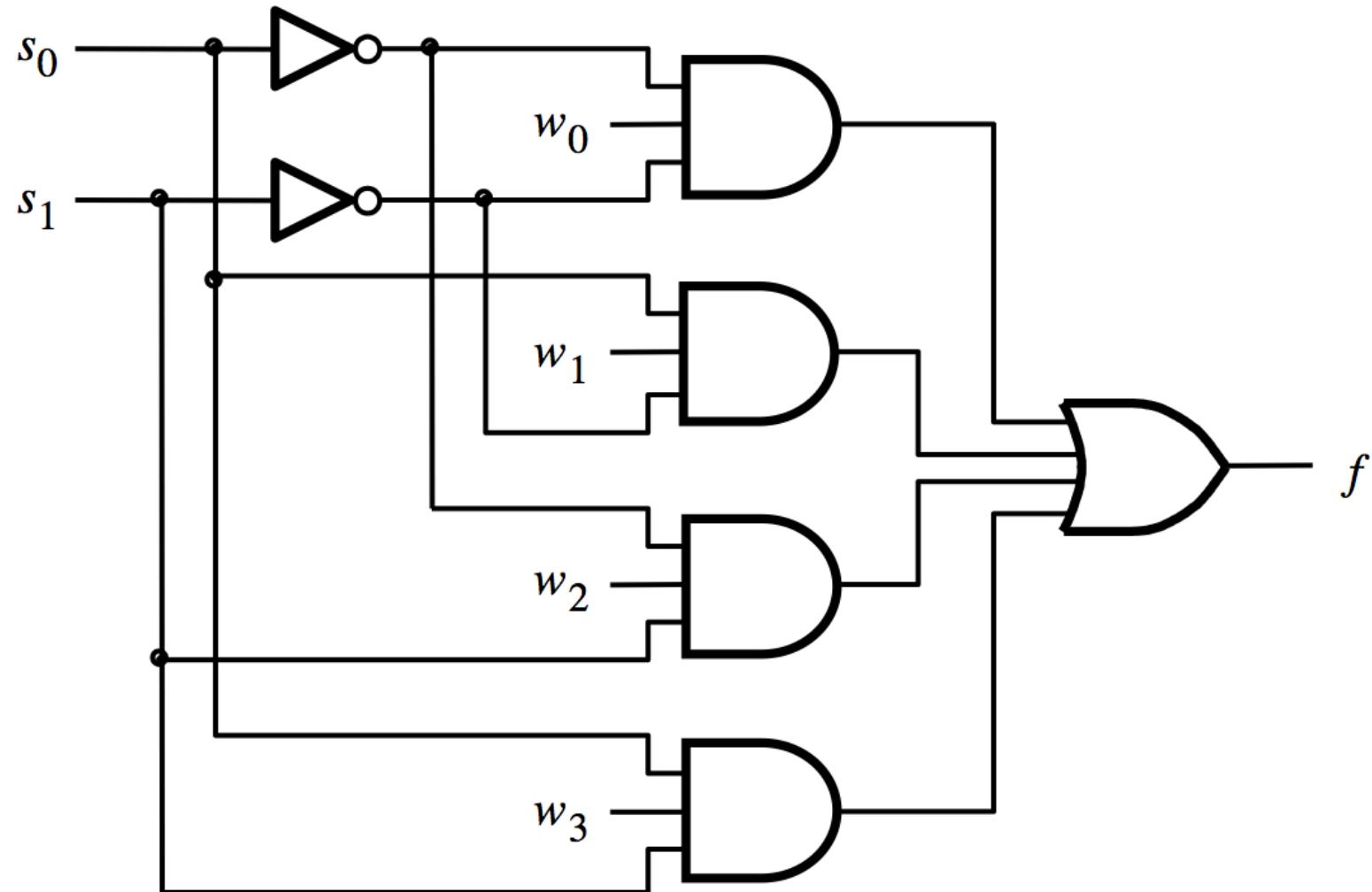That is different from the SOP form of the 4-1 multiplexer shown below, which uses fewer gates



16-1 Multiplexer

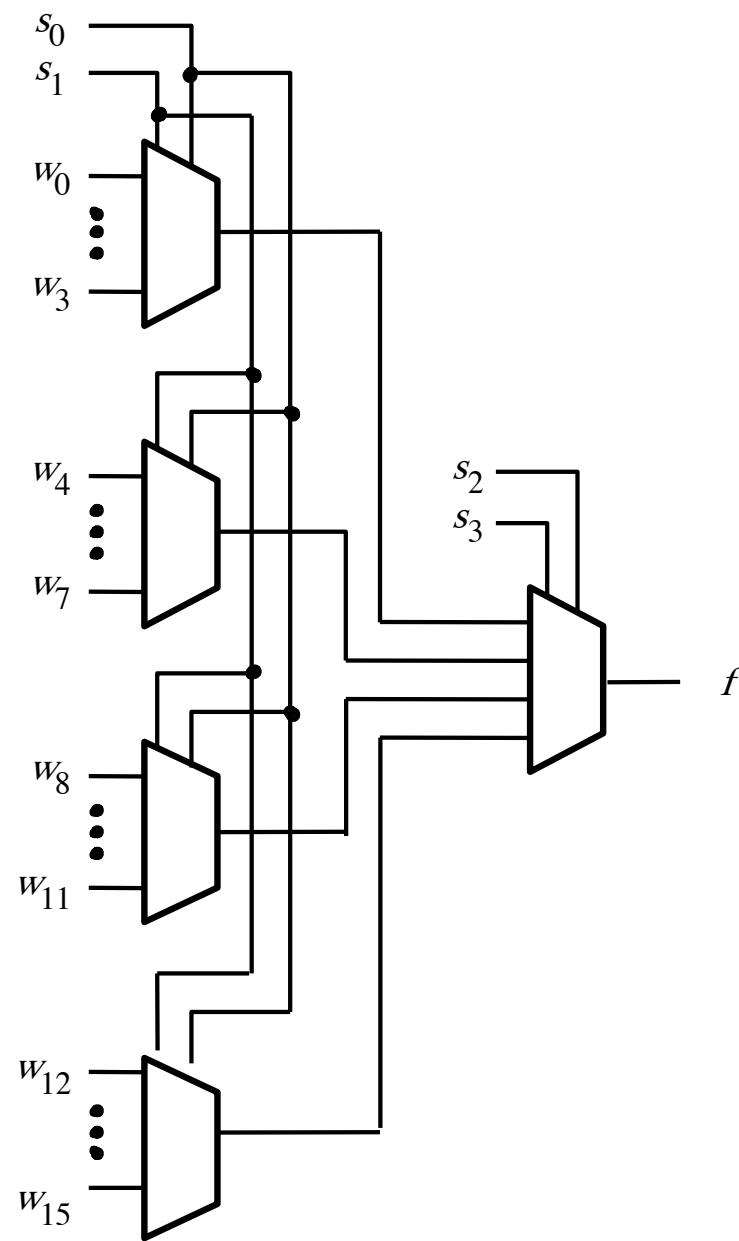


[Figure 4.4 from the textbook]



[<http://upload.wikimedia.org/wikipedia/commons/2/26/SunsetTracksCrop.JPG>]

7-Segment Display Example

Display of numbers

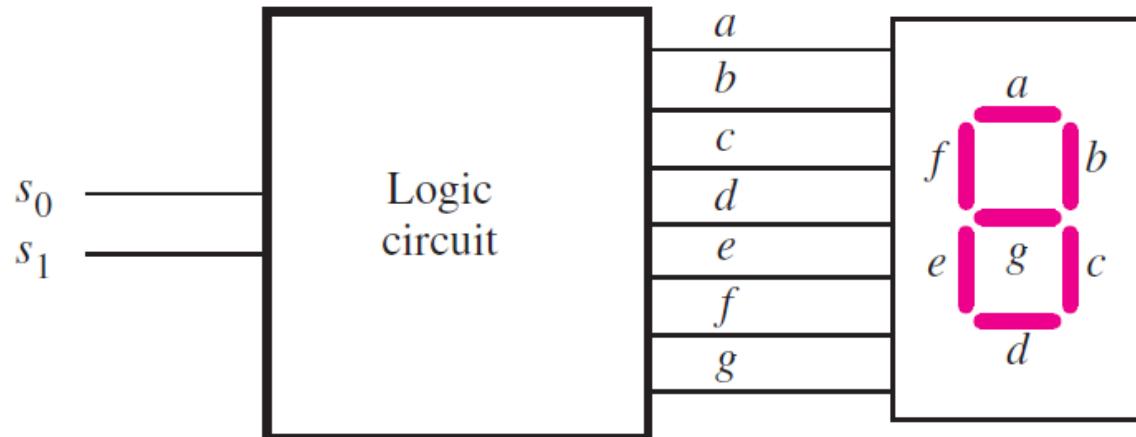

(a) Logic circuit and 7-segment display

	s_1	s_0	a	b	c	d	e	f	g
0	0	0	1	1	1	1	1	1	0
1	0	1	0	1	1	0	0	0	0
2	1	0	1	1	0	1	1	0	1

(b) Truth table

[Figure 2.34 from the textbook]

Display of numbers

	s_1	s_0	a	b	c	d	e	f	g
0	0	0	1	1	1	1	1	1	0
1	0	1	0	1	1	0	0	0	0
2	1	0	1	1	0	1	1	0	1

Display of numbers

	s_1	s_0	a	b	c	d	e	f	g
0	0	0	1	1	1	1	1	1	0
1	0	1	0	1	1	0	0	0	0
2	1	0	1	1	0	1	1	0	1

$$a = \overline{s_0}$$

$$c = \overline{s_1}$$

$$e = \overline{s_0}$$

$$g = s_1 \overline{s_0}$$

$$b = 1$$

$$d = \overline{s_0}$$

$$f = \overline{s_1} \overline{s_0}$$

Intro to Verilog

History


- **Created in 1983/1984**
- **Verilog-95 (IEEE standard 1364-1995)**
- **Verilog 2001 (IEEE Standard 1364-2001)**
- **Verilog 2005 (IEEE Standard 1364-2005)**
- **SystemVerilog**
- **SystemVerilog 2009 (IEEE Standard 1800-2009).**

HDL

- **Hardware Description Language**
- **Verilog HDL**
- **VHDL**

Verilog HDL != VHDL

- These are two different Languages!
- Verilog is closer to C
- VHDL is closer to Ada

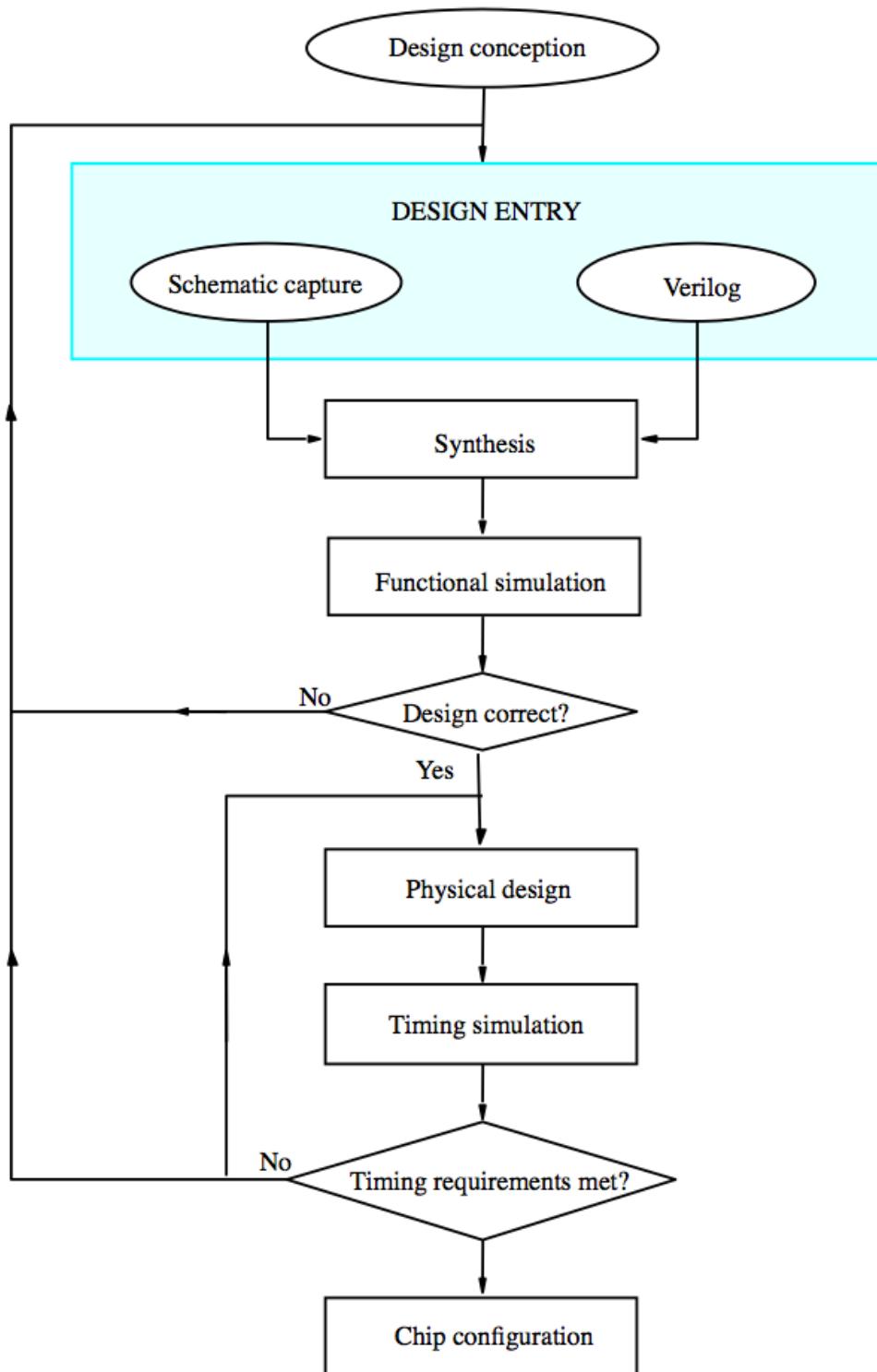


[Figure 2.35 from the textbook]


“Hello World” in Verilog

```
module main;
    initial
        begin
            $display("Hello world!");
            $finish;
        end
    endmodule
```


The Three Basic Logic Gates

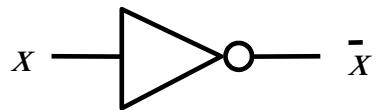

NOT gate

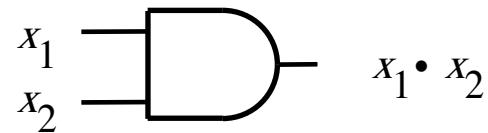


AND gate

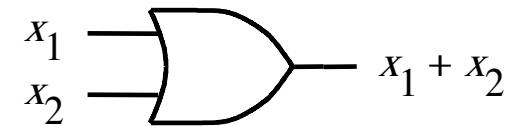

OR gate

You can build any circuit using only these three gates


How to specify a NOT gate in Verilog

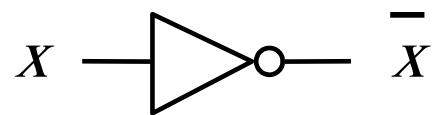

NOT gate


How to specify a NOT gate in Verilog

we'll use the letter y for the output

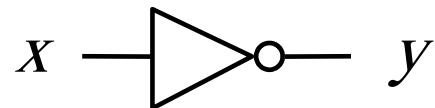

NOT gate

How to specify a NOT gate in Verilog

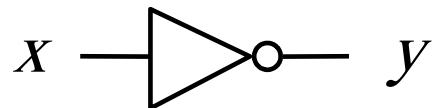


NOT gate

not (y, x)

Verilog code

How to specify an AND gate in Verilog

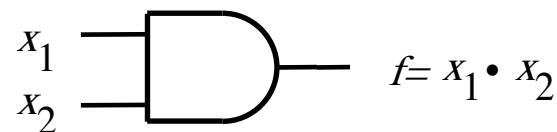


AND gate

and (f, x1, x2)

Verilog code

How to specify an OR gate in Verilog

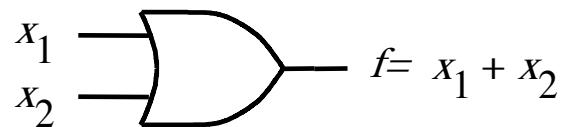


OR gate

or (f, x1, x2)


Verilog code

2-1 Multiplexer

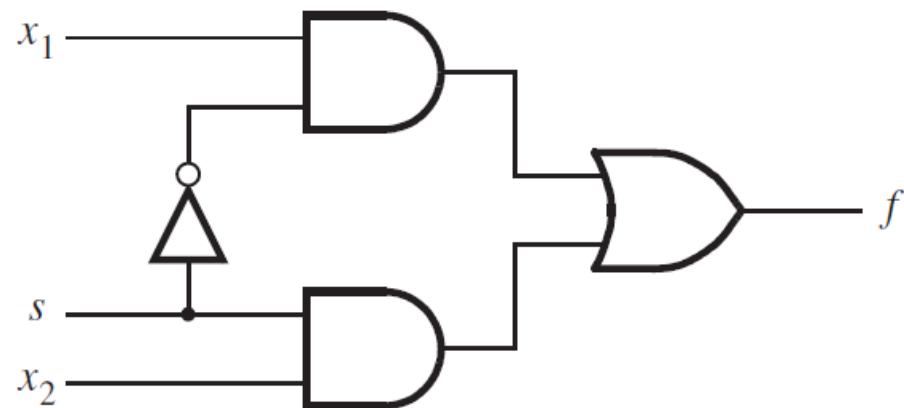

[Figure 2.36 from the textbook]

Verilog Code for a 2-1 Multiplexer

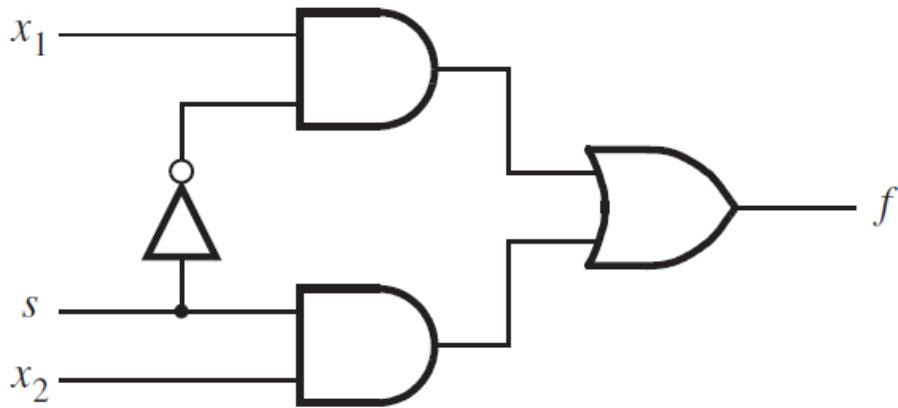

```
module example1 (x1, x2, s, f);
    input x1, x2, s;
    output f;


    not (k, s);
    and (g, k, x1);
    and (h, s, x2);
    or (f, g, h);

endmodule
```

[Figure 2.36 from the textbook]

[Figure 2.37 from the textbook]

Verilog Code for a 2-1 Multiplexer

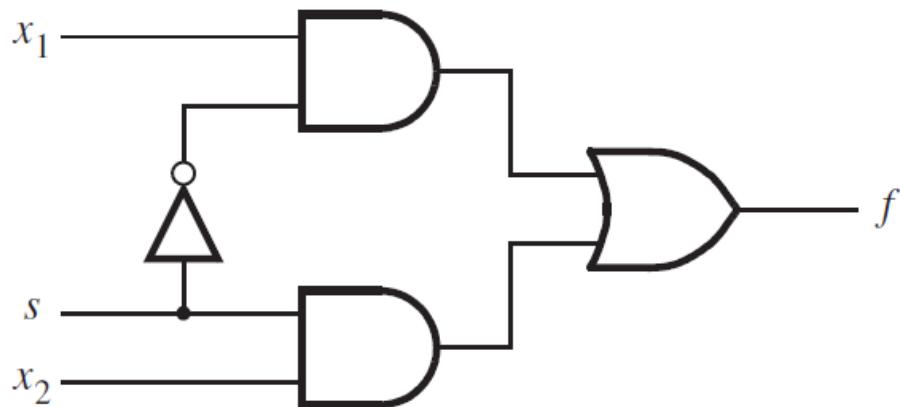

```
module example3 (x1, x2, s, f);
    input x1, x2, s;
    output f;


    assign f = (~s & x1) | (s & x2);

endmodule
```

[Figure 2.36 from the textbook]

[Figure 2.40 from the textbook]

Verilog Code for a 2-1 Multiplexer

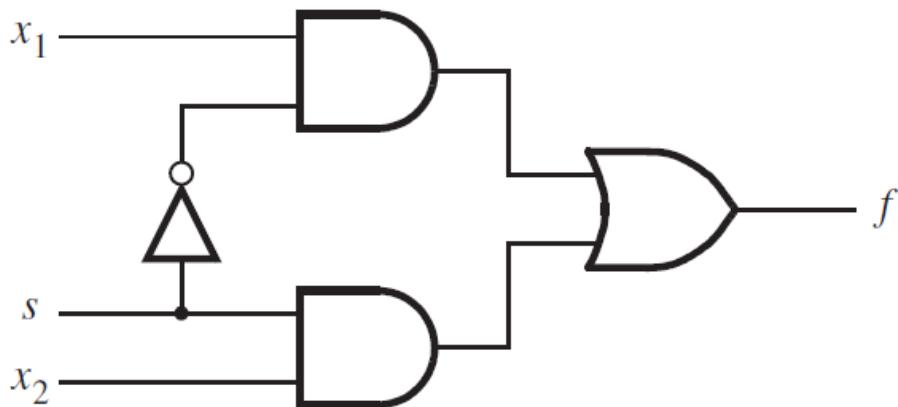

```
// Behavioral specification
module example5 (x1, x2, s, f);
    input x1, x2, s;
    output f;    I
    reg f;


    always @ (x1 or x2 or s)
        if (s == 0)
            f = x1;
        else
            f = x2;

endmodule
```

[Figure 2.36 from the textbook]

[Figure 2.42 from the textbook]

Verilog Code for a 2-1 Multiplexer

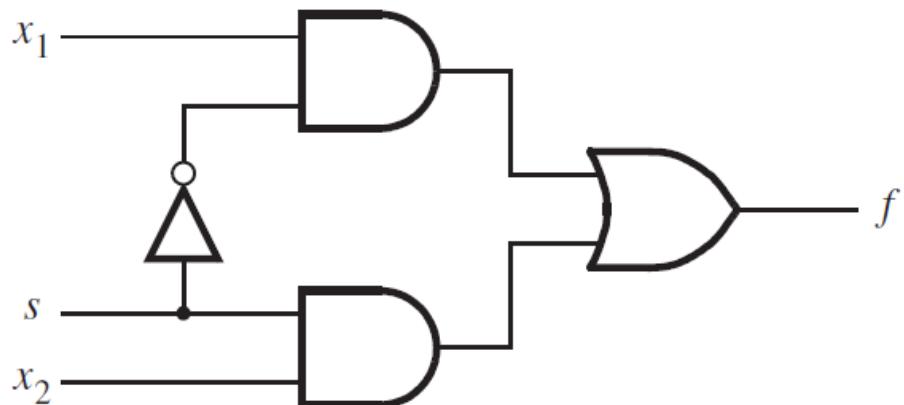

```
// Behavioral specification
module example5 (input x1, x2, s, output reg f);

always @ (x1, x2, s)
  if (s == 0)
    f = x1;
  else
    f = x2;


endmodule
```

[Figure 2.36 from the textbook]

[Figure 2.43 from the textbook]


Another Example

Let's Write the Code for This Circuit

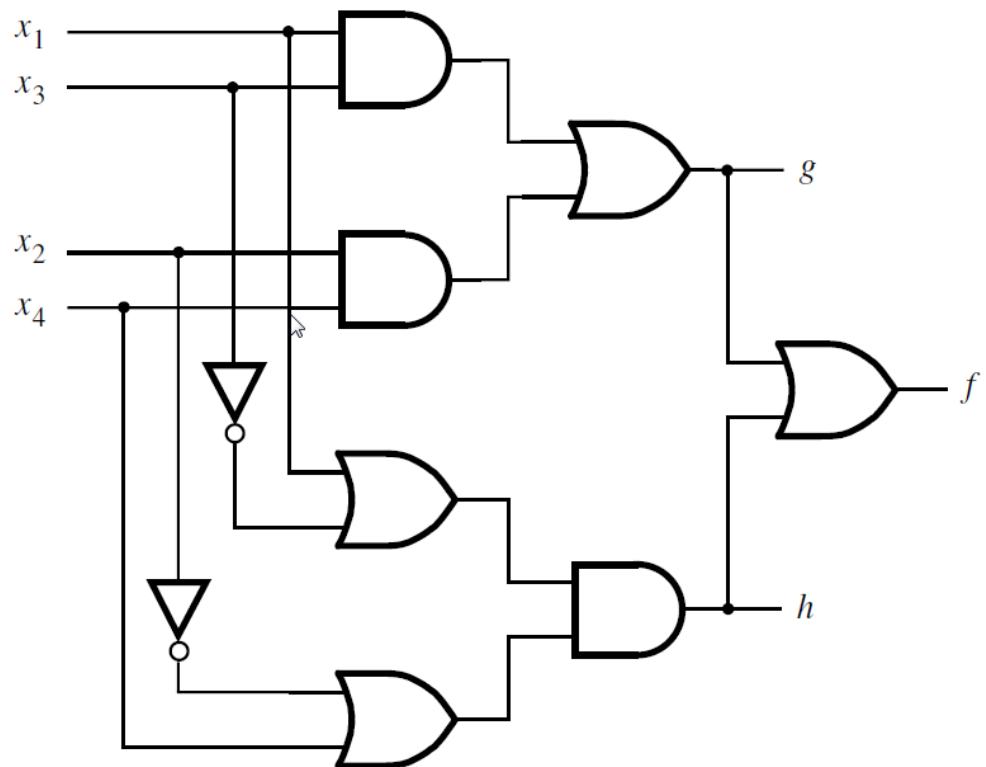

[Figure 2.39 from the textbook]

Let's Write the Code for This Circuit

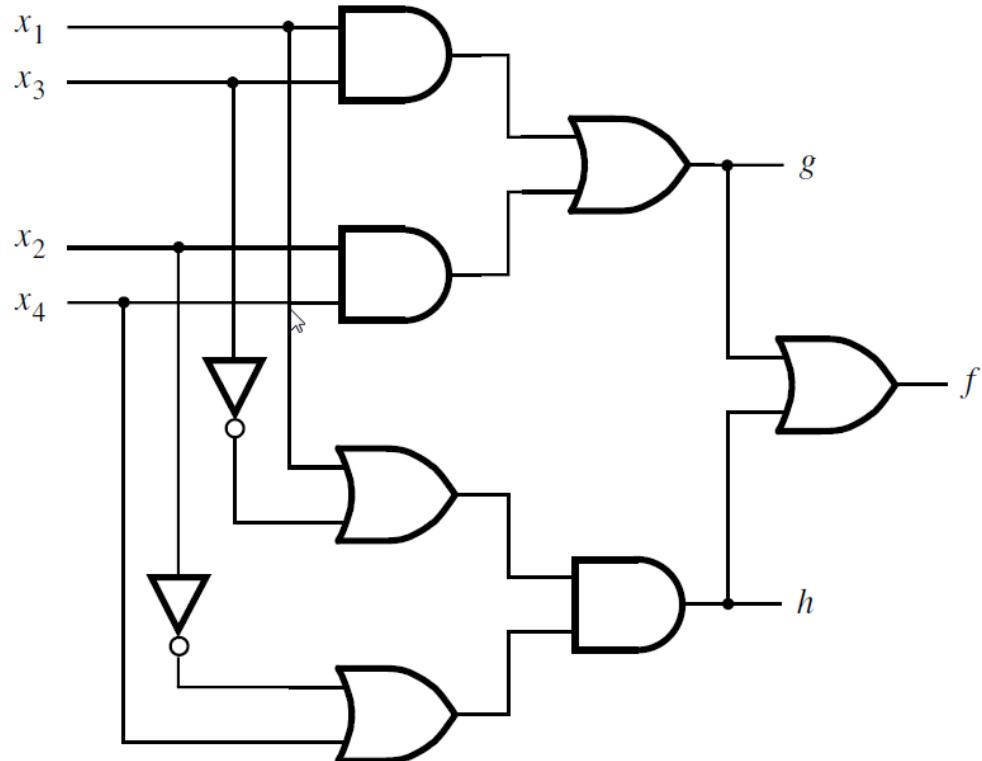

```
module example2 (x1, x2, x3, x4, f, g, h);
    input x1, x2, x3, x4;
    output f, g, h;


    and (z1, x1, x3);
    and (z2, x2, x4);
    or (g, z1, z2);
    or (z3, x1, ~x3);
    or (z4, ~x2, x4);
    and (h, z3, z4);
    or (f, g, h);

endmodule
```

[Figure 2.39 from the textbook]

[Figure 2.38 from the textbook]

Let's Write the Code for This Circuit

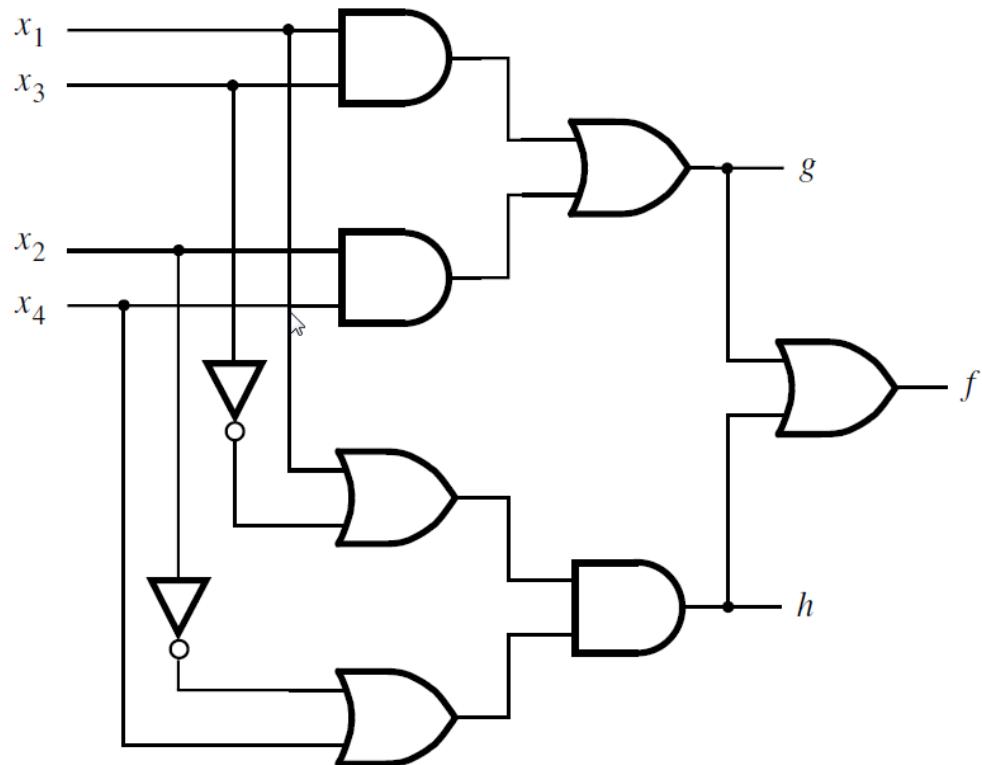

```
module example4 (x1, x2, x3, x4, f, g, h);
    input x1, x2, x3, x4;
    output f, g, h;

    assign g = (x1 & x3) | (x2 & x4);
    assign h = (x1 | ~x3) & (~x2 | x4);
    assign f = g | h;


endmodule
```

[Figure 2.39 from the textbook]

[Figure 2.41 from the textbook]

Yet Another Example

A logic circuit with two modules

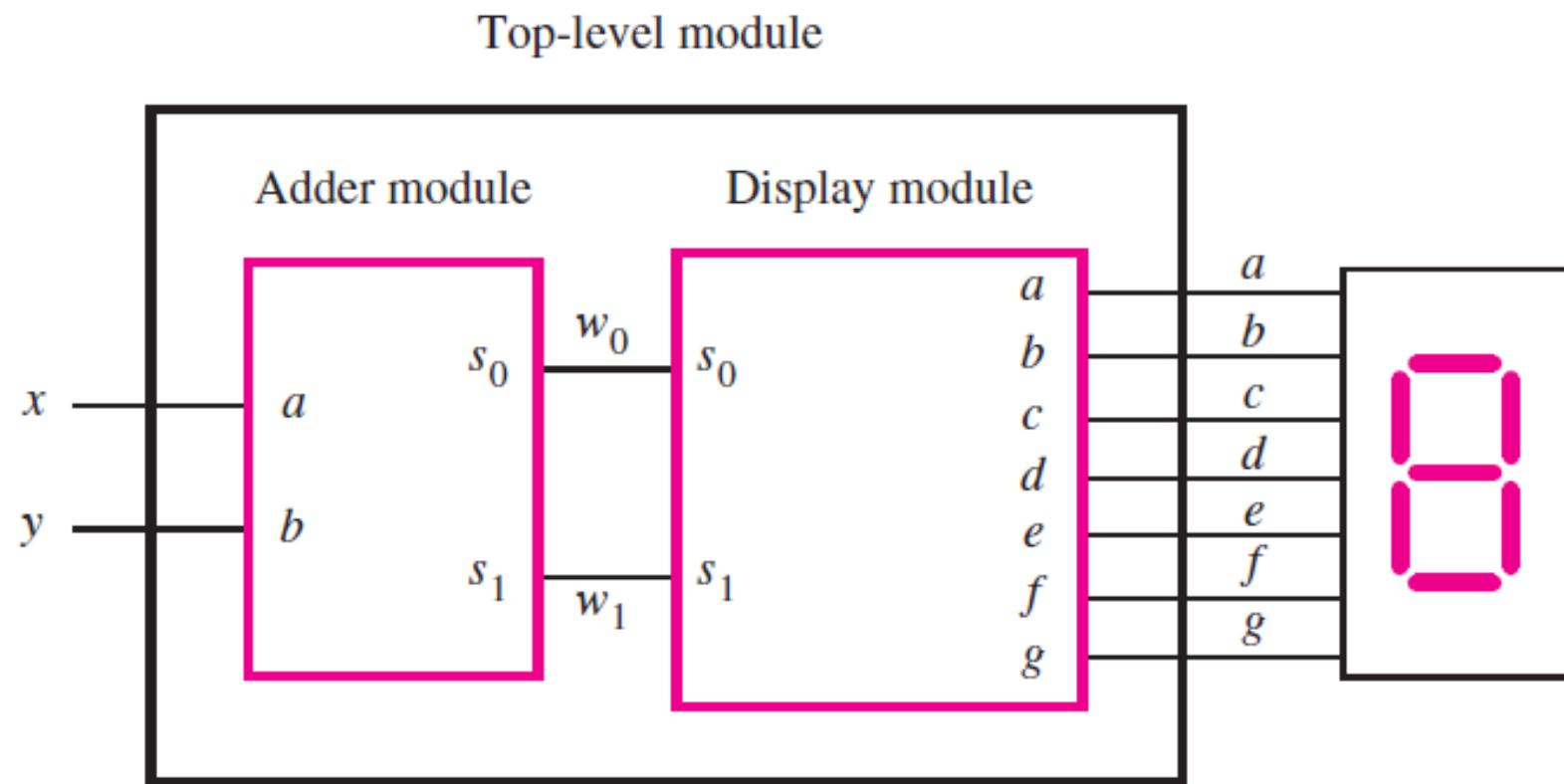

[Figure 2.44 from the textbook]


The adder module

$$\begin{array}{r} a \\ + b \\ \hline s_1 \ s_0 \end{array} \quad \begin{array}{c} 0 \\ + 0 \\ \hline 0 \ 0 \end{array} \quad \begin{array}{c} 0 \\ + 1 \\ \hline 0 \ 1 \end{array} \quad \begin{array}{c} 1 \\ + 0 \\ \hline 0 \ 1 \end{array} \quad \begin{array}{c} 1 \\ + 1 \\ \hline 1 \ 0 \end{array}$$

(a) Evaluation of $S = a + b$


a	b	s_1	s_0
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

(b) Truth table

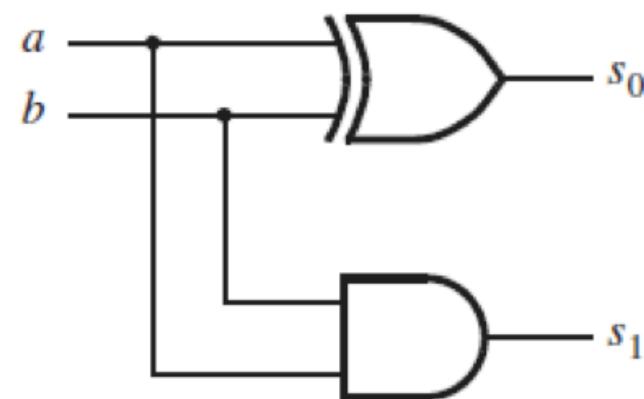

(c) Logic network

The adder module

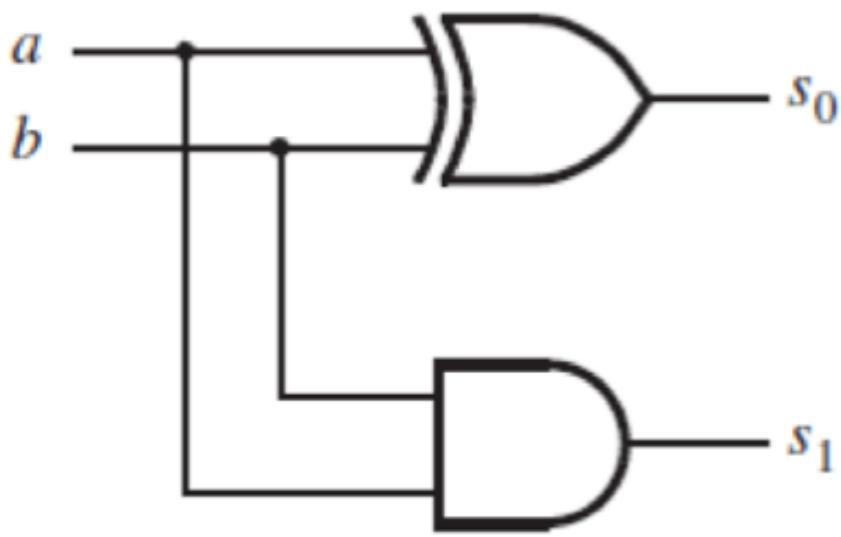

```
// An adder module
module adder (a, b, s1, s0);
    input a, b;
    output s1, s0;
    assign s1 = a & b;
    assign s0 = a ^ b;
endmodule
```

The display module

	s_1	s_0	a	b	c	d	e	f	g
0	0	0	1	1	1	1	1	1	0
1	0	1	0	1	1	0	0	0	0
2	1	0	1	1	0	1	1	0	1

$$a = \overline{s_0}$$

$$c = \overline{s_1}$$

$$e = \overline{s_0}$$

$$g = s_1 \overline{s_0}$$

$$b = 1$$

$$d = \overline{s_0}$$

$$f = \overline{s_1} \overline{s_0}$$

The display module

$$a = \overline{s_0}$$

$$b = 1$$

$$c = \overline{s_1}$$

$$d = \overline{s_0}$$

$$e = \overline{s_0}$$

$$f = \overline{s_1} \overline{s_0}$$

$$g = s_1 \overline{s_0}$$


```
// A module for driving a 7-segment display
module display (s1, s0, a, b, c, d, e, f, g);
    input s1, s0;
    output a, b, c, d, e, f, g;

    assign a = ~s0;
    assign b = 1;
    assign c = ~s1;
    assign d = ~s0;
    assign e = ~s0;
    assign f = ~s1 & ~s0;
    assign g = s1 & ~s0;

endmodule
```

Putting it all together

Top-level module

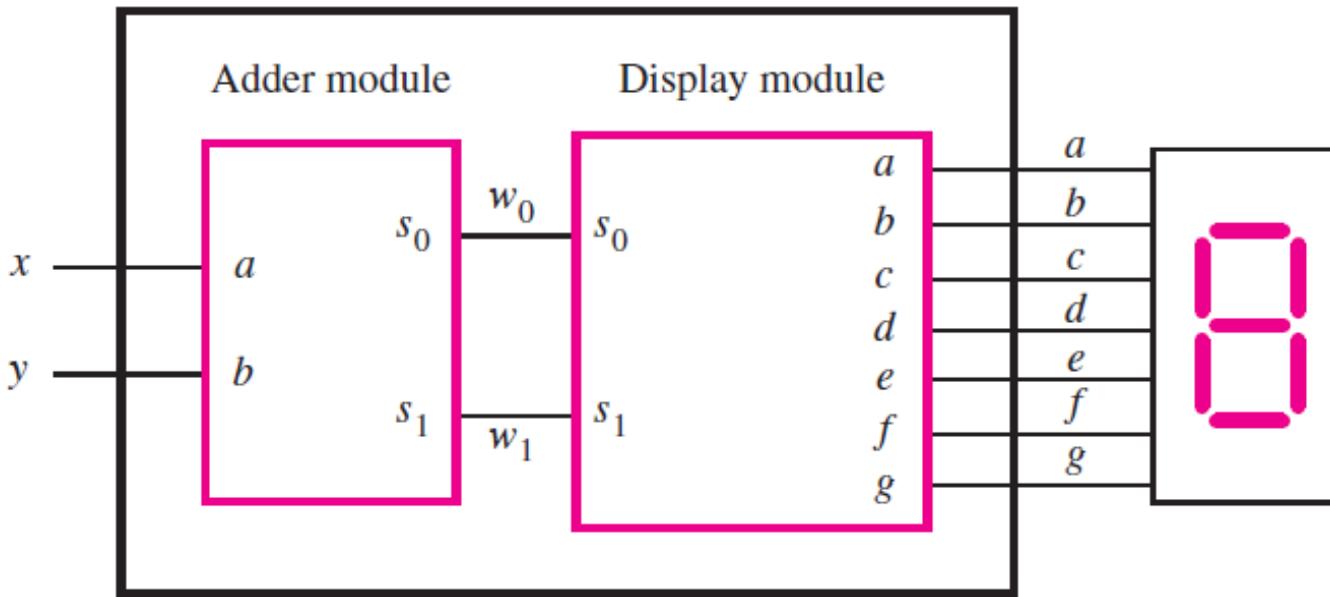

```
// An adder module
module adder (a, b, s1, s0)
    input a, b;
    output s1, s0;

    assign s1 = a & b;
    assign s0 = a ^ b;

endmodule
```

endmodule

```
// A module for driving a 7-segment display
module display (s1, s0, a, b, c, d, e, f, g);
    input s1, s0;
    output a, b, c, d, e, f, g;

    assign a = ~s0;
    assign b = 1;
    assign c = ~s1;
    assign d = ~s0;
    assign e = ~s0;
    assign f = ~s1 & ~s0;
    assign g = s1 & ~s0;
```

endmodule

```
module adder_display (x, y, a, b, c, d, e, f, g);
    input x, y;
    output a, b, c, d, e, f, g;
    wire w1, w0;

    adder U1 (x, y, w1, w0);
    display U2 (w1, w0, a, b, c, d, e, f, g);

endmodule
```

Questions?

THE END