



CprE 281: Digital Logic

Instructor: Alexander Stoytchev

<http://www.ece.iastate.edu/~alexs/classes/>

Examples of Solved Problems

CprE 281: Digital Logic
Iowa State University, Ames, IA
Copyright © Alexander Stoytchev

Administrative Stuff

- **HW5 is out**
- **It is due on Monday Oct 1 @ 4pm.**
- **Please write clearly on the first page (in block capital letters) the following three things:**
 - **Your First and Last Name**
 - **Your Student ID Number**
 - **Your Lab Section Letter**
- **Also, staple all of your pages together**

Administrative Stuff

- **No homework is due next week.**

Administrative Stuff

- **Midterm Exam #1**
- **When: Friday Sep 21.**
- **Where: This classroom**
- **What: Chapter 1 and Chapter 2 plus number systems**
- **The exam will be open book and open notes (you can bring up to 3 pages of handwritten notes).**

Topics for the Midterm Exam

- **Binary Numbers**
- **Octal Numbers**
- **Hexadecimal Numbers**
- **Conversion between the different number systems**
- **Truth Tables**
- **Boolean Algebra**
- **Logic Gates**
- **Circuit Synthesis with AND, OR, NOT**
- **Circuit Synthesis with NAND, NOR**
- **Converting an AND/OR/NOT circuit to NAND circuit**
- **Converting an AND/OR/NOT circuit to NOR circuit**
- **SOP and POS expressions**

Topics for the Midterm Exam

- **Mapping a Circuit to Verilog code**
- **Mapping Verilog code to a circuit**

- **Multiplexers**
- **Venn Diagrams**
- **K-maps for 2, 3, and 4 variables**

- **Minimization of Boolean expressions using theorems**
- **Minimization of Boolean expressions with K-maps**

- **Incompletely specified functions (with don't cares)**
- **Functions with multiple outputs**

Example 1

Determine if the following equation is valid

$$\bar{x}_1\bar{x}_3 + x_2x_3 + x_1\bar{x}_2 = \bar{x}_1x_2 + x_1x_3 + \bar{x}_2\bar{x}_3$$

$$\bar{x}_1\bar{x}_3 + x_2x_3 + x_1\bar{x}_2 \stackrel{?}{=} \bar{x}_1x_2 + x_1x_3 + \bar{x}_2\bar{x}_3$$

$$\underbrace{\bar{x}_1\bar{x}_3 + x_2x_3 + x_1\bar{x}_2}_{\text{LHS}} \stackrel{?}{=} \underbrace{\bar{x}_1x_2 + x_1x_3 + \bar{x}_2\bar{x}_3}_{\text{RHS}}$$

LHS

RHS

Left-Hand Side (LHS)

Row number	x_1	x_2	x_3	$\overline{x_1} \overline{x_3}$	$x_2 x_3$	$x_1 \overline{x_2}$	f
0	0	0	0				
1	0	0	1				
2	0	1	0				
3	0	1	1				
4	1	0	0				
5	1	0	1				
6	1	1	0				
7	1	1	1				

Left-Hand Side (LHS)

Row number	x_1	x_2	x_3	$\overline{x_1 x_3}$	$x_2 x_3$	$x_1 \overline{x_2}$	f
0	0	0	0	1	0	0	
1	0	0	1	0	0	0	
2	0	1	0	1	0	0	
3	0	1	1	0	1	0	
4	1	0	0	0	0	1	
5	1	0	1	0	0	1	
6	1	1	0	0	0	0	
7	1	1	1	0	1	0	

Left-Hand Side (LHS)

Row number	x_1	x_2	x_3	$\overline{x_1 x_3}$	$x_2 x_3$	$x_1 \overline{x_2}$	f
0	0	0	0	1	0	0	1
1	0	0	1	0	0	0	0
2	0	1	0	1	0	0	1
3	0	1	1	0	1	0	1
4	1	0	0	0	0	1	1
5	1	0	1	0	0	1	1
6	1	1	0	0	0	0	0
7	1	1	1	0	1	0	1

Right-Hand Side (RHS)

Row number	x_1	x_2	x_3	$\overline{x_1 x_2}$	$x_1 x_3$	$\overline{x_2} \overline{x_3}$	f
0	0	0	0				
1	0	0	1				
2	0	1	0				
3	0	1	1				
4	1	0	0				
5	1	0	1				
6	1	1	0				
7	1	1	1				

Right-Hand Side (RHS)

Row number	x_1	x_2	x_3	$\overline{x_1 x_2}$	$x_1 x_3$	$\overline{x_2} \overline{x_3}$	f
0	0	0	0	0	0	1	
1	0	0	1	0	0	0	
2	0	1	0	1	0	0	
3	0	1	1	1	0	0	
4	1	0	0	0	0	1	
5	1	0	1	0	1	0	
6	1	1	0	0	0	0	
7	1	1	1	0	1	0	

Right-Hand Side (RHS)

Row number	x_1	x_2	x_3	$\overline{x_1 x_2}$	$x_1 x_3$	$\overline{x_2} \overline{x_3}$	f
0	0	0	0	0	0	1	1
1	0	0	1	0	0	0	0
2	0	1	0	1	0	0	1
3	0	1	1	1	0	0	1
4	1	0	0	0	0	1	1
5	1	0	1	0	1	0	1
6	1	1	0	0	0	0	0
7	1	1	1	0	1	0	1

$$\bar{x}_1\bar{x}_3 + x_2x_3 + x_1\bar{x}_2 \stackrel{?}{=} \bar{x}_1x_2 + x_1x_3 + \bar{x}_2\bar{x}_3$$

LHS
RHS

f
1
0
1
1
1
1
1
0
1

f
1
0
1
1
1
1
1
0
1

They are equal.

Example 2

Design the minimum-cost product-of-sums expression for the function

$$f(x_1, x_2, x_3) = \sum m(0, 2, 4, 5, 6, 7)$$

Minterms and Maxterms (with three variables)

Row number	x_1	x_2	x_3	Minterm	Maxterm
0	0	0	0	$m_0 = \bar{x}_1\bar{x}_2\bar{x}_3$	$M_0 = x_1 + x_2 + x_3$
1	0	0	1	$m_1 = \bar{x}_1\bar{x}_2x_3$	$M_1 = x_1 + x_2 + \bar{x}_3$
2	0	1	0	$m_2 = \bar{x}_1x_2\bar{x}_3$	$M_2 = x_1 + \bar{x}_2 + x_3$
3	0	1	1	$m_3 = \bar{x}_1x_2x_3$	$M_3 = x_1 + \bar{x}_2 + \bar{x}_3$
4	1	0	0	$m_4 = x_1\bar{x}_2\bar{x}_3$	$M_4 = \bar{x}_1 + x_2 + x_3$
5	1	0	1	$m_5 = x_1\bar{x}_2x_3$	$M_5 = \bar{x}_1 + x_2 + \bar{x}_3$
6	1	1	0	$m_6 = x_1x_2\bar{x}_3$	$M_6 = \bar{x}_1 + \bar{x}_2 + x_3$
7	1	1	1	$m_7 = x_1x_2x_3$	$M_7 = \bar{x}_1 + \bar{x}_2 + \bar{x}_3$

Minterms and Maxterms (with three variables)

Row number	x_1	x_2	x_3	Minterm	Maxterm
0	0	0	0	$m_0 = \bar{x}_1\bar{x}_2\bar{x}_3$	$M_0 = x_1 + x_2 + x_3$
1	0	0	1	$m_1 = \bar{x}_1\bar{x}_2x_3$	$M_1 = x_1 + x_2 + \bar{x}_3$
2	0	1	0	$m_2 = \bar{x}_1x_2\bar{x}_3$	$M_2 = x_1 + \bar{x}_2 + x_3$
3	0	1	1	$m_3 = \bar{x}_1x_2x_3$	$M_3 = x_1 + \bar{x}_2 + \bar{x}_3$
4	1	0	0	$m_4 = x_1\bar{x}_2\bar{x}_3$	$M_4 = \bar{x}_1 + x_2 + x_3$
5	1	0	1	$m_5 = x_1\bar{x}_2x_3$	$M_5 = \bar{x}_1 + x_2 + \bar{x}_3$
6	1	1	0	$m_6 = x_1x_2\bar{x}_3$	$M_6 = \bar{x}_1 + \bar{x}_2 + x_3$
7	1	1	1	$m_7 = x_1x_2x_3$	$M_7 = \bar{x}_1 + \bar{x}_2 + \bar{x}_3$

**The function is
1 for these rows**

Minterms and Maxterms (with three variables)

Row number	x_1	x_2	x_3	Minterm	Maxterm
0	0	0	0	$m_0 = \bar{x}_1\bar{x}_2\bar{x}_3$	$M_0 = x_1 + x_2 + x_3$
1	0	0	1	$m_1 = \bar{x}_1\bar{x}_2x_3$	$M_1 = x_1 + x_2 + \bar{x}_3$
2	0	1	0	$m_2 = \bar{x}_1x_2\bar{x}_3$	$M_2 = x_1 + \bar{x}_2 + x_3$
3	0	1	1	$m_3 = \bar{x}_1x_2x_3$	$M_3 = x_1 + \bar{x}_2 + \bar{x}_3$
4	1	0	0	$m_4 = x_1\bar{x}_2\bar{x}_3$	$M_4 = \bar{x}_1 + x_2 + x_3$
5	1	0	1	$m_5 = x_1\bar{x}_2x_3$	$M_5 = \bar{x}_1 + x_2 + \bar{x}_3$
6	1	1	0	$m_6 = x_1x_2\bar{x}_3$	$M_6 = \bar{x}_1 + \bar{x}_2 + x_3$
7	1	1	1	$m_7 = x_1x_2x_3$	$M_7 = \bar{x}_1 + \bar{x}_2 + \bar{x}_3$

**The function is
1 for these rows**

**The function is
0 for these rows**

Two different ways to specify the same function f of three variables

$$f(x_1, x_2, x_3) = \sum m(0, 2, 4, 5, 6, 7)$$

$$f(x_1, x_2, x_3) = \prod M(1, 3)$$

The POS Expression

$$M_1 = x_1 + x_2 + \bar{x}_3$$

$$M_3 = x_1 + \bar{x}_2 + \bar{x}_3$$

$$f(x_1, x_2, x_3) = \Pi M(1, 3)$$

$$= M_1 \cdot M_3$$

$$= (x_1 + x_2 + \bar{x}_3) \cdot (x_1 + \bar{x}_2 + \bar{x}_3)$$

The Minimum POS Expression

$$\begin{aligned}f(x_1, x_2, x_3) &= (x_1 + x_2 + \bar{x}_3) \cdot (x_1 + \bar{x}_2 + \bar{x}_3) \\ &= (x_1 + \bar{x}_3 + x_2) \cdot (x_1 + \bar{x}_3 + \bar{x}_2) \\ &= (x_1 + \bar{x}_3)\end{aligned}$$

Hint: Use the following Boolean Algebra theorem

$$**14b. \quad (x + y) \cdot (x + \bar{y}) = x**$$

Alternative Solution Using K-Maps

x_1	x_2	x_3	
0	0	0	m_0
0	0	1	m_1
0	1	0	m_2
0	1	1	m_3
1	0	0	m_4
1	0	1	m_5
1	1	0	m_6
1	1	1	m_7

(a) Truth table

x_3	$x_1 x_2$	00	01	11	10
0		m_0	m_2	m_6	m_4
1		m_1	m_3	m_7	m_5

(b) Karnaugh map

Alternative Solution Using K-Maps

x_1	x_2	x_3	
0	0	0	m_0
0	0	1	m_1
0	1	0	m_2
0	1	1	m_3
1	0	0	m_4
1	0	1	m_5
1	1	0	m_6
1	1	1	m_7

(a) Truth table

		$x_1 x_2$			
		00	01	11	10
x_3	0	m_0	m_2	m_6	m_4
	1	m_1	m_3	m_7	m_5

(b) Karnaugh map

Alternative Solution Using K-Maps

x_1	x_2	x_3	
0	0	0	m_0
0	0	1	m_1
0	1	0	m_2
0	1	1	m_3
1	0	0	m_4
1	0	1	m_5
1	1	0	m_6
1	1	1	m_7

(a) Truth table

		$x_1 x_2$			
		00	01	11	10
x_3	0	m_0	m_2	m_6	m_4
	1	m_1	m_3	m_7	m_5

(b) Karnaugh map

Alternative Solution Using K-Maps

		x_1x_2			
		00	01	11	10
x_3	0	m_0	m_2	m_6	m_4
	1	m_1	m_3	m_7	m_5

Alternative Solution Using K-Maps

x_3 \ x_1x_2	00	01	11	10
0	1	1	1	1
1	0	0	1	1

Alternative Solution Using K-Maps

		x_1x_2			
		00	01	11	10
x_3	0	1	1	1	1
	1	0	0	1	1

($x_1 + \bar{x}_3$)

Example 3

Problem: A circuit that controls a given digital system has three inputs: x_1 , x_2 , and x_3 . It has to recognize three different conditions:

- Condition A is true if x_3 is true and either x_1 is true or x_2 is false
- Condition B is true if x_1 is true and either x_2 or x_3 is false
- Condition C is true if x_2 is true and either x_1 is true or x_3 is false

The control circuit must produce an output of 1 if at least two of the conditions A , B , and C are true. Design the simplest circuit that can be used for this purpose.

Condition A

Condition A is true if x_3 is true and either x_1 is true or x_2 is false

Condition A

Condition A is true if x_3 is true and either x_1 is true or x_2 is false

$$A = x_3(x_1 + \bar{x}_2) = x_3x_1 + x_3\bar{x}_2$$

Condition B

Condition B is true if x_1 is true and either x_2 or x_3 is false

Condition B

Condition B is true if x_1 is true and either x_2 or x_3 is false

$$B = x_1(\bar{x}_2 + \bar{x}_3) = x_1\bar{x}_2 + x_1\bar{x}_3$$

Condition C

Condition C is true if x_2 is true and either x_1 is true or x_3 is false

Condition C

Condition C is true if x_2 is true and either x_1 is true or x_3 is false

$$C = x_2(x_1 + \bar{x}_3) = x_2x_1 + x_2\bar{x}_3$$

The output of the circuit can be expressed as

$$f = \mathbf{AB} + AC + BC$$

$$AB = (x_3x_1 + x_3\bar{x}_2)(x_1\bar{x}_2 + x_1\bar{x}_3)$$

$$= x_3x_1x_1\bar{x}_2 + x_3x_1x_1\bar{x}_3 + x_3\bar{x}_2x_1\bar{x}_2 + x_3\bar{x}_2x_1\bar{x}_3$$

$$= x_3x_1\bar{x}_2 + 0 + x_3\bar{x}_2x_1 + 0$$

$$= x_1\bar{x}_2x_3$$

The output of the circuit can be expressed as

$$f = AB + AC + BC$$

$$AC = (x_3x_1 + x_3\bar{x}_2)(x_2x_1 + x_2\bar{x}_3)$$

$$= x_3x_1x_2x_1 + x_3x_1x_2\bar{x}_3 + x_3\bar{x}_2x_2x_1 + x_3\bar{x}_2x_2\bar{x}_3$$

$$= x_3x_1x_2 + 0 + 0 + 0$$

$$= x_1x_2x_3$$

The output of the circuit can be expressed as

$$f = AB + AC + BC$$

$$BC = (x_1\bar{x}_2 + x_1\bar{x}_3)(x_2x_1 + x_2\bar{x}_3)$$

$$= x_1\bar{x}_2x_2x_1 + x_1\bar{x}_2x_2\bar{x}_3 + x_1\bar{x}_3x_2x_1 + x_1\bar{x}_3x_2\bar{x}_3$$

$$= 0 + 0 + x_1\bar{x}_3x_2 + x_1\bar{x}_3x_2$$

$$= x_1x_2\bar{x}_3$$

Finally, we get


$$\begin{aligned} f &= x_1 \bar{x}_2 x_3 + x_1 x_2 x_3 + x_1 x_2 \bar{x}_3 \\ &= x_1 (\bar{x}_2 + x_2) x_3 + x_1 x_2 (x_3 + \bar{x}_3) \\ &= x_1 x_3 + x_1 x_2 \\ &= x_1 (x_3 + x_2) \end{aligned}$$

Example 4

Solve the previous problem using Venn diagrams.


Venn Diagrams

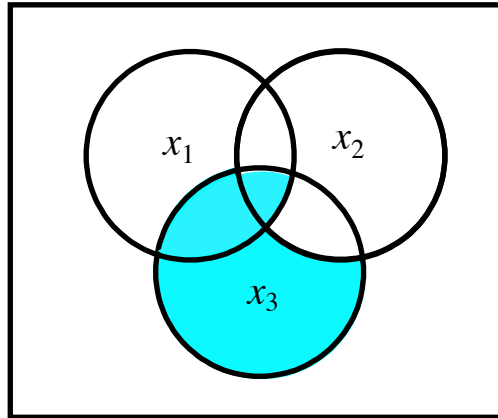(find the areas that are shaded at least two times)




(a) Function A :

$$x_3x_1 + x_3\bar{x}_2$$

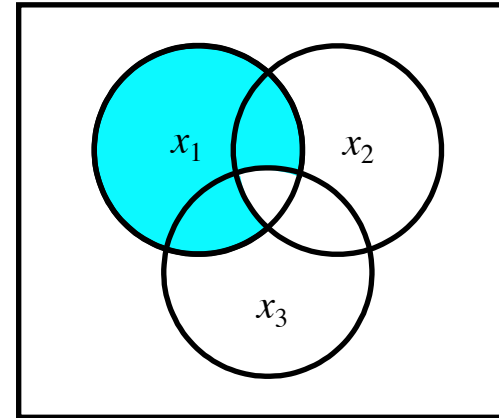


(b) Function B

$$x_1\bar{x}_2 + x_1\bar{x}_3$$

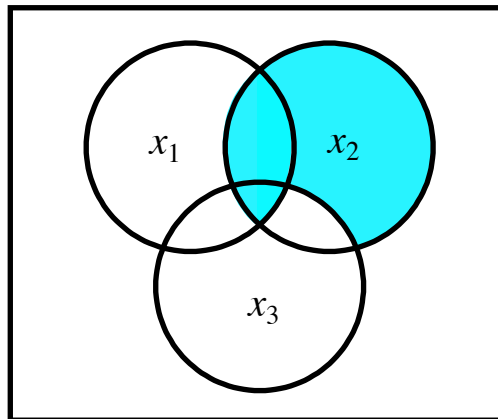

(c) Function C

$$x_2x_1 + x_2\bar{x}_3$$

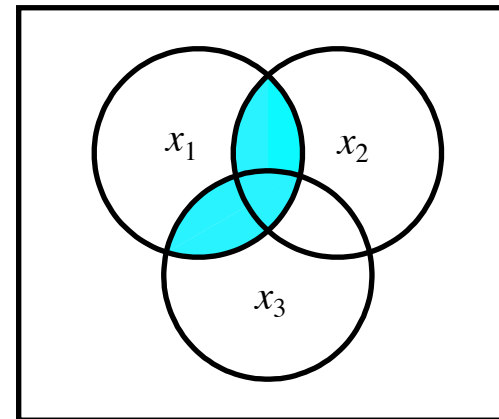

(d) Function f

$$x_1(x_3 + x_2)$$


Example 5

Design the minimum-cost SOP and POS expression for the function

$$f(x_1, x_2, x_3, x_4) = \sum m(4, 6, 8, 10, 11, 12, 15) + D(3, 5, 7, 9)$$

Let's Use a K-Map
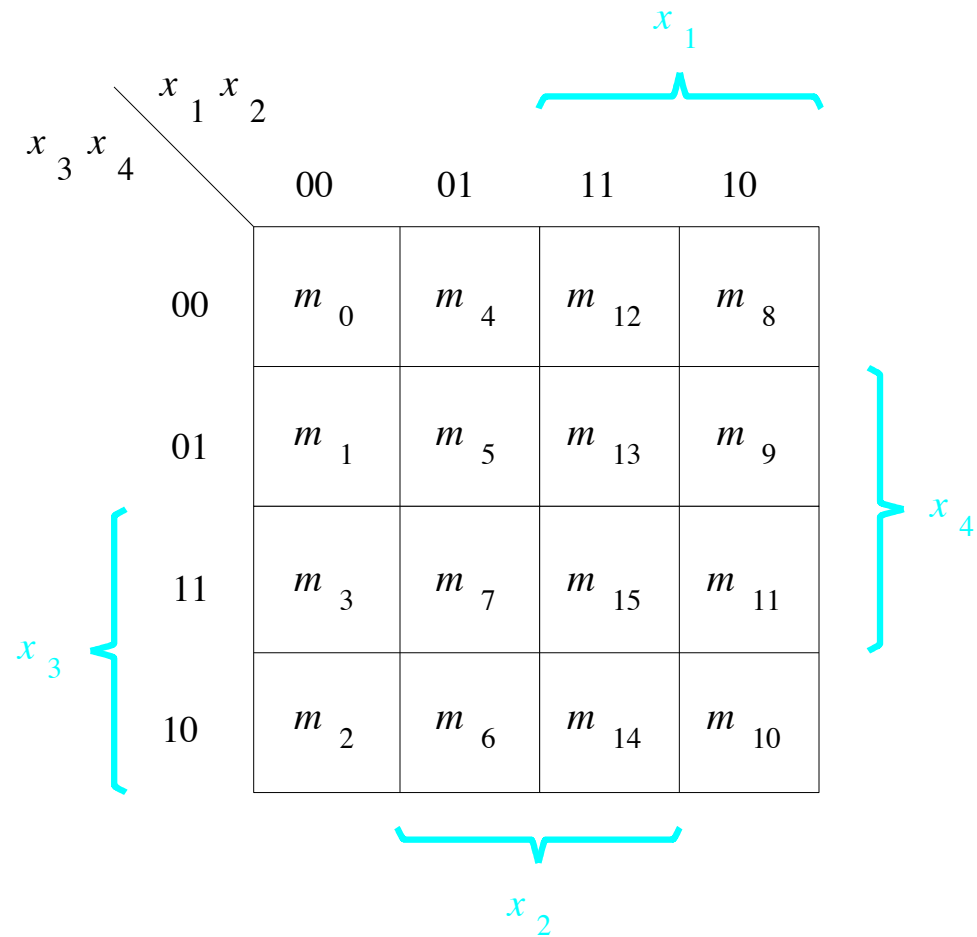
$$f(x_1, x_2, x_3, x_4) = \sum m(4, 6, 8, 10, 11, 12, 15) + D(3, 5, 7, 9)$$




Let's Use a K-Map

$$f(x_1, x_2, x_3, x_4) = \sum m(4, 6, 8, 10, 11, 12, 15) + D(3, 5, 7, 9)$$

$x_3 x_4 \backslash x_1 x_2$	00	01	11	10
00	0	1	1	1
01	0	d	0	d
11	d	d	1	1
10	0	1	0	1

The Karnaugh map is annotated with cyan brackets indicating groupings for variables x_1 , x_2 , and x_4 . A bracket above the columns 11 and 10 is labeled x_1 . A bracket below the columns 00 and 01 is labeled x_2 . A bracket to the right of the rows 01 and 11 is labeled x_4 . A bracket to the left of the rows 11 and 10 is labeled x_3 .

The SOP Expression

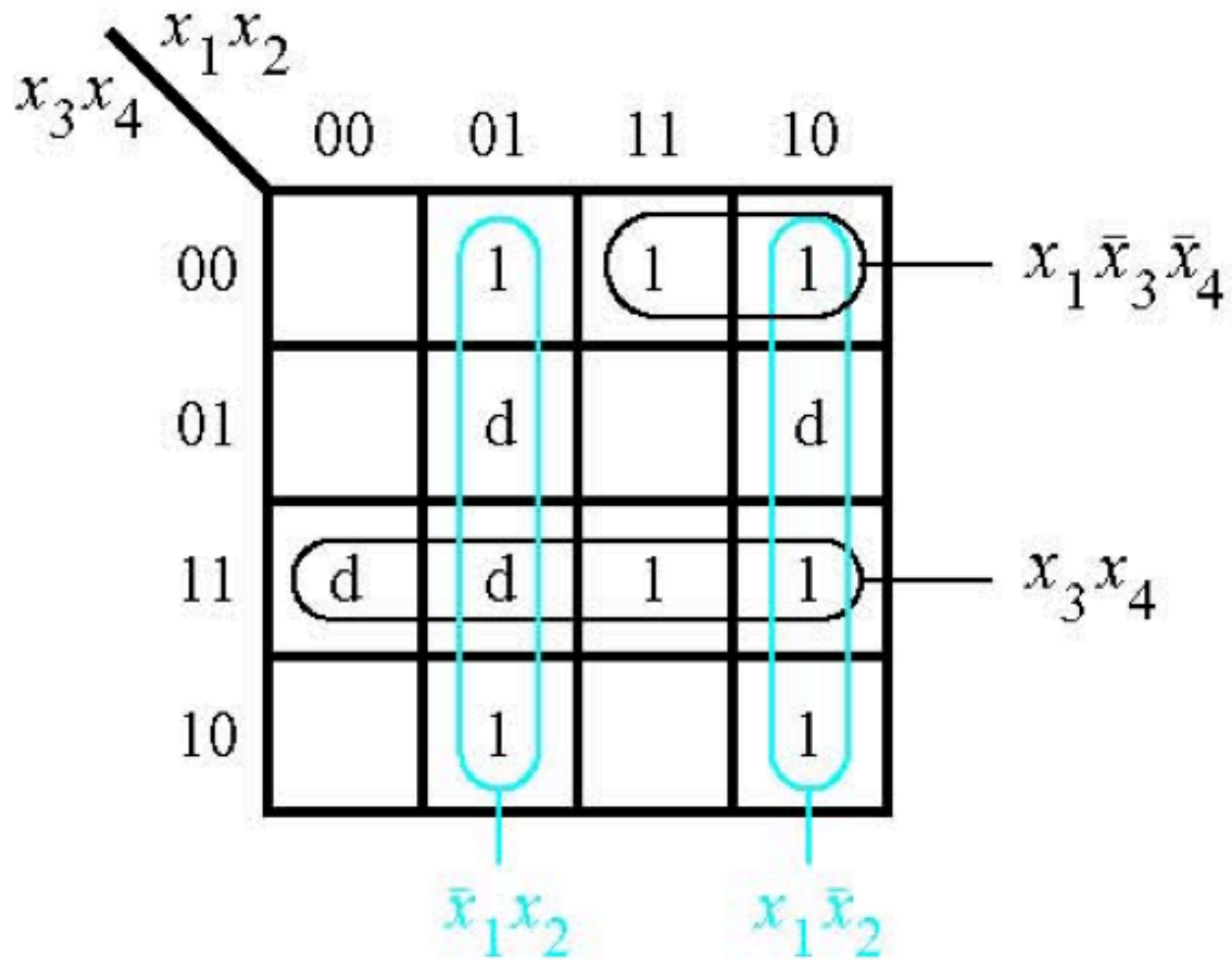


[Figure 2.67a from the textbook]

What about the POS Expression?

$$f(x_1, x_2, x_3, x_4) = \sum m(4, 6, 8, 10, 11, 12, 15) + D(3, 5, 7, 9)$$

$x_3 \ x_4$		$x_1 \ x_2$					
		00	01	11	10		
00	00	0	1	1	1		
	01	0	d	0	d		
11	11	d	d	1	1		
	10	0	1	0	1		

The POS Expression

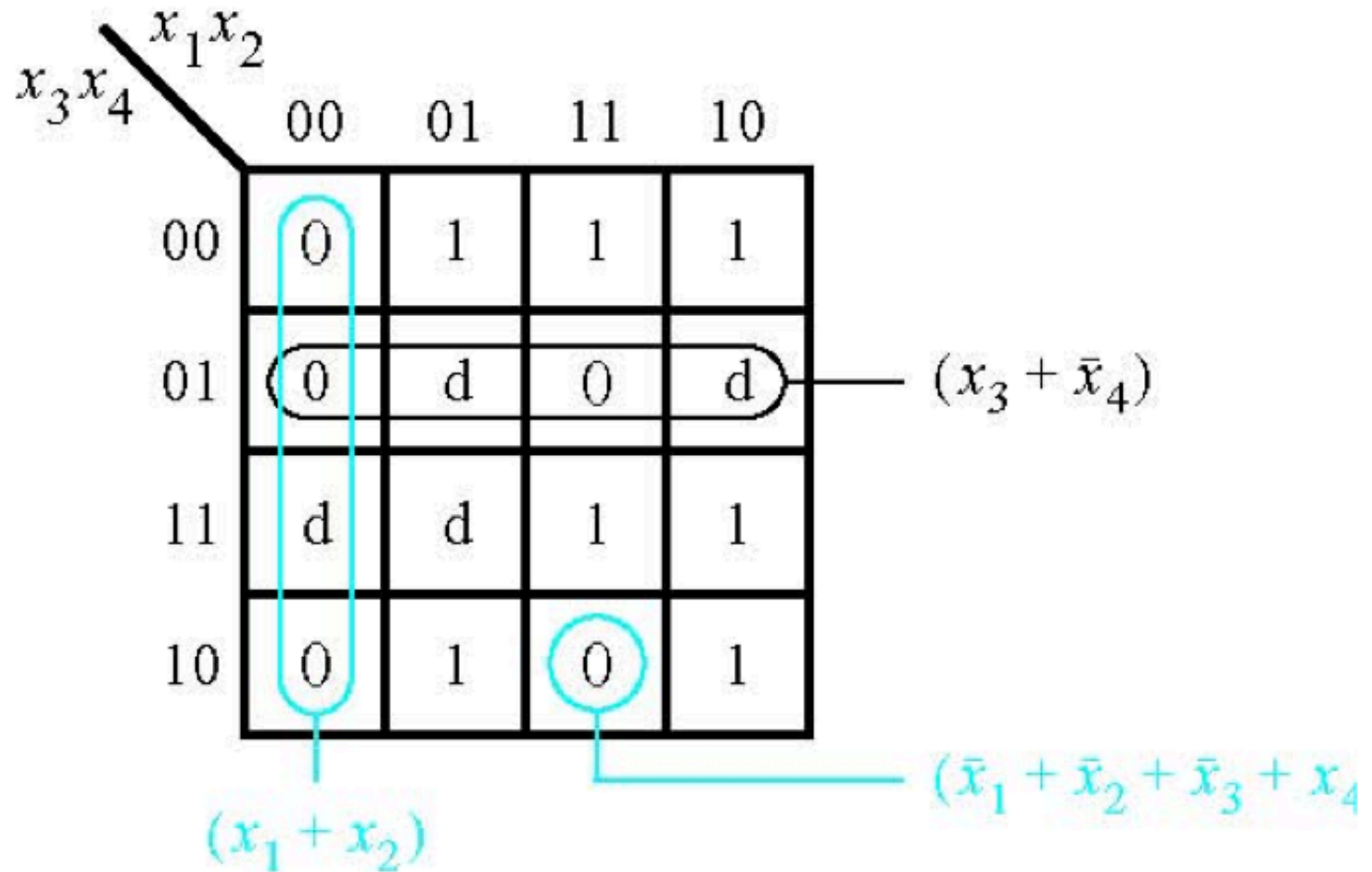

[Figure 2.67b from the textbook]

Example 6

Use K-maps to find the minimum-cost SOP and POS expression for the function

$$f(x_1, \dots, x_4) = \bar{x}_1\bar{x}_3\bar{x}_4 + x_3x_4 + \bar{x}_1\bar{x}_2x_4 + x_1x_2\bar{x}_3x_4$$

assuming that there are also don't-cares defined as $D = \sum(9, 12, 14)$.

Let's map the expression to the K-Map

$$f(x_1, \dots, x_4) = \bar{x}_1\bar{x}_3\bar{x}_4 + x_3x_4 + \bar{x}_1\bar{x}_2x_4 + x_1x_2\bar{x}_3x_4$$

$$D = \sum(9, 12, 14).$$

The Karnaugh map is a 4x4 grid with the following structure:

		$x_1 x_2$			
		00	01	11	10
$x_3 x_4$	00	m_0	m_4	m_{12}	m_8
	01	m_1	m_5	m_{13}	m_9
	11	m_3	m_7	m_{15}	m_{11}
	10	m_2	m_6	m_{14}	m_{10}

Red brackets indicate groupings for variables x_1 , x_2 , x_3 , and x_4 .

Let's map the expression to the K-Map

$$f(x_1, \dots, x_4) = \bar{x}_1\bar{x}_3\bar{x}_4 + x_3x_4 + \bar{x}_1\bar{x}_2x_4 + x_1x_2\bar{x}_3x_4$$

$$D = \sum(9, 12, 14).$$

$x_3 \ x_4$		$x_1 \ x_2$			
		00	01	11	10
x_3	00	m_0	m_4	d	m_8
	01	m_1	m_5	m_{13}	d
	11	m_3	m_7	m_{15}	m_{11}
	10	m_2	m_6	d	m_{10}


Let's map the expression to the K-Map

$$f(x_1, \dots, x_4) = \bar{x}_1\bar{x}_3\bar{x}_4 + x_3x_4 + \bar{x}_1\bar{x}_2x_4 + x_1x_2\bar{x}_3x_4$$

		$x_1 x_2$			
		00	01	11	10
$x_3 x_4$	00	m_0	m_4	d	m_8
	01	m_1	m_5	m_{13}	d
	11	m_3	m_7	m_{15}	m_{11}
	10	m_2	m_6	d	m_{10}

The SOP Expression
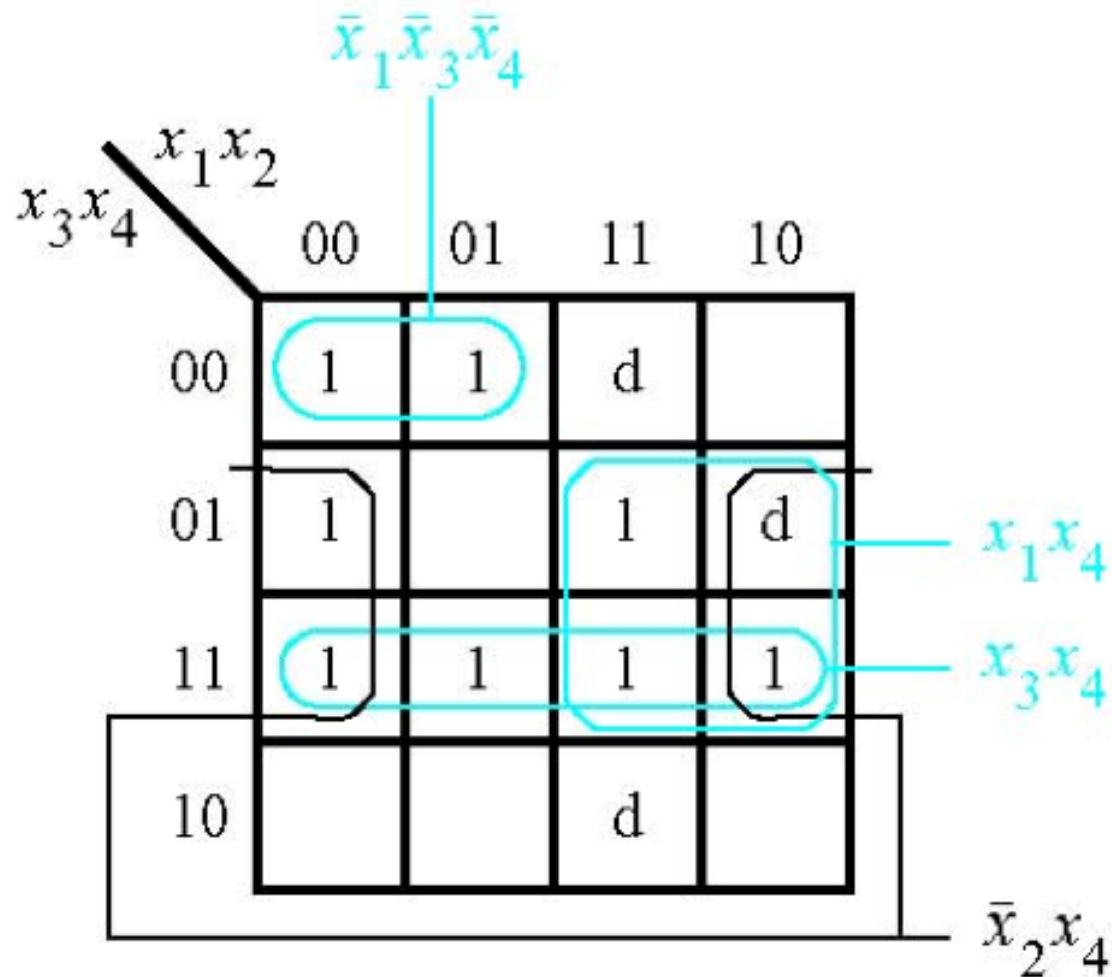
$$f(x_1, \dots, x_4) = \bar{x}_1\bar{x}_3\bar{x}_4 + x_3x_4 + \bar{x}_1\bar{x}_2x_4 + x_1x_2\bar{x}_3x_4$$



$$f = x_3x_4 + \bar{x}_1\bar{x}_3\bar{x}_4 + \bar{x}_2x_4 + x_1x_4$$

What about the POS Expression?


A Karnaugh map for a 4-variable function with variables x_1, x_2, x_3, x_4 . The map is a 4x4 grid with the following values:

$x_3 \backslash x_1 x_2$	00	01	11	10
00	1	1	d	0
01	1	0	1	d
11	1	1	1	1
10	0	0	d	0

The map is annotated with cyan brackets indicating prime implicants for each variable:

- x_1 : A horizontal bracket above the columns for $x_1 x_2 = 11$ and 10 .
- x_2 : A horizontal bracket below the columns for $x_1 x_2 = 00$ and 01 .
- x_3 : A vertical bracket to the left of the rows for $x_3 x_4 = 11$ and 10 .
- x_4 : A vertical bracket to the right of the rows for $x_3 x_4 = 01$ and 11 .

The POS Expression

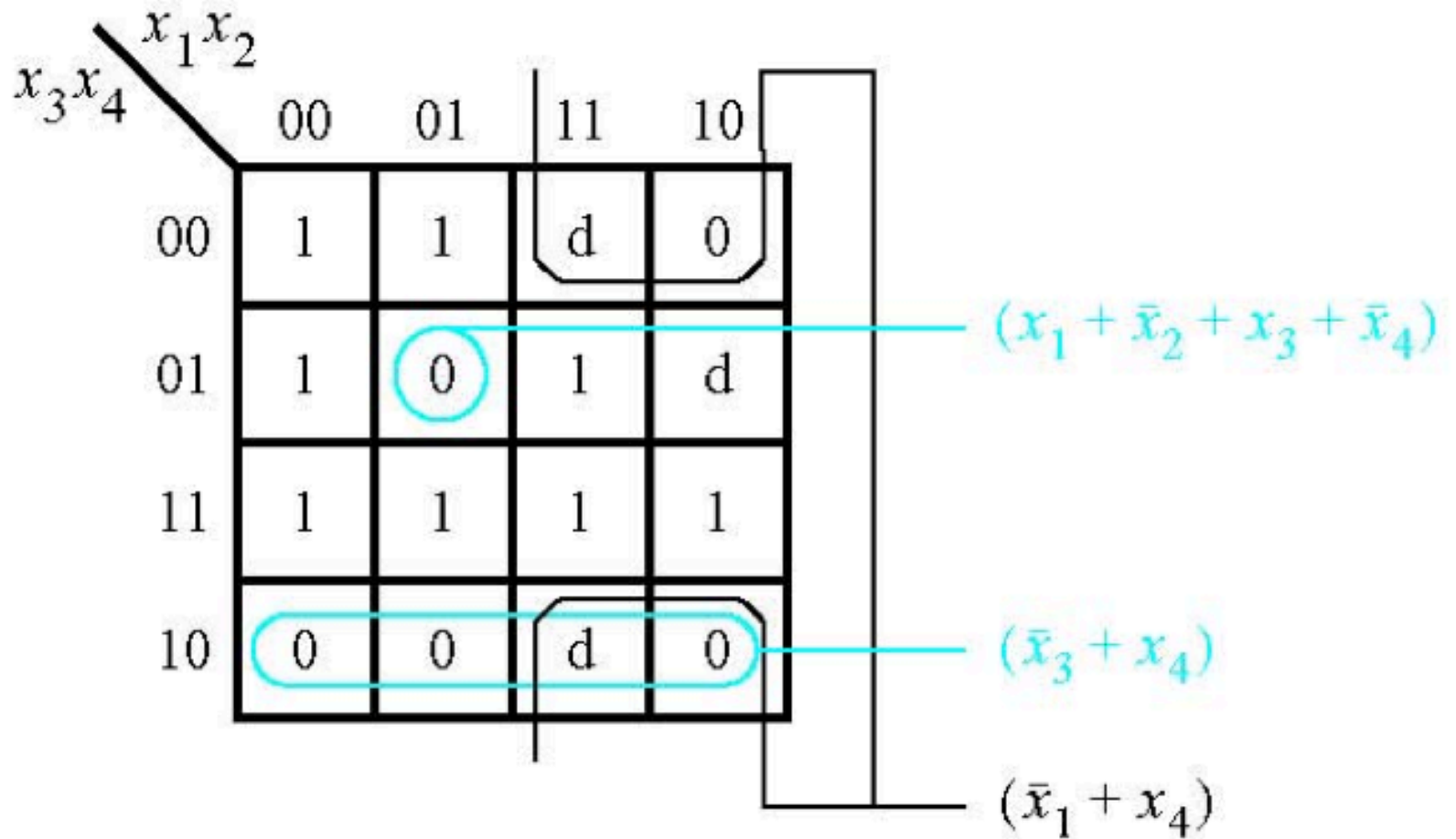

$$f = (\bar{x}_3 + x_4)(\bar{x}_1 + x_4)(x_1 + \bar{x}_2 + x_3 + \bar{x}_4)$$

Example 7

Derive the minimum-cost SOP expression for

$$f = s_3(\bar{s}_1 + \bar{s}_2) + s_1s_2$$

**First, expand the expression
using property 12a**

$$f = s_3(\bar{s}_1 + \bar{s}_2) + s_1s_2$$

$$f = \bar{s}_1s_3 + \bar{s}_2s_3 + s_1s_2$$

Construct the K-Map for this expression

$$f = \bar{s}_1 s_3 + \bar{s}_2 s_3 + s_1 s_2$$

s_1	s_2	s_3	
0	0	0	m_0
0	0	1	m_1
0	1	0	m_2
0	1	1	m_3
1	0	0	m_4
1	0	1	m_5
1	1	0	m_6
1	1	1	m_7


(a) Truth table

		$s_1 s_2$			
		00	01	11	10
s_3	0	m_0	m_2	m_6	m_4
	1	m_1	m_3	m_7	m_5

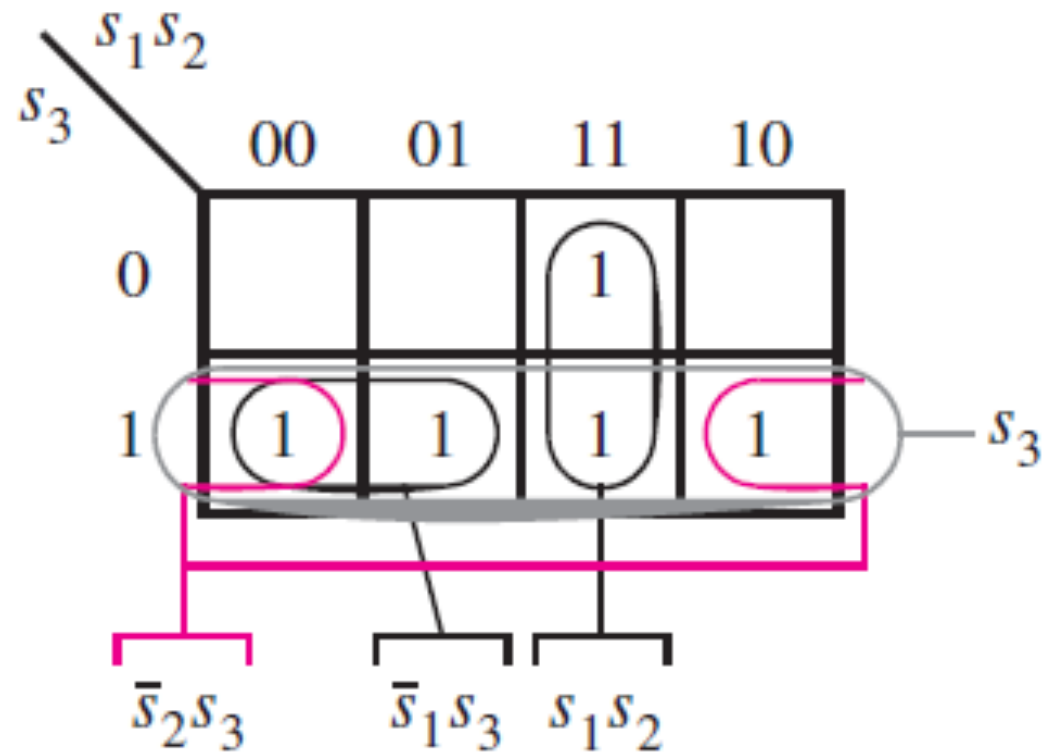(b) Karnaugh map


Construct the K-Map for this expression

$$f = \bar{s}_1 s_3 + \bar{s}_2 s_3 + s_1 s_2$$



Construct the K-Map for this expression
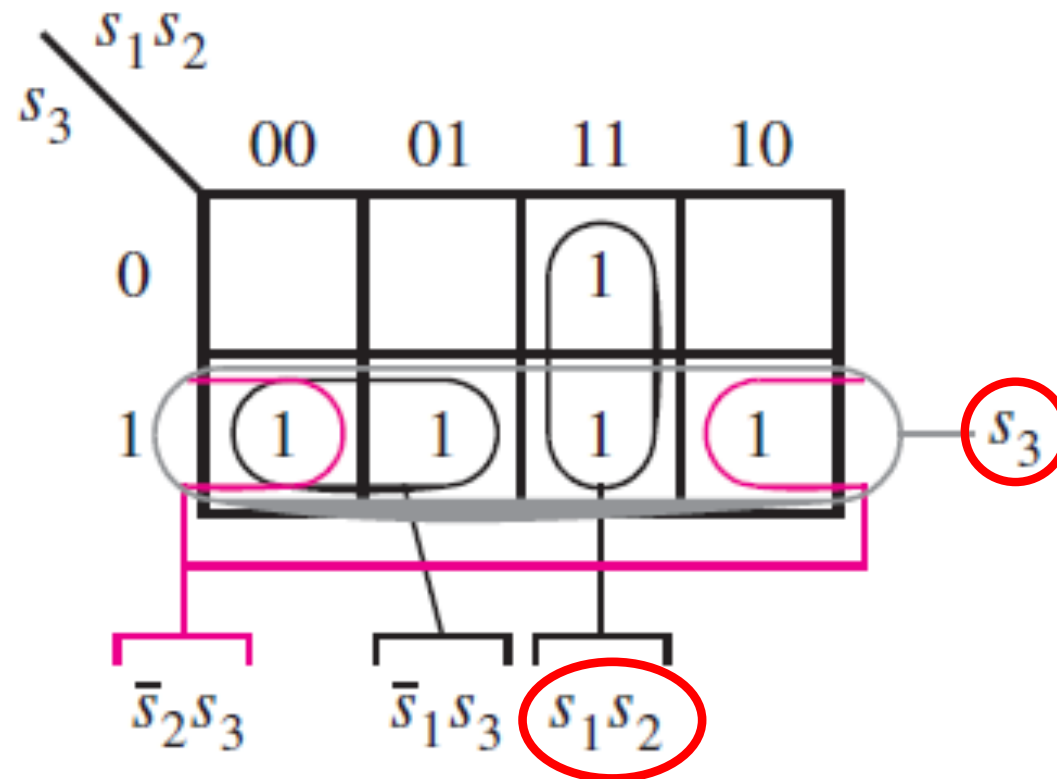
$$f = \bar{s}_1 s_3 + \bar{s}_2 s_3 + s_1 s_2$$




Simplified Expression: $f = s_3 + s_1 s_2$

Example 8


Write the Verilog code for the following circuit ...

Logic Circuit

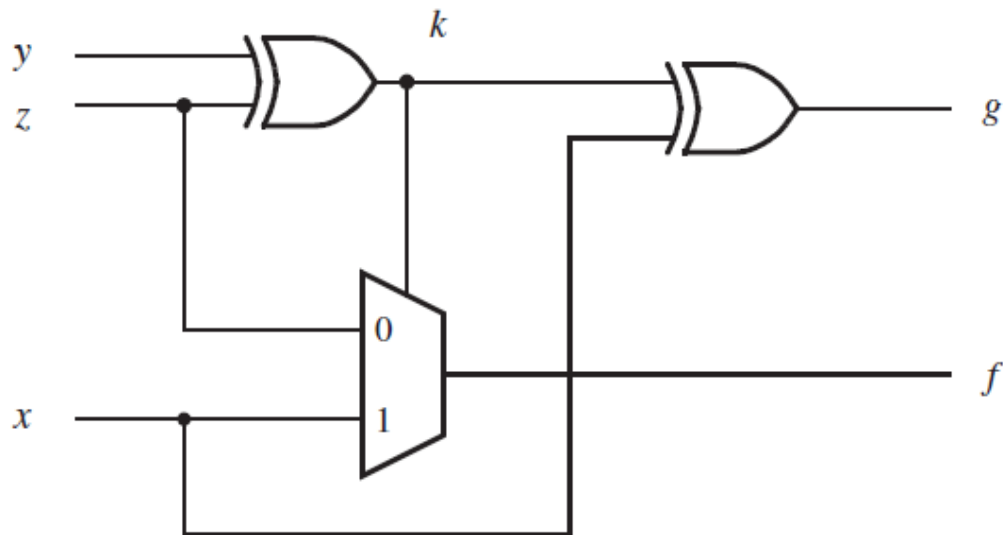


[Figure 2.70 from the textbook]

Circuit for 2-1 Multiplexer

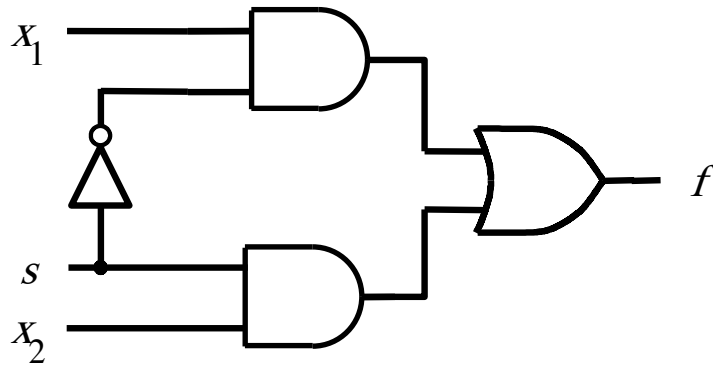


(b) Circuit

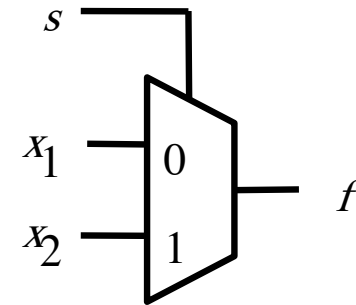

(c) Graphical symbol

$$f(s, x_1, x_2) = \bar{s} x_1 + s x_2$$

Logic Circuit vs Verilog Code

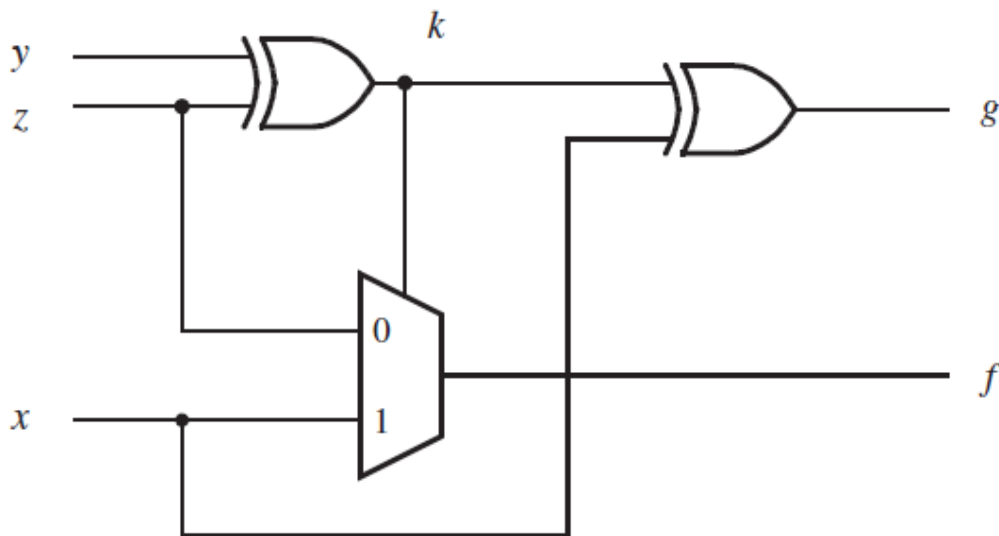


```
module f_g (x, y, z, f, g);  
  input x, y, z;  
  output f, g;  
  wire k;  
  
  assign k = y ^ z;  
  assign g = k ^ x;  
  assign f = (~k & z) | (k & x);  
  
endmodule
```


Example 9

Write the Verilog code for the following circuit ...


The Logic Circuit for this Example

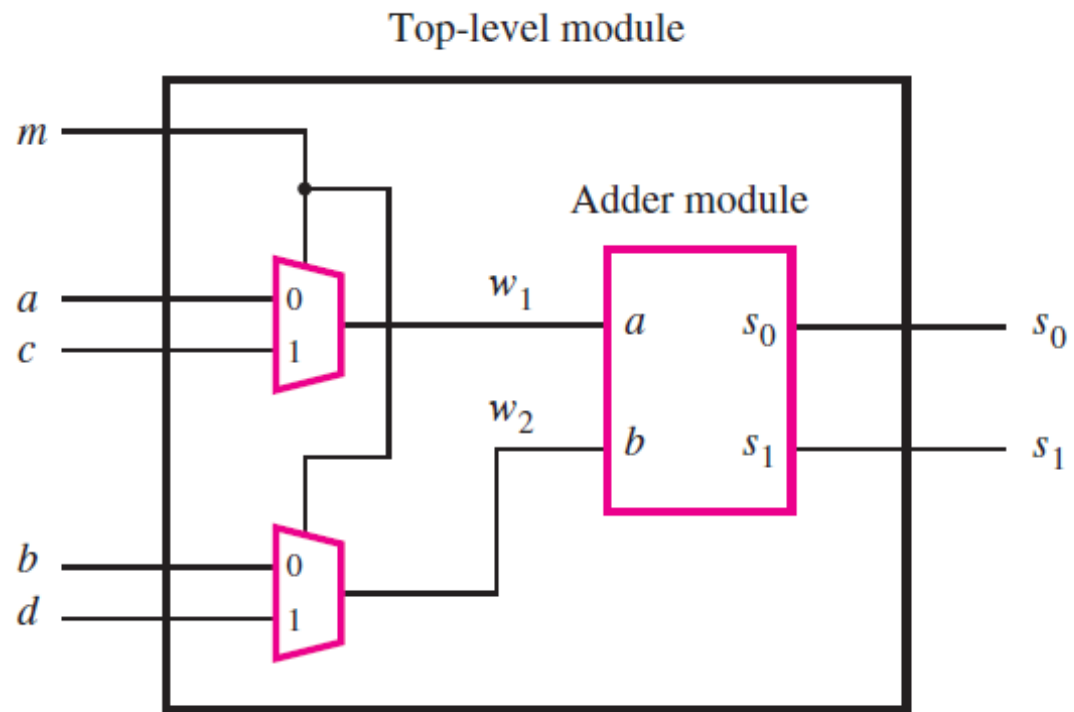

Circuit for 2-1 Multiplexer

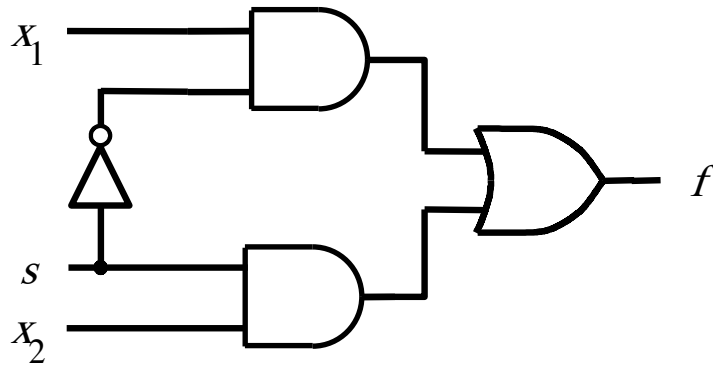


(b) Circuit

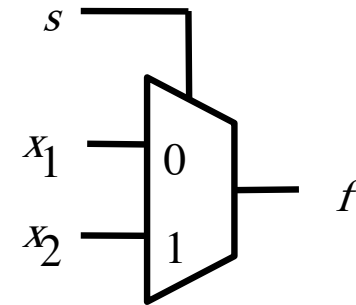

(c) Graphical symbol


$$f(s, x_1, x_2) = \bar{s} x_1 + s x_2$$

Addition of Binary Numbers

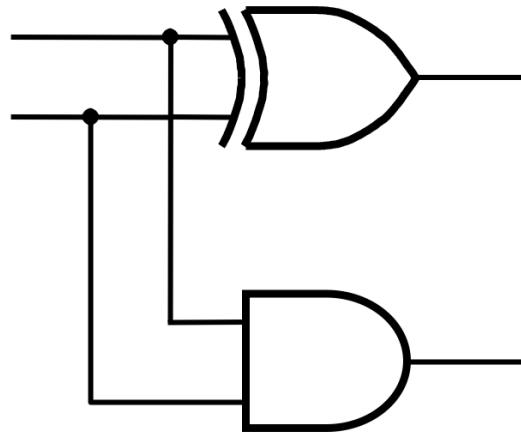

a	b	s_1	s_0
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

Logic Circuit vs Verilog Code

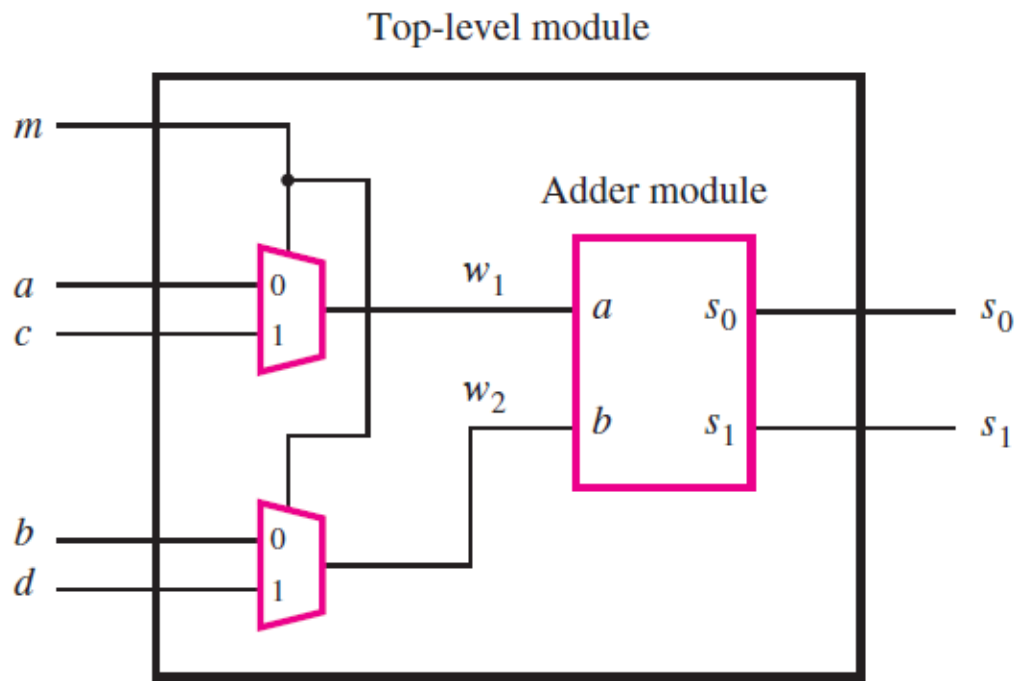


```
module shared (a, b, c, d, m, s1, s0);  
  input a, b, c, d, m;  
  output s1, s0;  
  wire w1, w2;  
  mux2to1 U1 (a, c, m, w1);  
  mux2to1 U2 (b, d, m, w2);  
  adder U3 (w1, w2, s1, s0);  
endmodule
```

```
module mux2to1 (x1, x2, s, f);  
  input x1, x2, s;  
  output f;  
  assign f = (~s & x1) | (s & x2);  
endmodule
```

```
module adder (a, b, s1, s0);  
  input a, b;  
  output s1, s0;  
  assign s1 = a & b;  
  assign s0 = a ^ b;  
endmodule
```


Some material from Appendix B

Programmable Logic Array (PLA)

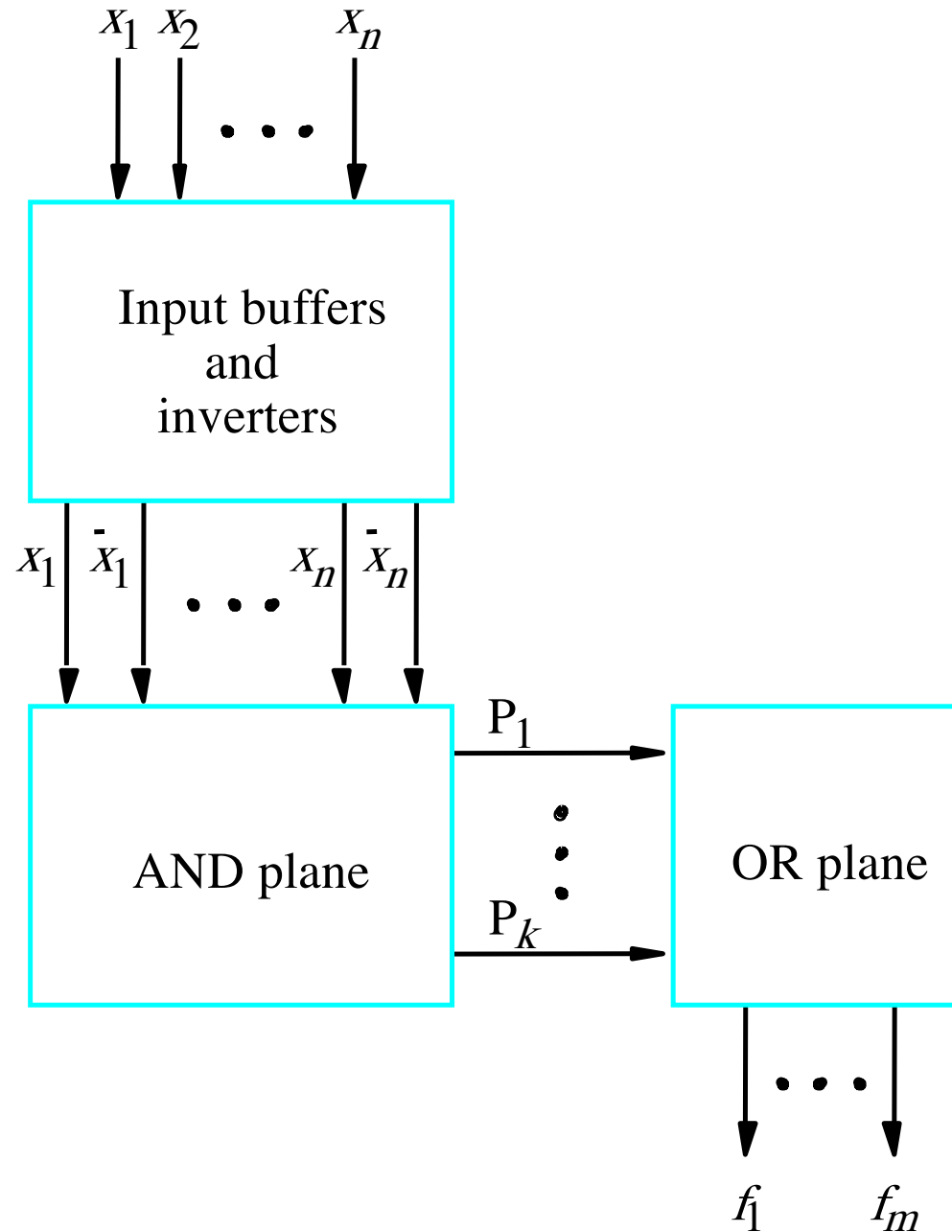


[Figure B.25 from textbook]

Gate-Level Diagram of a PLA

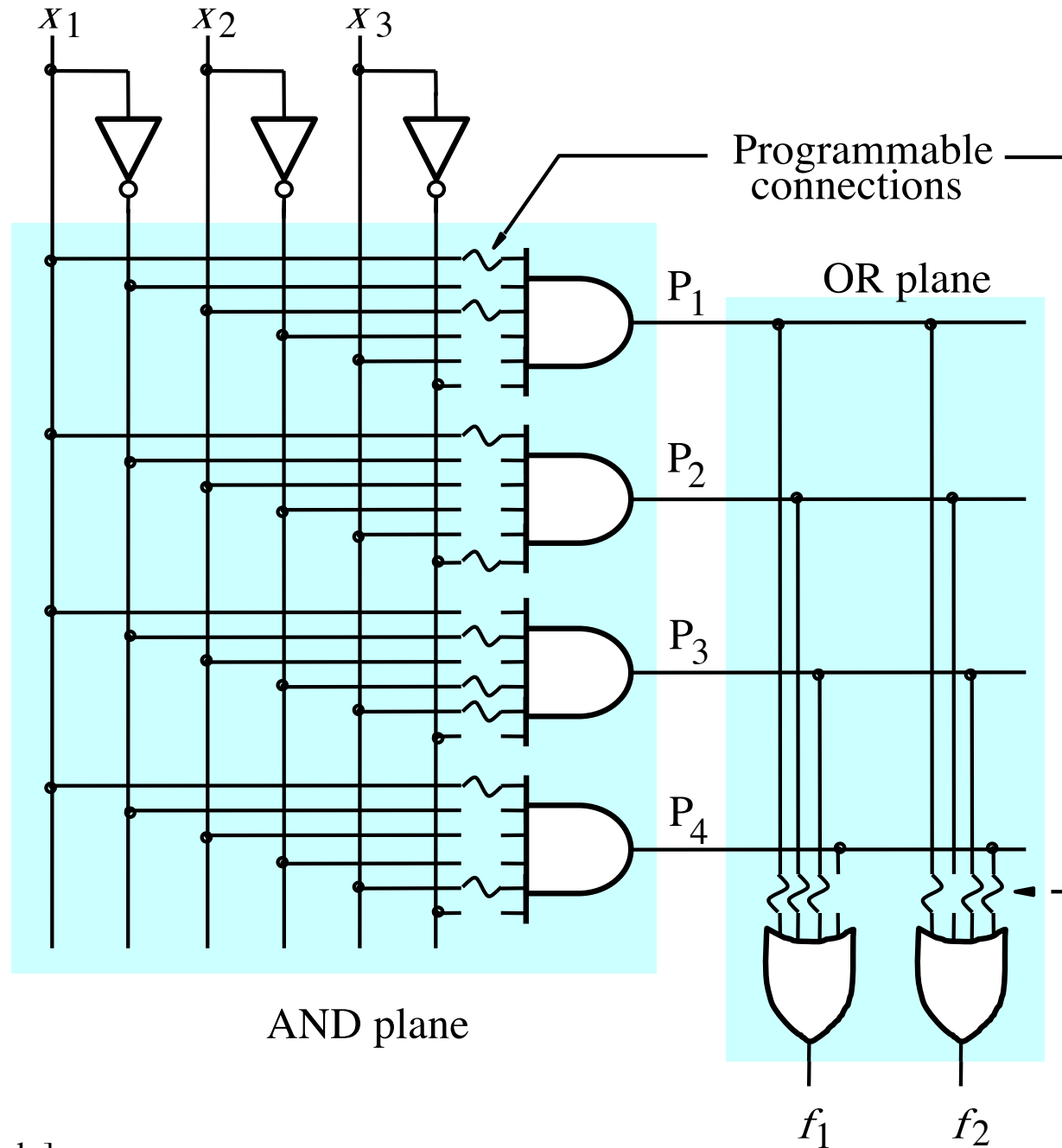


[Figure B.26 from textbook]

Customary Schematic for PLA

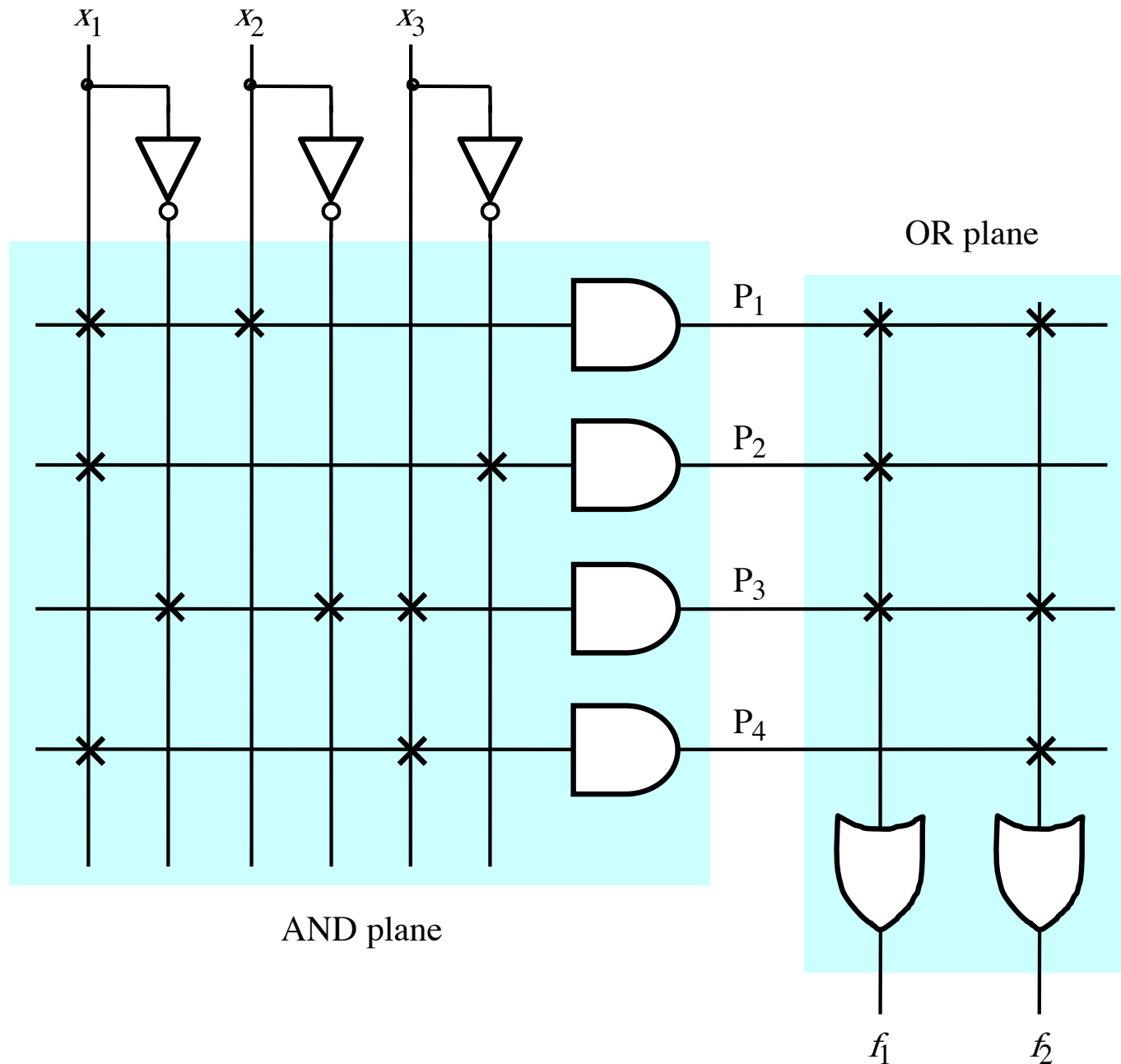


[Figure B.27 from textbook]

Programmable Array Logic (PAL)

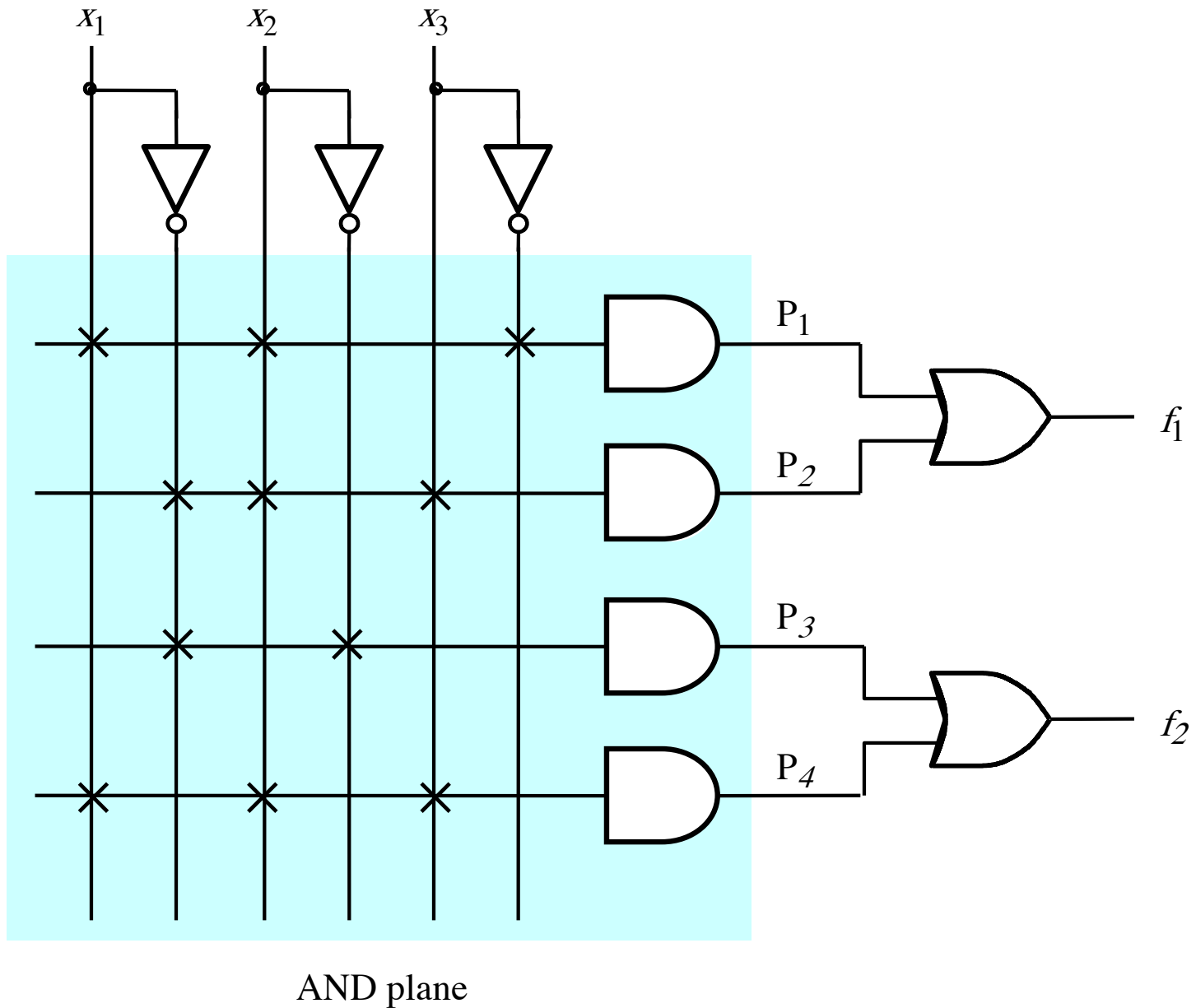

[Figure B.28 from textbook]

Programmable Array Logic (PAL)

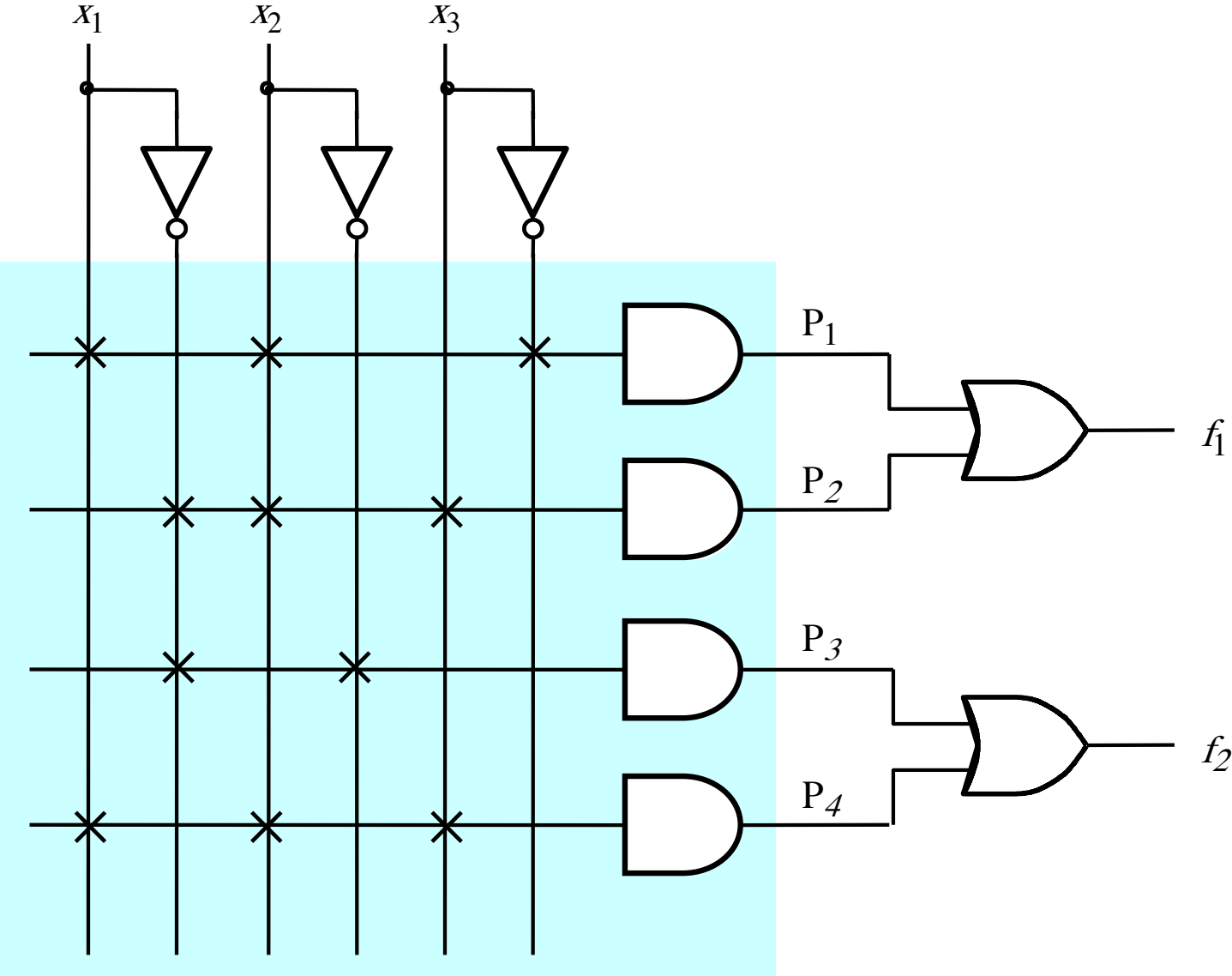

AND plane

Only the AND plane is programmable.
The OR plane is fixed.

[Figure B.28 from textbook]

Questions?

THE END