

3. Minimization with K-maps (3 x 5p each = 15p)

a) Draw the truth table for $f(a,b,c,d) = \prod M(0, 2, 3, 7, 14) + D(8,15)$. (5p)

b) Use a K-map to derive the minimum-cost SOP expression for this function. (5p)

c) Use a K-map to derive the minimum-cost POS expression for this function. (5p)

(a)

a	b	c	d	f
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	d
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	0
1	1	1	1	d

(b)

cd \ ab	ab			
	00	01	11	10
00	0	1	1	d
01	1	1	1	1
11	0	0	d	1
10	0	1	0	1

$$f = \bar{c}d + \bar{a}b\bar{d} + \bar{c}b + a\bar{b}$$

(c)


cd \ ab	ab			
	00	01	11	10
00	0	1	1	d
01	1	1	1	1
11	0	0	d	1
10	0	1	0	1

$$f = (a + b + d) \cdot (a + \bar{c} + \bar{d}) \cdot (\bar{a} + \bar{b} + \bar{c})$$


4. Basic Circuits (3 x 5p each = 15p).

In all sub-problems, draw the complete wiring diagram using logic gates (no high-level graphical symbols are allowed in this problem). Clearly label all inputs and outputs.

 (a) Gated D Latch (with NAND gates for the latch).




(b) 4-to-1 multiplexer.

 

(c) XOR gate, implemented using only AND, OR, and NOT gates.

$$XOR(a, b) = \bar{a}b + a\bar{b}$$

 

5. Number Conversions (3p + 4p + 4p + 4p = 15p)

(a) Convert 163_{10} to binary.

$$\begin{array}{r}
 163/2 = 81 \quad 1 \\
 81/2 = 40 \quad 1 \\
 40/2 = 20 \quad 0 \\
 20/2 = 10 \quad 0 \\
 10/2 = 5 \quad 0 \\
 5/2 = 2 \quad 1 \\
 2/2 = 1 \quad 0 \\
 1/2 = 0 \quad 1
 \end{array}$$

$$10100011_2$$

(b) Convert the following 32-bit float number (in IEEE 754 format) to decimal.

negative $128 + 2 + 1 = 131$

$$\overset{2^{-1}}{\underbrace{1}} \overset{2^{-2}}{\underbrace{1}} \overset{2^{-3}}{\underbrace{0}} \overset{2^{-4}}{\underbrace{1}} 1 \underbrace{000100000000000000000000}_{20 \text{ zeros}}$$

$$\begin{aligned}
 (-1)^1 \times 2^{131-127} \times (1 + 2^{-4}) &= -2^4 (1 + 2^{-4}) = -2^4 - \underbrace{2^4 \cdot 2^{-4}}_{-1} = \\
 &= -16 - 1 = -17
 \end{aligned}$$

(c) Write down the 32-bit floating point representation (in IEEE 754 format) for 15.0

$$\begin{array}{r}
 15/8 = 1.875 \\
 \underline{-8} \\
 70 \\
 \underline{-64} \\
 60 \\
 \underline{-56} \\
 40 \\
 \underline{-40} \\
 0
 \end{array}$$

$$\begin{aligned}
 8 &= 2^3 = 2^{130-127} \\
 1.875 &= 1 + 0.5 + 0.25 + 0.125
 \end{aligned}$$

$$0:10000010:11100 \dots 0$$

20 ZEROS

(d) Convert -53_{10} to an 8-bit binary number in 2's complement representation.


$$\begin{array}{r}
 53/2 = 26 \quad 1 \\
 26/2 = 13 \quad 0 \\
 13/2 = 6 \quad 1 \\
 6/2 = 3 \quad 0 \\
 3/2 = 1 \quad 1 \\
 1/2 = 0 \quad 1
 \end{array}$$

$$\begin{array}{r}
 110101 \\
 \downarrow \text{pad to 8-bit} \\
 00110101 \\
 \downarrow \text{negate} \\
 11001011
 \end{array}$$


6. Flip-Flops and Timing Diagrams (3 x 5p = 15p)

Complete the timing diagram for the specified flip-flop such that the output Q will be as indicated. Assume that the input signal can change only on the vertical lines. Also, assume that the setup time t_{su} and the hold time t_h are each equal to the width of one square.

 
a) Complete the timing diagram for the D input to a negative-edge triggered D flip-flop.



 b) Complete the timing diagram for the T input to a negative-edge triggered T flip-flop.



 c) Complete the timing diagram for the J input to a negative-edge triggered JK flip-flop.




7. Full Adder (5p + 10p = 15p)

a) Draw the truth table for a full adder with inputs X_i , Y_i , and C_i and outputs C_{i+1} and S_i . (5p)

X_i	Y_i	C_i	C_{i+1}	S_i
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

C_{i+1}	S_i
0	C_i
C_i	$\overline{C_i}$
C_i	$\overline{C_i}$
1	C_i

 b) Implement a full adder with a minimal number of 4-to-1 multiplexers and no other logic gates. Assume that the input signals are available only in their non-inverted form, along with the constants 0 and 1. Clearly label all inputs, outputs, and pins of your circuit. (10p)



this implements a NOT gate

8. Alternative Implementation (10p)

Implement the logic expression in each sub-problem in three different ways using the circuits below. In this problem, you are not allowed to use any other logic gates. Assume that a and b are available in both their inverted and non-inverted form, along with the constants 0 and 1. Indicate with words if some implementations are not possible. Label all inputs and outputs.

a) Implement in three different ways: $f = a + b$.

a	b	f
0	0	0
0	1	1
1	0	1
1	1	1




Handwritten notes: } b for (0,1) and (1,0); } 1 for (1,1)

$$\overline{\overline{a} \cdot 1} = a$$

$$\overline{\overline{b} \cdot 1} = b$$

$$\text{XOR}(a, 0) = a$$

$$\text{XOR}(b, 0) = b$$

   

b) Implement in three different ways: $f = a + \overline{b}$.

a	b	f
0	0	1
0	1	0
1	0	1
1	1	1




Handwritten notes: } b-bar for (0,0) and (1,0); } 1 for (1,1)

$$\overline{\overline{a} \cdot 1} = a$$

$$\overline{\overline{b} \cdot 1} = \overline{b}$$

$$\text{XOR}(a, 0) = a$$

$$\text{XOR}(b, 1) = \overline{b}$$

   

c) Implement in three different ways: $f = \overline{a \cdot b}$.

a	b	f
0	0	1
0	1	1
1	0	1
1	1	0

Handwritten notes: } 1 for (0,0), (0,1), (1,0); } b-bar for (1,1)

$$\overline{a \cdot b} = \overline{a} + \overline{b}$$




$$\overline{a \cdot 1} = \overline{a}$$

$$\overline{b \cdot 1} = \overline{b}$$

$$\overline{a \cdot b} = \overline{a} + \overline{b}$$


$$\text{XOR}(a, 1) = \overline{a}$$

$$\text{XOR}(b, 1) = \overline{b}$$

   

9. Adder/Subtractor with Overflow Detection (10p + 5p = 15p)

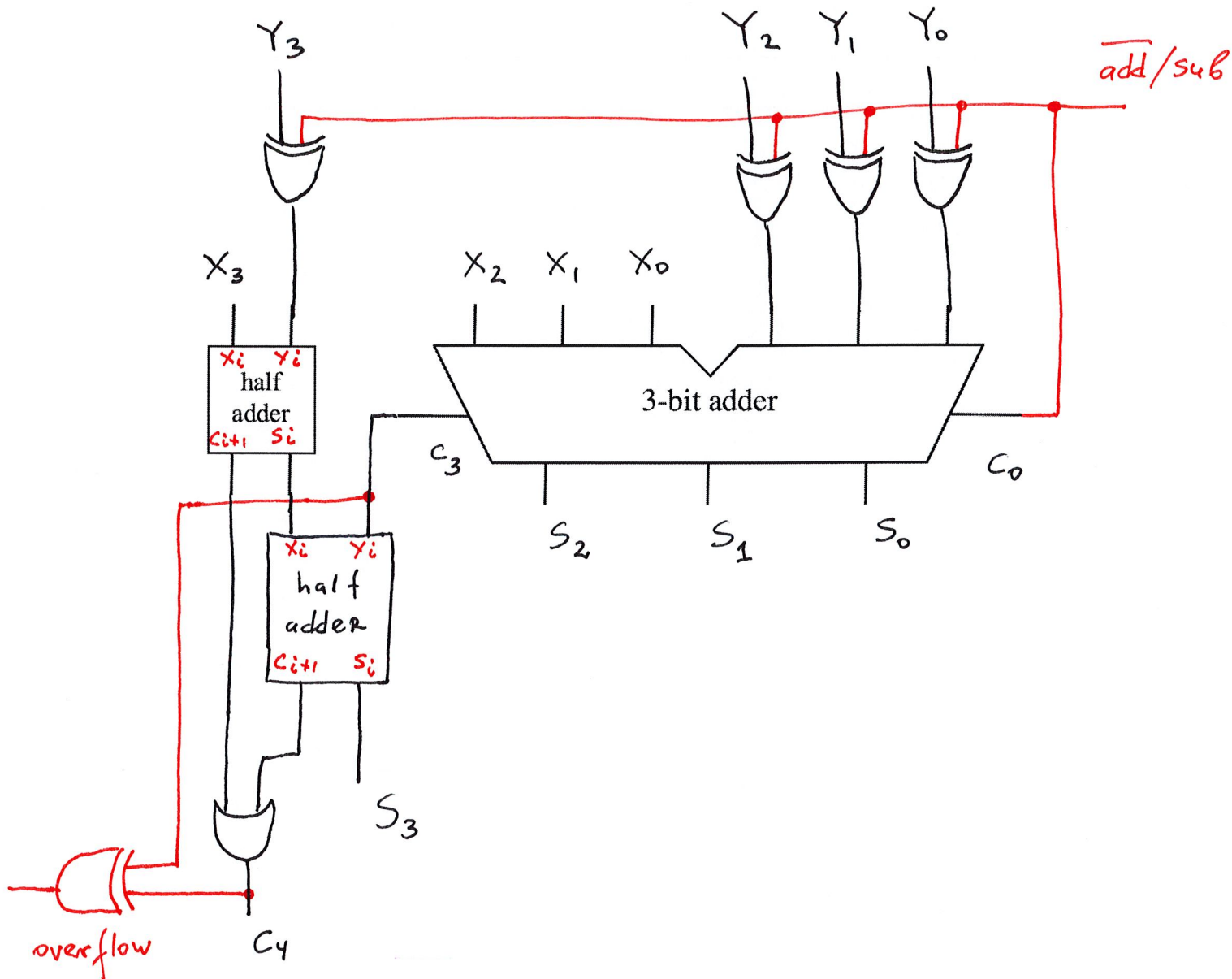(a) You are given a 3-bit adder, but it is too small for what you need, and it also does not compute an overflow flag. Complete the wiring diagram below to implement a functional 4-bit adder/subtractor unit that can also detect when an overflow has occurred. Clearly label all inputs, outputs, and pins of your circuit.



(b) Explain the correct solution in 3-4 sentences.

We need another half-adder in order to implement a full adder, plus an OR gate. To get a subtractor unit we also need additional XOR gates, including one on the new input Y_3 . The overflow flag is computed as an XOR of c_3 and c_4 .




10. Shifter Circuit (10p + 5p = 15p)

(a) Implement a shifter circuit that takes in a 4-bit unsigned binary number W and shifts all of its bits either to the left or to the right by 1 position. The direction of the shift is determined by one of the inputs to this circuit that is called R . If $R=0$, then the circuit shifts to the left. If $R=1$, then the circuit shifts to the right. In both cases the bit that is shifted out is ignored and the empty space that is created is padded with a zero. Label all inputs and outputs.

Let the input be $W = W_3 W_2 W_1 W_0$ and the output be $X = X_3 X_2 X_1 X_0$. The control input is R .

$R=0$, shift left

$R=1$, shift right

   

(b) Explain the correct solution in 3-4 sentences.

The shifting is done with four 2-to-1 multiplexers. The input R acts as the select line for all of them. The bits of $W = W_3 W_2 W_1 W_0$ are arranged on the 0 and 1 inputs to map to left/right shift. The padding is done with two zeros.

Question	Max	Score
1. True/False	10	
2. Venn Diagrams	5	
3. Minimization with K-maps	15	
4. Basic Circuits	15	
5. Number Conversions	15	
6. Flip-Flops	15	
7. Full Adder	15	
8. Alternative Implementation	10	
9. Adder/Subtractor	15	
10. Shifter Circuit	15	
TOTAL:	130	