

# **CprE 281: Digital Logic**

**Instructor: Alexander Stoytchev**

**<http://www.ece.iastate.edu/~alexs/classes/>**

# Incompletely Specified Functions & Multiple-Output Circuits

*CprE 281: Digital Logic  
Iowa State University, Ames, IA  
Copyright © Alexander Stoytchev*

# Administrative Stuff

- **HW4 is out**
- **It is due on Monday Sep 23 @ 4pm.**
- **Please write clearly on the first page (in block capital letters) the following three things:**
  - **Your First and Last Name**
  - **Your Student ID Number**
  - **Your Lab Section Letter**
- **Also, staple all of your pages together**

# **Administrative Stuff**

- **HW4 typo in P7.c**
- **Originally it said SOP instead of POS**
- **This has now been corrected on the web page**

# **Administrative Stuff**

- **HW5 is out**
- **It is due on Monday Sep 30 @ 4pm.**
- **Please write clearly on the first page (in block capital letters) the following three things:**
  - **Your First and Last Name**
  - **Your Student ID Number**
  - **Your Lab Section Letter**
- **Also, staple all of your pages together**

# **Administrative Stuff**

- **Midterm Exam #1**
- **When: Friday Sep 27.**
- **Where: This classroom**
- **What: Chapter 1 and Chapter 2 plus number systems**
- **The exam will be closed book but open notes (you can bring up to 3 pages of handwritten notes).**
- **Sample exams are posted on the class web page**

# Topics for the Midterm Exam

- **Binary Numbers**
- **Octal Numbers**
- **Hexadecimal Numbers**
- **Conversion between the different number systems**
- **Truth Tables**
- **Boolean Algebra**
- **Logic Gates**
- **Circuit Synthesis with AND, OR, NOT**
- **Circuit Synthesis with NAND, NOR**
- **Converting an AND/OR/NOT circuit to NAND circuit**
- **Converting an AND/OR/NOT circuit to NOR circuit**
- **SOP and POS expressions**

# Topics for the Midterm Exam

- **Mapping a Circuit to Verilog code**
- **Mapping Verilog code to a circuit**
  
- **Multiplexers**
- **Venn Diagrams**
- **K-maps for 2, 3, and 4 variables**
  
- **Minimization of Boolean expressions using theorems**
- **Minimization of Boolean expressions with K-maps**
  
- **Incompletely specified functions (with don't cares)**
- **Functions with multiple outputs**
  
- **Something from Star Wars**



# **Quick Review**

# The Combining Theorems of Boolean Algebra


$$14a. \quad \mathbf{x \cdot y + x \cdot \bar{y} = x}$$

$$14b. \quad \mathbf{(x + y) \cdot (x + \bar{y}) = x}$$

# One-Variable K-map

$x_1$	
0	$m_0$
1	$m_1$

(a) Truth table

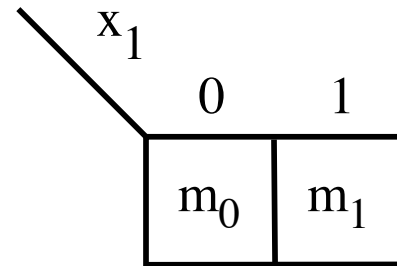


(b) Karnaugh map

# One-Variable K-map

$x_1$	
0	1
1	0

(a) Truth table

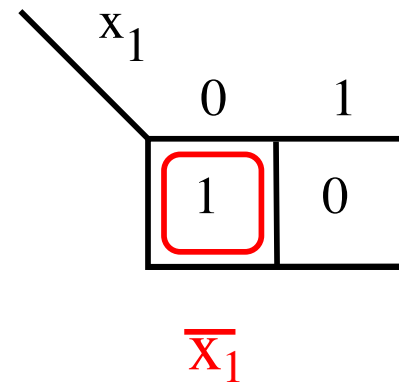


(b) Karnaugh map

# Two-Variable K-map


$x_1$	$x_2$	
0	0	$m_0$
0	1	$m_1$
1	0	$m_2$
1	1	$m_3$

(a) Truth table

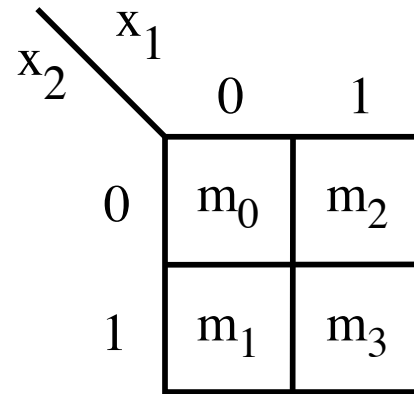

(b) Karnaugh map

# Two-Variable K-map

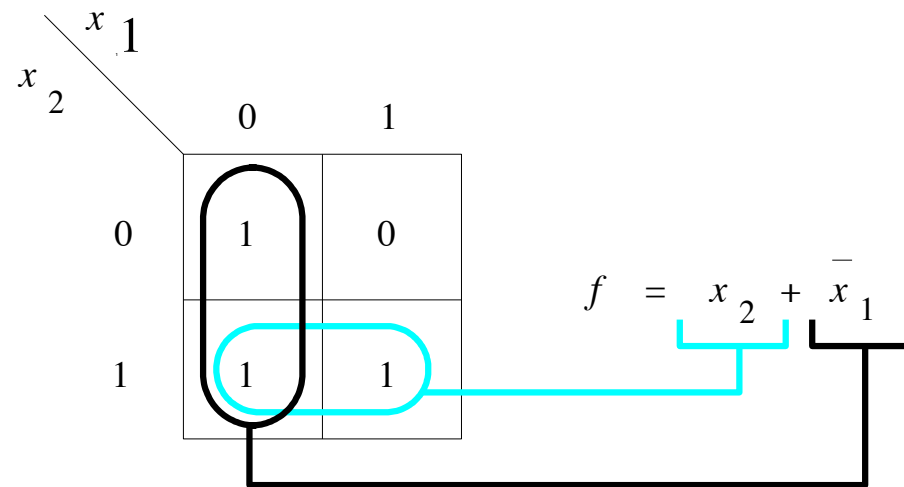

# These are all valid groupings

$x_2 \backslash x_1$	0	1
0	$m_0$	$m_2$
1	$m_1$	$m_3$

Grouping:  $m_0, m_1$  (vertical)

$x_2 \backslash x_1$	0	1
0	$m_0$	$m_2$
1	$m_1$	$m_3$

Grouping:  $m_2, m_3$  (vertical)

$x_2 \backslash x_1$	0	1
0	$m_0$	$m_2$
1	$m_1$	$m_3$

Grouping:  $m_0, m_2$  (horizontal)

$x_2 \backslash x_1$	0	1
0	$m_0$	$m_2$
1	$m_1$	$m_3$

Grouping:  $m_1, m_3$  (horizontal)

# These are also valid

	$x_1$		
$x_2$		0	1
0		$m_0$	$m_2$
1		$m_1$	$m_3$

	$x_1$		
$x_2$		0	1
0		$m_0$	$m_2$
1		$m_1$	$m_3$

	$x_1$		
$x_2$		0	1
0		$m_0$	$m_2$
1		$m_1$	$m_3$

	$x_1$		
$x_2$		0	1
0		$m_0$	$m_2$
1		$m_1$	$m_3$

But try to use larger rectangles if possible.



# These two are not valid

	$x_1$		
$x_2$		0	1
0		$m_0$	$m_2$
1		$m_1$	$m_3$

	$x_1$		
$x_2$		0	1
0		$m_0$	$m_2$
1		$m_1$	$m_3$

# Three-Variable K-map

$x_1$	$x_2$	$x_3$	
0	0	0	$m_0$
0	0	1	$m_1$
0	1	0	$m_2$
0	1	1	$m_3$
1	0	0	$m_4$
1	0	1	$m_5$
1	1	0	$m_6$
1	1	1	$m_7$

(a) Truth table

$x_3$	$x_1 x_2$	00	01	11	10
0		$m_0$	$m_2$	$m_6$	$m_4$
1		$m_1$	$m_3$	$m_7$	$m_5$

(b) Karnaugh map

# Location of three-variable minterms

$x_1$	$x_2$	$x_3$	
0	0	0	$m_0$
0	0	1	$m_1$
<hr/>			
0	1	0	$m_2$
0	1	1	$m_3$
<hr/>			
1	0	0	$m_4$
1	0	1	$m_5$
<hr/>			
1	1	0	$m_6$
1	1	1	$m_7$

(a) Truth table

$x_3$	$x_1 x_2$	00	01	11	10
0		$m_0$	$m_2$	$m_6$	$m_4$
1		$m_1$	$m_3$	$m_7$	$m_5$

(b) Karnaugh map

**Notice the placement of**


- **Variables**
- **Binary pair values**
- **Minterms**

# Adjacency Rules

		$x_1x_2$			
		00	01	11	10
$x_3$	0	$m_0$	$m_2$	$m_6$	$m_4$
	1	$m_1$	$m_3$	$m_7$	$m_5$



adjacent  
columns

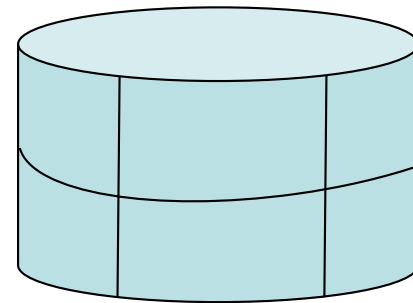


As if the K-map were  
drawn on a cylinder

# Adjacency Rules

		$x_1x_2$			
		00	01	11	10
$x_3$	0	$m_0$	$m_2$	$m_6$	$m_4$
	1	$m_1$	$m_3$	$m_7$	$m_5$




adjacent  
columns

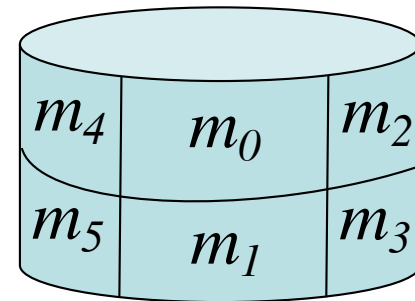


As if the K-map were  
drawn on a cylinder

# Three-Variable K-map

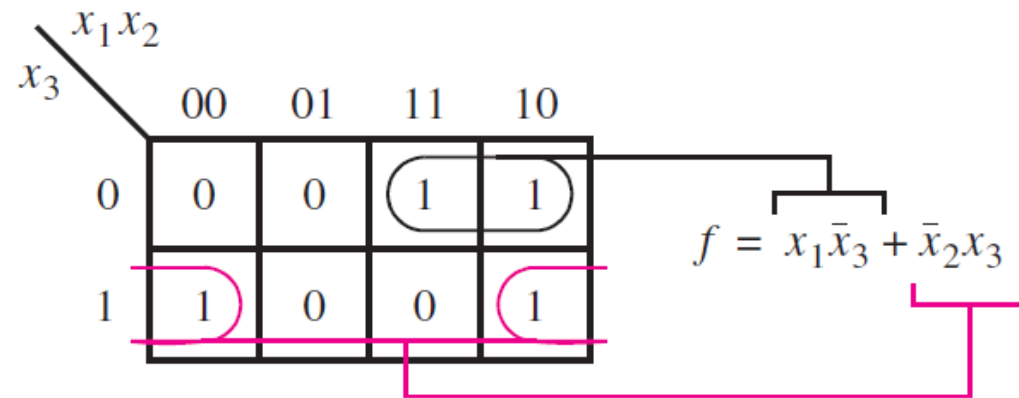

(a) The function of Figure 2.23

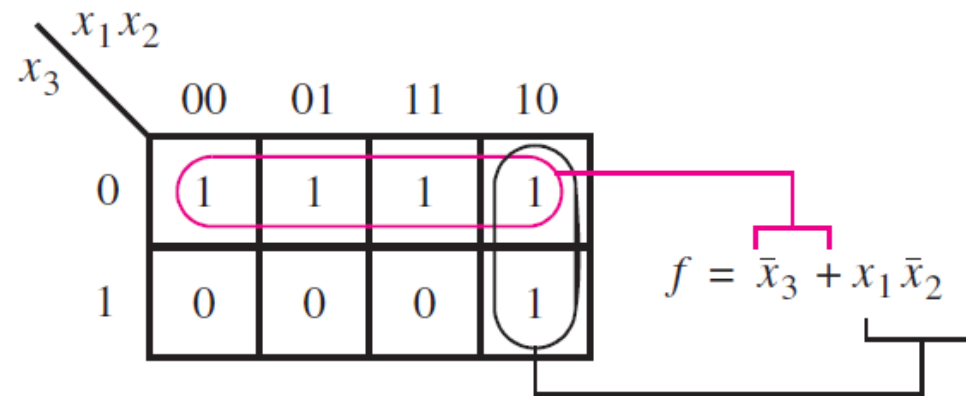

(b) The function of Figure 2.48

# Two Different Ways to Draw the K-map

$x_1$	$x_2$	$x_3$	
0	0	0	$m_0$
0	0	1	$m_1$
0	1	0	$m_2$
0	1	1	$m_3$
1	0	0	$m_4$
1	0	1	$m_5$
1	1	0	$m_6$
1	1	1	$m_7$

(a) Truth table

		$x_1 x_2$			
		00	01	11	10
$x_3$	0	$m_0$	$m_2$	$m_6$	$m_4$
	1	$m_1$	$m_3$	$m_7$	$m_5$

(b) Karnaugh map

		$x_2 x_3$			
		00	01	11	10
$x_1$	0	$m_0$	$m_1$	$m_3$	$m_2$
	1	$m_4$	$m_5$	$m_7$	$m_6$

# Another Way to Draw 3-variable K-map

$x_1$	$x_2$	$x_3$	
0	0	0	$m_0$
0	0	1	$m_1$
0	1	0	$m_2$
0	1	1	$m_3$
1	0	0	$m_4$
1	0	1	$m_5$
1	1	0	$m_6$
1	1	1	$m_7$

(a) Truth table

		$x_1 x_2$			
		00	01	11	10
$x_3$	0	$m_0$	$m_2$	$m_6$	$m_4$
	1	$m_1$	$m_3$	$m_7$	$m_5$

(b) Karnaugh map

		$x_1$	
		0	1
$x_2 x_3$	00	$m_0$	$m_4$
	01	$m_1$	$m_5$
	11	$m_3$	$m_7$
	10	$m_2$	$m_6$



# Gray Code

- **Sequence of binary codes**
- **Consecutive lines vary by only 1 bit**

	000
	001
00	011
01	010
11	110
10	111
	101
	100

# Gray Code & K-map

	$s$	$x_1$	$x_2$
$m_0$	0	0	0
$m_1$	0	0	1
$m_2$	0	1	0
$m_3$	0	1	1
$m_4$	1	0	0
$m_5$	1	0	1
$m_6$	1	1	0
$m_7$	1	1	1

		$s x_1$			
		00	01	11	10
$x_2$	0	$m_0$	$m_2$	$m_6$	$m_4$
	1	$m_1$	$m_3$	$m_7$	$m_5$

# Gray Code & K-map

	$s$	$x_1$	$x_2$
$m_0$	0	0	0
$m_1$	0	0	1
$m_2$	0	1	0
$m_3$	0	1	1
$m_4$	1	0	0
$m_5$	1	0	1
$m_6$	1	1	0
$m_7$	1	1	1

		$s x_1$			
		00	01	11	10
$x_2$	0	000	010	110	100
	1	001	011	111	101

# Gray Code & K-map

	$s$	$x_1$	$x_2$
$m_0$	0	0	0
$m_1$	0	0	1
$m_2$	0	1	0
$m_3$	0	1	1
$m_4$	1	0	0
$m_5$	1	0	1
$m_6$	1	1	0
$m_7$	1	1	1

		$s \ x_1$			
		00	01	11	10
$x_2$	0	000	010	110	100
	1	001	011	111	101

These two neighbors  
differ only in the LAST bit

# Gray Code & K-map

	$s$	$x_1$	$x_2$
$m_0$	0	0	0
$m_1$	0	0	1
$m_2$	0	1	0
$m_3$	0	1	1
$m_4$	1	0	0
$m_5$	1	0	1
$m_6$	1	1	0
$m_7$	1	1	1

		$s \ x_1$			
		00	01	11	10
$x_2$	0	000	010	110	100
	1	001	011	111	101

These two neighbors  
differ only in the LAST bit

# Gray Code & K-map

	$s$	$x_1$	$x_2$
$m_0$	0	0	0
$m_1$	0	0	1
$m_2$	0	1	0
$m_3$	0	1	1
$m_4$	1	0	0
$m_5$	1	0	1
$m_6$	1	1	0
$m_7$	1	1	1

		$s \ x_1$			
		00	01	11	10
$x_2$	0	000	010	110	100
	1	001	011	111	101

These two neighbors  
differ only in the FIRST bit

# Gray Code & K-map

	$s$	$x_1$	$x_2$
$m_0$	0	0	0
$m_1$	0	0	1
$m_2$	0	1	0
$m_3$	0	1	1
$m_4$	1	0	0
$m_5$	1	0	1
$m_6$	1	1	0
$m_7$	1	1	1

$x_2$	$s$	$x_1$				
			00	01	11	10
0			000	010	110	100
1			001	011	111	101

These two neighbors  
differ only in the FIRST bit

# Gray Code & K-map

	$s$	$x_1$	$x_2$
$m_0$	0	0	0
$m_1$	0	0	1
$m_2$	0	1	0
$m_3$	0	1	1
$m_4$	1	0	0
$m_5$	1	0	1
$m_6$	1	1	0
$m_7$	1	1	1


		$s \ x_1$			
		00	01	11	10
$x_2$	0	000	010	110	100
	1	001	011	111	101

These four neighbors  
differ in the FIRST and LAST bit

They are similar in their MIDDLE bit




# A four-variable Karnaugh map

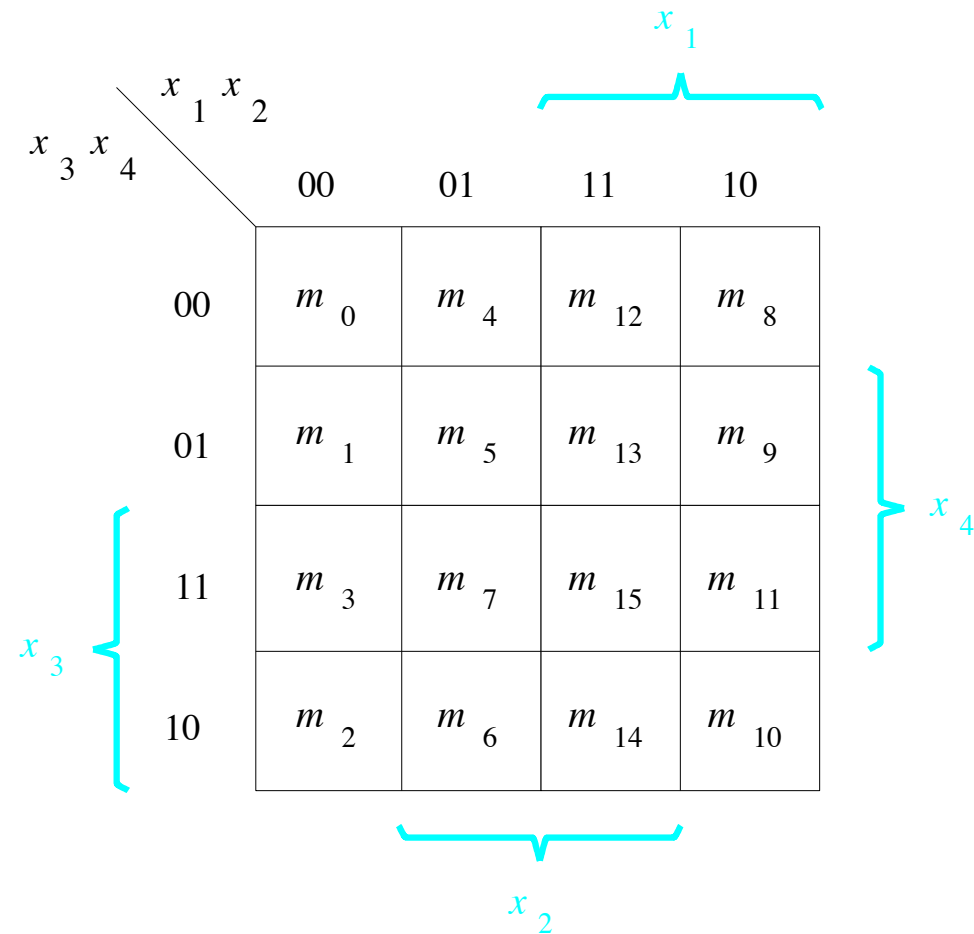


# A four-variable Karnaugh map

x1	x2	x3	x4	
0	0	0	0	m0
0	0	0	1	m1
0	0	1	0	m2
0	0	1	1	m3
<hr/>				
0	1	0	0	m4
0	1	0	1	m5
0	1	1	0	m6
0	1	1	1	m7
<hr/>				
1	0	0	0	m8
1	0	0	1	m9
1	0	1	0	m10
1	0	1	1	m11
<hr/>				
1	1	0	0	m12
1	1	0	1	m13
1	1	1	0	m14
1	1	1	1	m15

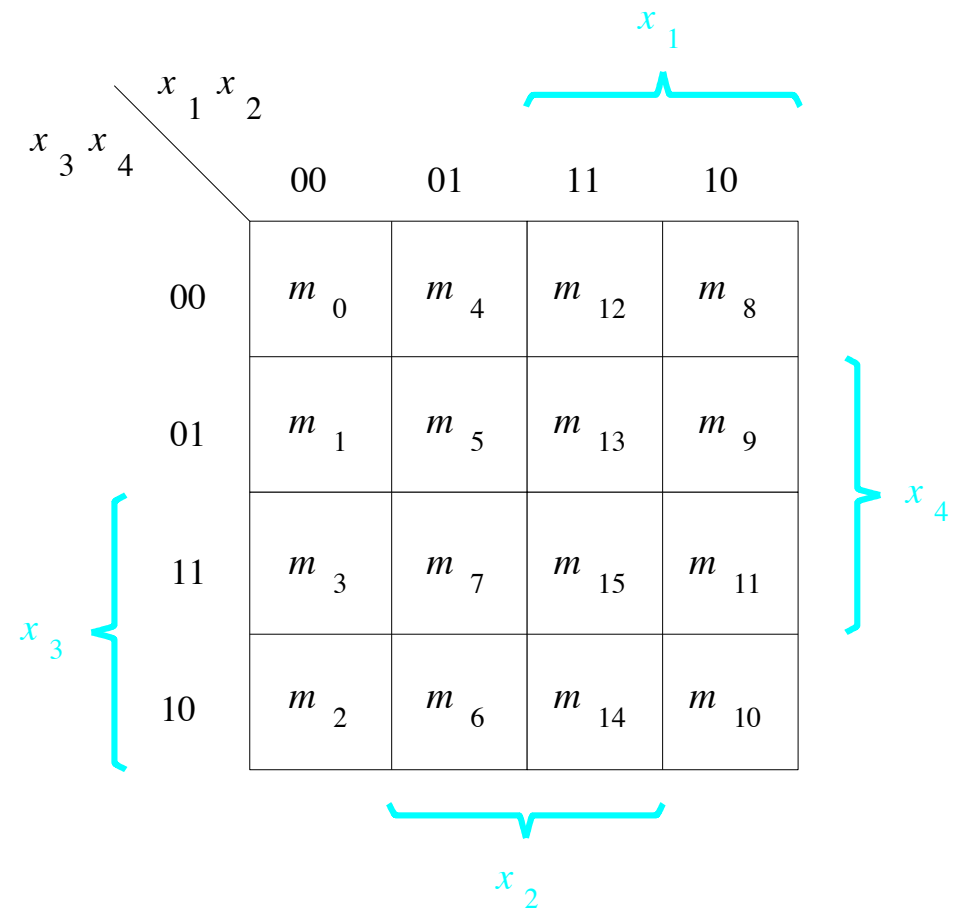


# Gray Code & K-map

x1	x2	x3	x4	
0	0	0	0	m0
0	0	0	1	m1
0	0	1	0	m2
0	0	1	1	m3
<hr/>				
0	1	0	0	m4
0	1	0	1	m5
0	1	1	0	m6
0	1	1	1	m7
<hr/>				
1	0	0	0	m8
1	0	0	1	m9
1	0	1	0	m10
1	0	1	1	m11
<hr/>				
1	1	0	0	m12
1	1	0	1	m13
1	1	1	0	m14
1	1	1	1	m15

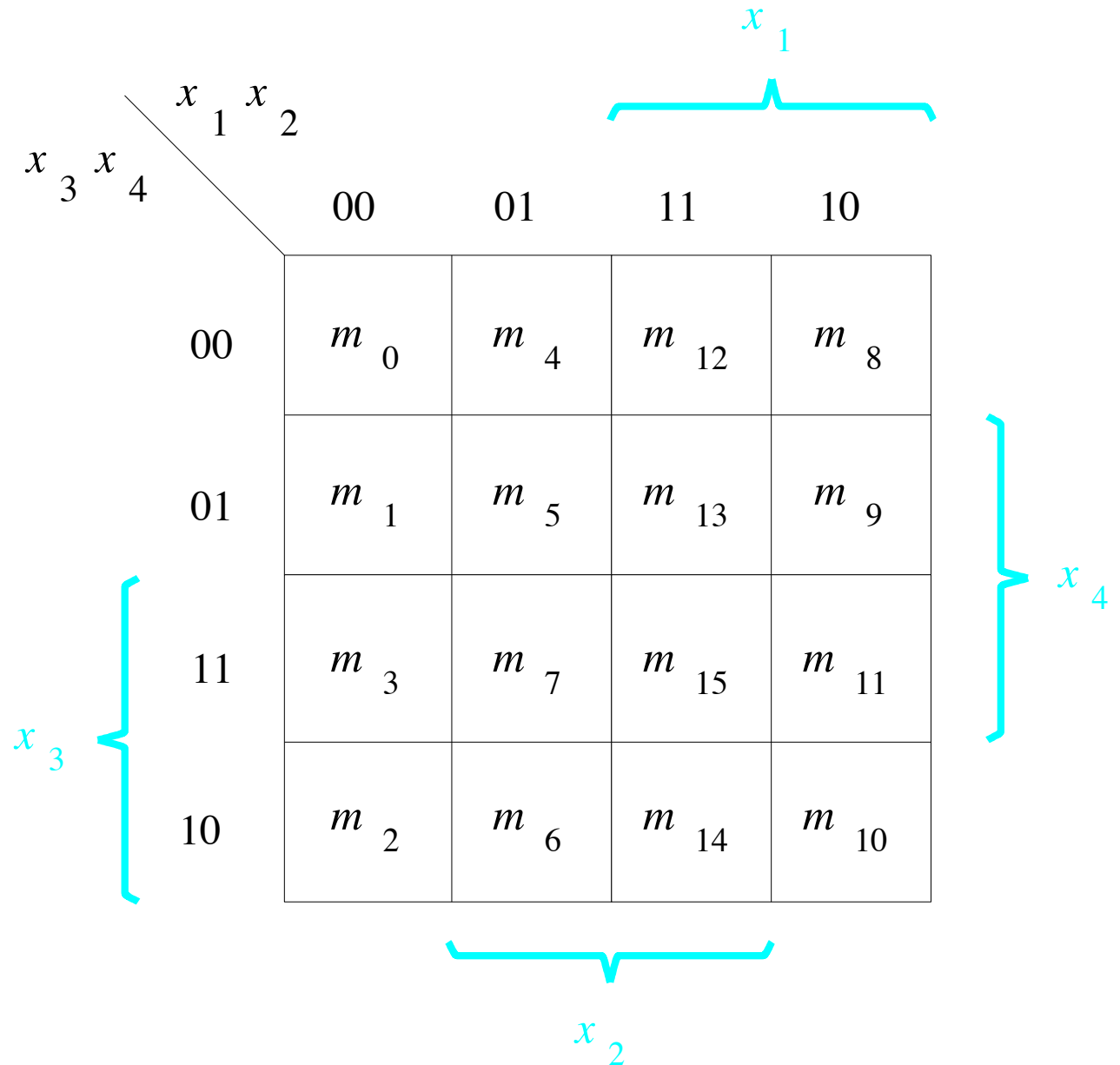

# Gray Code & K-map

x1	x2	x3	x4	
0	0	0	0	m0
0	0	0	1	m1
0	0	1	0	m2
0	0	1	1	m3
<hr/>				
0	1	0	0	m4
0	1	0	1	m5
0	1	1	0	m6
0	1	1	1	m7
<hr/>				
1	0	0	0	m8
1	0	0	1	m9
1	0	1	0	m10
1	0	1	1	m11
<hr/>				
1	1	0	0	m12
1	1	0	1	m13
1	1	1	0	m14
1	1	1	1	m15

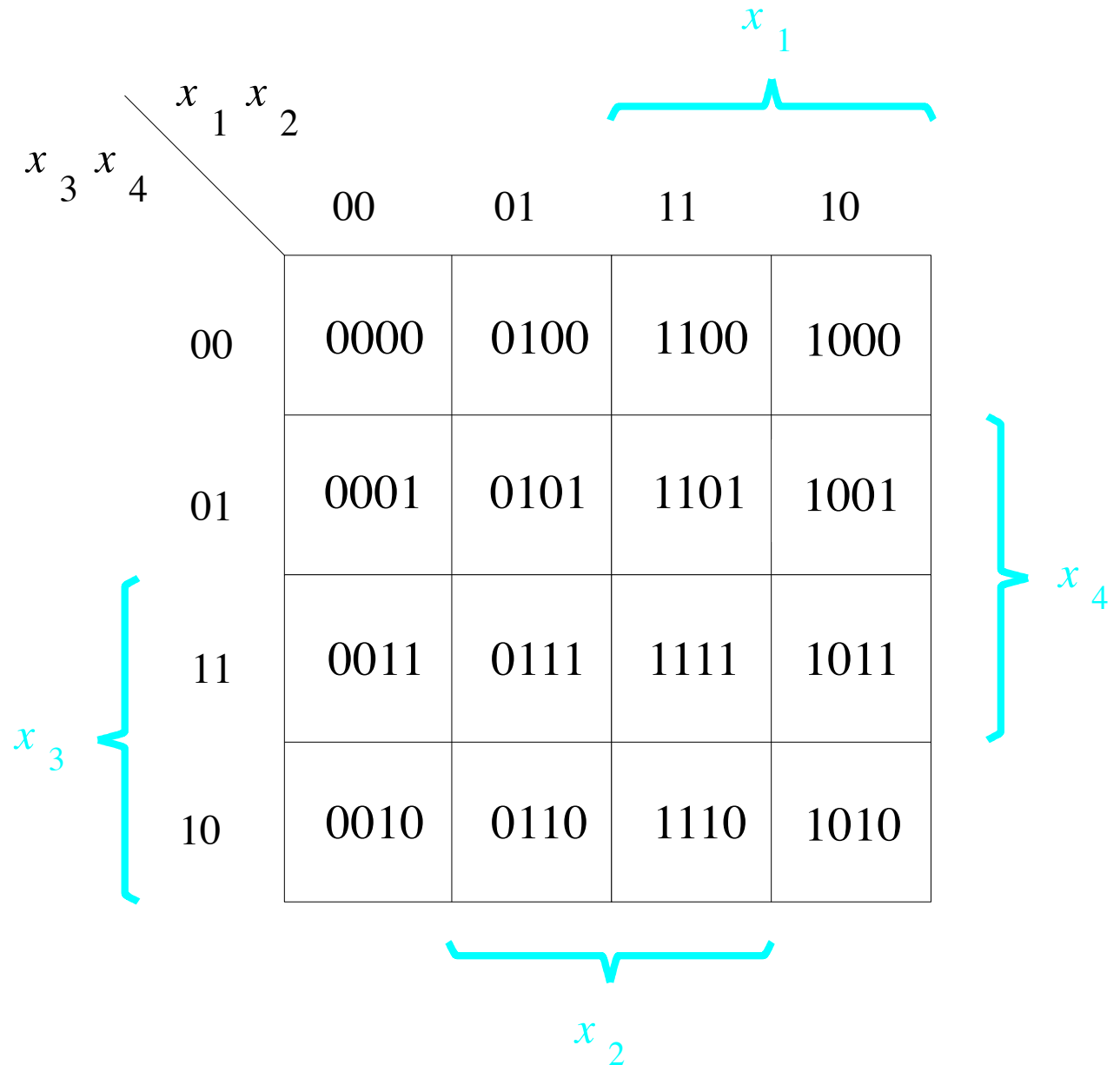

# Adjacency Rules

$x_3$ \ $x_1x_2$	00	01	11	10
0	$m_0$	$m_2$	$m_6$	$m_4$
1	$m_1$	$m_3$	$m_7$	$m_5$

adjacent  
columns

$x_3x_4$ \ $x_1x_2$	00	01	11	10
00	$m_0$	$m_4$	$m_{12}$	$m_8$
01	$m_1$	$m_5$	$m_{13}$	$m_9$
11	$m_3$	$m_7$	$m_{15}$	$m_{11}$
10	$m_2$	$m_6$	$m_{14}$	$m_{10}$

adjacent  
rows


adjacent  
columns

# Adjacency Rules

$x_3x_4 \backslash x_1x_2$	00	01	11	10
00	$m_0$	$m_4$	$m_{12}$	$m_8$
01	$m_1$	$m_5$	$m_{13}$	$m_9$
11	$m_3$	$m_7$	$m_{15}$	$m_{11}$
10	$m_2$	$m_6$	$m_{14}$	$m_{10}$

adjacent  
rows

adjacent  
columns

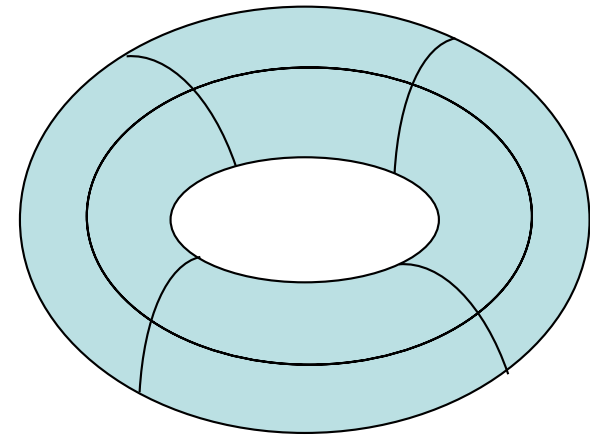


As if the K-map were  
drawn on a torus

# Adjacency Rules

$x_3x_4 \backslash x_1x_2$	00	01	11	10
00	$m_0$	$m_4$	$m_{12}$	$m_8$
01	$m_1$	$m_5$	$m_{13}$	$m_9$
11	$m_3$	$m_7$	$m_{15}$	$m_{11}$
10	$m_2$	$m_6$	$m_{14}$	$m_{10}$


adjacent  
rows

adjacent  
columns

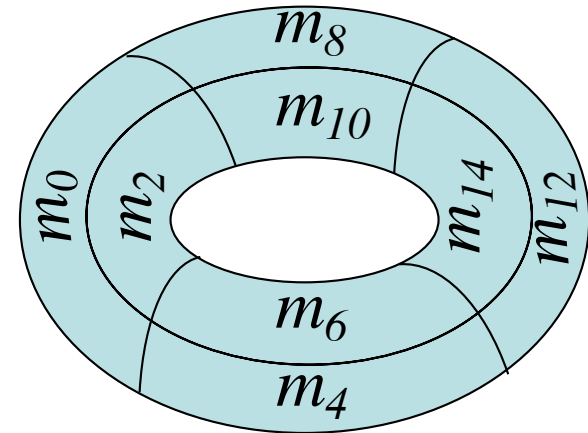

As if the K-map were  
drawn on a torus


# Example of a four-variable Karnaugh map

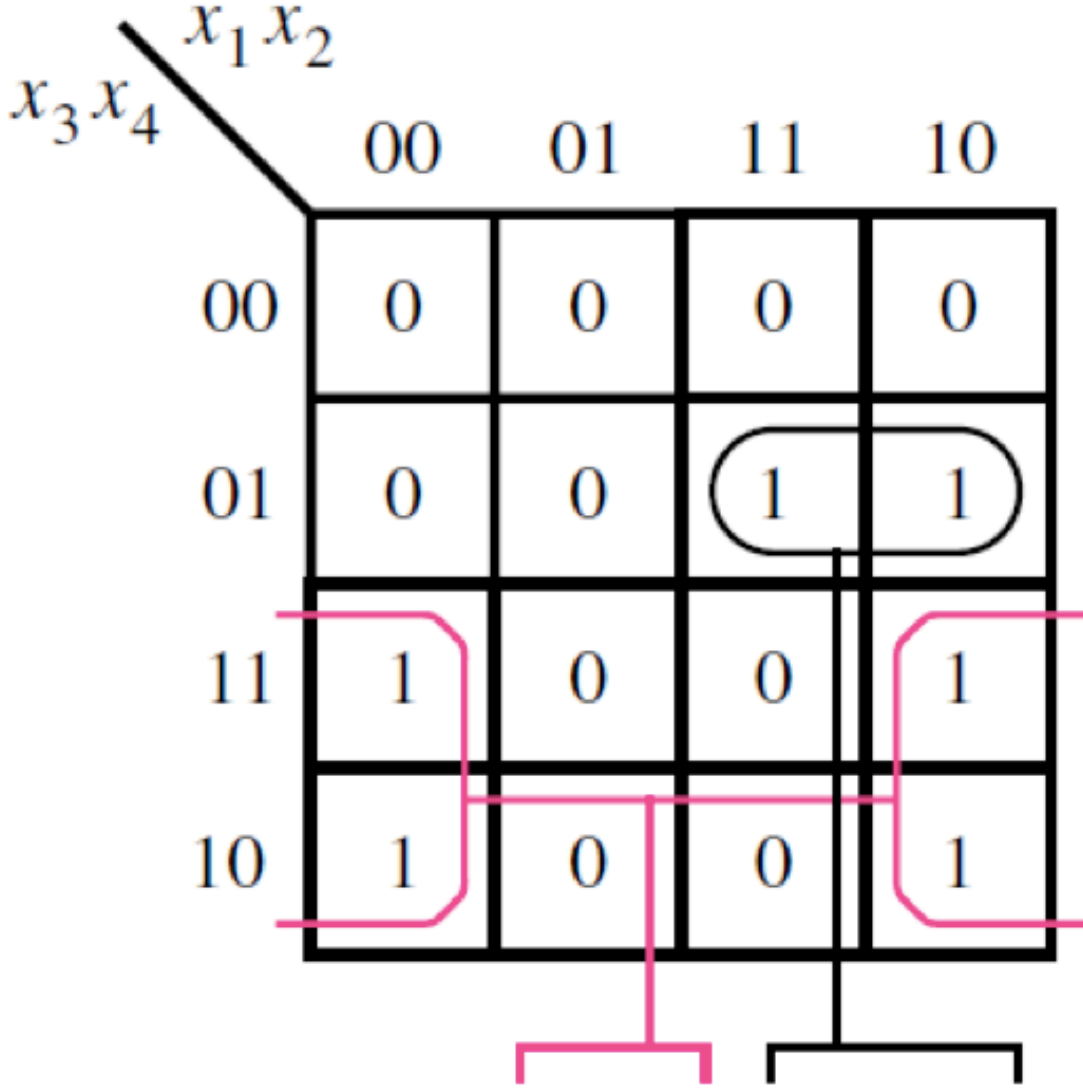

[ Figure 2.54 from the textbook ]




# Example of a four-variable Karnaugh map

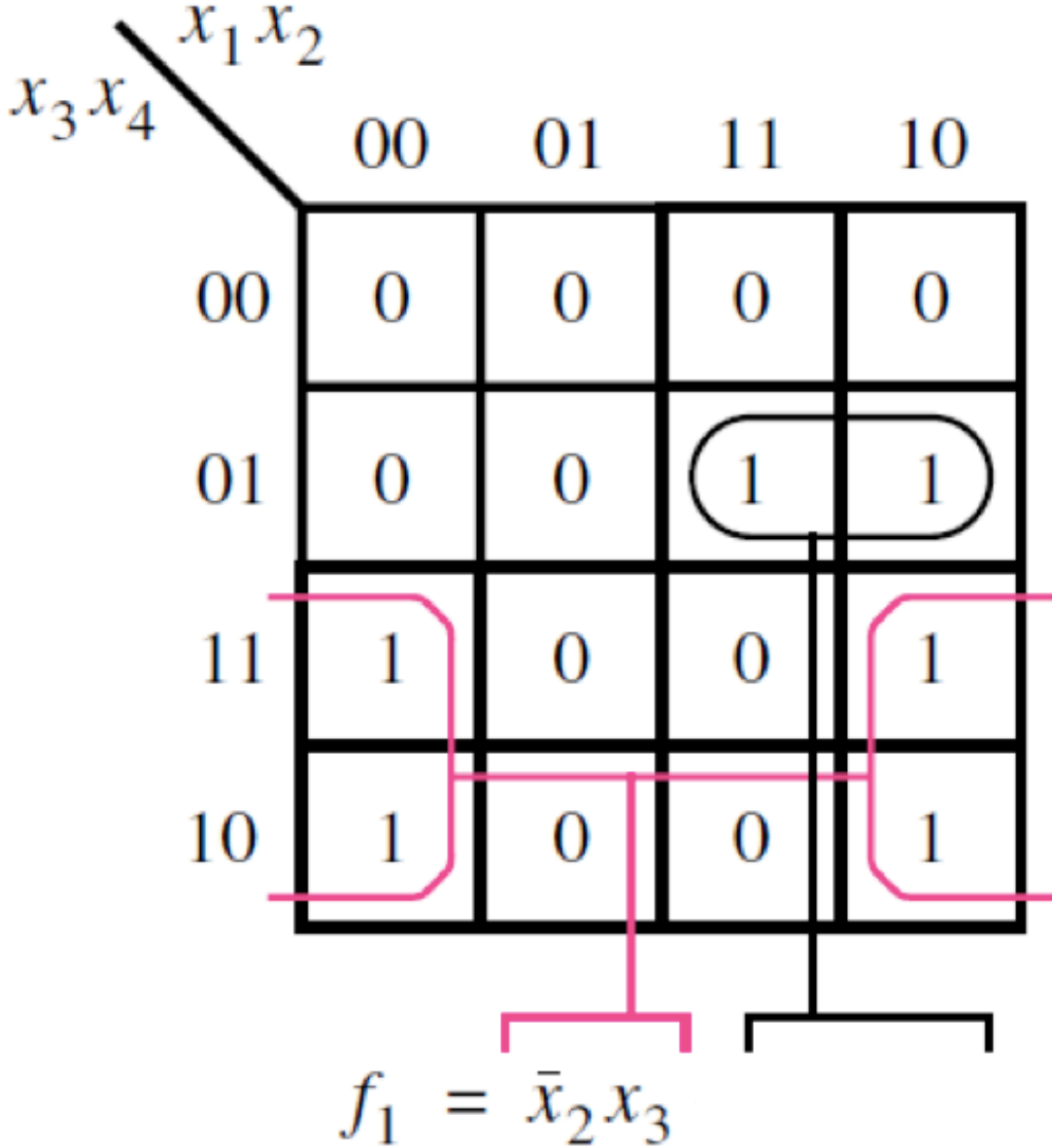


[ Figure 2.54 from the textbook ]

# Example of a four-variable Karnaugh map

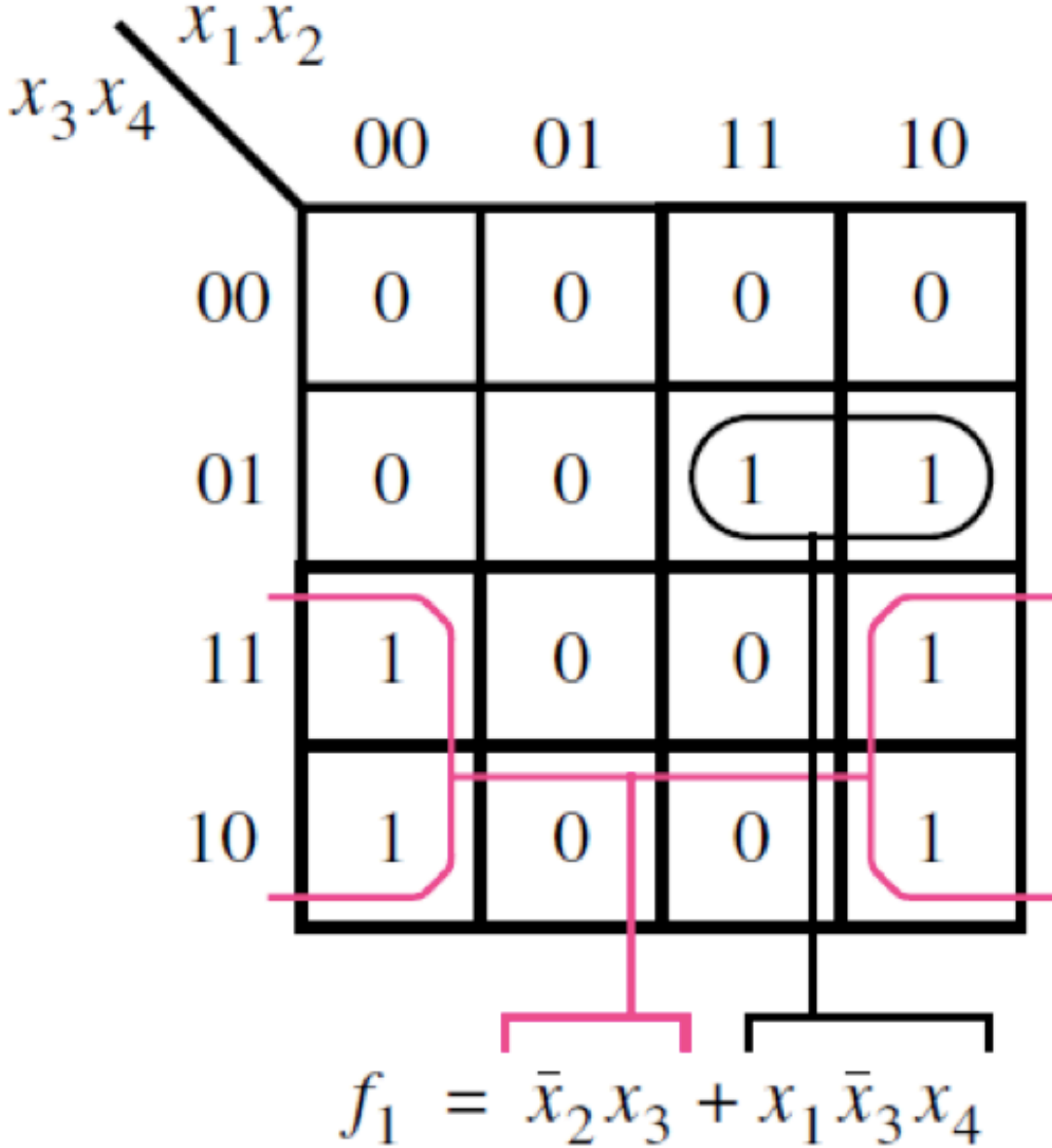


[ Figure 2.54 from the textbook ]

# Example of a four-variable Karnaugh map

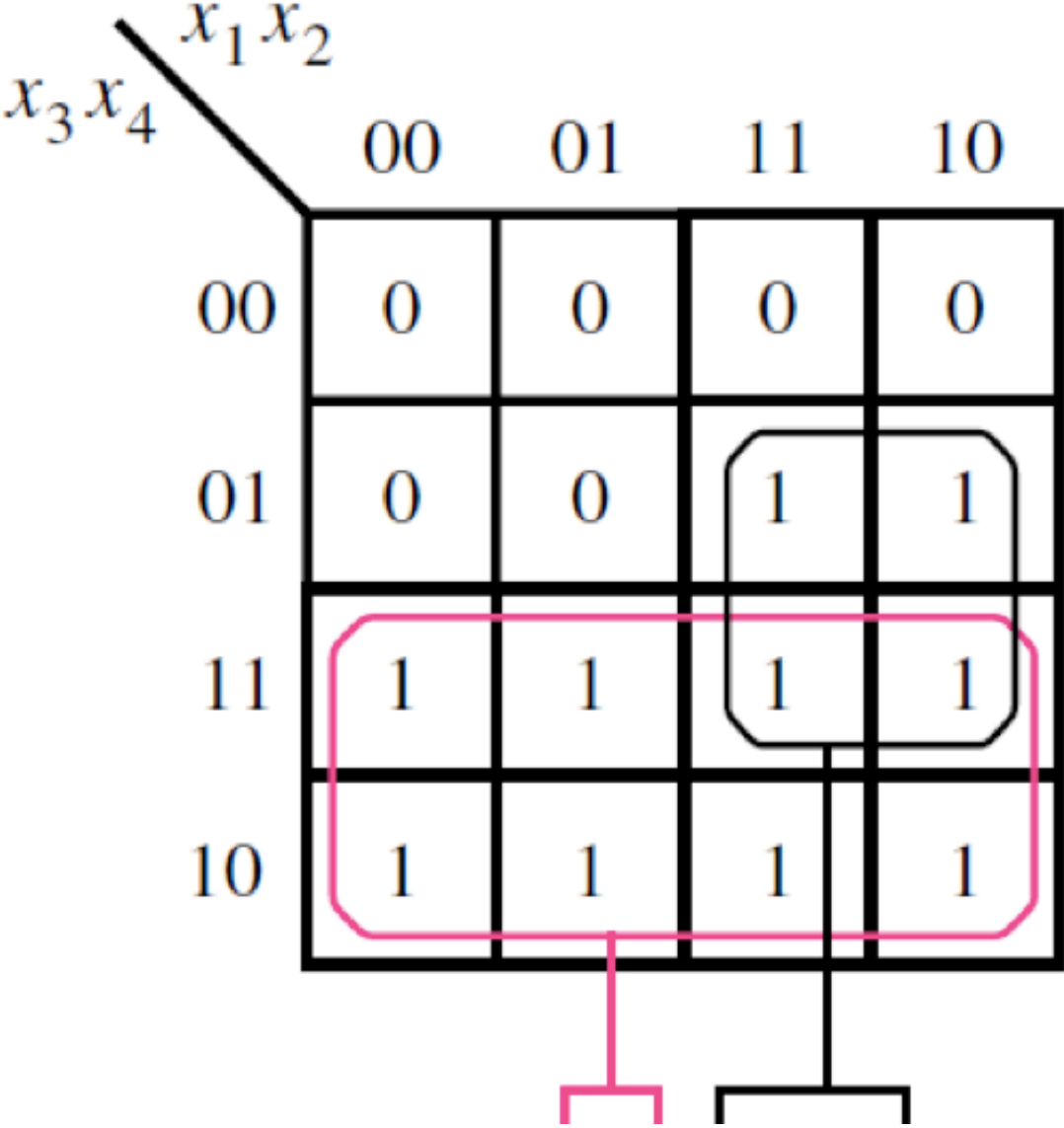


[ Figure 2.54 from the textbook ]

# Example of a four-variable Karnaugh map

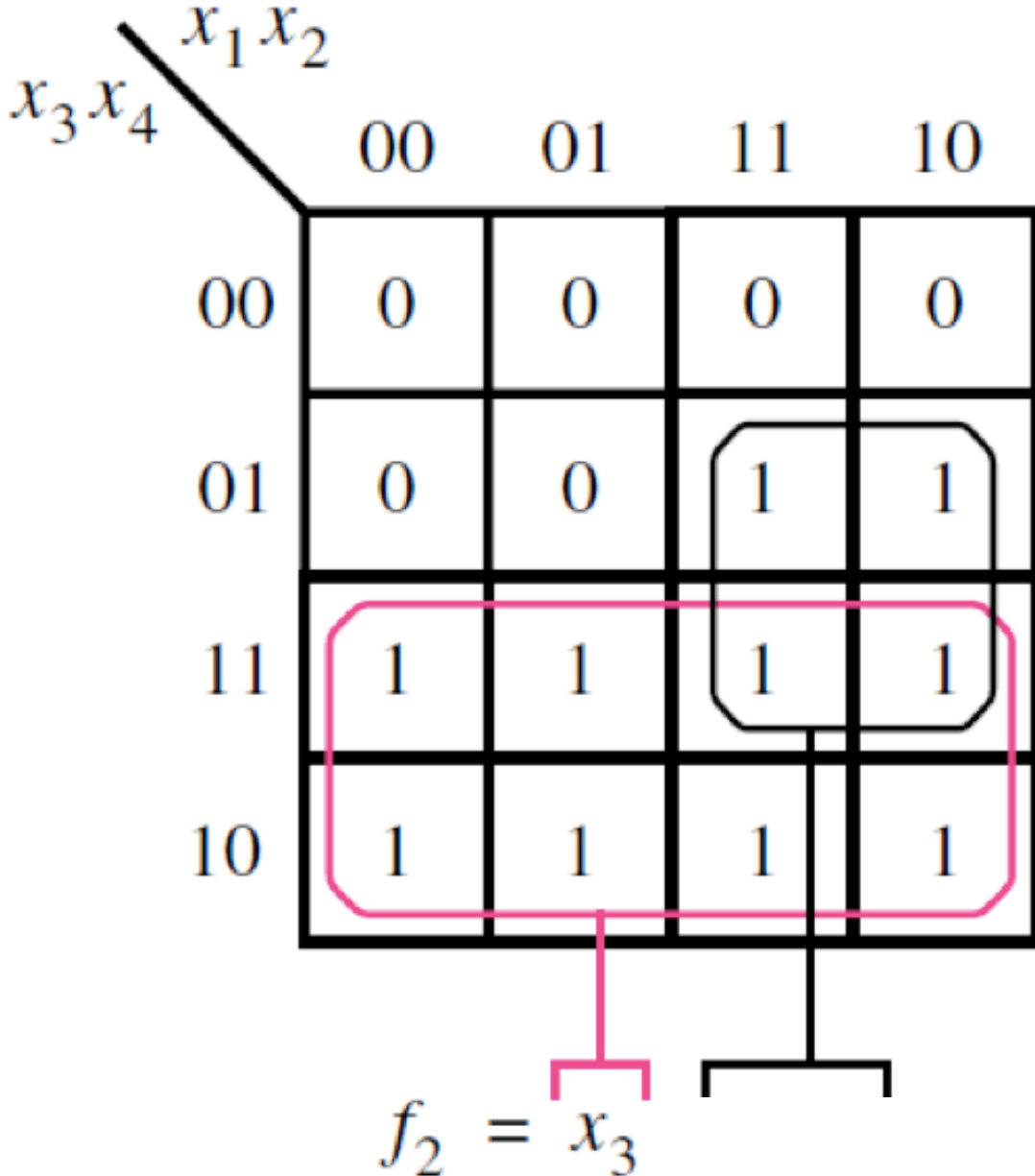





[ Figure 2.54 from the textbook ]

# Example of a four-variable Karnaugh map

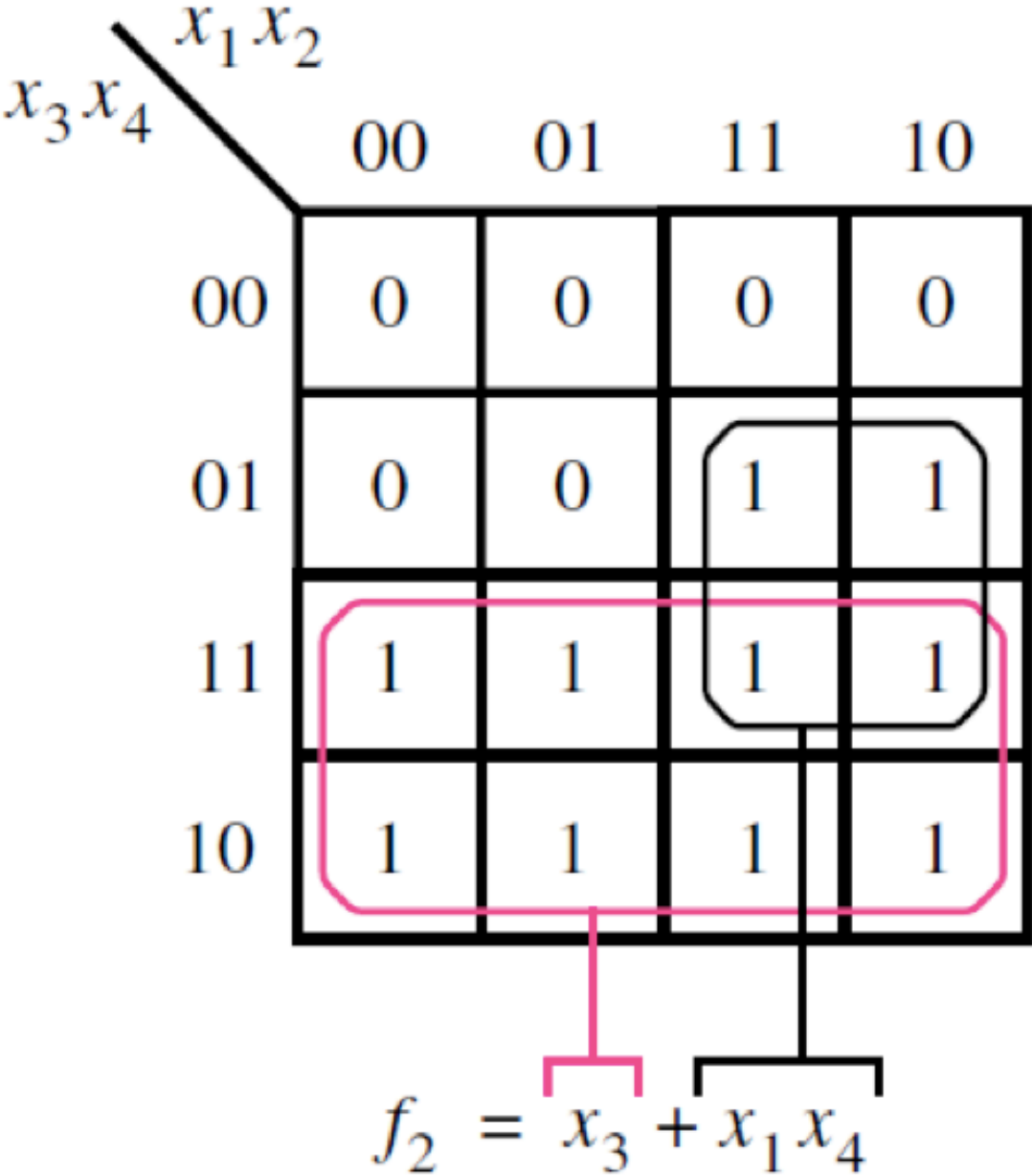

[ Figure 2.54 from the textbook ]

# Other Four-Variable K-map Examples

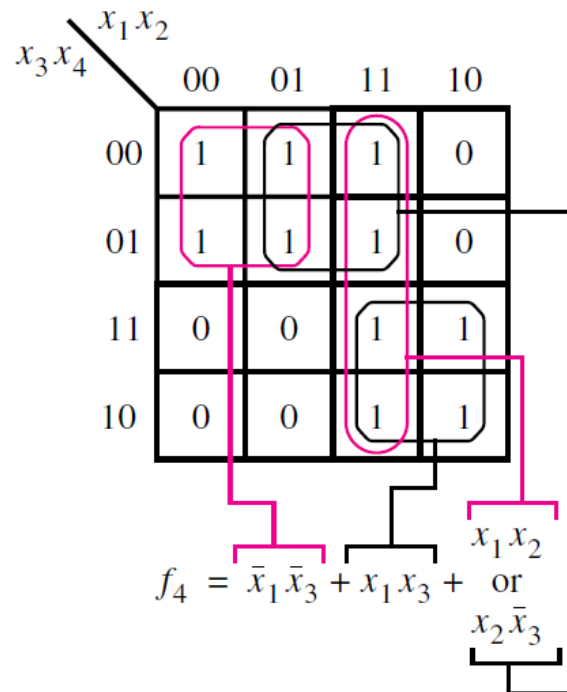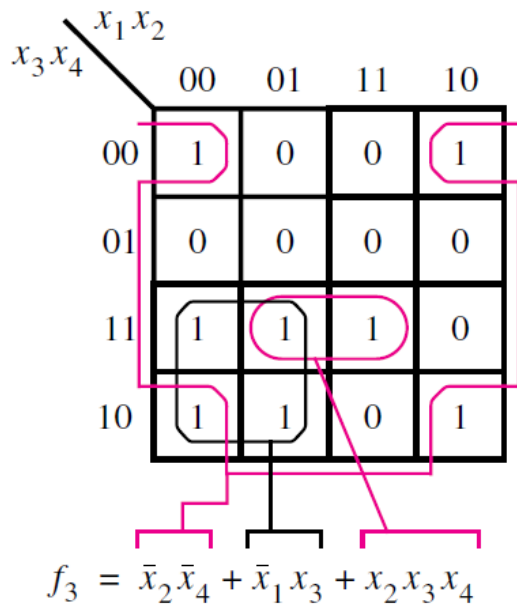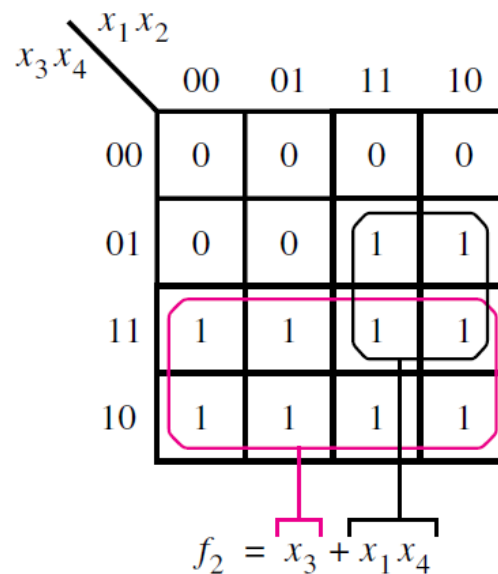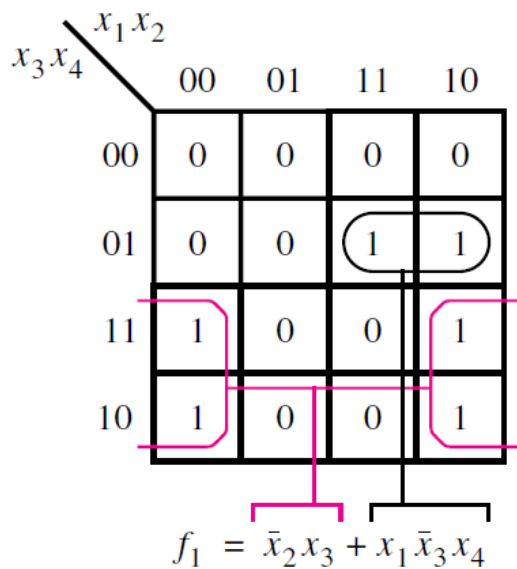

[ Figure 2.54 from the textbook ]

# **Strategy For Minimization**

# Grouping Rules

- **Group “1”s with rectangles**
- **Both sides a power of 2:**
  - **1x1, 1x2, 2x1, 2x2, 1x4, 4x1, 2x4, 4x2, 4x4**
- **Can use the same minterm more than once**
- **Can wrap around the edges of the map**
- **Some rules in selecting groups:**
  - **Try to use as few groups as possible to cover all “1”s.**
  - **For each group, try to make it as large as you can (i.e., if you can use a 2x2, don't use a 2x1 even if that is enough).**



# Terminology

**Literal: a variable, complemented or uncomplemented**

**Some Examples:**

- $\bar{X}_1$
- $X_2$

# Terminology

- **Implicant: product term that indicates the input combinations for which the function output is 1**

- **Example**

- $\bar{x}_1$  - indicates that  $\bar{x}_1\bar{x}_2$  and  $\bar{x}_1x_2$  yield output of 1

		$x_1$	
		0	1
$x_2$	0	1	0
	1	1	0

# Terminology

- **Prime Implicant**

- Implicant that cannot be combined into another implicant with fewer literals

- **Some Examples**

$x_3 \backslash x_1 x_2$	00	01	11	10
0	0	1	1	1
1	1	1	1	0

Not prime

$x_3 \backslash x_1 x_2$	00	01	11	10
0	0	1	1	1
1	1	1	1	0

Prime

# Terminology

- **Essential Prime Implicant**
  - Prime implicant that includes a minterm not covered by any other prime implicant
  - **Some Examples**

		$x_1 x_2$			
		00	01	11	10
$x_3$	0	0	1	1	1
	1	1	1	0	0

The Karnaugh map shows a 2x4 grid of cells. The columns are labeled 00, 01, 11, and 10, and the rows are labeled 0 and 1. The cells contain the following values: (0,00)=0, (0,01)=1, (0,11)=1, (0,10)=1, (1,00)=1, (1,01)=1, (1,11)=0, (1,10)=0. A blue circle highlights the 1s in the (0,01) and (1,01) cells. A red circle highlights the 1s in the (0,11) and (1,00) cells. Another red circle highlights the 1s in the (0,10) and (1,00) cells. The 1s in the (0,01) and (0,11) cells are also covered by the blue and red circles respectively.

# Terminology

- **Cover**

- **Collection of implicants that account for all possible input valuations where output is 1**

- **Ex.  $x_1' x_2 x_3 + x_1 x_2 x_3' + x_1 x_2' x_3'$**

- **Ex.  $x_1' x_2 x_3 + x_1 x_3'$**

		$x_1 x_2$			
		00	01	11	10
$x_3$	0	0	0	1	1
	1	0	1	0	0

# Example


- Give the Number of
  - Implicants?
  - Prime Implicants?
  - Essential Prime Implicants?

$x_3$ \ $x_1 x_2$	00	01	11	10
0	1	1	0	0
1	1	1	1	0

# Why concerned with minimization?

- **Simplified function**
- **Reduce the cost of the circuit**
  - **Cost: Gates + Inputs**
  - **Transistors**
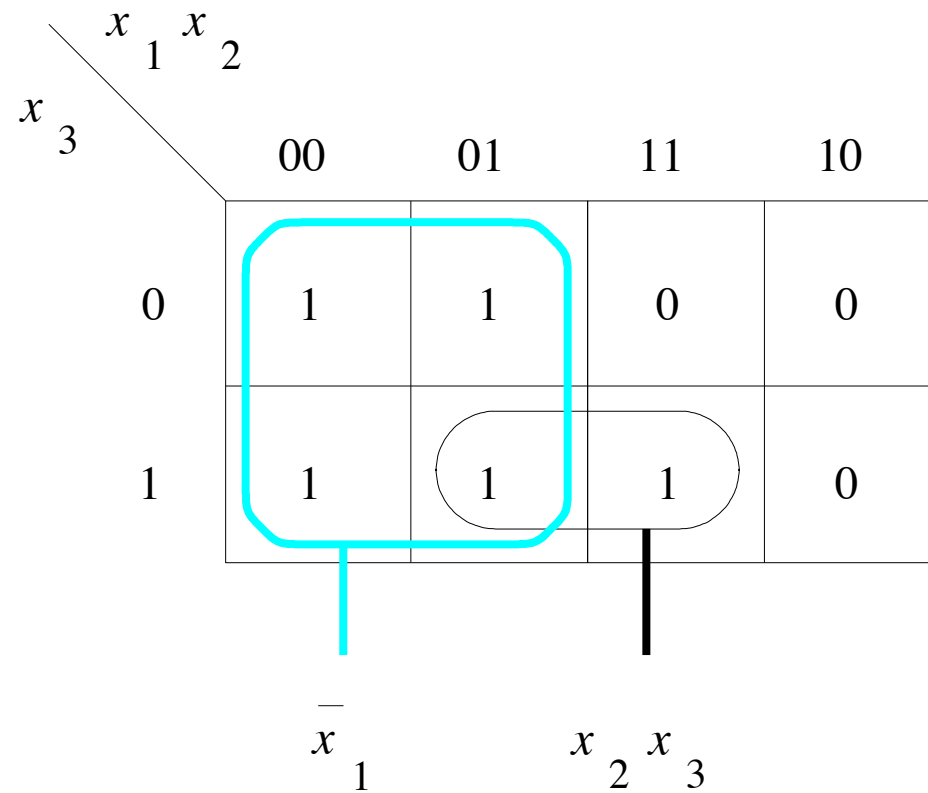
# Three-variable function $f(x_1, x_2, x_3) = \sum m(0, 1, 2, 3, 7)$







# Example

$x_3 x_4$		$x_1 x_2$			
		00	01	11	10
00	1	1			
01		1	1		
11			1	1	
10	1			1	


# Example

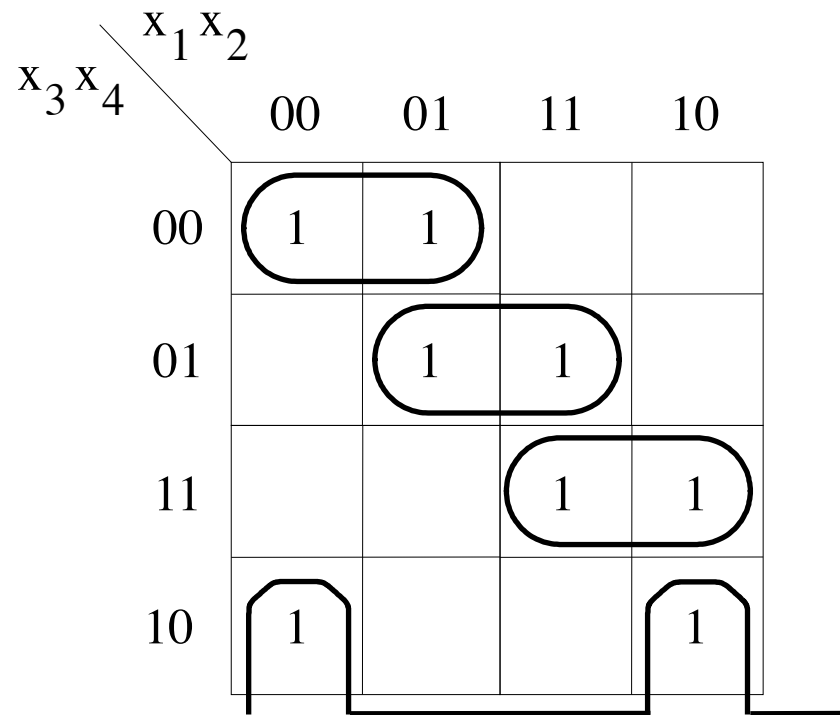

# Example

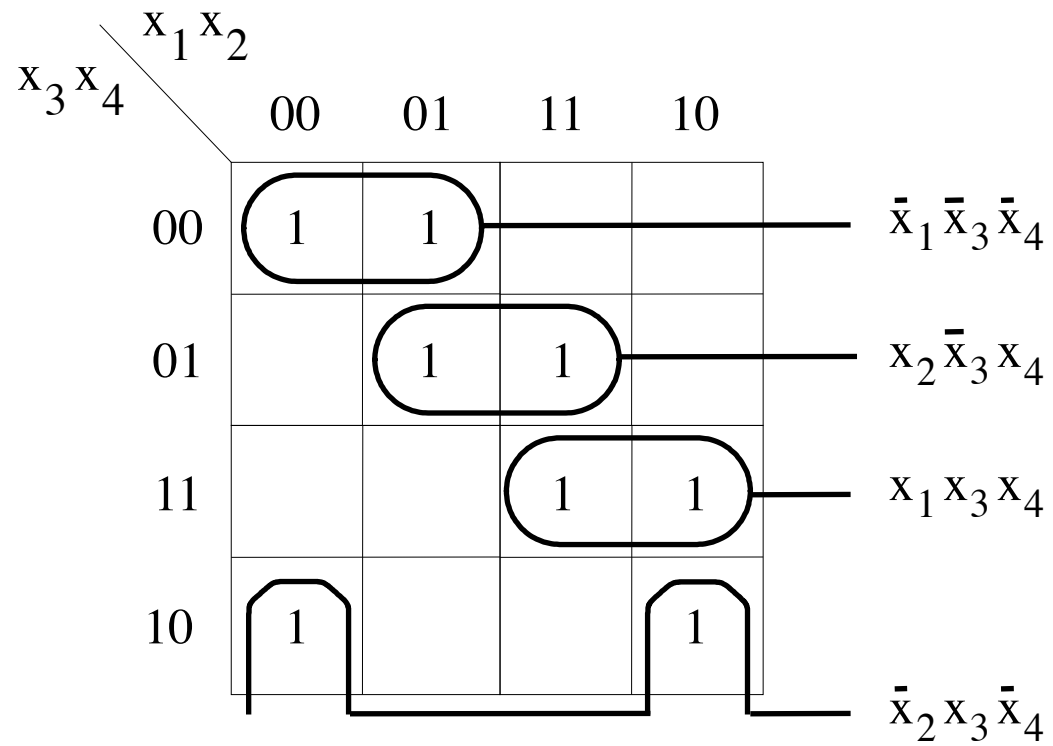

# Example

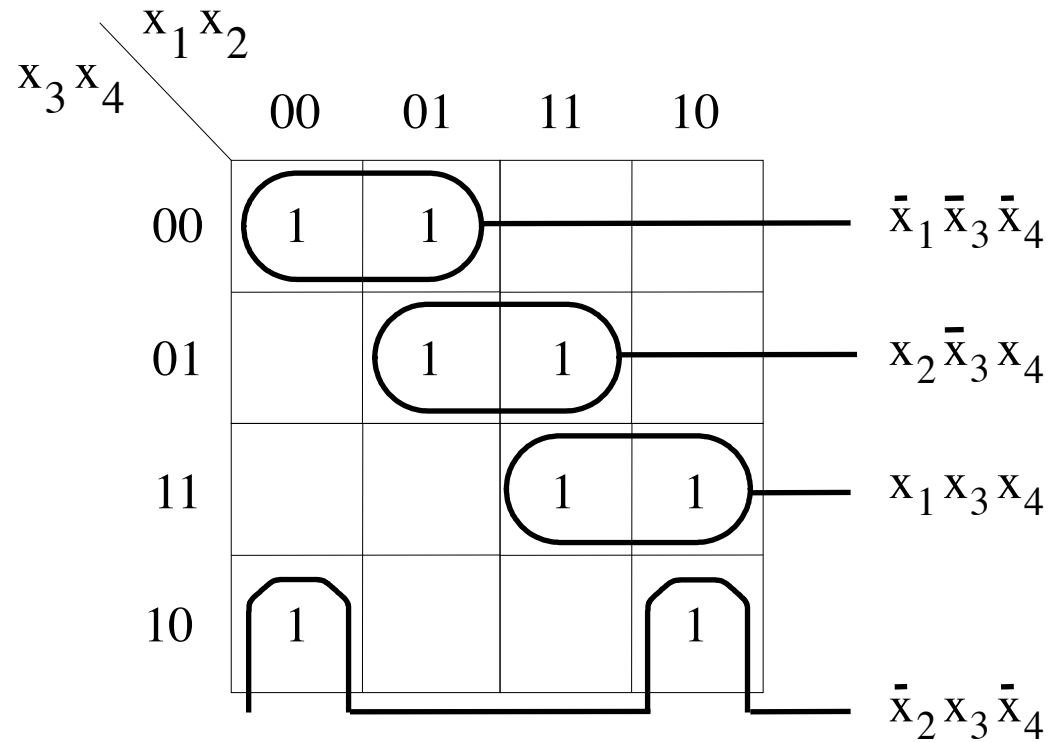


$$f = \bar{x}_1 \bar{x}_3 \bar{x}_4 + x_2 \bar{x}_3 x_4 + x_1 x_3 x_4 + \bar{x}_2 x_3 \bar{x}_4$$


# Example: Another Solution

$x_3 x_4$		$x_1 x_2$			
		00	01	11	10
00	1	1			
01		1	1		
11			1	1	
10	1			1	


# Example: Another Solution

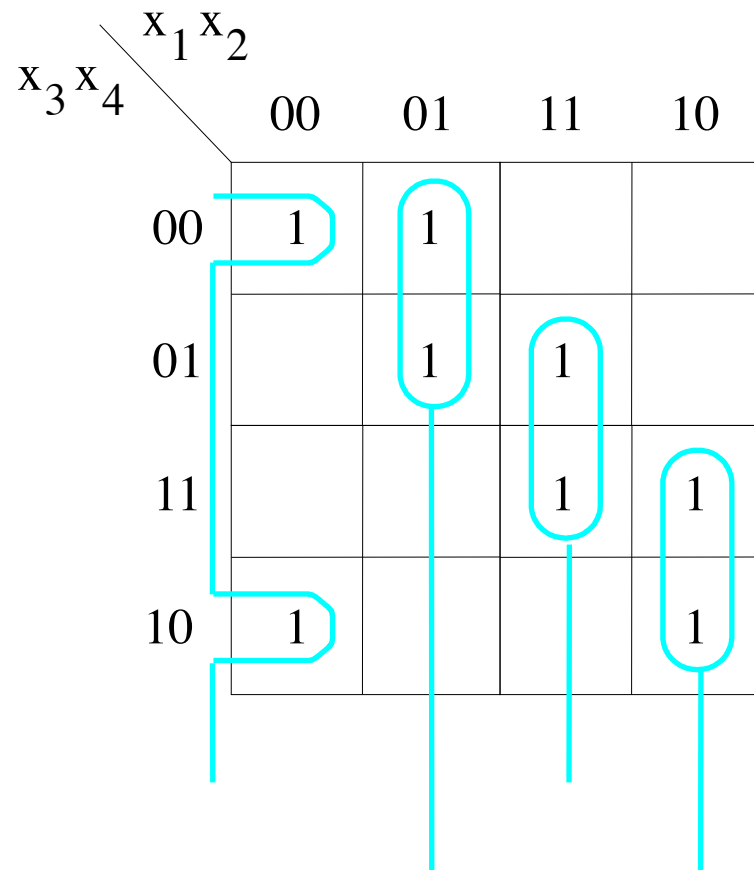

# Example: Another Solution

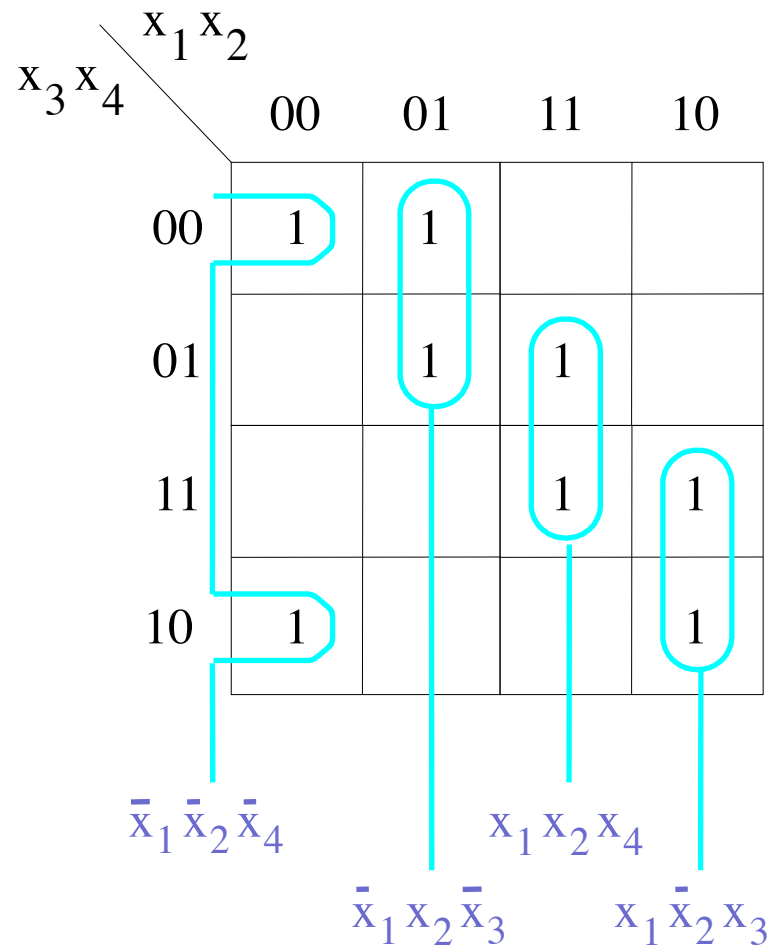


# Example: Another Solution

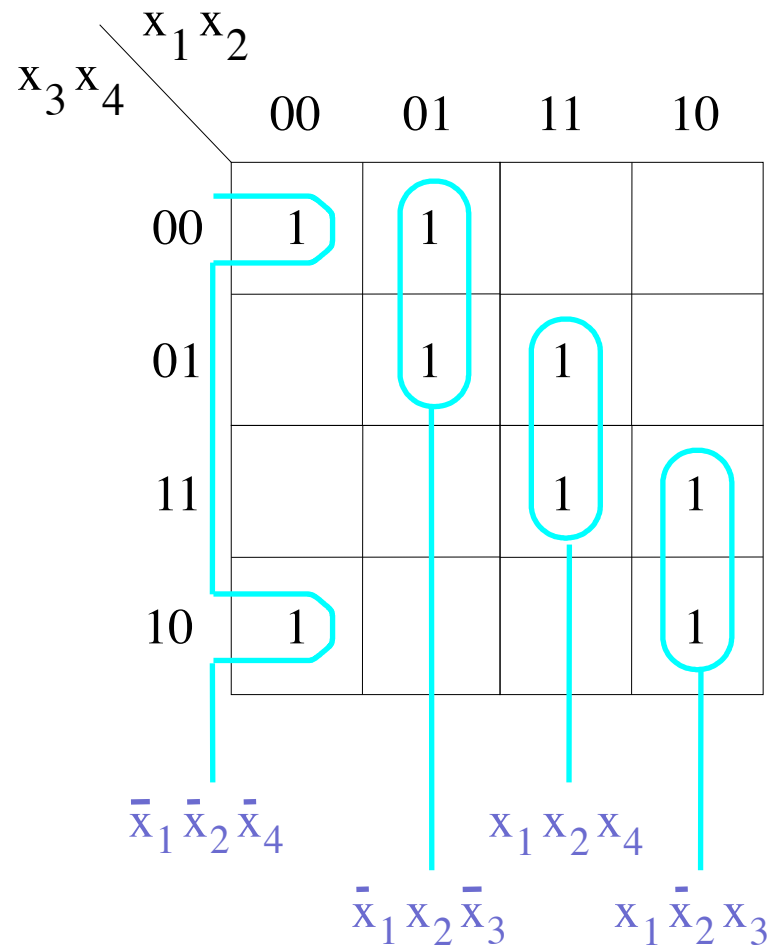


$$f = \bar{x}_1 \bar{x}_2 \bar{x}_4 + \bar{x}_1 x_2 \bar{x}_3 + x_1 x_2 x_4 + x_1 \bar{x}_2 x_3$$



# Example: Both Are Valid Solutions

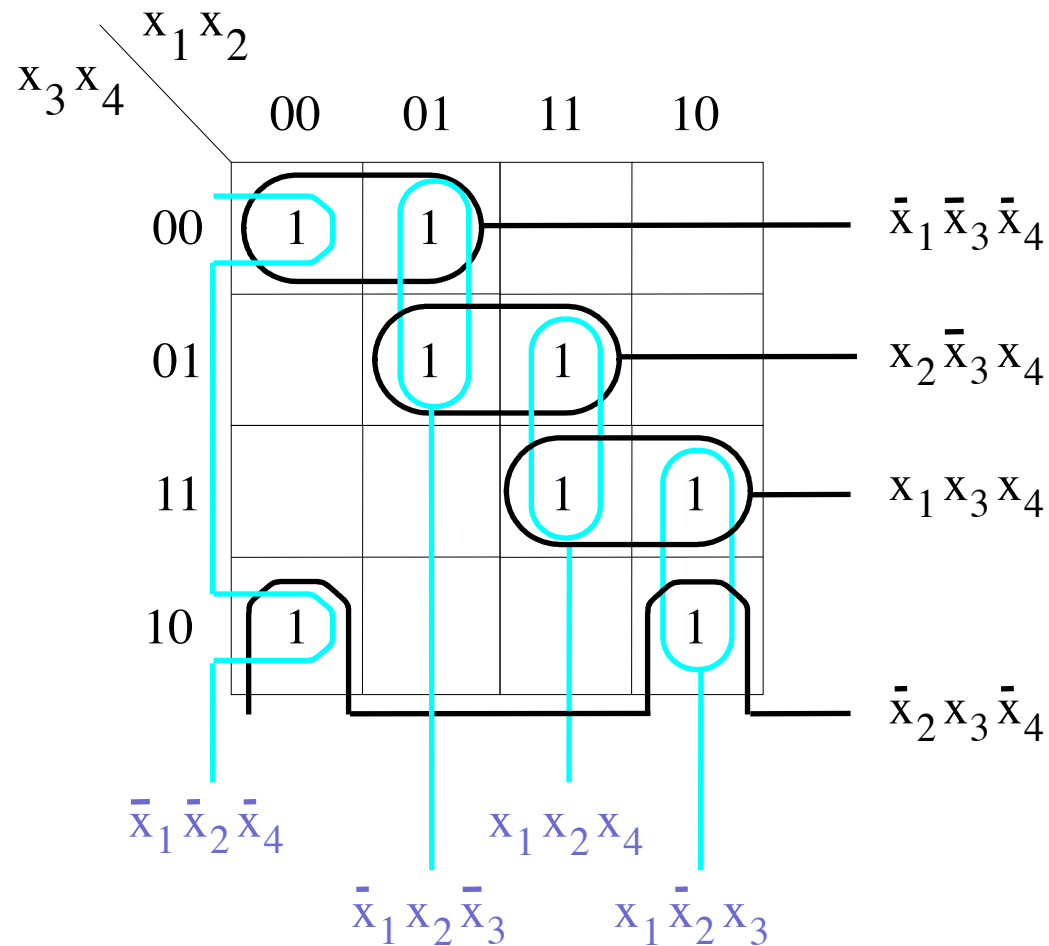

# Example: Both Are Valid Solutions

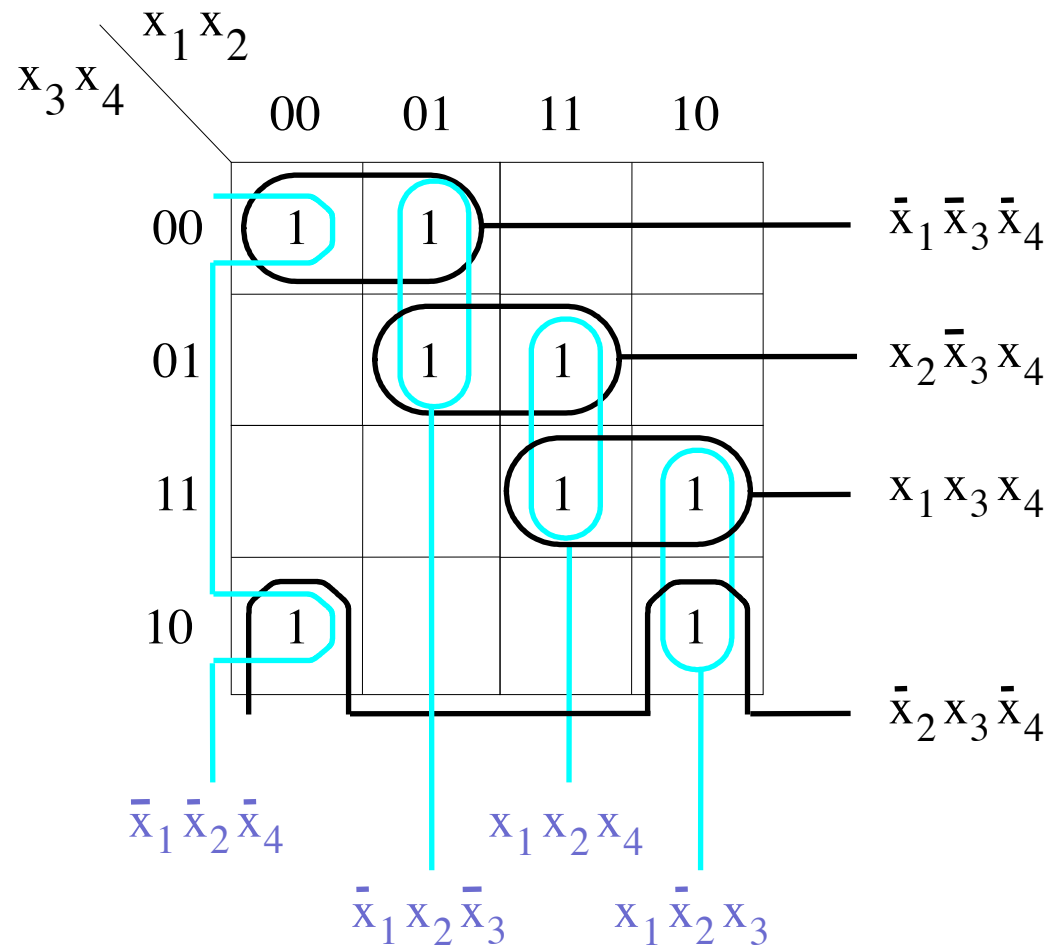

$$f = \bar{x}_1 \bar{x}_3 \bar{x}_4 + x_2 \bar{x}_3 x_4 + x_1 x_3 x_4 + \bar{x}_2 x_3 \bar{x}_4$$


$$f = \bar{x}_1 \bar{x}_2 \bar{x}_4 + \bar{x}_1 x_2 \bar{x}_3 + x_1 x_2 x_4 + x_1 \bar{x}_2 x_3$$

**Example:**  
**Incompletely Specified Function**

# Three Ways to Specify the Function

$$f(x_1, x_2, x_3, x_4) = \Sigma m(2, 4, 5, 6, 10) + D(12, 13, 14, 15)$$

$x_1$	$x_2$	$x_3$	$x_4$	$f$
0	0	0	0	$m_0$
0	0	0	1	$m_1$
0	0	1	0	$m_2$
0	0	1	1	$m_3$
0	1	0	0	$m_4$
0	1	0	1	$m_5$
0	1	1	0	$m_6$
0	1	1	1	$m_7$
1	0	0	0	$m_8$
1	0	0	1	$m_9$
1	0	1	0	$m_{10}$
1	0	1	1	$m_{11}$
1	1	0	0	$m_{12}$
1	1	0	1	$m_{13}$
1	1	1	0	$m_{14}$
1	1	1	1	$m_{15}$

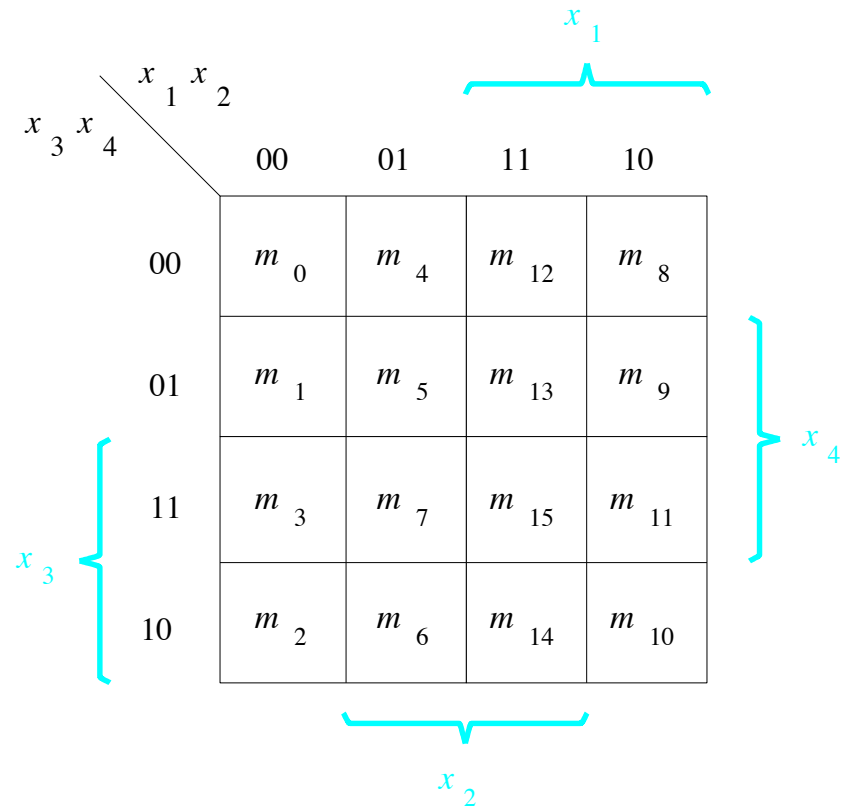

# Three Ways to Specify the Function

$$f(x_1, x_2, x_3, x_4) = \Sigma m(2, 4, 5, 6, 10) + D(12, 13, 14, 15)$$

$x_1$	$x_2$	$x_3$	$x_4$	$f$
0	0	0	0	$m_0$
0	0	0	1	$m_1$
0	0	1	0	$m_2$
0	0	1	1	$m_3$
0	1	0	0	$m_4$
0	1	0	1	$m_5$
0	1	1	0	$m_6$
0	1	1	1	$m_7$
1	0	0	0	$m_8$
1	0	0	1	$m_9$
1	0	1	0	$m_{10}$
1	0	1	1	$m_{11}$
1	1	0	0	$m_{12}$
1	1	0	1	$m_{13}$
1	1	1	0	$m_{14}$
1	1	1	1	$m_{15}$

		$x_1 x_2$			
		00	01	11	10
$x_3 x_4$	00	0	1	d	0
	01	0	1	d	0
	11	0	0	d	0
	10	1	1	d	1

# SOP implementation

A Karnaugh map for a 4-variable function with variables  $x_1, x_2, x_3, x_4$ . The horizontal axis is labeled  $x_1 x_2$  with values 00, 01, 11, 10. The vertical axis is labeled  $x_3 x_4$  with values 00, 01, 11, 10. The map contains 1s in cells (01,00), (01,01), (10,00), (10,01), and (10,10). Don't care cells (d) are in (11,00), (11,01), and (11,10). Two prime implicants are circled in cyan: a vertical one covering (01,00) and (01,01) labeled  $x_2 \bar{x}_3$ , and a horizontal one covering (10,00), (10,01), and (10,10) labeled  $x_3 \bar{x}_4$ .

$x_3 x_4 \backslash x_1 x_2$	00	01	11	10
00	0	1	d	0
01	0	1	d	0
11	0	0	d	0
10	1	1	d	1

(a) SOP implementation

# POS implementation

		$x_1 x_2$			
		00	01	11	10
$x_3 x_4$	00	0	1	d	0
	01	0	1	d	0
	11	0	0	d	0
	10	1	1	d	1

$(x_2 + x_3)$


$(\bar{x}_3 + \bar{x}_4)$

(b) POS implementation

**Example:**  
**A circuit with multiple outputs**




# Seven-Segment Indicator

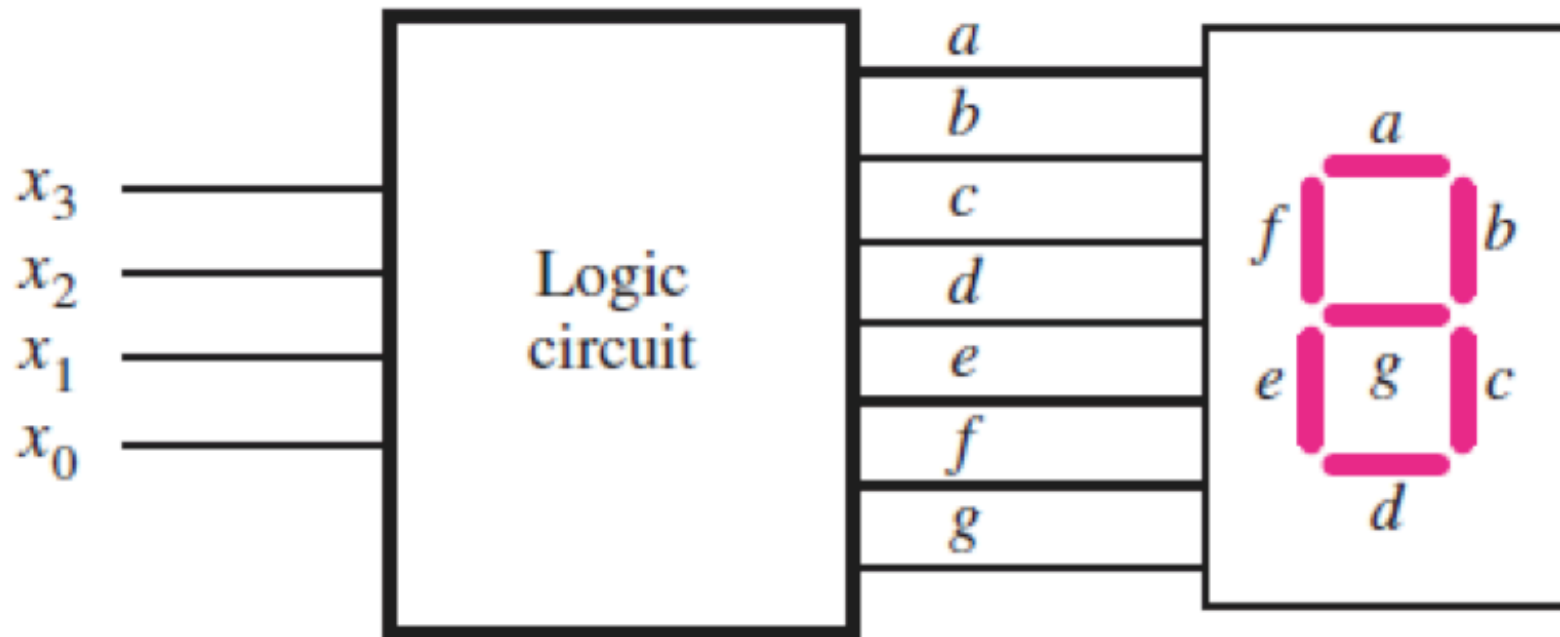

(a) Logic circuit and 7-segment display

# Seven-Segment Indicator

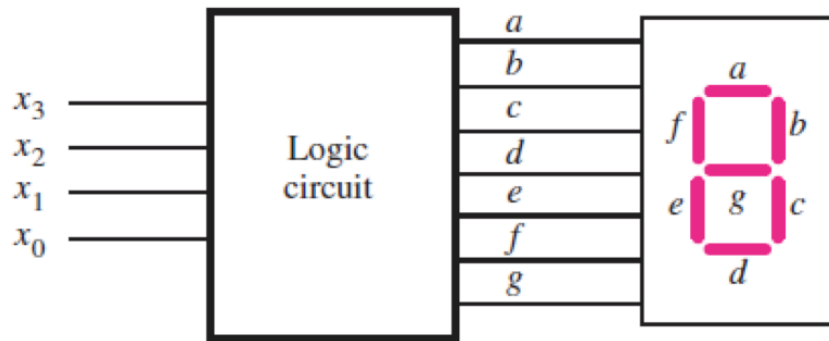

(a) Logic circuit and 7-segment display

	$x_3$	$x_2$	$x_1$	$x_0$	$a$	$b$	$c$	$d$	$e$	$f$	$g$
0	0	0	0	0	1	1	1	1	1	1	0
1	0	0	0	1	0	1	1	0	0	0	0
2	0	0	1	0	1	1	0	1	1	0	1
3	0	0	1	1	1	1	1	1	0	0	1
4	0	1	0	0	0	1	1	0	0	1	1
5	0	1	0	1	1	0	1	1	0	1	1
6	0	1	1	0	1	0	1	1	1	1	1
7	0	1	1	1	1	1	1	0	0	0	0
8	1	0	0	0	1	1	1	1	1	1	1
9	1	0	0	1	1	1	1	1	0	1	1

(b) Truth table

# Seven-Segment Indicator

	$x_3$	$x_2$	$x_1$	$x_0$	$a$	$b$	$c$	$d$	$e$	$f$	$g$
0000	0	0	0	0	1	1	1	1	1	1	0
0001	0	0	0	1	0	1	1	0	0	0	0
0010	0	0	1	0	1	1	0	1	1	0	1
0011	0	0	1	1	1	1	1	1	0	0	1
0100	0	1	0	0	0	1	1	0	0	1	1
0101	0	1	0	1	1	0	1	1	0	1	1
0110	0	1	1	0	1	0	1	1	1	1	1
0111	0	1	1	1	1	1	1	0	0	0	0
1000	1	0	0	0	1	1	1	1	1	1	1
1001	1	0	0	1	1	1	1	1	0	1	1
1010	1	0	1	0							
1011	1	0	1	1							
1100	1	1	0	0							
1101	1	1	0	1							
1110	1	1	1	0							
1111	1	1	1	1							

# Seven-Segment Indicator



	$x_3$	$x_2$	$x_1$	$x_0$	$a$	$b$	$c$	$d$	$e$	$f$	$g$
0	0	0	0	0	1	1	1	1	1	1	0
1	0	0	0	1	0	1	1	0	0	0	0
2	0	0	1	0	1	1	0	1	1	0	1
3	0	0	1	1	1	1	1	1	0	0	1
4	0	1	0	0	0	1	1	0	0	1	1
5	0	1	0	1	1	0	1	1	0	1	1
6	0	1	1	0	1	0	1	1	1	1	1
7	0	1	1	1	1	1	1	0	0	0	0
8	1	0	0	0	1	1	1	1	1	1	1
9	1	0	0	1	1	1	1	1	0	1	1
d	1	0	1	0	d	d	d	d	d	d	d
d	1	0	1	1	d	d	d	d	d	d	d
d	1	1	0	0	d	d	d	d	d	d	d
d	1	1	0	1	d	d	d	d	d	d	d
d	1	1	1	0	d	d	d	d	d	d	d
d	1	1	1	1	d	d	d	d	d	d	d

# Seven-Segment Indicator

	$x_3$	$x_2$	$x_1$	$x_0$	<i>a</i>	<i>b</i>	<i>c</i>	<i>d</i>	<i>e</i>	<i>f</i>	<i>g</i>
0000	0	0	0	0	1	1	1	1	1	1	0
0001	0	0	0	1	0	1	1	0	0	0	0
0010	0	0	1	0	1	1	0	1	1	0	1
0011	0	0	1	1	1	1	1	1	0	0	1
0100	0	1	0	0	0	1	1	0	0	1	1
0101	0	1	0	1	1	0	1	1	0	1	1
0110	0	1	1	0	1	0	1	1	1	1	1
0111	0	1	1	1	1	1	1	0	0	0	0
1000	1	0	0	0	1	1	1	1	1	1	1
1001	1	0	0	1	1	1	1	1	0	1	1
1010	1	0	1	0	d	d	d	d	d	d	d
1011	1	0	1	1	d	d	d	d	d	d	d
1100	1	1	0	0	d	d	d	d	d	d	d
1101	1	1	0	1	d	d	d	d	d	d	d
1110	1	1	1	0	d	d	d	d	d	d	d
1111	1	1	1	1	d	d	d	d	d	d	d



# Seven-Segment Indicator

	$x_3$	$x_2$	$x_1$	$x_0$	<i>a</i>	<i>b</i>	<i>c</i>	<i>d</i>	<i>e</i>	<i>f</i>	<i>g</i>
0000	0	0	0	0	1	1	1	1	1	1	0
0001	0	0	0	1	0	1	1	0	0	0	0
0010	0	0	1	0	1	1	0	1	1	0	1
0011	0	0	1	1	1	1	1	1	0	0	1
0100	0	1	0	0	0	1	1	0	0	1	1
0101	0	1	0	1	1	0	1	1	0	1	1
0110	0	1	1	0	1	0	1	1	1	1	1
0111	0	1	1	1	1	1	1	0	0	0	0
1000	1	0	0	0	1	1	1	1	1	1	1
1001	1	0	0	1	1	1	1	1	0	1	1
1010	1	0	1	0	d	d	d	d	d	d	d
1011	1	0	1	1	d	d	d	d	d	d	d
1100	1	1	0	0	d	d	d	d	d	d	d
1101	1	1	0	1	d	d	d	d	d	d	d
1110	1	1	1	0	d	d	d	d	d	d	d
1111	1	1	1	1	d	d	d	d	d	d	d

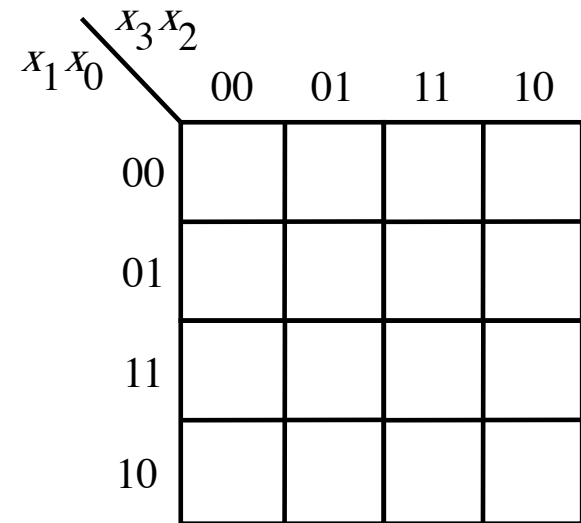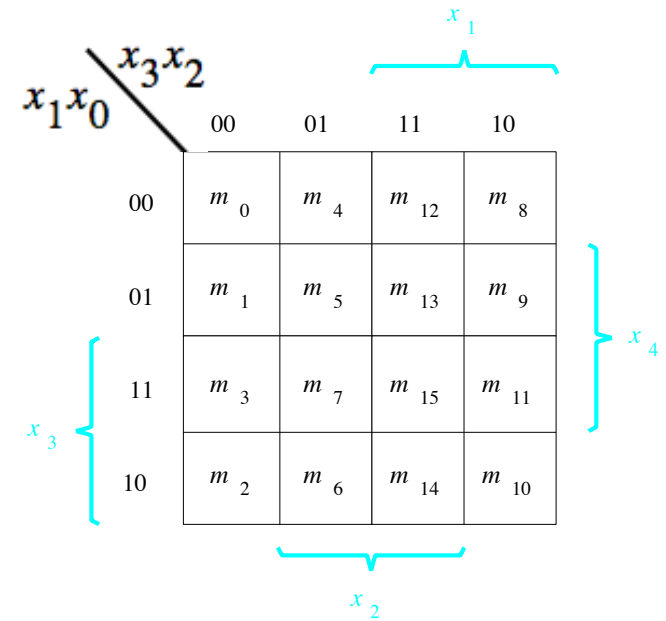



# Seven-Segment Indicator

	$x_3$	$x_2$	$x_1$	$x_0$	<i>a</i>	<i>b</i>	<i>c</i>	<i>d</i>	<i>e</i>	<i>f</i>	<i>g</i>
0	0	0	0	0	1	1	1	1	1	1	0
0	0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	1	0	0	1
0	1	0	0	0	0	1	1	0	0	1	1
0	1	0	1	1	1	0	1	1	0	1	1
0	1	1	0	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	1	0	0	0	0
1	0	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	1	0	1	1
1	0	1	0	0	d	d	d	d	d	d	d
1	0	1	1	1	d	d	d	d	d	d	d
1	1	0	0	0	d	d	d	d	d	d	d
1	1	0	1	1	d	d	d	d	d	d	d
1	1	1	0	0	d	d	d	d	d	d	d
1	1	1	1	1	d	d	d	d	d	d	d

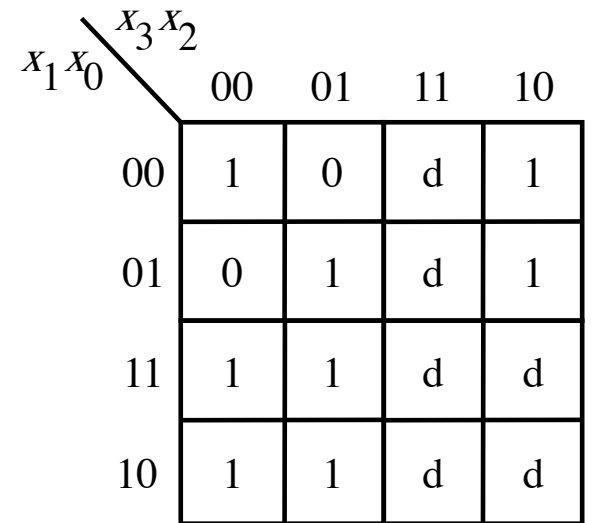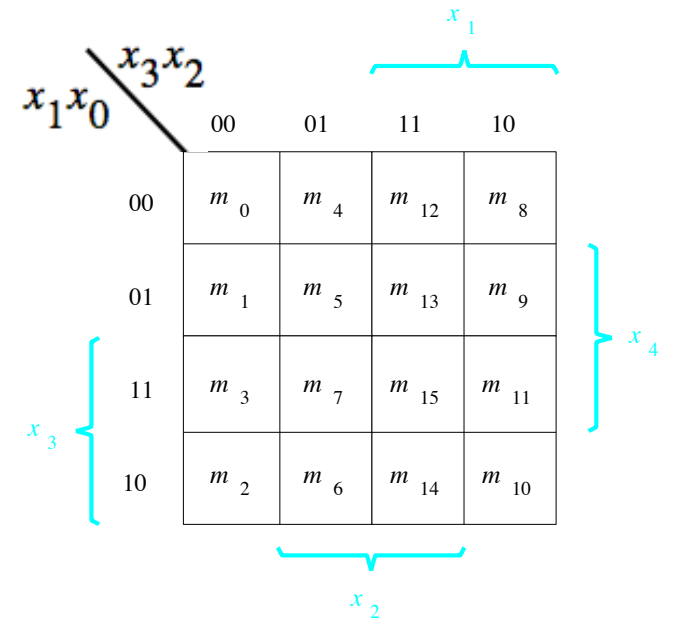

# Seven-Segment Indicator



$x_3$	$x_2$	$x_1$	$x_0$	$a$	$b$	$c$	$d$	$e$	$f$	$g$
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1
1	0	1	0	d	d	d	d	d	d	d
1	0	1	1	d	d	d	d	d	d	d
1	1	0	0	d	d	d	d	d	d	d
1	1	0	1	d	d	d	d	d	d	d
1	1	1	0	d	d	d	d	d	d	d
1	1	1	1	d	d	d	d	d	d	d

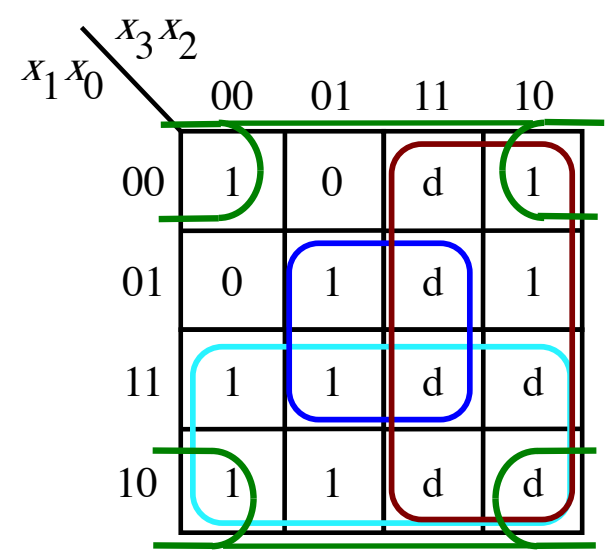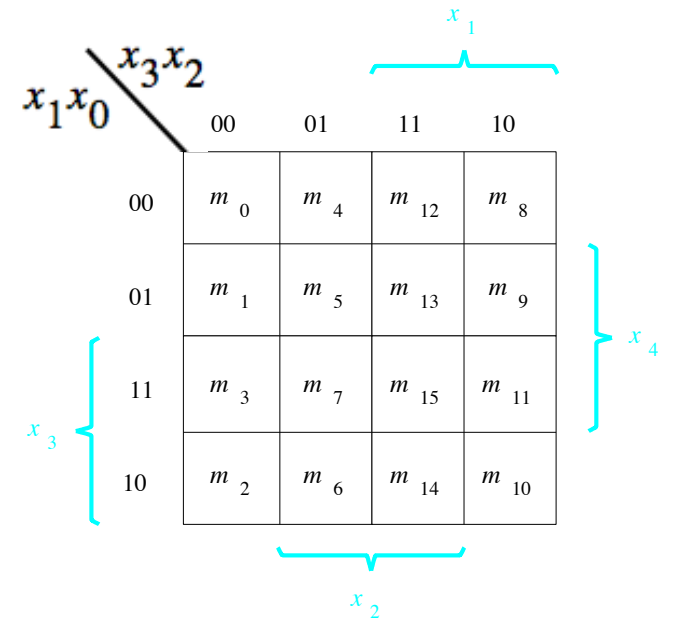



# Seven-Segment Indicator

	$x_3$	$x_2$	$x_1$	$x_0$	$a$	$b$	$c$	$d$	$e$	$f$	$g$
0000	0	0	0	0	1	1	1	1	1	1	0
0001	0	0	0	1	0	1	1	0	0	0	0
0010	0	0	1	0	1	1	0	1	1	0	1
0011	0	0	1	1	1	1	1	1	0	0	1
0100	0	1	0	0	0	1	1	0	0	1	1
0101	0	1	0	1	1	0	1	1	0	1	1
0110	0	1	1	0	1	0	1	1	1	1	1
0111	0	1	1	1	1	1	1	0	0	0	0
1000	1	0	0	0	1	1	1	1	1	1	1
1001	1	0	0	1	1	1	1	1	0	1	1
1010	1	0	1	0	1	d	d	d	d	d	d
1011	1	0	1	1	1	d	d	d	d	d	d
1100	1	1	0	0	1	d	d	d	d	d	d
1101	1	1	0	1	1	d	d	d	d	d	d
1110	1	1	1	0	1	d	d	d	d	d	d
1111	1	1	1	1	1	d	d	d	d	d	d

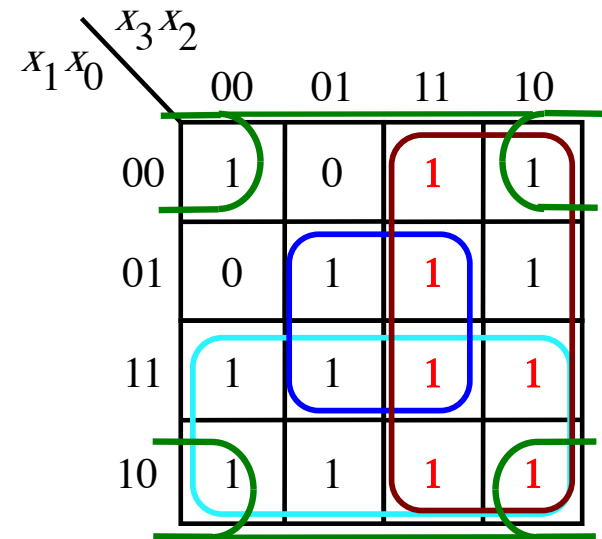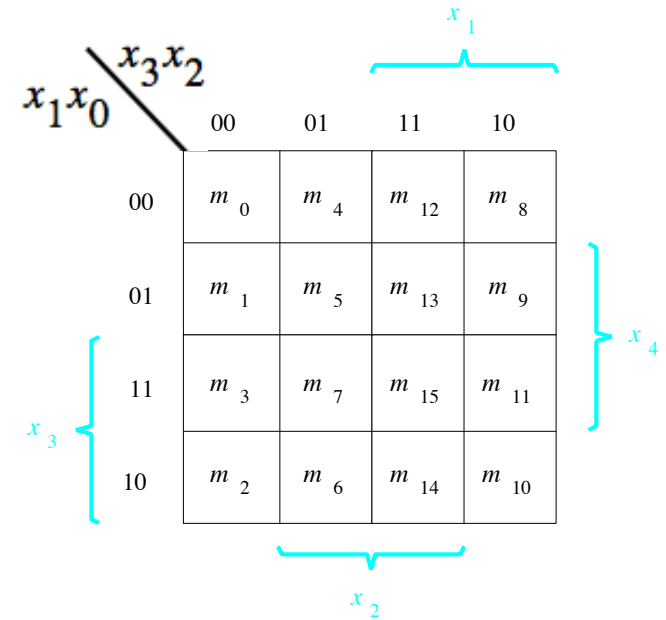



In this case all d's were treated as 1's.

# Seven-Segment Indicator

	$x_3$	$x_2$	$x_1$	$x_0$	$a$	$b$	$c$	$d$	$e$	$f$	$g$
0	0	0	0	0	1	1	1	1	1	1	0
1	0	0	0	1	0	1	1	0	0	0	0
2	0	0	1	0	1	1	0	1	1	0	1
3	0	0	1	1	1	1	1	1	0	0	1
4	0	1	0	0	0	1	1	0	0	1	1
5	0	1	0	1	1	0	1	1	0	1	1
6	0	1	1	0	1	0	1	1	1	1	1
7	0	1	1	1	1	1	1	0	0	0	0
8	1	0	0	0	1	1	1	1	1	1	1
9	1	0	0	1	1	1	1	1	0	1	1
d	1	0	1	0	1	d	d	d	d	d	d
d	1	0	1	1	1	d	d	d	d	d	d
d	1	1	0	0	1	d	d	d	d	d	d
d	1	1	0	1	1	d	d	d	d	d	d
d	1	1	1	0	1	d	d	d	d	d	d
d	1	1	1	1	1	d	d	d	d	d	d



# Seven-Segment Indicator

$x_3$	$x_2$	$x_1$	$x_0$	$a$	$b$	$c$	$d$	$e$	$f$	$g$
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1
1	0	1	0	1	d	d	d	d	d	d
1	0	1	1	1	d	d	d	d	d	d
1	1	0	0	1	d	d	d	d	d	d
1	1	0	1	1	d	d	d	d	d	d
1	1	1	0	1	d	d	d	d	d	d
1	1	1	1	1	d	d	d	d	d	d

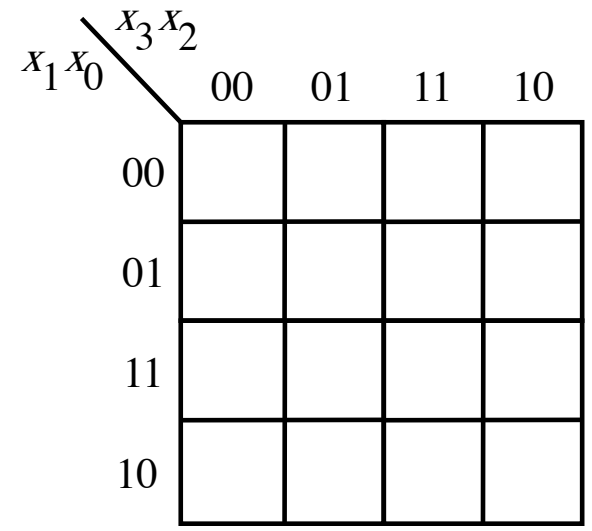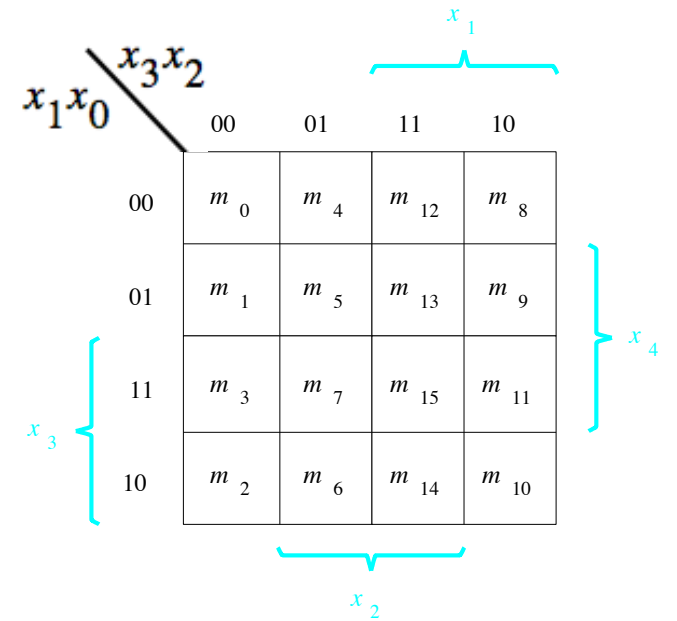



# Seven-Segment Indicator

$x_3$	$x_2$	$x_1$	$x_0$	$a$	$b$	$c$	$d$	$e$	$f$	$g$
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1
1	0	1	0	1	d	d	d	d	d	d
1	0	1	1	1	d	d	d	d	d	d
1	1	0	0	1	d	d	d	d	d	d
1	1	0	1	1	d	d	d	d	d	d
1	1	1	0	1	d	d	d	d	d	d
1	1	1	1	1	d	d	d	d	d	d

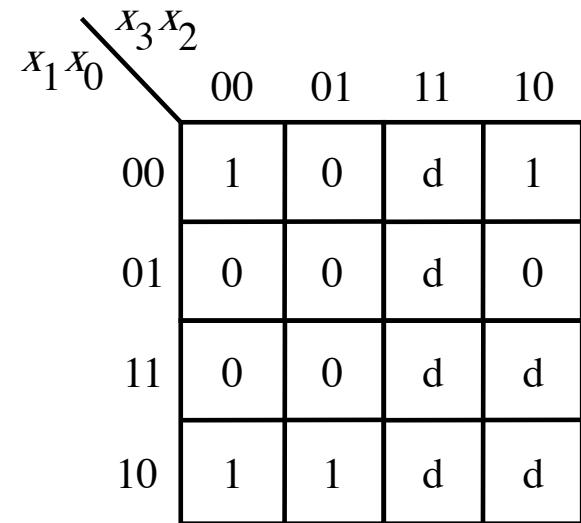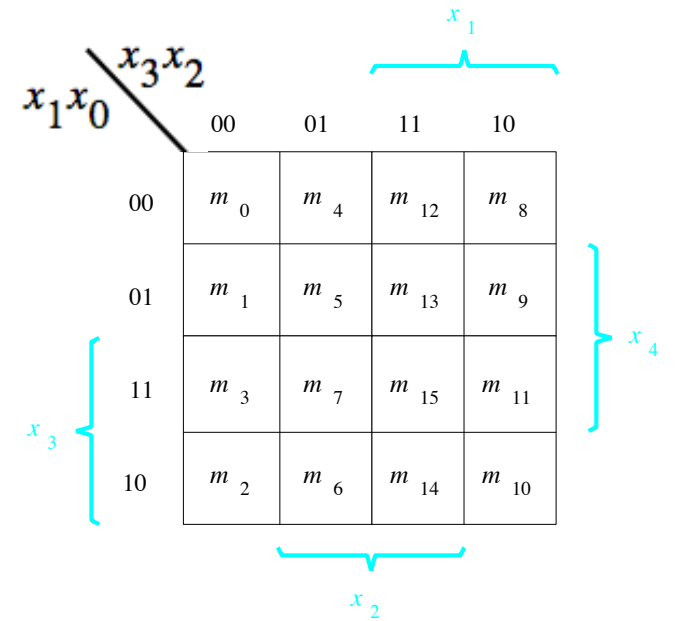



# Seven-Segment Indicator

$x_3$	$x_2$	$x_1$	$x_0$	$a$	$b$	$c$	$d$	$e$	$f$	$g$
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1
1	0	1	0	1	d	d	d	d	d	d
1	0	1	1	1	d	d	d	d	d	d
1	1	0	0	1	d	d	d	d	d	d
1	1	0	1	1	d	d	d	d	d	d
1	1	1	0	1	d	d	d	d	d	d
1	1	1	1	1	d	d	d	d	d	d

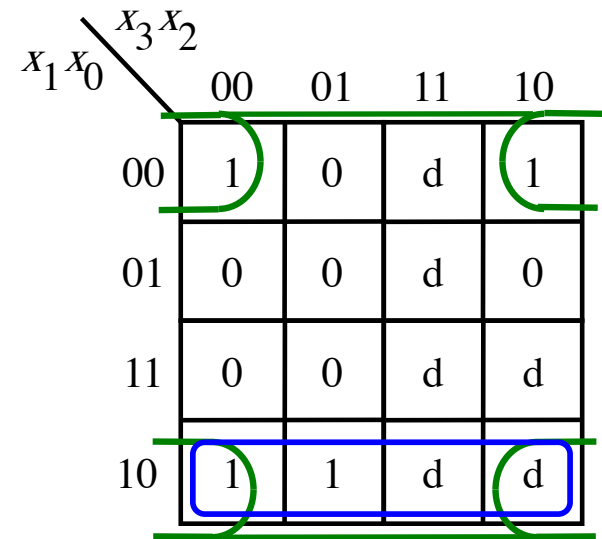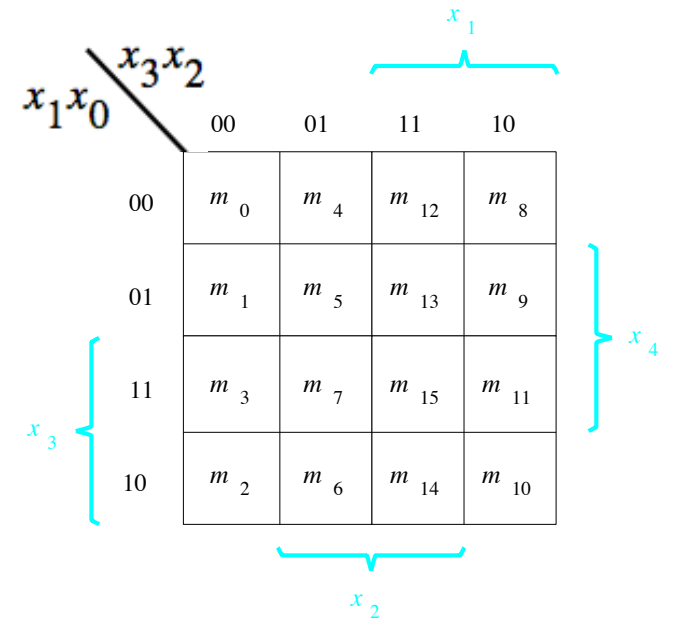

# Seven-Segment Indicator

$x_3$	$x_2$	$x_1$	$x_0$	$a$	$b$	$c$	$d$	$e$	$f$	$g$
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1
1	0	1	0	1	d	d	d	1	d	d
1	0	1	1	1	d	d	d	0	d	d
1	1	0	0	1	d	d	d	0	d	d
1	1	0	1	1	d	d	d	0	d	d
1	1	1	0	1	d	d	d	1	d	d
1	1	1	1	1	d	d	d	0	d	d

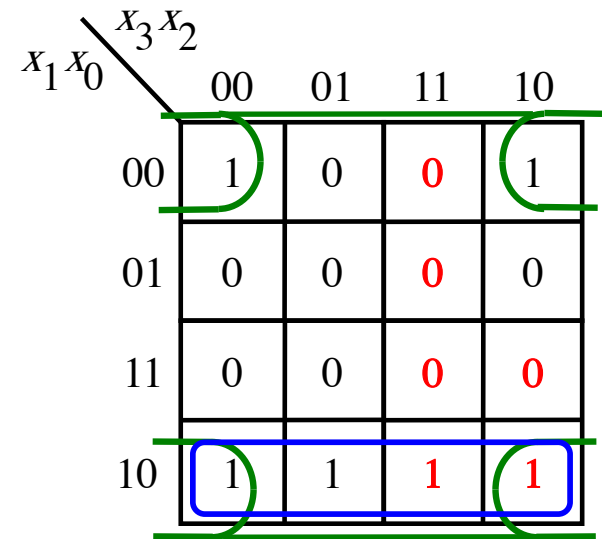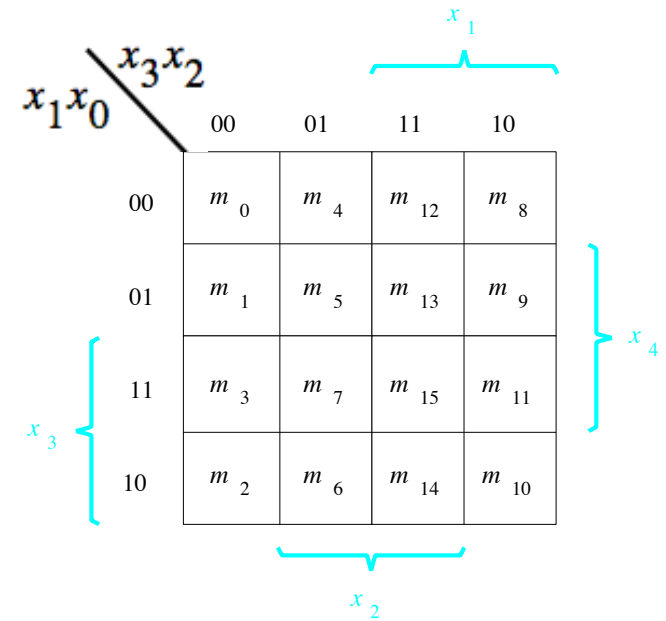


In this case some d's were treated as 1's, others as 0's.

# Seven-Segment Indicator

	$x_3$	$x_2$	$x_1$	$x_0$	$a$	$b$	$c$	$d$	$e$	$f$	$g$
0	0	0	0	0	1	1	1	1	1	1	0
1	0	0	0	1	0	1	1	0	0	0	0
2	0	0	1	0	1	1	0	1	1	0	1
3	0	0	1	1	1	1	1	1	0	0	1
4	0	1	0	0	0	1	1	0	0	1	1
5	0	1	0	1	1	0	1	1	0	1	1
6	0	1	1	0	1	0	1	1	1	1	1
7	0	1	1	1	1	1	1	0	0	0	0
8	1	0	0	0	1	1	1	1	1	1	1
9	1	0	0	1	1	1	1	1	0	1	1

(b) Truth table

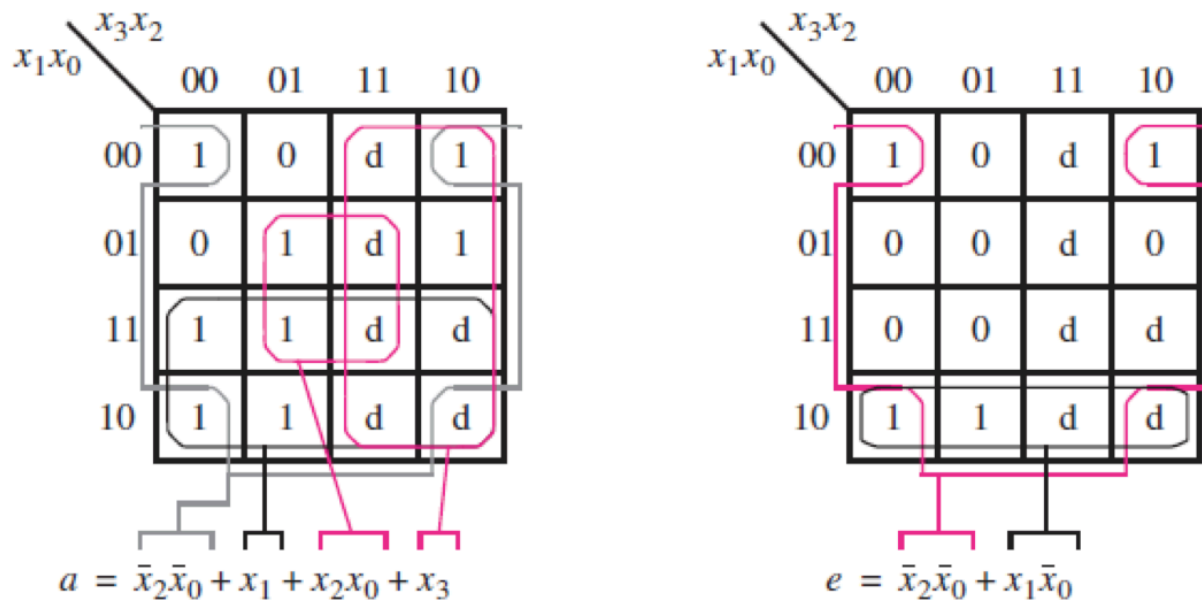

(c) The Karnaugh maps for outputs  $a$  and  $e$ .

# **Another Example**



$x_3 x_4 \backslash x_1 x_2$	00	01	11	10
00			1	1
01		1	1	1
11	1	1		
10	1	1		

(a) Function  $f_1$

$x_3 x_4 \backslash x_1 x_2$	00	01	11	10
00			1	1
01			1	1
11	1	1	1	
10	1	1		

(b) Function  $f_2$

$x_3 x_4 \backslash x_1 x_2$	00	01	11	10
00			1	1
01		1	1	1
11	1	1		
10	1	1		

(a) Function  $f_1$

$x_3 x_4 \backslash x_1 x_2$	00	01	11	10
00			1	1
01			1	1
11	1	1		
10	1	1		

(b) Function  $f_2$


$x_3 x_4 \backslash x_1 x_2$	00	01	11	10
00			1	1
01		1	1	1
11	1	1		
10	1	1		

(a) Function  $f_1$

$x_3 x_4 \backslash x_1 x_2$	00	01	11	10
00			1	1
01			1	1
11	1	1		
10	1	1		

(b) Function  $f_2$

$\bar{x}_1 x_3$

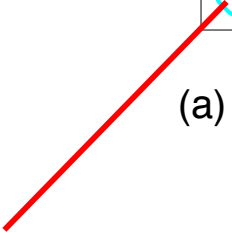

$x_3 x_4 \backslash x_1 x_2$	00	01	11	10
00			1	1
01		1	1	1
11	1	1		
10	1	1		

(a) Function  $f_1$

$x_3 x_4 \backslash x_1 x_2$	00	01	11	10
00			1	1
01			1	1
11	1	1	1	
10	1	1		

(b) Function  $f_2$

$\bar{x}_1 x_3$

$x_3 x_4 \backslash x_1 x_2$	00	01	11	10
00			1	1
01		1	1	1
11	1	1		
10	1	1		

(a) Function  $f_1$

$$\overline{x_1} x_3$$

$x_3 x_4 \backslash x_1 x_2$	00	01	11	10
00			1	1
01			1	1
11	1	1	1	
10	1	1		

(b) Function  $f_2$

$$\overline{x_1} x_3$$

$x_3 x_4 \backslash x_1 x_2$	00	01	11	10
00			1	1
01		1	1	1
11	1	1		
10	1	1		

(a) Function  $f_1$

$\overline{x_1} x_3$

$x_3 x_4 \backslash x_1 x_2$	00	01	11	10
00			1	1
01			1	1
11	1	1	1	
10	1	1		

(b) Function  $f_2$

$\overline{x_1} x_3$

$x_3 x_4 \backslash x_1 x_2$	00	01	11	10
00			1	1
01		1	1	1
11	1	1		
10	1	1		

(a) Function  $f_1$

$\bar{X}_1 \bar{X}_3$

$x_3 x_4 \backslash x_1 x_2$	00	01	11	10
00			1	1
01			1	1
11	1	1	1	
10	1	1		

(b) Function  $f_2$

$\bar{X}_1 X_3$

$\bar{X}_1 X_3$

$x_3 x_4 \backslash x_1 x_2$	00	01	11	10
00			1	1
01		1	1	1
11	1	1		
10	1	1		

(a) Function  $f_1$

$$\bar{x}_1 x_3$$

$$x_1 \bar{x}_3$$

$$\bar{x}_2 x_3 x_4$$

$x_3 x_4 \backslash x_1 x_2$	00	01	11	10
00			1	1
01			1	1
11	1	1	1	
10	1	1		

(b) Function  $f_2$

$$x_2 x_3 x_4$$

$$\bar{x}_1 x_3$$



$x_3 x_4 \backslash x_1 x_2$	00	01	11	10
00			1	1
01		1	1	1
11	1	1		
10	1	1		

(a) Function  $f_1$

$\bar{X}_1 \bar{X}_3$

$\bar{X}_2 \bar{X}_3 X_4$


$x_3 x_4 \backslash x_1 x_2$	00	01	11	10
00			1	1
01			1	1
11	1	1	1	
10	1	1		

(b) Function  $f_2$

$X_2 X_3 X_4$

$\bar{X}_1 X_3$

$\bar{X}_1 X_3$

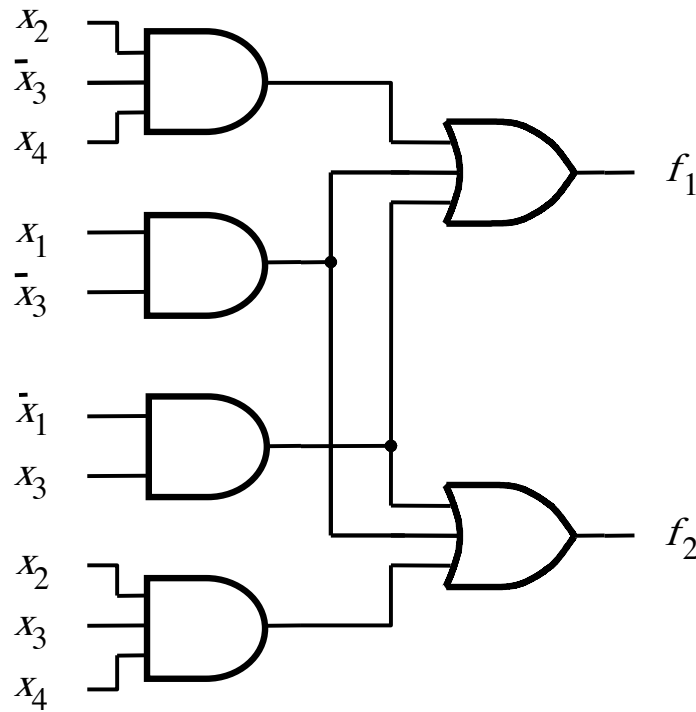

(c) Combined circuit for  $f_1$  and  $f_2$

$x_3 x_4 \backslash x_1 x_2$	00	01	11	10
00			1	1
01		1	1	1
11	1	1		
10	1	1		

(a) Function  $f_1$

$$\bar{X}_1 \bar{X}_3$$

$$\bar{X}_2 \bar{X}_3 X_4$$


$x_3 x_4 \backslash x_1 x_2$	00	01	11	10
00			1	1
01			1	1
11	1	1	1	
10	1	1		

(b) Function  $f_2$

$$X_2 X_3 X_4$$

$$\bar{X}_1 \bar{X}_3$$

$$\bar{X}_1 \bar{X}_3$$

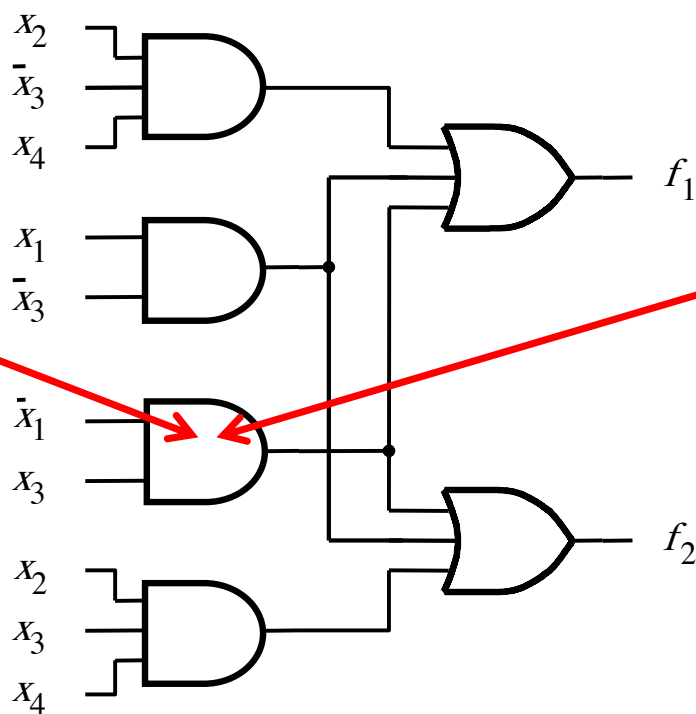

(c) Combined circuit for  $f_1$  and  $f_2$

$x_3 x_4$ \ $x_1 x_2$	00	01	11	10
00			1	1
01		1	1	1
11	1	1		
10	1	1		

(a) Function  $f_1$

$x_3 x_4$ \ $x_1 x_2$	00	01	11	10
00			1	1
01			1	1
11	1	1	1	
10	1	1		


(b) Function  $f_2$

$$\bar{x}_2 \bar{x}_3 x_4$$

$$x_2 x_3 x_4$$

$$\bar{x}_1 x_3$$

$$\bar{x}_1 x_3$$

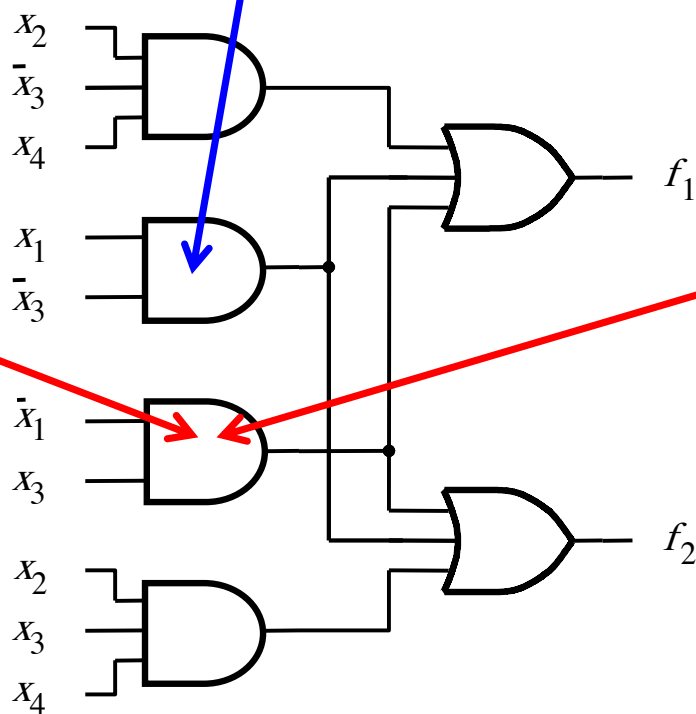

(c) Combined circuit for  $f_1$  and  $f_2$

$x_3 x_4 \backslash x_1 x_2$	00	01	11	10
00			1	1
01		1	1	1
11	1	1		
10	1	1		

(a) Function  $f_1$

$x_3 x_4 \backslash x_1 x_2$	00	01	11	10
00			1	1
01			1	1
11	1	1	1	
10	1	1		


(b) Function  $f_2$

$\bar{x}_2 \bar{x}_3 x_4$

$x_2 x_3 x_4$

$\bar{x}_1 \bar{x}_3$

$\bar{x}_1 x_3$

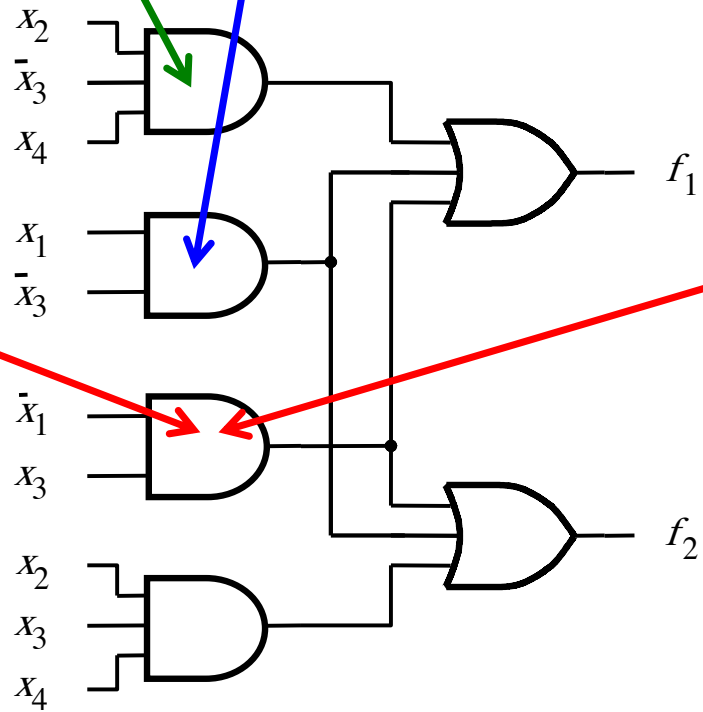


(c) Combined circuit for  $f_1$  and  $f_2$

$x_3 x_4$ \ $x_1 x_2$	00	01	11	10
00			1	1
01		1	1	1
11	1	1		
10	1	1		

(a) Function  $f_1$

$x_3 x_4$ \ $x_1 x_2$	00	01	11	10
00			1	1
01			1	1
11	1	1	1	
10	1	1		

(b) Function  $f_2$

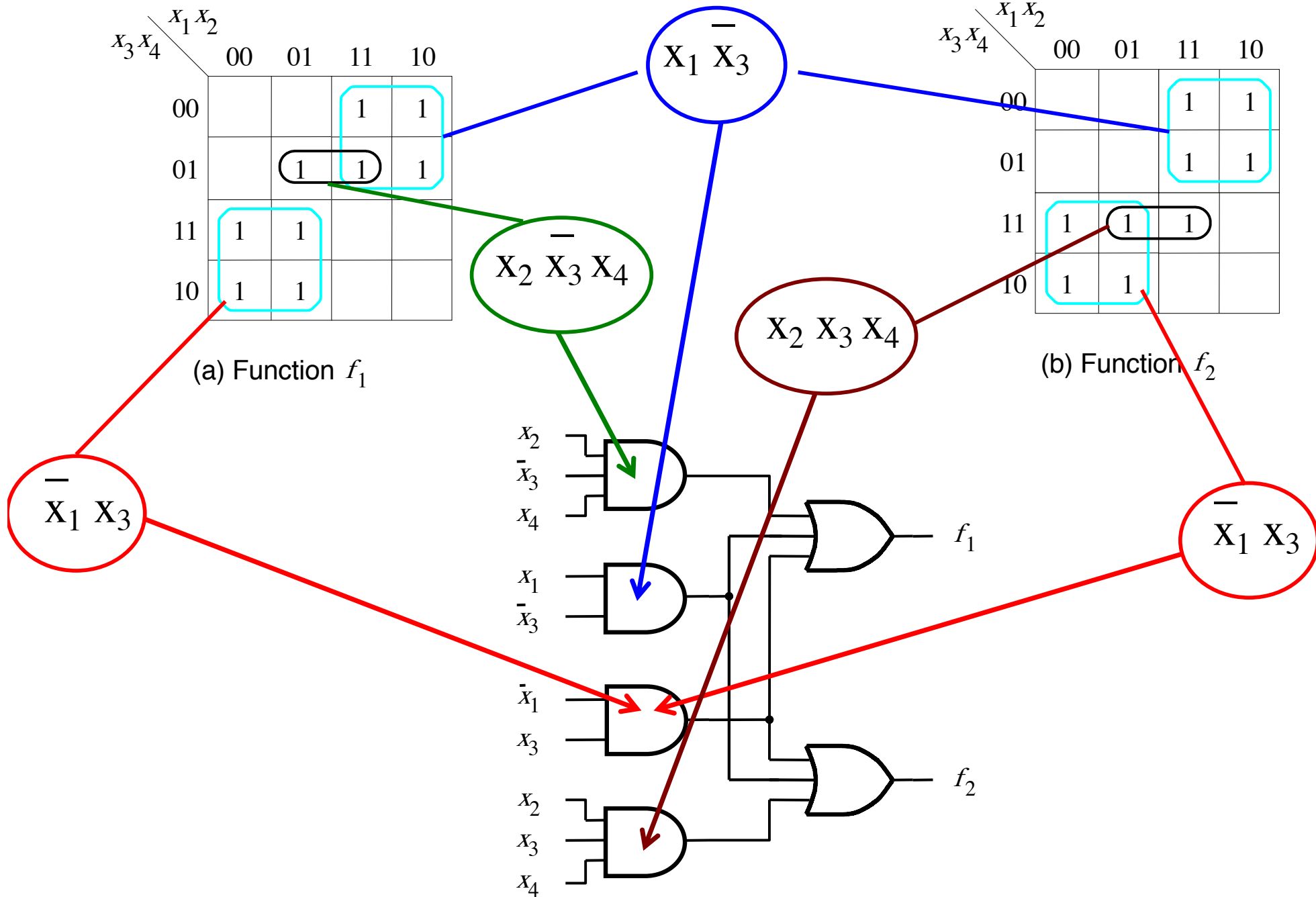


(c) Combined circuit for  $f_1$  and  $f_2$

	$x_1 x_2$			
$x_3 x_4$	00	01	11	10
00			1	1
01		1	1	1
11	1	1		
10	1	1		

(a) Function  $f_1$

	$x_1 x_2$			
$x_3 x_4$	00	01	11	10
00			1	1
01			1	1
11	1	1		
10	1	1		


(b) Function  $f_2$

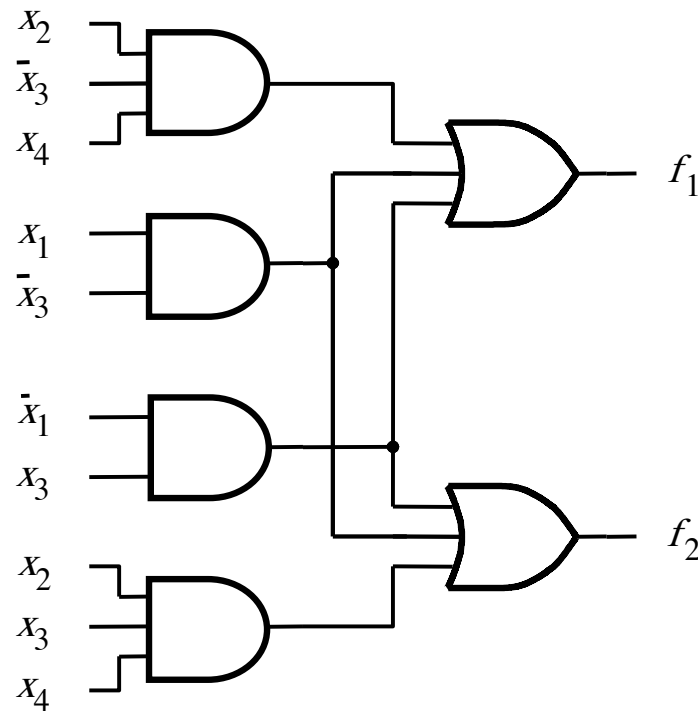


(c) Combined circuit for  $f_1$  and  $f_2$

**Yet Another Example**


# Individual vs Joint Optimization

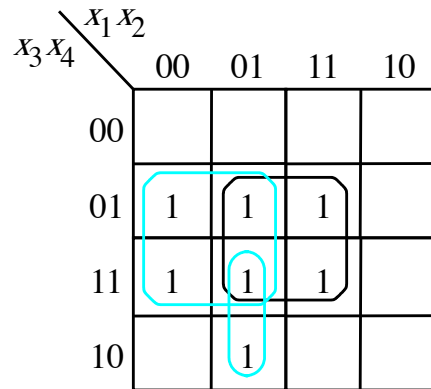

(a) Optimal realization of  $f_3$

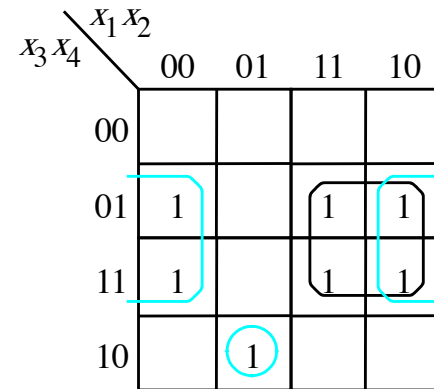


(b) Optimal realization of  $f_4$

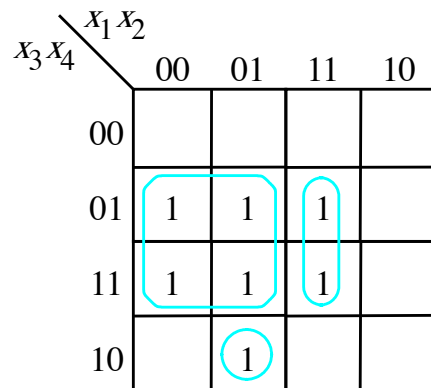


(c) Optimal realization of  $f_3$  and  $f_4$  together



# Individual vs Joint Optimization

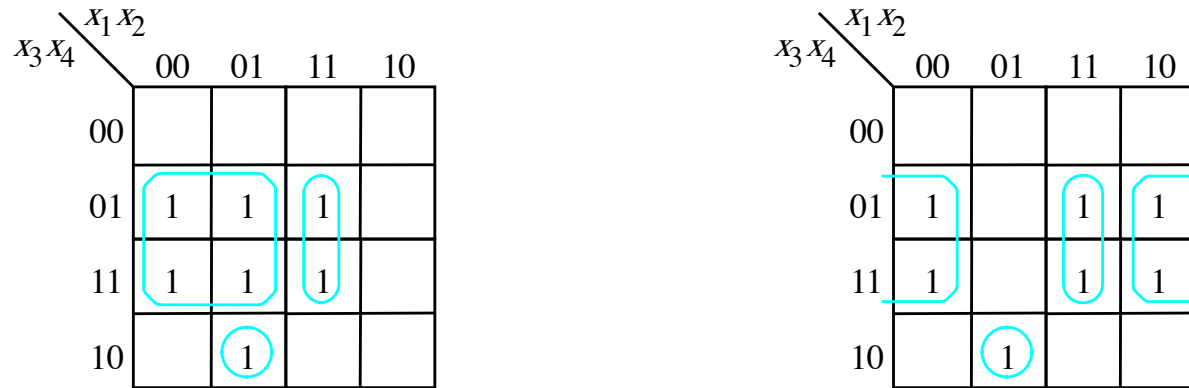


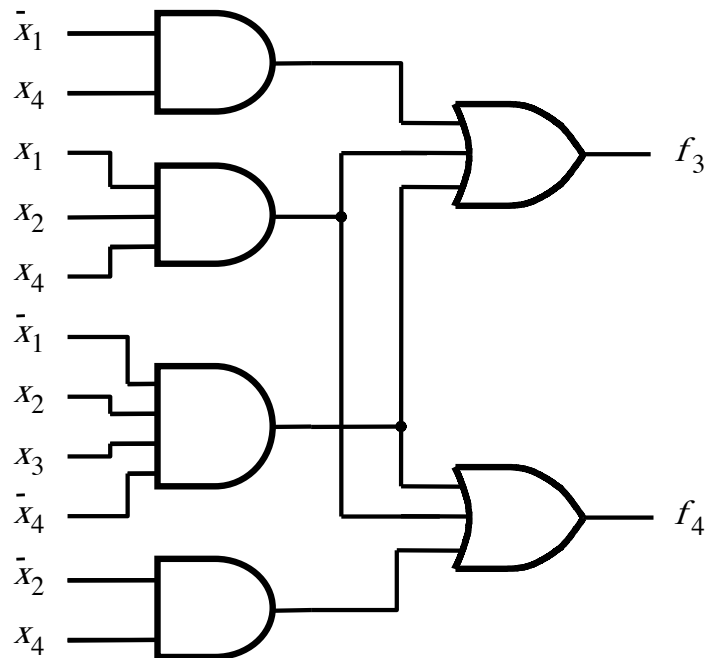(c) Optimal realization of  $f_3$  and  $f_4$  together




(d) Combined circuit for  $f_3$  and  $f_4$

# Individual vs Joint Optimization

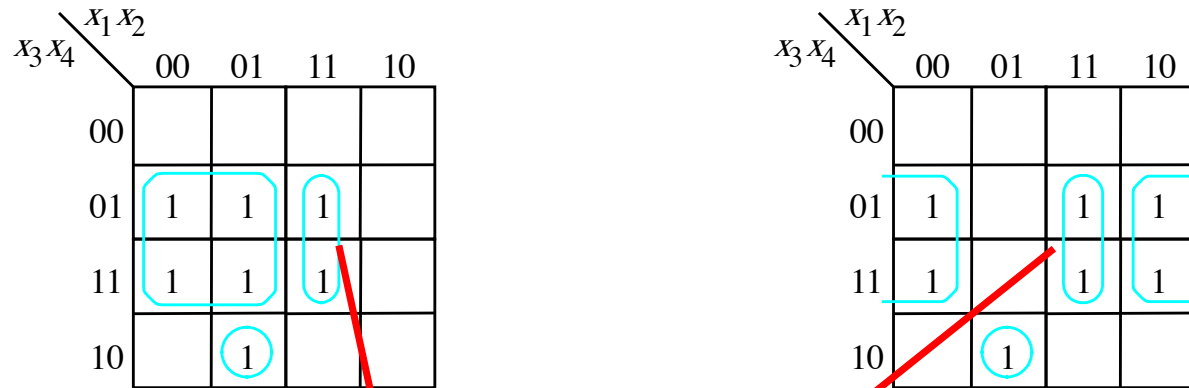


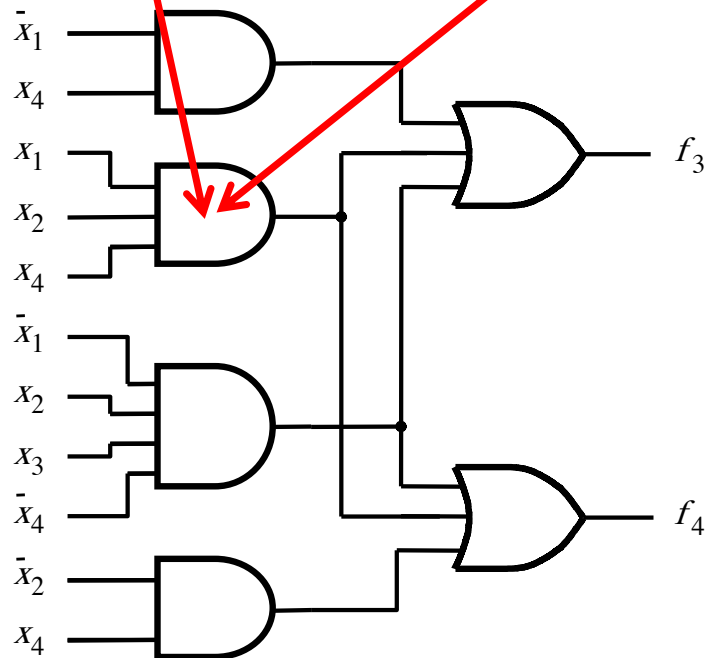(c) Optimal realization of  $f_3$  and  $f_4$  together




(d) Combined circuit for  $f_3$  and  $f_4$

# Individual vs Joint Optimization

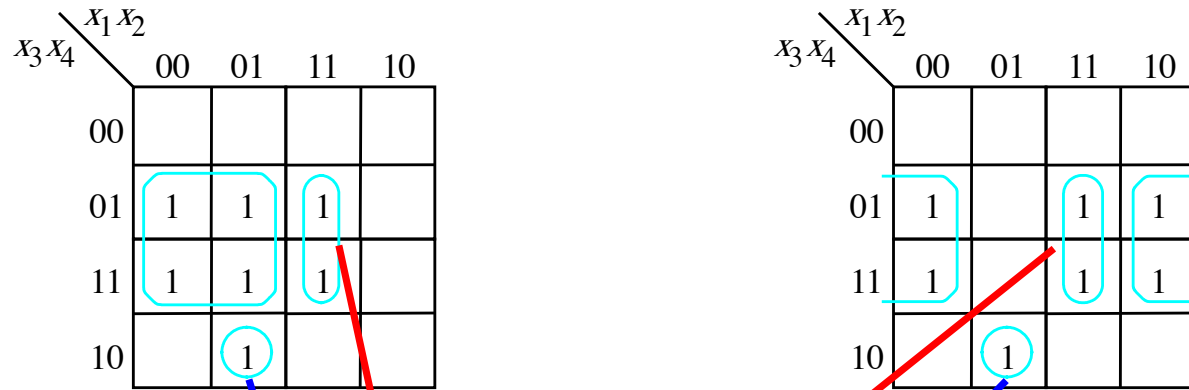

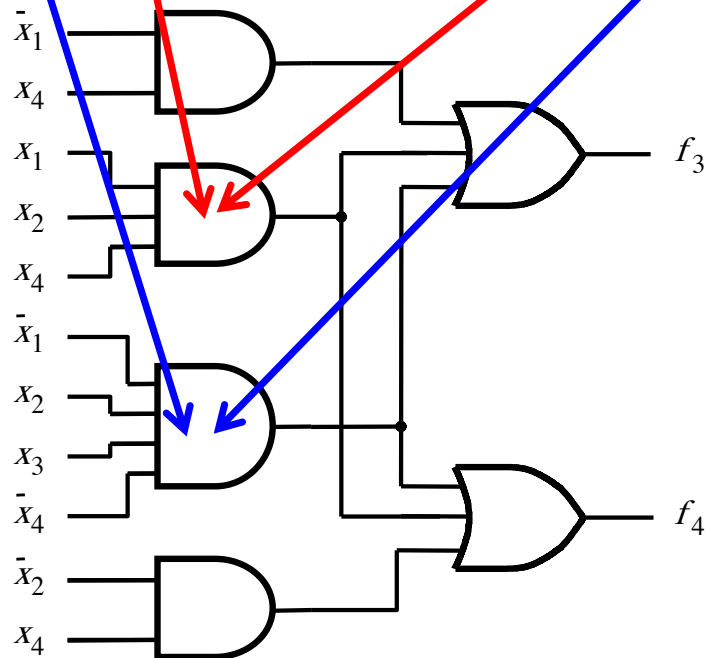(c) Optimal realization of  $f_3$  and  $f_4$  together



(d) Combined circuit for  $f_3$  and  $f_4$

**Questions?**

**THE END**