

P1 (10 points):


Briefly explain the major difference between a Moore state machine and a Mealy state machine.

P2 (15 points): Design a Moore FSM that has one-bit input A and one-bit output B, where $B=1$ if the last six bits of A are 100111 (from earliest to latest). Draw the state diagram for this FSM.

P3 (15 points): Design a Mealy FSM that has one-bit input A and one-bit output B, where $B=1$ if the last six bits of A are 111001 (from earliest to latest). Draw the state diagram for this FSM.

P4 (15 points): Create a Moore FSM for a circuit that outputs $z=1$ if input $w=1$ for the last three clock cycles. The states should be as follows: SA=00, SB=10, SC=11, and SD=01. These states encountered in order from reset to completion of the three clock cycles.

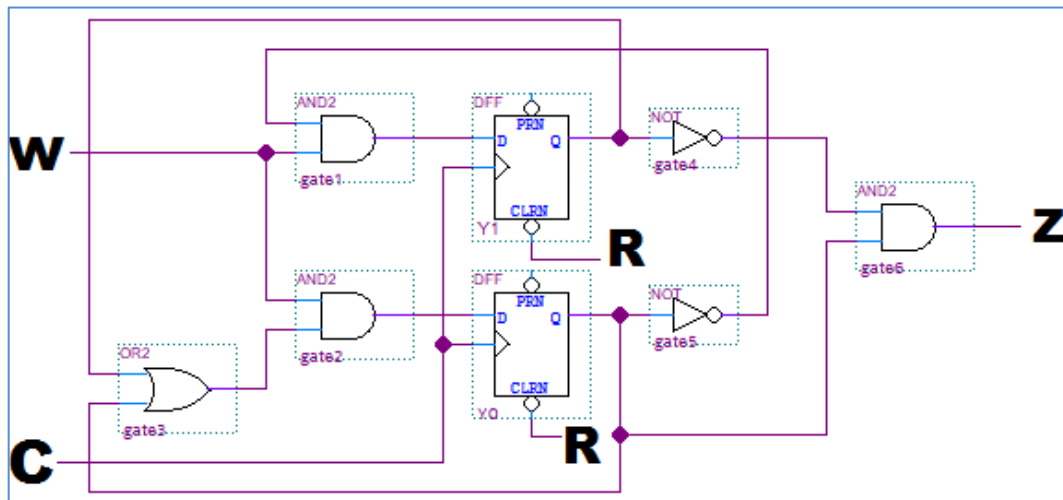- Draw a state diagram for this FSM.
- Create a state-assigned table for this FSM.
- Use K-maps to show that the following circuit implements this FSM. Note the expressions should be in POS form, in accordance with the circuit below.




P5 (10 points): Design a Mealy FSM with the following specifications:

- There is a one-bit input X
- There is a one-bit output Z
- On each cycle, a three-bit value stored in the FSM (V) is shifted left and X replaces the least significant bit of V
 - e.g. if $X=0$ and $V=101_2$ then $V^{new}=010_2$
- The output $Z=1$ if V is greater than 4.

Draw the state table for this Mealy FSM.

 
P6 (20 points): A FSM has five states, five state variables, one-bit input W , one-bit reset R , and one-bit output M . The FSM has an output that corresponds with the timing diagram shown below. Answer the following questions.



- The five states encountered in this timing diagram, in order, are A, B, C, D, and then E. What are the state encodings for these states?
- Draw a state diagram for this FSM.
- Draw a state-assigned table for this FSM.
- This circuit is implemented using five DFFs. Derive expressions for the next state variables and the output M .
- Explain why this particular circuit has the same number of states as it does state variables and why this isn't necessarily true of other circuits?

P7 (15 points):

 A FSM has two D flip-flops, an input w , and an output z . The circuit diagram is shown below.



- (5 points) Find the logic expressions of Y_1 , Y_0 , and the output z .
- (5 points) Show the state-assigned table of the FSM.
- (5 points) Draw the state diagram of the FSM.