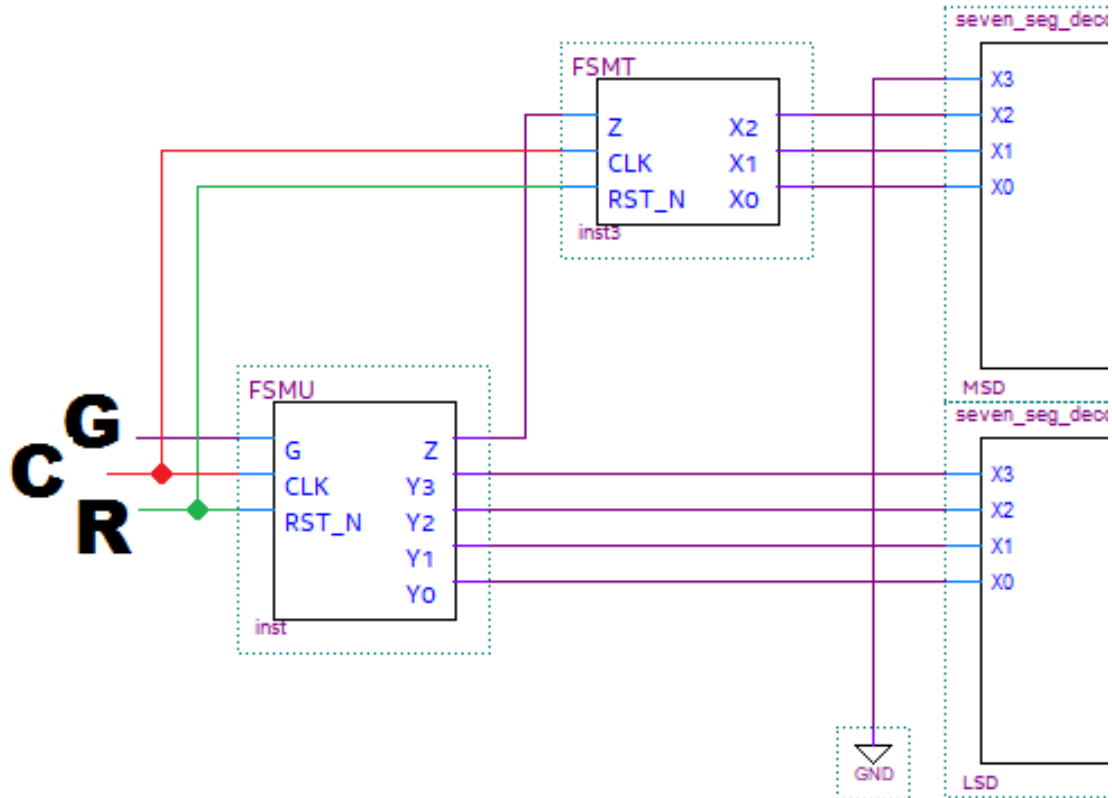


P1 (20 points): For this problem, you are given two FSMs: FSM T has six states, one-bit input Z, and three-bit output $X_2 X_1 X_0$. FSM U has ten states, one-bit input G, and five-bit output $Z Y_3 Y_2 Y_1 Y_0$. These FSMs are connected as shown below:



Each FSM shown here has states determined by a sufficient number of positive-edge-triggered DFFs.


- Draw the state table for FSM U, a modulo-10 counter that counts *down* when $G=1$ and holds its value constant when $G=0$. Upon reset, FSM U should return to a state which outputs $Y=9$. The output $Z=1$ if $Y=0$ and $G=1$. Make state assignments such that the output Y is equal to the current state (note: the state variable and the output should not have the same name).
- FSM U has one input and four state variables, so each expression for the next state is a function of five inputs. To avoid using a 5-variable K-map, we will instead implement FSM U using four 2-to-1 MUXes with G as the select line. Let us assume that $G=1$. Derive the next state expressions assuming that $G=1$. Show that the K-maps for the next state variables produce these expressions.

$$\text{For } G = 1: S_3^{new} = \bar{S}_3 \bar{S}_2 \bar{S}_1 \bar{S}_0 + S_3 S_0, S_2^{new} = S_3 \bar{S}_0 + S_2 S_1 + S_2 S_0$$

$$S_1^{new} = S_2 \bar{S}_1 \bar{S}_0 + S_3 \bar{S}_0 + S_1 S_0, S_0^{new} = \bar{S}_0$$

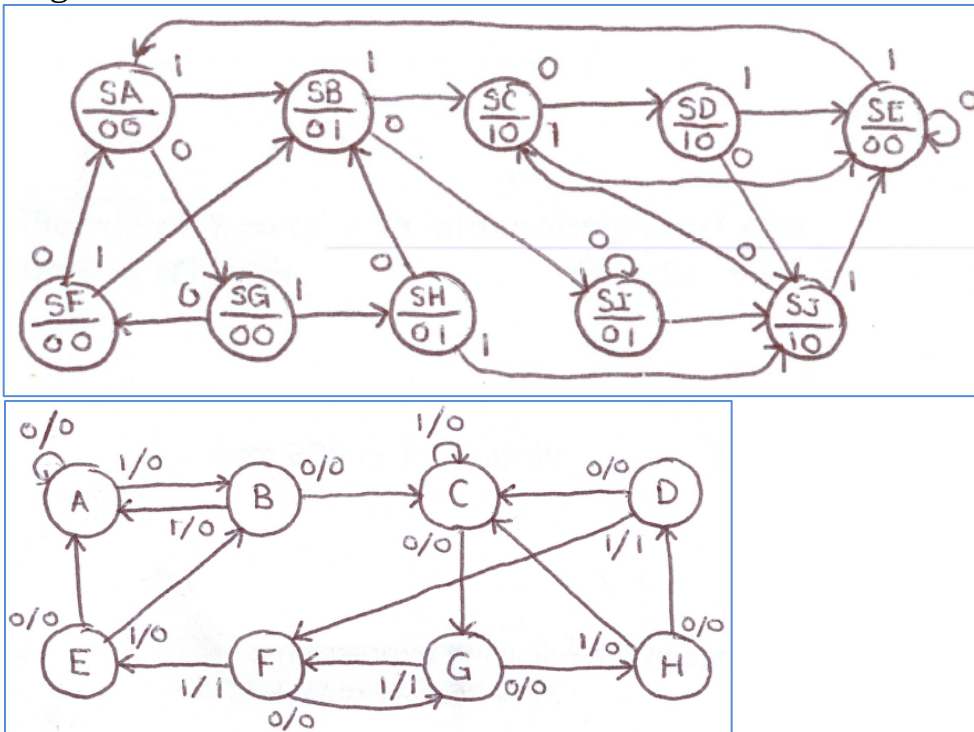- c) FSM T is a modulo-6 counter that also counts down when Z=1 and resets to a state which outputs X=5. Draw the state table for FSM T.
- d) If both FSMs are treated as a single FSM as shown in the initial diagram, what type of circuit does it create? Please specify the direction, encoding, and modulus.


P2 (15 points): Perform state minimization on the following state diagrams.




P3 (10 points): Consider a state machine that detects if a number (F) is a multiple of three (3, 6, 9, 12...). Draw the specified ASM chart that will output Z=1 based on the input W. Let F be the number of clock cycles for which the input W has been one. Draw a Moore type ASM chart that outputs Z=1 if F is a multiple of 3.

P4 (10 points): For each of the following, convert each ASM chart to a FSM diagram.

a)

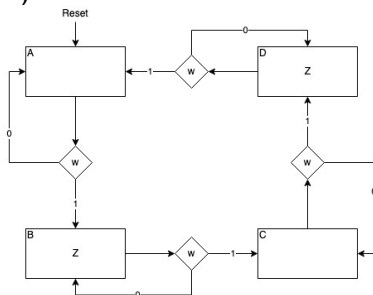

b)

 

P5 (10 points): Answer the following questions about register machines.

- How many possible operations can be performed in a register machine? List and explain each operation.
- How does a register machine perform an if statement? Explain your answer.

P6 (15 points): Consider the following register machine:

Step	Instruction	Register	Go to step	[Branch to step]
1	Deb	1	2	7
2	Deb	2	3	5
3	Inc	0	4	
4	Inc	3	2	
5	Deb	3	6	1
6	Inc	2	5	
7	End			

Syntax note: register 0 is shortened to R0, register 1 is R1, and so on.

- Let $R0 = 0$, $R1 = 3$, $R2 = 2$, and $R3 = 0$.
 What will be the values stored in R0, R1, R2, and R3 after the machine finishes running?
- Let $R0 = 0$, $R1 = 0$, $R2 = 100$, and $R3 = 0$.
 What will be the values stored in R0, R1, R2, and R3 after the machine finishes running?

- c) Let $R0 = 0$, $R1 = \mathbf{x}$, $R2 = \mathbf{y}$, and $R3 = 0$ where \mathbf{x} and \mathbf{y} are two random integers.
Write the value of $R0$, $R1$, $R2$, and $R3$ in terms of \mathbf{x} , \mathbf{y} , and necessary constant numbers. (e.g. $R0 = \mathbf{x} + \mathbf{y}$, $R1 = 3$, and so on).

P7 (15 points): Consider a register machine with three registers ($R0$, $R1$, and $R2$). Let $R0 = ?$, $R1 = \mathbf{x}$, and $R2 = \mathbf{y}$. The value stored in $R0$ is unknown, and the values \mathbf{x} and \mathbf{y} are two random integers. Write out the instructions for the register machine that will add \mathbf{x} and \mathbf{y} and store the sum in $R0$ (e.g. $R0 = \mathbf{x} + \mathbf{y}$, $R1 = 0$, $R2 = 0$).

P8 (5 points): Refer to the lecture slides for *the i281 CPU* to answer the following questions about the i281 CPU:

- How many control signals (number of wires) does the i281 CPU have?
- What control signal(s) select the ALU operation?
- What is the name of control signal C17 and what block does it control?
- How many bits does each instruction have (e.g. how wide is each register in the instruction memory)?
- How many bits of each instruction go to the OpCode Decoder?
Which part of each instruction?