
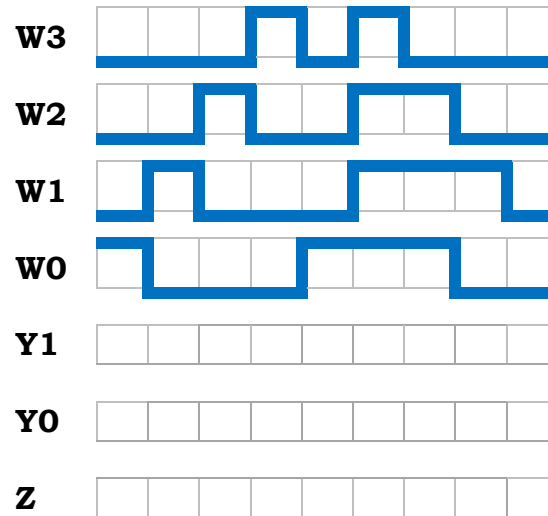


**P1 (10 points):** Fill in the timing diagrams below:

a) For a 4-to-2 priority encoder.

 

b) For a 4-to-2 binary encoder.



**P2. (10 points)** Consider the following truth table for the function  $f(a, b, c, d)$ .


| <b>a</b> | <b>b</b> | <b>c</b> | <b>d</b> | <b>f</b> |
|----------|----------|----------|----------|----------|
| 0        | 0        | 0        | 0        | 0        |
| 0        | 0        | 0        | 1        | 0        |
| 0        | 0        | 1        | 0        | 0        |
| 0        | 0        | 1        | 1        | 0        |
| 0        | 1        | 0        | 0        | 1        |
| 0        | 1        | 0        | 1        | 1        |
| 0        | 1        | 1        | 0        | 1        |
| 0        | 1        | 1        | 1        | 1        |
| 1        | 0        | 0        | 0        | 0        |
| 1        | 0        | 0        | 1        | 1        |
| 1        | 0        | 1        | 0        | 1        |
| 1        | 0        | 1        | 1        | 1        |
| 1        | 1        | 0        | 0        | 0        |
| 1        | 1        | 0        | 1        | 1        |
| 1        | 1        | 1        | 0        | 1        |
| 1        | 1        | 1        | 1        | 0        |

- Implement  $f$  using one 4-to-16 decoder and a minimal number of gates.
- Implement  $f$  using two 2-to-4 decoders, one 4-to-1 multiplexer, and a minimal number of gates.

**P3 (20 points):** 8-to-1 multiplexer

 - a) Write the Boolean function for an 8-to-1 multiplexor that has inputs  $\{X_0, X_1, X_2, X_3, X_4, X_5, X_6, X_7\}$  and select lines  $\{A, B, C\}$ .
  
- b) Implement the multiplexer using AND, OR, and NOT gates.
  
- c) Implement the multiplexer using 2-to-1 multiplexers and a minimal number of additional gates
  
- d) Implement the multiplexer using 4-to-1 multiplexers and a minimal number of additional gates


**P4 (10 points):** Consider the SR Latch shown below.




a) Complete the characteristic table.

| G | S | R | Q | P |
|---|---|---|---|---|
| 0 | 0 | 0 |   |   |
| 0 | 0 | 1 |   |   |
| 0 | 1 | 0 |   |   |
| 0 | 1 | 1 |   |   |
| 1 | 0 | 0 |   |   |
| 1 | 0 | 1 |   |   |
| 1 | 1 | 0 |   |   |
| 1 | 1 | 1 |   |   |

 b) Complete the timing diagram shown below for outputs Q and P.




 **P5 (15 points):** Answer the following questions based on the circuit shown below.



a) The latch that appears (twice) in the above circuit is a D Latch. Show the characteristic table for a D Latch.

 b) Fill in the timing diagram for the values shown above.




c) What is the name of this circuit? Is it a positive or negative edge circuit?

**P6 (15 points):** We want to create an LM-latch with the characteristic table shown below:

| L | M | Q         | P         |
|---|---|-----------|-----------|
| 0 | 0 | 0         | 1         |
| 0 | 1 | No change | No change |
| 1 | 0 | No change | No change |
| 1 | 1 | 1         | 0         |

 a) Show the characteristic table for the SR Latch shown below.



- b) For each input combination to the LM-latch characteristic table shown above, write the values of S and R that will produce the output combinations. Then derive expressions for S and R in terms of L and M.
- c) Draw the completed circuit for the LM-latch with the characteristic table based on the expressions derived in part B.

**P7 (20 points):** Answer the following questions about the Negative-Edge-Triggered Master-Slave DFF with PRESET\_N and CLEAR\_N connections, as shown in Figure 5.12 from the book. Suppose that  $D=1$  and  $CLK=0$ . Answer the following questions about Q.

- a) Ignoring PRESET\_N and CLEAR\_N (assume that they are not connected), what effect does pulsing the clock have on Q in this circuit?
- b) What effect does pulsing PRESET\_N have on this circuit?
- c) What effect does pulsing CLEAR\_N have on this circuit?
- d) What will be the value of Q if PRESET\_N=0 and CLEAR\_N=1?
- e) What will be the value of Q if PRESET\_N=0 and CLEAR\_N=0?
- f) What will be the value of Q if the clock is pulsed while PRESET\_N=0?
- g) What will be the value of Q if the clock is pulsed while CLEAR\_N=0?
- h) What will be the value of Q if the clock is pulsed while CLEAR\_N=1 and PRESET\_N=1?