 


Recitation #11 Solutions

1.



2. State-assigned table for next state:

q2	q1	q0	Input I	Q2	Q1	Q0
0	0	0	0	0	0	0
0	0	0	1	0	0	1
0	0	1	0	0	1	0
0	0	1	1	0	1	1
0	1	0	0	1	0	0
0	1	0	1	1	0	1
0	1	1	0	1	1	0
0	1	1	1	1	1	1
1	0	0	0	0	0	0
1	0	0	1	0	0	1
1	0	1	0	0	1	0
1	0	1	1	0	1	1
1	1	0	0	1	0	0
1	1	0	1	1	0	1
1	1	1	0	1	1	0
1	1	1	1	1	1	1


Q2 = q1
 Q1 = q0
 Q0 = I

State-assigned table for output:

q2	q1	q0	Output F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

$F = q2' \cdot q1 \cdot q0$

Circuit diagram:

 

3. Let S be the Start/Stop signal, C be the Clear signal, and F be the Freeze signal. We first design a 3-bit synchronous up-counter with Start/Stop and Clear using T flip-flops. Assume the current count value is $QQ2\ QQ1\ QQ0$.

S	C	Behavior	T2	T1	T0
0	0	Keep count value	0	0	0
0	1	Clear	$QQ2$	$QQ1$	$QQ0$
1	0	Increment count value	$QQ1.QQ0$	$QQ0$	1
1	1	Clear	$QQ2$	$QQ1$	$QQ0$


$$T2 = C.QQ2 + C'.S.QQ1.QQ0$$

$$T1 = C.QQ1 + C'.S.QQ0$$

$$T0 = C.QQ0 + C'.S$$

Then we add the Freeze feature using some D flip-flops and multiplexers.

The value displayed is $Q2\ Q1\ Q0$.

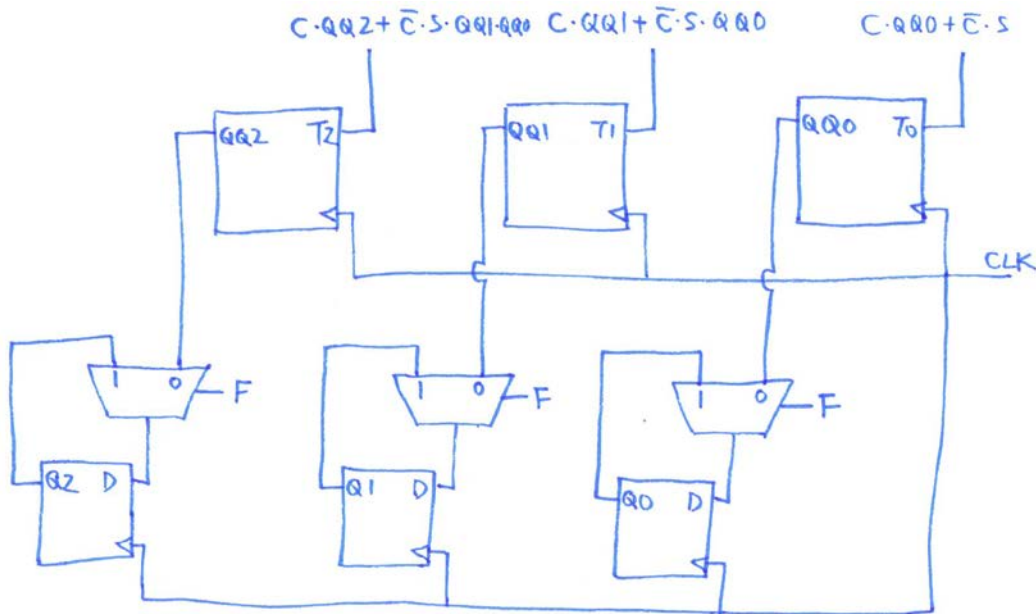

4. Solution not provided.