

P1. (10 points) Write the following expressions as Verilog behavioral assign statements:

E.g., $F = \bar{A}$ as a Verilog assign statement would be "assign F = ~A":

- A. $F = A \cdot B$
- B. $F = A + B$
- C. $F = (A + B) \cdot (\bar{A} + \bar{B})$
- D. $F = \overline{(A \cdot B \cdot C)} + (\bar{A} \cdot \bar{B} \cdot \bar{C})$

P2. (10 points) Match the following descriptions to the Verilog code representation it describes. I.e., Structural or Behavioral Verilog code

- A. Verilog code used to abstractly describe a circuit using logic expressions and programming constructs.
- B. Verilog code used to describe a circuit in terms of circuit elements, such as logic gates.

P3. (10 points) Given the behavioral-continuous Verilog code below:

```

module Q1(f, a, b, c);
    output f;
    input a, b, c;

    assign f = (~(a&b) | c) & (b | (~a&c));

endmodule

```

- A. Rewrite using structural Verilog
- B. Rewrite using behavioral-procedural Verilog

P4. (20 points) Given the truth table shown below:

W	X	Y	Z
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

- A. Find the simplified boolean expression for this table
- B. Write the structural Verilog code for the circuit
- C. Write the behavioral-continuous Verilog code for the circuit.
- D. Write the behavioral-procedural Verilog code for the circuit

- P5. (20 points) Given the expression $F(A, B, C) = \sum m(0,1,3,5)$:
- A. Write the expression as a simplified SOP expression
 - B. Write the expression as a simplified POS expression
 - C. Implement the expression using only NOR gates
 - D. Implement the expression using only NAND gates
 - E. Which expression did you use for part C? For part D? Why?

- P6. (15 points) Show how to implement the following:
- a) 3-input XOR using NAND gates
Hint: How would you implement a 3-input XOR with 2-input XOR gates?
 - b) 4-input NOR gate using five 2-input NOR gates.
 - c) 16-to-1 MUX using five 4-to-1 MUX's

- P7. (15 points) Given the truth table shown below:

A	B	C	H
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

- a) Write the expression for H, then use boolean algebra to obtain the simplified POS expression
- b) Write the shorthand SOP expression for H as the sum of the maxterms.
- c) Implement a circuit for H which uses exactly 4 NOR gates and no other gates.