

P1 (20 points): Given the following K-maps:

F_1		AB			
		00	01	11	10
C	0	1	0	0	1
	1	1	0	0	1

F_2		WX			
		00	01	11	10
YZ	00	0	0	0	0
	01	1	1	1	1
	11	0	0	0	0
	10	1	0	0	1

- Produce the simplified sum-of-products (SOP) expressions
- Produce the simplified product-of-sums (POS) expressions

P2 (15 points): Find the minimized sum-of-products expression for the logical sum $F = G_1 + G_2$:

- $G_1(w, x, y, z) = \sum m(1,4,5,6,7,12,13,15)$
 $G_2(w, x, y, z) = \sum m(5,8,9)$
- $G_1(x, y, z) = \sum m(0,1,2,6)$
 $G_2(x, y, z) = \sum m(0,1,2,6,7)$
- $G_1(a, b, c) = \prod M(0,1,2,7)$
 $G_2(a, b, c) = \prod M(1,3,4,5)$

P3 (20 points) Given the logic expression $F = ABCD + \bar{A}\bar{B}CD + \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}\bar{C}\bar{D}$

- Draw the circuit for the expression F.
- Use a K-map to derive the simplest SOP expression for F
- Redraw the circuit for F using the simplified SOP expression from b).
- Compare the costs of the circuits implementing the expressions in part(b) and part(c) in terms of the total number of gates plus the total number of inputs.

P4 (15 points): For each expression below, derive the simplest POS expression using don't care terms for simplification wherever possible:

a. $H_1(a, b, c, d) = \prod M(0,4,7,11,14) + D(6,8,9,13)$

b. $H_2(a, b, c) = \prod M(2,3,6,7) + D(1,4)$

c. $H_3(a, b, c, d) = \prod M(0,4,5,7,8,11,12) + D(1,2,3)$

P5 (15 points): Given the shorthand expression

$$Z(A,B,C,D) = \prod M(0,1,3,4,5,7,9,13,15):$$

- Derive the simplest POS expression for Z.
- Derive the simplest SOP expression for Z.
- Which expression would produce a lower cost? Why?

P6 (15 points): Use Karnaugh Maps to convert the following expressions to simplified SOP expressions:

a. $Q_1(A, B, C, D) = \bar{A}\bar{C}D + \bar{A}B\bar{C} + BD + A\bar{C}D + A\bar{B}C$

b. $Q_2(A, B, C, D) = \prod M(5,7,14)$

c. $Q_3(A, B, C, D) = (B + \bar{C} + D)(A + C + D)(\bar{B} + \bar{C} + D)$