



CprE 281: Digital Logic

Instructor: Alexander Stoytchev

<http://www.ece.iastate.edu/~alexs/classes/>


Mealy State Model

*CprE 281: Digital Logic
Iowa State University, Ames, IA
Copyright © Alexander Stoytchev*

Administrative Stuff


- Homework 10 is due on Nov 12 @ 10 pm
- Homework 11 is due on Nov 16 @ 10 pm
- Final project ideas:
 - emails to your TAs due on Friday Nov 11

The general form of a synchronous sequential circuit

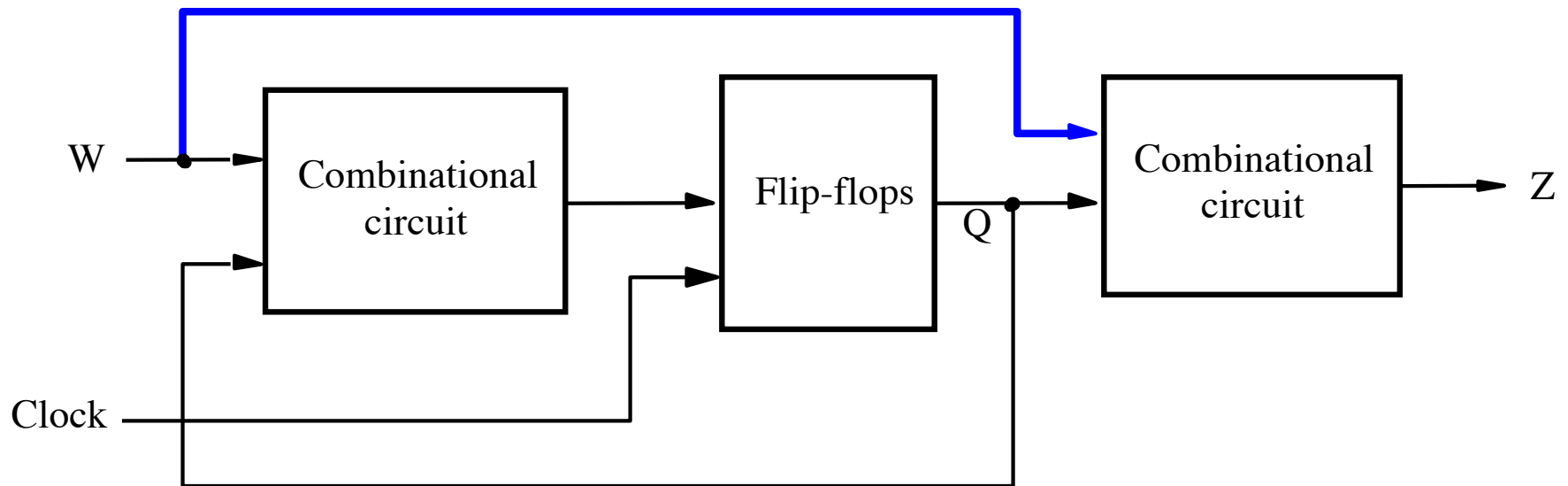


[Figure 6.1 from the textbook]

Moore Type

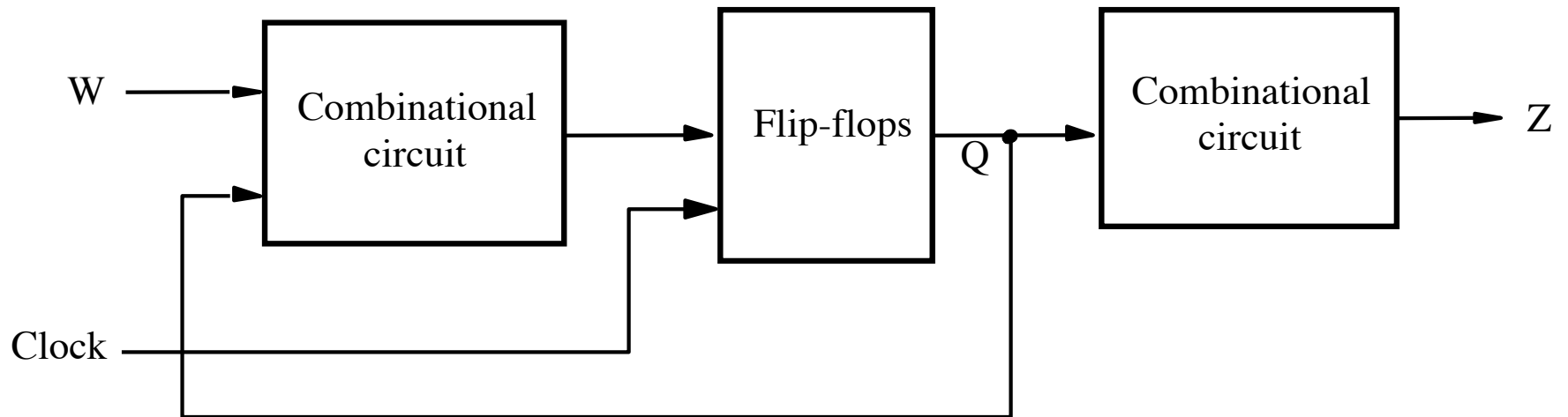

Mealy Type

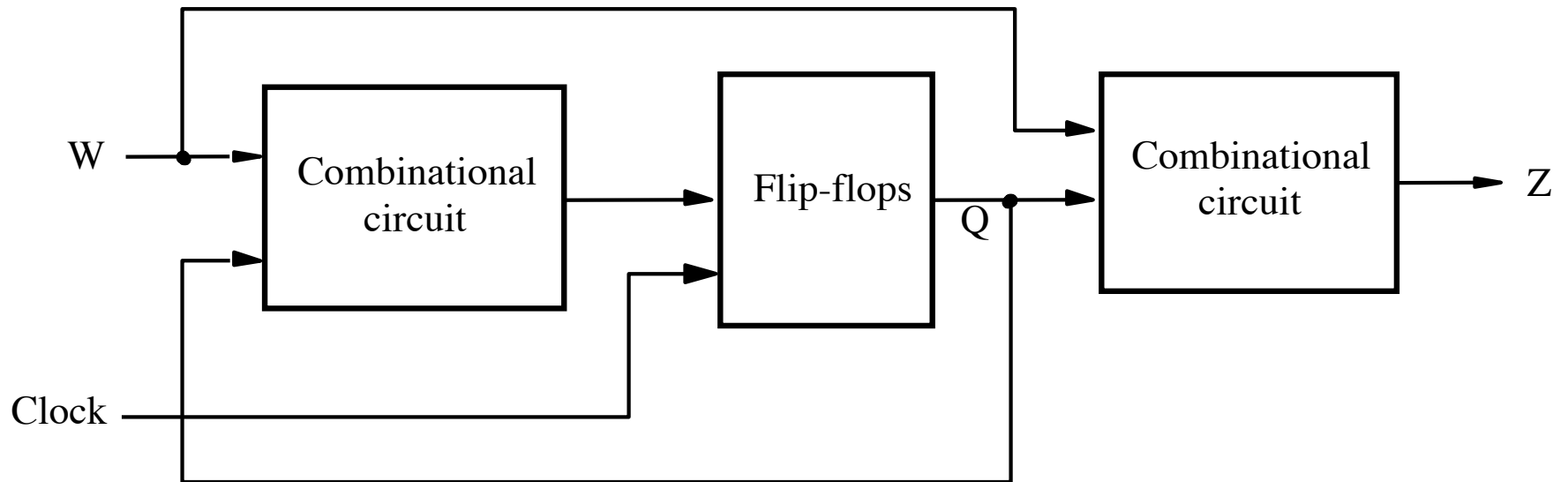


Sample Problem


Implement a 11 detector. In other words, the output should be equal to 1 if two consecutive 1's have been detected on the input line.

The output should become 1 as soon as the second 1 is detected in the input.


Moore Machine Implementation

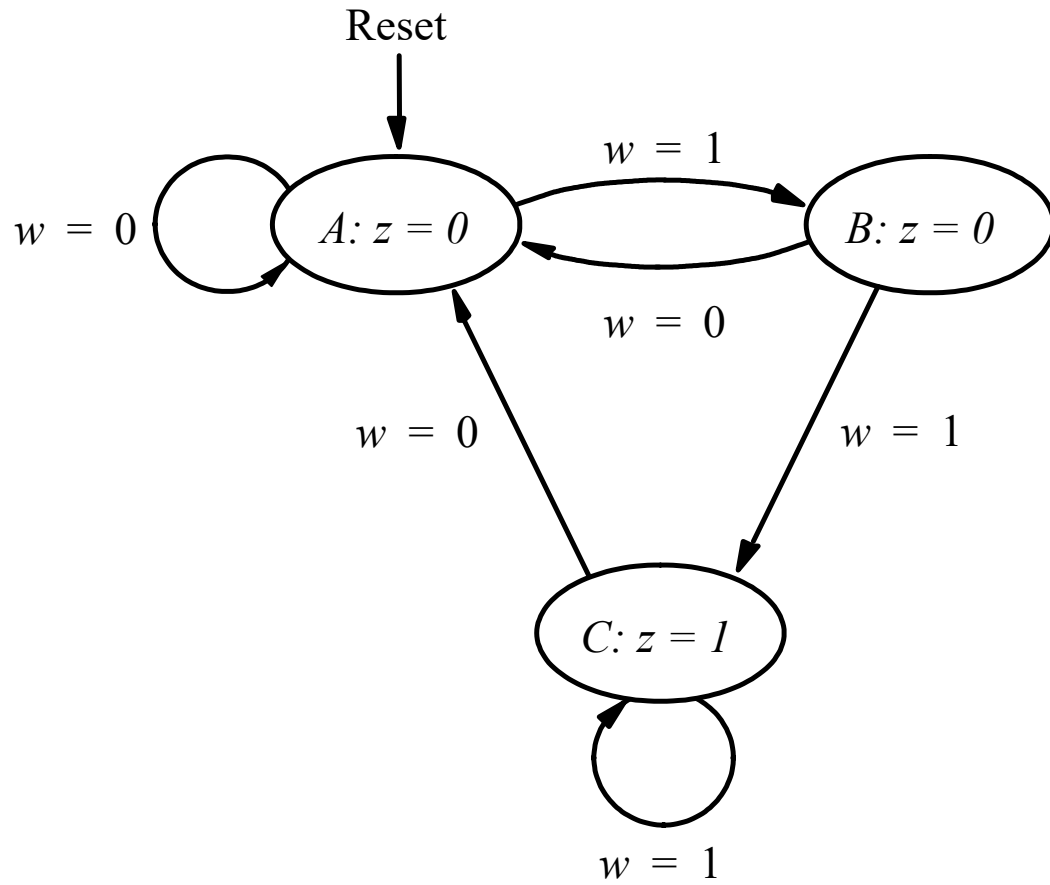


| Clockcycle: | t_0 | t_1 | t_2 | t_3 | t_4 | t_5 | t_6 | t_7 | t_8 | t_9 | t_{10} |
|-------------|-------|-------|-------|-------|-------|-------|-------|-------|-------|-------|----------|
| w : | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 1 | 0 | 1 |
| z : | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 1 | 0 |

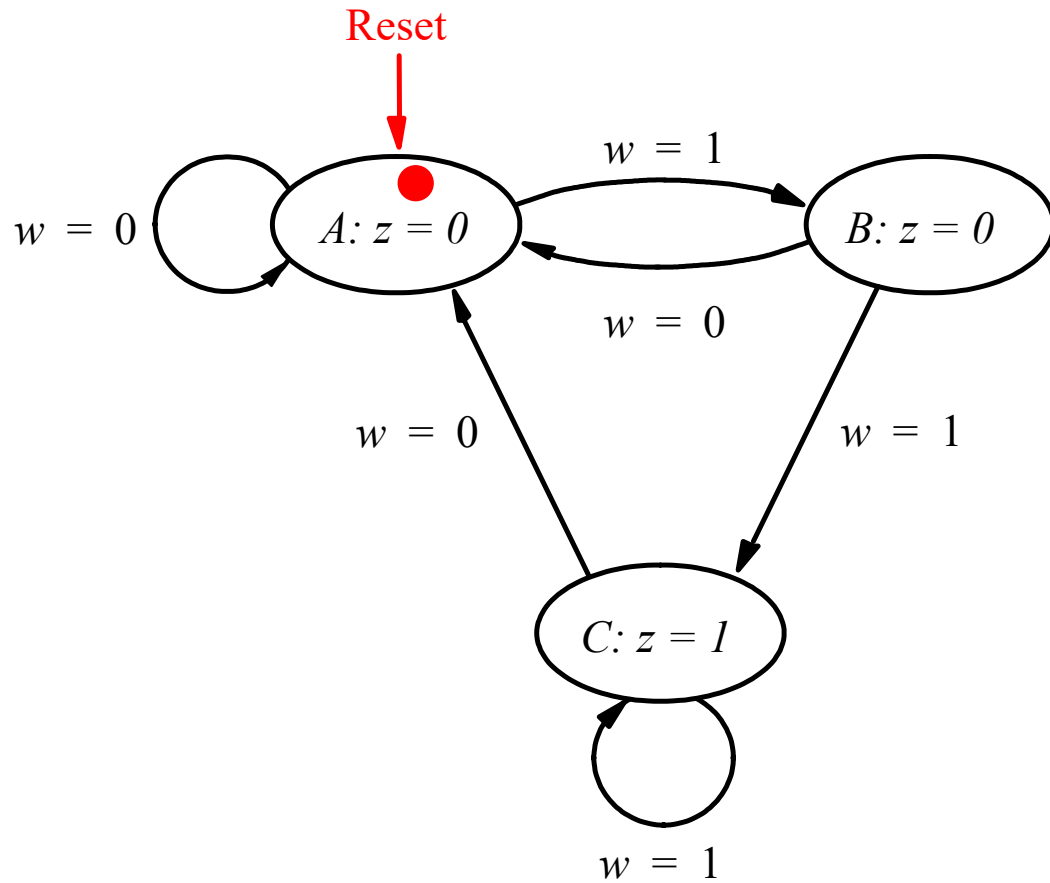


| Clockcycle: | t_0 | t_1 | t_2 | t_3 | t_4 | t_5 | t_6 | t_7 | t_8 | t_9 | t_{10} |
|-------------|-------|-------|-------|-------|-------|-------|-------|-------|-------|-------|----------|
| w : | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 1 | 0 | 1 |
| z : | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 1 | 0 |

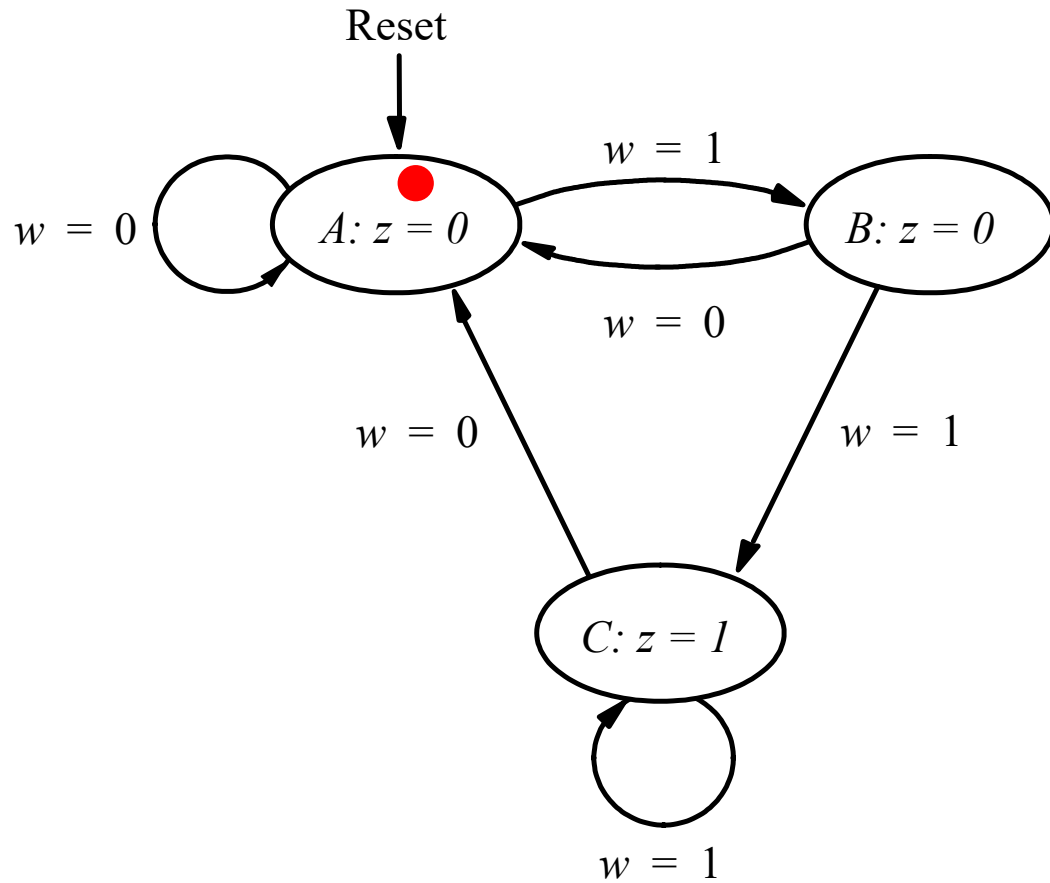


| Clockcycle: | t_0 | t_1 | t_2 | t_3 | t_4 | t_5 | t_6 | t_7 | t_8 | t_9 | t_{10} |
|-------------|-------|-------|-------|-------|-------|-------|-------|-------|-------|-------|----------|
| w : | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 1 | 0 | 1 |
| z : | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 1 | 0 |

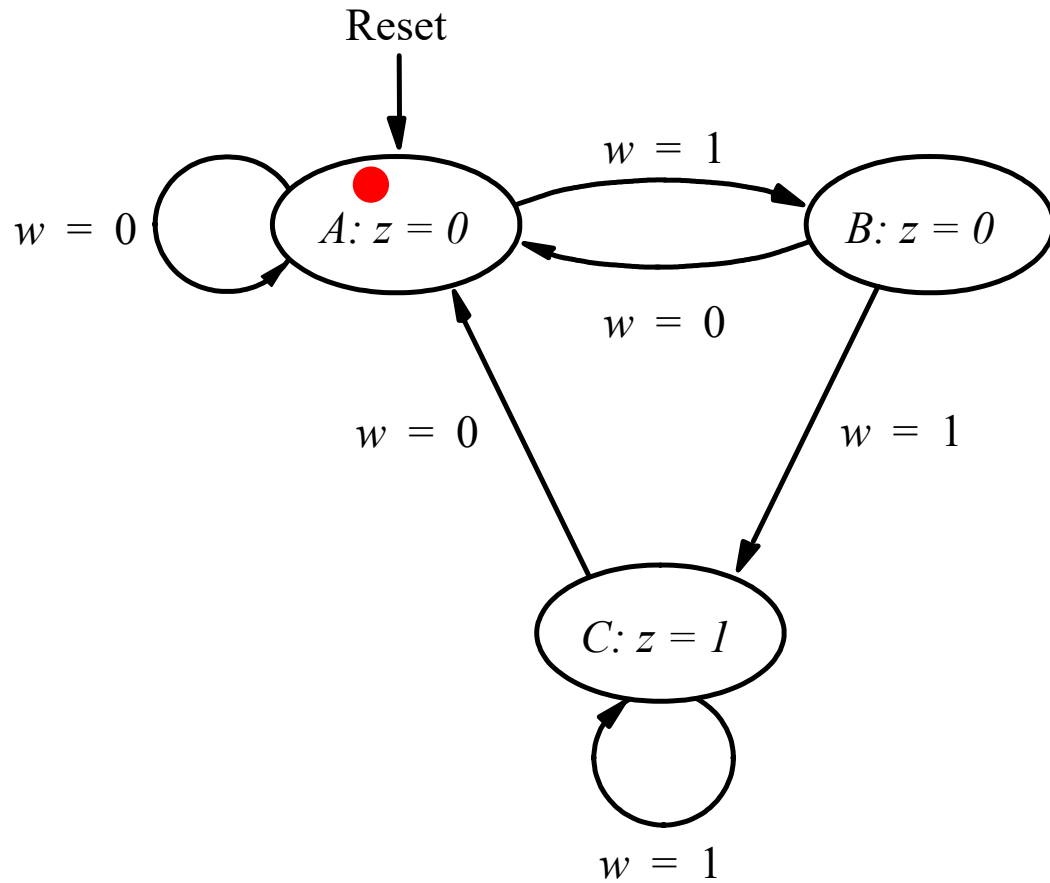


| Clockcycle: | t_0 | t_1 | t_2 | t_3 | t_4 | t_5 | t_6 | t_7 | t_8 | t_9 | t_{10} |
|-------------|-------|-------|-------|-------|-------|-------|-------|-------|-------|-------|----------|
| w : | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 1 | 0 | 1 |
| z : | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 1 | 0 |

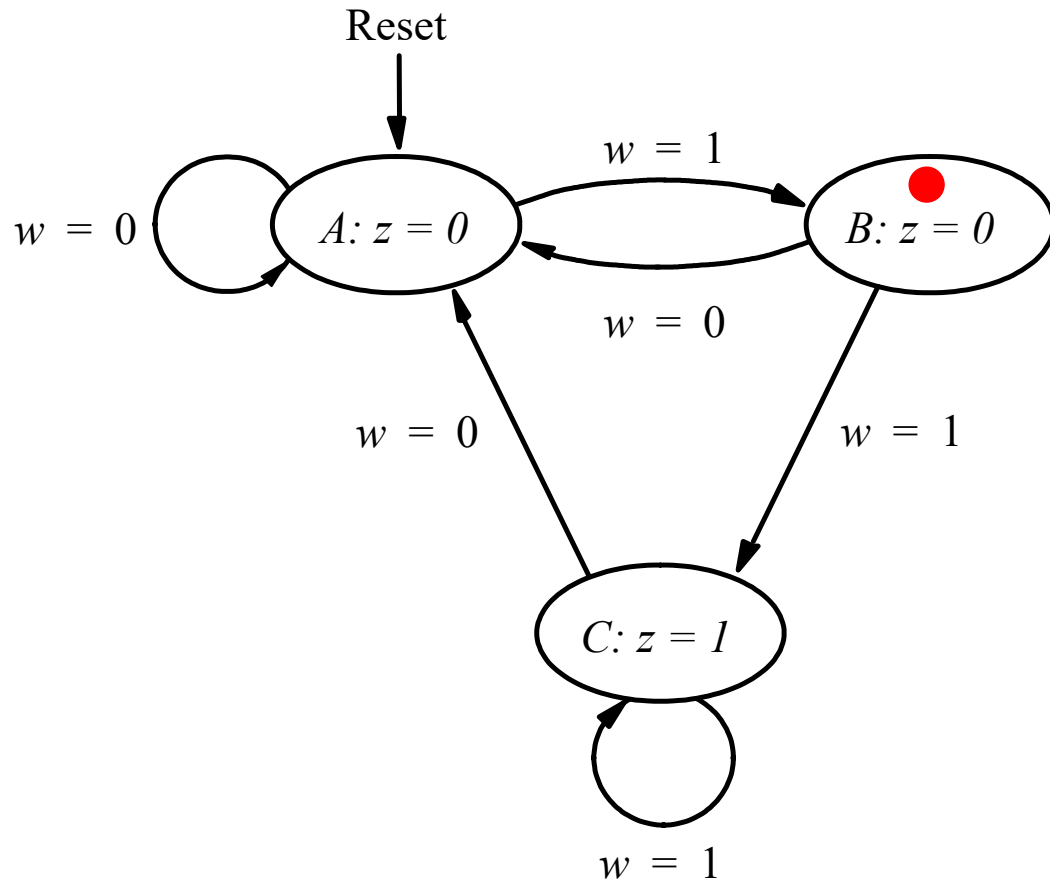


| Clockcycle: | t_0 | t_1 | t_2 | t_3 | t_4 | t_5 | t_6 | t_7 | t_8 | t_9 | t_{10} |
|-------------|-------|-------|-------|-------|-------|-------|-------|-------|-------|-------|----------|
| w : | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 1 | 0 | 1 |
| z : | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 1 | 0 |

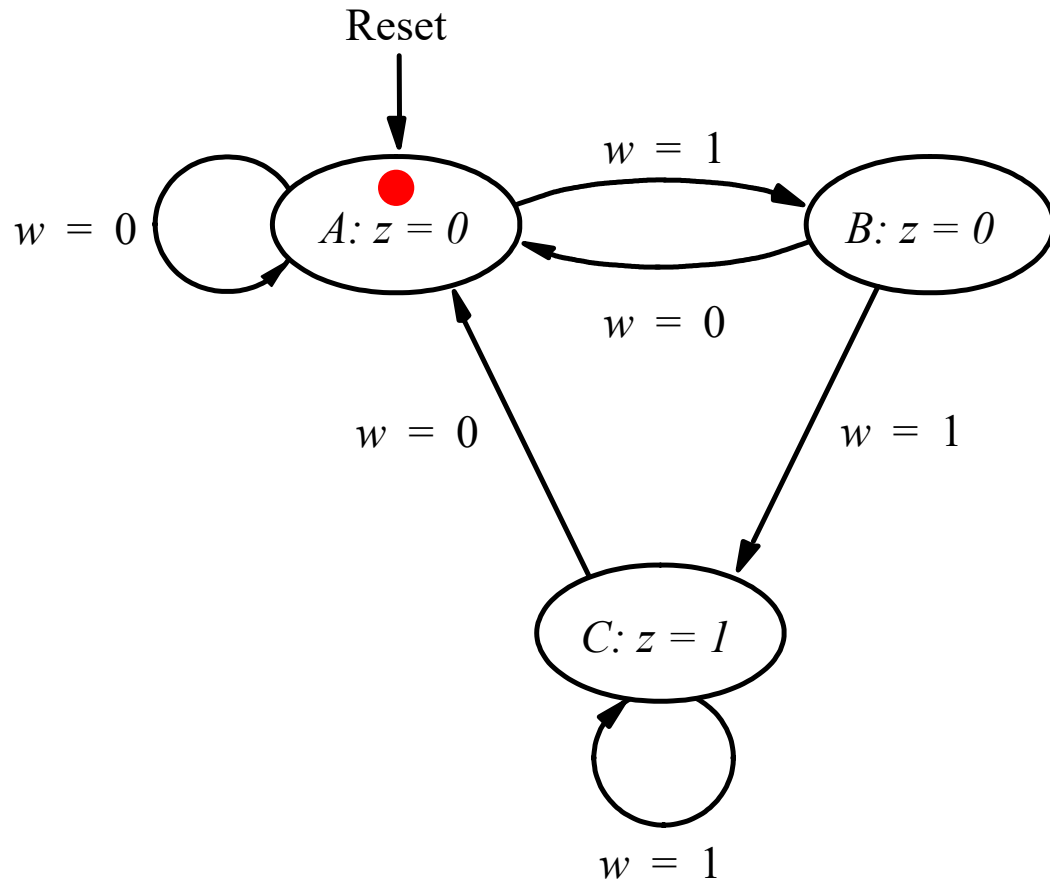


| Clockcycle: | t_0 | t_1 | t_2 | t_3 | t_4 | t_5 | t_6 | t_7 | t_8 | t_9 | t_{10} |
|-------------|-------|-------|-------|-------|-------|-------|-------|-------|-------|-------|----------|
| w : | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 1 | 0 | 1 |
| z : | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 1 | 0 |

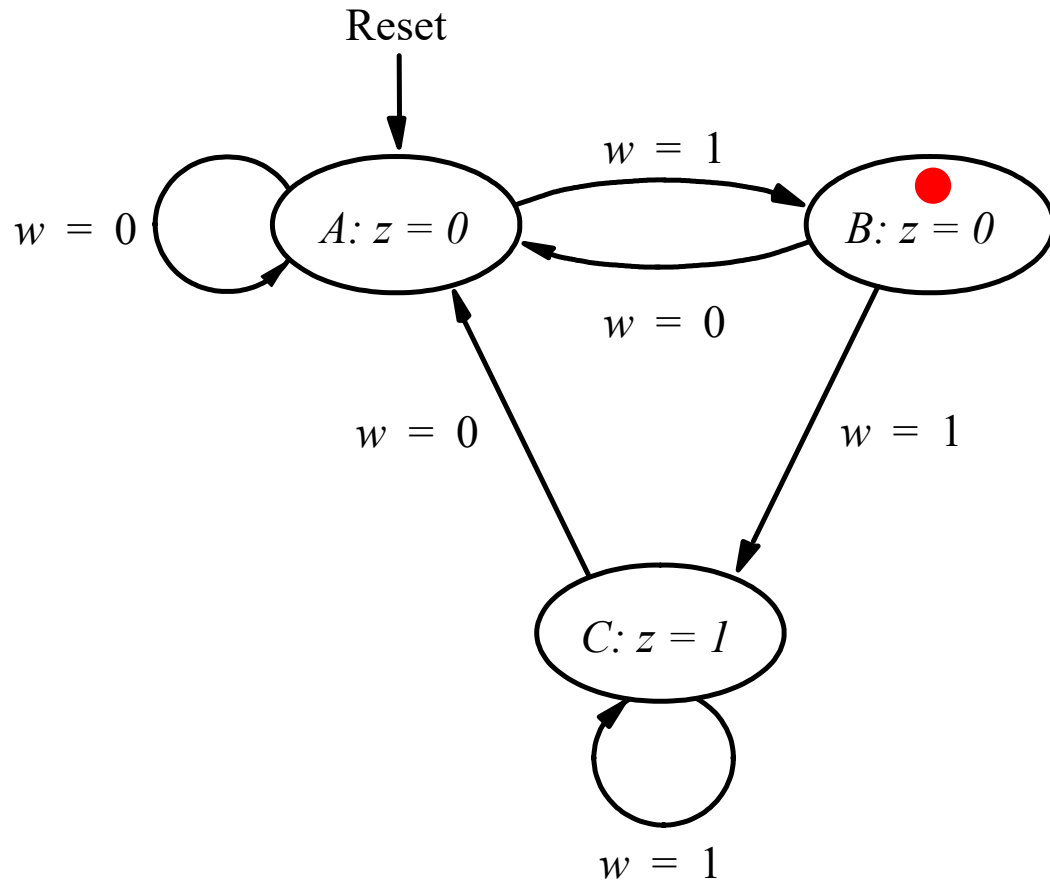


| Clockcycle: | t_0 | t_1 | t_2 | t_3 | t_4 | t_5 | t_6 | t_7 | t_8 | t_9 | t_{10} |
|-------------|-------|-------|-------|-------|-------|-------|-------|-------|-------|-------|----------|
| w : | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 1 | 0 | 1 |
| z : | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 1 | 0 |

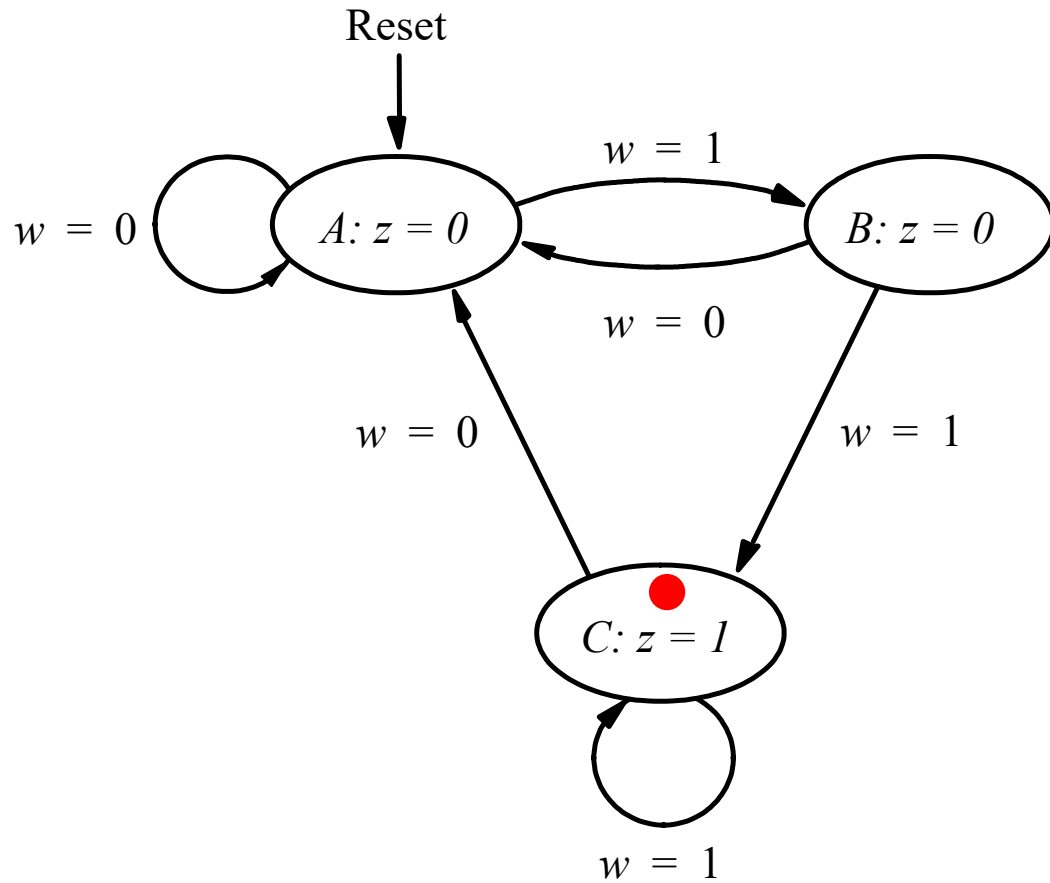


| Clockcycle: | t_0 | t_1 | t_2 | t_3 | t_4 | t_5 | t_6 | t_7 | t_8 | t_9 | t_{10} |
|-------------|-------|-------|-------|-------|-------|-------|-------|-------|-------|-------|----------|
| w : | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 1 | 0 | 1 |
| z : | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 1 | 0 |

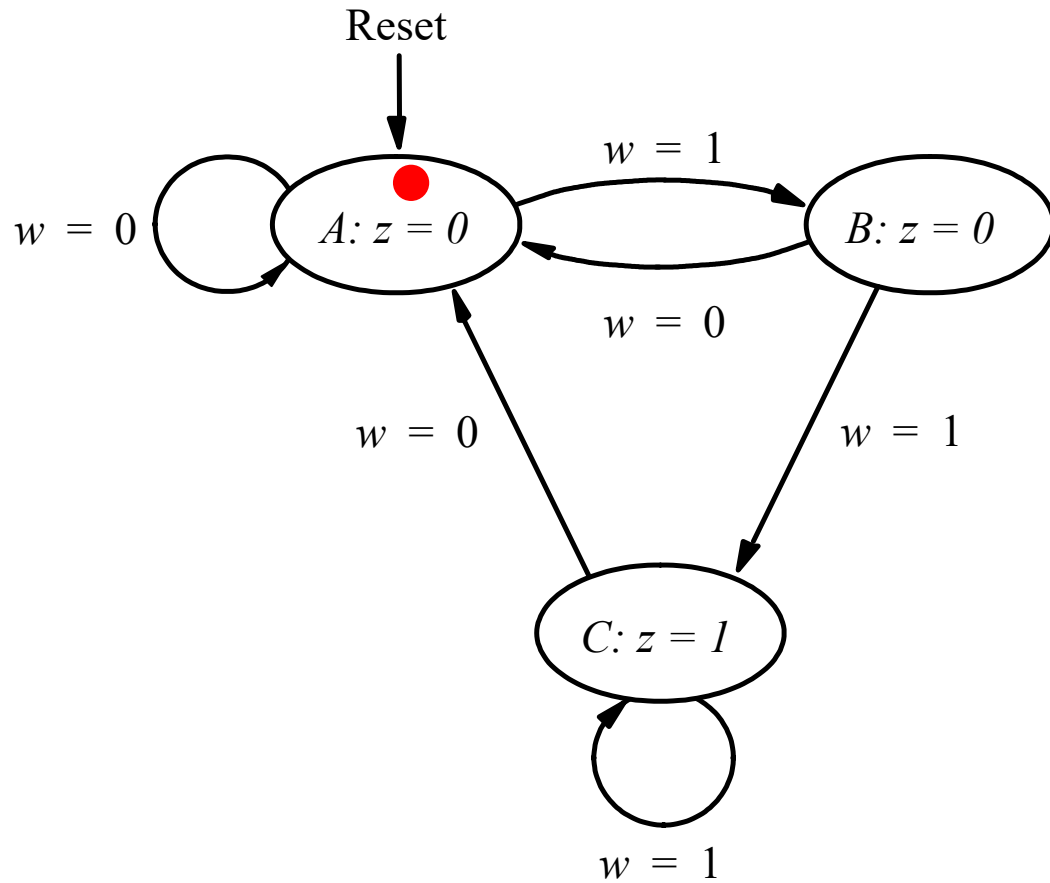


| Clockcycle: | t_0 | t_1 | t_2 | t_3 | t_4 | t_5 | t_6 | t_7 | t_8 | t_9 | t_{10} |
|-------------|-------|-------|-------|-------|-------|-------|-------|-------|-------|-------|----------|
| w : | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 1 | 0 | 1 |
| z : | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 1 | 0 |

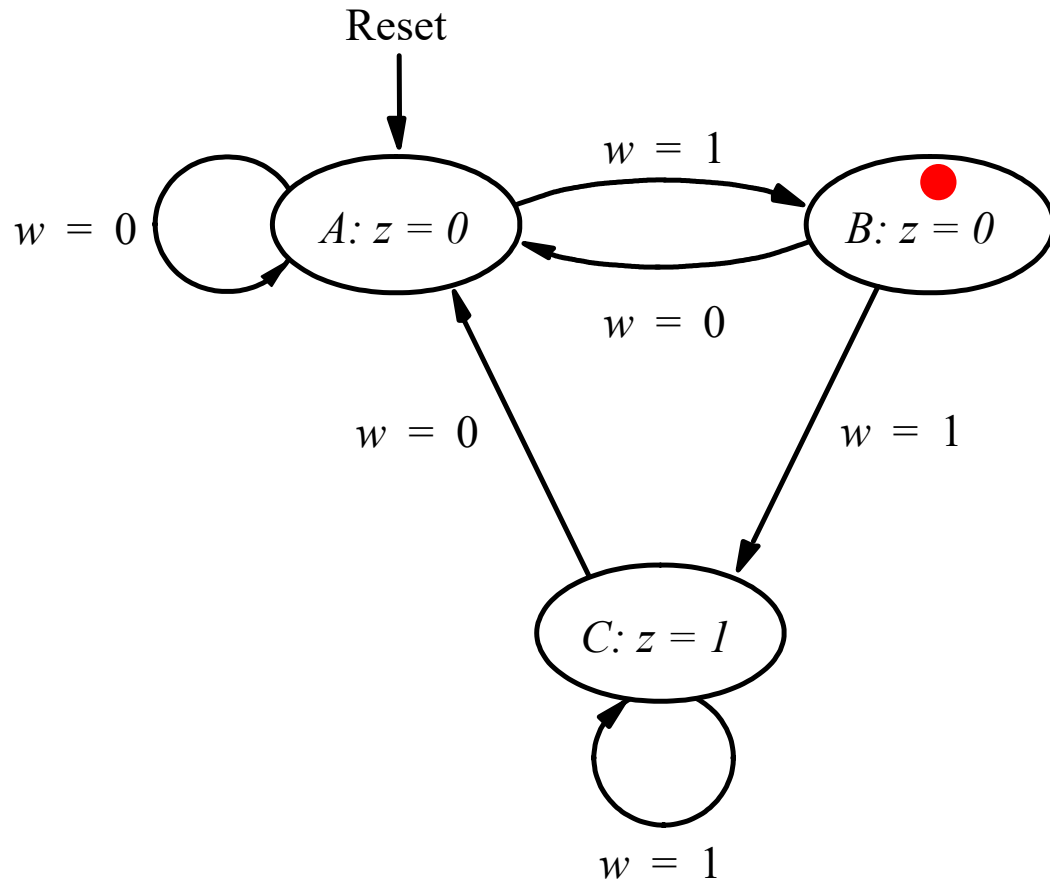


| Clockcycle: | t_0 | t_1 | t_2 | t_3 | t_4 | t_5 | t_6 | t_7 | t_8 | t_9 | t_{10} |
|-------------|-------|-------|-------|-------|-------|-------|-------|-------|-------|-------|----------|
| w : | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 1 | 0 | 1 |
| z : | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 1 | 0 |

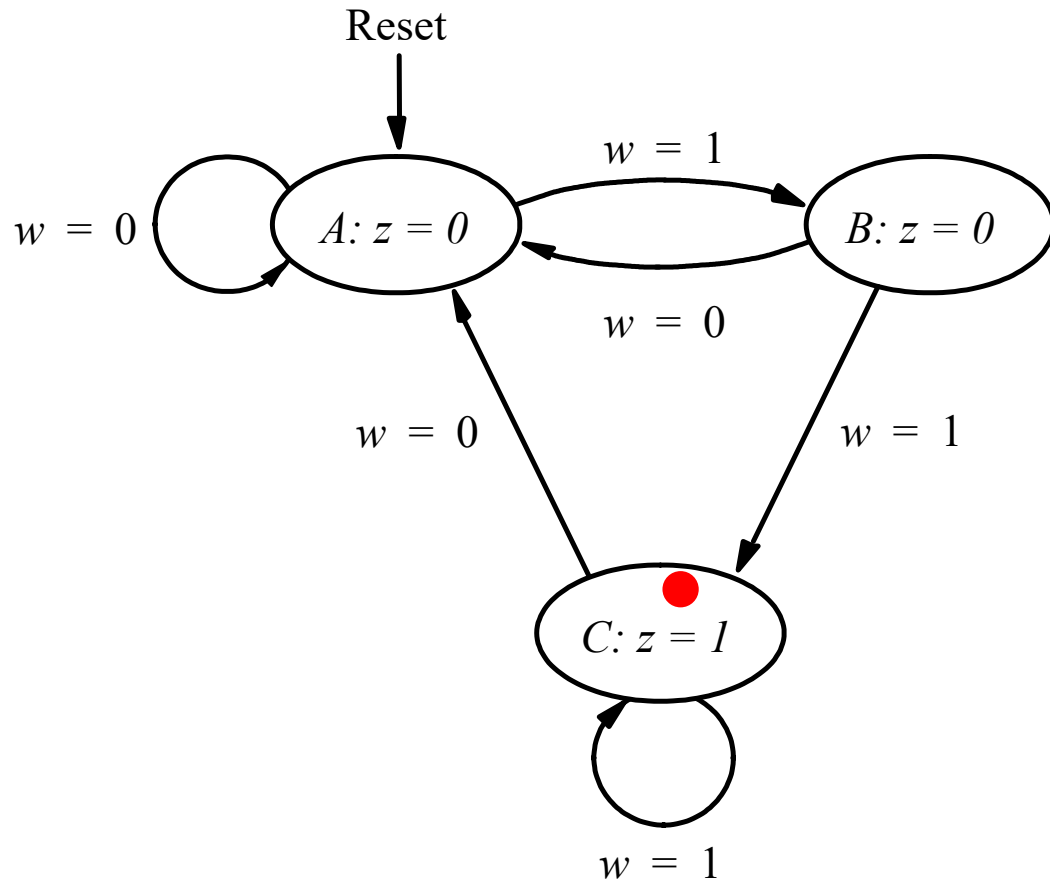

| Clockcycle: | t_0 | t_1 | t_2 | t_3 | t_4 | t_5 | t_6 | t_7 | t_8 | t_9 | t_{10} |
|-------------|-------|-------|-------|-------|-------|-------|-------|-------|-------|-------|----------|
| w : | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 1 | 0 | 1 |
| z : | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 1 | 0 |

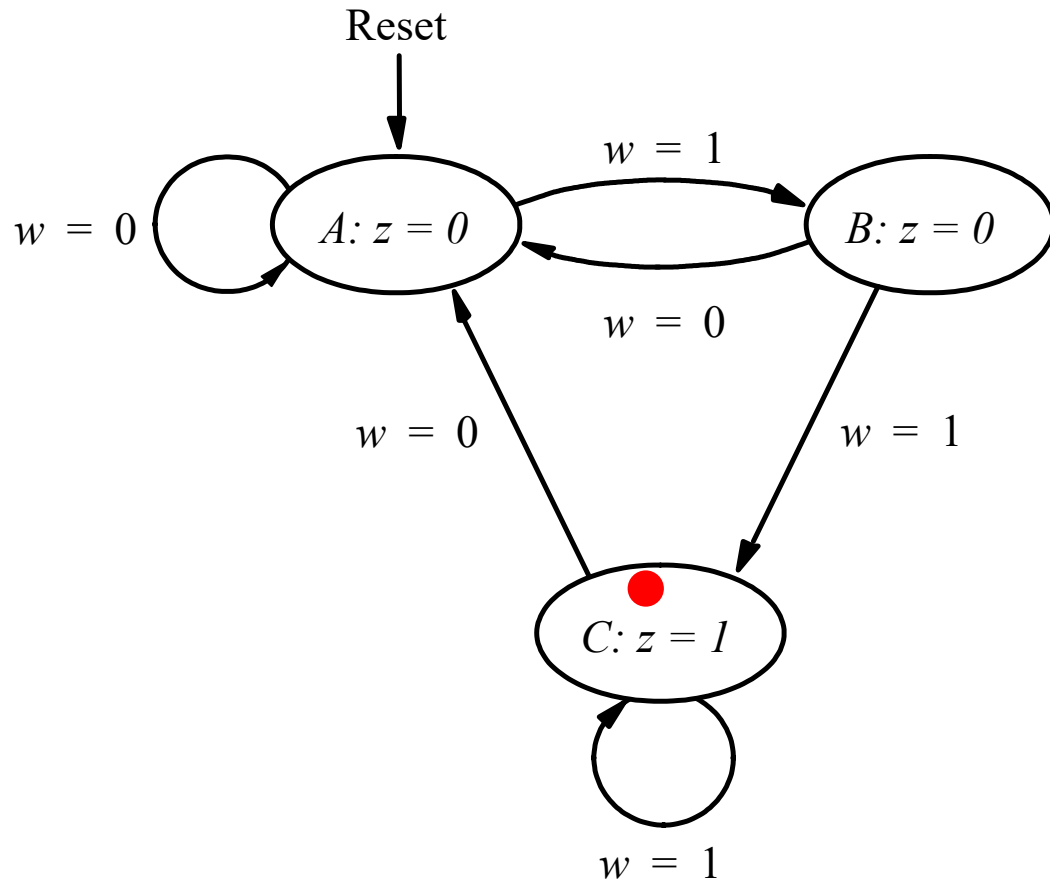


| Clockcycle: | t_0 | t_1 | t_2 | t_3 | t_4 | t_5 | t_6 | t_7 | t_8 | t_9 | t_{10} |
|-------------|-------|-------|-------|-------|-------|-------|-------|-------|-------|-------|----------|
| w : | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 1 | 0 | 1 |
| z : | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 1 | 0 |

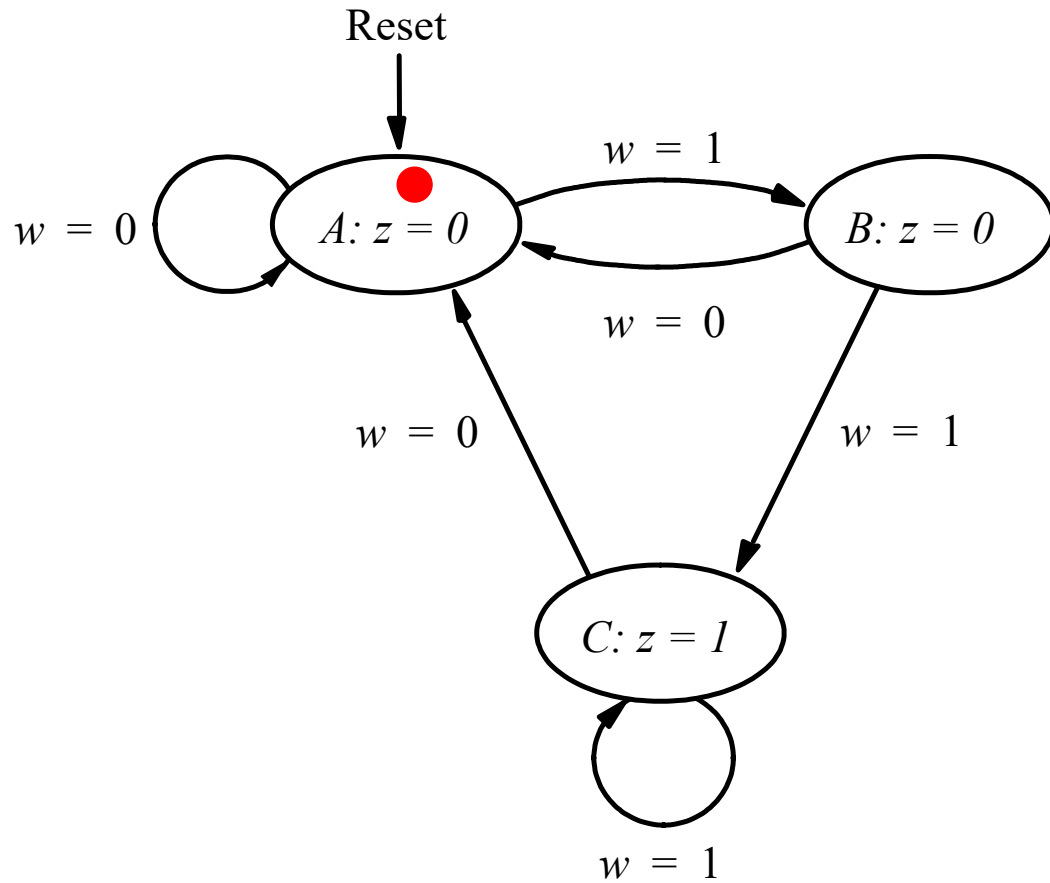


| Clockcycle: | t_0 | t_1 | t_2 | t_3 | t_4 | t_5 | t_6 | t_7 | t_8 | t_9 | t_{10} |
|-------------|-------|-------|-------|-------|-------|-------|-------|-------|-------|-------|----------|
| w : | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 1 | 0 | 1 |
| z : | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 1 | 0 |

Inferring the States

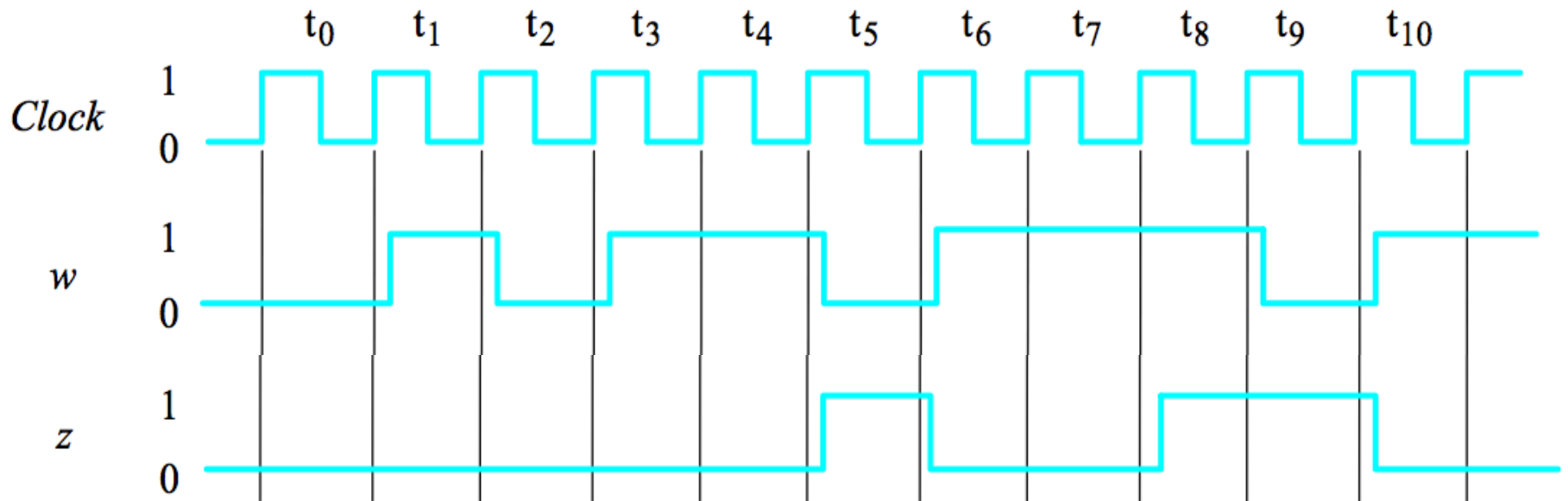


| Clockcycle: | t_0 | t_1 | t_2 | t_3 | t_4 | t_5 | t_6 | t_7 | t_8 | t_9 | t_{10} |
|-------------|-------|-------|-------|-------|-------|-------|-------|-------|-------|-------|----------|
| <i>w</i> : | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 1 | 0 | 1 |
| <i>z</i> : | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 1 | 0 |

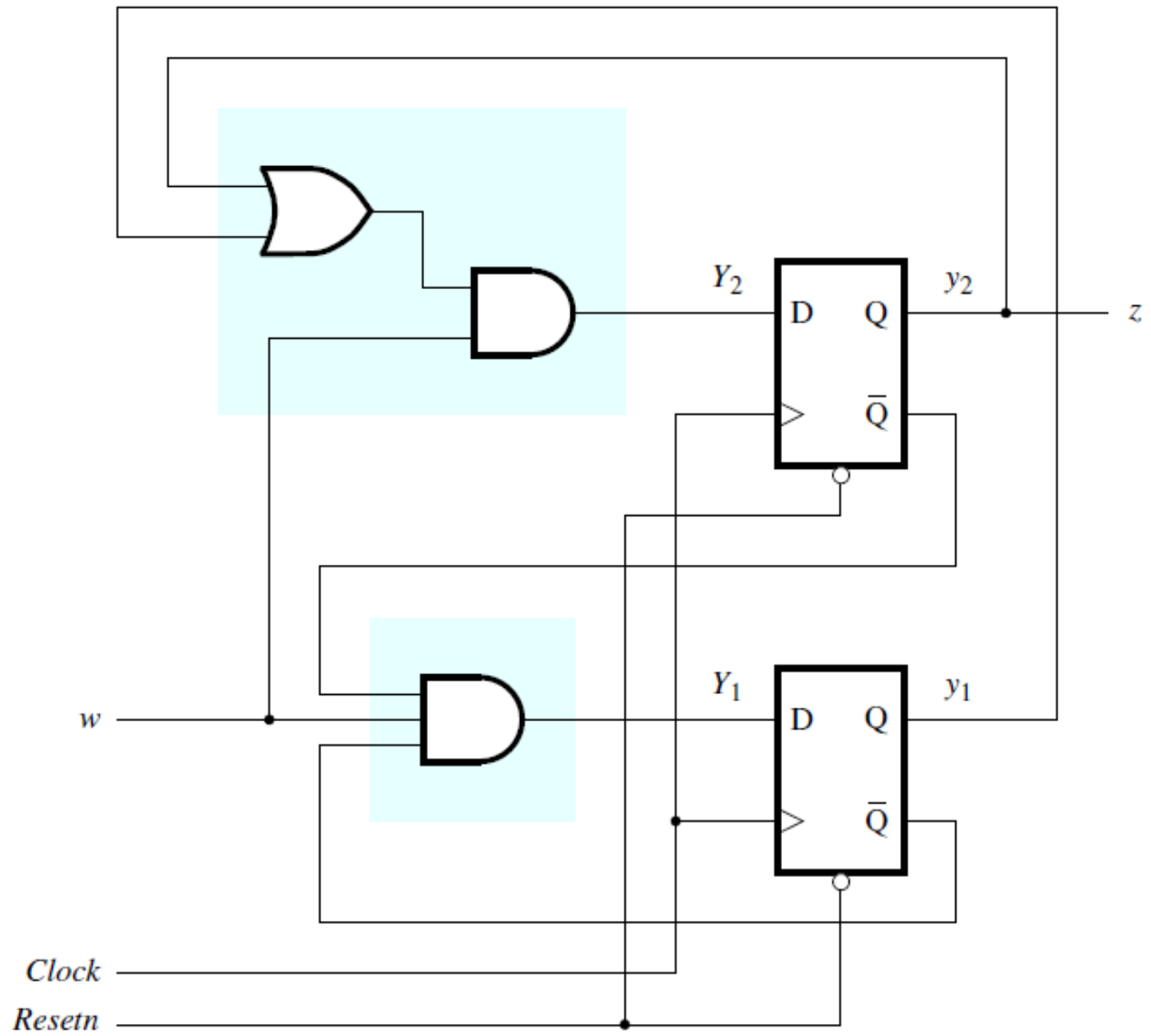


[Figure 6.8 from the textbook]

The New and Improved Circuit Diagram

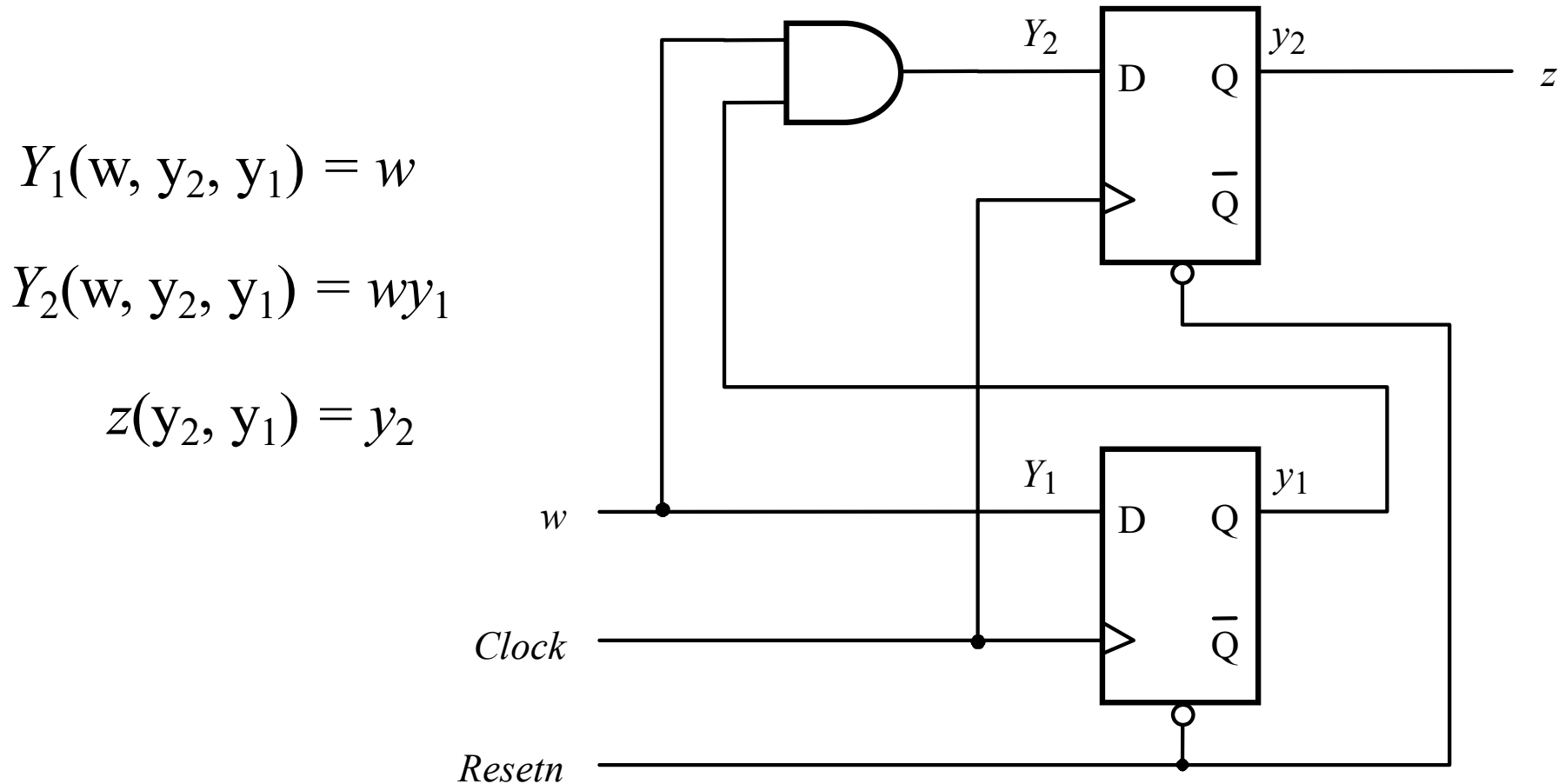


Mealy Machine Implementation

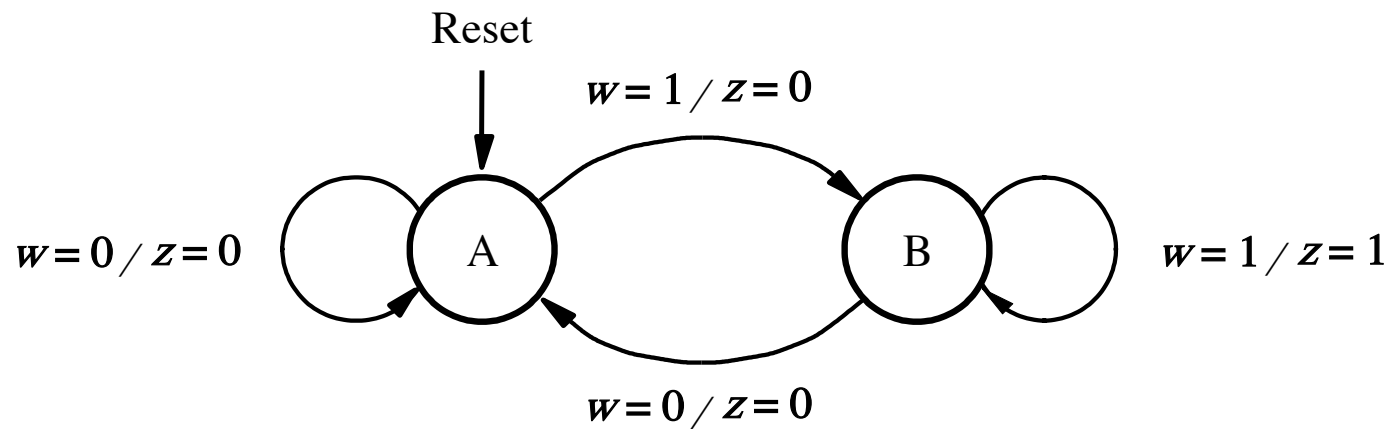State diagram of an FSM that realizes the task




Let's Do a Simulation

| Clock cycle: | t_0 | t_1 | t_2 | t_3 | t_4 | t_5 | t_6 | t_7 | t_8 | t_9 | t_{10} |
|--------------|----------------------------|-------|-------|-------|-------|-------|-------|-------|-------|-------|----------|
| input w : | <input type="checkbox"/> 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 1 | 0 | 1 |
| output z : | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 1 | 0 | 0 |

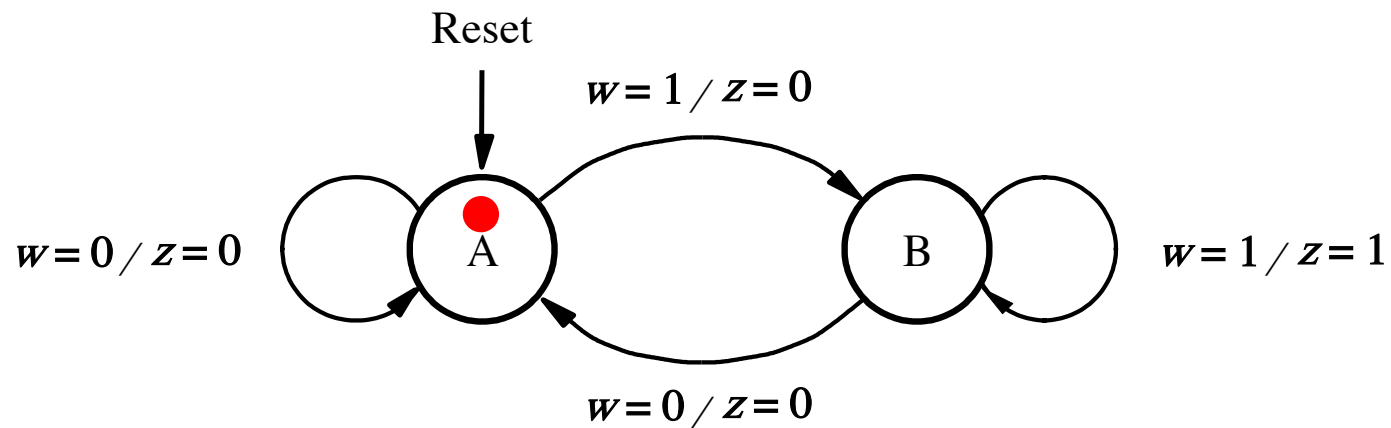


Let's Do a Simulation

| Clock cycle: | t_0 | t_1 | t_2 | t_3 | t_4 | t_5 | t_6 | t_7 | t_8 | t_9 | t_{10} |
|---------------------|-------|-------|-------|-------|-------|-------|-------|-------|-------|-------|----------|
| input w : | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 1 | 0 | 1 |
| output z : | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 1 | 0 | 0 |

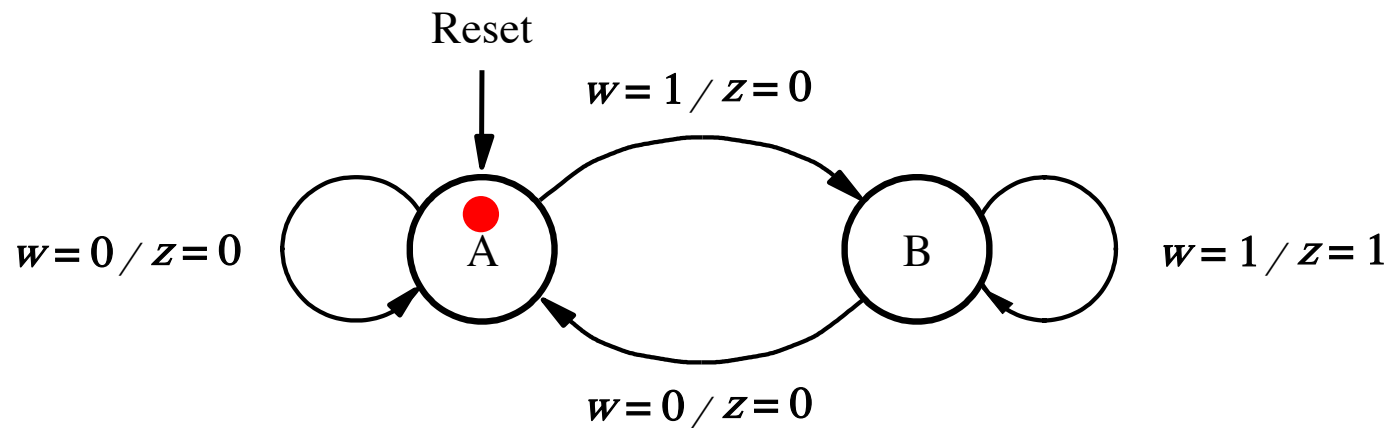


Let's Do a Simulation

| Clock cycle: | t_0 | t_1 | t_2 | t_3 | t_4 | t_5 | t_6 | t_7 | t_8 | t_9 | t_{10} |
|---------------------|-------|-------|-------|-------|-------|-------|-------|-------|-------|-------|----------|
| input w : | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 1 | 0 | 1 |
| output z : | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 1 | 0 | 0 |

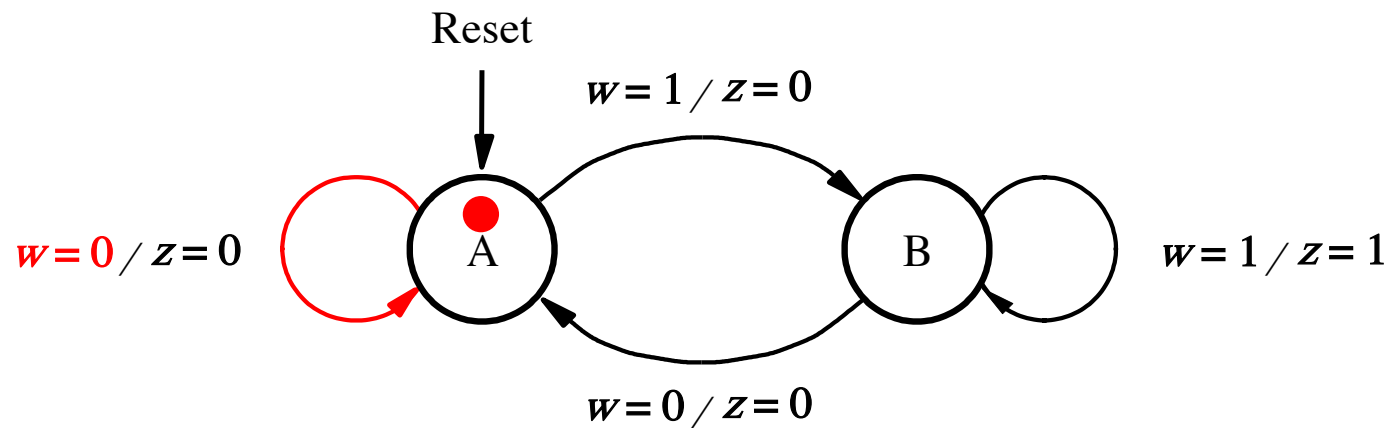


Let's Do a Simulation

| Clock cycle: | t_0 | t_1 | t_2 | t_3 | t_4 | t_5 | t_6 | t_7 | t_8 | t_9 | t_{10} |
|--------------|-------|-------|-------|-------|-------|-------|-------|-------|-------|-------|----------|
| input w : | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 1 | 0 | 1 |
| output z : | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 1 | 0 | 0 |

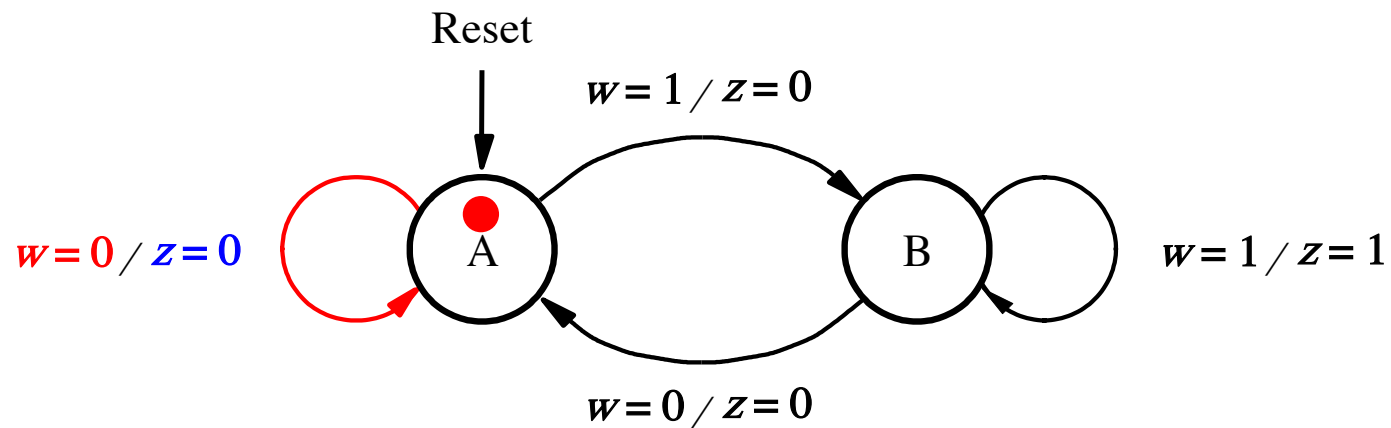


Let's Do a Simulation

| Clock cycle: | t_0 | t_1 | t_2 | t_3 | t_4 | t_5 | t_6 | t_7 | t_8 | t_9 | t_{10} |
|---------------------|-------|-------|-------|-------|-------|-------|-------|-------|-------|-------|----------|
| input w : | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 1 | 0 | 1 |
| output z : | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 1 | 0 | 0 |

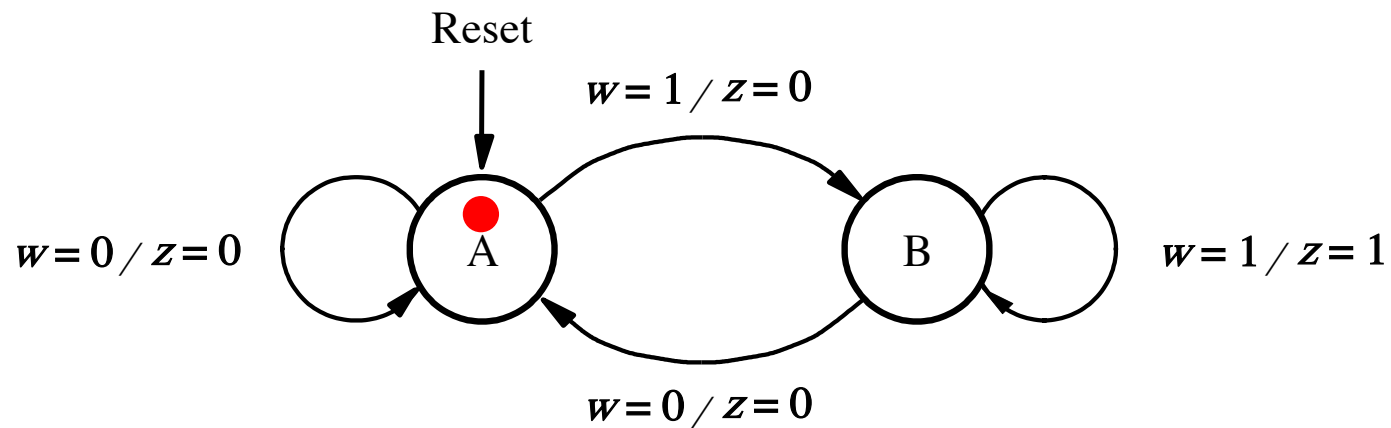


Let's Do a Simulation

| Clock cycle: | t_0 | t_1 | t_2 | t_3 | t_4 | t_5 | t_6 | t_7 | t_8 | t_9 | t_{10} |
|---------------------|-------|-------|-------|-------|-------|-------|-------|-------|-------|-------|----------|
| input w : | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 1 | 0 | 1 |
| output z : | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 1 | 0 | 0 |

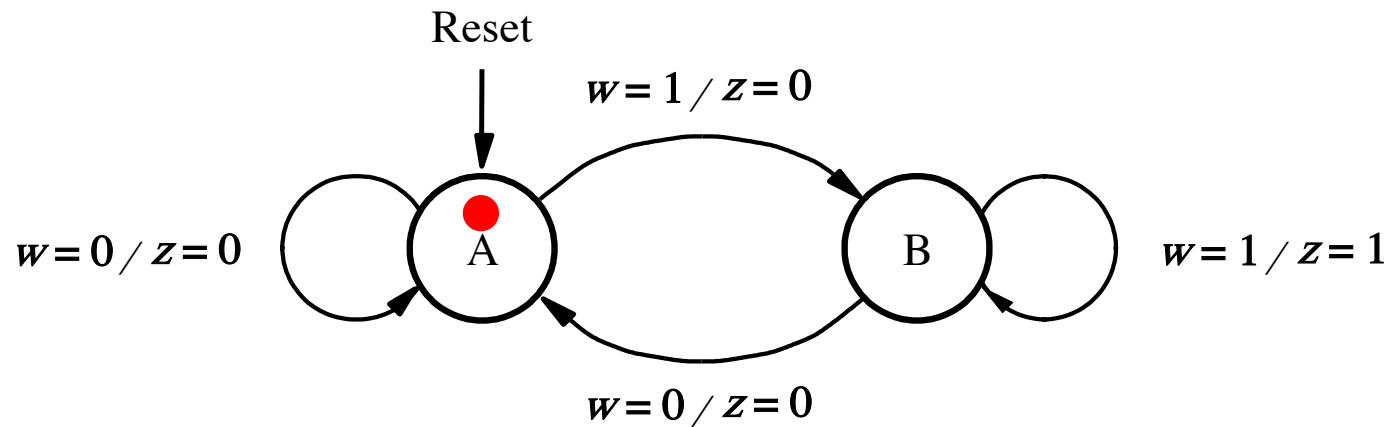


Let's Do a Simulation

| Clock cycle: | t_0 | t_1 | t_2 | t_3 | t_4 | t_5 | t_6 | t_7 | t_8 | t_9 | t_{10} |
|---------------------|-------|-------|-------|-------|-------|-------|-------|-------|-------|-------|----------|
| input w : | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 1 | 0 | 1 |
| output z : | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 1 | 0 | 0 |

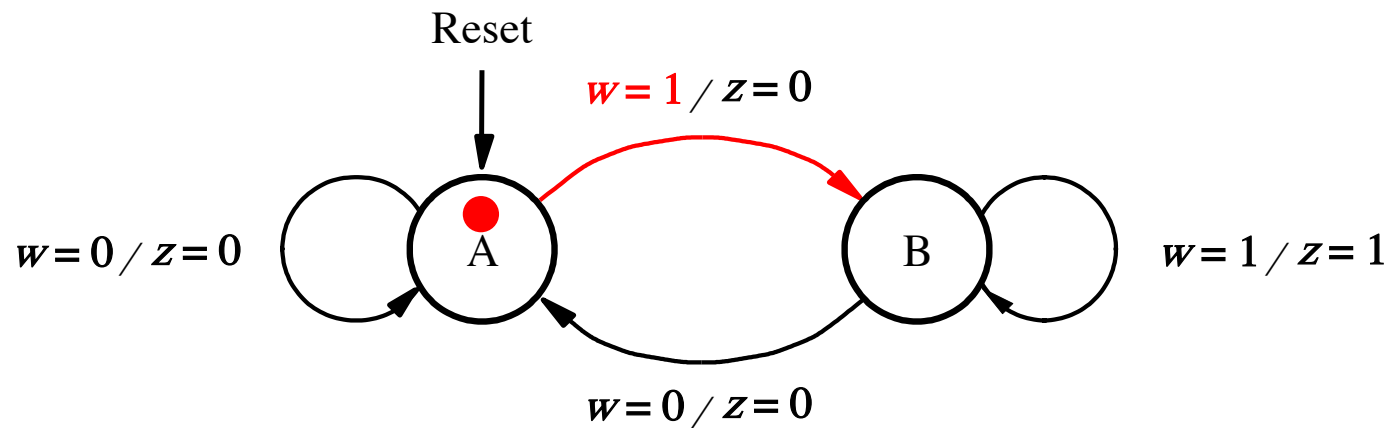


Let's Do a Simulation

| Clock cycle: | t_0 | t_1 | t_2 | t_3 | t_4 | t_5 | t_6 | t_7 | t_8 | t_9 | t_{10} |
|---------------------|-------|-------|-------|-------|-------|-------|-------|-------|-------|-------|----------|
| input w : | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 1 | 0 | 1 |
| output z : | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 1 | 0 | 0 |

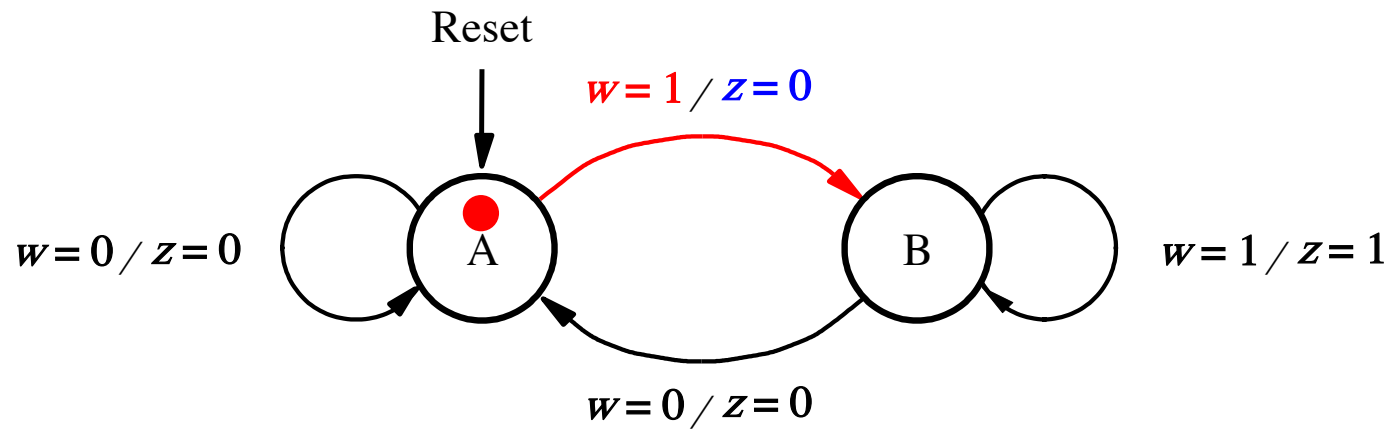


Let's Do a Simulation

| Clock cycle: | t_0 | t_1 | t_2 | t_3 | t_4 | t_5 | t_6 | t_7 | t_8 | t_9 | t_{10} |
|---------------------|-------|-------|-------|-------|-------|-------|-------|-------|-------|-------|----------|
| input w : | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 1 | 0 | 1 |
| output z : | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 1 | 0 | 0 |

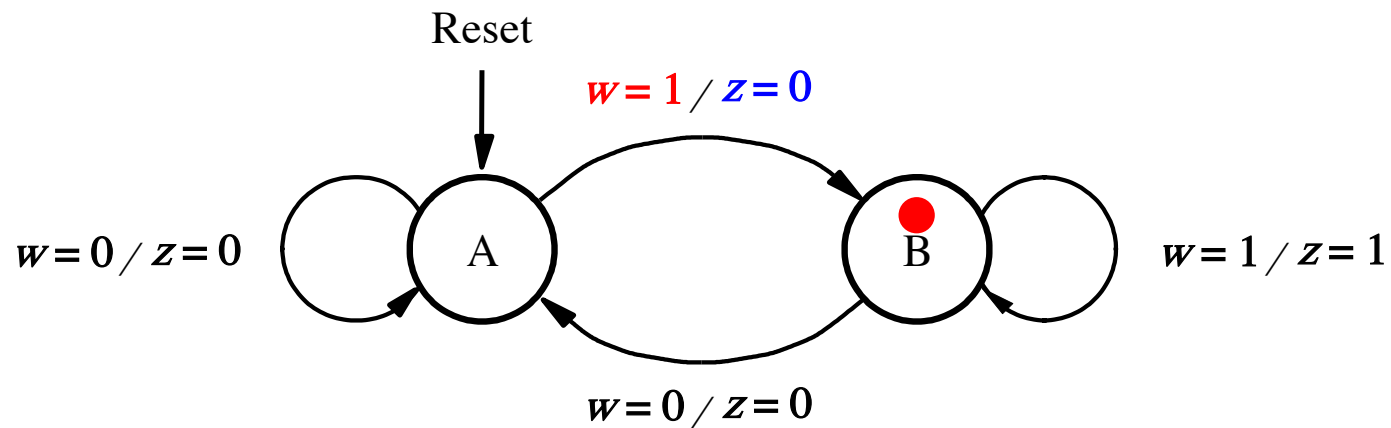


Let's Do a Simulation

| Clock cycle: | t_0 | t_1 | t_2 | t_3 | t_4 | t_5 | t_6 | t_7 | t_8 | t_9 | t_{10} |
|---------------------|-------|-------|-------|-------|-------|-------|-------|-------|-------|-------|----------|
| input w : | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 1 | 0 | 1 |
| output z : | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 1 | 0 | 0 |

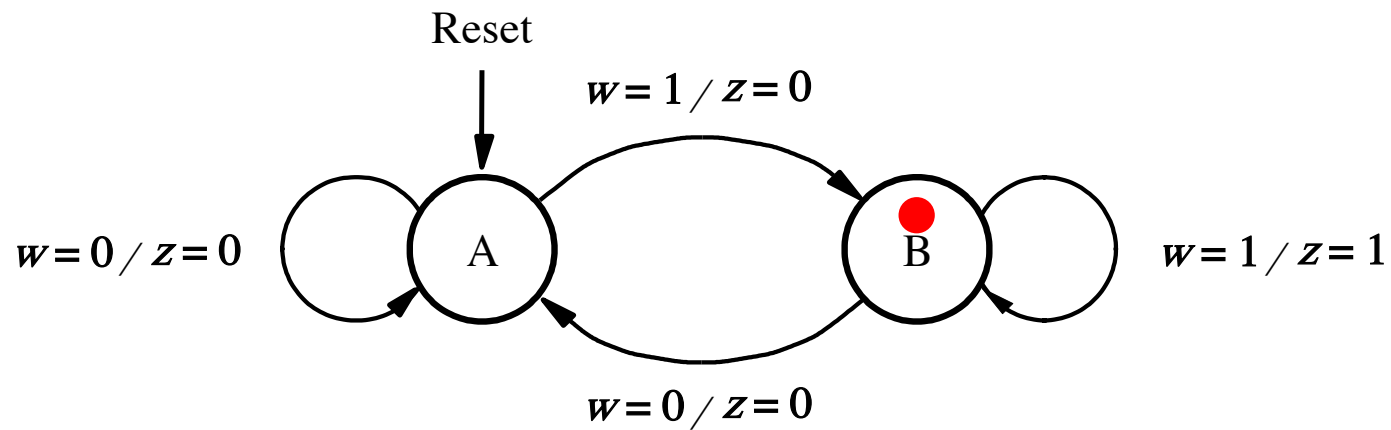


Let's Do a Simulation

| Clock cycle: | t_0 | t_1 | t_2 | t_3 | t_4 | t_5 | t_6 | t_7 | t_8 | t_9 | t_{10} |
|---------------------|-------|-------|-------|-------|-------|-------|-------|-------|-------|-------|----------|
| input w : | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 1 | 0 | 1 |
| output z : | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 1 | 0 | 0 |

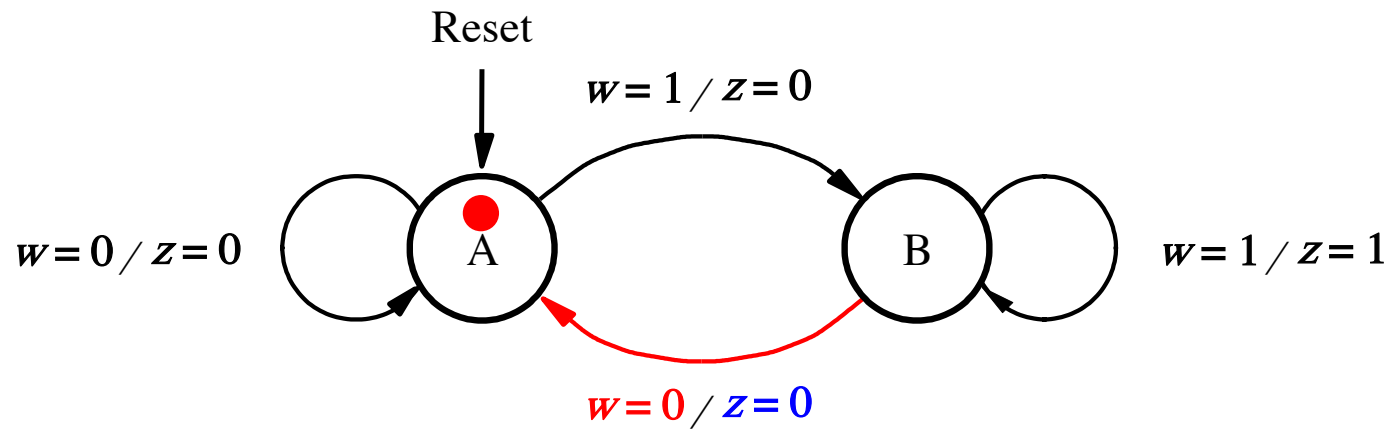


Let's Do a Simulation

| Clock cycle: | t_0 | t_1 | t_2 | t_3 | t_4 | t_5 | t_6 | t_7 | t_8 | t_9 | t_{10} |
|---------------------|-------|-------|-------|-------|-------|-------|-------|-------|-------|-------|----------|
| input w : | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 1 | 0 | 1 |
| output z : | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 1 | 0 | 0 |

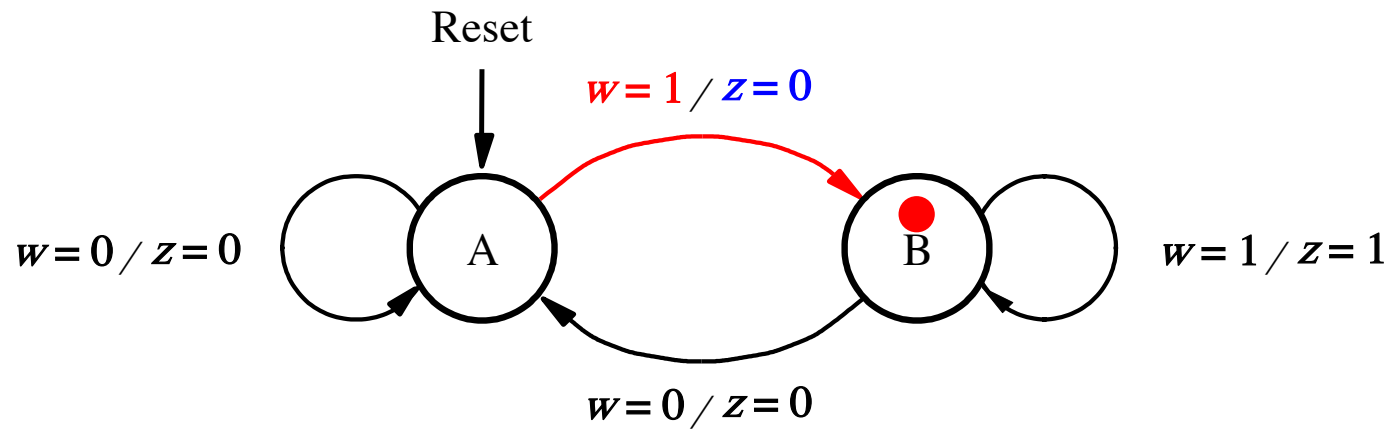


Let's Do a Simulation

| Clock cycle: | t_0 | t_1 | t_2 | t_3 | t_4 | t_5 | t_6 | t_7 | t_8 | t_9 | t_{10} |
|---------------------|-------|-------|-------|-------|-------|-------|-------|-------|-------|-------|----------|
| input w : | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 1 | 0 | 1 |
| output z : | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 1 | 0 | 0 |

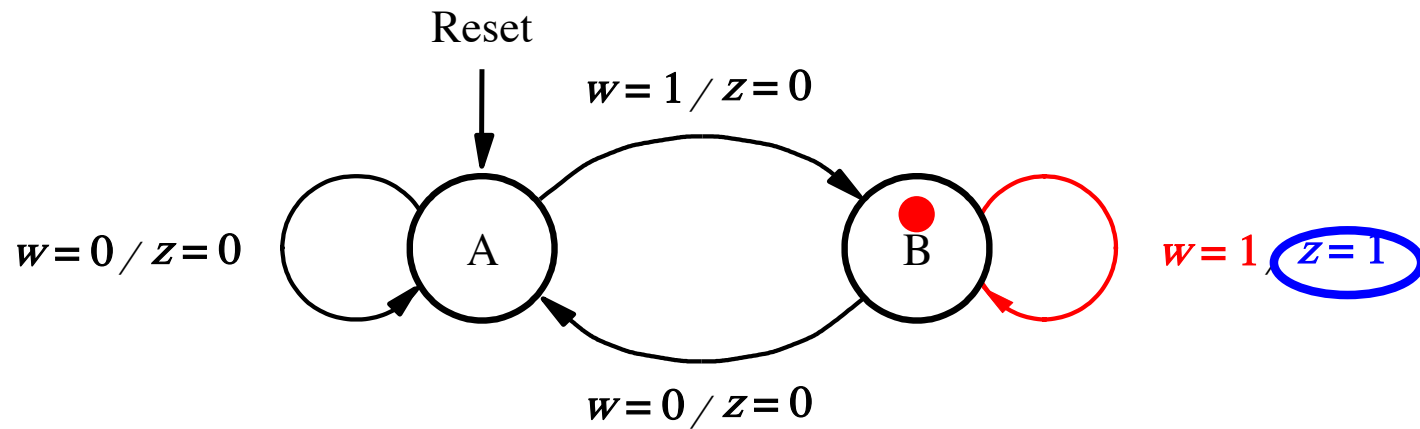


Let's Do a Simulation

| Clock cycle: | t_0 | t_1 | t_2 | t_3 | t_4 | t_5 | t_6 | t_7 | t_8 | t_9 | t_{10} |
|---------------------|-------|-------|-------|-------|-------|-------|-------|-------|-------|-------|----------|
| input w : | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 1 | 0 | 1 |
| output z : | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 1 | 0 | 0 |

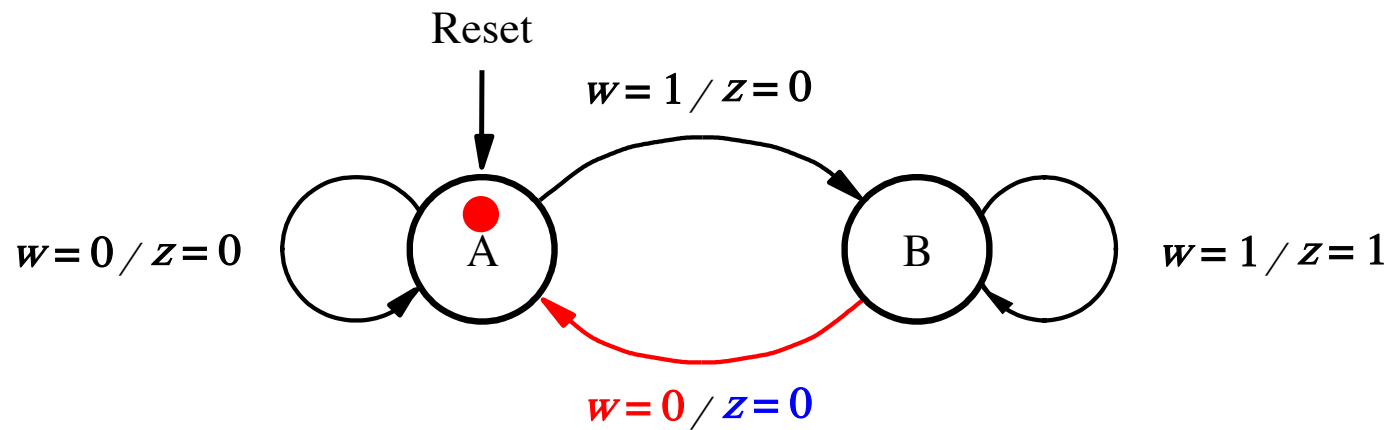


Let's Do a Simulation

| Clock cycle: | t_0 | t_1 | t_2 | t_3 | t_4 | t_5 | t_6 | t_7 | t_8 | t_9 | t_{10} |
|---------------------|-------|-------|-------|-------|-------|-------|-------|-------|-------|-------|----------|
| input w : | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 1 | 0 | 1 |
| output z : | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 1 | 0 | 0 |

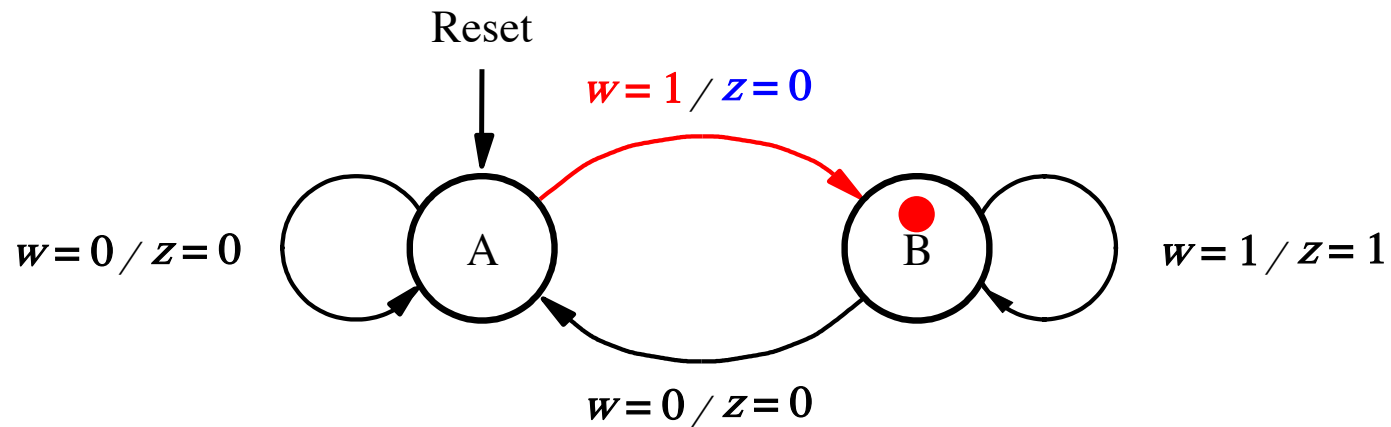


Let's Do a Simulation

| Clock cycle: | t_0 | t_1 | t_2 | t_3 | t_4 | t_5 | t_6 | t_7 | t_8 | t_9 | t_{10} |
|---------------------|-------|-------|-------|-------|-------|-------|-------|-------|-------|-------|----------|
| input w : | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 1 | 0 | 1 |
| output z : | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 1 | 0 | 0 |

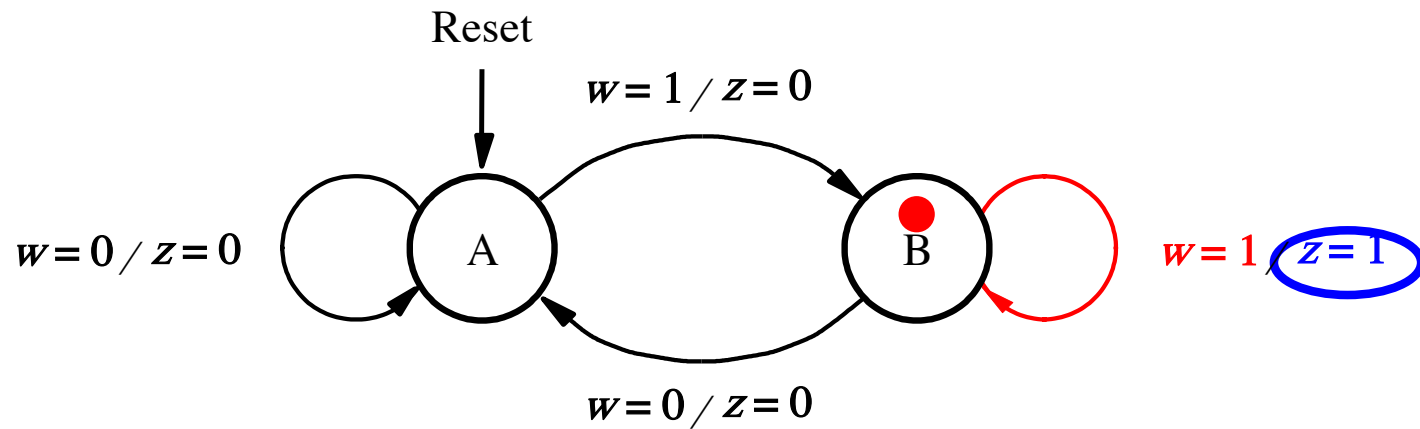


Let's Do a Simulation

| Clock cycle: | t_0 | t_1 | t_2 | t_3 | t_4 | t_5 | t_6 | t_7 | t_8 | t_9 | t_{10} |
|---------------------|-------|-------|-------|-------|-------|-------|-------|-------|-------|-------|----------|
| input w : | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 1 | 0 | 1 |
| output z : | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 1 | 0 | 0 |

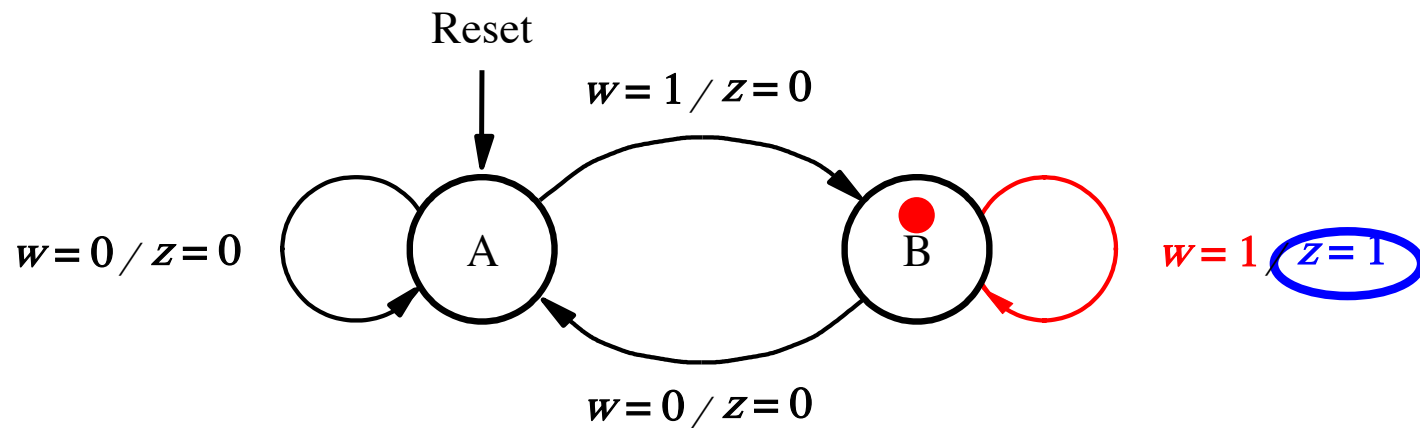


Let's Do a Simulation

| Clock cycle: | t_0 | t_1 | t_2 | t_3 | t_4 | t_5 | t_6 | t_7 | t_8 | t_9 | t_{10} |
|---------------------|-------|-------|-------|-------|-------|-------|-------|-------|-------|-------|----------|
| input w : | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 1 | 0 | 1 |
| output z : | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 1 | 0 | 0 |

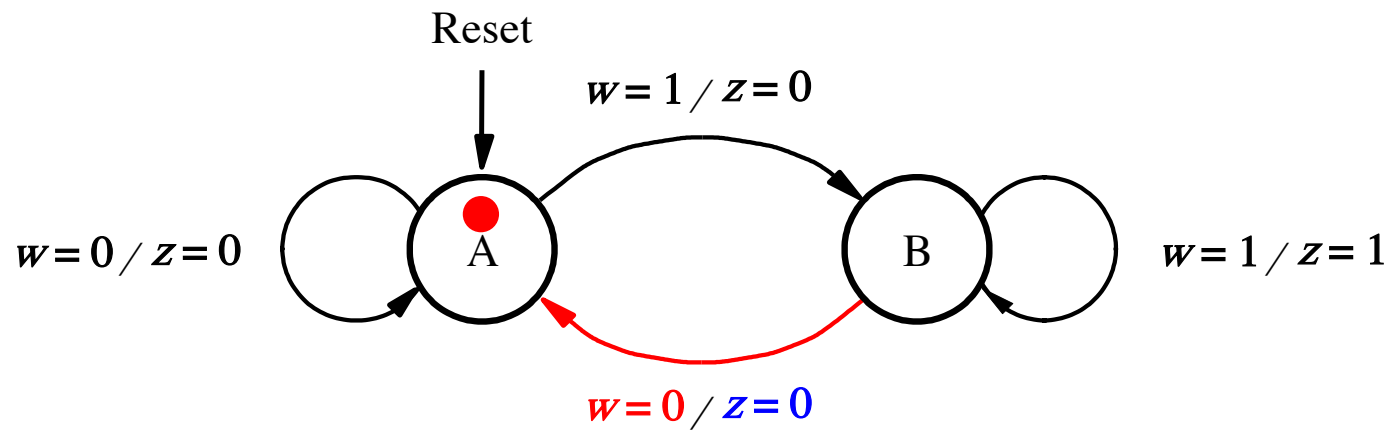


Let's Do a Simulation

| Clock cycle: | t_0 | t_1 | t_2 | t_3 | t_4 | t_5 | t_6 | t_7 | t_8 | t_9 | t_{10} |
|--------------|-------|-------|-------|-------|-------|-------|-------|-------|-------|-------|----------|
| input w : | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 1 | 0 | 1 |
| output z : | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 1 | 0 | 0 |

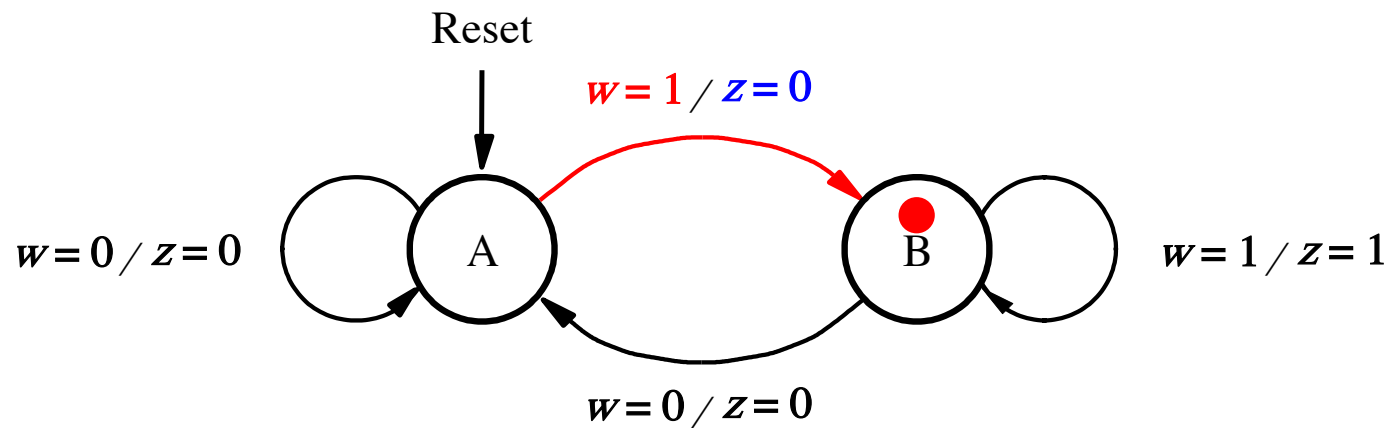


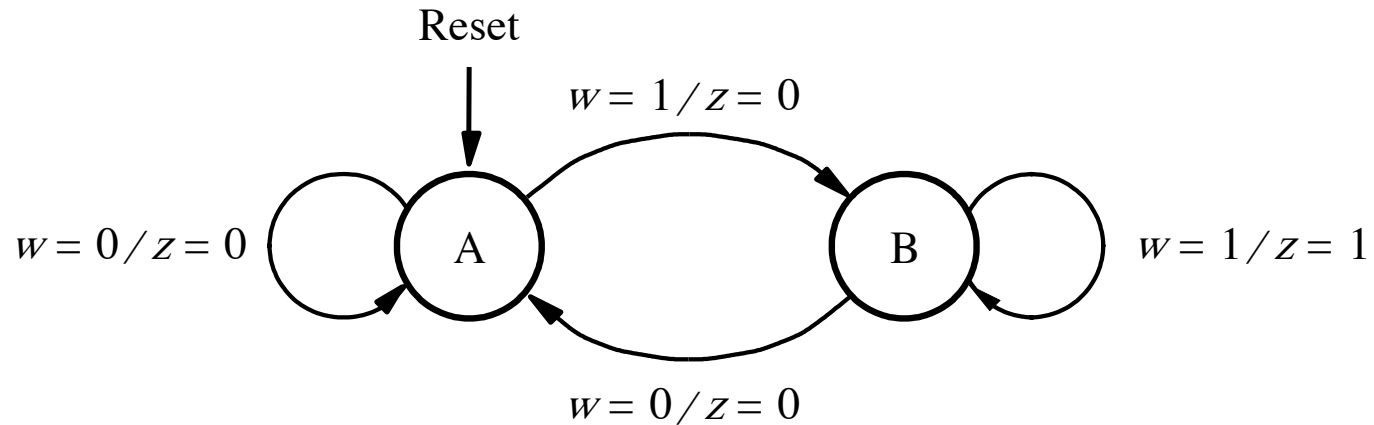Now Let's Do the State Table for this FSM



| Present state | Next state | | Output z | |
|---------------|------------|---------|------------|---------|
| | $w = 0$ | $w = 1$ | $w = 0$ | $w = 1$ |
| A | | | | |
| B | | | | |

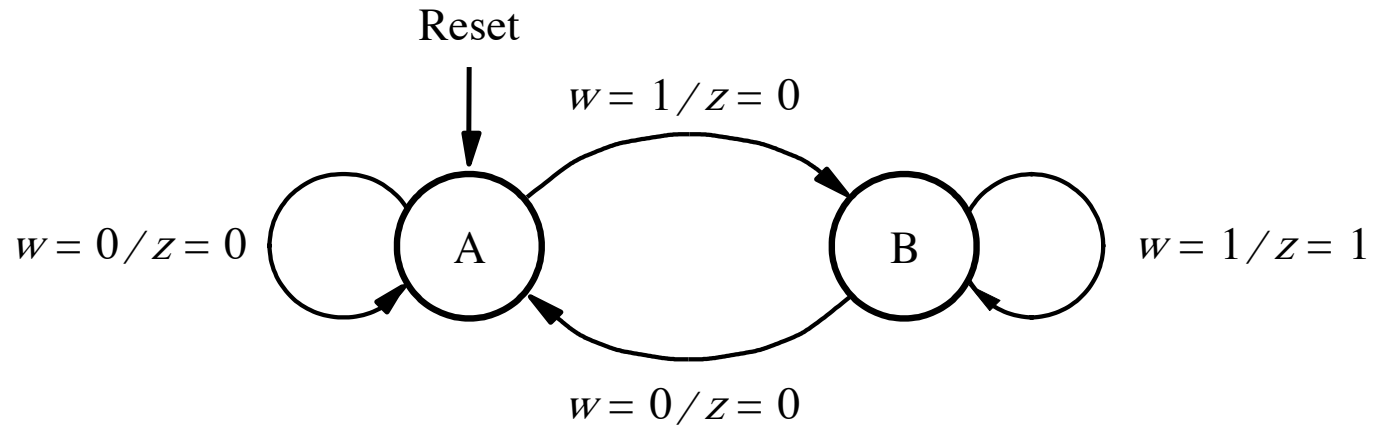Now Let's Do the State Table for this FSM



| Present state | Next state | | Output z | |
|---------------|------------|---------|------------|---------|
| | $w = 0$ | $w = 1$ | $w = 0$ | $w = 1$ |
| A | A | B | 0 | 0 |
| B | A | B | 0 | 1 |

The State Table for this FSM

| Present state | Next state | | Output z | |
|---------------|------------|---------|------------|---------|
| | $w = 0$ | $w = 1$ | $w = 0$ | $w = 1$ |
| A | A | B | 0 | 0 |
| B | A | B | 0 | 1 |

Let's Do the State-assigned Table

| Present state | Next state | | Output z | |
|---------------|------------|---------|------------|---------|
| | $w = 0$ | $w = 1$ | $w = 0$ | $w = 1$ |
| A | A | B | 0 | 0 |
| B | A | B | 0 | 1 |

| Present state | Next state | | Output | |
|---------------|------------|---------|---------|---------|
| | $w = 0$ | $w = 1$ | $w = 0$ | $w = 1$ |
| y | Y | Y | z | z |
| A 0 | | | | |
| B 1 | | | | |

Let's Do the State-assigned Table

| Present state | Next state | | Output z | |
|---------------|------------|---------|------------|---------|
| | $w = 0$ | $w = 1$ | $w = 0$ | $w = 1$ |
| A | A | B | 0 | 0 |
| B | A | B | 0 | 1 |

| | Present state | Next state | | Output | |
|---|---------------|------------|---------|---------|---------|
| | | $w = 0$ | $w = 1$ | $w = 0$ | $w = 1$ |
| | y | Y | Y | z | z |
| A | 0 | 0 | 1 | 0 | 0 |
| B | 1 | 0 | 1 | 0 | 1 |

The State-assigned Table

| | Present state | Next state | | Output | |
|---|---------------|------------|---------|---------|---------|
| | | $w = 0$ | $w = 1$ | $w = 0$ | $w = 1$ |
| | y | Y | Y | z | z |
| A | 0 | 0 | 1 | 0 | 0 |
| B | 1 | 0 | 1 | 0 | 1 |

The State-assigned Table


| | Present state | Next state | | Output | |
|---|---------------|------------|---------|---------|---------|
| | | $w = 0$ | $w = 1$ | $w = 0$ | $w = 1$ |
| | y | Y | Y | z | z |
| A | 0 | 0 | 1 | 0 | 0 |
| B | 1 | 0 | 1 | 0 | 1 |

$$Y = D = w \quad z = wy$$

The State-assigned Table


| | Present state | Next state | | Output | |
|---|---------------|------------|---------|---------|---------|
| | | $w = 0$ | $w = 1$ | $w = 0$ | $w = 1$ |
| | y | Y | Y | z | z |
| A | 0 | 0 | 1 | 0 | 0 |
| B | 1 | 0 | 1 | 0 | 1 |

$$Y = D = w \quad z = wy$$

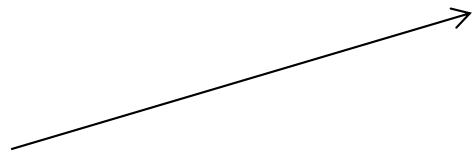


This assumes D flip-flop

Circuit Implementation of the FSM

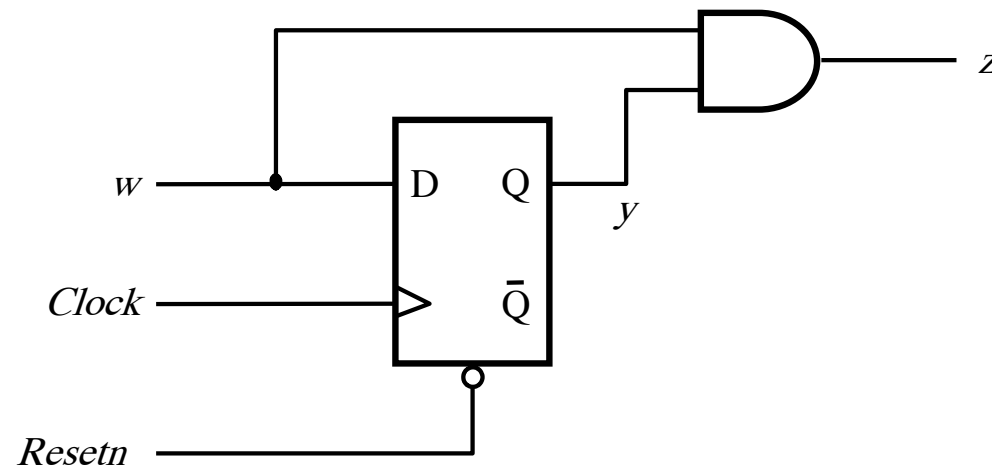


$$Y = D = w \quad z = wy$$

Circuit & Timing Diagram

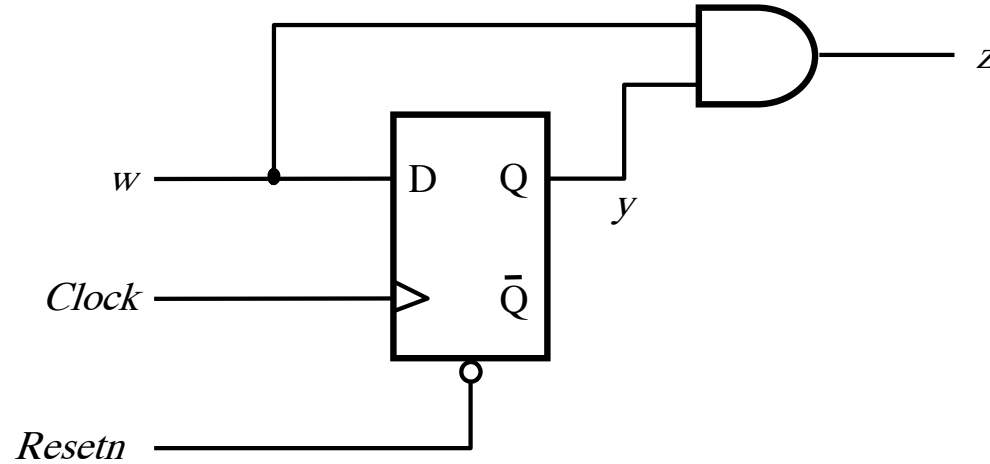

(a) Circuit

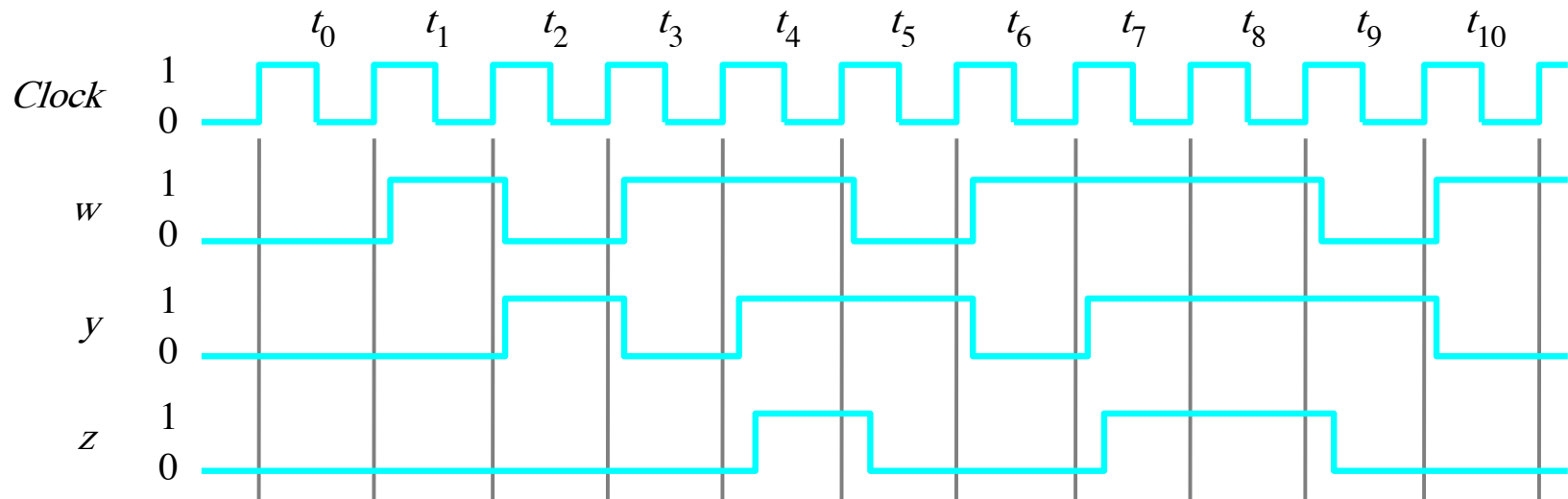


(b) Timing diagram

[Figure 6.26 from the textbook]


What if we wanted the output signal to be delayed by 1 clock cycle?

Circuit Implementation of the Modified FSM

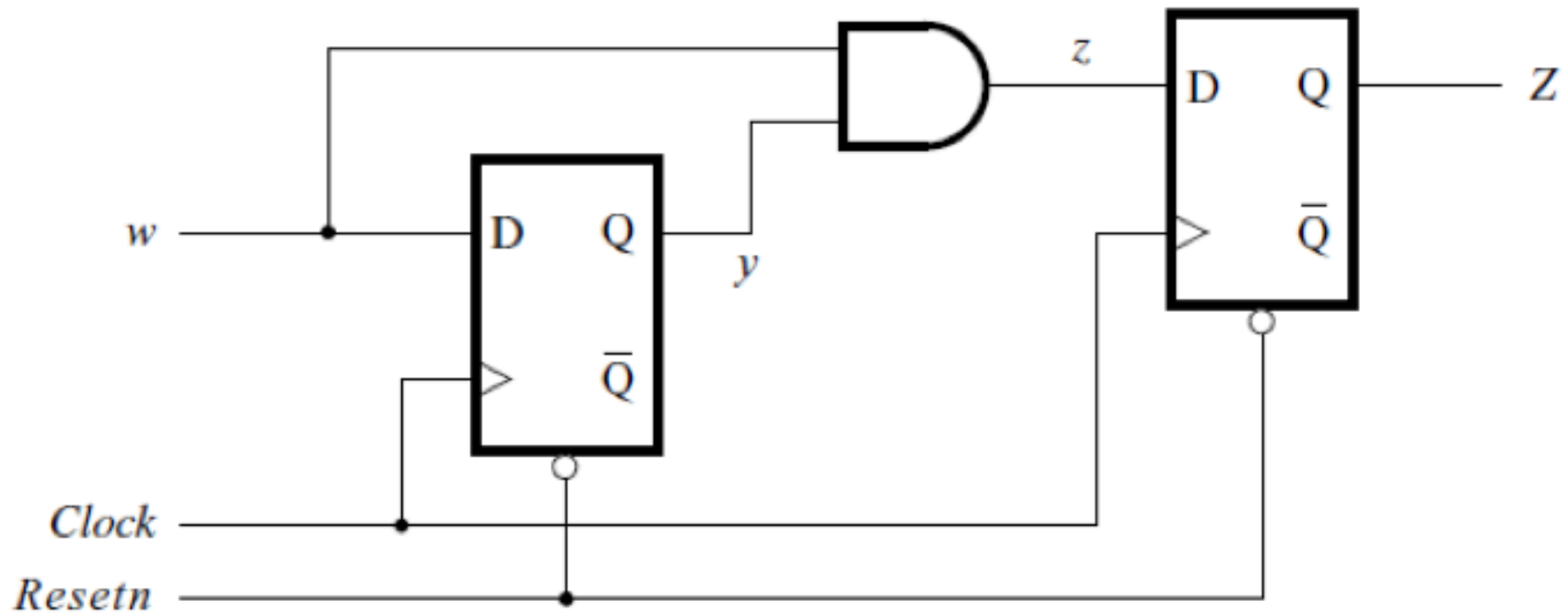

[Figure 6.27a from the textbook]

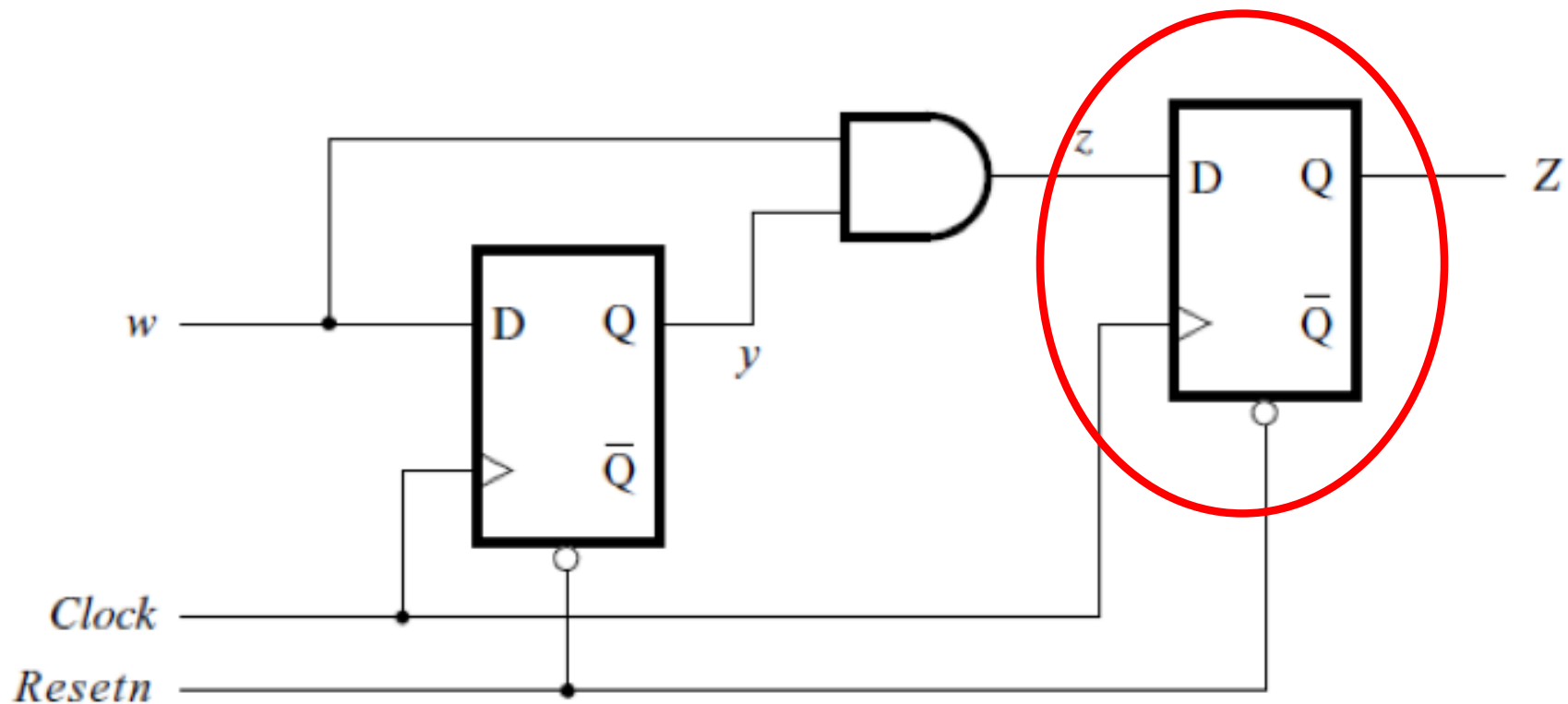Circuit Implementation of the Modified FSM




This flip-flop delays the output signal by one clock cycle

We Have Seen This Diagram Before


$$Y_1(w, y_2, y_1) = w$$

$$Y_2(w, y_2, y_1) = wy_1$$


$$z(y_2, y_1) = y_2$$

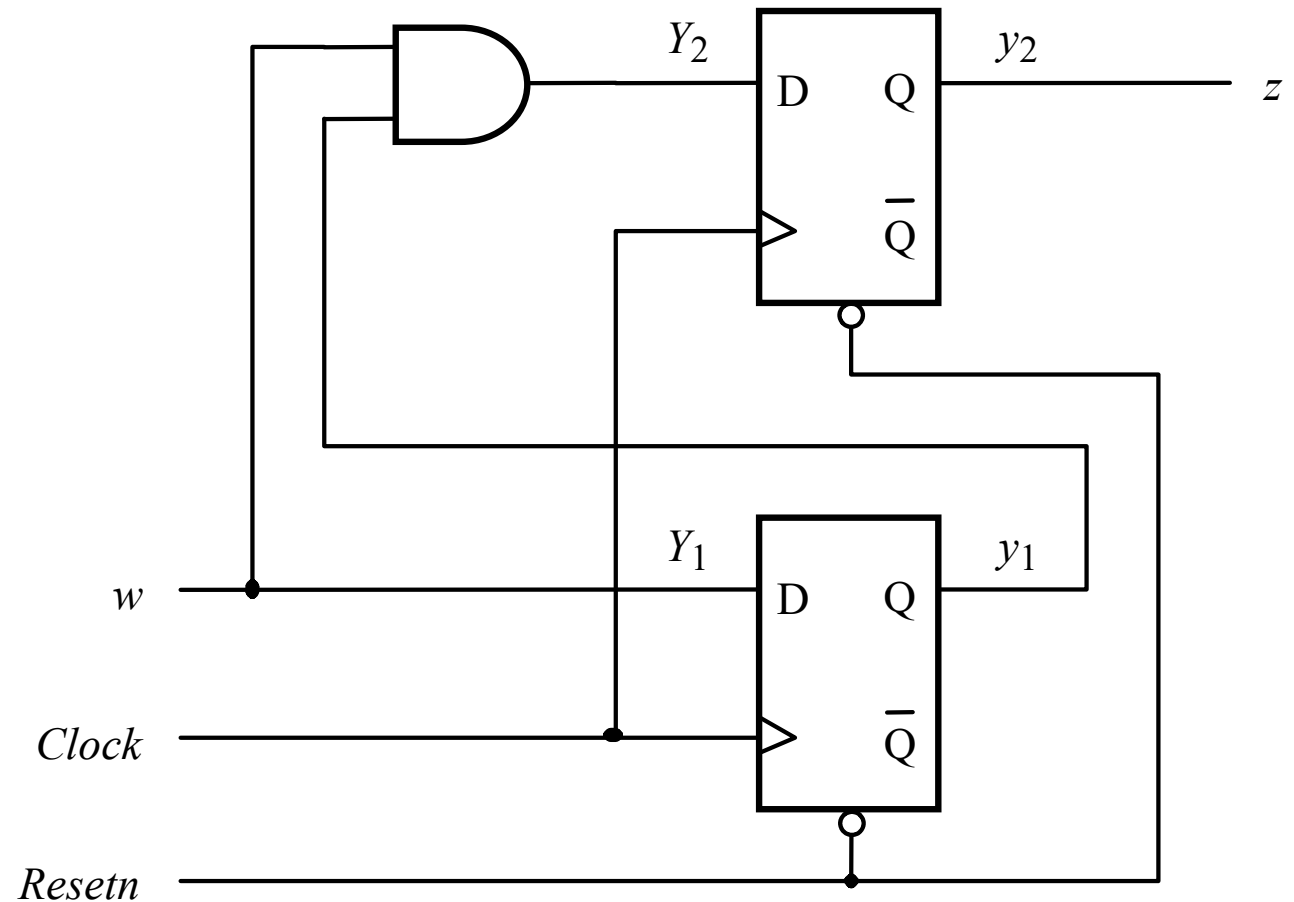


Circuit & Timing Diagram

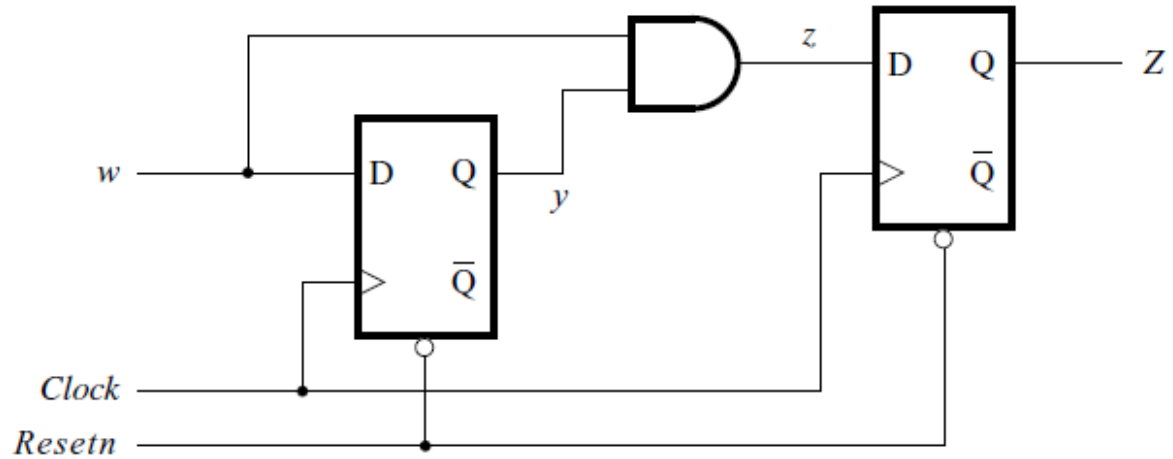

(a) Circuit

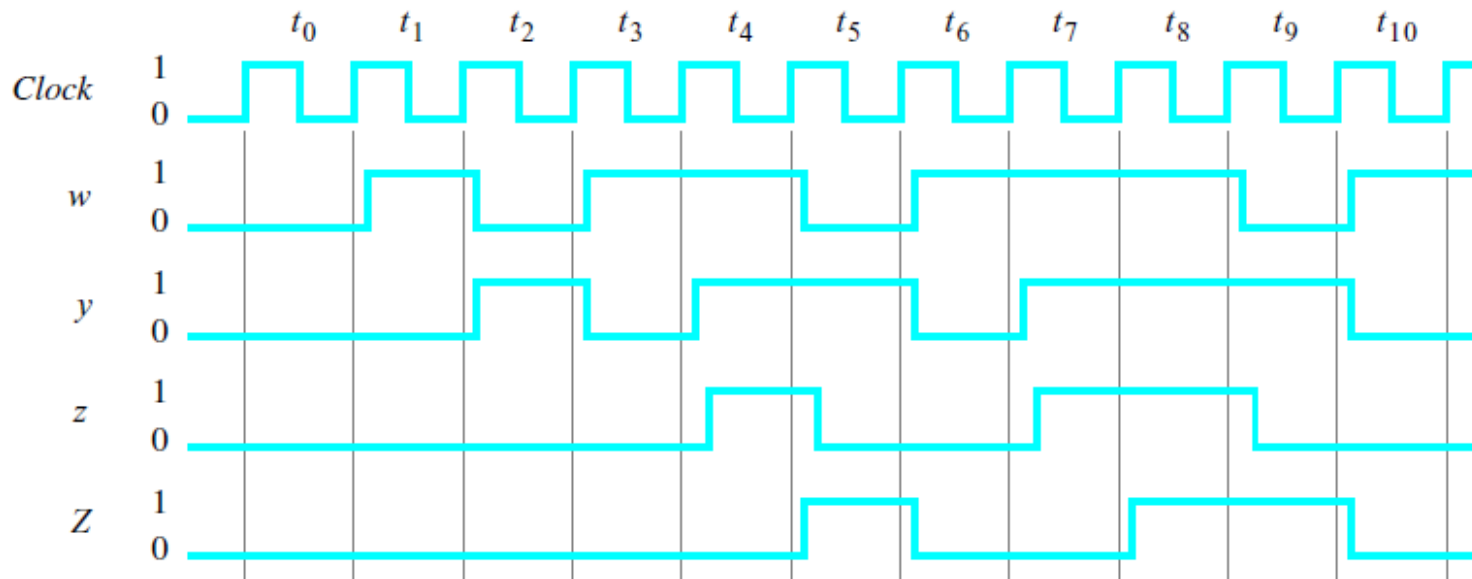


The general form of a synchronous sequential circuit

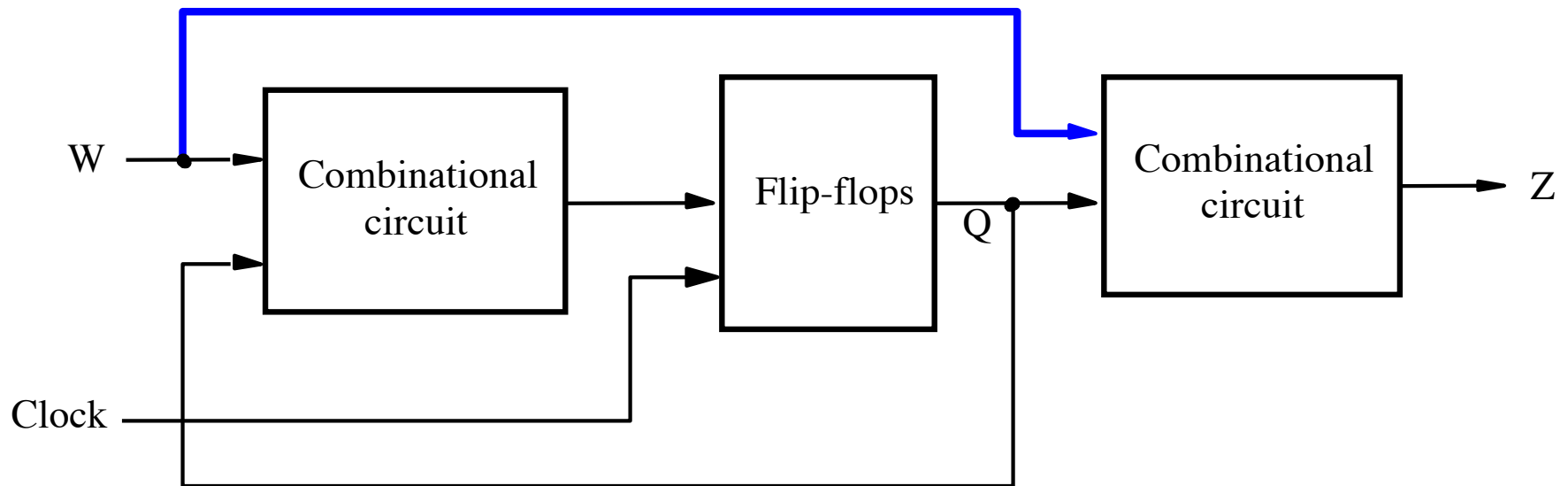


[Figure 6.1 from the textbook]


Moore Type

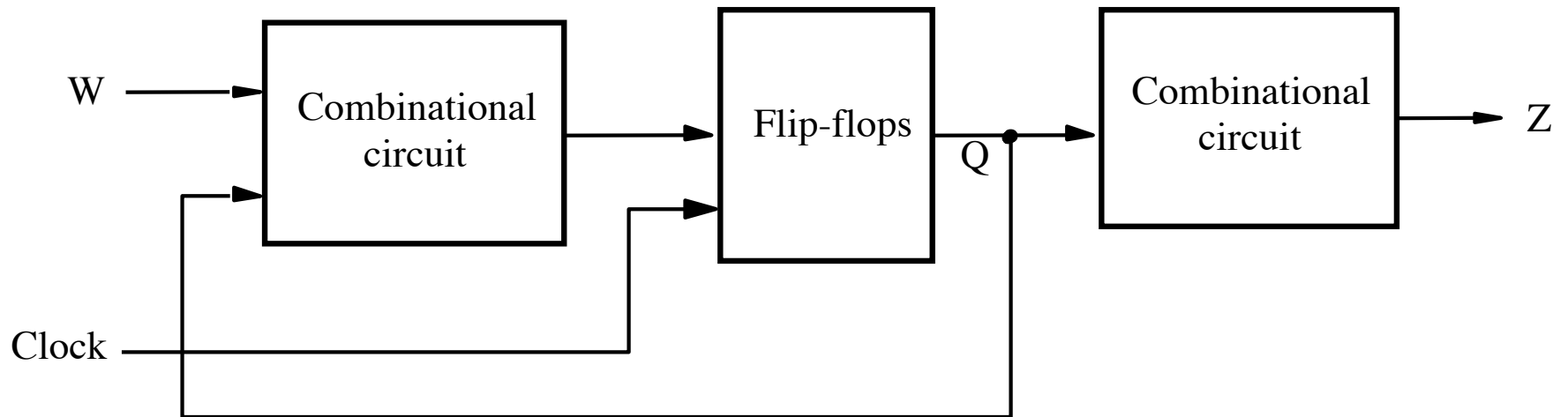


Mealy Type

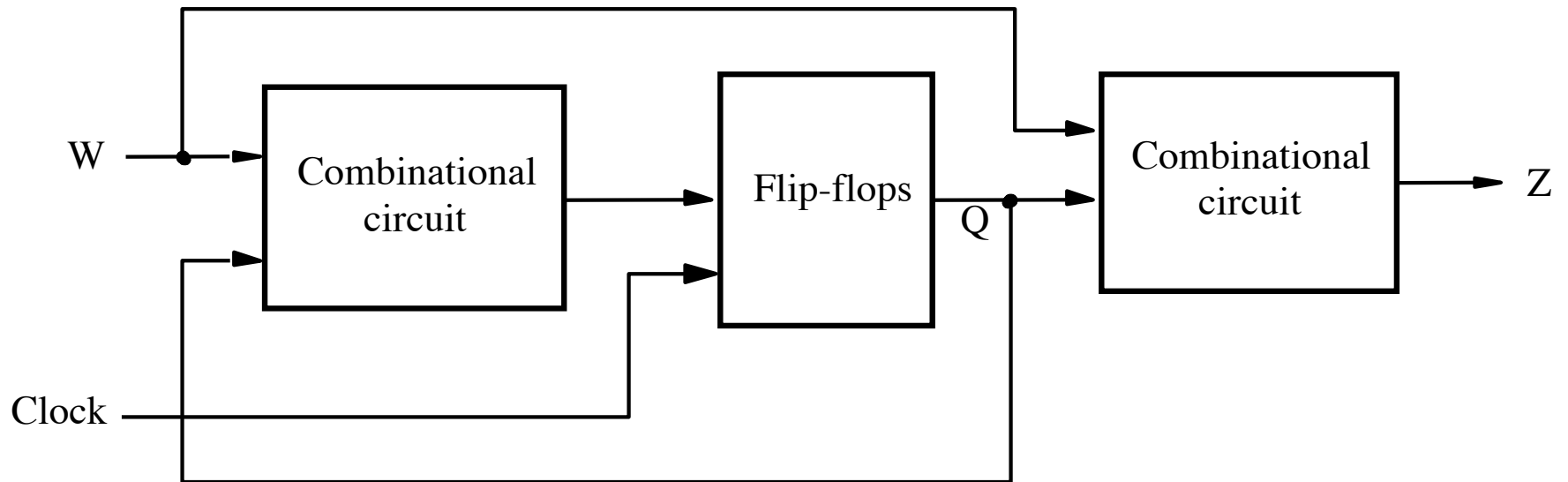



Moore

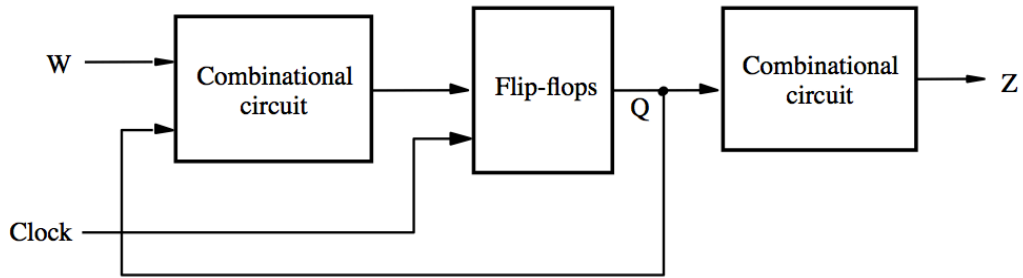



Mealy

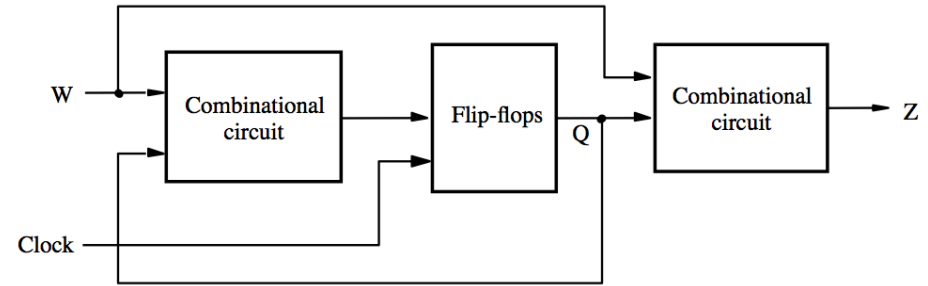


Moore

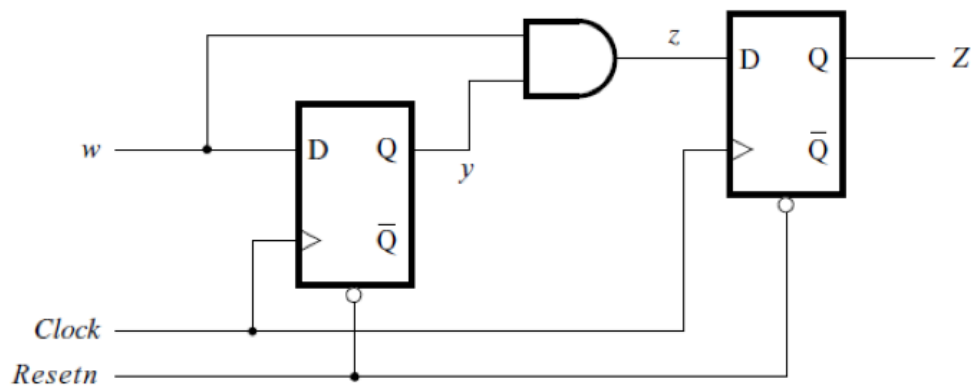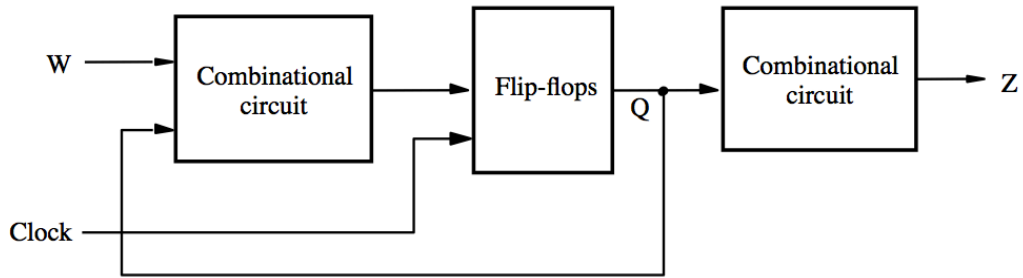


Mealy

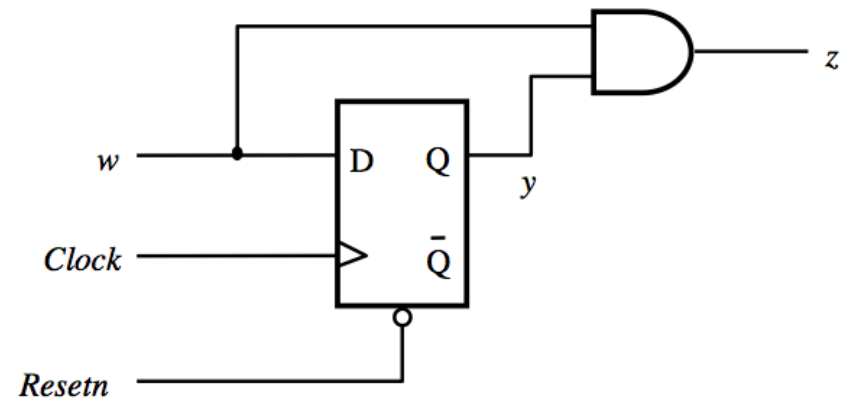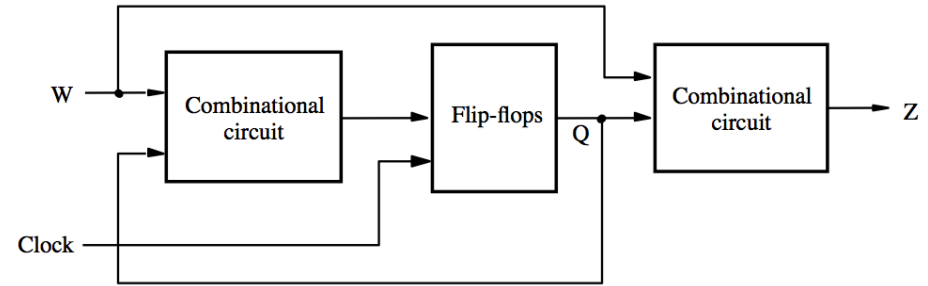

Mealy

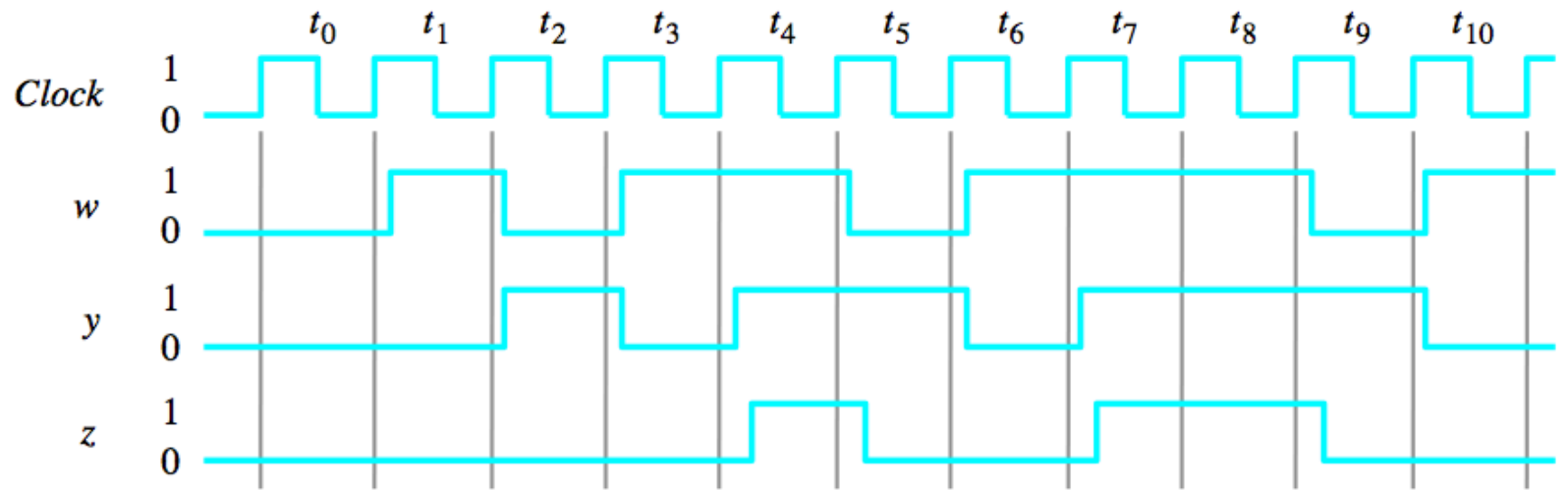


Moore

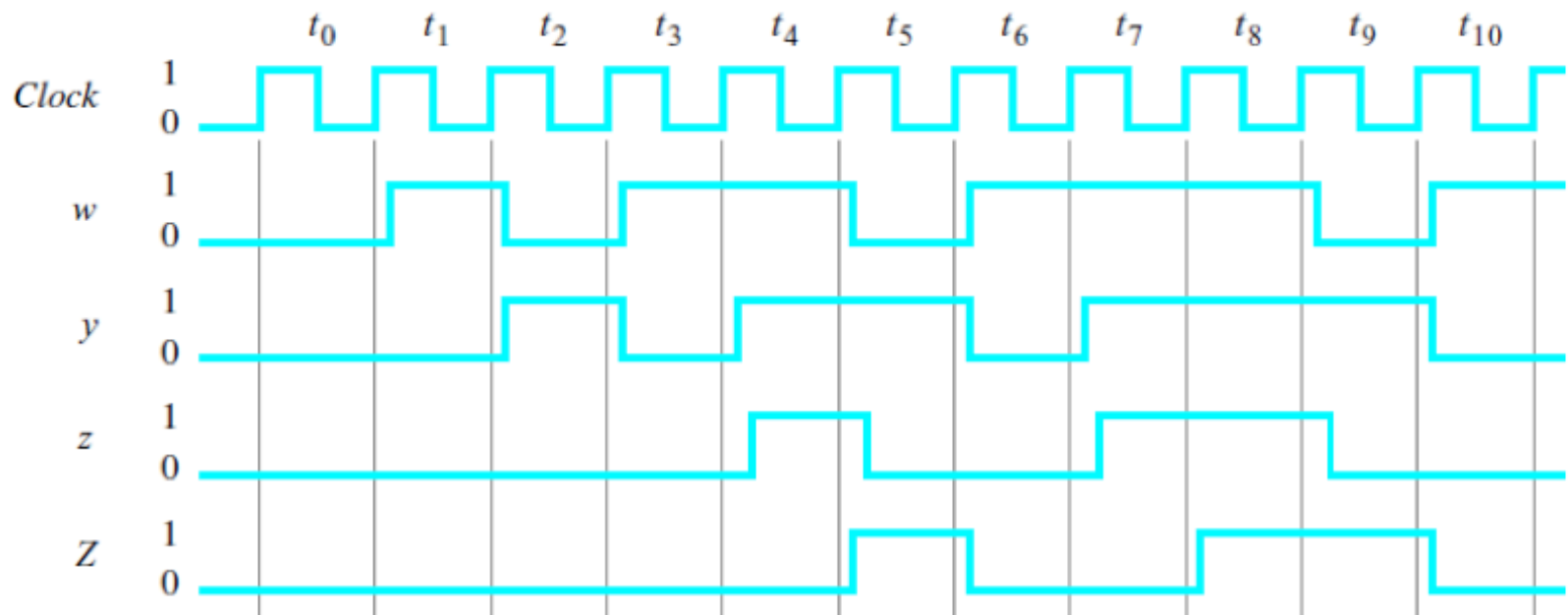


Notice that the output of the Moore machine is delayed by one clock cycle

Mealy

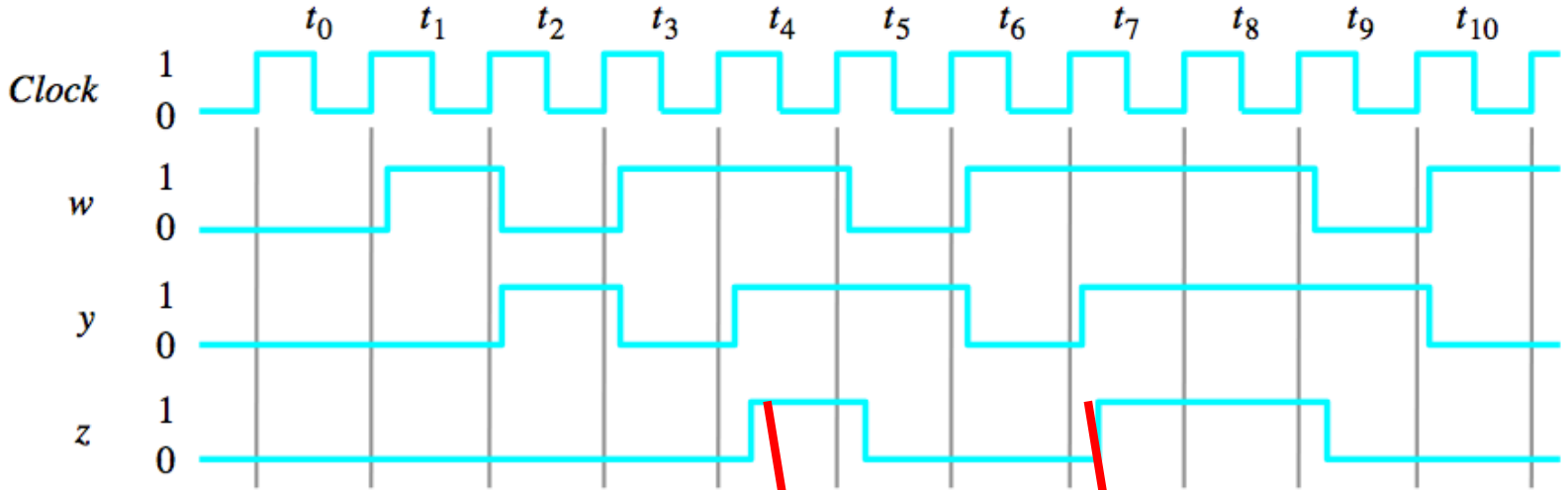

Moore

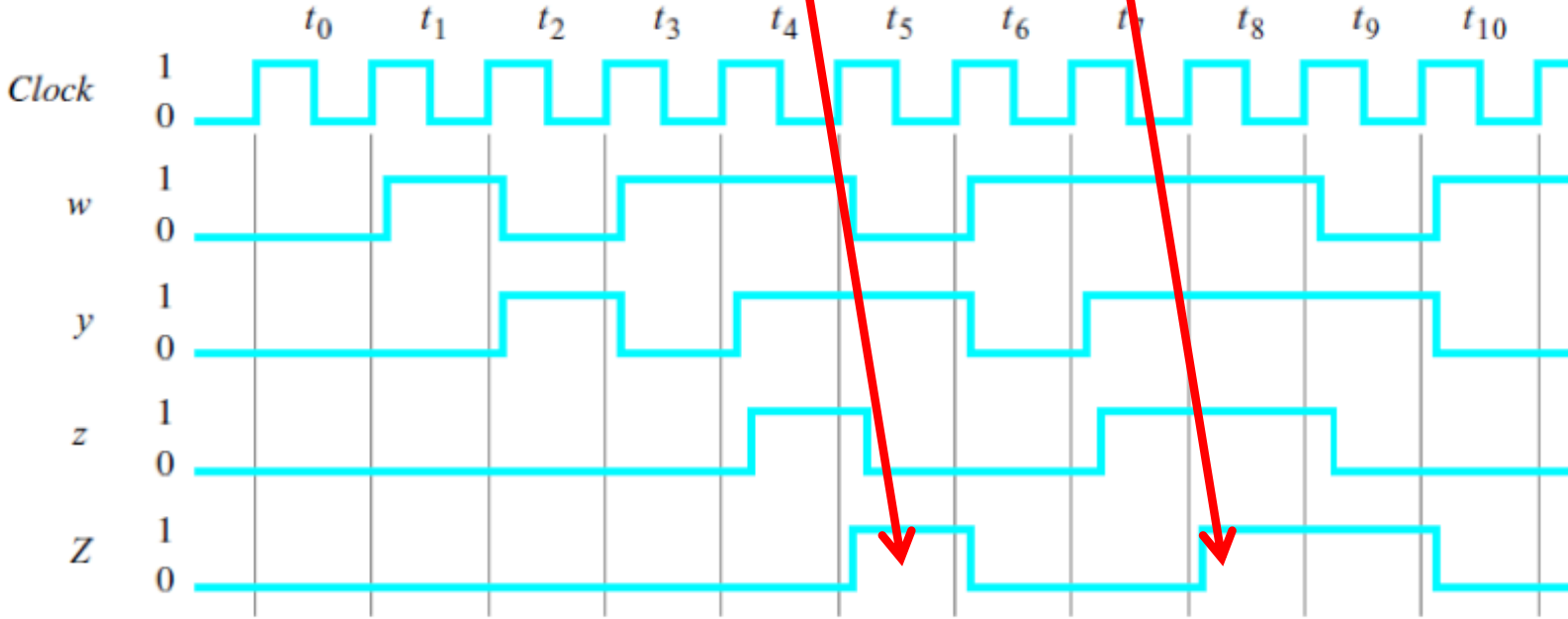

Notice that the output of the Moore machine is delayed by one clock cycle

Mealy

| | | | | | | | | | | | |
|--------------|-------|-------|-------|-------|-------|-------|-------|-------|-------|-------|----------|
| Clock cycle: | t_0 | t_1 | t_2 | t_3 | t_4 | t_5 | t_6 | t_7 | t_8 | t_9 | t_{10} |
| input w : | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 1 | 0 | 1 |
| output z : | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 1 | 0 | 0 |

Moore


| | | | | | | | | | | | |
|--------------|-------|-------|-------|-------|-------|-------|-------|-------|-------|-------|----------|
| Clockcycle: | t_0 | t_1 | t_2 | t_3 | t_4 | t_5 | t_6 | t_7 | t_8 | t_9 | t_{10} |
| input w : | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 1 | 0 | 1 |
| output z : | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 1 | 0 |

Questions?


**More slides for
the State Assignment Problem**

Example #2

Register Swap Controller

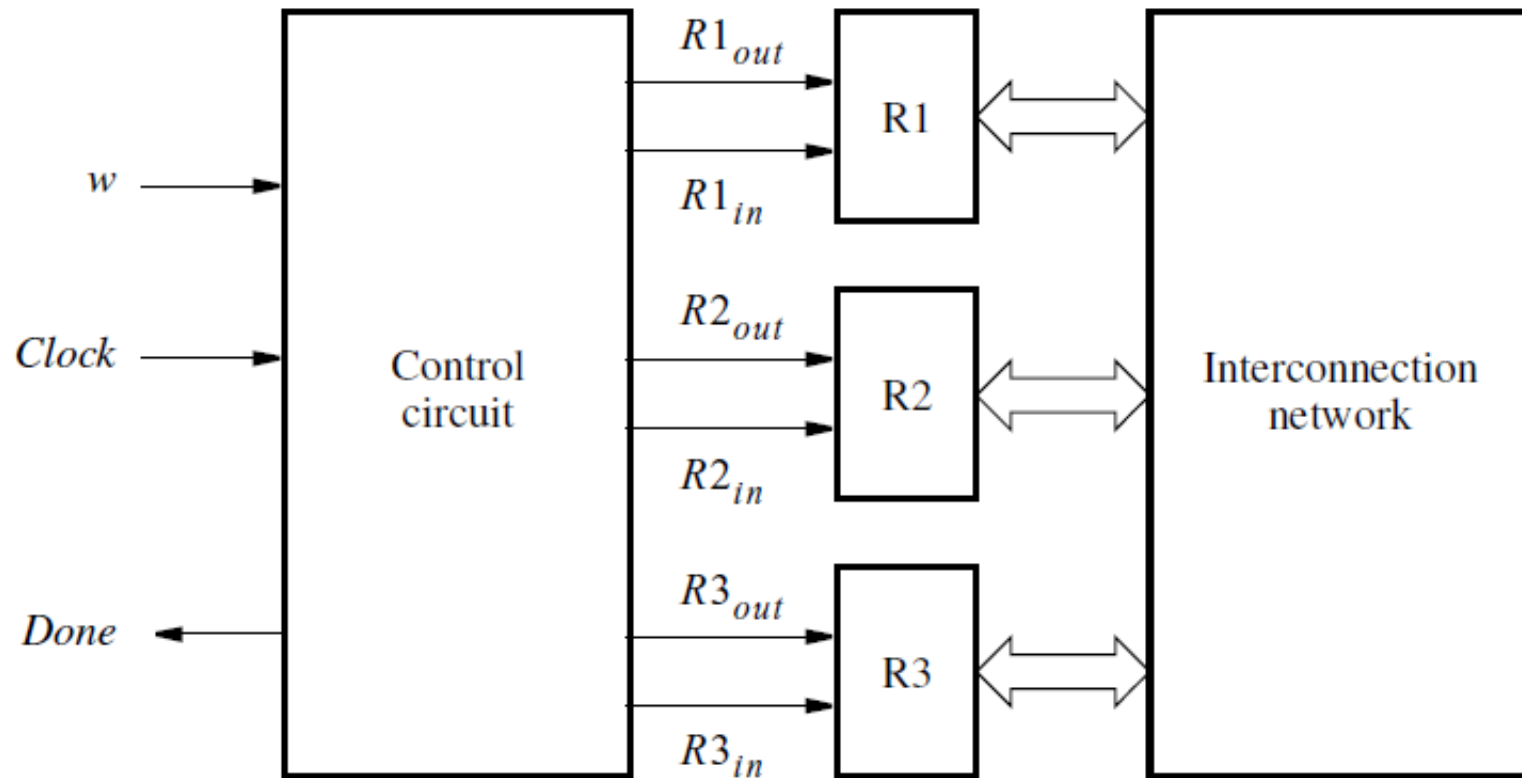


Register Swap Controller

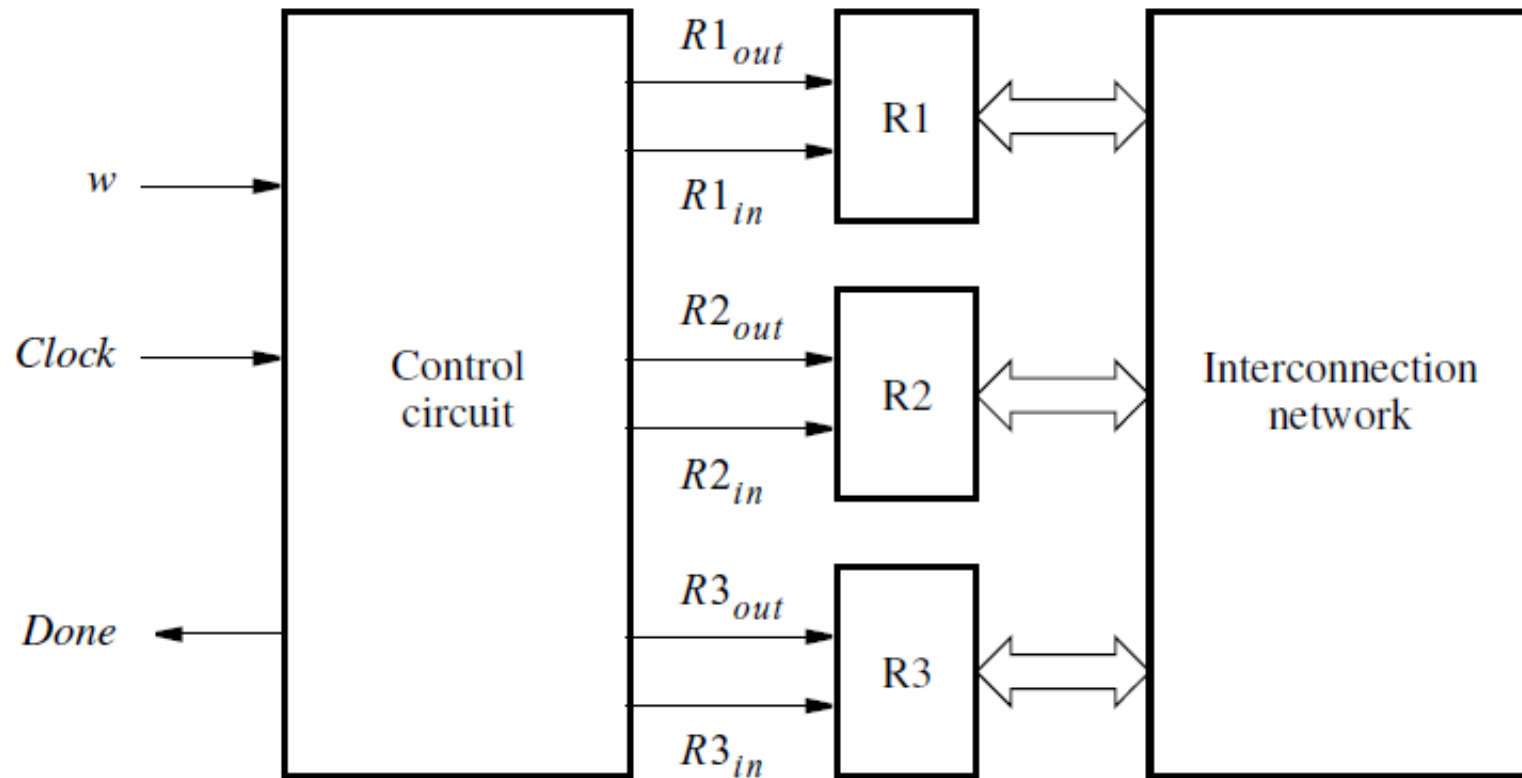


Design a Moore machine control circuit for swapping the contents of registers R1 and R2 by using R3 as a temporary.

State Diagram

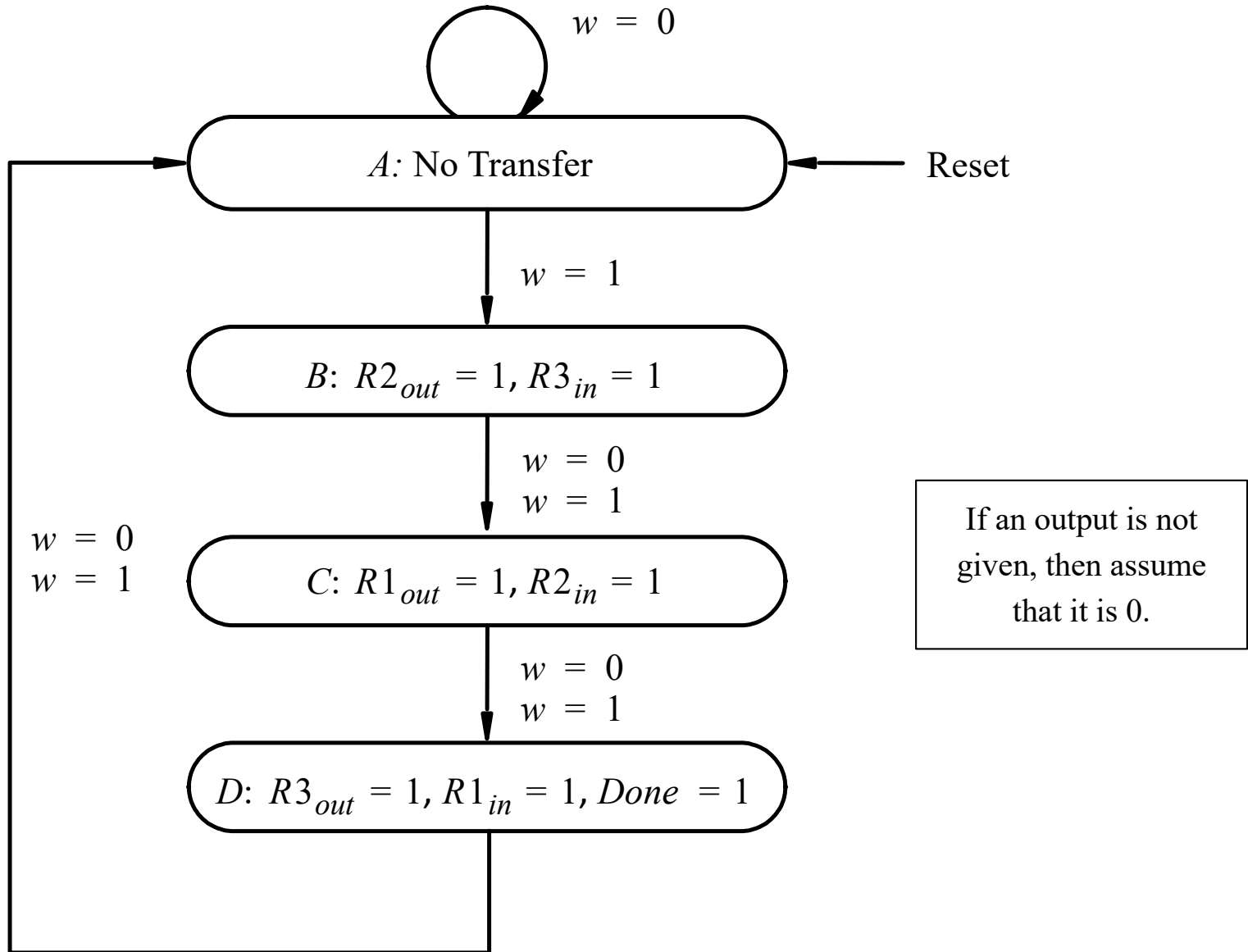


[Figure 6.11 from the textbook]

Animated Register Swap

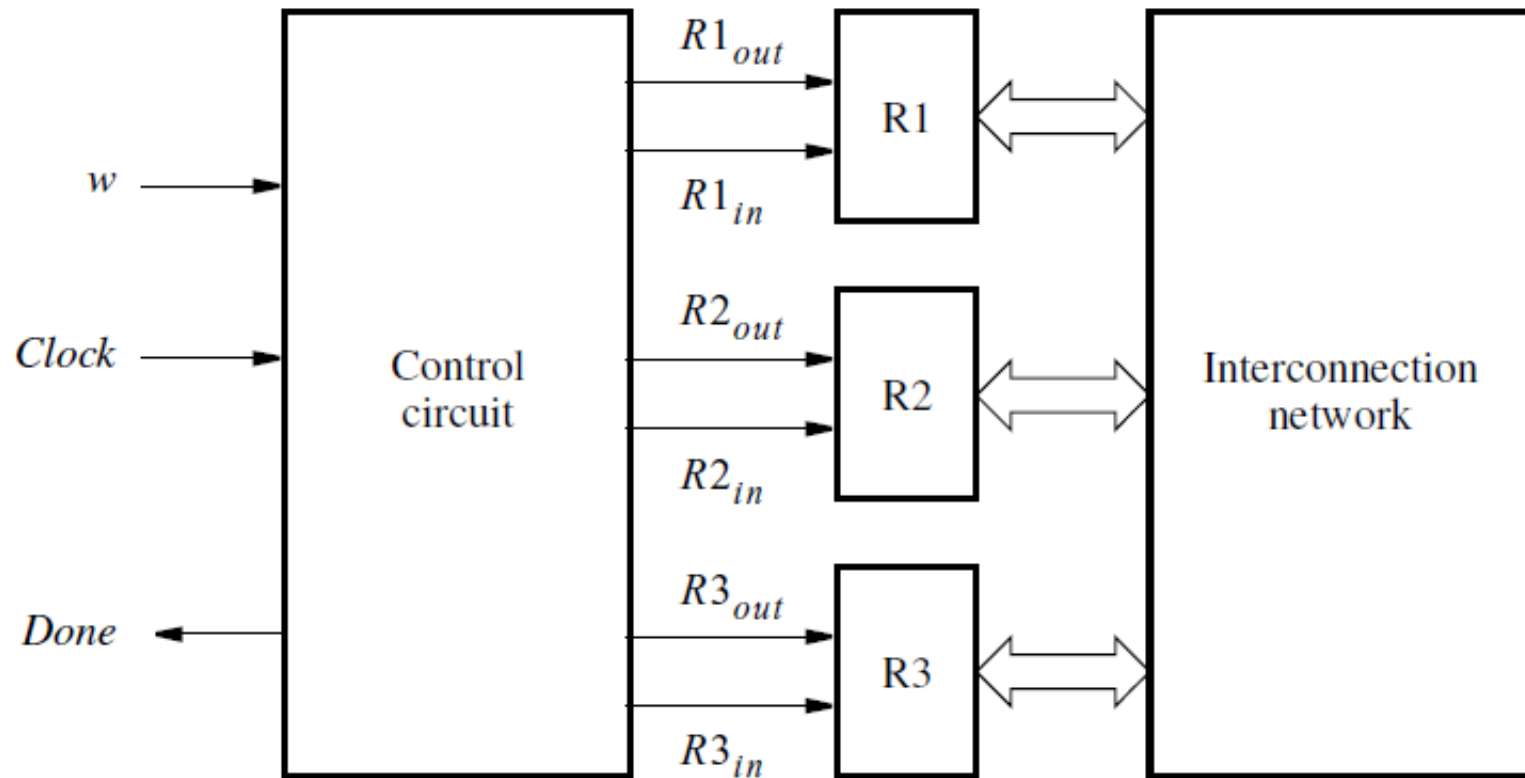


Animated Register Swap

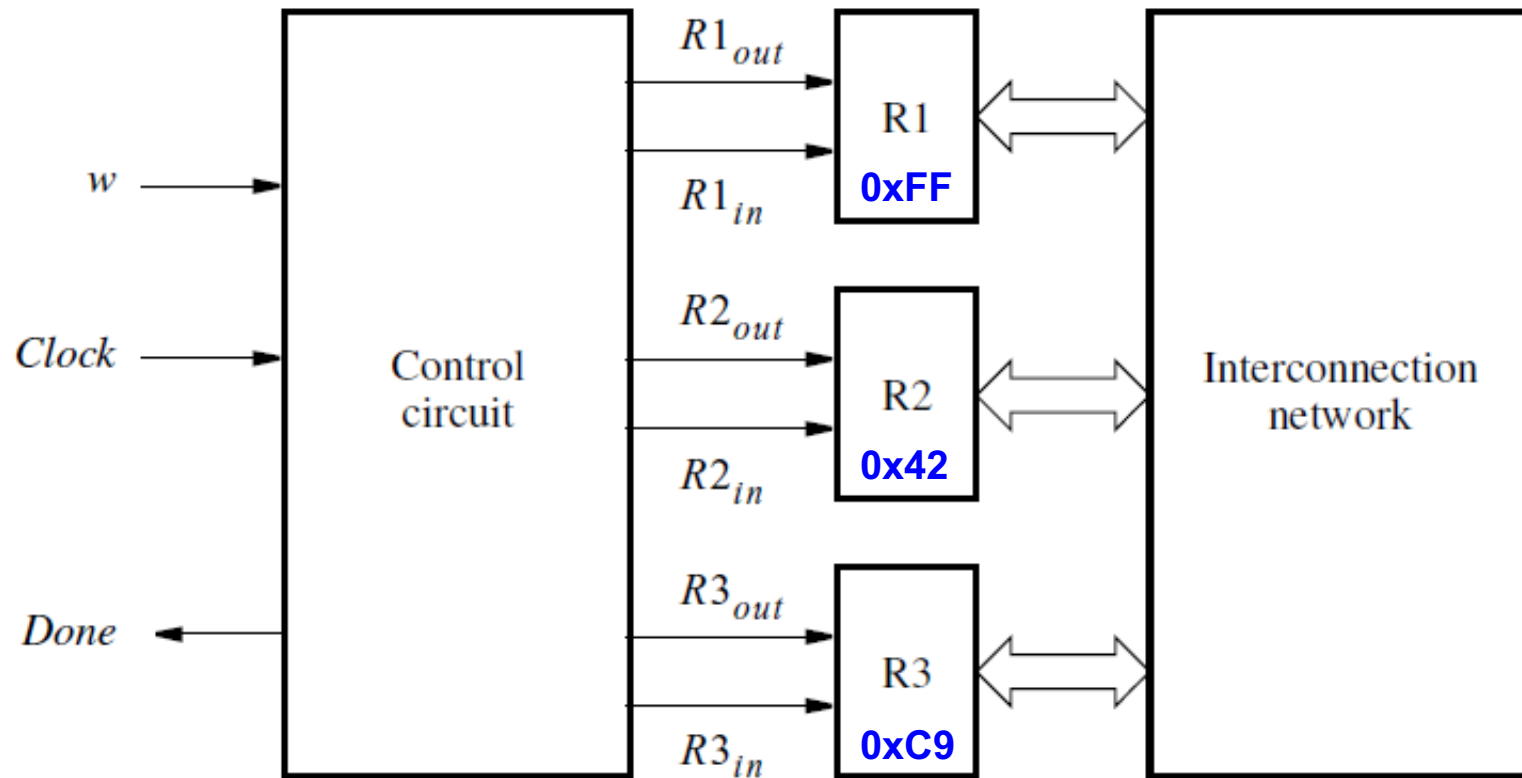


These are the original values of the 8-bit registers

Animated Register Swap

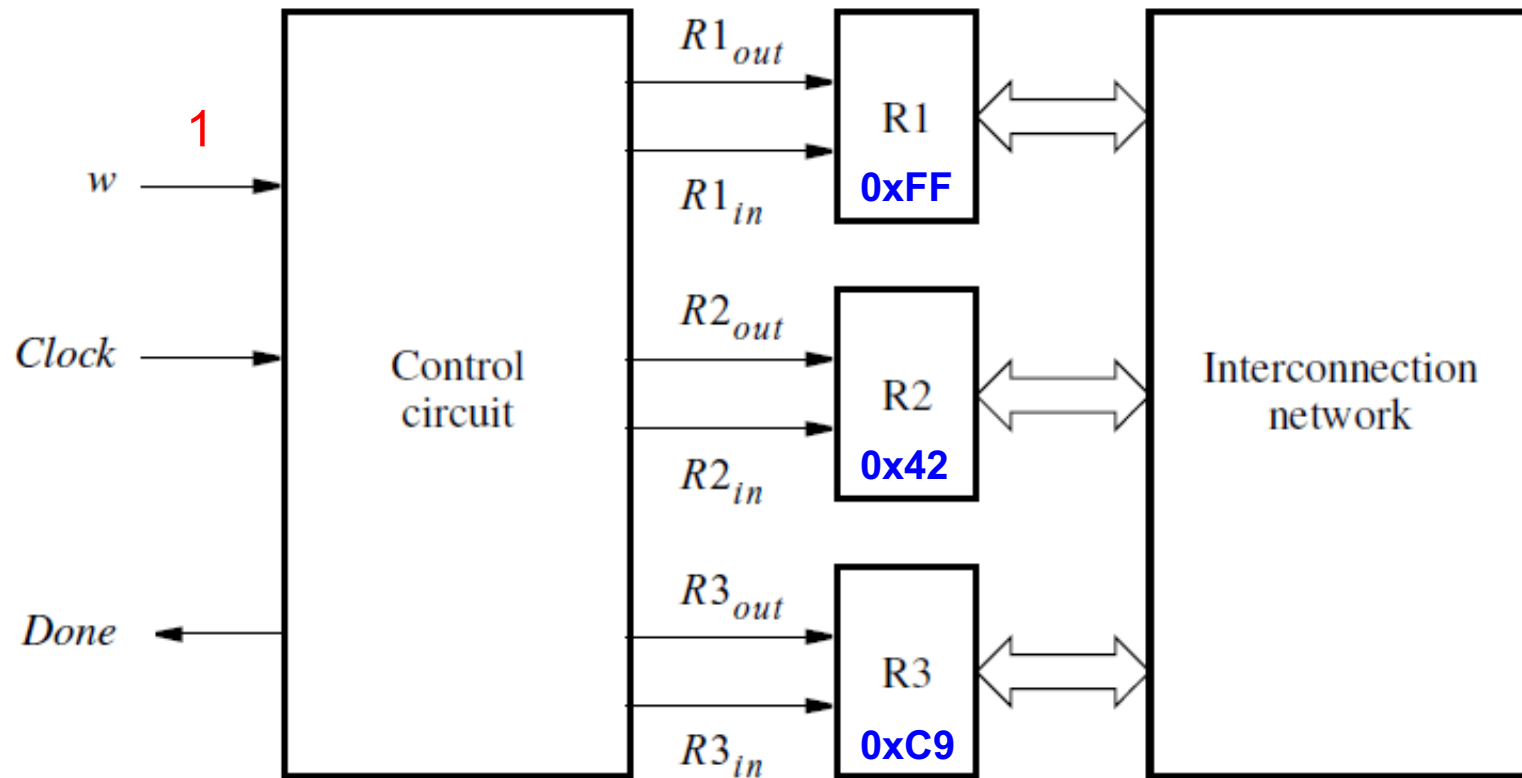


For clarity, only inputs that are equal to 1 will be shown.


Animated Register Swap

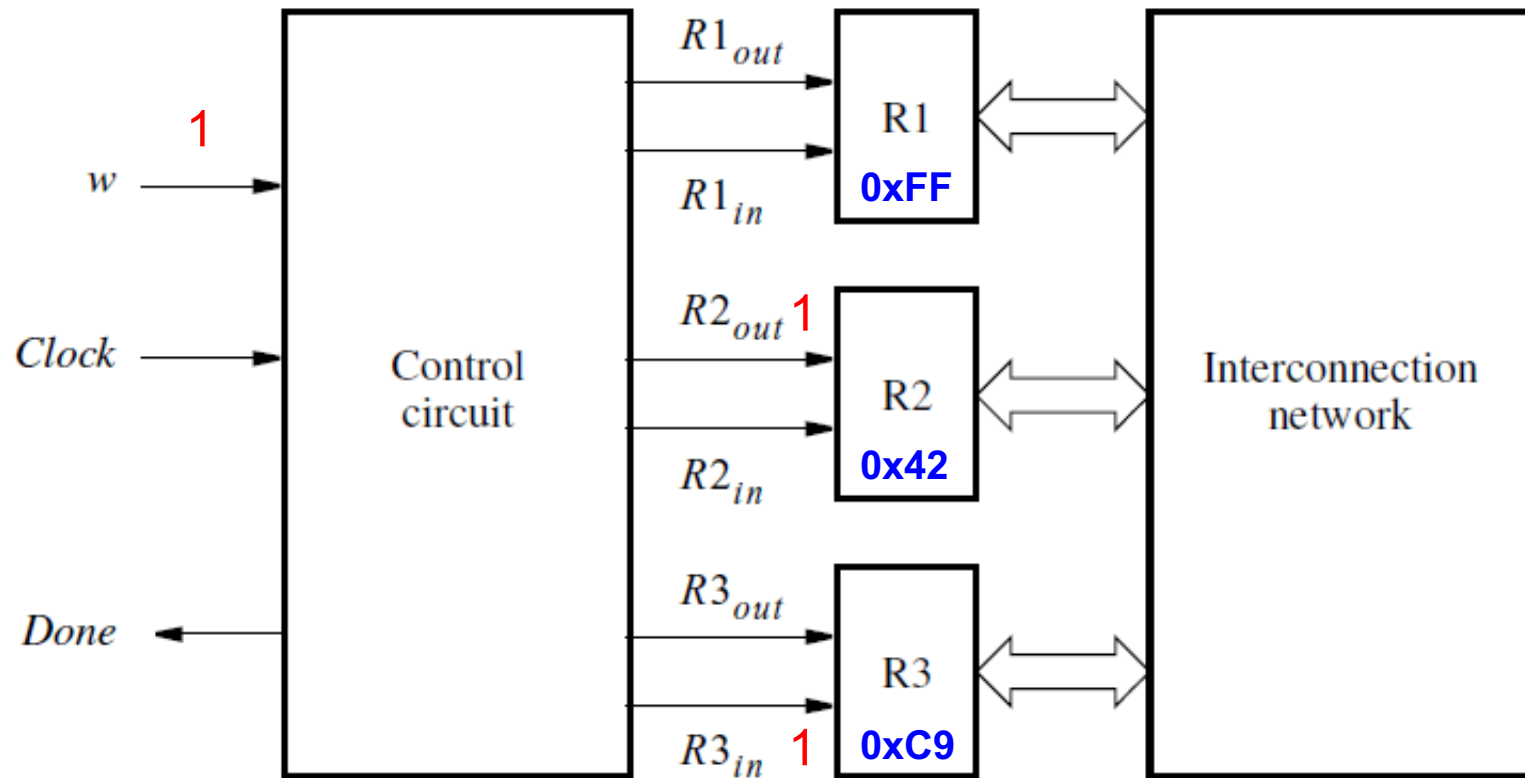


Animated Register Swap

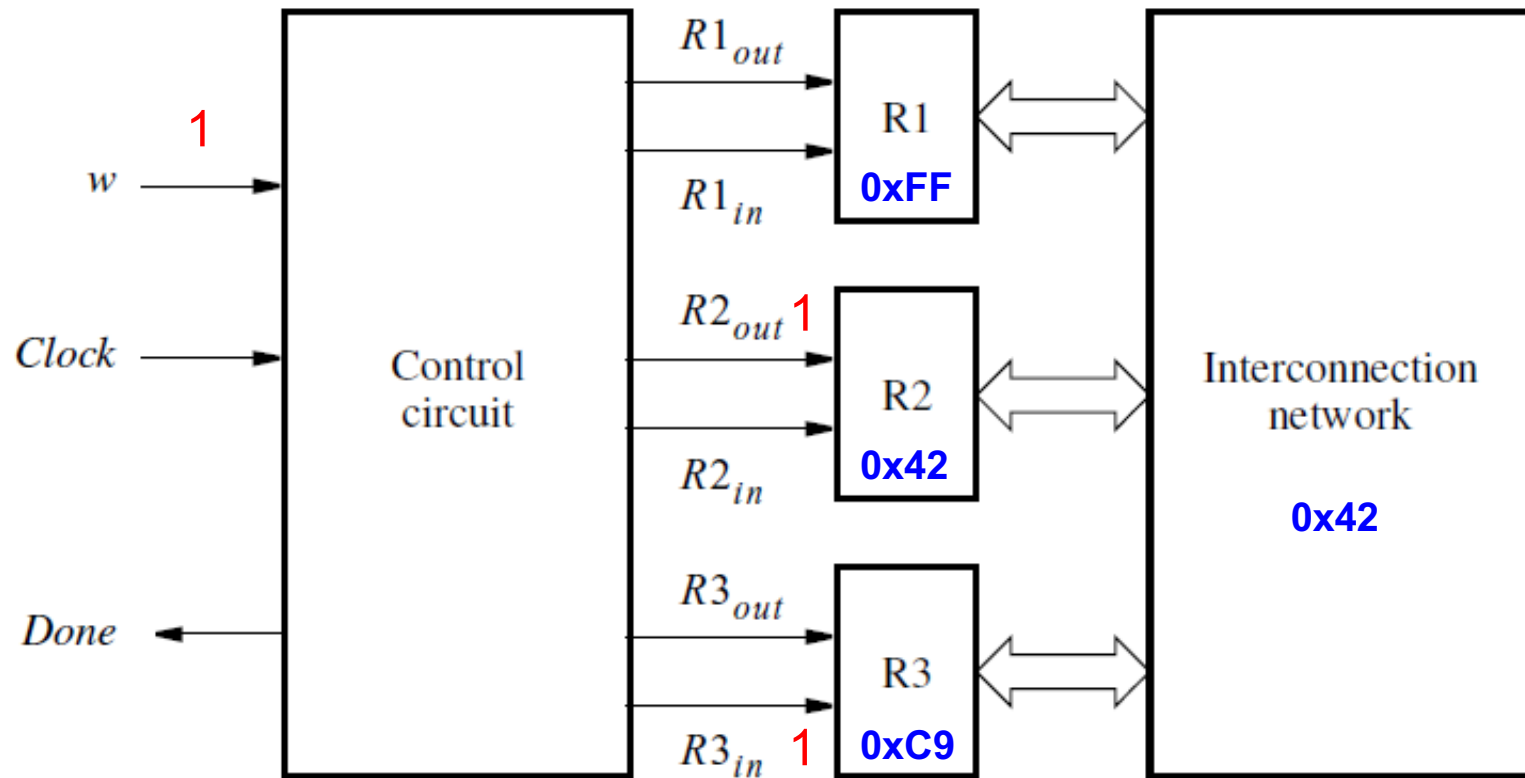


Animated Register Swap

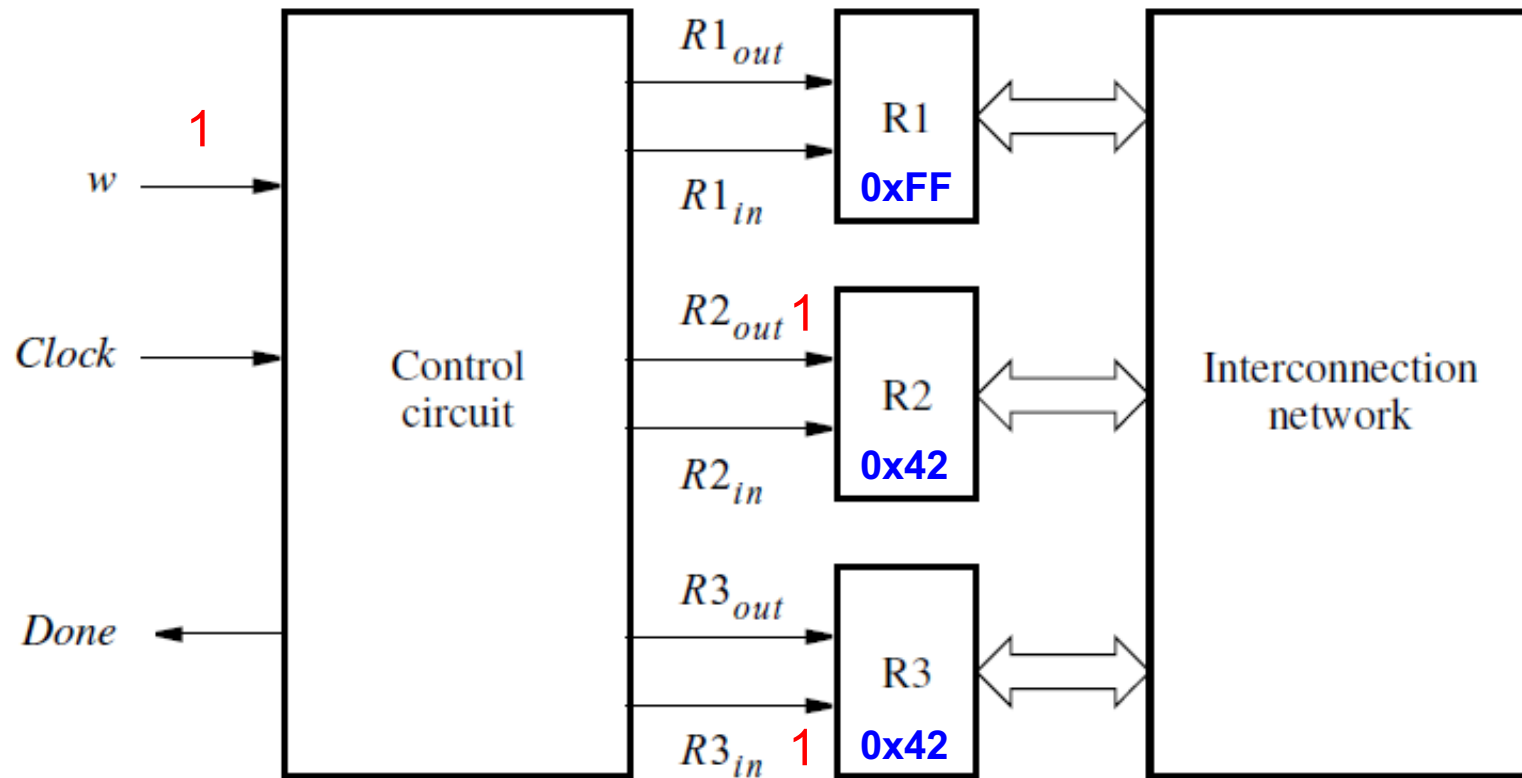


Animated Register Swap

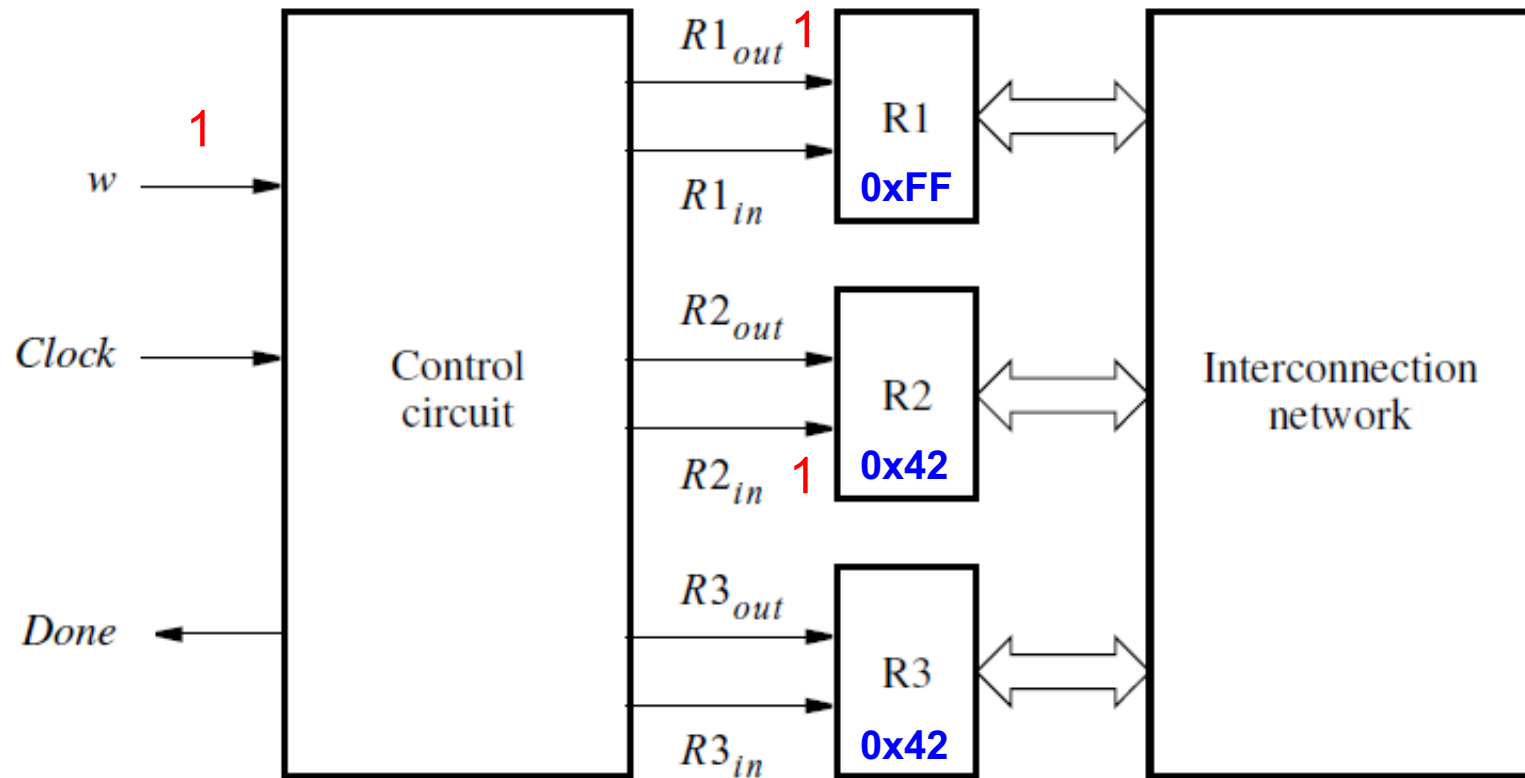


Animated Register Swap

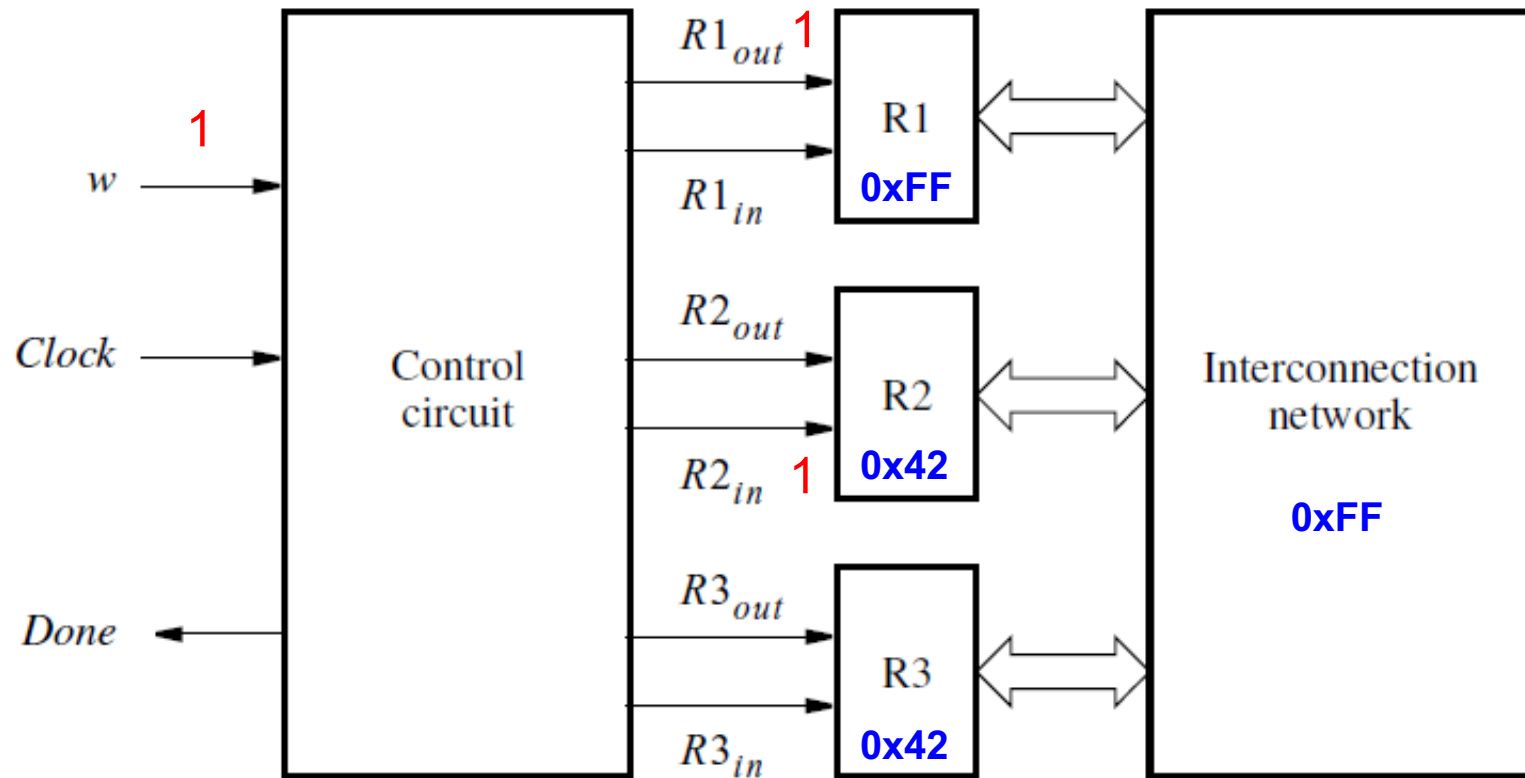


Animated Register Swap

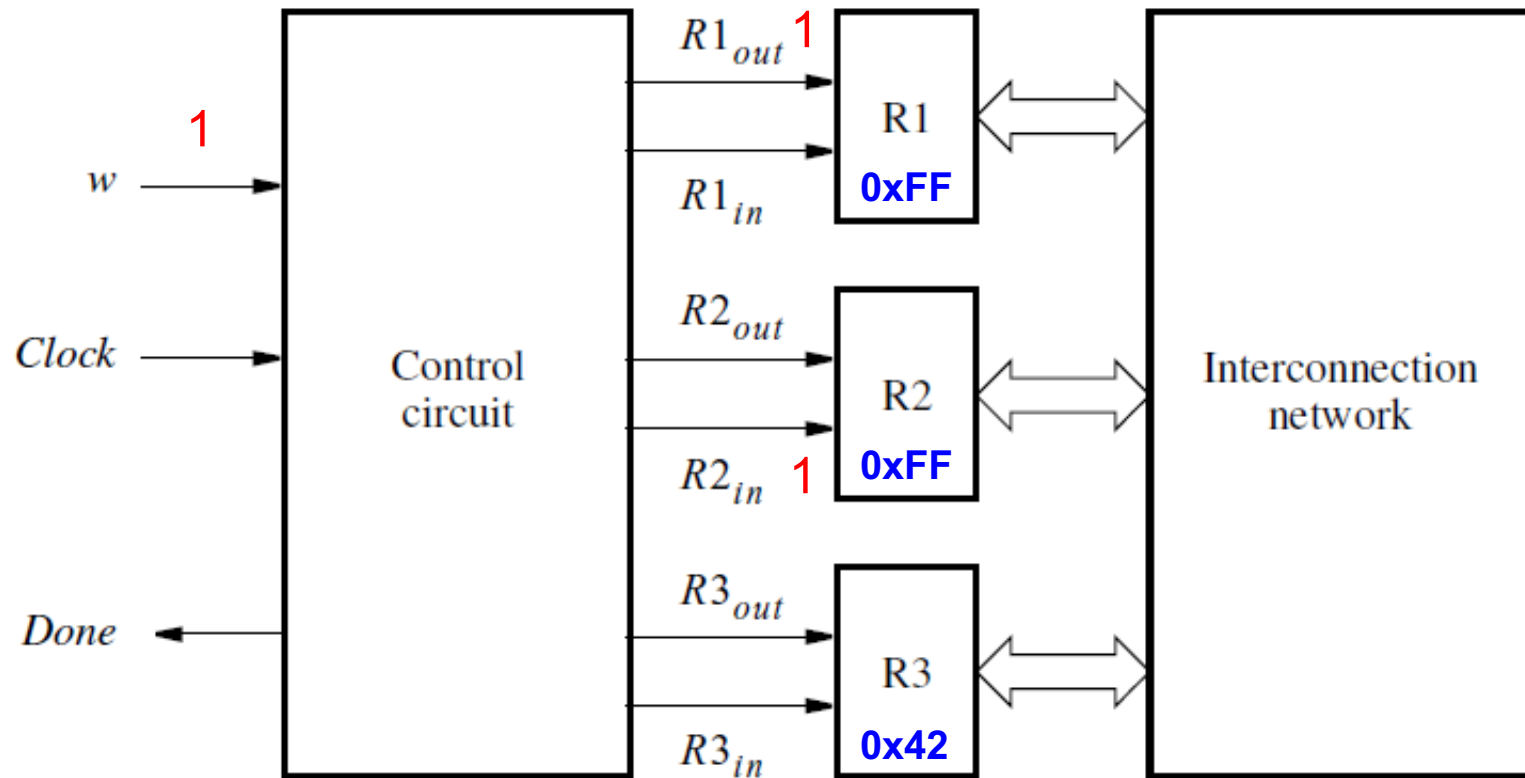


Animated Register Swap

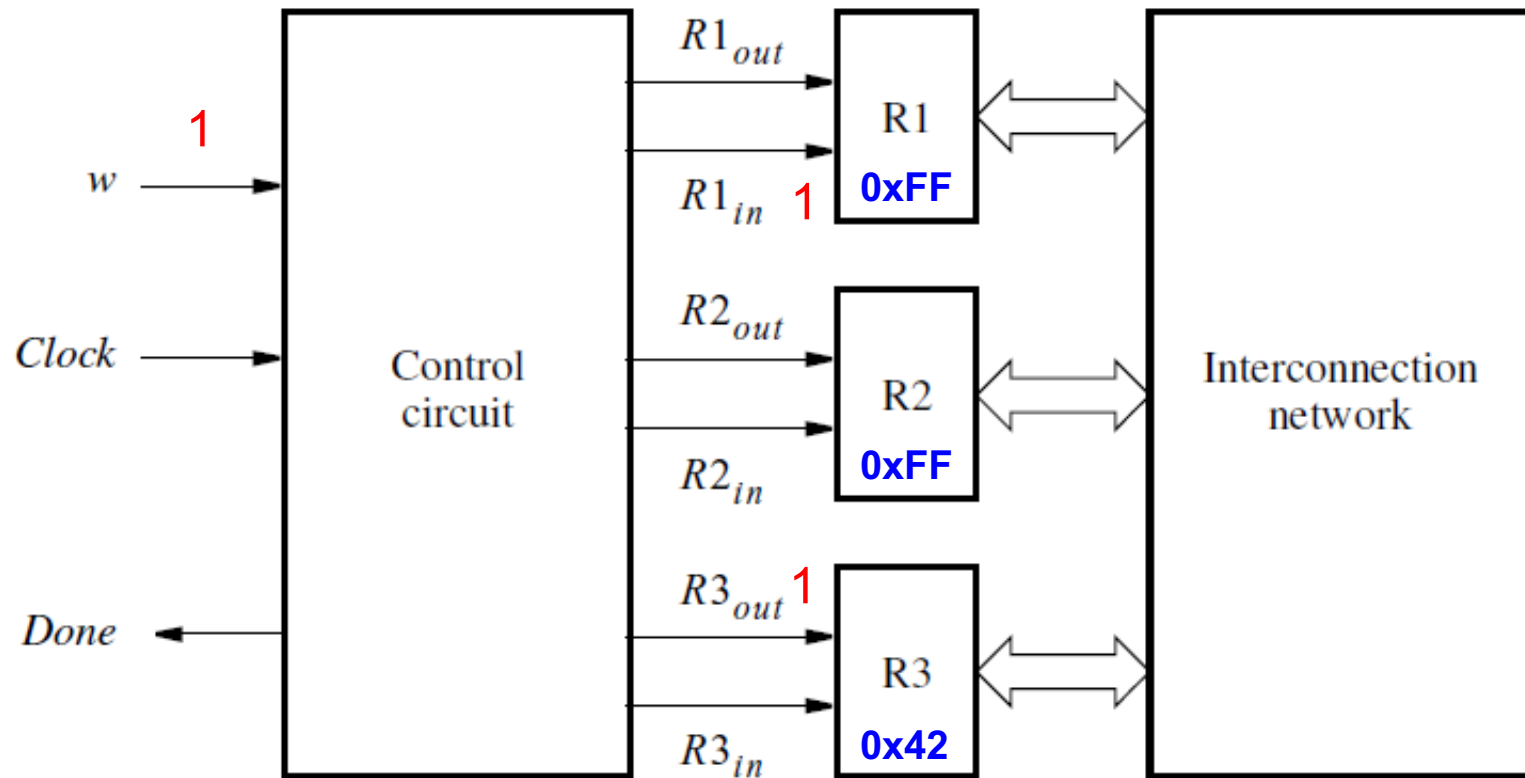


Animated Register Swap

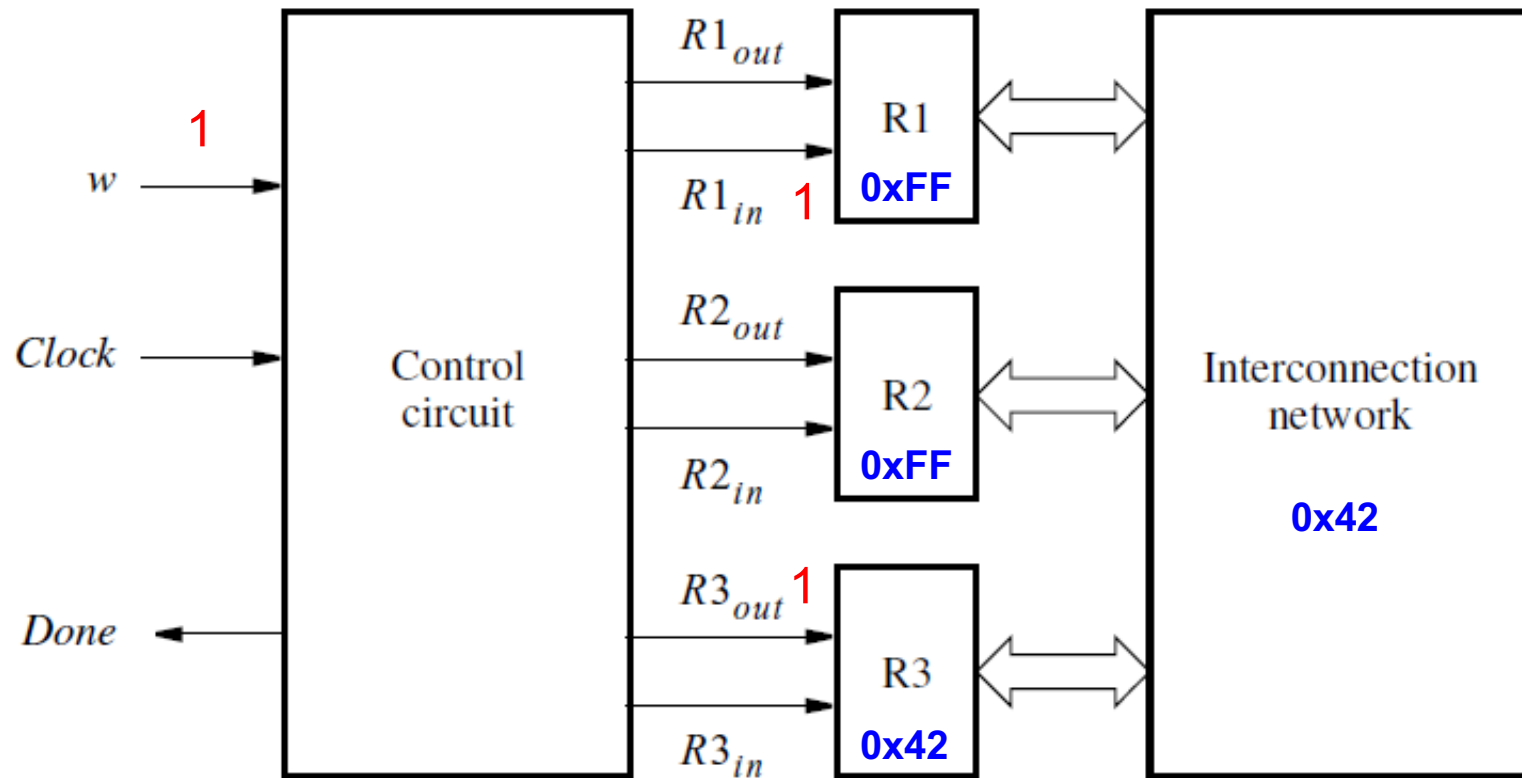


Animated Register Swap

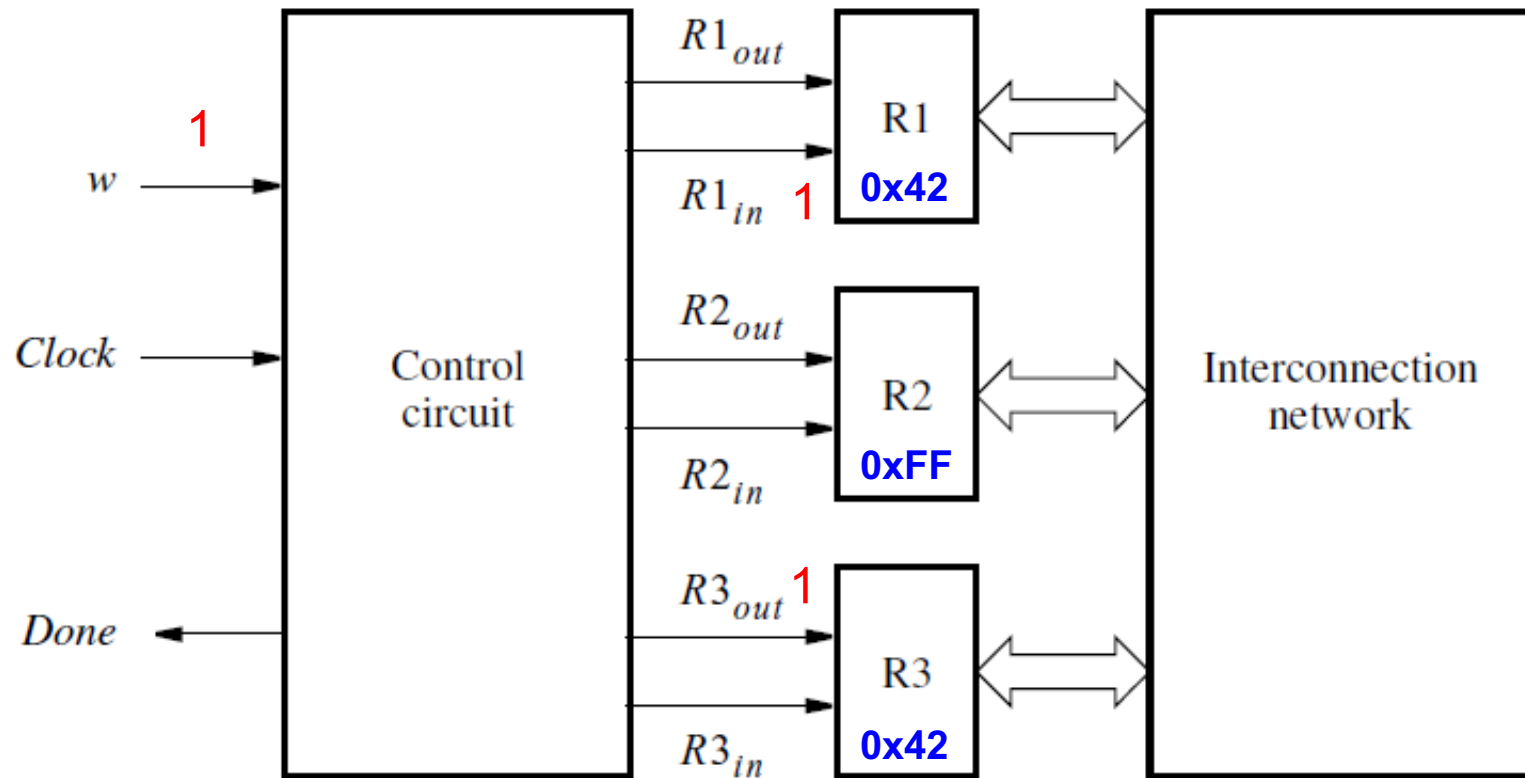

Animated Register Swap

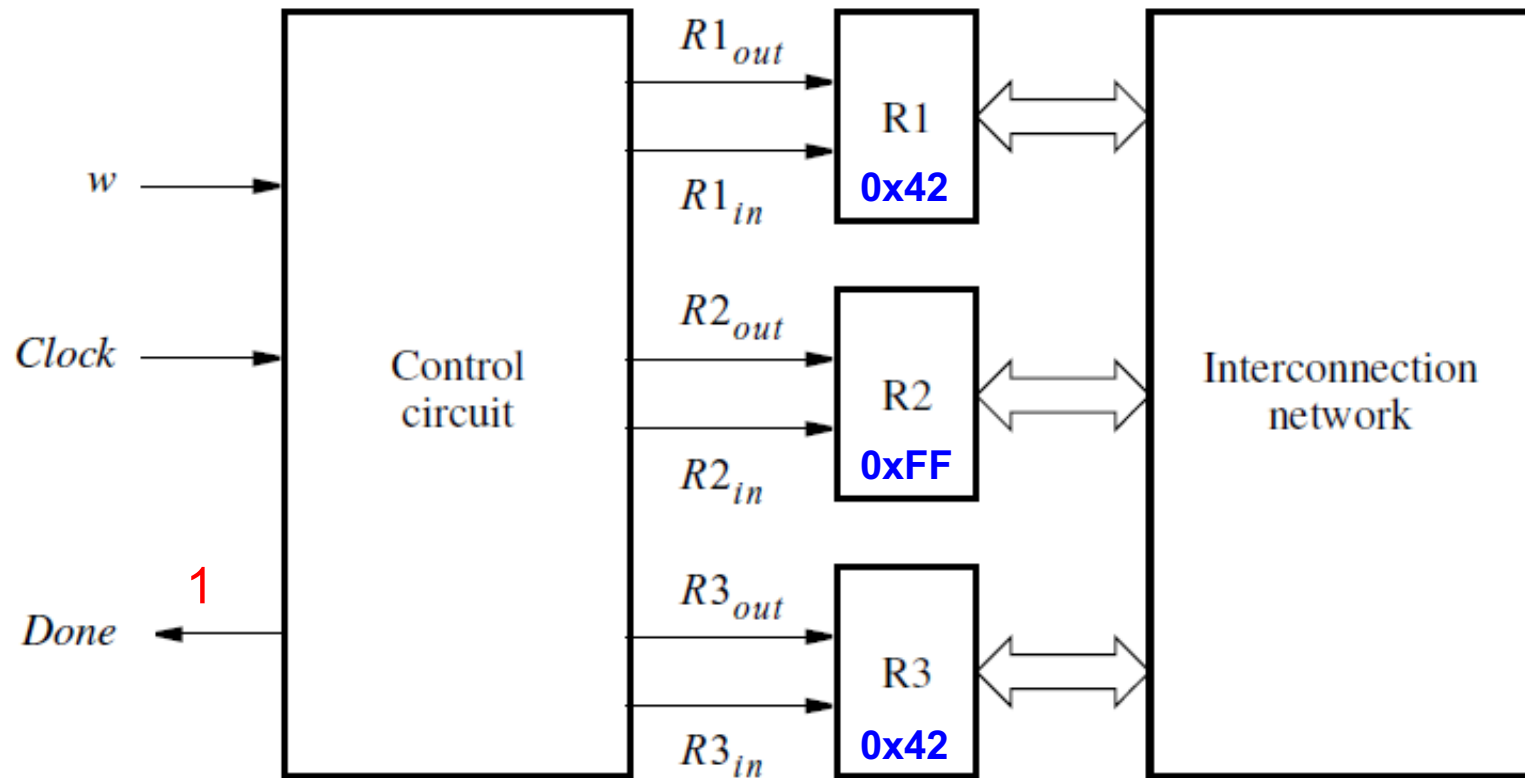



State Diagram


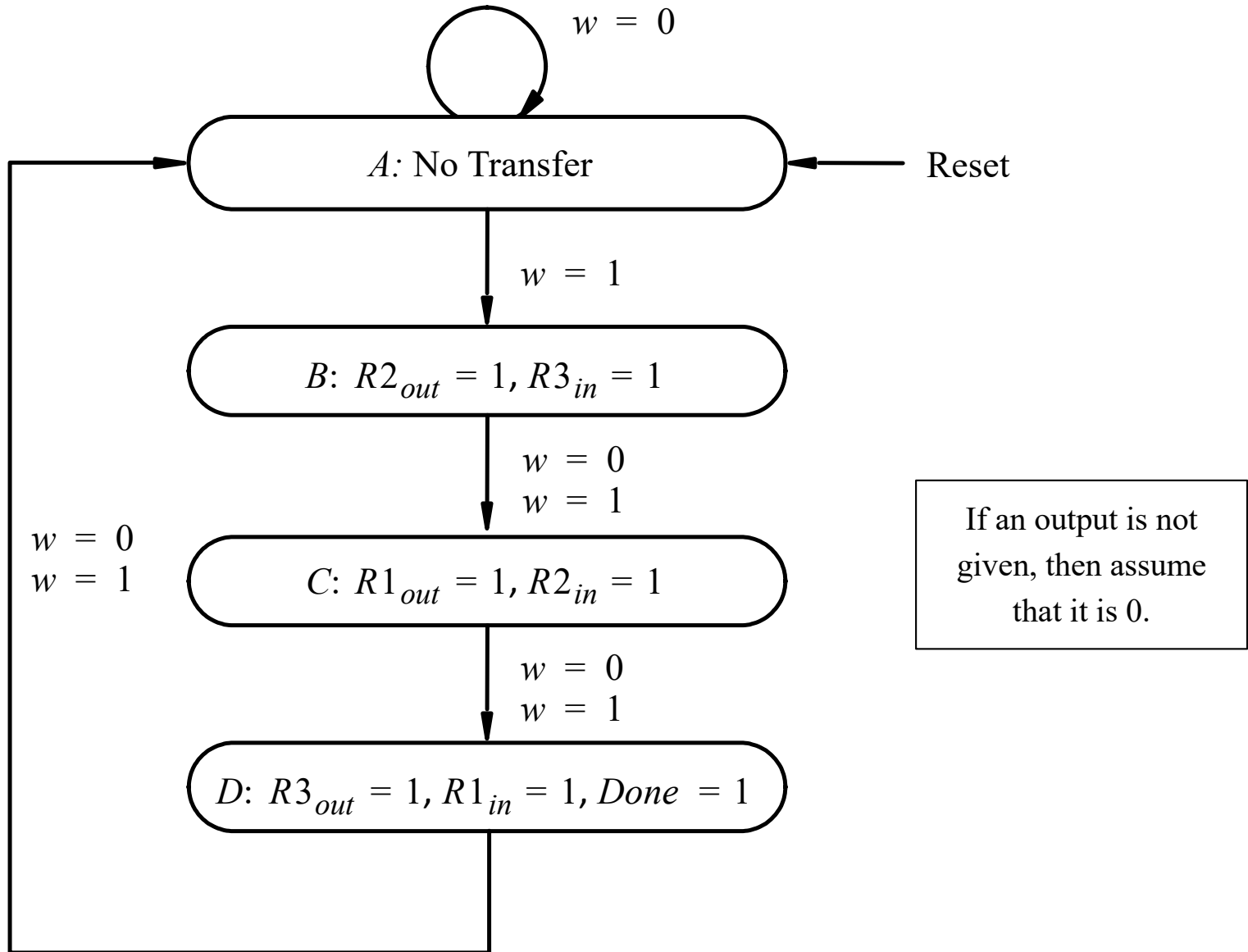



[Figure 6.11 from the textbook]

Some Questions

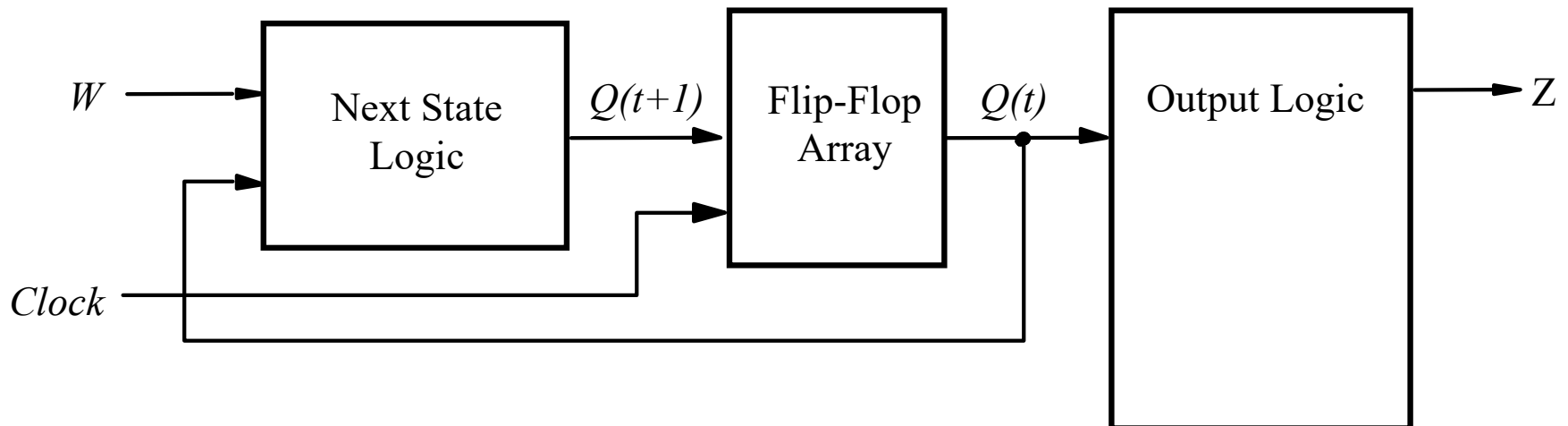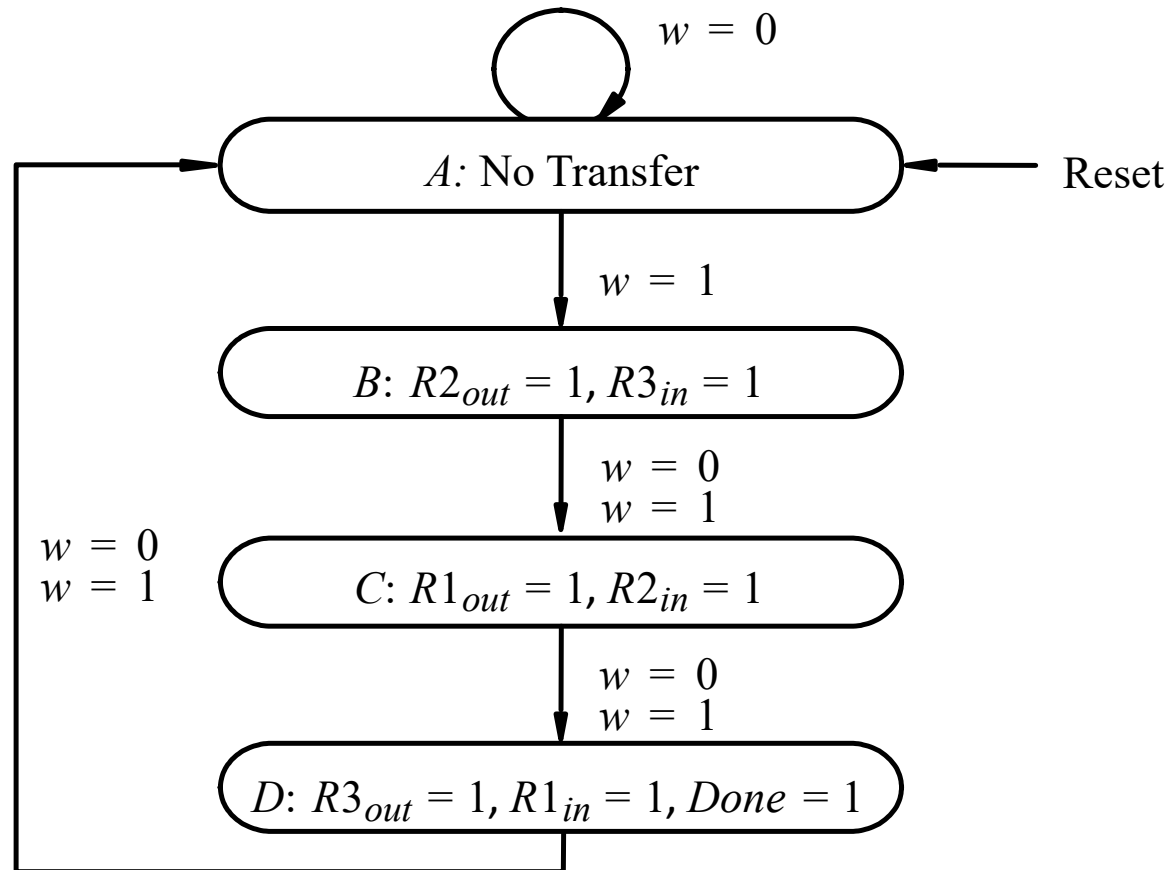- **How many flip-flops are we going to use?**
- **How many logic expressions do we need to find?**



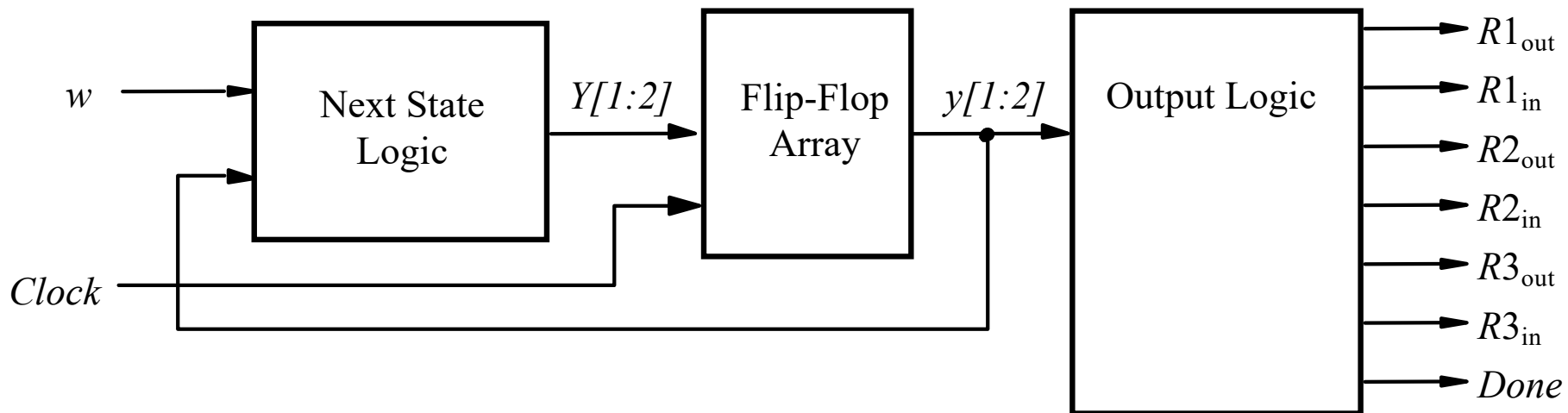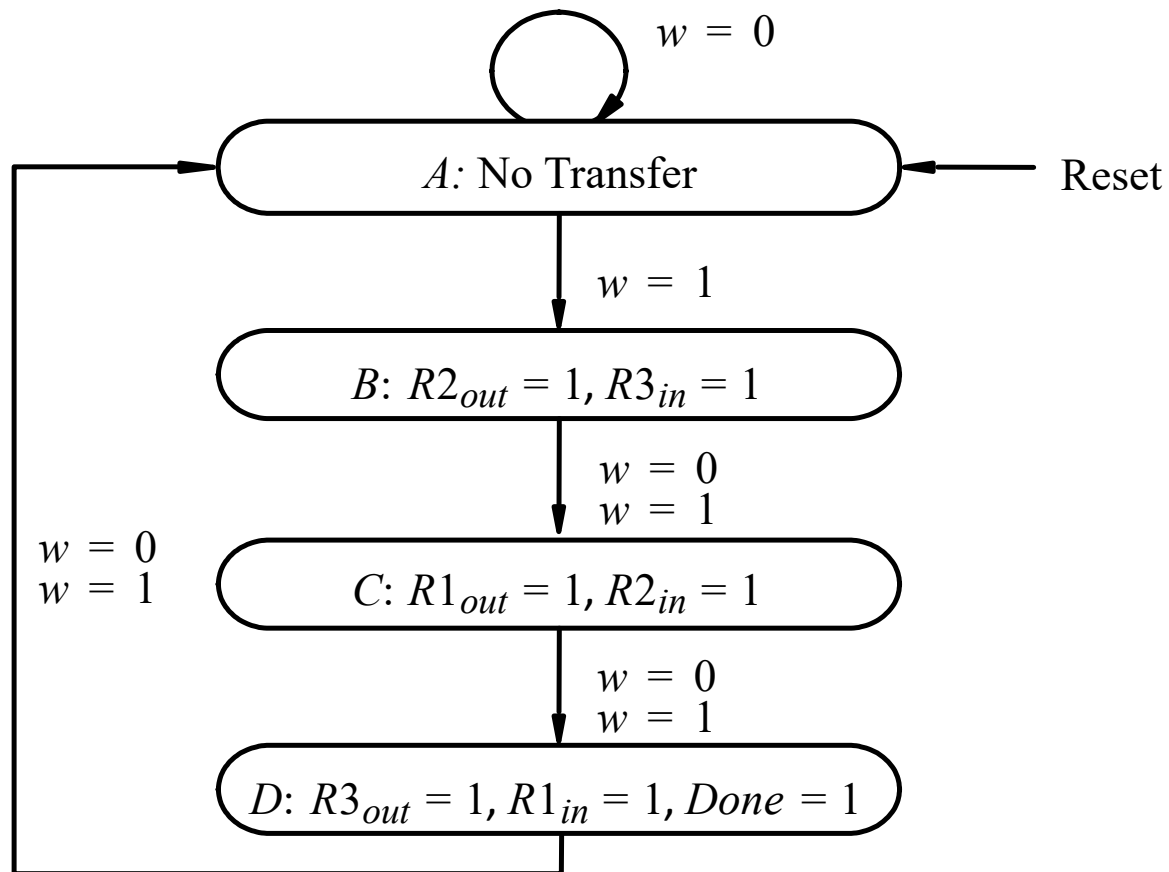

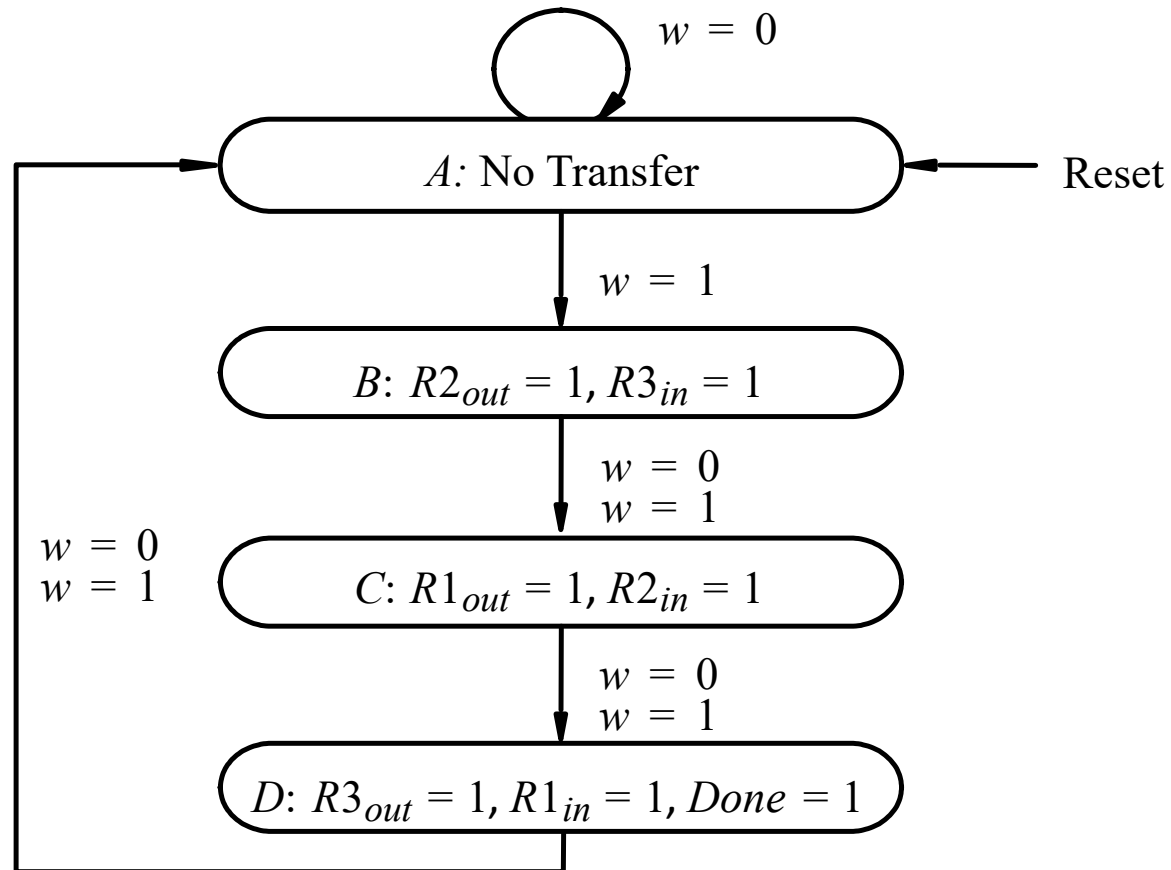

| Present state | Next state | | Outputs | | | | | | |
|---------------|------------|---------|------------|-----------|------------|-----------|------------|-----------|-------------|
| | $w = 0$ | $w = 1$ | $R1_{out}$ | $R1_{in}$ | $R2_{out}$ | $R2_{in}$ | $R3_{out}$ | $R3_{in}$ | <i>Done</i> |
| A | A | B | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| B | C | C | 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| C | D | D | 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| D | A | A | 0 | 1 | 0 | 0 | 1 | 0 | 1 |

As we saw before, we can expect that some state encodings will be better than others.

We will consider three encoding schemes.

Encoding #1:
A=00, B=01, C=10, D=11

(Uses Two Flip-Flops)

State Table

| Present state | Next state | | Outputs | | | | | | |
|---------------|------------|---------|-------------------|------------------|-------------------|------------------|-------------------|------------------|-------------|
| | $w = 0$ | $w = 1$ | R1 _{out} | R1 _{in} | R2 _{out} | R2 _{in} | R3 _{out} | R3 _{in} | <i>Done</i> |
| A | A | B | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| B | C | C | 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| C | D | D | 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| D | A | A | 0 | 1 | 0 | 0 | 1 | 0 | 1 |

State-Assigned Table

| Present state | Next state | | Outputs | | | | | | | |
|---------------|------------|----------|----------|-------------------|------------------|-------------------|------------------|-------------------|------------------|-------------|
| | $w = 0$ | $w = 1$ | | | | | | | | |
| | y_2y_1 | Y_2Y_1 | Y_2Y_1 | R1 _{out} | R1 _{in} | R2 _{out} | R2 _{in} | R3 _{out} | R3 _{in} | <i>Done</i> |
| A | | | | | | | | | | |
| B | | | | | | | | | | |
| C | | | | | | | | | | |
| D | | | | | | | | | | |

State Table

| Present state | Next state | | Outputs | | | | | | |
|---------------|------------|---------|-------------------|------------------|-------------------|------------------|-------------------|------------------|-------------|
| | $w = 0$ | $w = 1$ | R1 _{out} | R1 _{in} | R2 _{out} | R2 _{in} | R3 _{out} | R3 _{in} | <i>Done</i> |
| A | A | B | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| B | C | C | 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| C | D | D | 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| D | A | A | 0 | 1 | 0 | 0 | 1 | 0 | 1 |

State Assigned Table

| | Present state | Next state | | Outputs | | | | | | |
|---|---------------|------------|----------|-------------------|------------------|-------------------|------------------|-------------------|------------------|-------------|
| | | $w = 0$ | $w = 1$ | | | | | | | |
| | y_2y_1 | Y_2Y_1 | Y_2Y_1 | R1 _{out} | R1 _{in} | R2 _{out} | R2 _{in} | R3 _{out} | R3 _{in} | <i>Done</i> |
| A | 00 | | | | | | | | | |
| B | 01 | | | | | | | | | |
| C | 10 | | | | | | | | | |
| D | 11 | | | | | | | | | |

State Table

| Present state | Next state | | Outputs | | | | | | |
|---------------|------------|---------|-------------------|------------------|-------------------|------------------|-------------------|------------------|-------------|
| | $w = 0$ | $w = 1$ | R1 _{out} | R1 _{in} | R2 _{out} | R2 _{in} | R3 _{out} | R3 _{in} | <i>Done</i> |
| A | A | B | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| B | C | C | 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| C | D | D | 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| D | A | A | 0 | 1 | 0 | 0 | 1 | 0 | 1 |

State Assigned Table

| | Present state | Next state | | Outputs | | | | | | |
|---|---------------|------------|----------|-------------------|------------------|-------------------|------------------|-------------------|------------------|-------------|
| | | $w = 0$ | $w = 1$ | | | | | | | |
| | y_2y_1 | Y_2Y_1 | Y_2Y_1 | R1 _{out} | R1 _{in} | R2 _{out} | R2 _{in} | R3 _{out} | R3 _{in} | <i>Done</i> |
| A | 00 | 00 | 01 | | | | | | | |
| B | 01 | 10 | 10 | | | | | | | |
| C | 10 | 11 | 11 | | | | | | | |
| D | 11 | 00 | 00 | | | | | | | |

State Table

| Present state | Next state | | Outputs | | | | | | |
|---------------|------------|---------|-------------------|------------------|-------------------|------------------|-------------------|------------------|-------------|
| | $w = 0$ | $w = 1$ | R1 _{out} | R1 _{in} | R2 _{out} | R2 _{in} | R3 _{out} | R3 _{in} | <i>Done</i> |
| A | A | B | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| B | C | C | 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| C | D | D | 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| D | A | A | 0 | 1 | 0 | 0 | 1 | 0 | 1 |

State Assigned Table

| | Present state | Next state | | Outputs | | | | | | |
|---|---------------|------------|---------|-------------------|------------------|-------------------|------------------|-------------------|------------------|-------------|
| | | $w = 0$ | $w = 1$ | R1 _{out} | R1 _{in} | R2 _{out} | R2 _{in} | R3 _{out} | R3 _{in} | <i>Done</i> |
| | Y_2Y_1 | Y_2Y_1 | | | | | | | | |
| A | 00 | 00 | 0 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| B | 01 | 10 | 1 0 | 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| C | 10 | 11 | 1 1 | 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| D | 11 | 00 | 0 0 | 0 | 1 | 0 | 0 | 1 | 0 | 1 |

| | Present state | Next state | | Outputs | | | | | | |
|---|---------------|------------|----------|------------|-----------|------------|-----------|------------|-----------|-------------|
| | | $w = 0$ | $w = 1$ | | | | | | | |
| | y_2y_1 | Y_2Y_1 | Y_2Y_1 | $R1_{out}$ | $R1_{in}$ | $R2_{out}$ | $R2_{in}$ | $R3_{out}$ | $R3_{in}$ | <i>Done</i> |
| A | 00 | 00 | 0 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| B | 01 | 10 | 1 0 | 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| C | 10 | 11 | 1 1 | 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| D | 11 | 00 | 0 0 | 0 | 1 | 0 | 0 | 1 | 0 | 1 |

| y_2 | y_1 | w | Y_2 | Y_1 |
|-------|-------|-----|-------|-------|
| 0 | 0 | 0 | | |
| 0 | 0 | 1 | | |
| 0 | 1 | 0 | | |
| 0 | 1 | 1 | | |
| 1 | 0 | 0 | | |
| 1 | 0 | 1 | | |
| 1 | 1 | 0 | | |
| 1 | 1 | 1 | | |

Let's derive the next-state expressions.



| | Present state | Next state | | Outputs | | | | | | |
|---|---------------|------------|----------|------------|-----------|------------|-----------|------------|-----------|-------------|
| | | $w = 0$ | $w = 1$ | | | | | | | |
| | y_2y_1 | Y_2Y_1 | Y_2Y_1 | $R1_{out}$ | $R1_{in}$ | $R2_{out}$ | $R2_{in}$ | $R3_{out}$ | $R3_{in}$ | <i>Done</i> |
| A | 00 | 00 | 0 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| B | 01 | 10 | 1 0 | 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| C | 10 | 11 | 1 1 | 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| D | 11 | 00 | 0 0 | 0 | 1 | 0 | 0 | 1 | 0 | 1 |

| y_2 | y_1 | w | Y_2 | Y_1 |
|-------|-------|-----|-------|-------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 | 1 |
| 1 | 0 | 1 | 1 | 1 |
| 1 | 1 | 0 | 0 | 0 |
| 1 | 1 | 1 | 0 | 0 |

Pay attention to the way the columns of the truth table are labeled.

| | Present state | Next state | | Outputs | | | | | | |
|---|---------------|------------|----------|------------|-----------|------------|-----------|------------|-----------|-------------|
| | | $w = 0$ | $w = 1$ | | | | | | | |
| | y_2y_1 | Y_2Y_1 | Y_2Y_1 | $R1_{out}$ | $R1_{in}$ | $R2_{out}$ | $R2_{in}$ | $R3_{out}$ | $R3_{in}$ | <i>Done</i> |
| A | 00 | 00 | 0 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| B | 01 | 10 | 1 0 | 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| C | 10 | 11 | 1 1 | 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| D | 11 | 00 | 0 0 | 0 | 1 | 0 | 0 | 1 | 0 | 1 |

| y_2 | y_1 | w | Y_2 | Y_1 |
|-------|-------|-----|-------|-------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 | 1 |
| 1 | 0 | 1 | 1 | 1 |
| 1 | 1 | 0 | 0 | 0 |
| 1 | 1 | 1 | 0 | 0 |

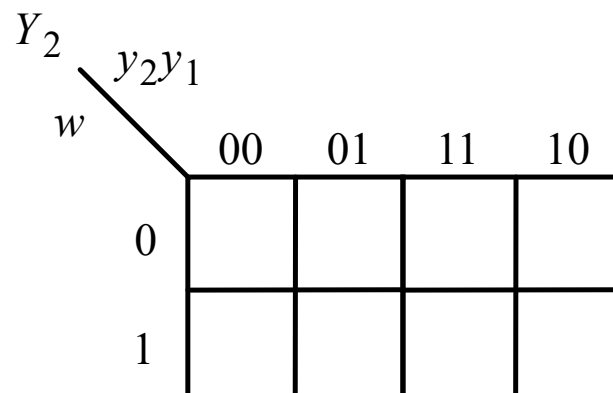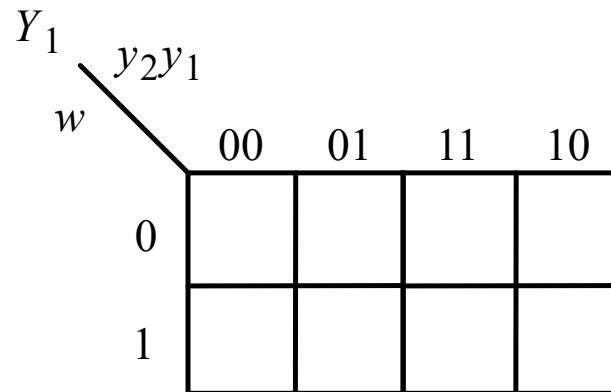

| | Present state | Next state | | Outputs | | | | | | |
|---|---------------|------------|----------|------------|-----------|------------|-----------|------------|-----------|-------------|
| | | $w = 0$ | $w = 1$ | | | | | | | |
| | y_2y_1 | Y_2Y_1 | Y_2Y_1 | $R1_{out}$ | $R1_{in}$ | $R2_{out}$ | $R2_{in}$ | $R3_{out}$ | $R3_{in}$ | <i>Done</i> |
| A | 00 | 00 | 0 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| B | 01 | 10 | 1 0 | 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| C | 10 | 11 | 1 1 | 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| D | 11 | 00 | 0 0 | 0 | 1 | 0 | 0 | 1 | 0 | 1 |

| y_2 | y_1 | w | Y_2 | Y_1 |
|-------|-------|-----|-------|-------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 | 1 |
| 1 | 0 | 1 | 1 | 1 |
| 1 | 1 | 0 | 0 | 0 |
| 1 | 1 | 1 | 0 | 0 |

Y_1



| w | y_2y_1 | 00 | 01 | 11 | 10 |
|-----|----------|----|----|----|----|
| 0 | | 0 | 0 | 0 | 1 |
| 1 | | 1 | 0 | 0 | 1 |

Y_2

| w | y_2y_1 | 00 | 01 | 11 | 10 |
|-----|----------|----|----|----|----|
| 0 | | 0 | 1 | 0 | 1 |
| 1 | | 0 | 1 | 0 | 1 |


| | Present state | Next state | | Outputs | | | | | | |
|---|---------------|------------|----------|------------|-----------|------------|-----------|------------|-----------|-------------|
| | | $w = 0$ | $w = 1$ | | | | | | | |
| | y_2y_1 | Y_2Y_1 | Y_2Y_1 | $R1_{out}$ | $R1_{in}$ | $R2_{out}$ | $R2_{in}$ | $R3_{out}$ | $R3_{in}$ | <i>Done</i> |
| A | 00 | 00 | 0 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| B | 01 | 10 | 1 0 | 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| C | 10 | 11 | 1 1 | 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| D | 11 | 00 | 0 0 | 0 | 1 | 0 | 0 | 1 | 0 | 1 |

| y_2 | y_1 | w | Y_2 | Y_1 |
|-------|-------|-----|-------|-------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 | 1 |
| 1 | 0 | 1 | 1 | 1 |
| 1 | 1 | 0 | 0 | 0 |
| 1 | 1 | 1 | 0 | 0 |

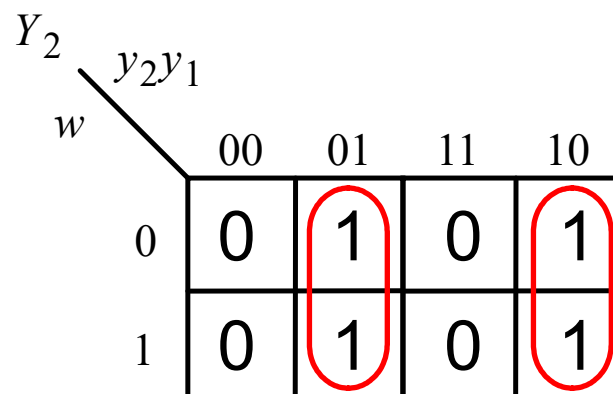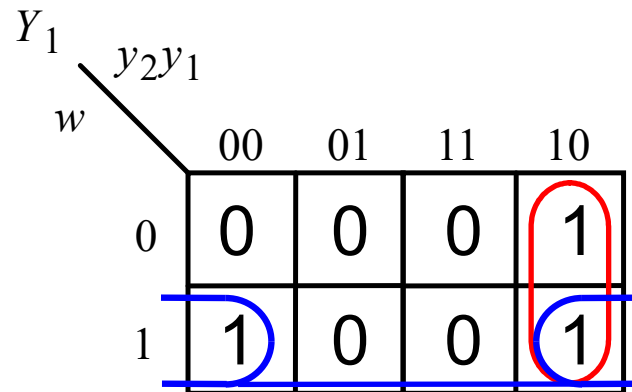


| | Present state | Next state | | Outputs | | | | | | |
|---|---------------|------------|----------|------------|-----------|------------|-----------|------------|-----------|-------------|
| | | $w = 0$ | $w = 1$ | $R1_{out}$ | $R1_{in}$ | $R2_{out}$ | $R2_{in}$ | $R3_{out}$ | $R3_{in}$ | <i>Done</i> |
| | y_2y_1 | Y_2Y_1 | Y_2Y_1 | | | | | | | |
| A | 00 | 00 | 01 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| B | 01 | 10 | 10 | 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| C | 10 | 11 | 11 | 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| D | 11 | 00 | 00 | 0 | 1 | 0 | 0 | 1 | 0 | 1 |

| y_2 | y_1 | w | Y_2 | Y_1 |
|-------|-------|-----|-------|-------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 | 1 |
| 1 | 0 | 1 | 1 | 1 |
| 1 | 1 | 0 | 0 | 0 |
| 1 | 1 | 1 | 0 | 0 |

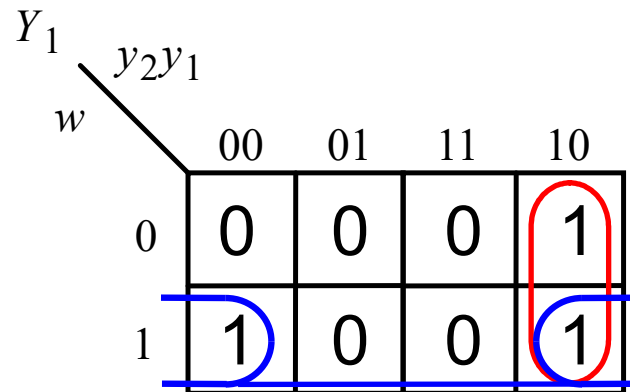

$$Y_1 = w\bar{y}_1 + \bar{y}_1y_2$$

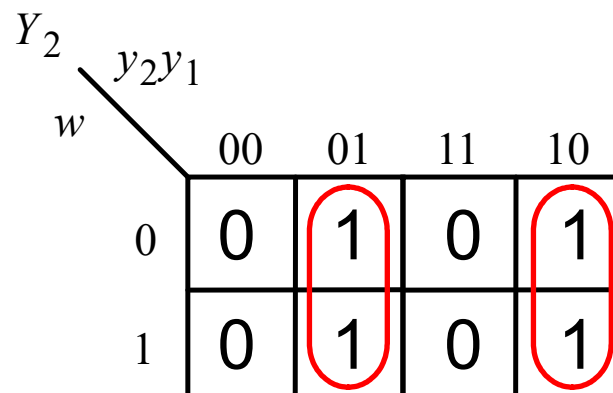

$$Y_2 = y_1\bar{y}_2 + \bar{y}_1y_2$$

| | Present state | Next state | | Outputs | | | | | | |
|---|---------------|------------|----------|------------|-----------|------------|-----------|------------|-----------|-------------|
| | | $w = 0$ | $w = 1$ | | | | | | | |
| | y_2y_1 | Y_2Y_1 | Y_2Y_1 | $R1_{out}$ | $R1_{in}$ | $R2_{out}$ | $R2_{in}$ | $R3_{out}$ | $R3_{in}$ | <i>Done</i> |
| A | 00 | 00 | 0 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| B | 01 | 10 | 1 0 | 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| C | 10 | 11 | 1 1 | 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| D | 11 | 00 | 0 0 | 0 | 1 | 0 | 0 | 1 | 0 | 1 |

| y_2 | y_1 | $R1_{out}$ | $R1_{in}$ | $R2_{out}$ |
|-------|-------|------------|-----------|------------|
| 0 | 0 | | | |
| 0 | 1 | | | |
| 1 | 0 | | | |
| 1 | 1 | | | |

Let's derive the output expressions

| | Present state | Next state | | Outputs | | | | | | |
|---|---------------|------------|----------|------------|-----------|------------|-----------|------------|-----------|-------------|
| | | $w = 0$ | $w = 1$ | | | | | | | |
| | y_2y_1 | Y_2Y_1 | Y_2Y_1 | $R1_{out}$ | $R1_{in}$ | $R2_{out}$ | $R2_{in}$ | $R3_{out}$ | $R3_{in}$ | <i>Done</i> |
| A | 00 | 00 | 0 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| B | 01 | 10 | 1 0 | 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| C | 10 | 11 | 1 1 | 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| D | 11 | 00 | 0 0 | 0 | 1 | 0 | 0 | 1 | 0 | 1 |

| y_2 | y_1 | $R1_{out}$ | $R1_{in}$ | $R2_{out}$ |
|-------|-------|------------|-----------|------------|
| 0 | 0 | | | |
| 0 | 1 | | | |
| 1 | 0 | | | |
| 1 | 1 | | | |

Let's derive the output expressions.

We need to derive only these 3 unique ones.

| | Present state | Next state | | Outputs | | | | | | |
|---|---------------|------------|----------|------------|-----------|------------|-----------|------------|-----------|-------------|
| | | $w = 0$ | $w = 1$ | | | | | | | |
| | y_2y_1 | Y_2Y_1 | Y_2Y_1 | $R1_{out}$ | $R1_{in}$ | $R2_{out}$ | $R2_{in}$ | $R3_{out}$ | $R3_{in}$ | <i>Done</i> |
| A | 00 | 00 | 0 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| B | 01 | 10 | 1 0 | 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| C | 10 | 11 | 1 1 | 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| D | 11 | 00 | 0 0 | 0 | 1 | 0 | 0 | 1 | 0 | 1 |

| y_2 | y_1 | $R1_{out}$ | $R1_{in}$ | $R2_{out}$ |
|-------|-------|------------|-----------|------------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 | 0 |
| 1 | 1 | 0 | 1 | 0 |


| | Present state | Next state | | Outputs | | | | | | |
|---|---------------|------------|-----------|------------|-----------|------------|-----------|------------|-----------|-------------|
| | | $w = 0$ | $w = 1$ | | | | | | | |
| | $y_2 y_1$ | $Y_2 Y_1$ | $Y_2 Y_1$ | $R1_{out}$ | $R1_{in}$ | $R2_{out}$ | $R2_{in}$ | $R3_{out}$ | $R3_{in}$ | <i>Done</i> |
| A | 00 | 00 | 0 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| B | 01 | 10 | 1 0 | 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| C | 10 | 11 | 1 1 | 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| D | 11 | 00 | 0 0 | 0 | 1 | 0 | 0 | 1 | 0 | 1 |

| y_2 | y_1 | $R1_{out}$ | $R1_{in}$ | $R2_{out}$ |
|-------|-------|------------|-----------|------------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 | 0 |
| 1 | 1 | 0 | 1 | 0 |

$$R1_{out} = R2_{in} = \overline{y_1} y_2$$

$$R1_{in} = R3_{out} = Done = y_1 y_2$$

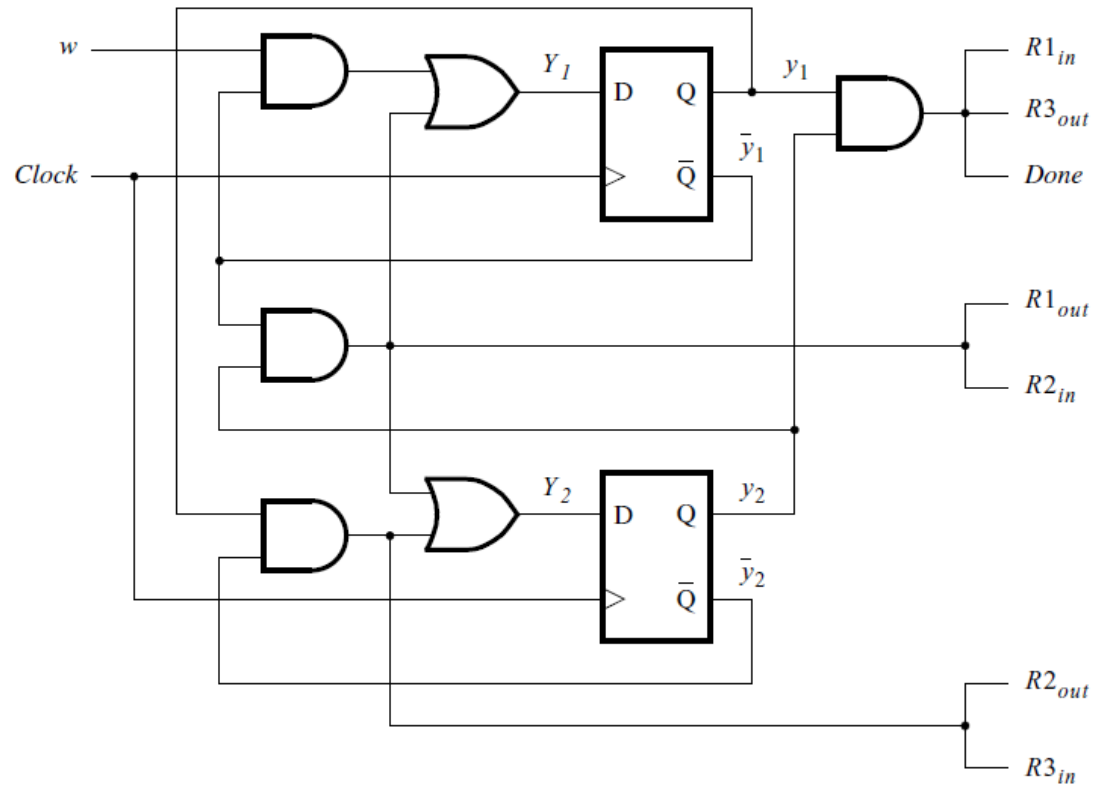
$$R2_{out} = R3_{in} = y_1 \overline{y_2}$$




| | Present state | Next state | | Outputs | | | | | | |
|---|---------------|------------|----------|------------|-----------|------------|-----------|------------|-----------|--------|
| | | $w = 0$ | $w = 1$ | | | | | | | |
| | y_2y_1 | Y_2Y_1 | Y_2Y_1 | $R1_{out}$ | $R1_{in}$ | $R2_{out}$ | $R2_{in}$ | $R3_{out}$ | $R3_{in}$ | $Done$ |
| A | 00 | 00 | 0 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| B | 01 | 10 | 1 0 | 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| C | 10 | 11 | 1 1 | 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| D | 11 | 00 | 0 0 | 0 | 1 | 0 | 0 | 1 | 0 | 1 |


$$Y_1 = w\bar{y}_1 + \bar{y}_1y_2$$


$$Y_2 = y_1\bar{y}_2 + \bar{y}_1y_2$$

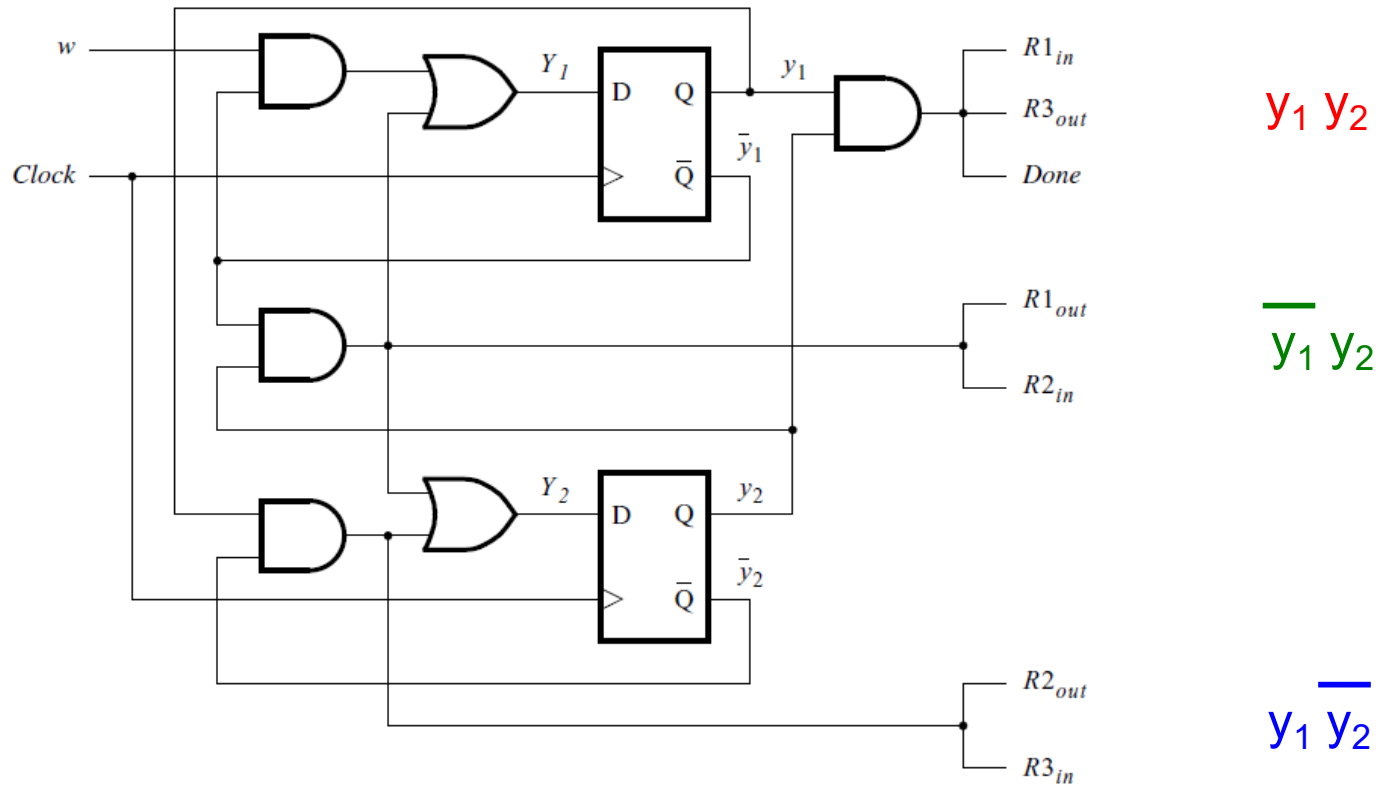



| | Present state | Next state | | Outputs | | | | | | |
|---|---------------|------------|----------|------------|-----------|------------|-----------|------------|-----------|--------|
| | | $w = 0$ | $w = 1$ | | | | | | | |
| | y_2y_1 | Y_2Y_1 | Y_2Y_1 | $R1_{out}$ | $R1_{in}$ | $R2_{out}$ | $R2_{in}$ | $R3_{out}$ | $R3_{in}$ | $Done$ |
| A | 00 | 00 | 0 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| B | 01 | 10 | 1 0 | 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| C | 10 | 11 | 1 1 | 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| D | 11 | 00 | 0 0 | 0 | 1 | 0 | 0 | 1 | 0 | 1 |


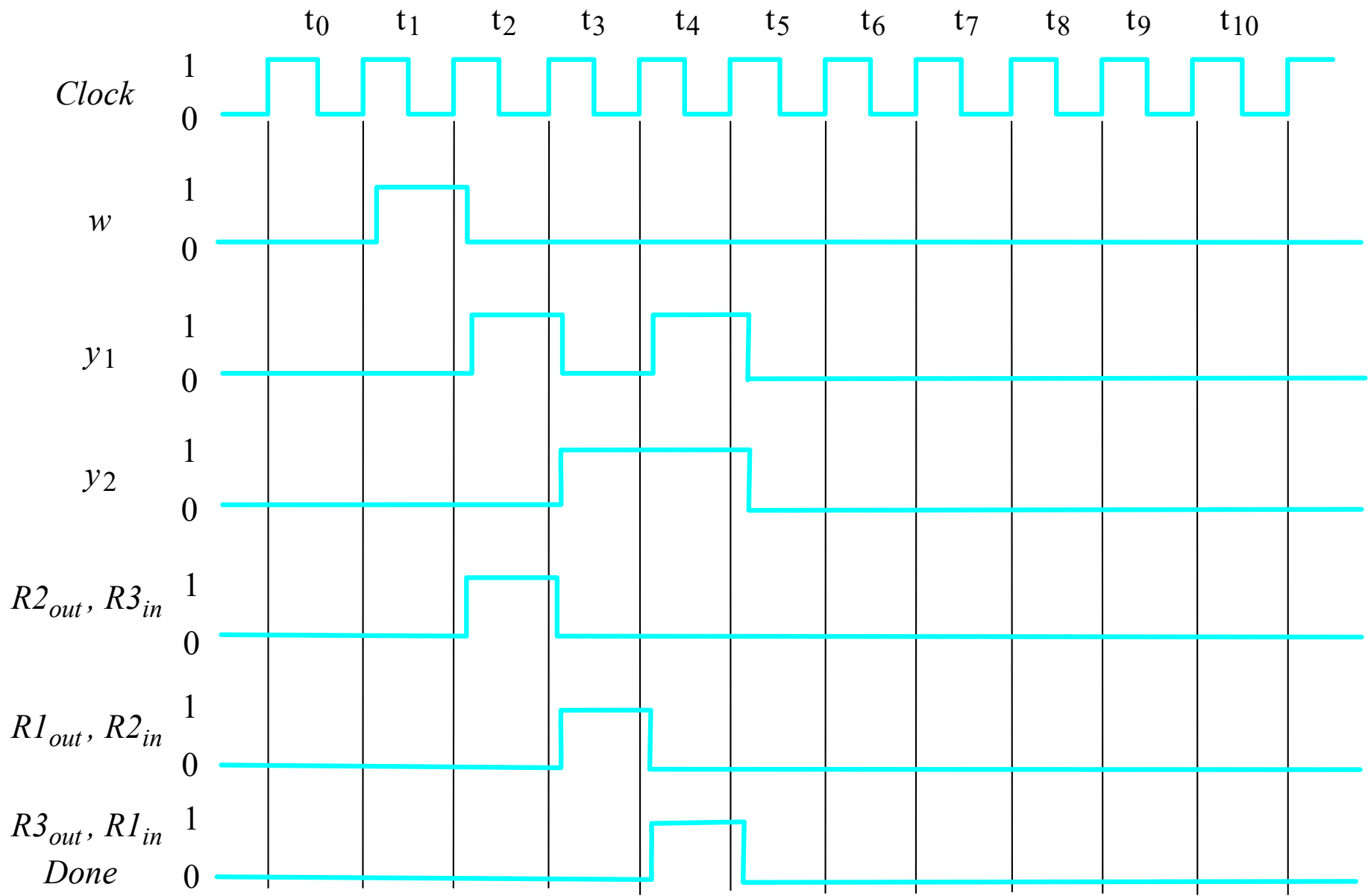


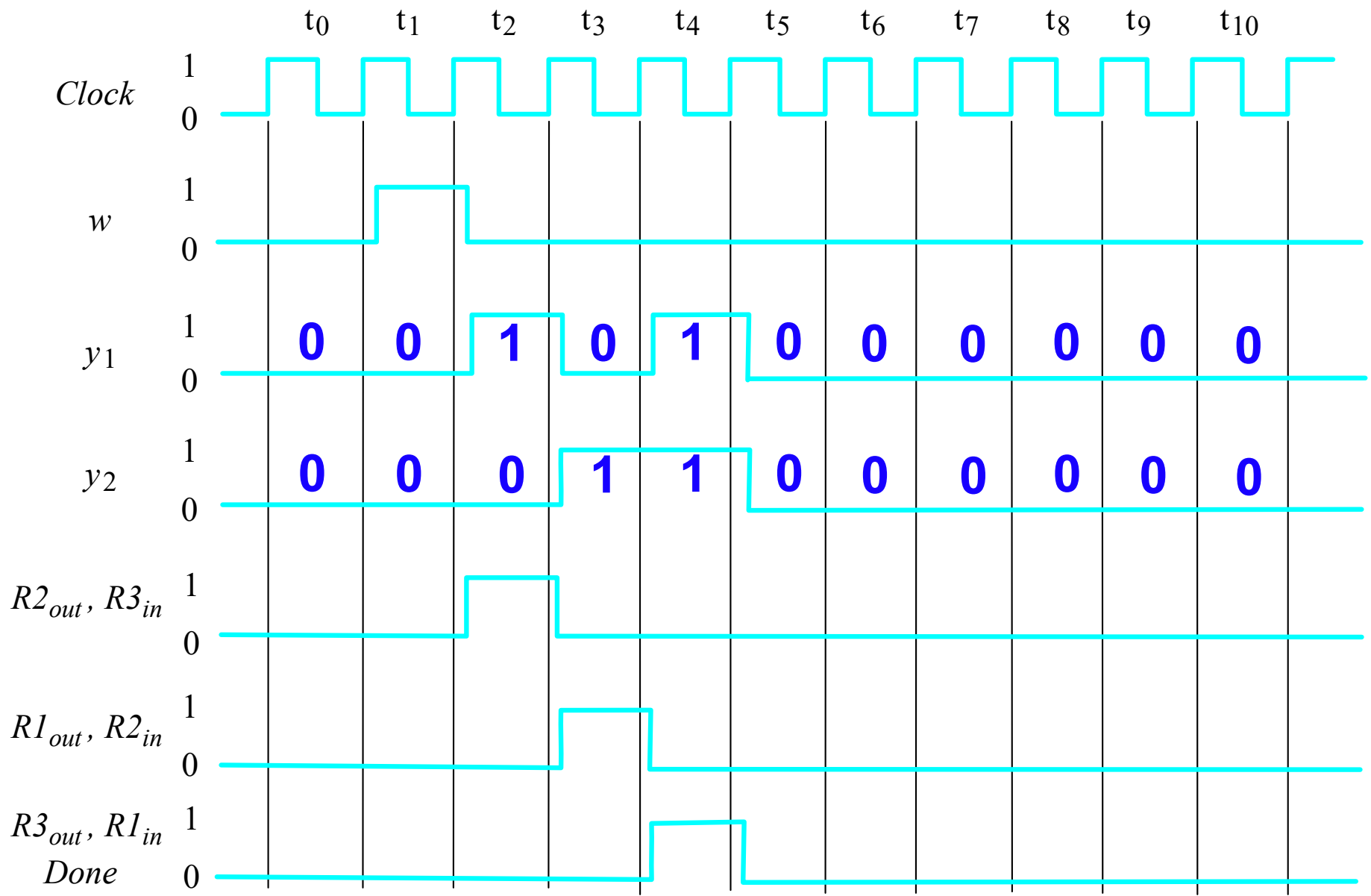


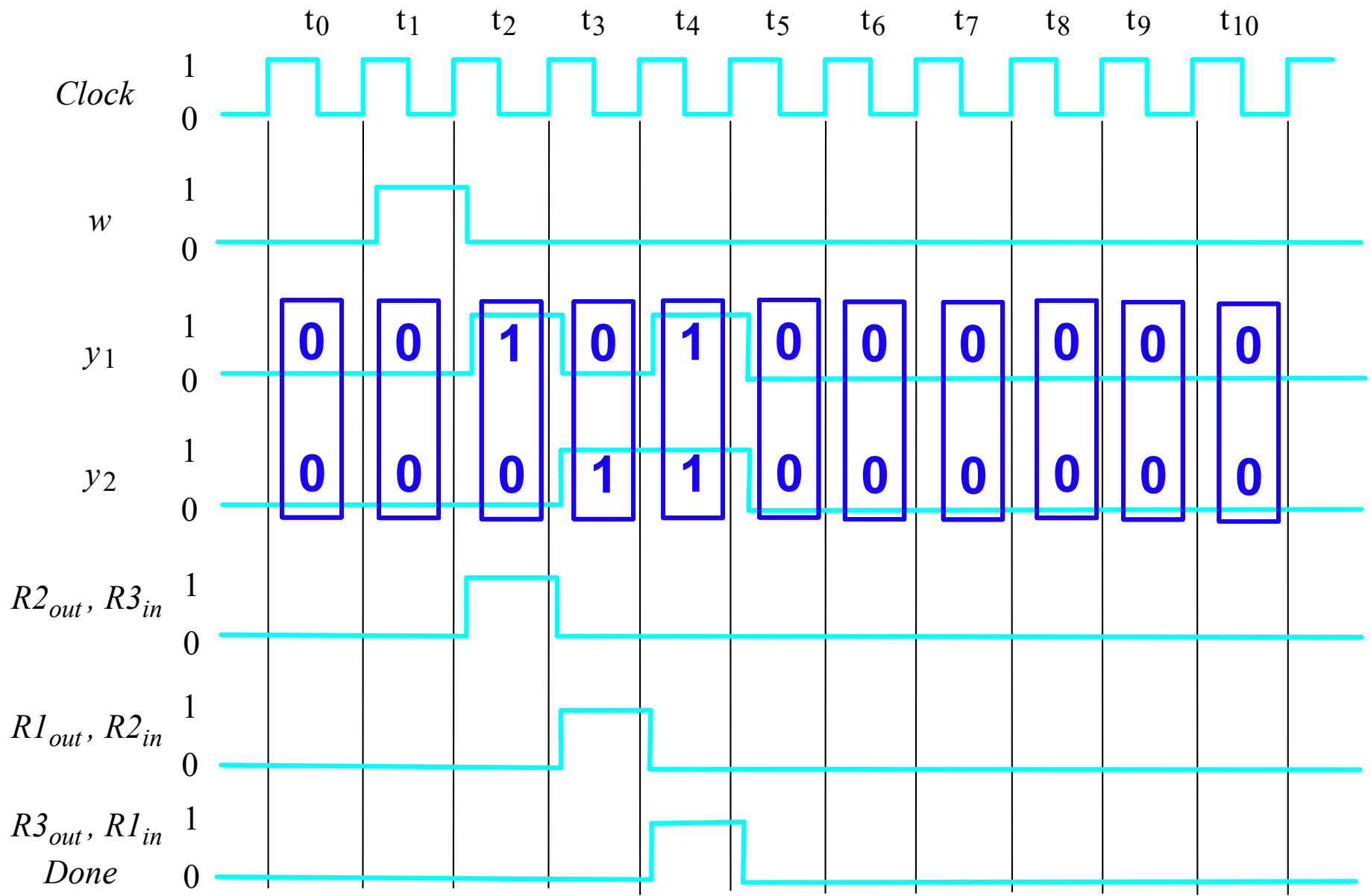

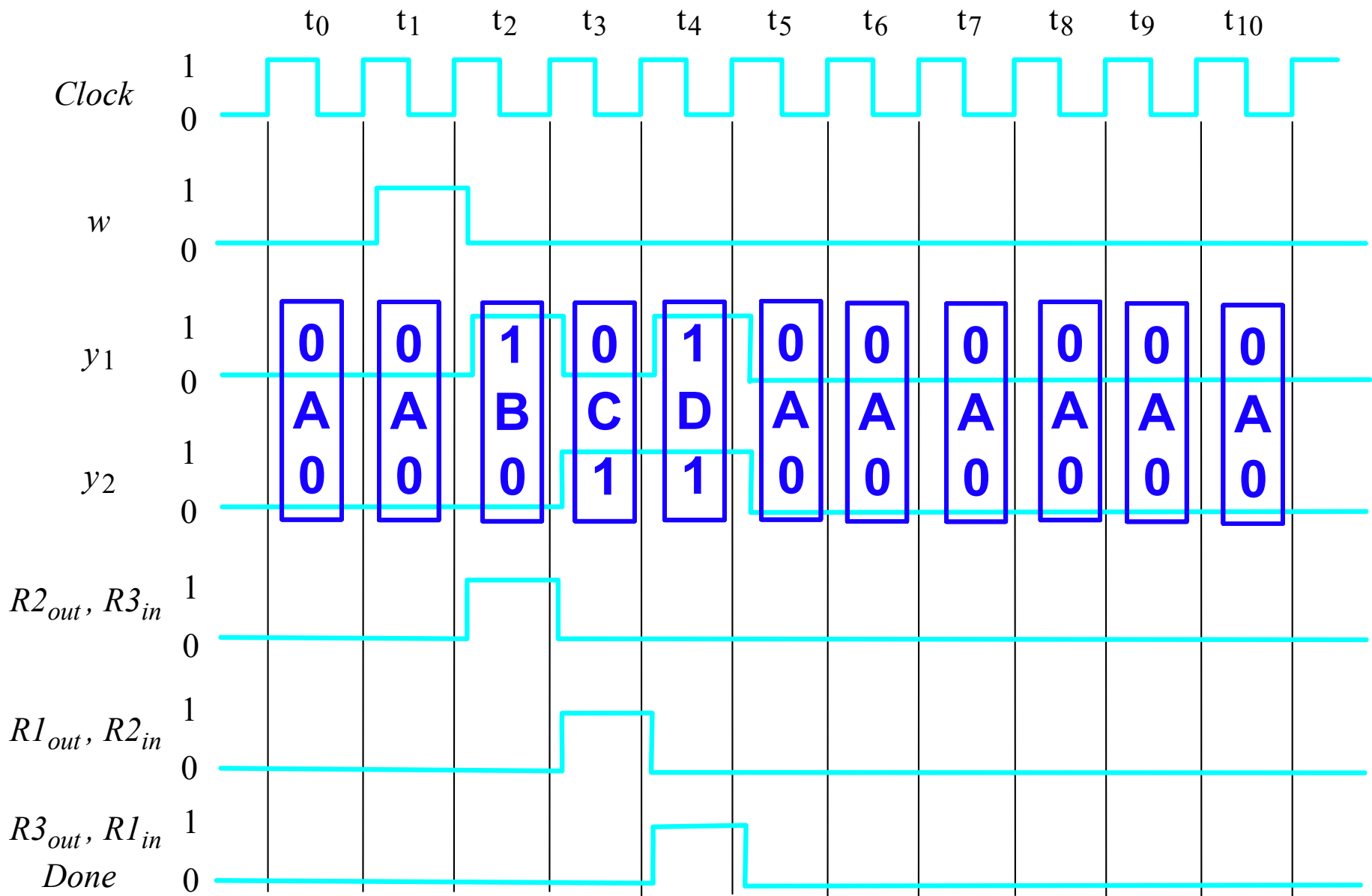

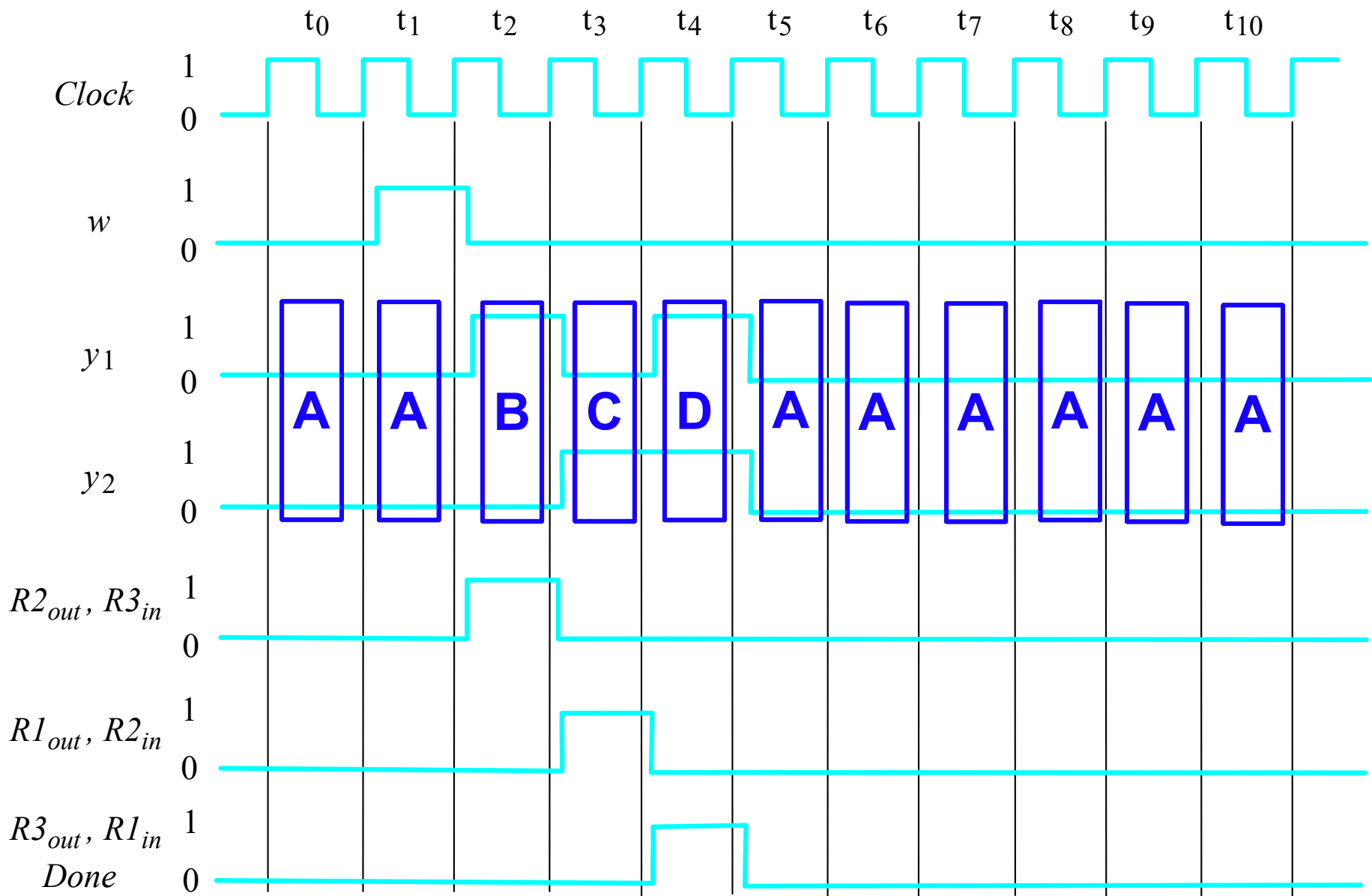

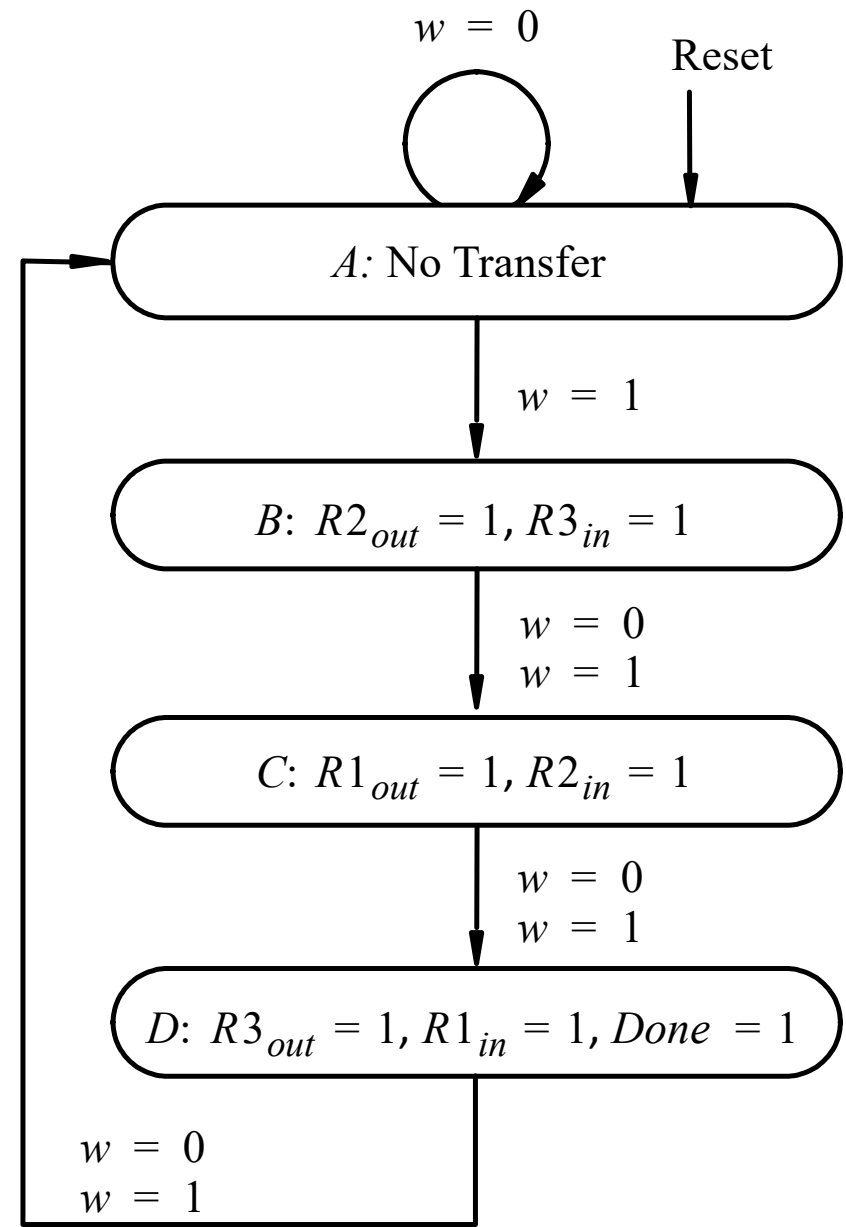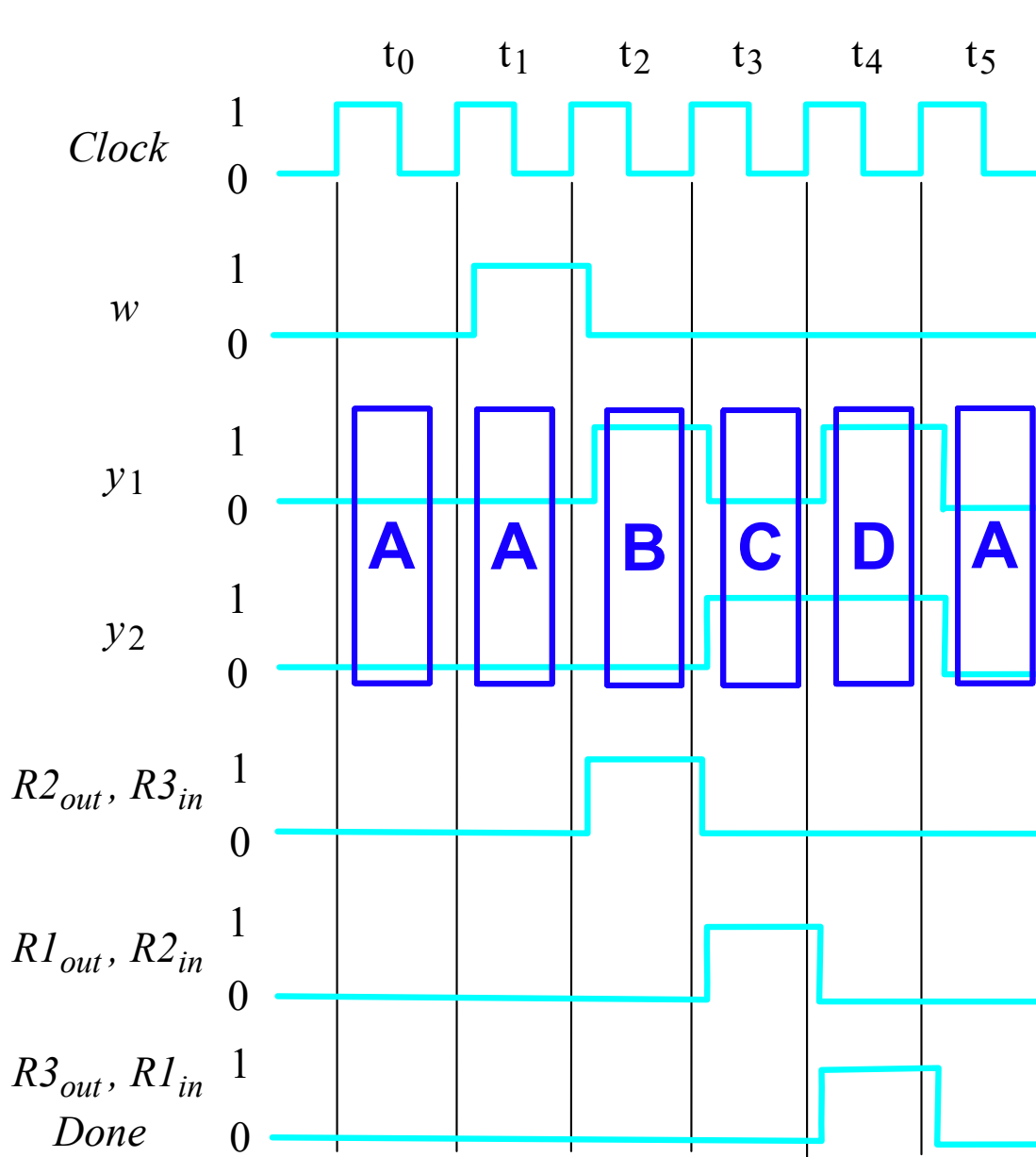

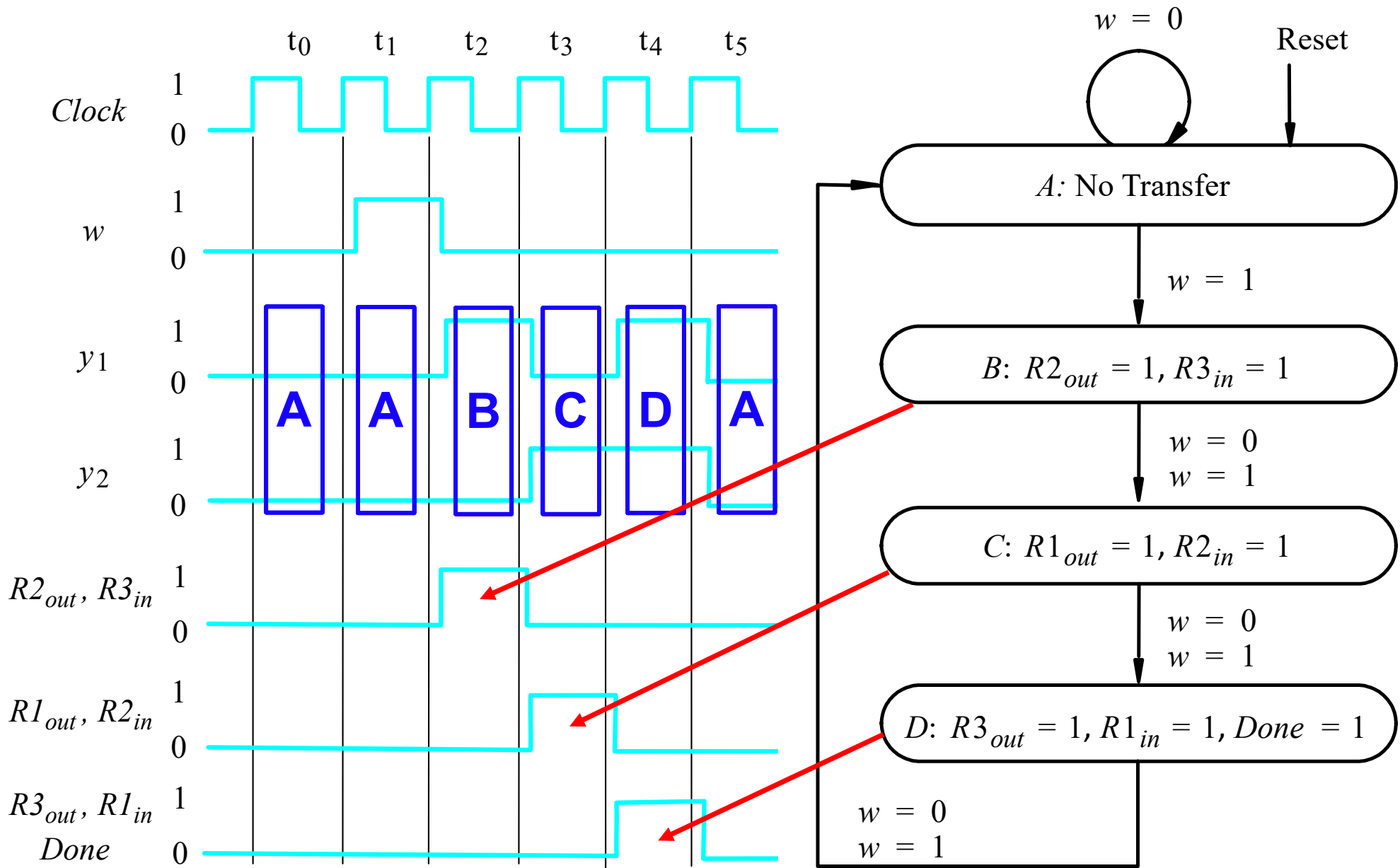

Encoding #2:

A=00, B=01, C=11, D=10

(Also Uses Two Flip-Flops)

State Table (same as before)

| Present state | Next state | | Outputs | | | | | | |
|------------------|------------|---------|-------------------|------------------|-------------------|------------------|-------------------|------------------|-------------|
| | $w = 0$ | $w = 1$ | R1 _{out} | R1 _{in} | R2 _{out} | R2 _{in} | R3 _{out} | R3 _{in} | <i>Done</i> |
| A | A | B | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| B | C | C | 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| C | D | D | 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| D | A | A | 0 | 1 | 0 | 0 | 1 | 0 | 1 |

State-Assigned Table

| Present state y_2y_1 | Next state | | Outputs | | | | | | |
|----------------------------------|------------|----------|-------------------|------------------|-------------------|------------------|-------------------|------------------|-------------|
| | $w = 0$ | $w = 1$ | | | | | | | |
| | Y_2Y_1 | Y_2Y_1 | R1 _{out} | R1 _{in} | R2 _{out} | R2 _{in} | R3 _{out} | R3 _{in} | <i>Done</i> |
| A | | | | | | | | | |
| B | | | | | | | | | |
| C | | | | | | | | | |
| D | | | | | | | | | |

State Table (same as before)

| Present state | Next state | | Outputs | | | | | | |
|------------------|------------|---------|-------------------|------------------|-------------------|------------------|-------------------|------------------|-------------|
| | $w = 0$ | $w = 1$ | R1 _{out} | R1 _{in} | R2 _{out} | R2 _{in} | R3 _{out} | R3 _{in} | <i>Done</i> |
| A | A | B | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| B | C | C | 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| C | D | D | 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| D | A | A | 0 | 1 | 0 | 0 | 1 | 0 | 1 |

State-Assigned Table

| | Present state | Next state | | Outputs | | | | | | |
|---|------------------|------------|----------|-------------------|------------------|-------------------|------------------|-------------------|------------------|-------------|
| | | $w = 0$ | $w = 1$ | | | | | | | |
| | y_2y_1 | Y_2Y_1 | Y_2Y_1 | R1 _{out} | R1 _{in} | R2 _{out} | R2 _{in} | R3 _{out} | R3 _{in} | <i>Done</i> |
| A | 00 | | | | | | | | | |
| B | 01 | | | | | | | | | |
| C | 11 | | | | | | | | | |
| D | 10 | | | | | | | | | |

State Table (same as before)

| Present state | Next state | | Outputs | | | | | | |
|------------------|------------|---------|-------------------|------------------|-------------------|------------------|-------------------|------------------|-------------|
| | $w = 0$ | $w = 1$ | R1 _{out} | R1 _{in} | R2 _{out} | R2 _{in} | R3 _{out} | R3 _{in} | <i>Done</i> |
| A | A | B | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| B | C | C | 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| C | D | D | 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| D | A | A | 0 | 1 | 0 | 0 | 1 | 0 | 1 |

State-Assigned Table

| | Present state | Next state | | Outputs | | | | | | |
|---|------------------|------------|----------|-------------------|------------------|-------------------|------------------|-------------------|------------------|-------------|
| | | $w = 0$ | $w = 1$ | | | | | | | |
| | y_2y_1 | Y_2Y_1 | Y_2Y_1 | R1 _{out} | R1 _{in} | R2 _{out} | R2 _{in} | R3 _{out} | R3 _{in} | <i>Done</i> |
| A | 00 | 00 | 0 1 | | | | | | | |
| B | 01 | 11 | 1 1 | | | | | | | |
| C | 11 | 10 | 1 0 | | | | | | | |
| D | 10 | 00 | 0 0 | | | | | | | |

State Table (same as before)

| Present state | Next state | | Outputs | | | | | | |
|---------------|------------|---------|-------------------|------------------|-------------------|------------------|-------------------|------------------|-------------|
| | $w = 0$ | $w = 1$ | R1 _{out} | R1 _{in} | R2 _{out} | R2 _{in} | R3 _{out} | R3 _{in} | <i>Done</i> |
| A | A | B | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| B | C | C | 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| C | D | D | 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| D | A | A | 0 | 1 | 0 | 0 | 1 | 0 | 1 |

State-Assigned Table

| | Present state | Next state | | Outputs | | | | | | |
|---|---------------|------------|----------|-------------------|------------------|-------------------|------------------|-------------------|------------------|-------------|
| | | $w = 0$ | $w = 1$ | | | | | | | |
| | y_2y_1 | Y_2Y_1 | Y_2Y_1 | R1 _{out} | R1 _{in} | R2 _{out} | R2 _{in} | R3 _{out} | R3 _{in} | <i>Done</i> |
| A | 00 | 00 | 0 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| B | 01 | 11 | 1 1 | 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| C | 11 | 10 | 1 0 | 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| D | 10 | 00 | 0 0 | 0 | 1 | 0 | 0 | 1 | 0 | 1 |

| | Present state | Next state | | Outputs | | | | | | |
|---|---------------|------------|----------|------------|-----------|------------|-----------|------------|-----------|-------------|
| | | $w = 0$ | $w = 1$ | | | | | | | |
| | y_2y_1 | Y_2Y_1 | Y_2Y_1 | $R1_{out}$ | $R1_{in}$ | $R2_{out}$ | $R2_{in}$ | $R3_{out}$ | $R3_{in}$ | <i>Done</i> |
| A | 00 | 00 | 0 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| B | 01 | 11 | 1 1 | 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| C | 11 | 10 | 1 0 | 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| D | 10 | 00 | 0 0 | 0 | 1 | 0 | 0 | 1 | 0 | 1 |

| y_2 | y_1 | w | Y_2 | Y_1 |
|-------|-------|-----|-------|-------|
| 0 | 0 | 0 | | |
| 0 | 0 | 1 | | |
| 0 | 1 | 0 | | |
| 0 | 1 | 1 | | |
| 1 | 0 | 0 | | |
| 1 | 0 | 1 | | |
| 1 | 1 | 0 | | |
| 1 | 1 | 1 | | |



Let's derive the next-state expressions

| | Present state | Next state | | Outputs | | | | | | |
|---|---------------|------------|----------|------------|-----------|------------|-----------|------------|-----------|-------------|
| | | $w = 0$ | $w = 1$ | | | | | | | |
| | y_2y_1 | Y_2Y_1 | Y_2Y_1 | $R1_{out}$ | $R1_{in}$ | $R2_{out}$ | $R2_{in}$ | $R3_{out}$ | $R3_{in}$ | <i>Done</i> |
| A | 00 | 00 | 0 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| B | 01 | 11 | 1 1 | 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| C | 11 | 10 | 1 0 | 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| D | 10 | 00 | 0 0 | 0 | 1 | 0 | 0 | 1 | 0 | 1 |

| y_2 | y_1 | w | Y_2 | Y_1 |
|-------|-------|-----|-------|-------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 1 | 1 |
| 0 | 1 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 | 0 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 1 | 0 |

| | Present state | Next state | | Outputs | | | | | | |
|---|---------------|------------|----------|------------|-----------|------------|-----------|------------|-----------|-------------|
| | | $w = 0$ | $w = 1$ | | | | | | | |
| | y_2y_1 | Y_2Y_1 | Y_2Y_1 | $R1_{out}$ | $R1_{in}$ | $R2_{out}$ | $R2_{in}$ | $R3_{out}$ | $R3_{in}$ | <i>Done</i> |
| A | 00 | 00 | 0 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| B | 01 | 11 | 1 1 | 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| C | 11 | 10 | 1 0 | 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| D | 10 | 00 | 0 0 | 0 | 1 | 0 | 0 | 1 | 0 | 1 |

| y_2 | y_1 | w | Y_2 | Y_1 |
|-------|-------|-----|-------|-------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 1 | 1 |
| 0 | 1 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 | 0 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 1 | 0 |

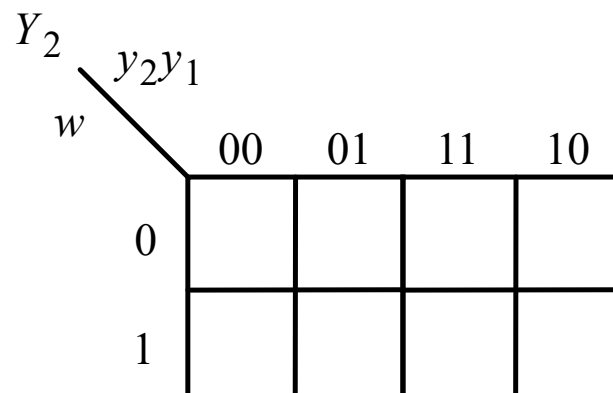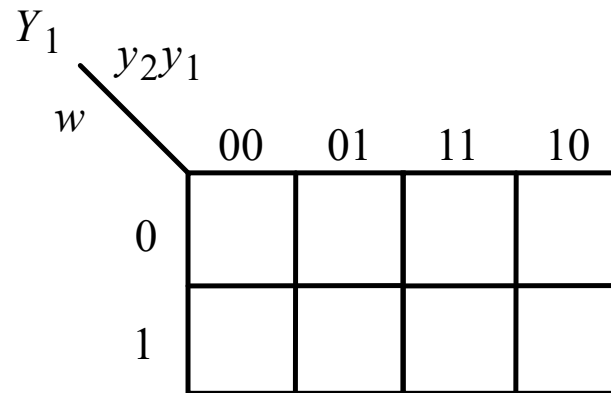

| | Present state | Next state | | Outputs | | | | | | |
|---|---------------|------------|----------|------------|-----------|------------|-----------|------------|-----------|-------------|
| | | $w = 0$ | $w = 1$ | | | | | | | |
| | y_2y_1 | Y_2Y_1 | Y_2Y_1 | $R1_{out}$ | $R1_{in}$ | $R2_{out}$ | $R2_{in}$ | $R3_{out}$ | $R3_{in}$ | <i>Done</i> |
| A | 00 | 00 | 0 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| B | 01 | 11 | 1 1 | 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| C | 11 | 10 | 1 0 | 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| D | 10 | 00 | 0 0 | 0 | 1 | 0 | 0 | 1 | 0 | 1 |

| y_2 | y_1 | w | Y_2 | Y_1 |
|-------|-------|-----|-------|-------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 1 | 1 |
| 0 | 1 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 | 0 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 1 | 0 |

Y_1



| | | | | | |
|-----|----------|----|----|----|----|
| | y_2y_1 | 00 | 01 | 11 | 10 |
| w | | | | | |
| 0 | | 0 | 1 | 0 | 0 |
| 1 | | 1 | 1 | 0 | 0 |

Y_2

| | | | | | |
|-----|----------|----|----|----|----|
| | y_2y_1 | 00 | 01 | 11 | 10 |
| w | | | | | |
| 0 | | 0 | 1 | 1 | 0 |
| 1 | | 0 | 1 | 1 | 0 |


| | Present state | Next state | | Outputs | | | | | | |
|---|---------------|------------|----------|------------|-----------|------------|-----------|------------|-----------|-------------|
| | | $w = 0$ | $w = 1$ | | | | | | | |
| | y_2y_1 | Y_2Y_1 | Y_2Y_1 | $R1_{out}$ | $R1_{in}$ | $R2_{out}$ | $R2_{in}$ | $R3_{out}$ | $R3_{in}$ | <i>Done</i> |
| A | 00 | 00 | 0 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| B | 01 | 11 | 1 1 | 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| C | 11 | 10 | 1 0 | 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| D | 10 | 00 | 0 0 | 0 | 1 | 0 | 0 | 1 | 0 | 1 |

| y_2 | y_1 | w | Y_2 | Y_1 |
|-------|-------|-----|-------|-------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 1 | 1 |
| 0 | 1 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 | 0 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 1 | 0 |

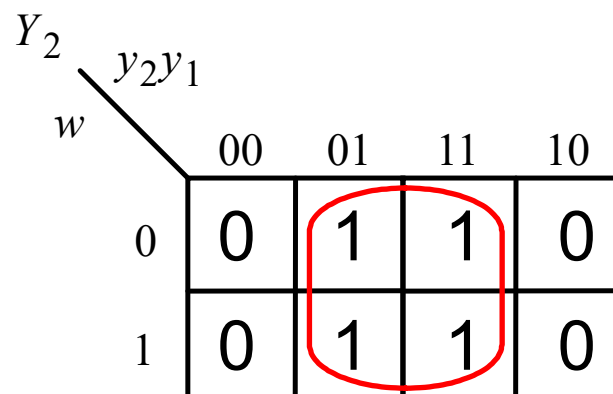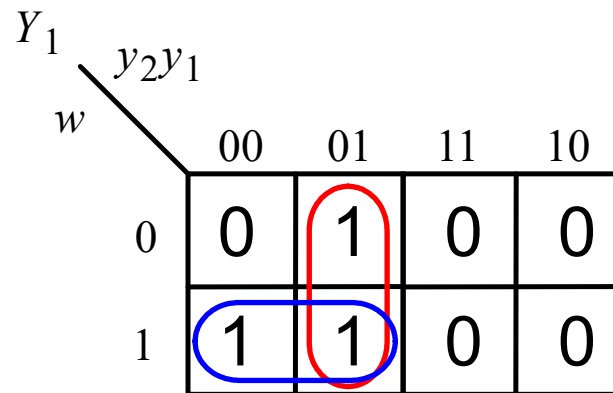


| | Present state | Next state | | Outputs | | | | | | |
|---|---------------|------------|----------|------------|-----------|------------|-----------|------------|-----------|-------------|
| | | $w = 0$ | $w = 1$ | | | | | | | |
| | y_2y_1 | Y_2Y_1 | Y_2Y_1 | $R1_{out}$ | $R1_{in}$ | $R2_{out}$ | $R2_{in}$ | $R3_{out}$ | $R3_{in}$ | <i>Done</i> |
| A | 00 | 00 | 0 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| B | 01 | 11 | 1 1 | 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| C | 11 | 10 | 1 0 | 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| D | 10 | 00 | 0 0 | 0 | 1 | 0 | 0 | 1 | 0 | 1 |

| y_2 | y_1 | w | Y_2 | Y_1 |
|-------|-------|-----|-------|-------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 1 | 1 |
| 0 | 1 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 | 0 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 1 | 0 |

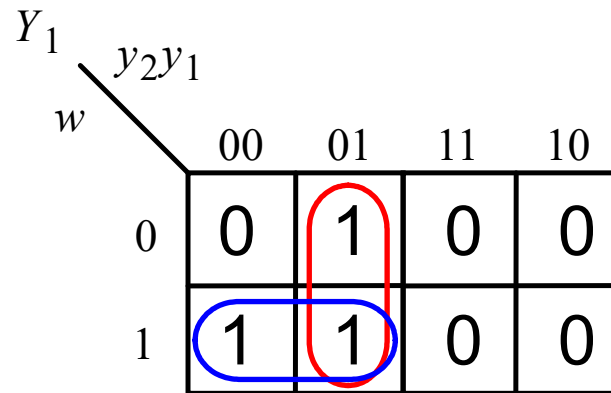

$$Y_1 = w\bar{y}_2 + y_1\bar{y}_2$$

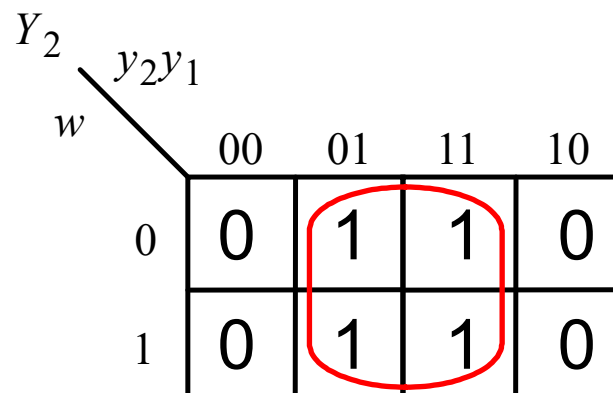

$$Y_2 = y_1$$

| | Present state | Next state | | Outputs | | | | | | |
|---|---------------|------------|----------|------------|-----------|------------|-----------|------------|-----------|-------------|
| | | $w = 0$ | $w = 1$ | $R1_{out}$ | $R1_{in}$ | $R2_{out}$ | $R2_{in}$ | $R3_{out}$ | $R3_{in}$ | <i>Done</i> |
| | y_2y_1 | Y_2Y_1 | Y_2Y_1 | | | | | | | |
| A | 00 | 00 | 0 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| B | 01 | 11 | 1 1 | 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| C | 11 | 10 | 1 0 | 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| D | 10 | 00 | 0 0 | 0 | 1 | 0 | 0 | 1 | 0 | 1 |

| y_2 | y_1 | $R1_{out}$ | $R1_{in}$ | $R2_{out}$ |
|-------|-------|------------|-----------|------------|
| 0 | 0 | | | |
| 0 | 1 | | | |
| 1 | 0 | | | |
| 1 | 1 | | | |

Let's derive the output expressions

| | Present state | Next state | | Outputs | | | | | | |
|---|---------------|------------|----------|------------|-----------|------------|-----------|------------|-----------|-------------|
| | | $w = 0$ | $w = 1$ | $R1_{out}$ | $R1_{in}$ | $R2_{out}$ | $R2_{in}$ | $R3_{out}$ | $R3_{in}$ | <i>Done</i> |
| | y_2y_1 | Y_2Y_1 | Y_2Y_1 | | | | | | | |
| A | 00 | 00 | 0 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| B | 01 | 11 | 1 1 | 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| C | 11 | 10 | 1 0 | 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| D | 10 | 00 | 0 0 | 0 | 1 | 0 | 0 | 1 | 0 | 1 |

| y_2 | y_1 | $R1_{out}$ | $R1_{in}$ | $R2_{out}$ |
|-------|-------|------------|-----------|------------|
| 0 | 0 | | | |
| 0 | 1 | | | |
| 1 | 0 | | | |
| 1 | 1 | | | |

Let's derive the output expressions

Once again, we only need to derive these three unique ones.

| | Present state | Next state | | Outputs | | | | | | |
|---|---------------|------------|----------|------------|-----------|------------|-----------|------------|-----------|-------------|
| | | $w = 0$ | $w = 1$ | $R1_{out}$ | $R1_{in}$ | $R2_{out}$ | $R2_{in}$ | $R3_{out}$ | $R3_{in}$ | <i>Done</i> |
| | y_2y_1 | Y_2Y_1 | Y_2Y_1 | | | | | | | |
| A | 00 | 00 | 0 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| B | 01 | 11 | 1 1 | 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| C | 11 | 10 | 1 0 | 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| D | 10 | 00 | 0 0 | 0 | 1 | 0 | 0 | 1 | 0 | 1 |

| | y_2 | y_1 | $R1_{out}$ | $R1_{in}$ | $R2_{out}$ |
|---|-------|-------|------------|-----------|------------|
| A | 0 | 0 | 0 | | |
| B | 0 | 1 | 0 | | |
| D | 1 | 0 | 0 | | |
| C | 1 | 1 | 1 | | |

Note that C and D are swapped in the truth table due to the new state encoding that was chosen.

| | Present state | Next state | | Outputs | | | | | | |
|---|---------------|------------|----------|------------|-----------|------------|-----------|------------|-----------|-------------|
| | | $w = 0$ | $w = 1$ | | | | | | | |
| | y_2y_1 | Y_2Y_1 | Y_2Y_1 | $R1_{out}$ | $R1_{in}$ | $R2_{out}$ | $R2_{in}$ | $R3_{out}$ | $R3_{in}$ | <i>Done</i> |
| A | 00 | 00 | 0 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| B | 01 | 11 | 1 1 | 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| C | 11 | 10 | 1 0 | 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| D | 10 | 00 | 0 0 | 0 | 1 | 0 | 0 | 1 | 0 | 1 |

| | y_2 | y_1 | $R1_{out}$ | $R1_{in}$ | $R2_{out}$ |
|---|-------|-------|------------|-----------|------------|
| A | 0 | 0 | 0 | 0 | 0 |
| B | 0 | 1 | 0 | 0 | 1 |
| D | 1 | 0 | 0 | 1 | 0 |
| C | 1 | 1 | 1 | 0 | 0 |

| | Present state | Next state | | Outputs | | | | | | |
|---|---------------|------------|-----------|------------|-----------|------------|-----------|------------|-----------|-------------|
| | | $w = 0$ | $w = 1$ | $R1_{out}$ | $R1_{in}$ | $R2_{out}$ | $R2_{in}$ | $R3_{out}$ | $R3_{in}$ | <i>Done</i> |
| | $y_2 y_1$ | $Y_2 Y_1$ | $Y_2 Y_1$ | | | | | | | |
| A | 00 | 00 | 0 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| B | 01 | 11 | 1 1 | 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| C | 11 | 10 | 1 0 | 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| D | 10 | 00 | 0 0 | 0 | 1 | 0 | 0 | 1 | 0 | 1 |


| | y_2 | y_1 | $R1_{out}$ | $R1_{in}$ | $R2_{out}$ |
|---|-------|-------|------------|-----------|------------|
| A | 0 | 0 | 0 | 0 | 0 |
| B | 0 | 1 | 0 | 0 | 1 |
| D | 1 | 0 | 0 | 1 | 0 |
| C | 1 | 1 | 1 | 0 | 0 |

$$R1_{out} = R2_{in} = y_1 y_2$$

$$R1_{in} = R3_{out} = Done = \overline{y_1} y_2$$

$$R2_{out} = R3_{in} = y_1 \overline{y_2}$$

Let's Complete the Circuit Diagram

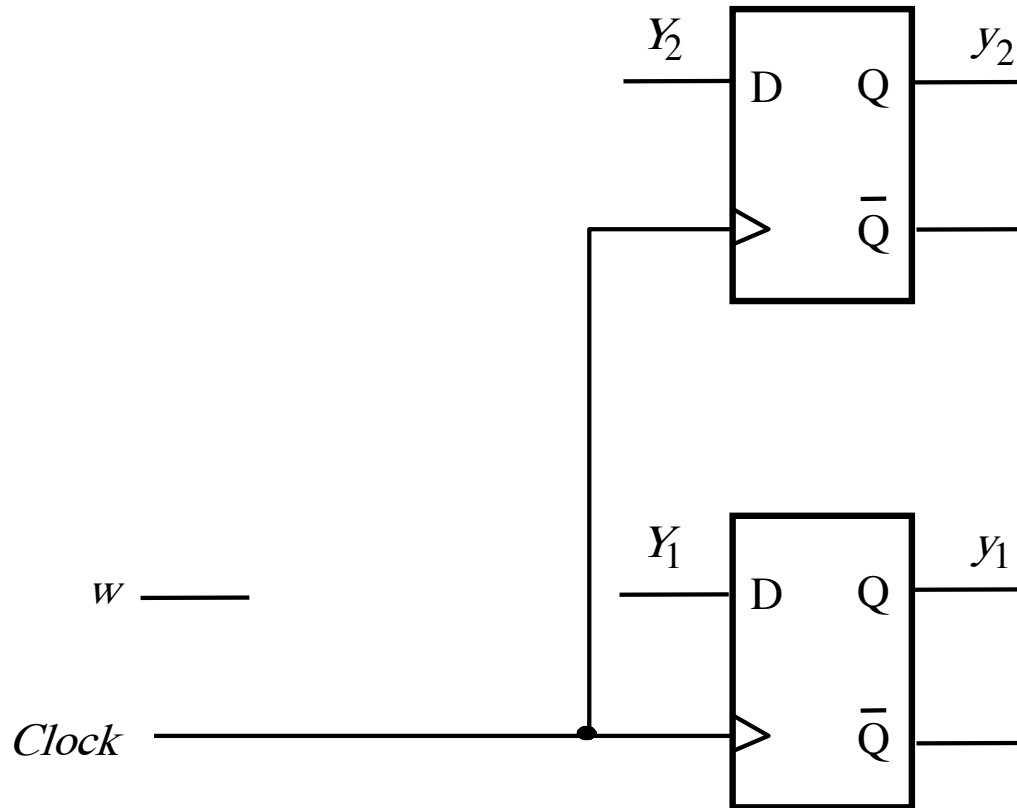

$$Y_1 = w \overline{y_2} + y_1 \overline{y_2}$$


$$Y_2 = y_1$$

$$R1_{out} = R2_{in} = y_1 y_2$$

$$R1_{in} = R3_{out} = \text{Done} = \overline{y_1} y_2$$

$$R2_{out} = R3_{in} = y_1 \overline{y_2}$$

Let's Complete the Circuit Diagram

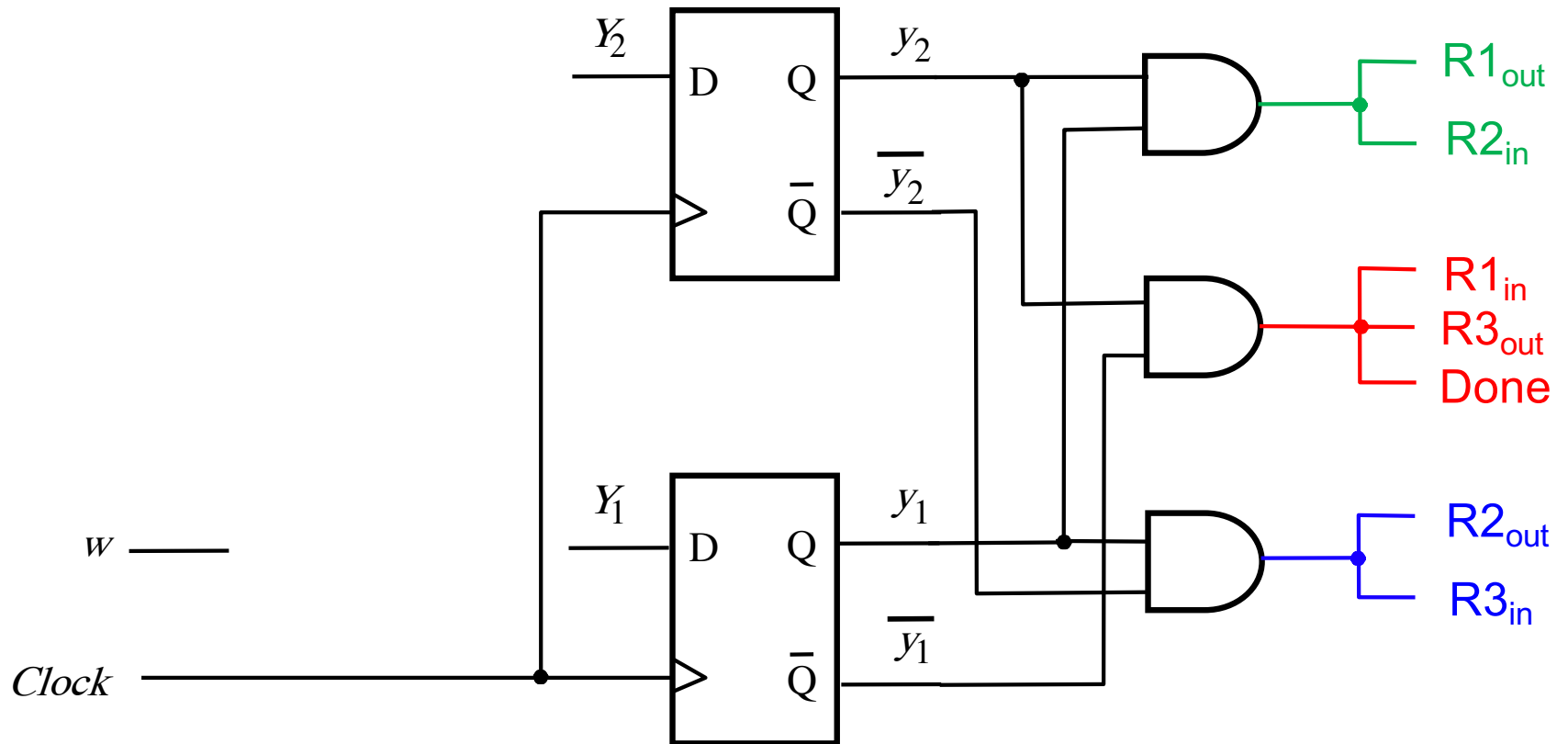

$$Y_1 = w \overline{y_2} + y_1 \overline{y_2}$$


$$Y_2 = y_1$$

$$R1_{out} = R2_{in} = y_1 y_2$$

$$R1_{in} = R3_{out} = Done = \overline{y_1} y_2$$

$$R2_{out} = R3_{in} = y_1 \overline{y_2}$$

Let's Complete the Circuit Diagram

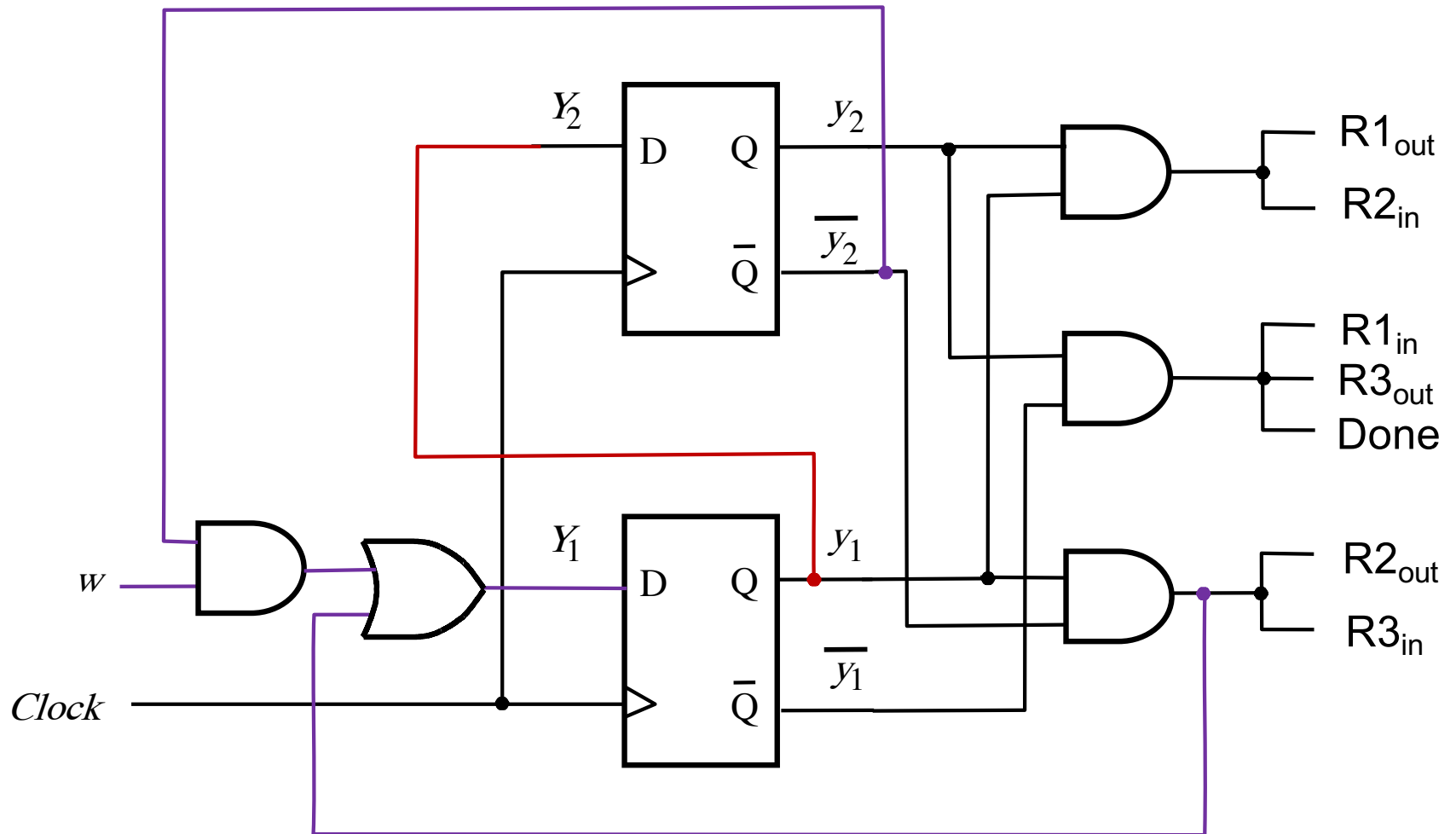

$$Y_1 = w \overline{y_2} + y_1 \overline{y_2}$$


$$Y_2 = y_1$$

$$R1_{out} = R2_{in} = y_1 y_2$$

$$R1_{in} = R3_{out} = \text{Done} = \overline{y_1} y_2$$

$$R2_{out} = R3_{in} = y_1 \overline{y_2}$$

Let's Complete the Circuit Diagram

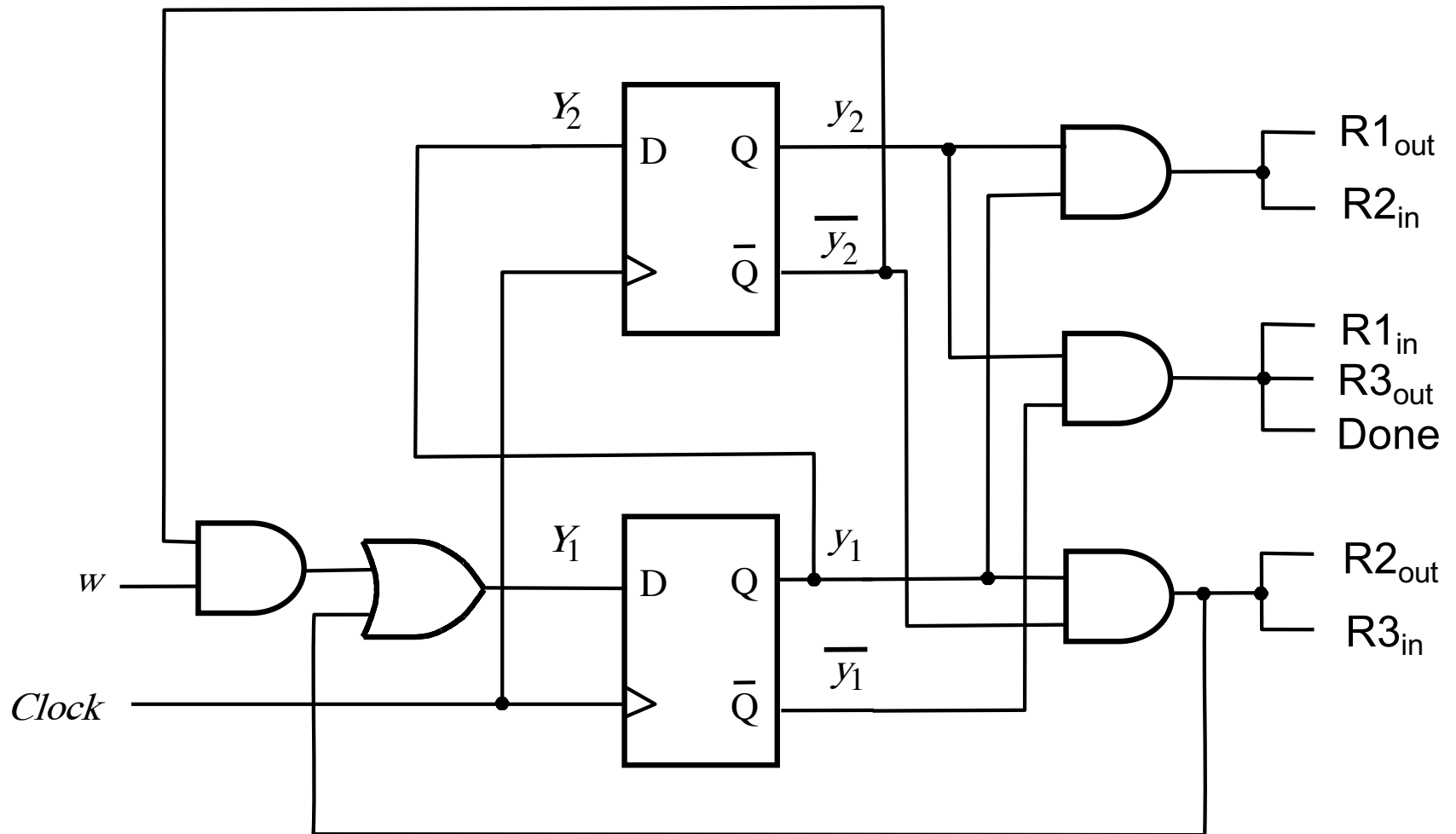

$$Y_1 = w \overline{y_2} + y_1 \overline{y_2}$$

$$Y_2 = y_1$$

$$R1_{out} = R2_{in} = y_1 y_2$$

$$R1_{in} = R3_{out} = Done = \overline{y_1} y_2$$

$$R2_{out} = R3_{in} = y_1 \overline{y_2}$$

Encoding #3:


A=0001, B=0010, C=0100, D=1000

(One-Hot Encoding – Uses Four Flip-Flops)


One-Hot State Encoding

- **So far, we have been encoding states in a way that minimizes the number of flip-flops.**
- **But sometimes we can decrease the complexity of our logic if we encode states more sparsely.**


Encoding for State A

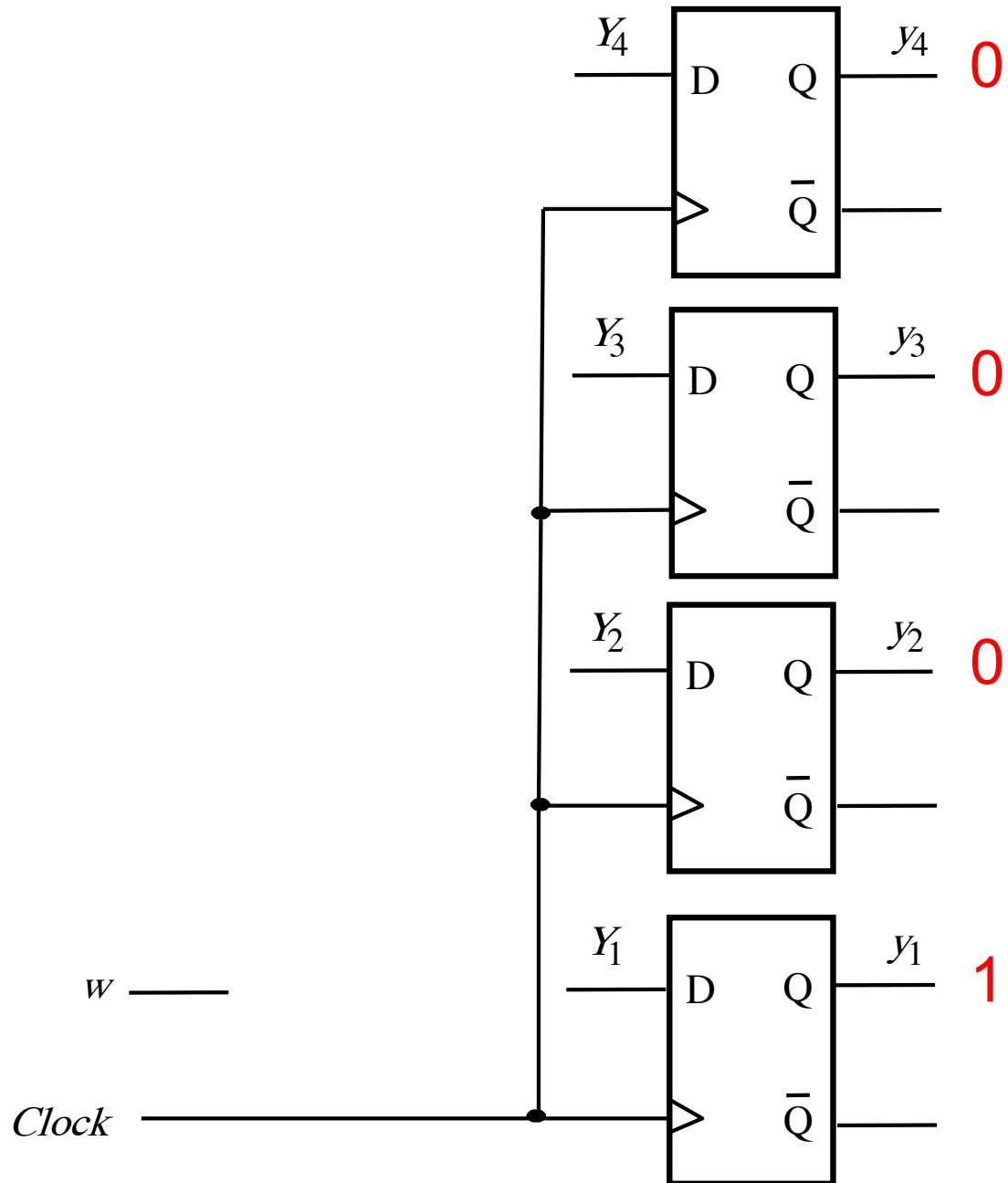


Encoding for State B

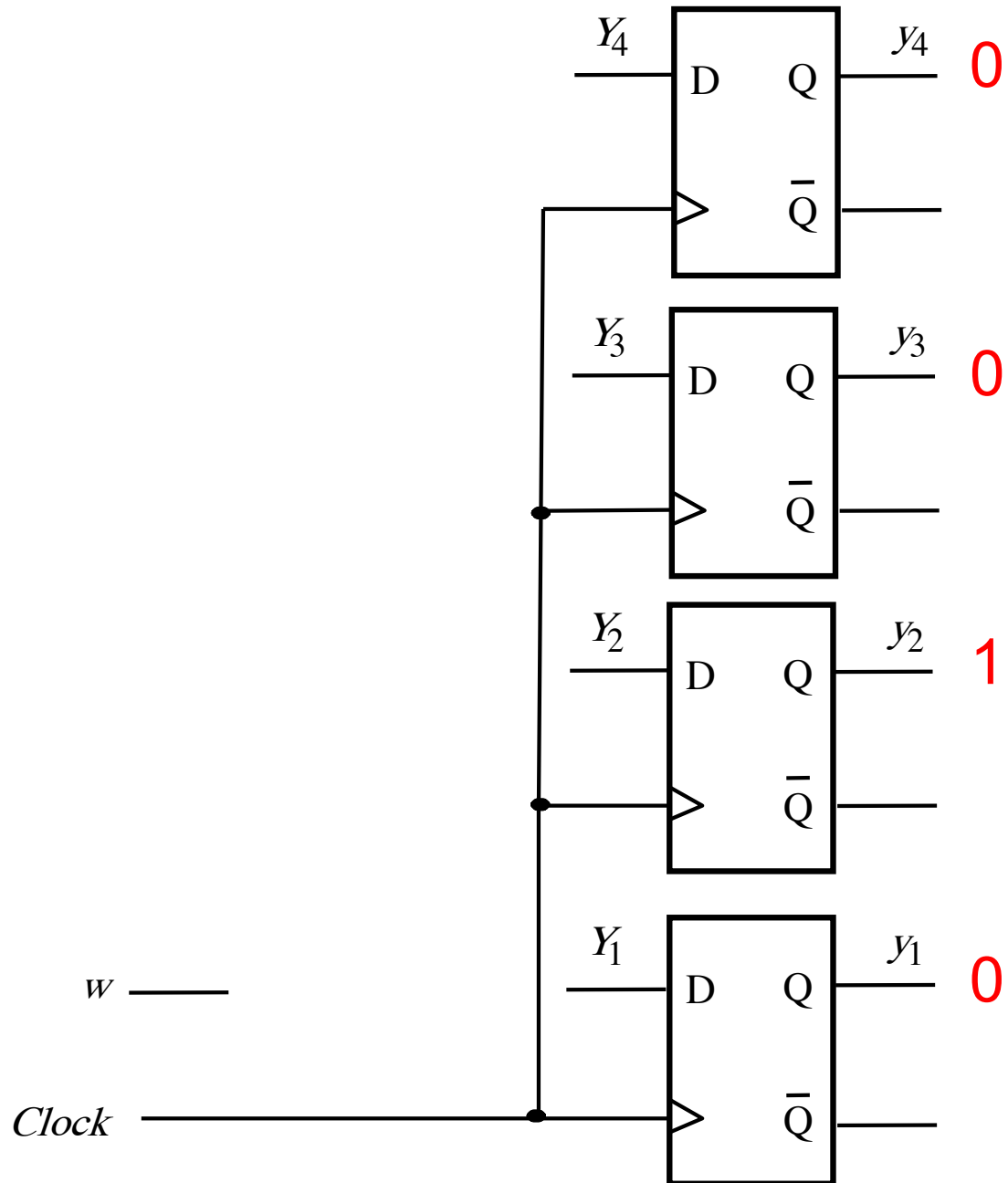

Encoding for State C

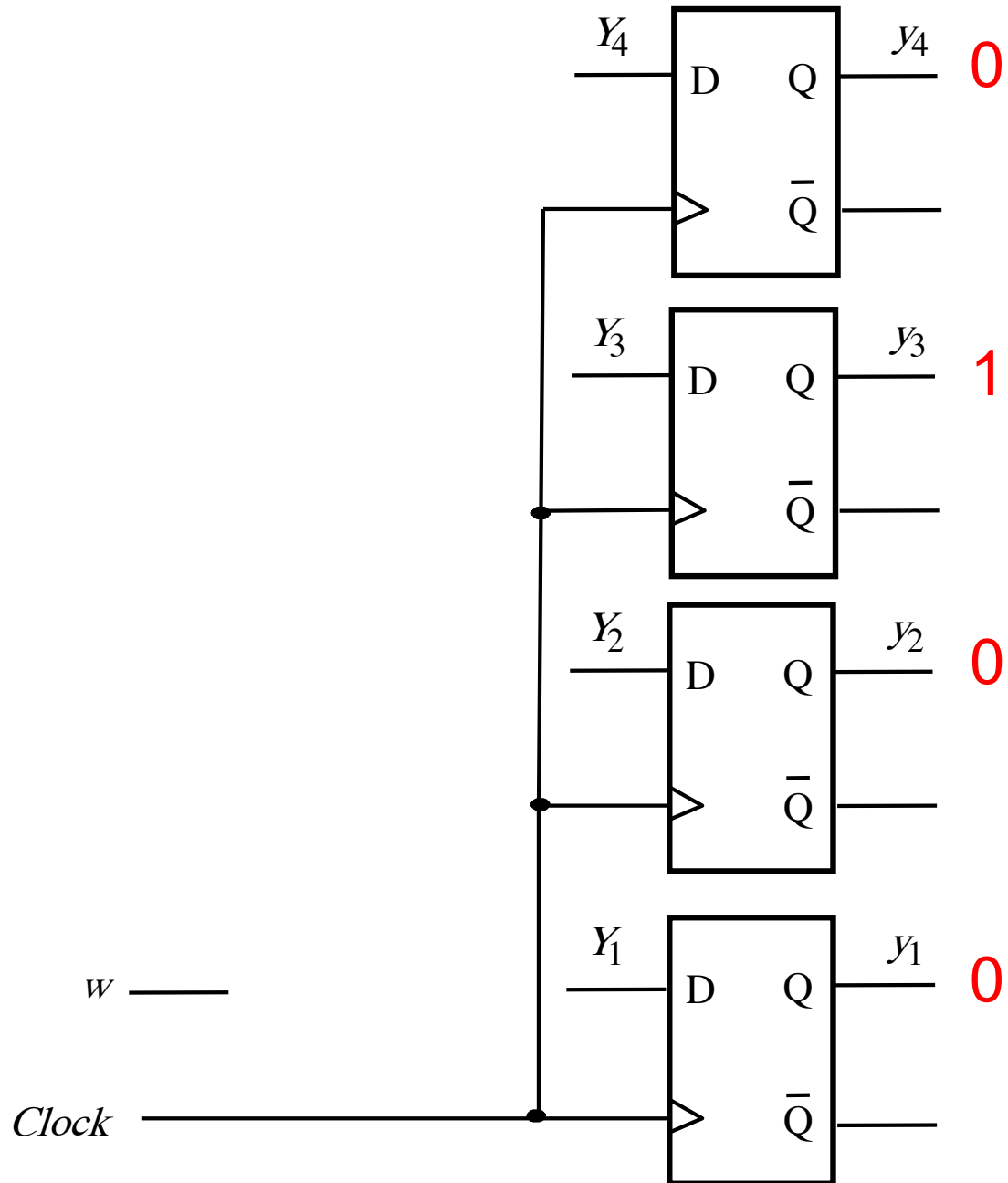

Encoding for State D

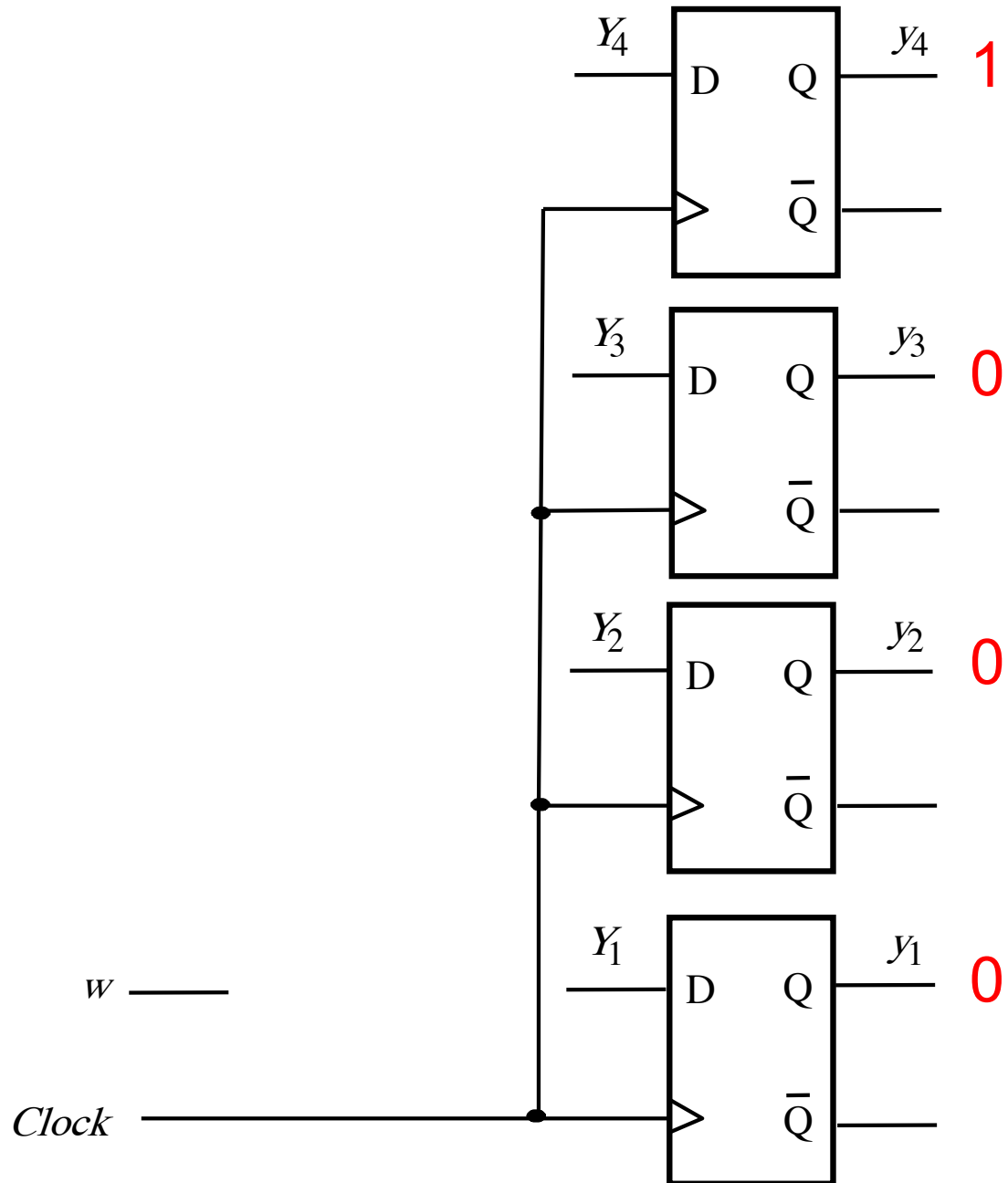

Register Swap Controller

| Present state | Next state | | Outputs | | | | | | |
|---------------|------------|---------|-------------------|------------------|-------------------|------------------|-------------------|------------------|-------------|
| | $w = 0$ | $w = 1$ | R1 _{out} | R1 _{in} | R2 _{out} | R2 _{in} | R3 _{out} | R3 _{in} | <i>Done</i> |
| A | A | B | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| B | C | C | 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| C | D | D | 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| D | A | A | 0 | 1 | 0 | 0 | 1 | 0 | 1 |

Register Swap Controller

| Present state | Next state | | Outputs | | | | | | |
|---------------|------------|---------|-------------------|------------------|-------------------|------------------|-------------------|------------------|-------------|
| | $w = 0$ | $w = 1$ | R1 _{out} | R1 _{in} | R2 _{out} | R2 _{in} | R3 _{out} | R3 _{in} | <i>Done</i> |
| A | A | B | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| B | C | C | 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| C | D | D | 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| D | A | A | 0 | 1 | 0 | 0 | 1 | 0 | 1 |

Let's use four flip-flops and the following one-hot state encoding scheme:

A = 0001

B = 0010

C = 0100

D = 1000

State Table (same as before)

| Present state | Next state | | Outputs | | | | | | |
|---------------|------------|---------|-------------------|------------------|-------------------|------------------|-------------------|------------------|-------------|
| | $w = 0$ | $w = 1$ | R1 _{out} | R1 _{in} | R2 _{out} | R2 _{in} | R3 _{out} | R3 _{in} | <i>Done</i> |
| A | A | B | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| B | C | C | 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| C | D | D | 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| D | A | A | 0 | 1 | 0 | 0 | 1 | 0 | 1 |

State-Assigned Table

| | Present State | Next State | | Outputs | | | | | | |
|---|----------------|----------------|----------------|-------------------|------------------|-------------------|------------------|-------------------|------------------|-------------|
| | | $w = 0$ | $w = 1$ | | | | | | | |
| | $y_4y_3y_2y_1$ | $Y_4Y_3Y_2Y_1$ | $Y_4Y_3Y_2Y_1$ | R1 _{out} | R1 _{in} | R2 _{out} | R2 _{in} | R3 _{out} | R3 _{in} | <i>Done</i> |
| A | | | | | | | | | | |
| B | | | | | | | | | | |
| C | | | | | | | | | | |
| D | | | | | | | | | | |

State Table (same as before)

| Present state | Next state | | Outputs | | | | | | |
|---------------|------------|---------|-------------------|------------------|-------------------|------------------|-------------------|------------------|-------------|
| | $w = 0$ | $w = 1$ | R1 _{out} | R1 _{in} | R2 _{out} | R2 _{in} | R3 _{out} | R3 _{in} | <i>Done</i> |
| A | A | B | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| B | C | C | 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| C | D | D | 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| D | A | A | 0 | 1 | 0 | 0 | 1 | 0 | 1 |

State-Assigned Table

| | Present State | Next State | | Outputs | | | | | | |
|---|----------------|----------------|----------------|-------------------|------------------|-------------------|------------------|-------------------|------------------|-------------|
| | | $w = 0$ | $w = 1$ | | | | | | | |
| | $y_4y_3y_2y_1$ | $Y_4Y_3Y_2Y_1$ | $Y_4Y_3Y_2Y_1$ | R1 _{out} | R1 _{in} | R2 _{out} | R2 _{in} | R3 _{out} | R3 _{in} | <i>Done</i> |
| A | 0 001 | | | | | | | | | |
| B | 0 010 | | | | | | | | | |
| C | 0 100 | | | | | | | | | |
| D | 1 000 | | | | | | | | | |

State Table (same as before)

| Present state | Next state | | Outputs | | | | | | |
|---------------|------------|---------|-------------------|------------------|-------------------|------------------|-------------------|------------------|-------------|
| | $w = 0$ | $w = 1$ | R1 _{out} | R1 _{in} | R2 _{out} | R2 _{in} | R3 _{out} | R3 _{in} | <i>Done</i> |
| A | A | B | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| B | C | C | 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| C | D | D | 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| D | A | A | 0 | 1 | 0 | 0 | 1 | 0 | 1 |

State-Assigned Table

| | Present State | Next State | | Outputs | | | | | | |
|---|----------------|----------------|----------------|-------------------|------------------|-------------------|------------------|-------------------|------------------|-------------|
| | | $w = 0$ | $w = 1$ | | | | | | | |
| | $y_4y_3y_2y_1$ | $Y_4Y_3Y_2Y_1$ | $Y_4Y_3Y_2Y_1$ | R1 _{out} | R1 _{in} | R2 _{out} | R2 _{in} | R3 _{out} | R3 _{in} | <i>Done</i> |
| A | 0 001 | 0001 | 0010 | | | | | | | |
| B | 0 010 | 0100 | 0100 | | | | | | | |
| C | 0 100 | 1000 | 1000 | | | | | | | |
| D | 1 000 | 0001 | 0001 | | | | | | | |

State Table (same as before)

| Present state | Next state | | Outputs | | | | | | |
|---------------|------------|---------|-------------------|------------------|-------------------|------------------|-------------------|------------------|-------------|
| | $w = 0$ | $w = 1$ | R1 _{out} | R1 _{in} | R2 _{out} | R2 _{in} | R3 _{out} | R3 _{in} | <i>Done</i> |
| A | A | B | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| B | C | C | 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| C | D | D | 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| D | A | A | 0 | 1 | 0 | 0 | 1 | 0 | 1 |

State-Assigned Table

| | Present State | Next State | | Outputs | | | | | | |
|---|----------------|----------------|----------------|-------------------|------------------|-------------------|------------------|-------------------|------------------|-------------|
| | | $w = 0$ | $w = 1$ | | | | | | | |
| | $y_4y_3y_2y_1$ | $Y_4Y_3Y_2Y_1$ | $Y_4Y_3Y_2Y_1$ | R1 _{out} | R1 _{in} | R2 _{out} | R2 _{in} | R3 _{out} | R3 _{in} | <i>Done</i> |
| A | 0 001 | 0001 | 0010 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| B | 0 010 | 0100 | 0100 | 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| C | 0 100 | 1000 | 1000 | 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| D | 1 000 | 0001 | 0001 | 0 | 1 | 0 | 0 | 1 | 0 | 1 |

Let's Derive the Next-State Expressions

| | Present State | Next State | | Outputs | | | | | | |
|---|----------------|----------------|----------------|-------------------|------------------|-------------------|------------------|-------------------|------------------|-------------|
| | | $w = 0$ | $w = 1$ | | | | | | | |
| | $y_4y_3y_2y_1$ | $Y_4Y_3Y_2Y_1$ | $Y_4Y_3Y_2Y_1$ | R1 _{out} | R1 _{in} | R2 _{out} | R2 _{in} | R3 _{out} | R3 _{in} | <i>Done</i> |
| A | 0 001 | 0001 | 0010 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| B | 0 010 | 0100 | 0100 | 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| C | 0 100 | 1000 | 1000 | 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| D | 1 000 | 0001 | 0001 | 0 | 1 | 0 | 0 | 1 | 0 | 1 |

Let's Derive the Next-State Expressions

- $Y_1(w, y_4, y_3, y_2, y_1)$

- $Y_2(w, y_4, y_3, y_2, y_1)$

- $Y_3(w, y_4, y_3, y_2, y_1)$

- $Y_4(w, y_4, y_3, y_2, y_1)$

We need to do four 5-variable K-maps!

| | Present State | Next State | | Outputs | | | | | | |
|---|-------------------|-------------------|-------------------|-------------------|------------------|-------------------|------------------|-------------------|------------------|------|
| | | $w = 0$ | $w = 1$ | | | | | | | |
| | $y_4 y_3 y_2 y_1$ | $Y_4 Y_3 Y_2 Y_1$ | $Y_4 Y_3 Y_2 Y_1$ | R1 _{out} | R1 _{in} | R2 _{out} | R2 _{in} | R3 _{out} | R3 _{in} | Done |
| A | 0 001 | 0001 | 0010 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| B | 0 010 | 0100 | 0100 | 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| C | 0 100 | 1000 | 1000 | 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| D | 1 000 | 0001 | 0001 | 0 | 1 | 0 | 0 | 1 | 0 | 1 |

Let's Derive the Next-State Expressions

- $Y_1(w, y_4, y_3, y_2, y_1) = \neg w y_1 + y_4$

- $Y_2(w, y_4, y_3, y_2, y_1) = w y_1$

- $Y_3(w, y_4, y_3, y_2, y_1) = y_2$

- $Y_4(w, y_4, y_3, y_2, y_1) = y_3$

Or we can be smarter than that 😊

| | Present State | Next State | | Outputs | | | | | | |
|---|-------------------|-------------------|-------------------|-------------------|------------------|-------------------|------------------|-------------------|------------------|------|
| | | $w = 0$ | $w = 1$ | | | | | | | |
| | $y_4 y_3 y_2 y_1$ | $Y_4 Y_3 Y_2 Y_1$ | $Y_4 Y_3 Y_2 Y_1$ | R1 _{out} | R1 _{in} | R2 _{out} | R2 _{in} | R3 _{out} | R3 _{in} | Done |
| A | 0 001 | 0001 | 0010 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| B | 0 010 | 0100 | 0100 | 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| C | 0 100 | 1000 | 1000 | 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| D | 1 000 | 0001 | 0001 | 0 | 1 | 0 | 0 | 1 | 0 | 1 |

Let's Derive the Next-State Expressions

• $Y_1(w, y_4, y_3, y_2, y_1) = \neg w y_1 + y_4$ (why?)

• $Y_2(w, y_4, y_3, y_2, y_1) = w y_1$ (why?)

• $Y_3(w, y_4, y_3, y_2, y_1) = y_2$ =1 only in B

• $Y_4(w, y_4, y_3, y_2, y_1) = y_3$ =1 only in C

Or we can be smarter than that 😊

| | Present State | Next State | | Outputs | | | | | | |
|---|-------------------|-------------------|-------------------|-------------------|------------------|-------------------|------------------|-------------------|------------------|------|
| | | $w = 0$ | $w = 1$ | | | | | | | |
| | $y_4 y_3 y_2 y_1$ | $Y_4 Y_3 Y_2 Y_1$ | $Y_4 Y_3 Y_2 Y_1$ | R1 _{out} | R1 _{in} | R2 _{out} | R2 _{in} | R3 _{out} | R3 _{in} | Done |
| A | 0 001 | 0001 | 0010 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| B | 0 010 | 0100 | 0100 | 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| C | 0 100 | 1000 | 1000 | 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| D | 1 000 | 0001 | 0001 | 0 | 1 | 0 | 0 | 1 | 0 | 1 |

Let's Derive the Output Expressions

| | Present State | Next State | | Outputs | | | | | | |
|---|----------------|----------------|----------------|-------------------|------------------|-------------------|------------------|-------------------|------------------|-------------|
| | | $w = 0$ | $w = 1$ | | | | | | | |
| | $y_4y_3y_2y_1$ | $Y_4Y_3Y_2Y_1$ | $Y_4Y_3Y_2Y_1$ | R1 _{out} | R1 _{in} | R2 _{out} | R2 _{in} | R3 _{out} | R3 _{in} | <i>Done</i> |
| A | 0 001 | 0001 | 0010 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| B | 0 010 | 0100 | 0100 | 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| C | 0 100 | 1000 | 1000 | 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| D | 1 000 | 0001 | 0001 | 0 | 1 | 0 | 0 | 1 | 0 | 1 |

Let's Derive the Output Expressions

- $R1_{out}(y_4, y_3, y_2, y_1)$
- $R1_{in}(y_4, y_3, y_2, y_1)$
- $R2_{out}(y_4, y_3, y_2, y_1)$
- $R2_{in}(y_4, y_3, y_2, y_1)$
- $R3_{out}(y_4, y_3, y_2, y_1)$
- $R3_{in}(y_4, y_3, y_2, y_1)$
- $Done(y_4, y_3, y_2, y_1)$

We need to do seven 4-variable K-maps!

| | Present State | Next State | | Outputs | | | | | | |
|---|----------------|----------------|----------------|------------|-----------|------------|-----------|------------|-----------|-------------|
| | | $w = 0$ | $w = 1$ | | | | | | | |
| | $y_4y_3y_2y_1$ | $Y_4Y_3Y_2Y_1$ | $Y_4Y_3Y_2Y_1$ | $R1_{out}$ | $R1_{in}$ | $R2_{out}$ | $R2_{in}$ | $R3_{out}$ | $R3_{in}$ | <i>Done</i> |
| A | 0 001 | 0001 | 0010 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| B | 0 010 | 0100 | 0100 | 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| C | 0 100 | 1000 | 1000 | 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| D | 1 000 | 0001 | 0001 | 0 | 1 | 0 | 0 | 1 | 0 | 1 |

Let's Derive the Output Expressions

- $R1_{out}(y_4, y_3, y_2, y_1) = y_3$ *equal to 1 only in State C*
- $R1_{in}(y_4, y_3, y_2, y_1) = y_4$ *equal to 1 only in State D*
- $R2_{out}(y_4, y_3, y_2, y_1) = y_2$ *equal to 1 only in State B*
- $R2_{in}(y_4, y_3, y_2, y_1) = y_3$ *equal to 1 only in State C*
- $R3_{out}(y_4, y_3, y_2, y_1) = y_4$ *equal to 1 only in State D*
- $R3_{in}(y_4, y_3, y_2, y_1) = y_2$ *equal to 1 only in State B*
- $Done(y_4, y_3, y_2, y_1) = y_4$ *equal to 1 only in State D*

Or we can be smarter than that by exploiting the one-hot encoded property

| | Present State | Next State | | Outputs | | | | | | |
|---|----------------|----------------|----------------|------------|-----------|------------|-----------|------------|-----------|-------------|
| | | $w = 0$ | $w = 1$ | | | | | | | |
| | $y_4y_3y_2y_1$ | $Y_4Y_3Y_2Y_1$ | $Y_4Y_3Y_2Y_1$ | $R1_{out}$ | $R1_{in}$ | $R2_{out}$ | $R2_{in}$ | $R3_{out}$ | $R3_{in}$ | <i>Done</i> |
| A | 0 001 | 0001 | 0010 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| B | 0 010 | 0100 | 0100 | 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| C | 0 100 | 1000 | 1000 | 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| D | 1 000 | 0001 | 0001 | 0 | 1 | 0 | 0 | 1 | 0 | 1 |

Let's Complete the Circuit Diagram

$$R1_{out} = R2_{in} = y_3$$

$$R1_{in} = R3_{out} = Done = y_4$$


$$R2_{out} = R3_{in} = y_2$$

$$Y_1 = \bar{w} y_1 + y_4$$

$$Y_2 = w y_1$$

$$Y_3 = y_2$$

$$Y_4 = y_3$$

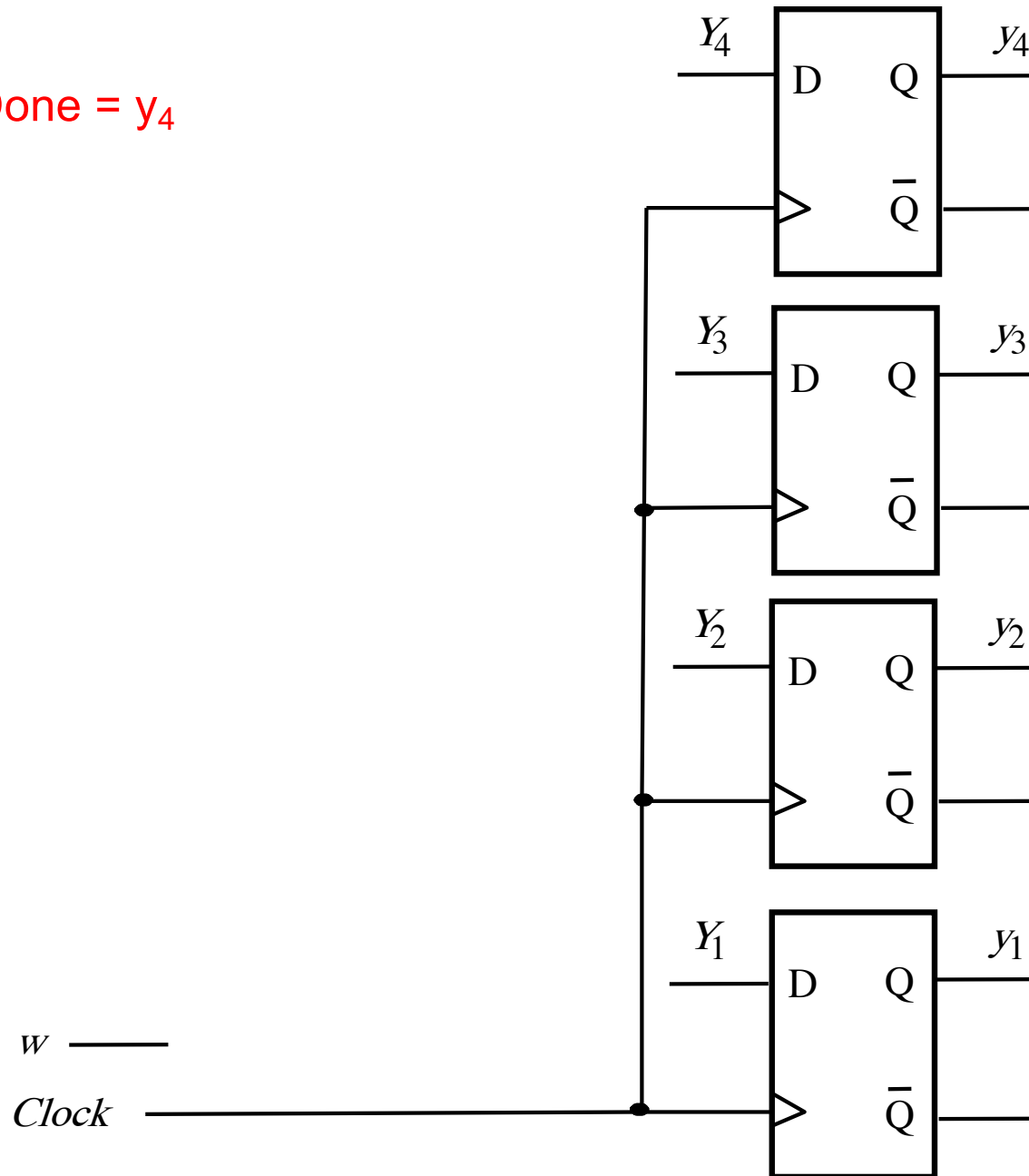

Let's Complete the Circuit Diagram

$$R1_{out} = R2_{in} = y_3$$

$$R1_{in} = R3_{out} = Done = y_4$$


$$R2_{out} = R3_{in} = y_2$$

$$Y_1 = \bar{w} y_1 + y_4$$

$$Y_2 = w y_1$$

$$Y_3 = y_2$$

$$Y_4 = y_3$$

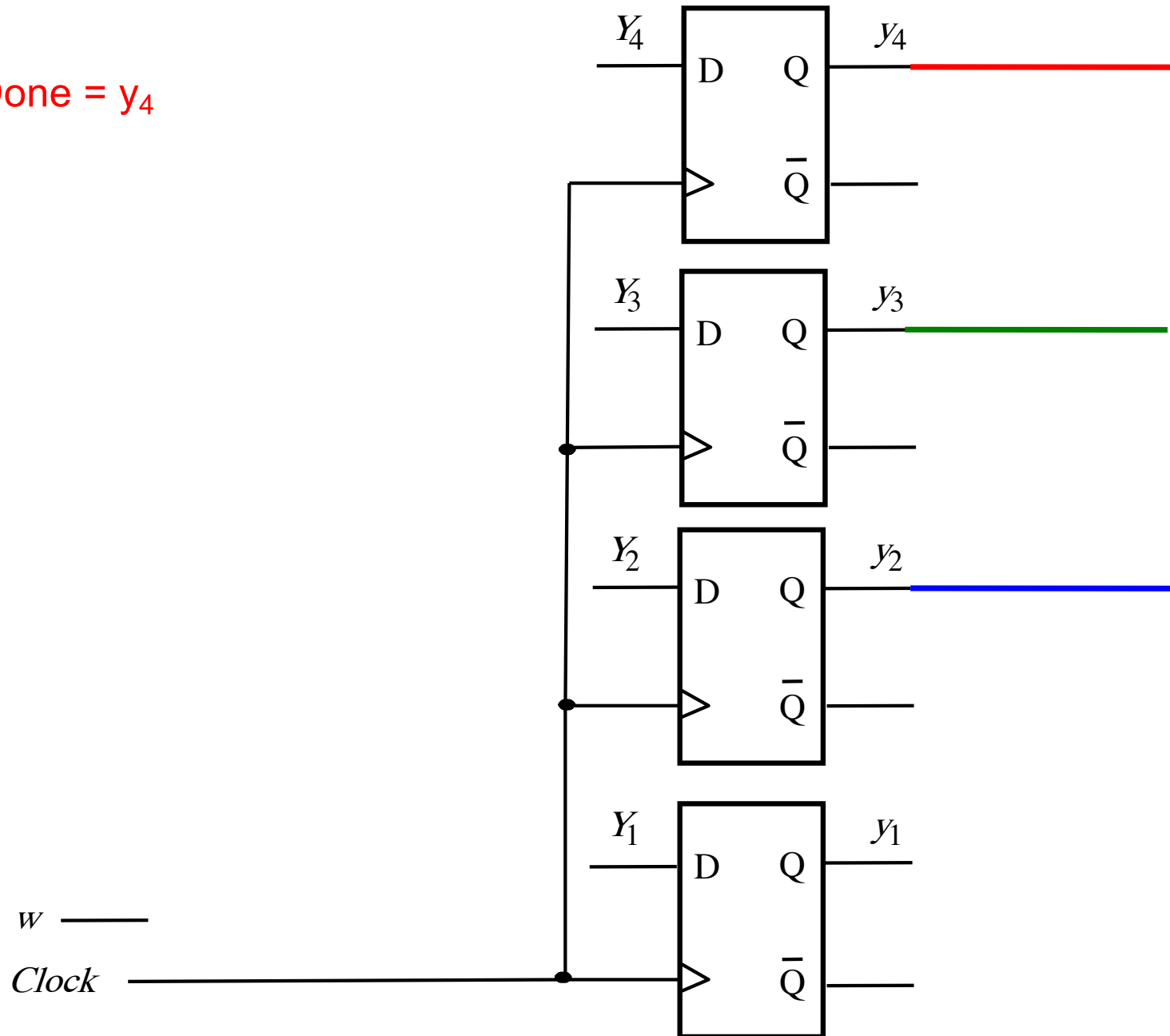

Let's Complete the Circuit Diagram

$$R1_{out} = R2_{in} = y_3$$

$$R1_{in} = R3_{out} = Done = y_4$$


$$R2_{out} = R3_{in} = y_2$$

$$Y_1 = \bar{w} y_1 + y_4$$

$$Y_2 = w y_1$$

$$Y_3 = y_2$$

$$Y_4 = y_3$$

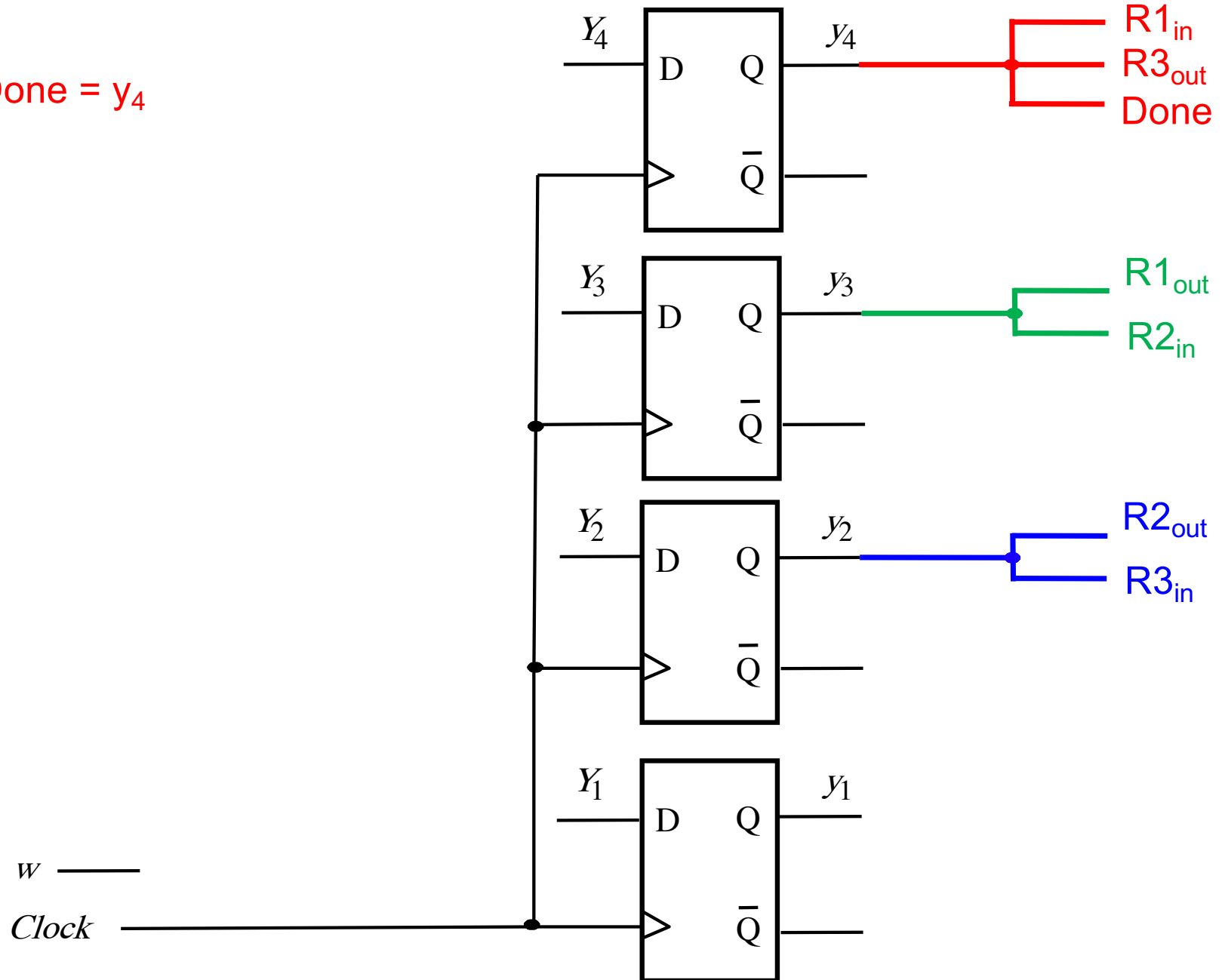


Let's Complete the Circuit Diagram

$$R1_{out} = R2_{in} = y_3$$

$$R1_{in} = R3_{out} = Done = y_4$$

$$R2_{out} = R3_{in} = y_2$$

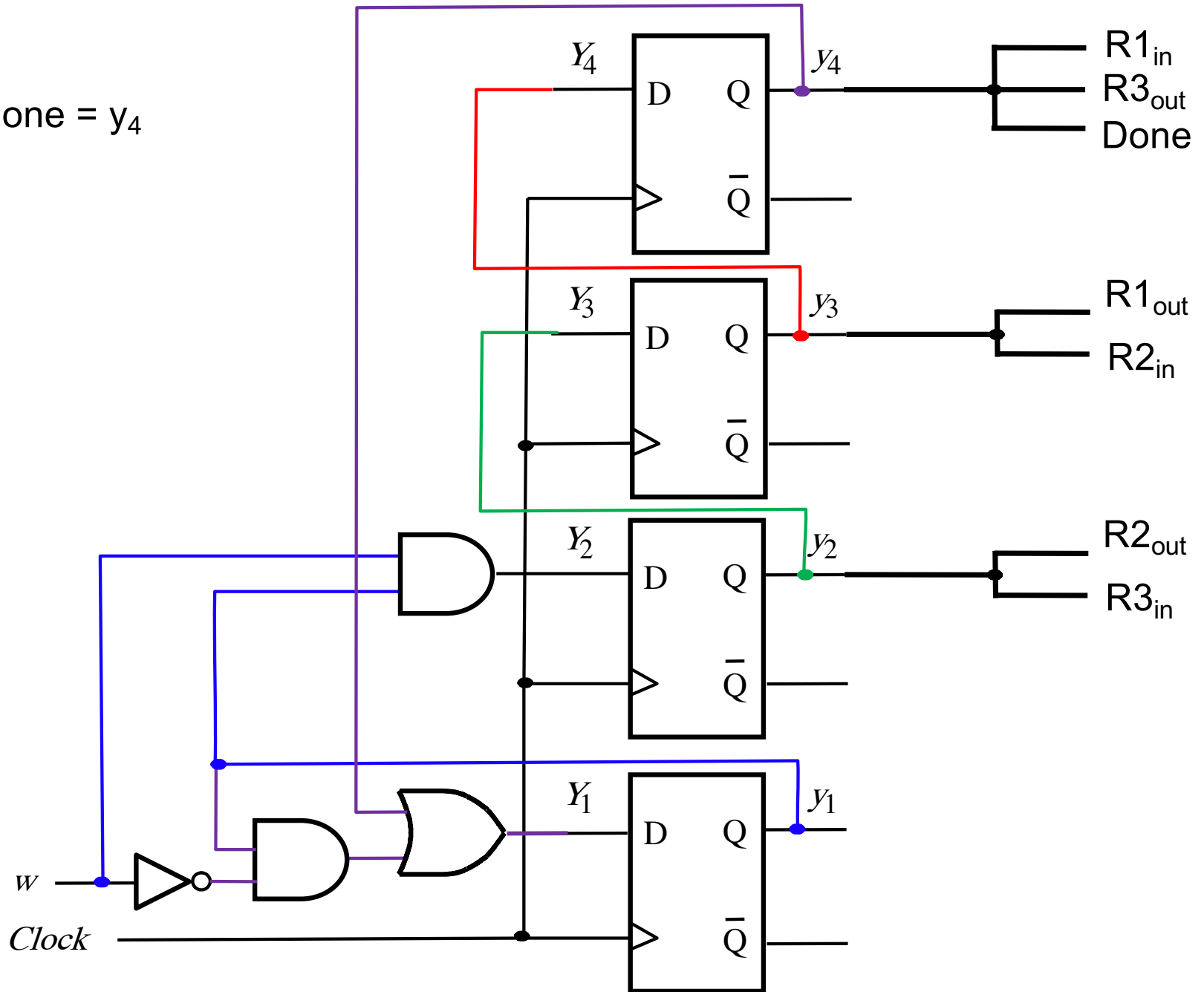

$$Y_1 = \bar{w} y_1 + y_4$$

$$Y_2 = w y_1$$

$$Y_3 = y_2$$


$$Y_4 = y_3$$

Let's Complete the Circuit Diagram

$$R1_{out} = R2_{in} = y_3$$

$$R1_{in} = R3_{out} = Done = y_4$$

$$R2_{out} = R3_{in} = y_2$$

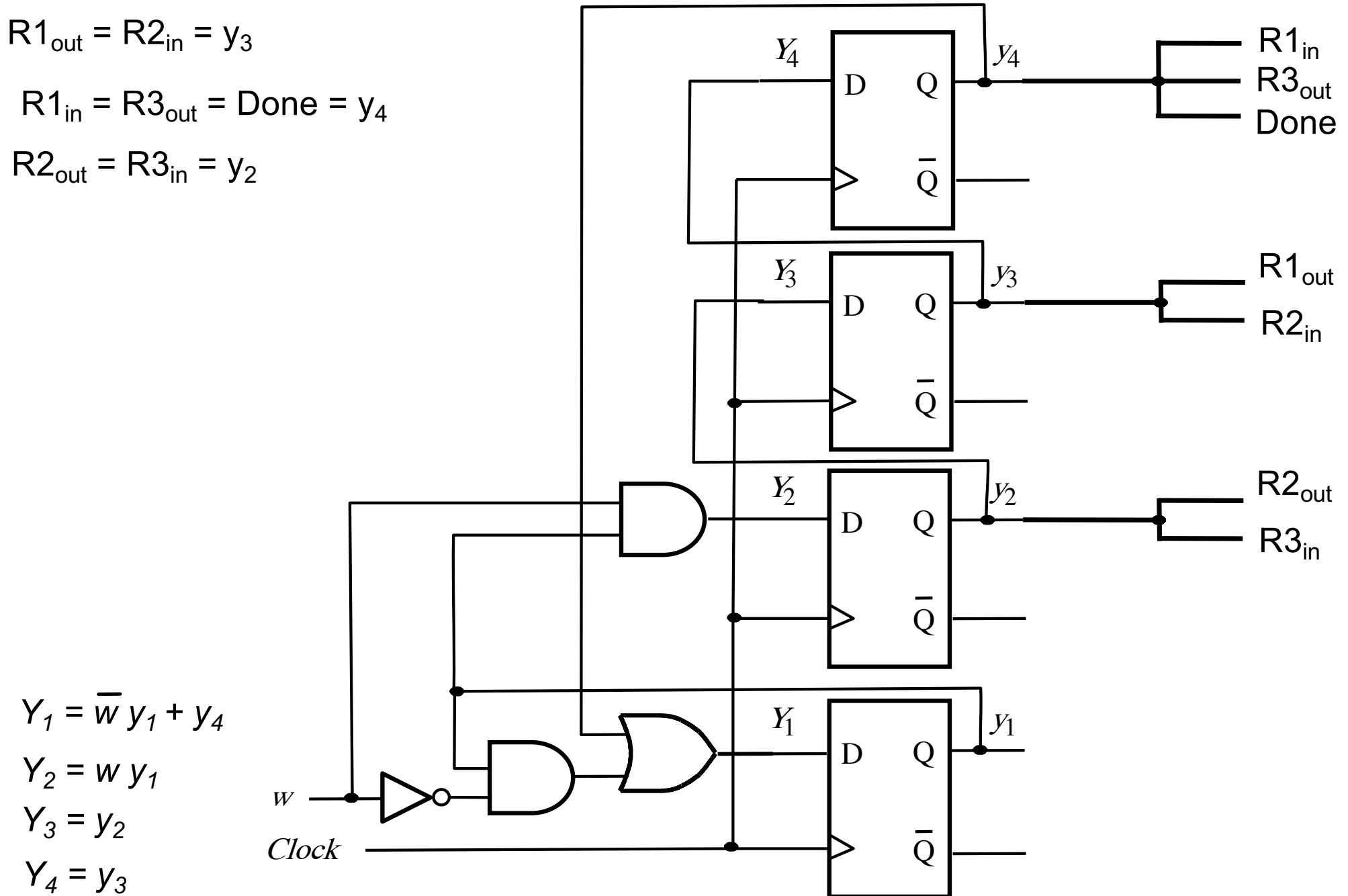


Encoding #4:

A=0001, B=0010, C=0100, D=1000


(same as before, but shows an alternative implementation with a 4-bit ring counter)

Exploit the Structure of the FSM

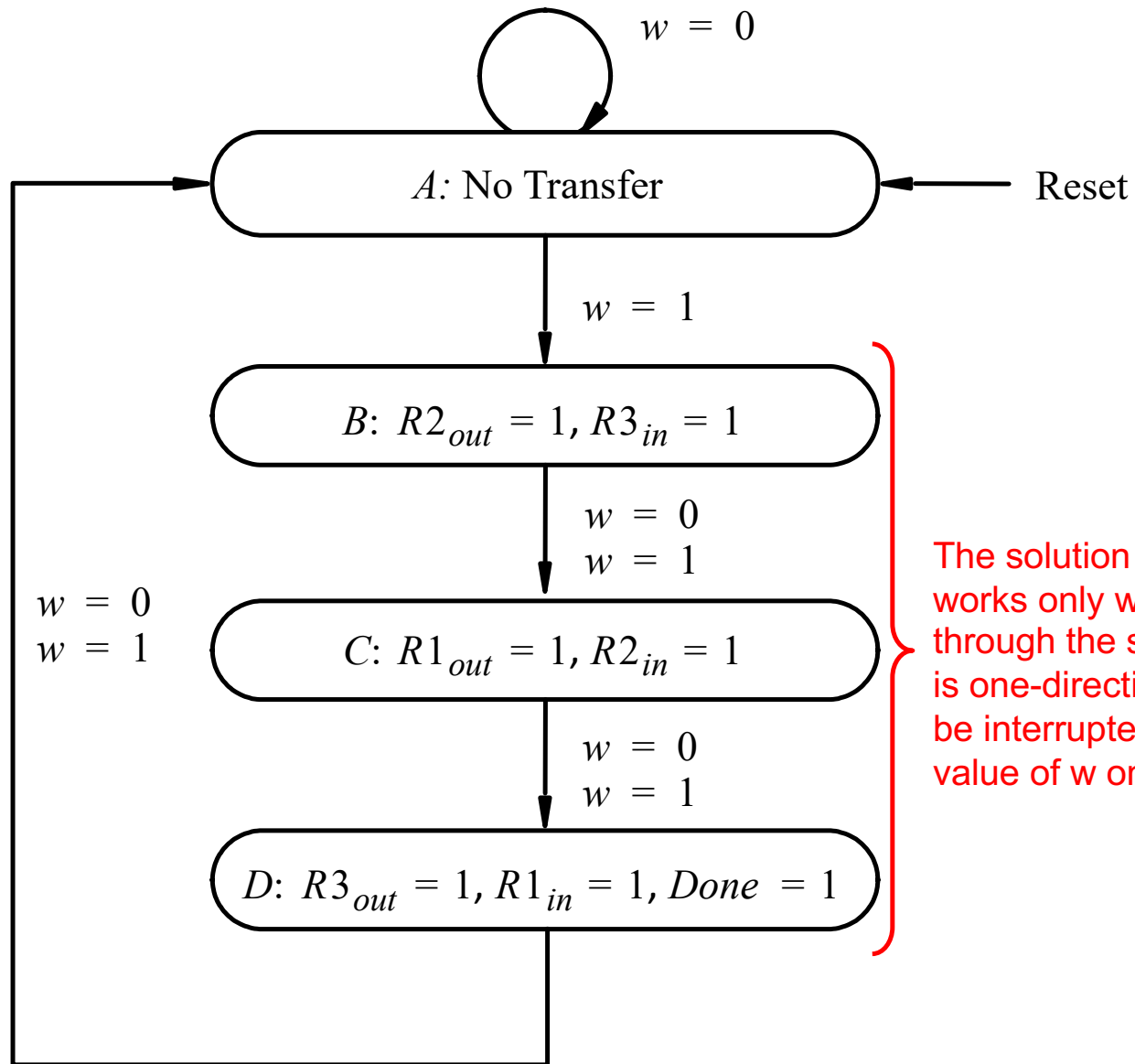

[Figure 6.11 from the textbook]

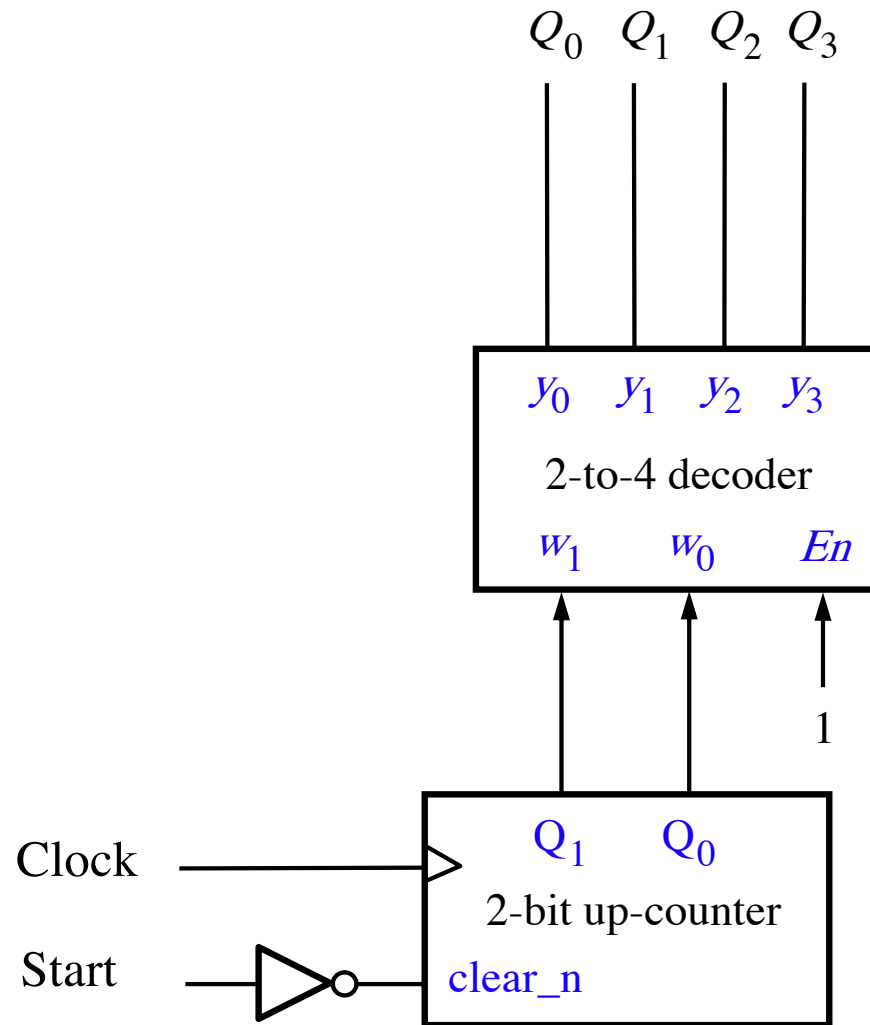Alternative version of a 4-bit ring counter





Alternative version of a 4-bit ring counter

Switch to 1-based indexing of the outputs →

Q_1 Q_2 Q_3 Q_4


Switch to 1-based indexing of the outputs →

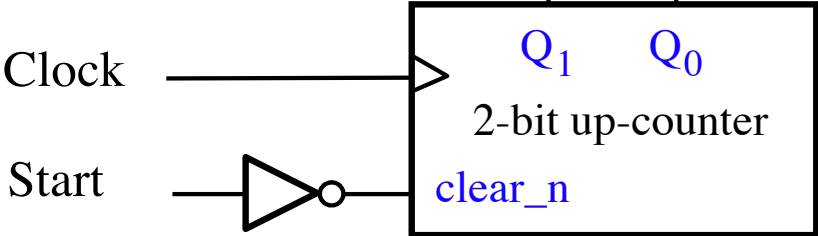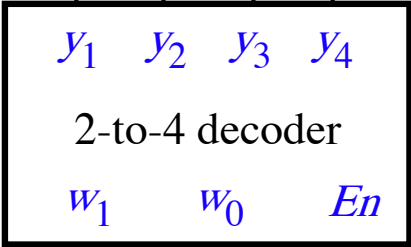(this is done to be consistent with the previous example)




Alternative version of a 4-bit ring counter


Also, omit these labels \rightarrow

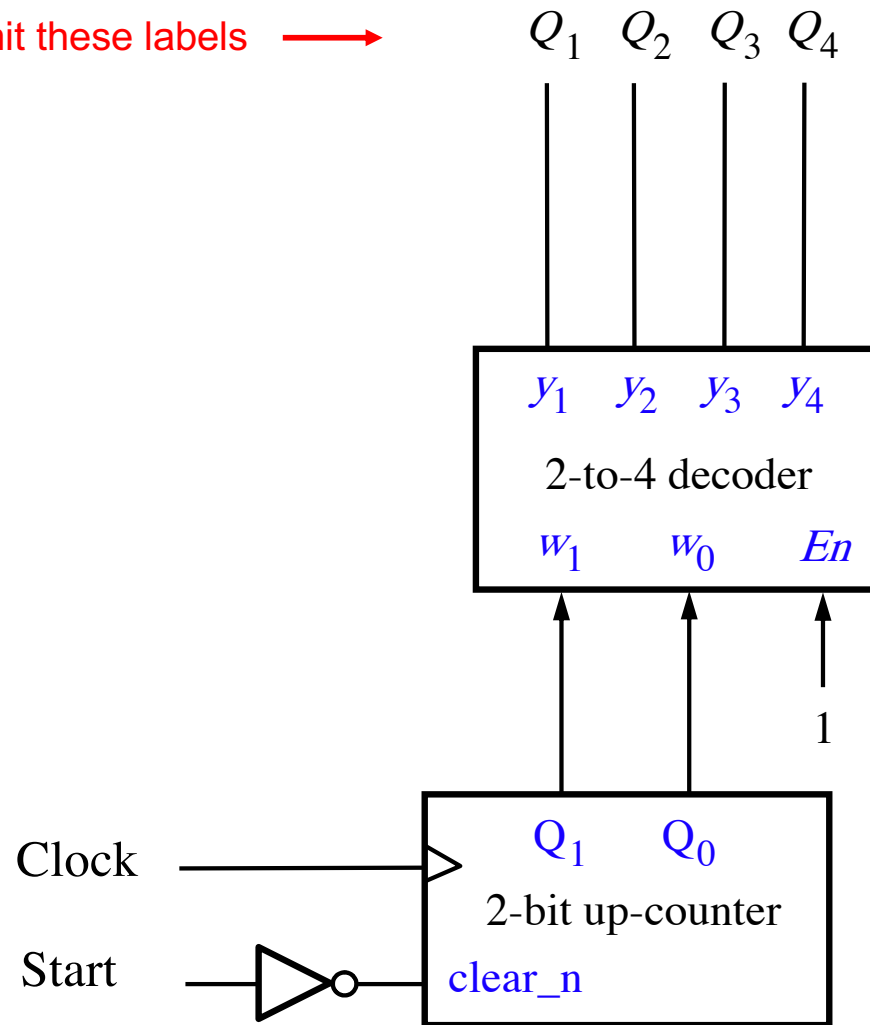

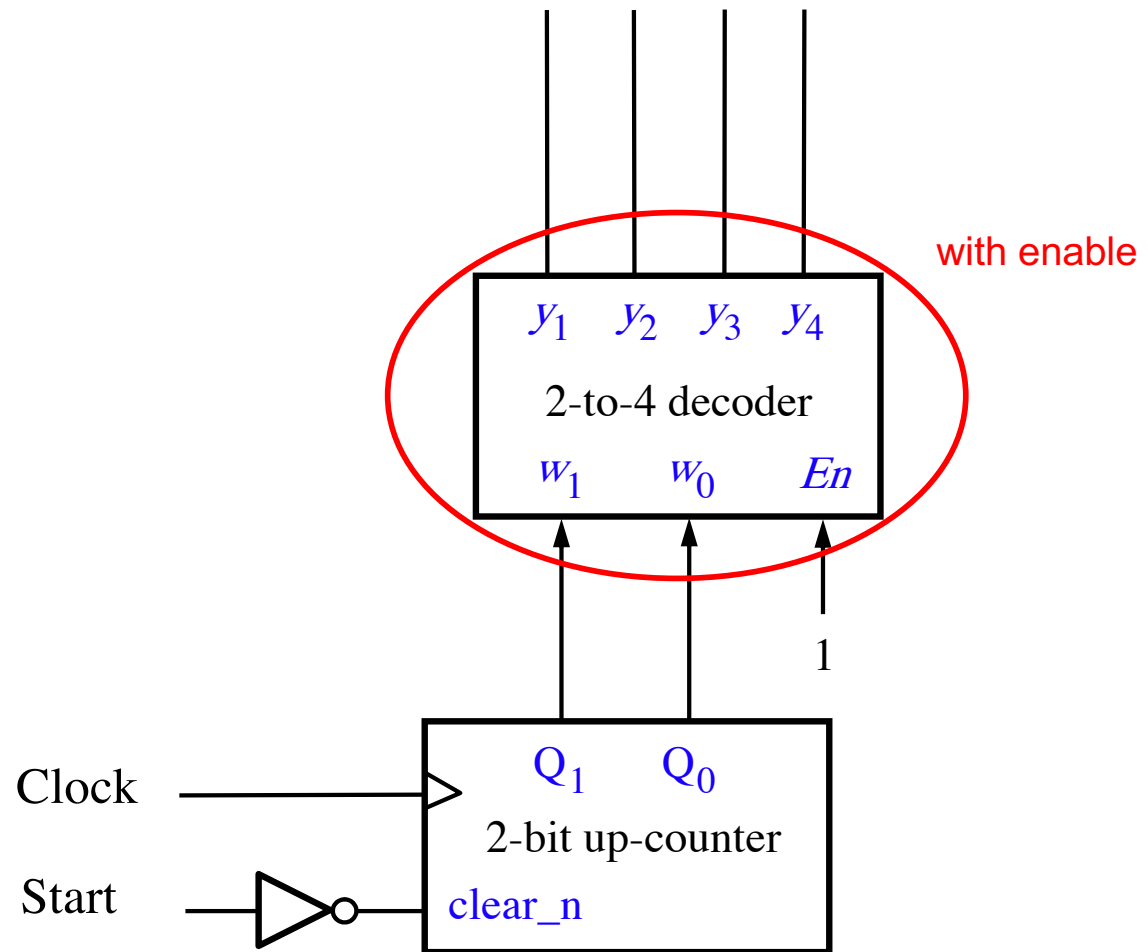Alternative version of a 4-bit ring counter




2-to-4 Decoder with Enable Input

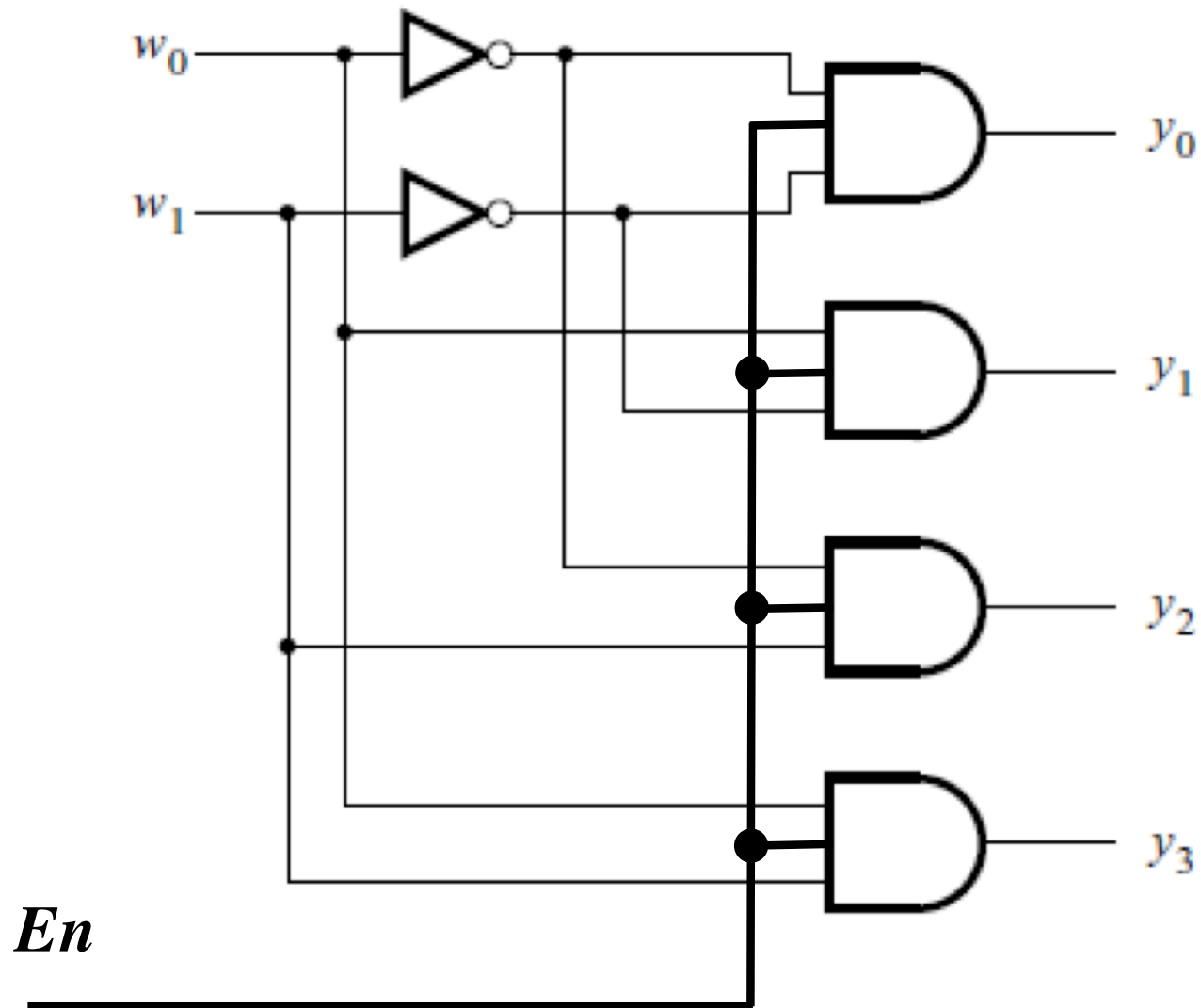

[Figure 4.14c from the textbook]


2-to-4 Decoder with Enable Input

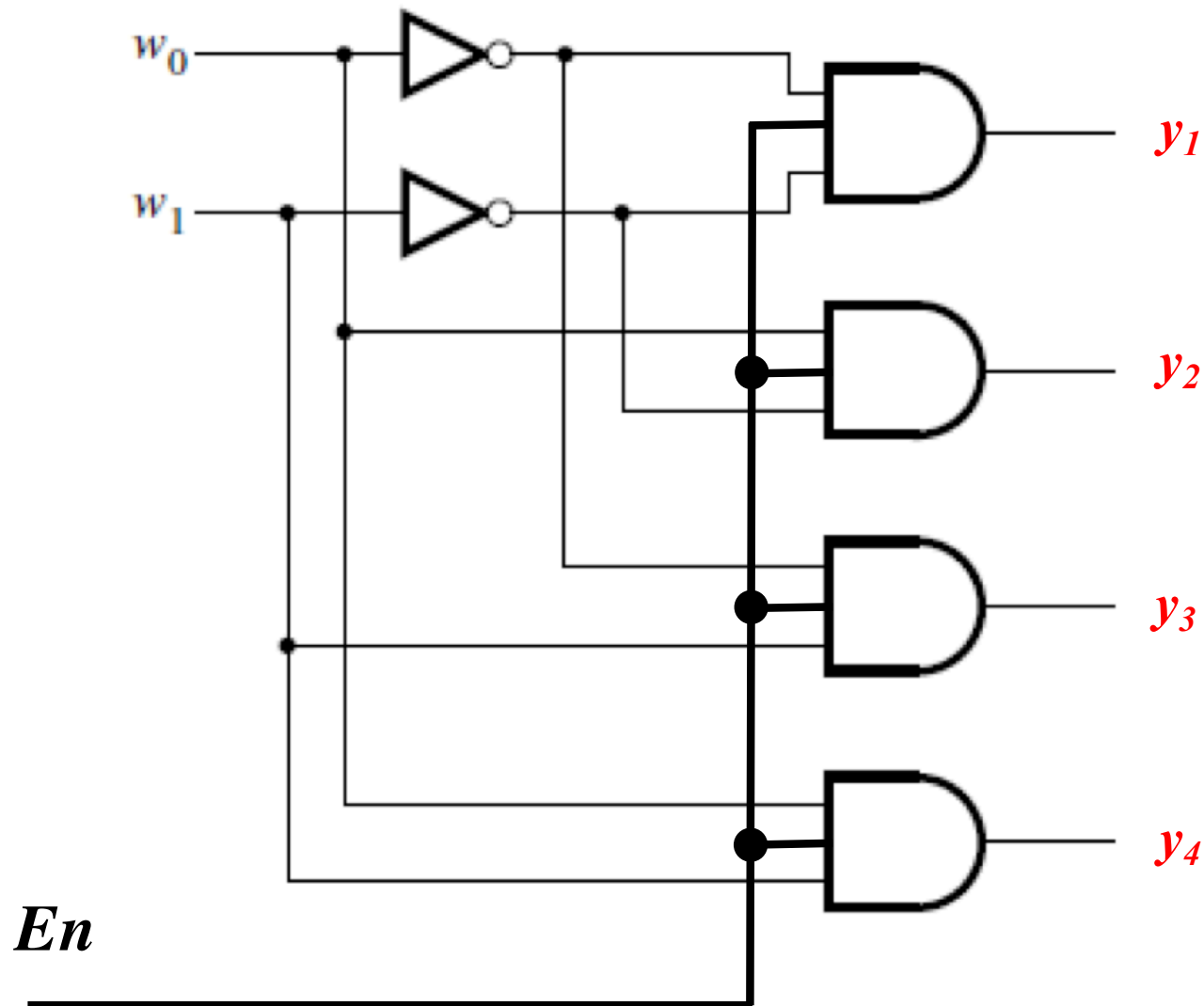

Switch to 1-based indexing of the outputs


(this is done to be consistent with the previous example)

2-to-4 Decoder with Enable Input

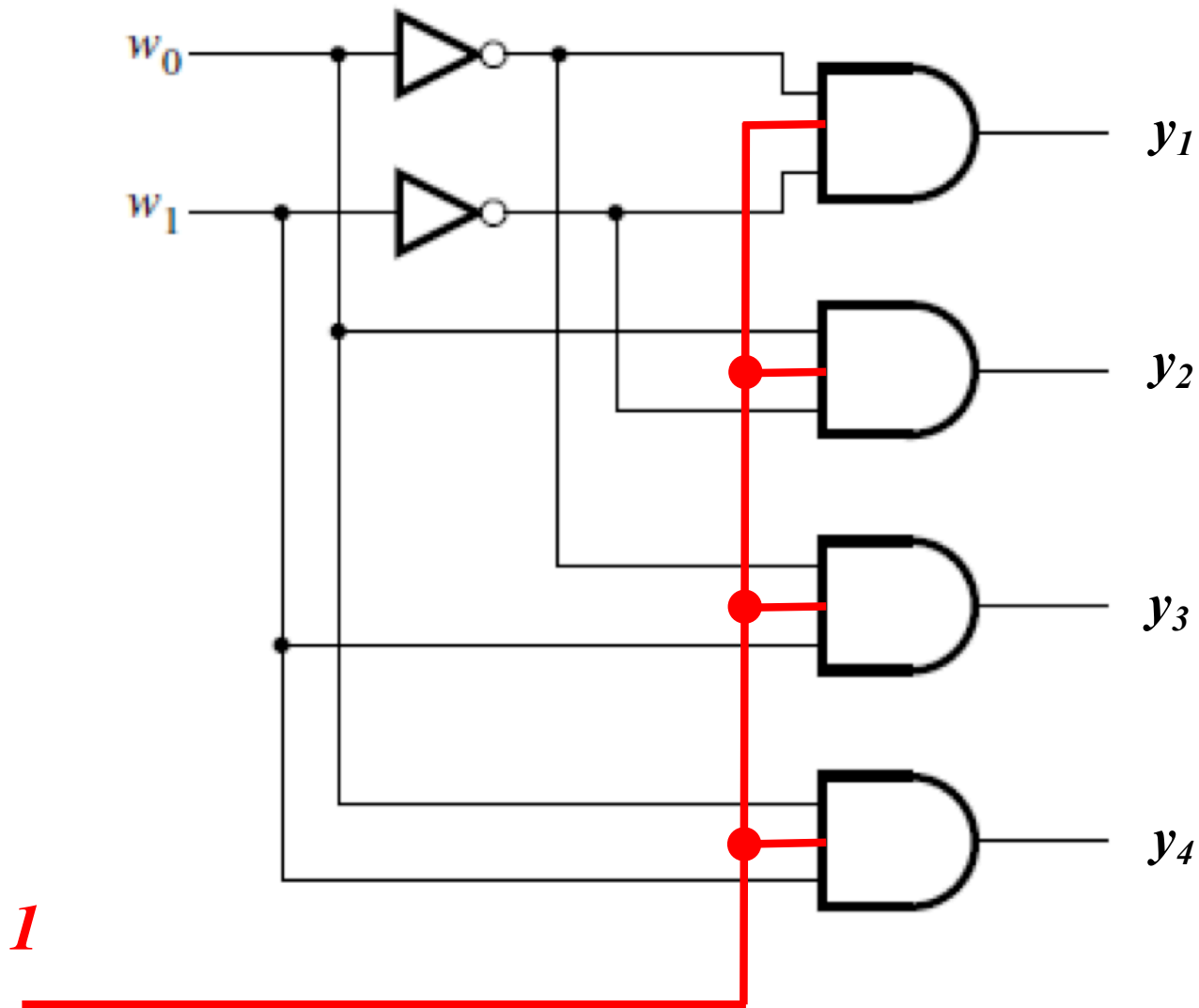


(always enabled in this example)

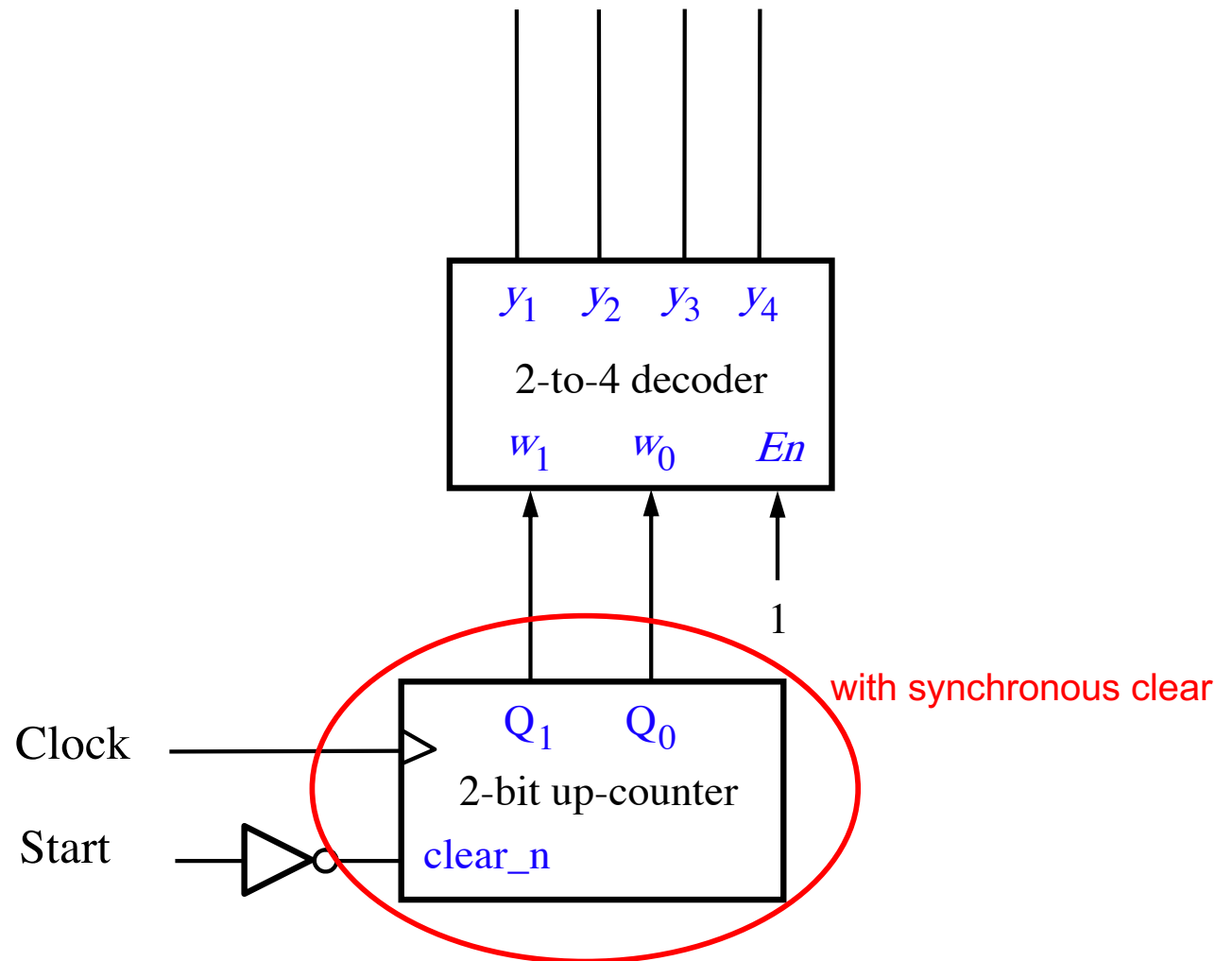Alternative version of a 4-bit ring counter




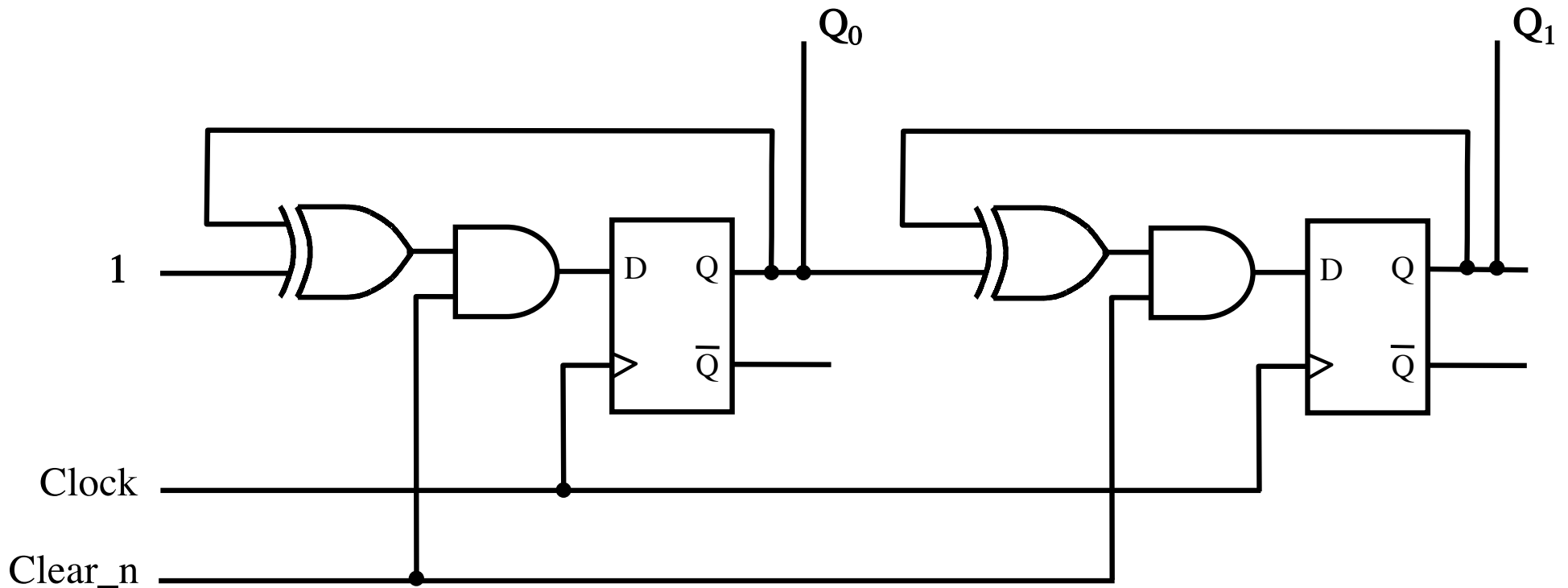2-Bit Synchronous Up-Counter (with synchronous clear)




This counter can be cleared only on the positive clock edge.


Let's Complete the Circuit Diagram

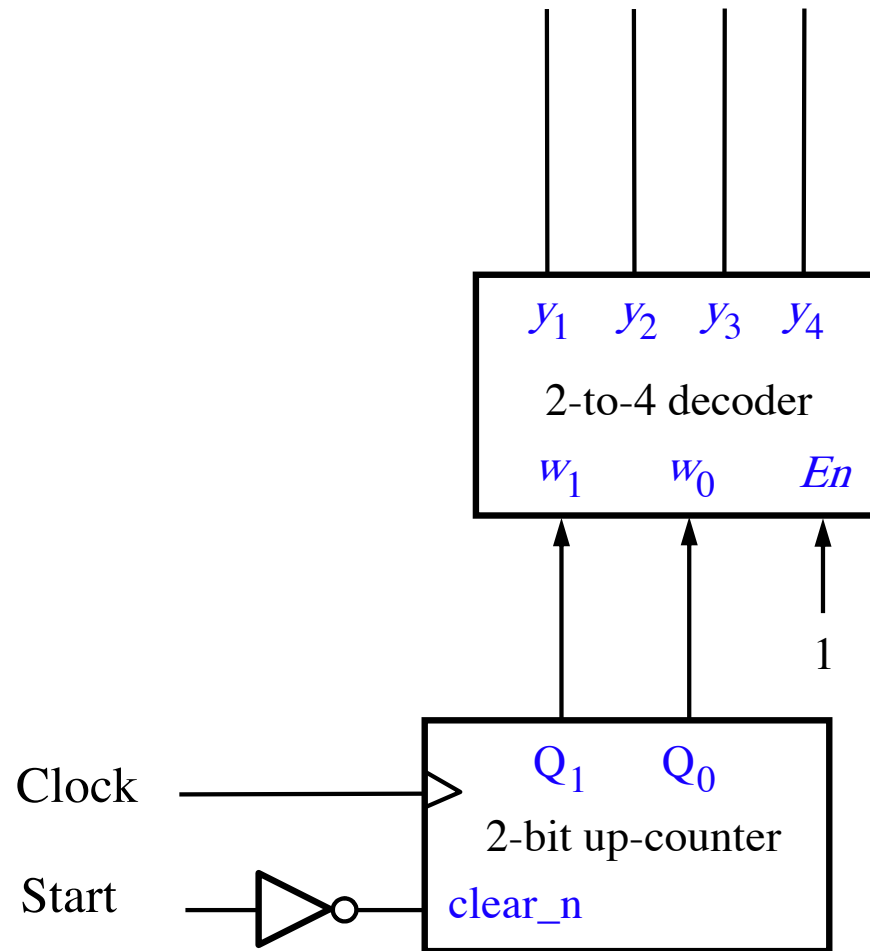


Let's Complete the Circuit Diagram

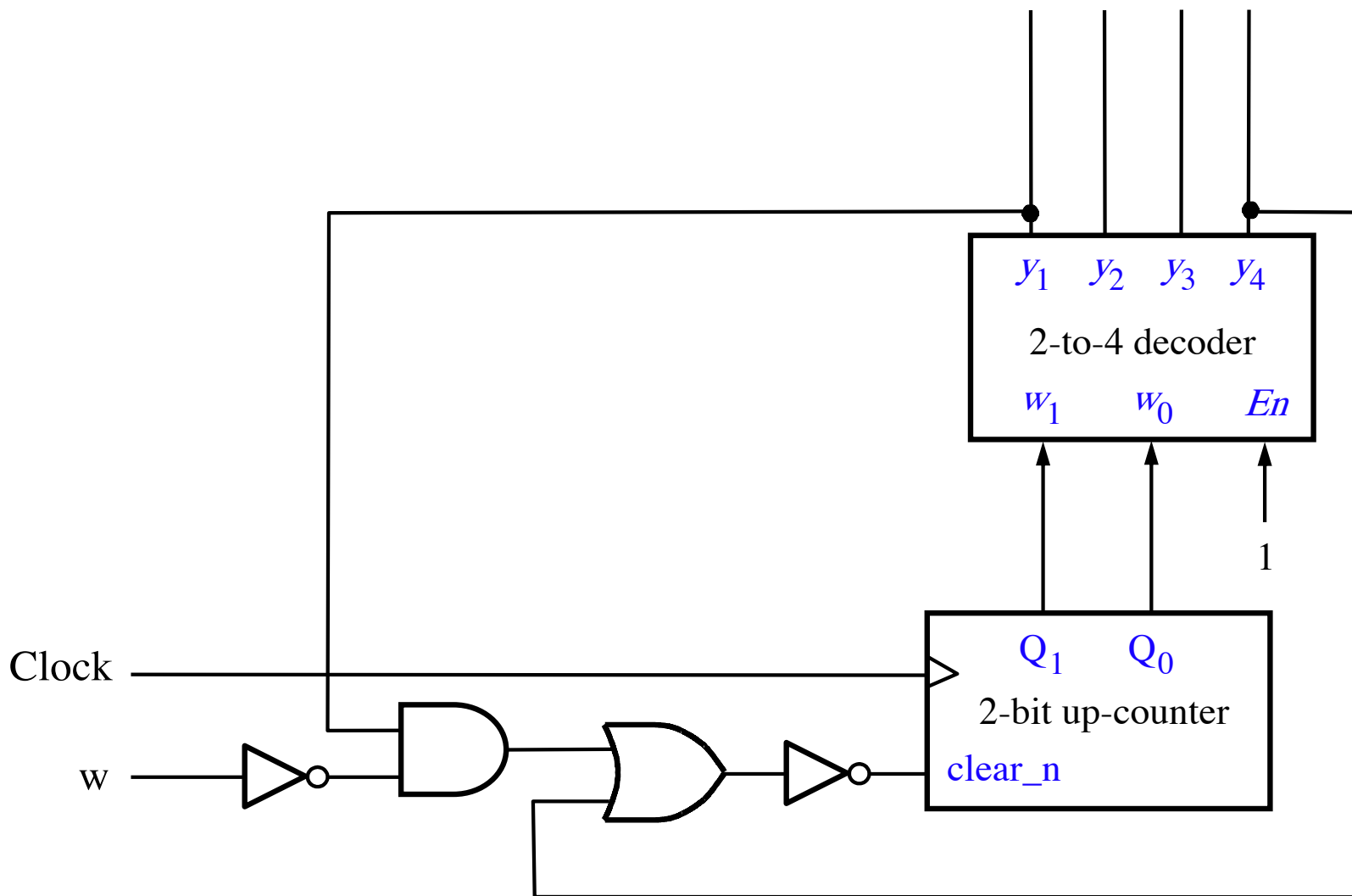

Let's Complete the Circuit Diagram

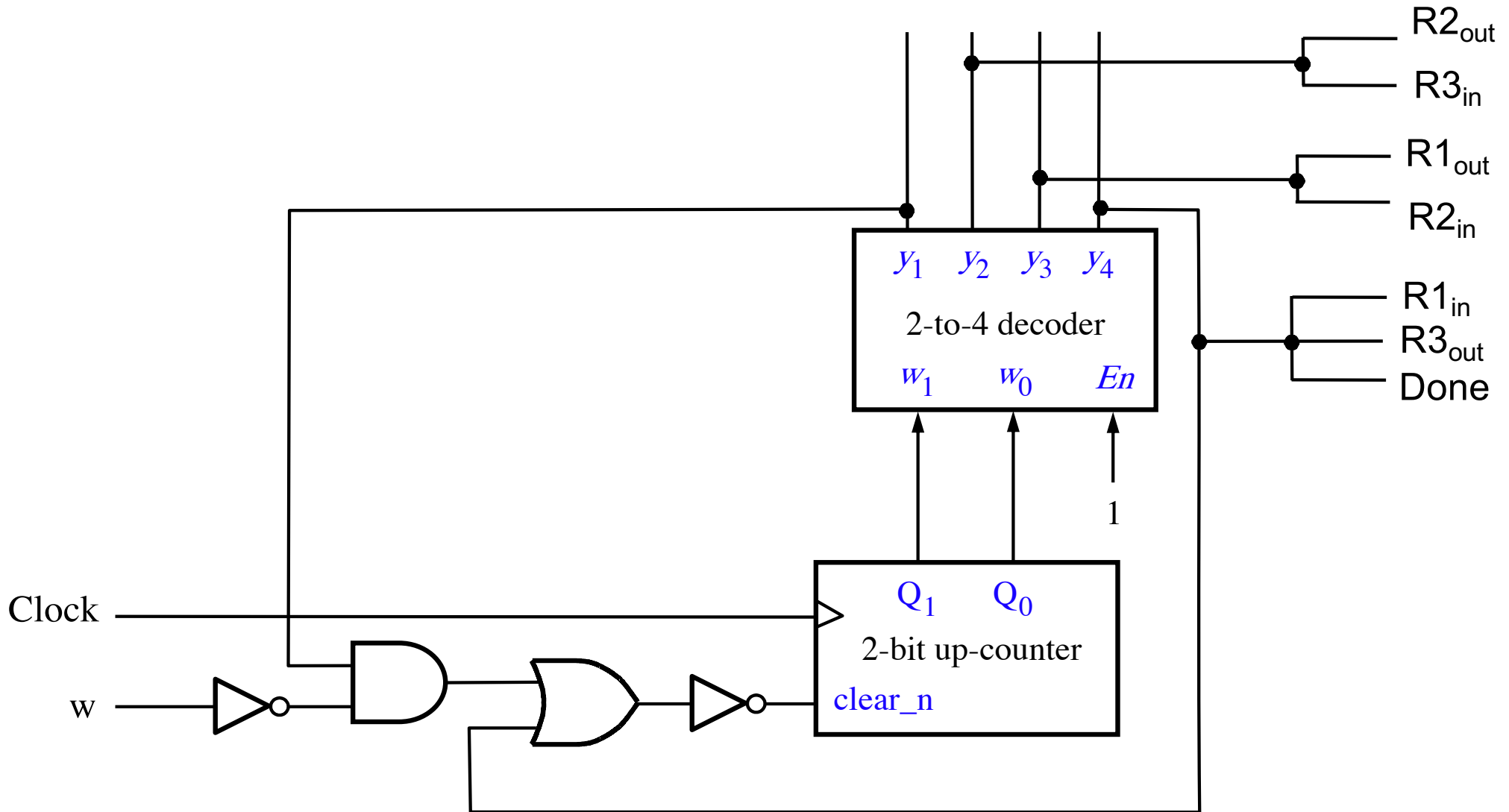

Let's Complete the Circuit Diagram

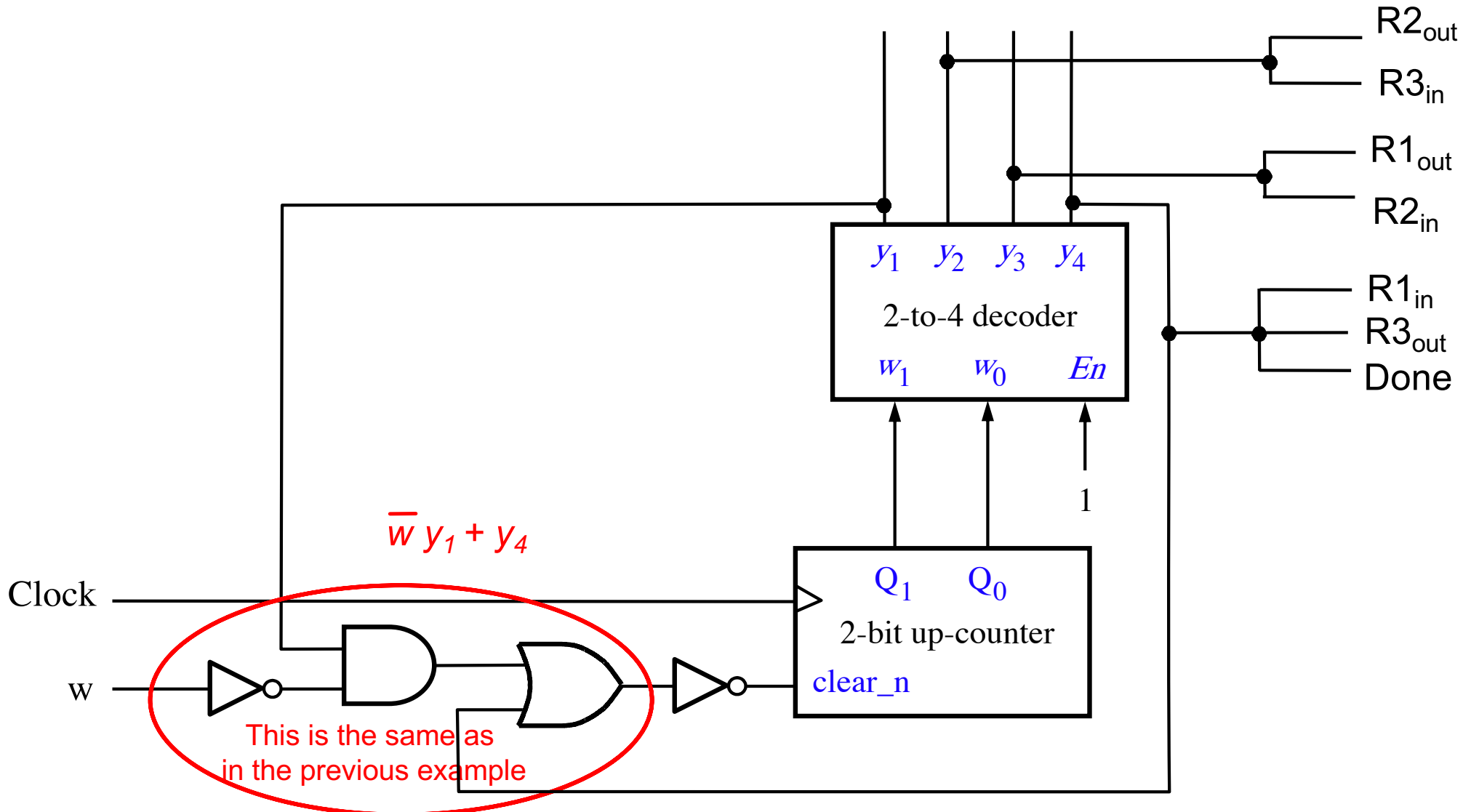


The Solution for Encoding #3

$$R1_{out} = R2_{in} = y_3$$

$$R1_{in} = R3_{out} = Done = y_4$$

$$R2_{out} = R3_{in} = y_2$$

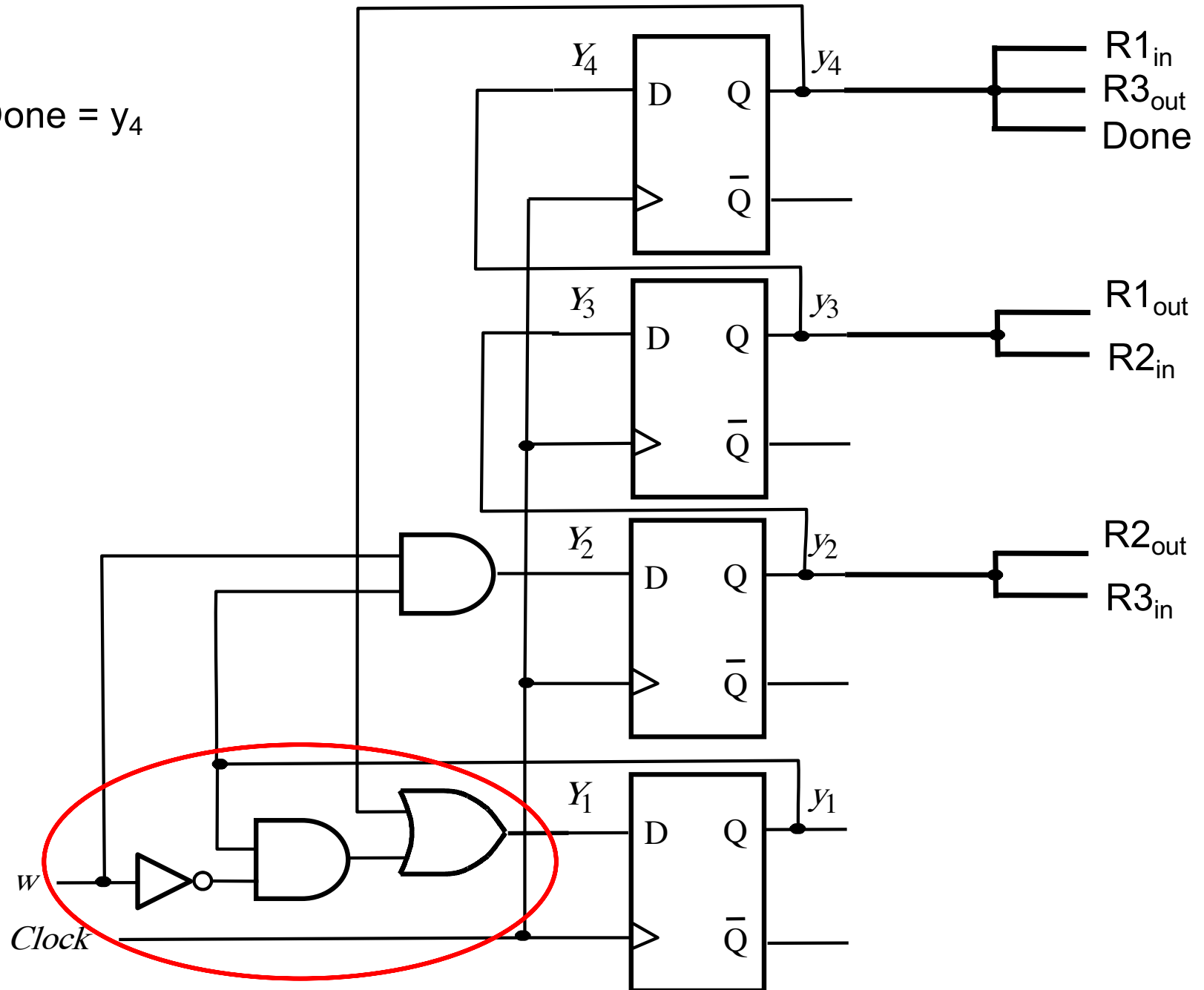


$$Y_1 = \bar{w} y_1 + y_4$$

$$Y_2 = w y_1$$


$$Y_3 = y_2$$

$$Y_4 = y_3$$


How Does It Work?

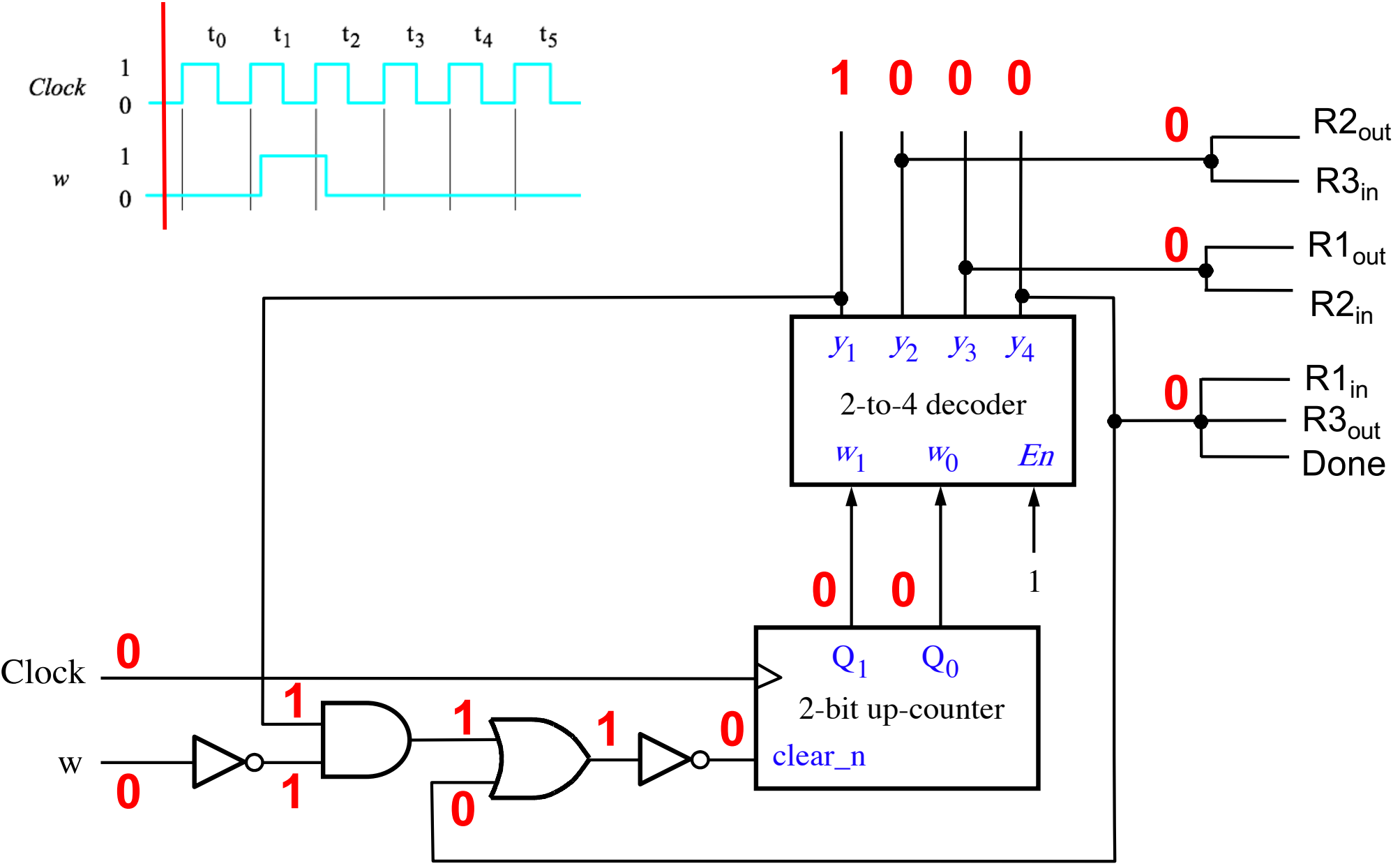


How Does It Work?

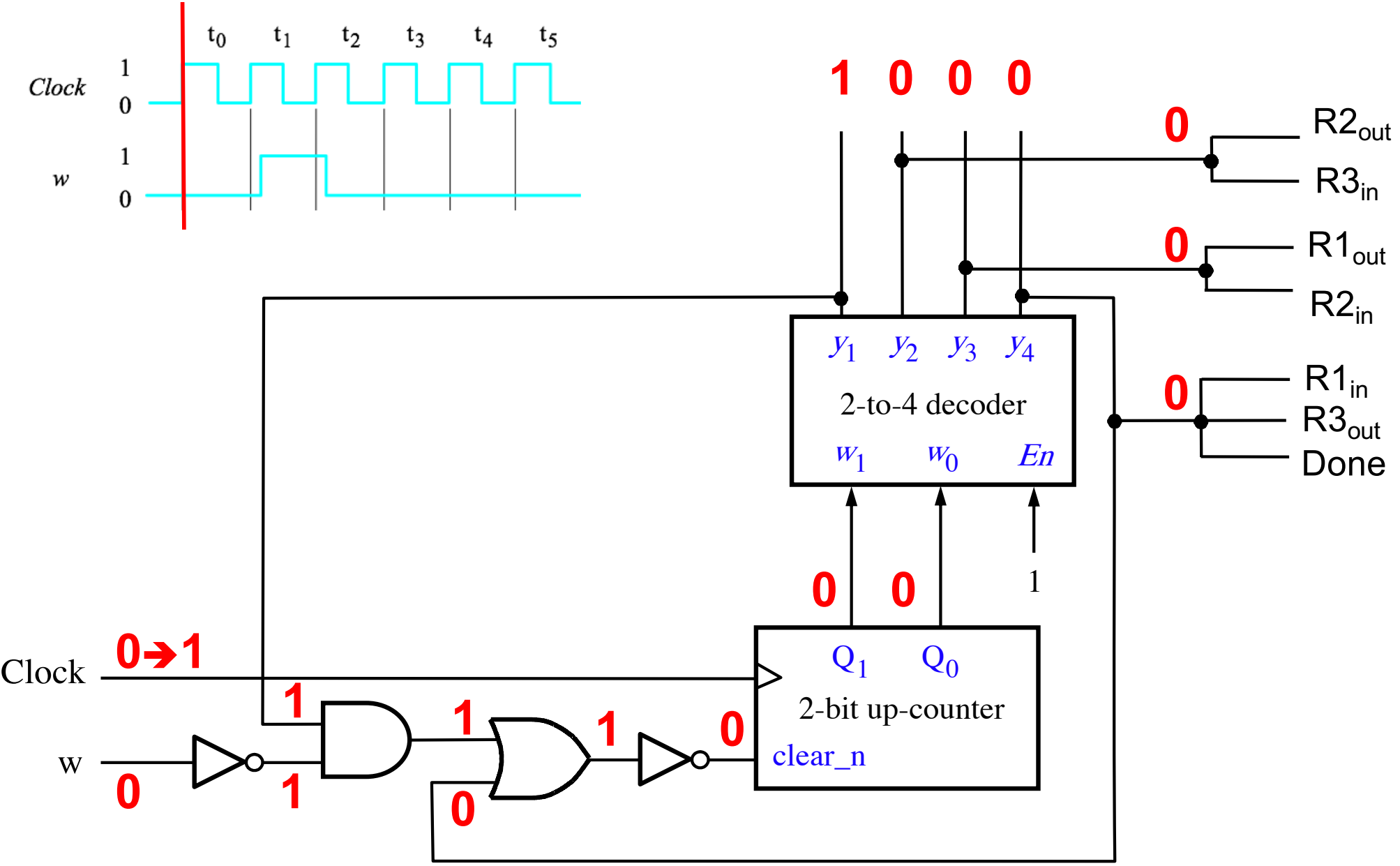


How Does It Work?

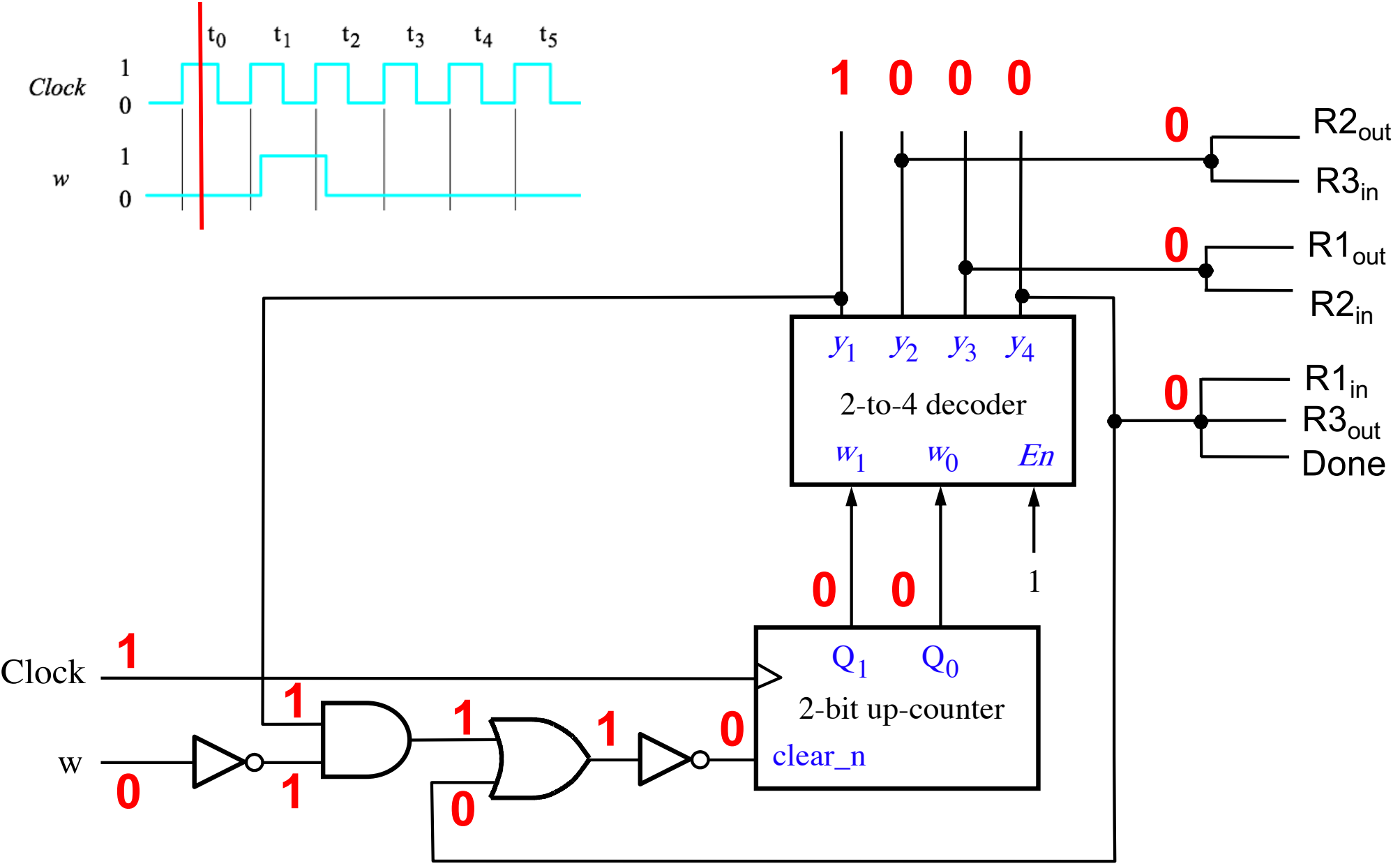


How Does It Work?

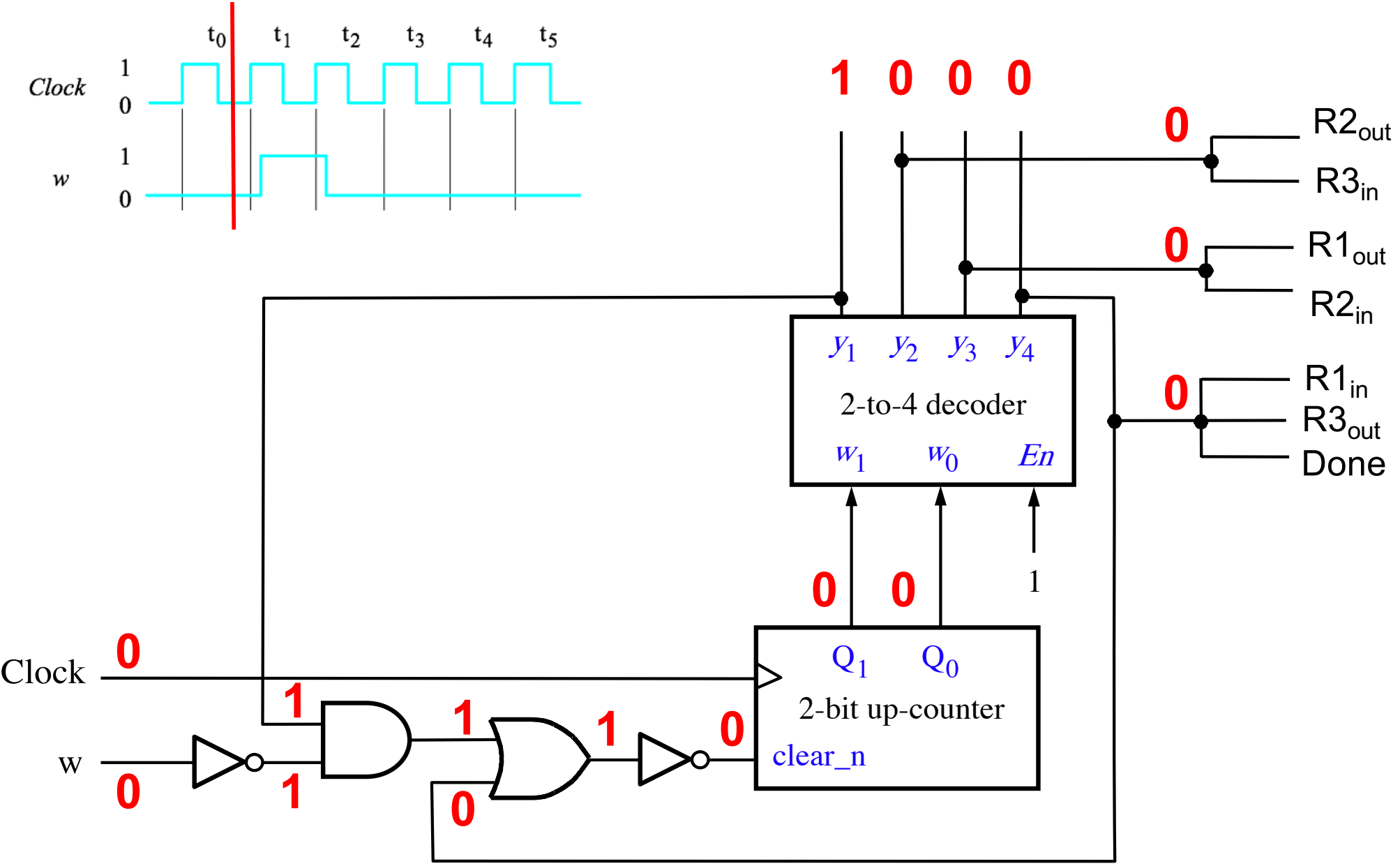


How Does It Work?

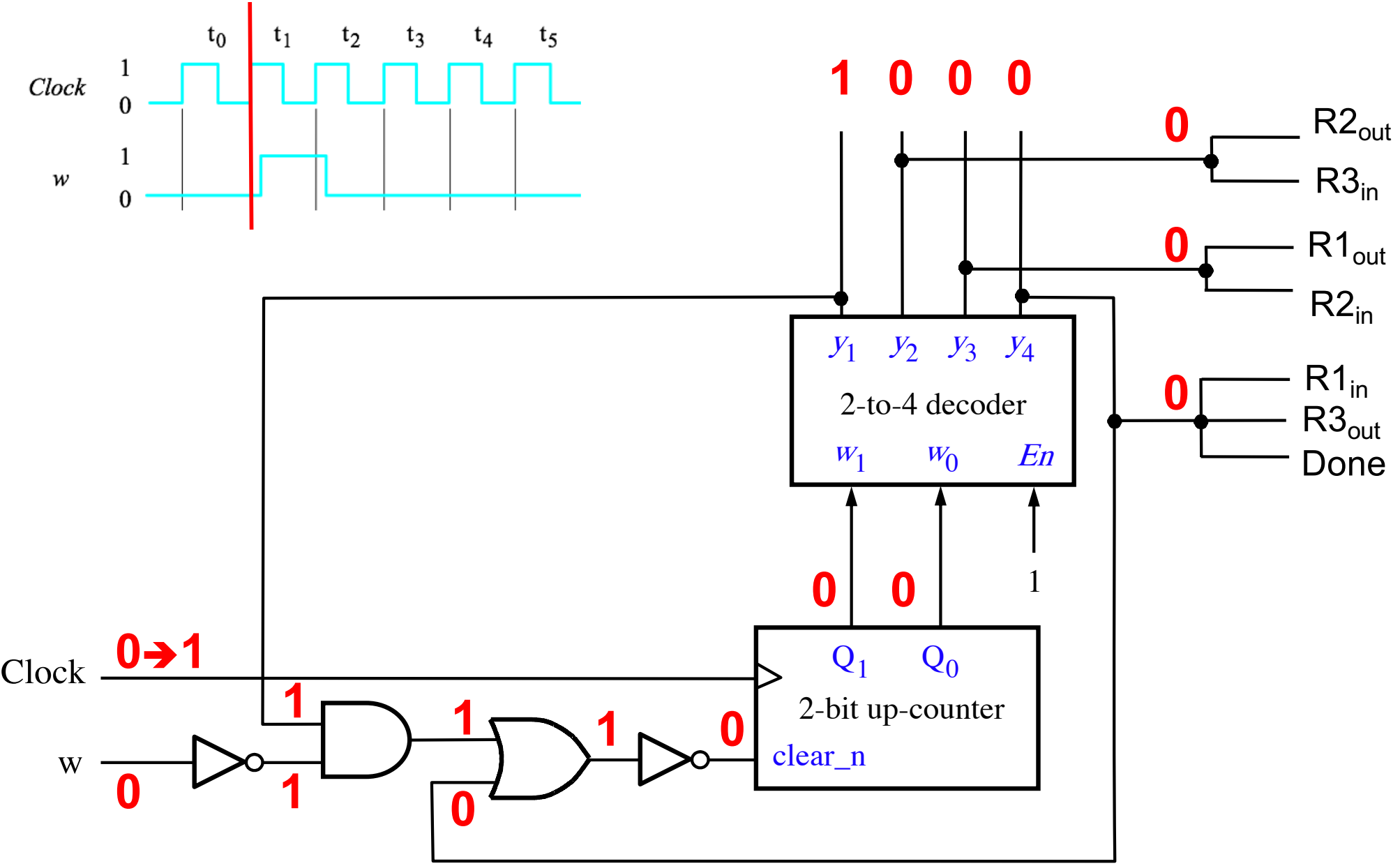


How Does It Work?

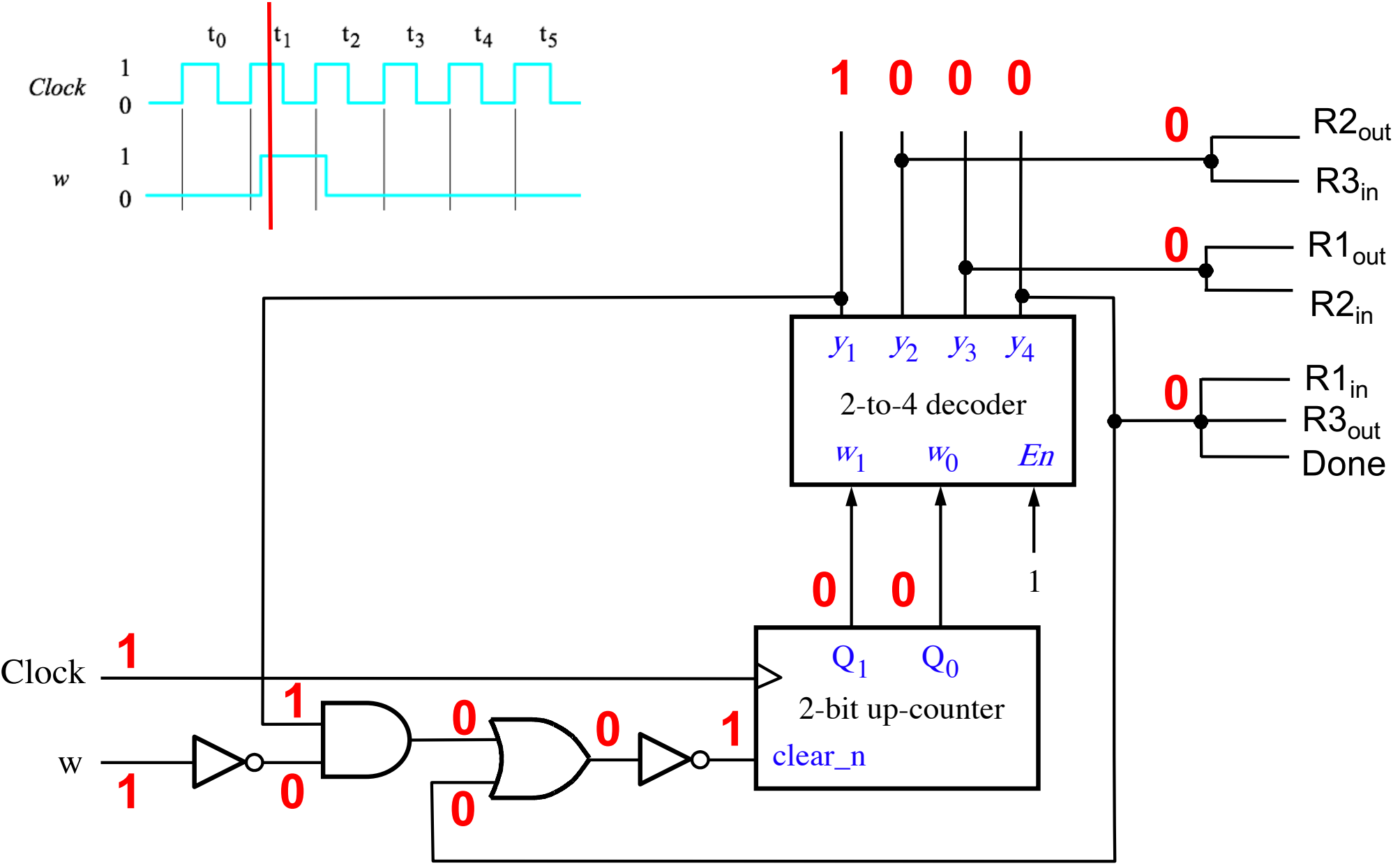


How Does It Work?

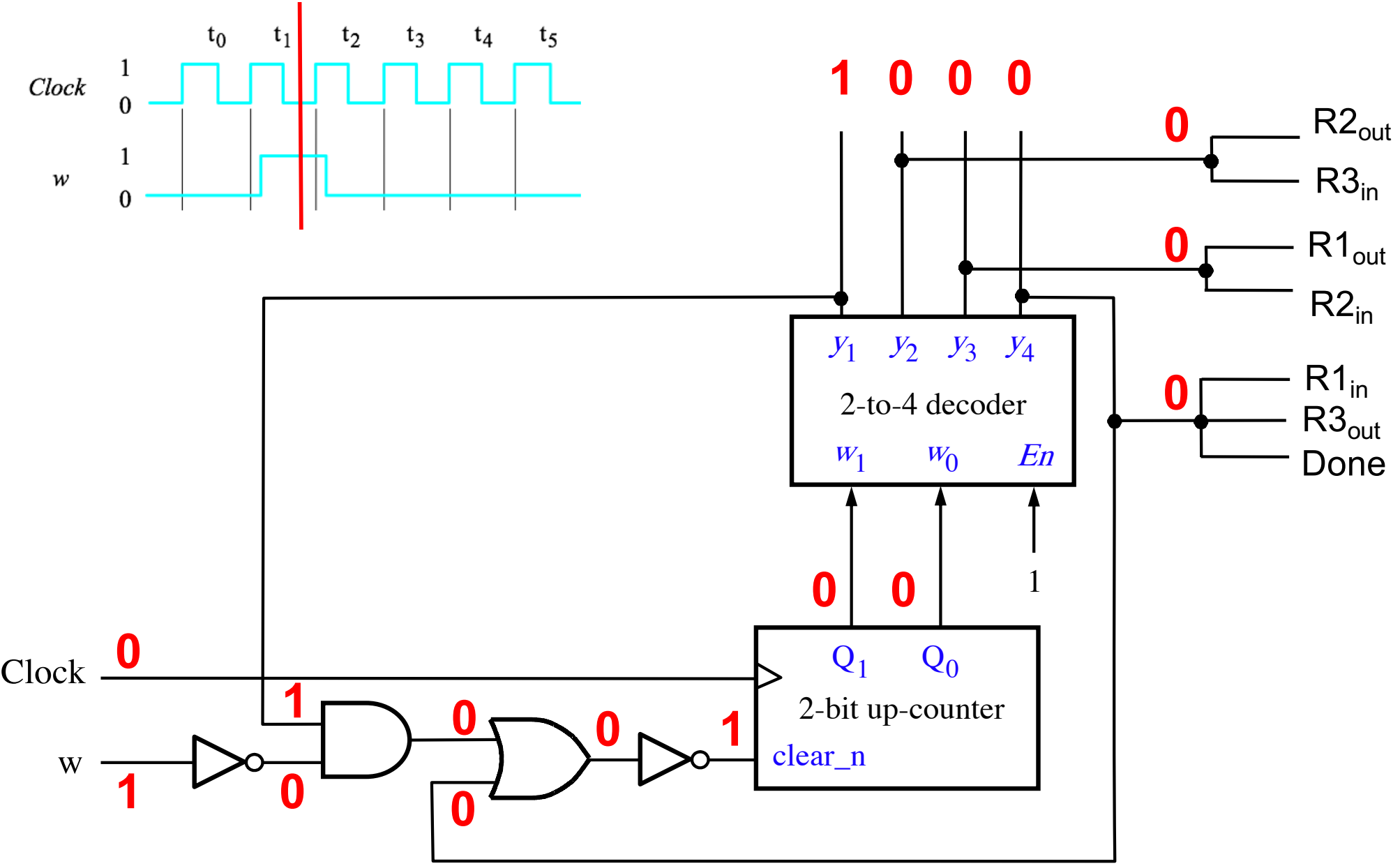


How Does It Work?

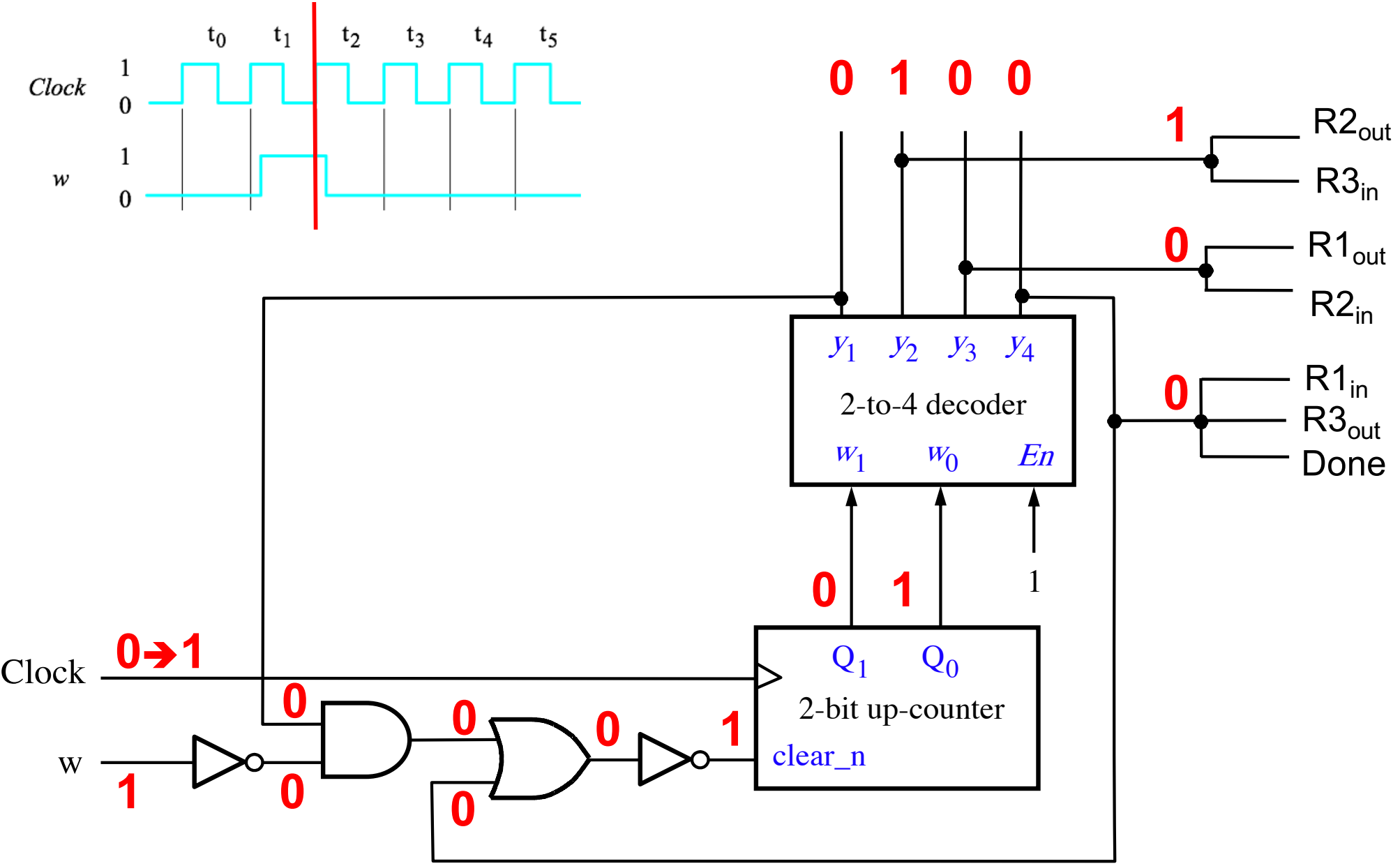


How Does It Work?

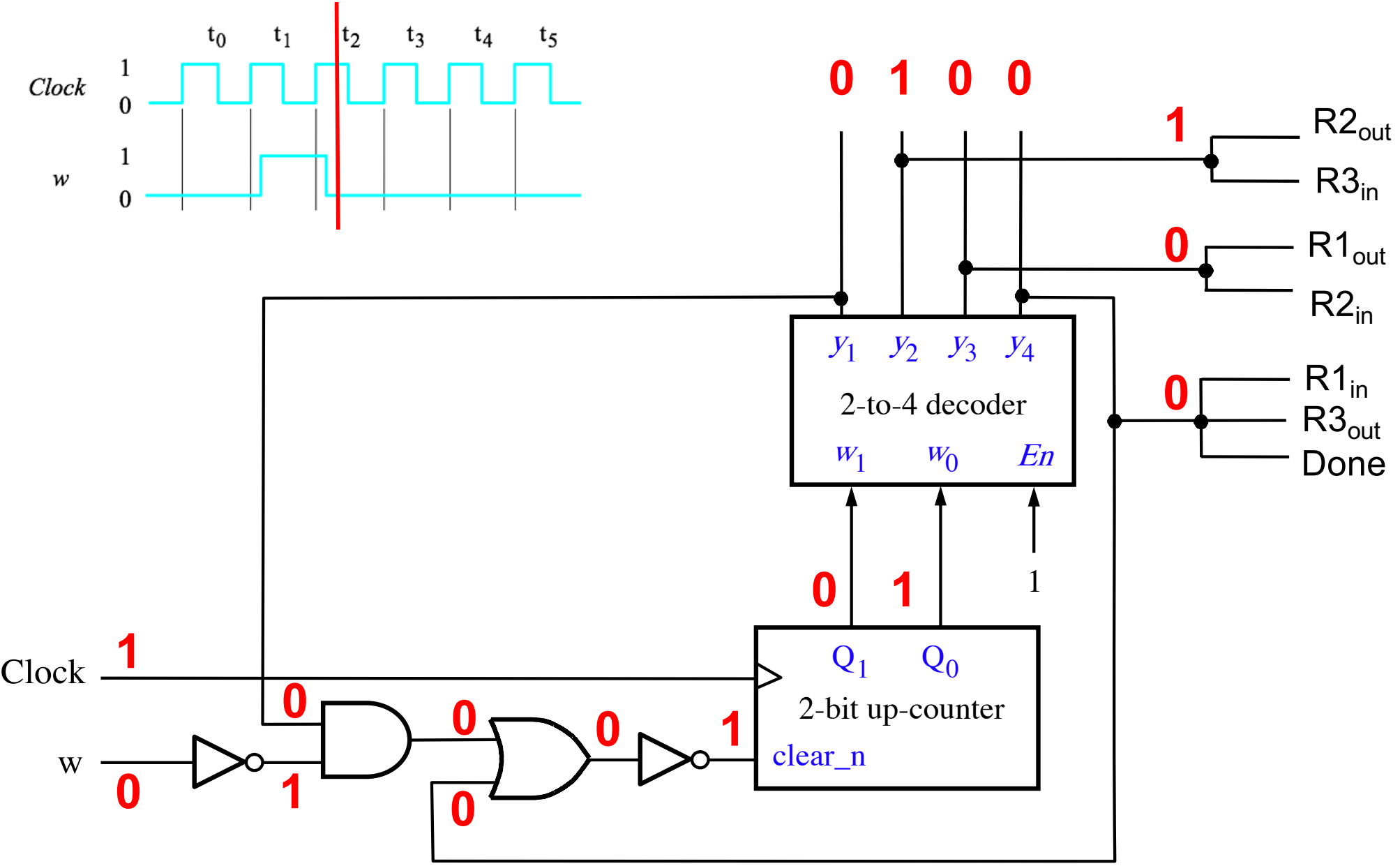


How Does It Work?

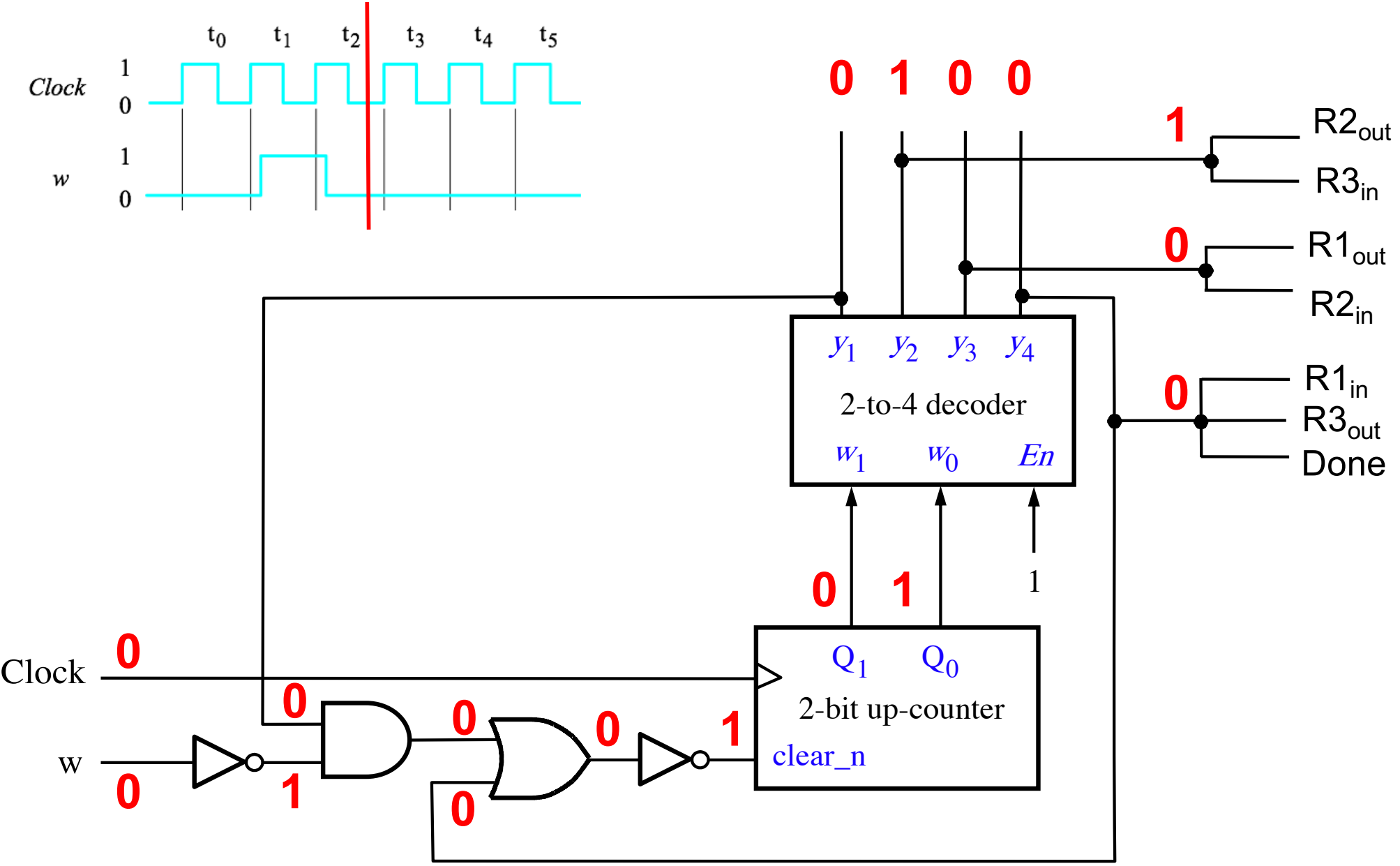


How Does It Work?

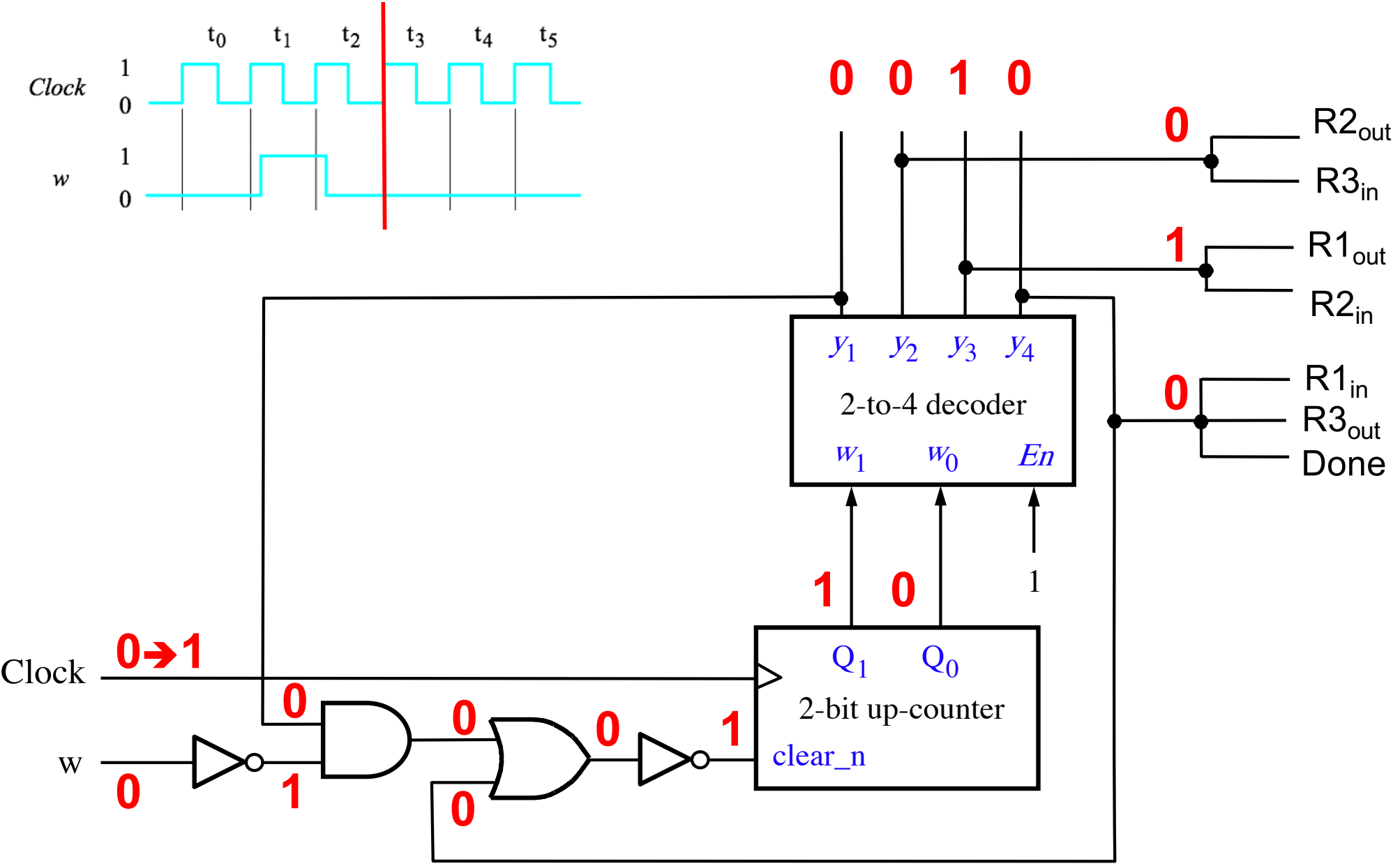


How Does It Work?

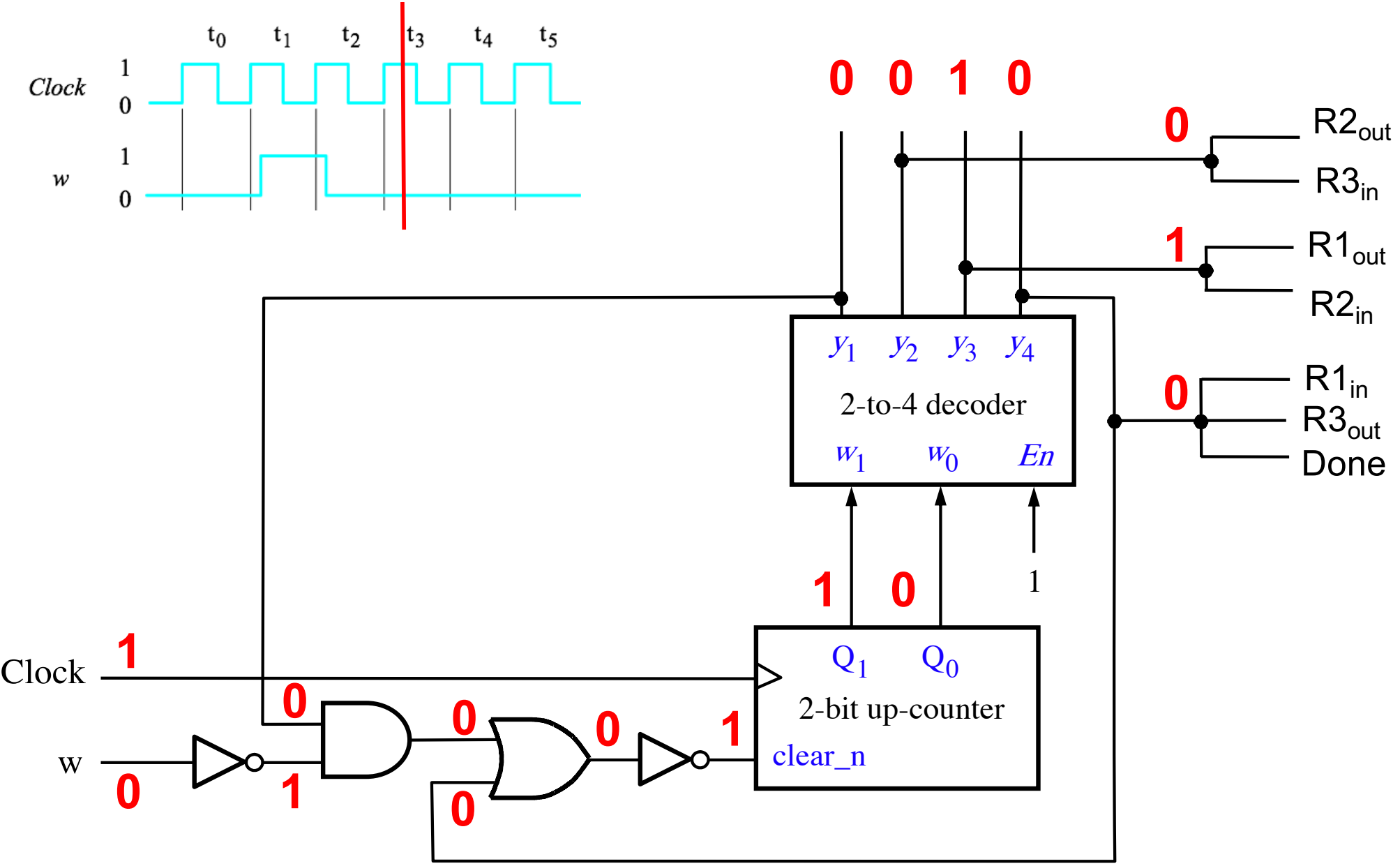


How Does It Work?

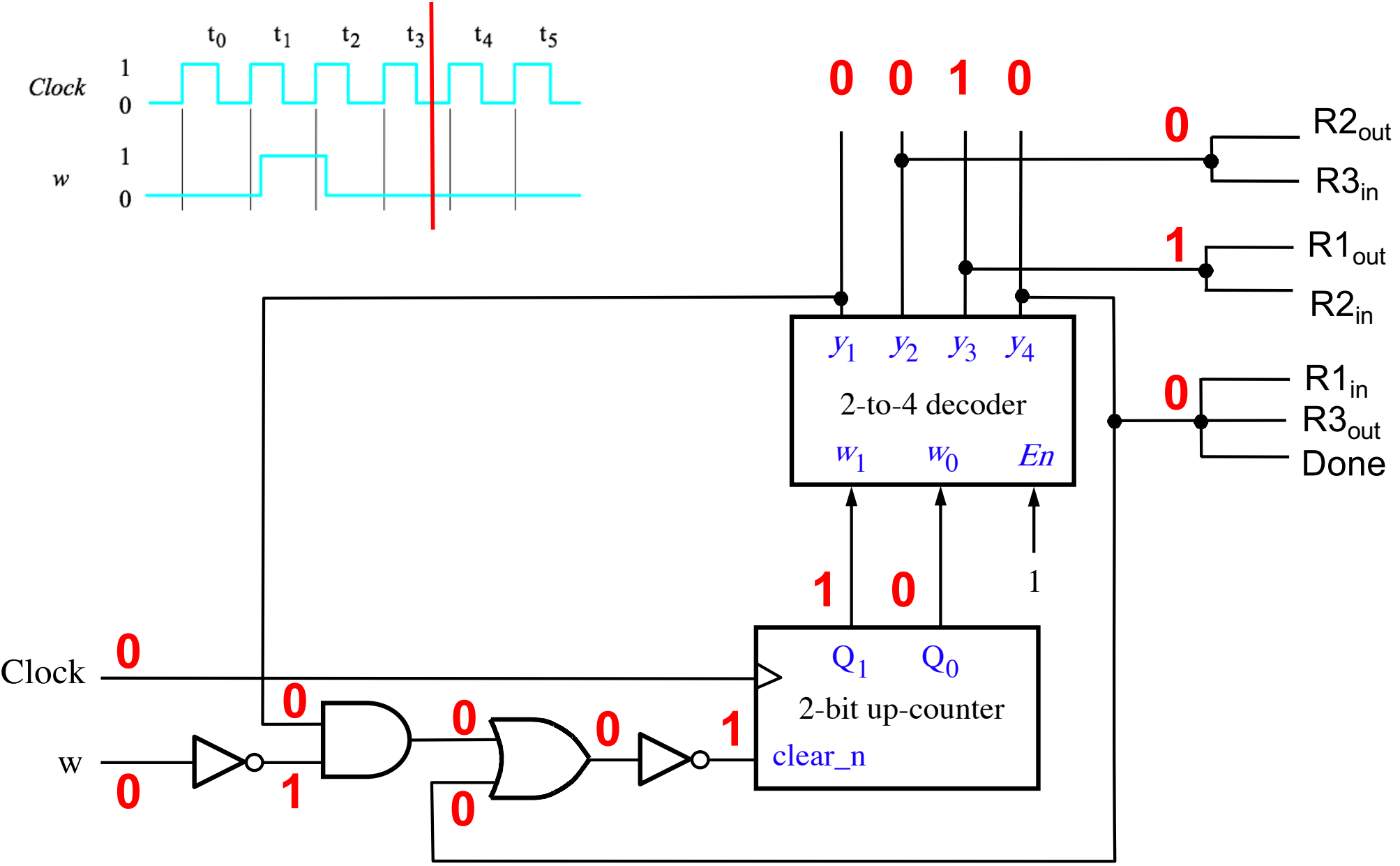


How Does It Work?

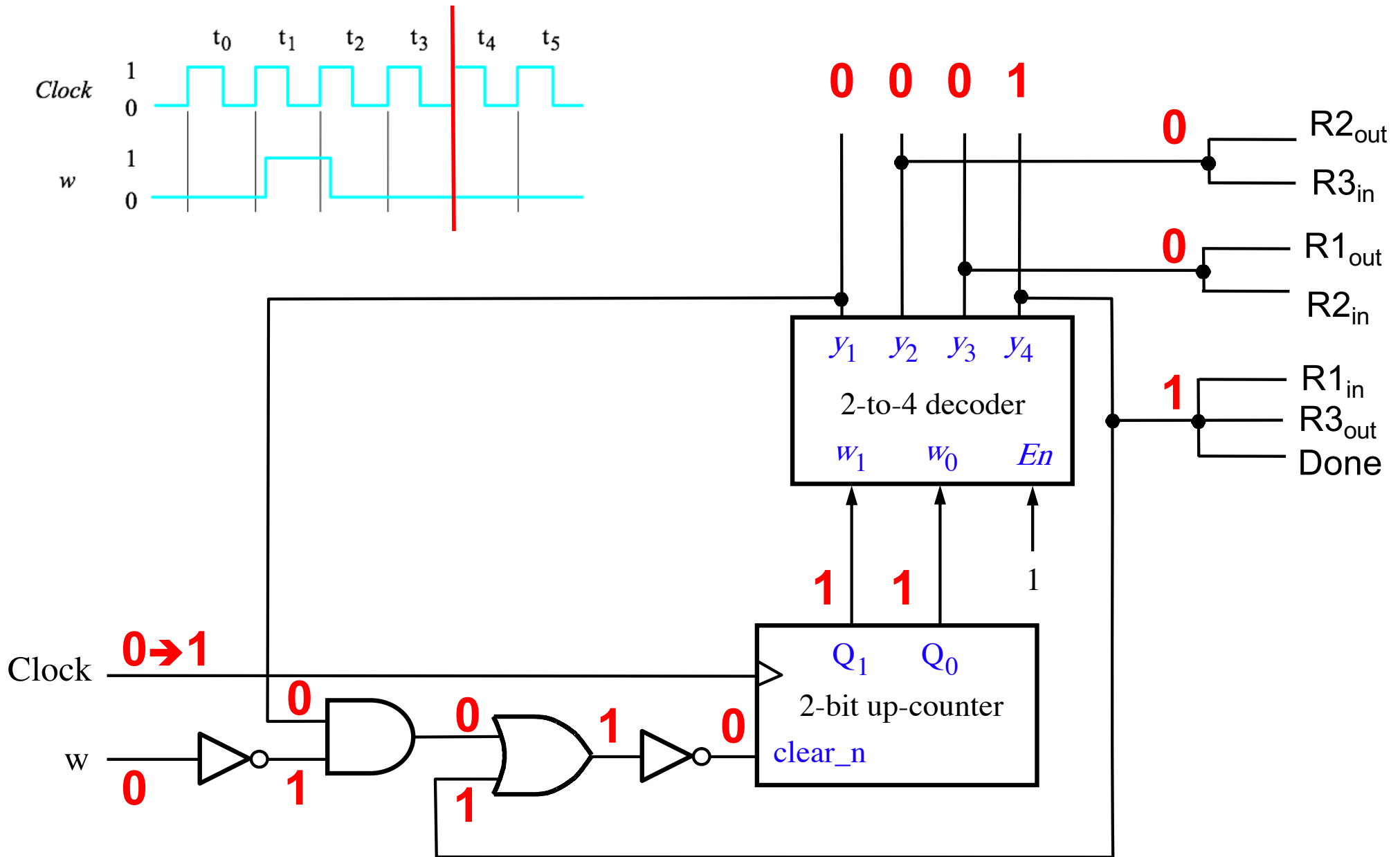


How Does It Work?

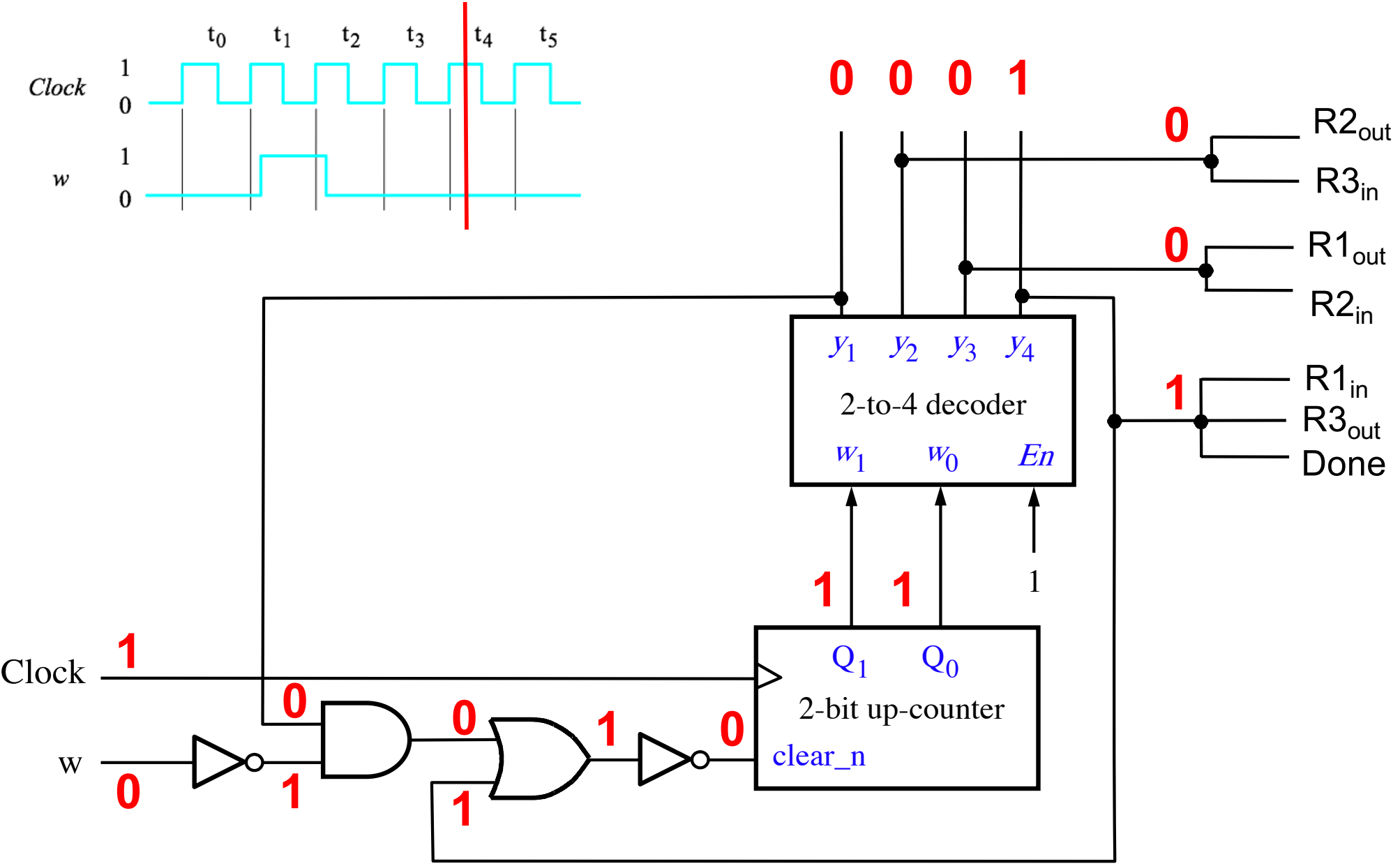


How Does It Work?

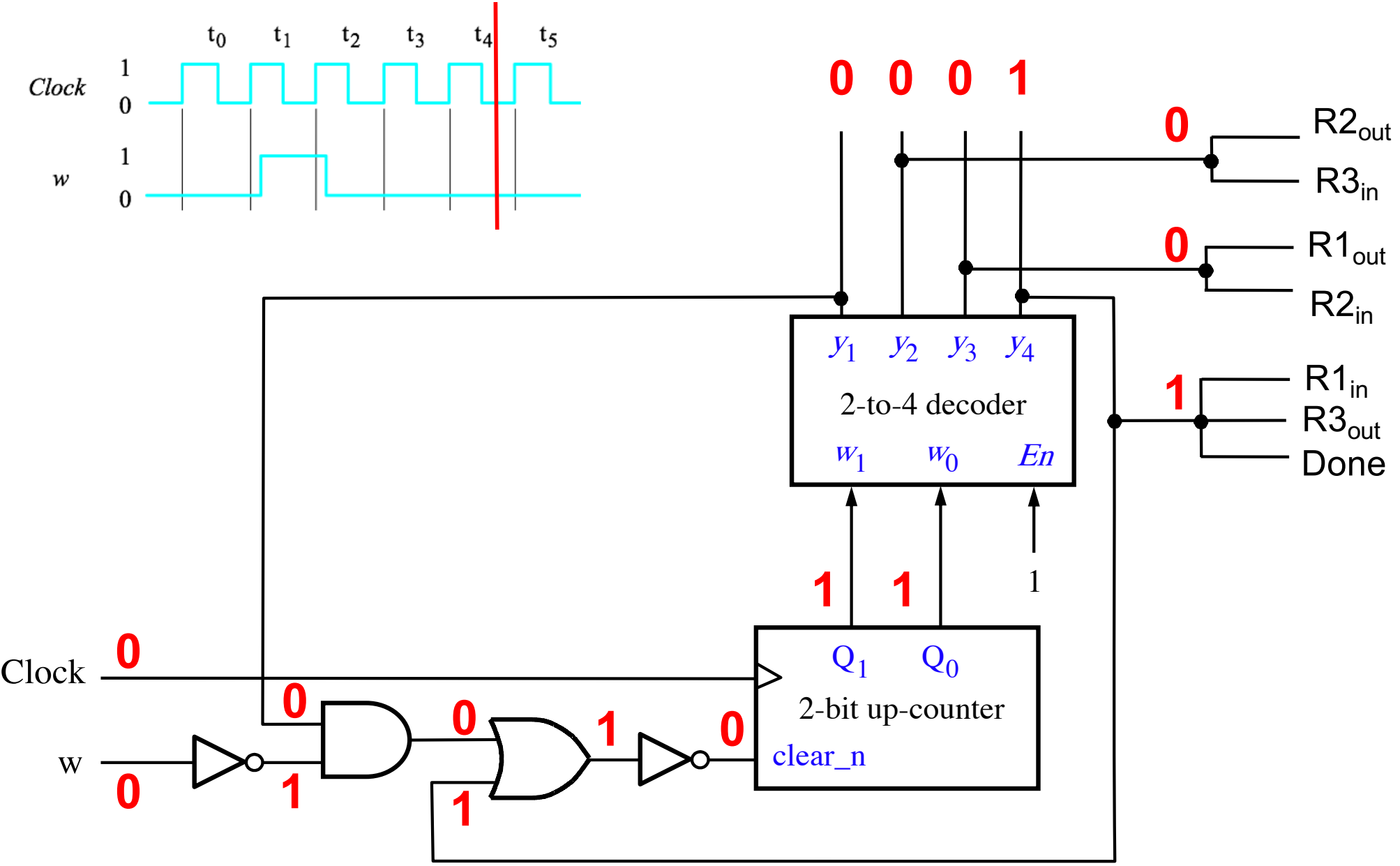

How Does It Work?

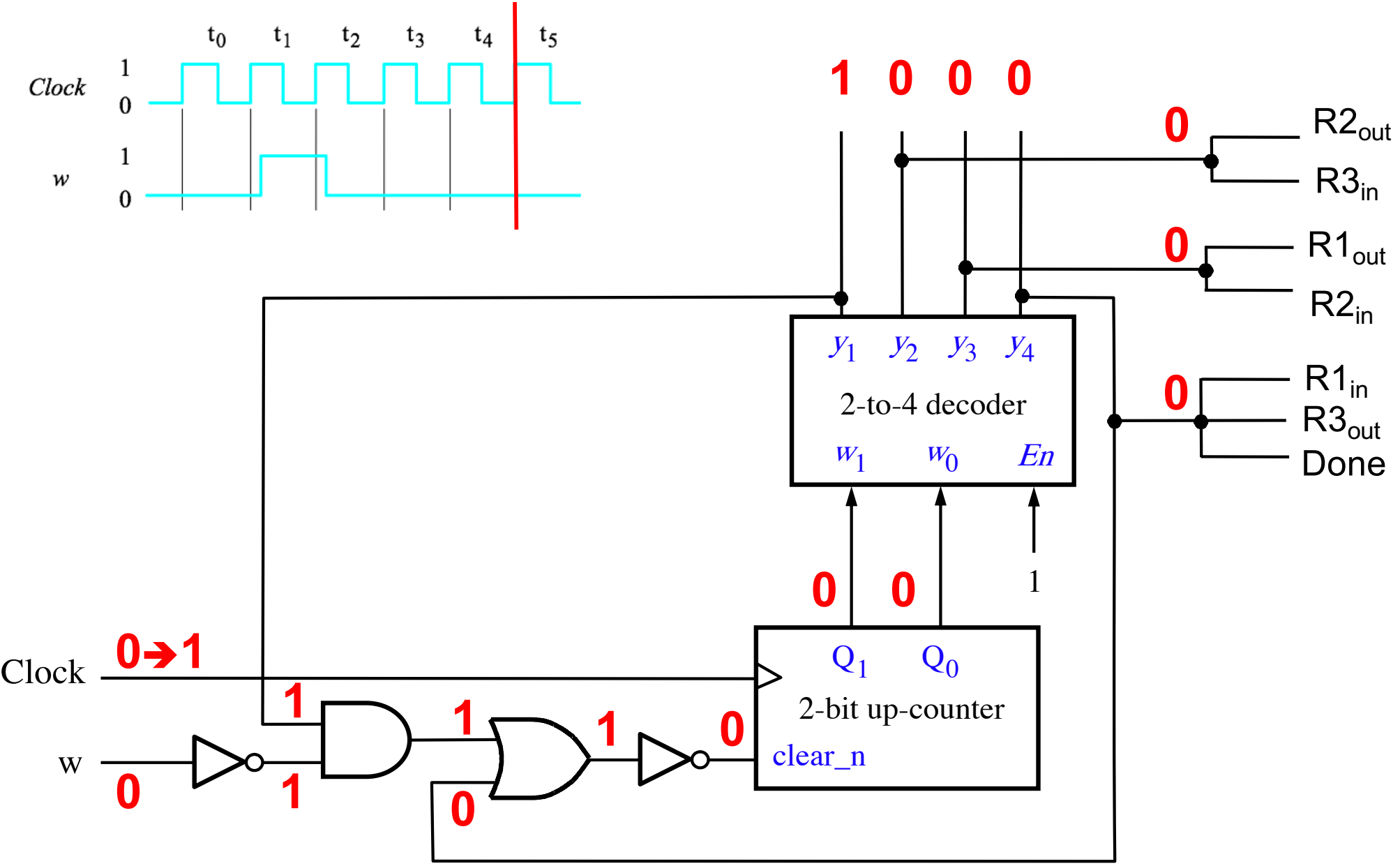

How Does It Work?

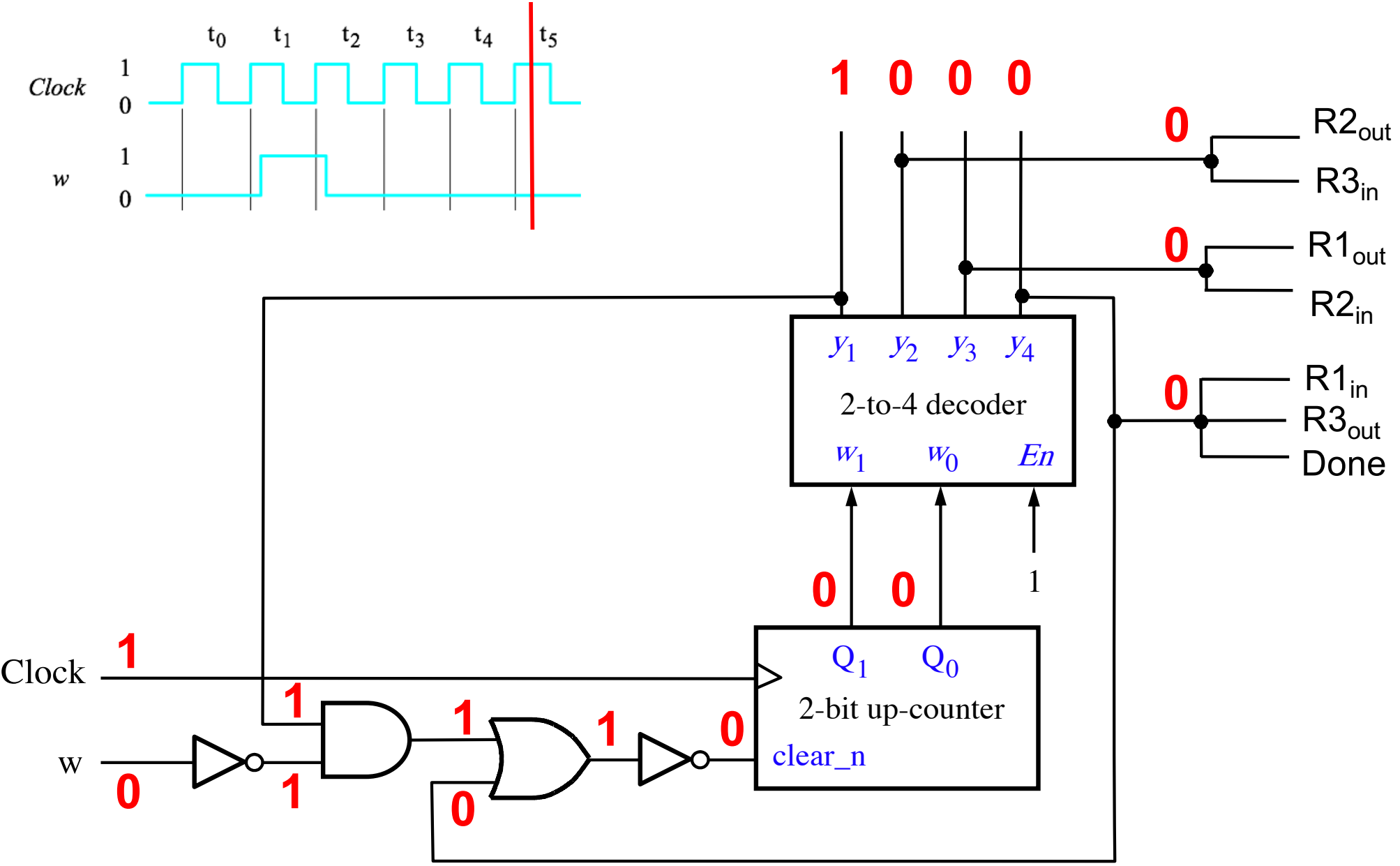

Questions?

THE END