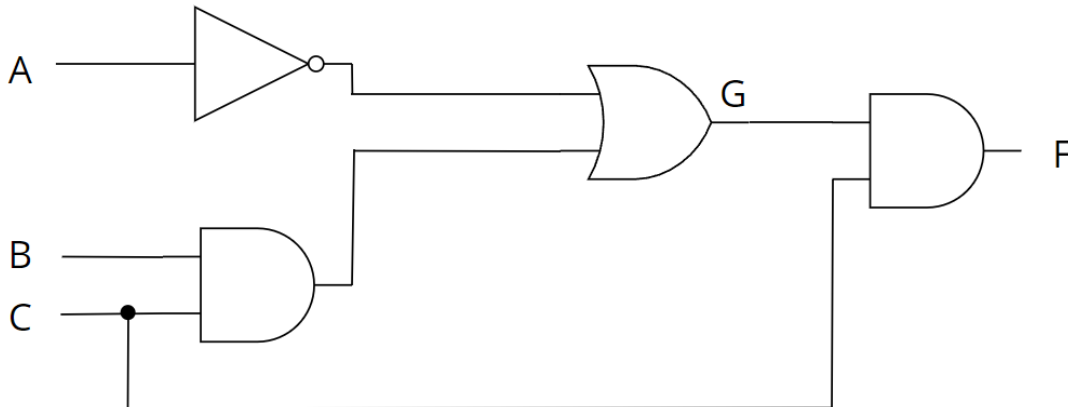
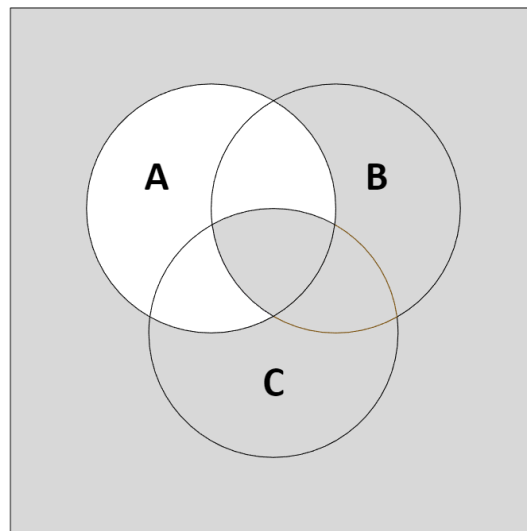


P1. (10 points): For the circuit below, find the Boolean expression for both G and F in terms of A, B and C (do not simplify the expression):



P2. (10 points): Given the following Venn Diagram for F, show the expression.



Boolean algebra,  
AND/OR/NAND/NOR gates  
Assigned Date: Second Week  
Finish by: Sep 6, 2023

P3 (25 points): Given the following truth table, show the following:

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

- A: Venn Diagram.
- B: Canonical Products-of-Sum expressions:
- C: Shorthand Notation for POS
- D: Canonical Sum-of-Products expressions:
- E: Shorthand Notation for SOP

P4. (10 points): Draw the following function using only NAND gates:

$$f = \bar{A}C + A\bar{B} + A$$

P5. (10 points): Draw the following function using only NOR gates:

$$f = (B + \bar{C})(A + C)\bar{B}$$

P6. (10 points): Use Boolean Algebra to verify the following expressions:

1.  $A\bar{B} + \overline{\bar{A}C + \bar{B}C} = A + \bar{C}$
2.  $A\bar{B}C + A\bar{B}\bar{C} + \bar{D}\bar{E}(B + G) + \bar{D} + (\bar{A} + B)D + A\bar{B}CDE + A\bar{B}DEG = 1$

P7. (25 points): Consider the logic function  $f(A, B, C) = (ABC\bar{C} + \overline{ABC} + \bar{A}BC + \overline{BC})$

- A. Draw the logic circuit for the function given above (do not use NAND gates or NOR gates).
- B. Let the cost of a logic circuit be the total number of gates plus the total number of inputs to all gates in the circuit. What is the cost of the circuit in A?
- C. Simplify  $f$  to only one term by using Boolean algebra.
- D. Draw the logic circuit for the simplified version of  $f$  in C.
- E. What is the cost of the circuit in D?