

Name and Std ID: _____ Lab Section: _____

Date: _____

PRELAB:

Q1. Read section 2.2 and write the Verilog code for a 4-to-1 multiplexer.

Q2. Design a 4-bit shifter as described in Section 3.1 of the lab description. Sketch the block diagram for your design showing the multiplexers, the inputs, outputs and the selectors to each multiplexer.

Q3. Refer to Section 3.1 of the lab description and complete the following table before you come to the lab:

X3	X2	X1	X0	Xc1	Xc2	Xc3	S1	S0	F3	F2	F1	F0
1	0	0	1	1	1	0	0	1	0	0	1	1
1	1	1	0	0	0	0	1	1				
1	1	1	0	0	1	1	0	0				
1	1	0	1	0	1	0	1	0				
1	0	1	1	0	1	1	0	1				

TA Initials: _____

LAB:

2.4 Hardware results demonstrate a good circuit. TA Initials: _____

3.1 ModelSim results demonstrate correct code. TA Initials: _____