

CprE 281: Digital Logic

Instructor: Alexander Stoytchev

<http://www.ece.iastate.edu/~alexs/classes/>

Boolean Algebra

*CprE 281: Digital Logic
Iowa State University, Ames, IA
Copyright © Alexander Stoytchev*


Administrative Stuff

- **HW1 is due today @ 10 pm**
(but the deadline pushed to Wednesday @ 10pm)
- **Sample solutions will be posted on Canvas after the deadline.**
- **No late homeworks will be accepted.**


Administrative Stuff

- **HW2 is out**
- **It is due on Wednesday Sep 6 @ 10pm.**
- **Submit it on Canvas before the deadline.**


Did you play with this toy?

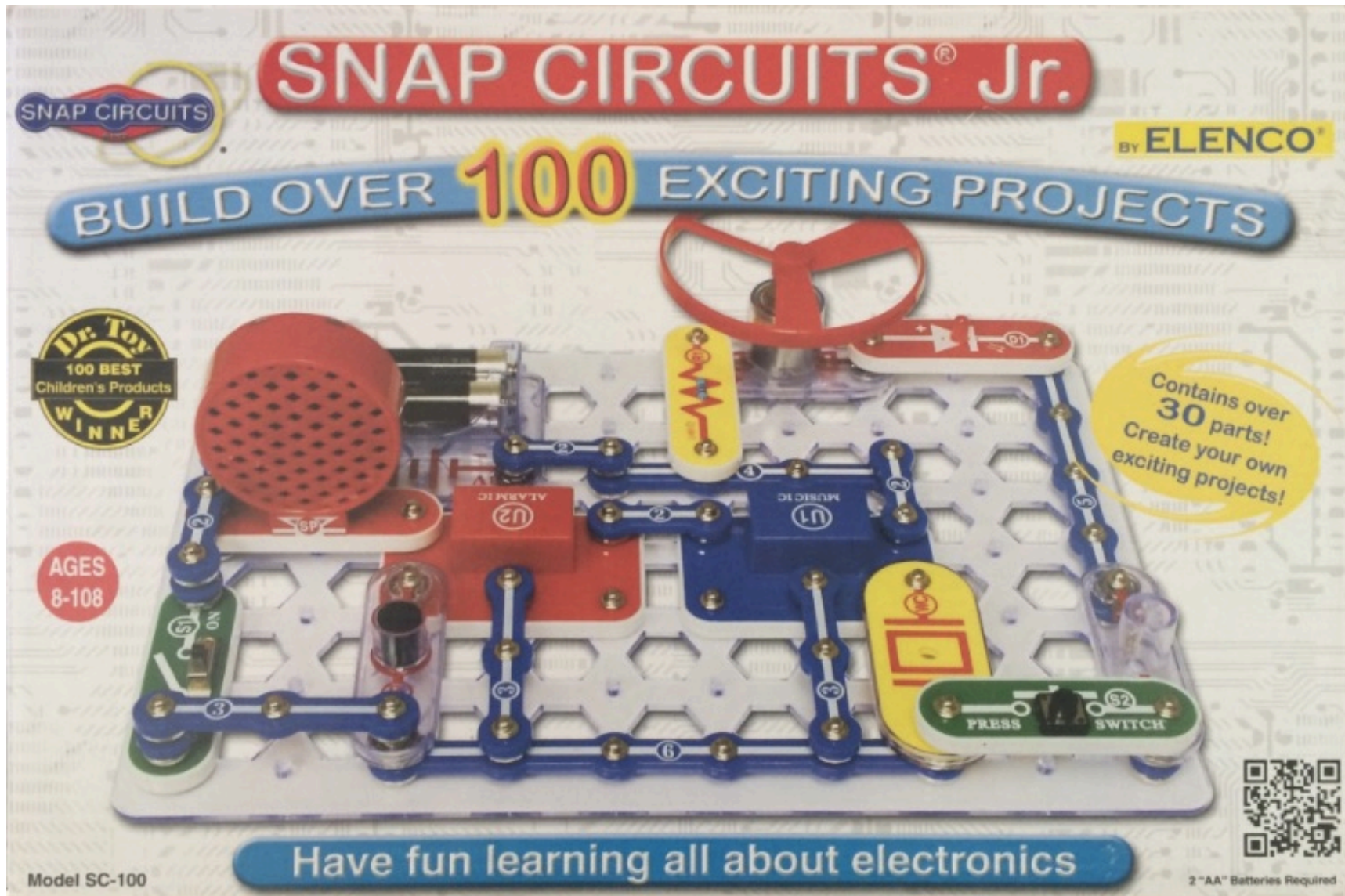

AND Gate

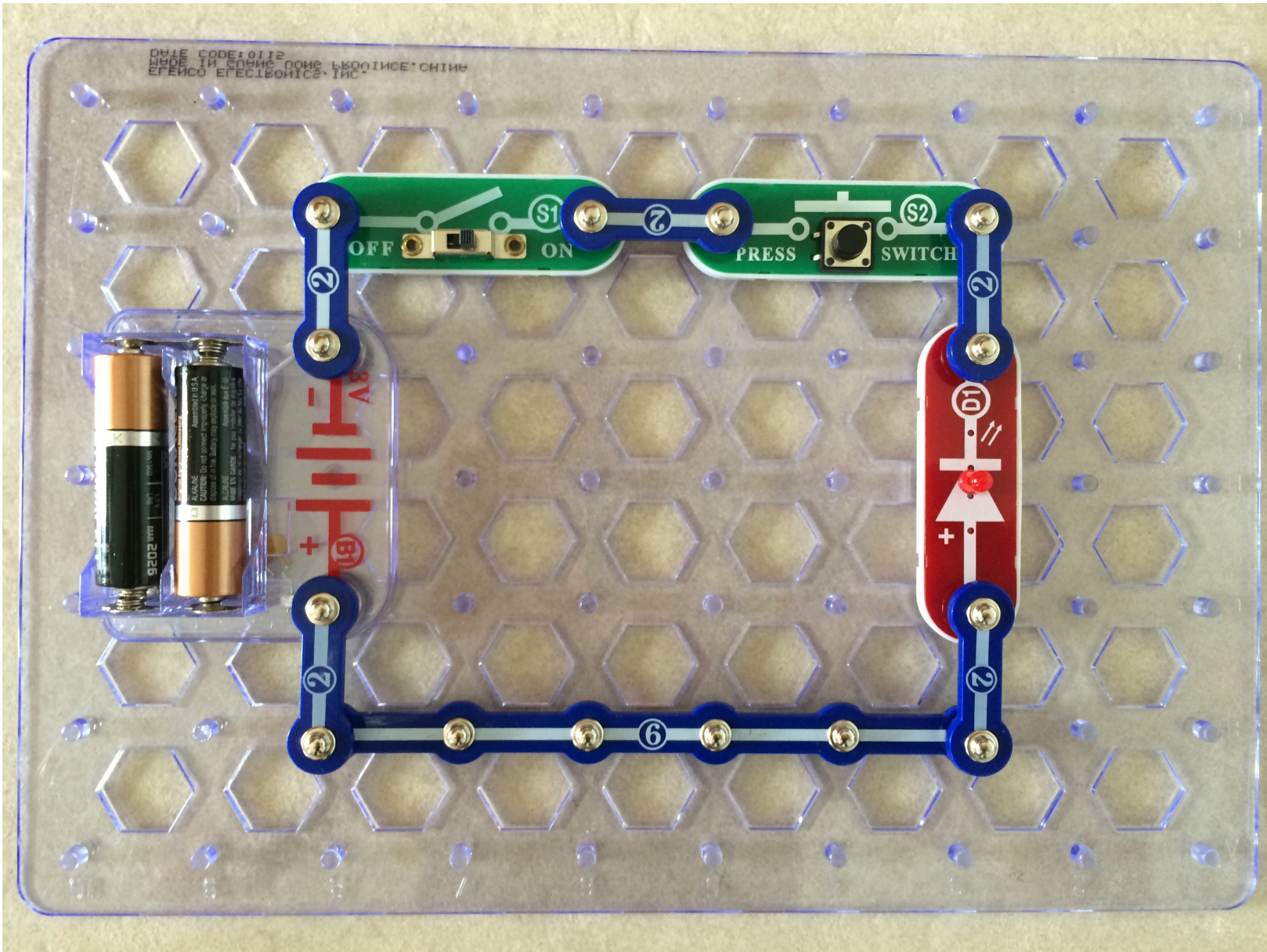


OR Gate

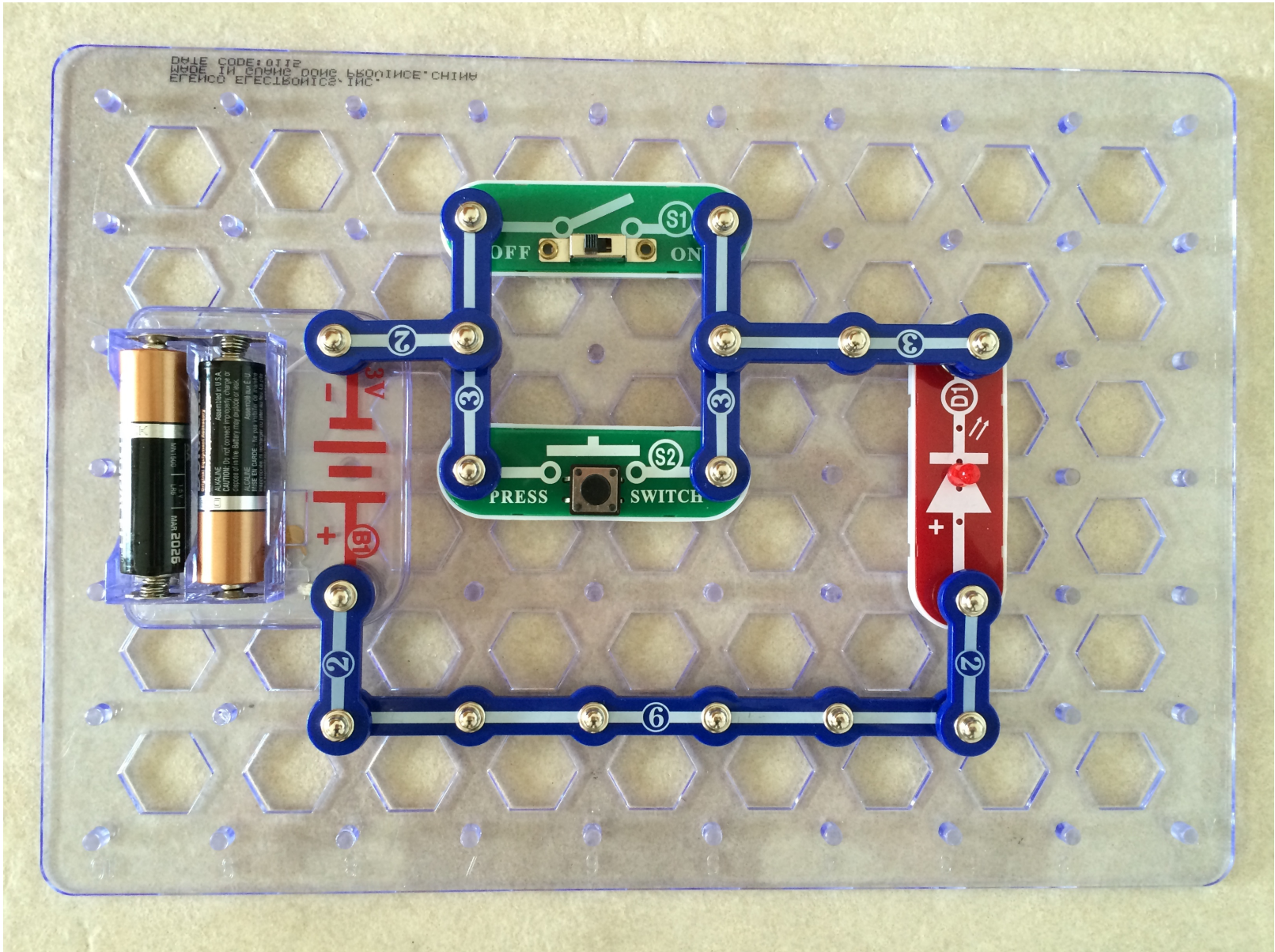


NOT Gate

(the switch is ON but the light is OFF)

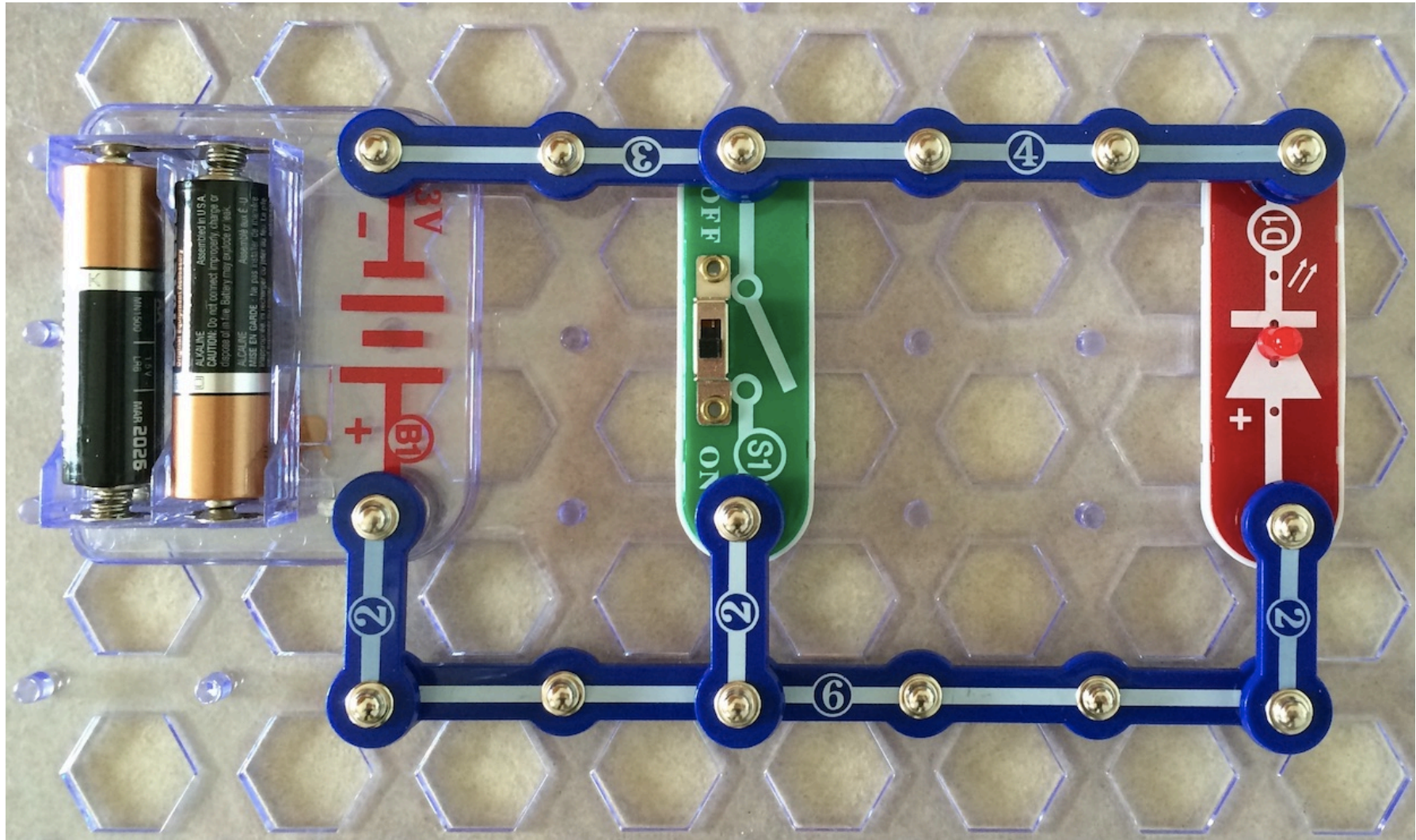


NOT Gate

(the switch is OFF but the light is ON)

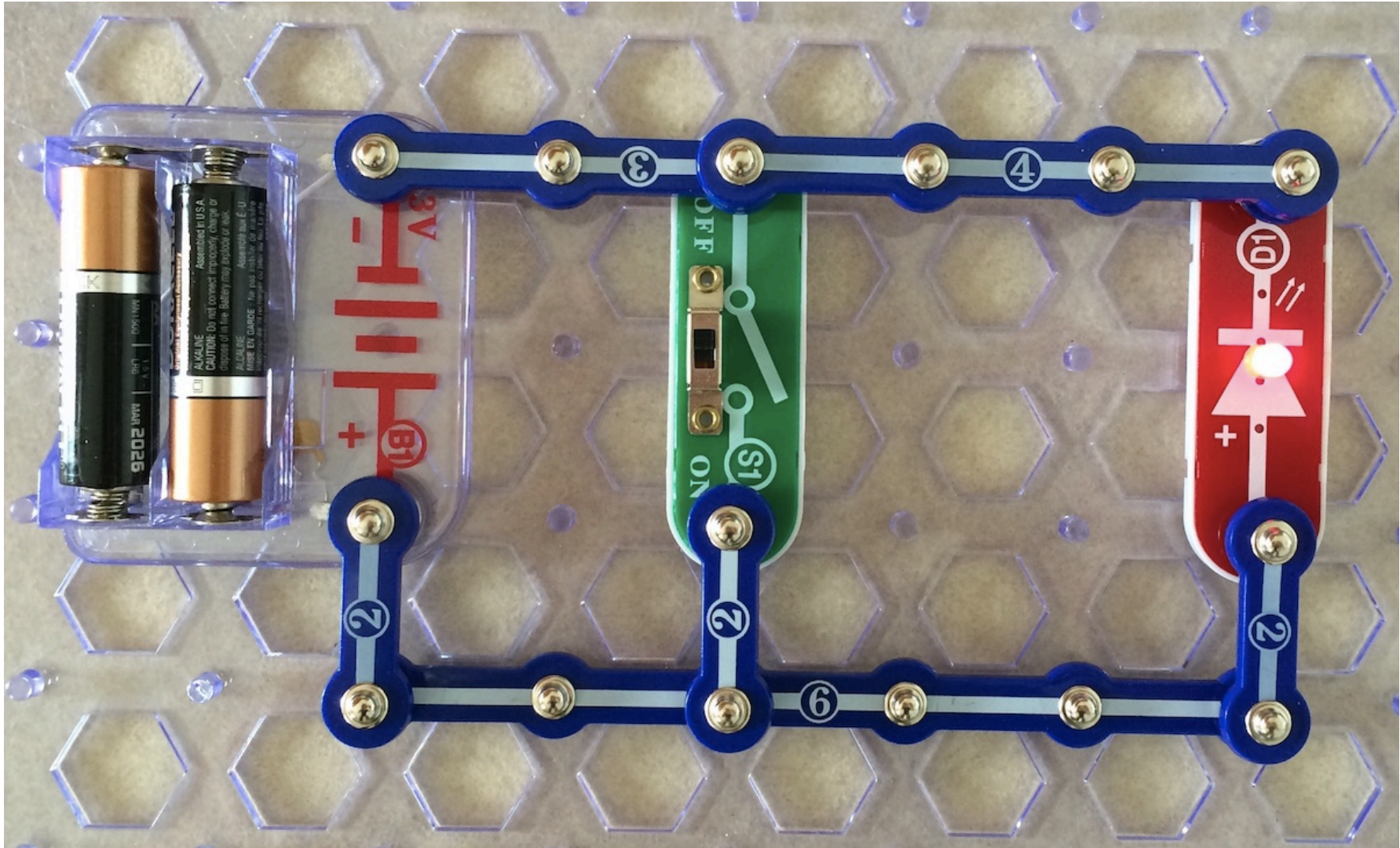

Boolean Algebra

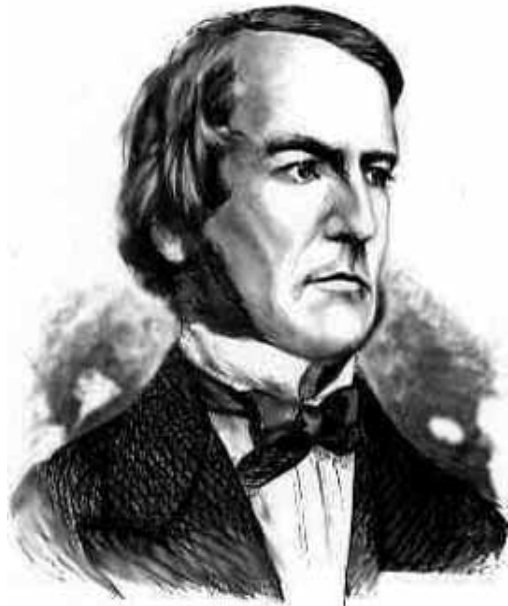

George Boole
1815-1864

- **An algebraic structure consists of**
 - a set of elements $\{0, 1\}$
 - binary operators $\{+, \cdot\}$
 - and a unary operator $\{ ' \}$ or $\{ \bar{\quad} \}$ or $\{ \sim \}$
- **Introduced by George Boole in 1854**
- **An effective means of describing circuits built with switches**
- **A powerful tool that can be used for designing and analyzing logic circuits**

Different Notations for Negation

- All three of these mean “negate x”
 - x'
 - \bar{x}
 - $\sim x$

Axioms of Boolean Algebra

1a. $0 \cdot 0 = 0$

1b. $1 + 1 = 1$

2a. $1 \cdot 1 = 1$

2b. $0 + 0 = 0$

3a. $0 \cdot 1 = 1 \cdot 0 = 0$

3b. $1 + 0 = 0 + 1 = 1$

4a. If $x=0$, then $\bar{x} = 1$

4b. If $x=1$, then $\bar{x} = 0$

Single-Variable Theorems

$$5a. \quad \mathbf{x \cdot 0 = 0}$$

$$5b. \quad \mathbf{x + 1 = 1}$$

$$6a. \quad \mathbf{x \cdot 1 = x}$$

$$6b. \quad \mathbf{x + 0 = x}$$

$$7a. \quad \mathbf{x \cdot x = x}$$

$$7b. \quad \mathbf{x + x = x}$$

$$8a. \quad \mathbf{x \cdot \bar{x} = 0}$$

$$8b. \quad \mathbf{x + \bar{x} = 1}$$

$$9. \quad \mathbf{\overline{\bar{x}} = x}$$

Two- and Three-Variable Properties

10a. $x \cdot y = y \cdot x$ **Commutative**

10b. $x + y = y + x$

11a. $x \cdot (y \cdot z) = (x \cdot y) \cdot z$ **Associative**

11b. $x + (y + z) = (x + y) + z$

12a. $x \cdot (y + z) = x \cdot y + x \cdot z$ **Distributive**

12b. $x + y \cdot z = (x + y) \cdot (x + z)$

13a. $x + x \cdot y = x$ **Absorption**

13b. $x \cdot (x + y) = x$

Two- and Three-Variable Properties

$$14a. \quad x \cdot y + x \cdot \bar{y} = x$$

Combining

$$14b. \quad (x + y) \cdot (x + \bar{y}) = x$$

$$15a. \quad \overline{x \cdot y} = \bar{x} + \bar{y}$$

DeMorgan's
theorem

$$15b. \quad \overline{x + y} = \bar{x} \cdot \bar{y}$$

$$16a. \quad x + \bar{x} \cdot y = x + y$$

$$16b. \quad x \cdot (\bar{x} + y) = x \cdot y$$

$$17a. \quad x \cdot y + y \cdot z + \bar{x} \cdot z = x \cdot y + \bar{x} \cdot z$$

Consensus

$$17b. \quad (x+y) \cdot (y+z) \cdot (\bar{x}+z) = (x+y) \cdot (\bar{x}+z)$$

Now, let's prove all of these

The First Four are Axioms (i.e., they don't require a proof)

1a. $0 \cdot 0 = 0$

1b. $1 + 1 = 1$

2a. $1 \cdot 1 = 1$

2b. $0 + 0 = 0$

3a. $0 \cdot 1 = 1 \cdot 0 = 0$


3b. $1 + 0 = 0 + 1 = 1$

4a. If $x=0$, then $\bar{x} = 1$

4b. If $x=1$, then $\bar{x} = 0$


**But here are some other ways
to think about them**

1a. $0 \cdot 0 = 0$

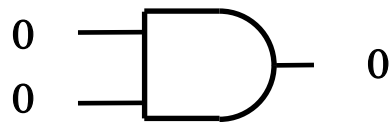


AND gate

1b. $1 + 1 = 1$

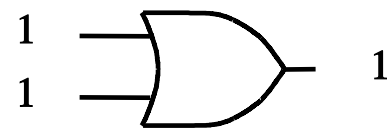

OR gate


1a. $0 \cdot 0 = 0$

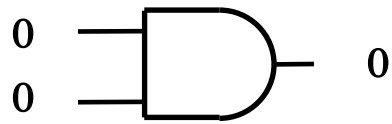

AND gate

x_1	x_2	f
0	0	0
0	1	0
1	0	0
1	1	1


1b. $1 + 1 = 1$

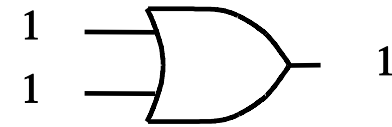

OR gate

x_1	x_2	f
0	0	0
0	1	1
1	0	1
1	1	1


1a. $0 \cdot 0 = 0$

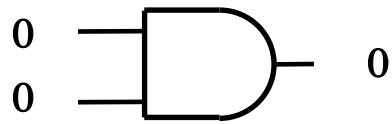

AND gate

x_1	x_2	f
0	0	0
0	1	0
1	0	0
1	1	1


1b. $1 + 1 = 1$

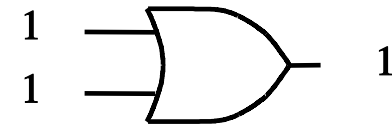

OR gate


x_1	x_2	f
0	0	0
0	1	1
1	0	1
1	1	1

2a. **$1 \cdot 1 = 1$**

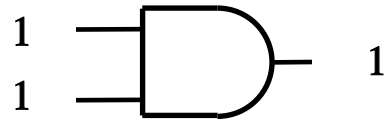

AND gate


2b. **$0 + 0 = 0$**

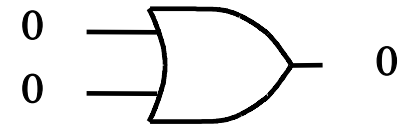


OR gate

2a. $1 \cdot 1 = 1$

2b. $0 + 0 = 0$

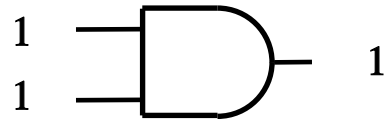

AND gate


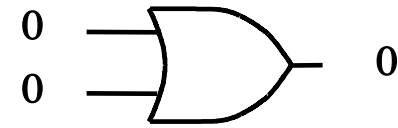


OR gate



x ₁	x ₂	f
0	0	0
0	1	0
1	0	0
1	1	1

x ₁	x ₂	f
0	0	0
0	1	1
1	0	1
1	1	1



3a. $0 \cdot 1 = 1 \cdot 0 = 0$

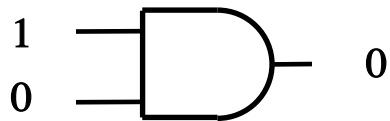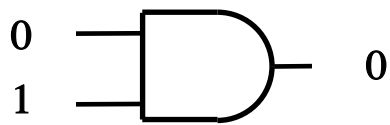

3b. $1 + 0 = 0 + 1 = 1$

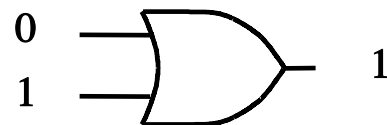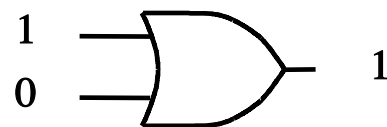



3a. $0 \cdot 1 = 1 \cdot 0 = 0$

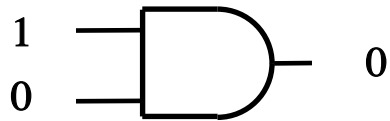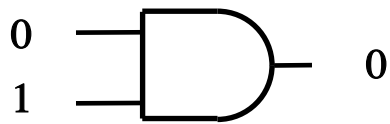

AND gate

x_1	x_2	f
0	0	0
0	1	0
1	0	0
1	1	1



3b. $1 + 0 = 0 + 1 = 1$

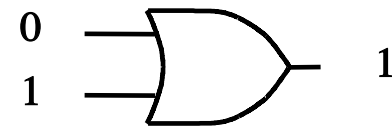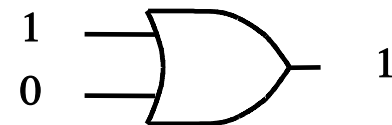

OR gate

x_1	x_2	f
0	0	0
0	1	1
1	0	1
1	1	1



3a. $0 \cdot 1 = 1 \cdot 0 = 0$

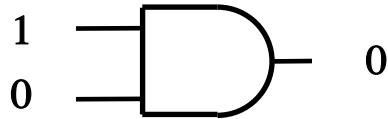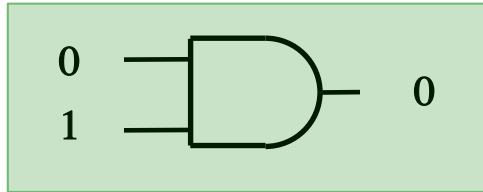

AND gate

x_1	x_2	f
0	0	0
0	1	0
1	0	0
1	1	1



3b. $1 + 0 = 0 + 1 = 1$

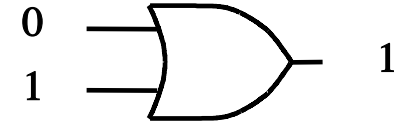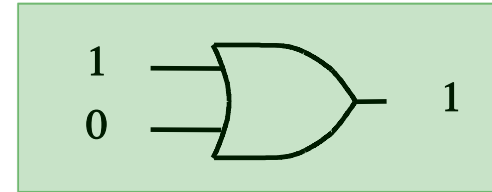

OR gate

x_1	x_2	f
0	0	0
0	1	1
1	0	1
1	1	1



3a. $0 \cdot 1 = 1 \cdot 0 = 0$

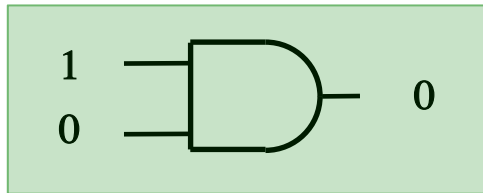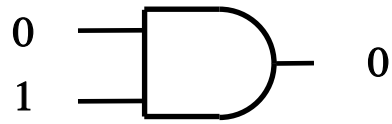

AND gate

x_1	x_2	f
0	0	0
0	1	0
1	0	0
1	1	1


3b. $1 + 0 = 0 + 1 = 1$

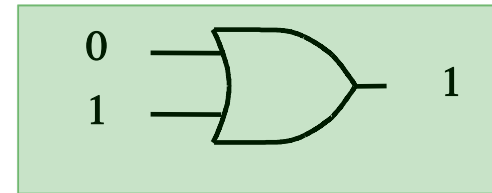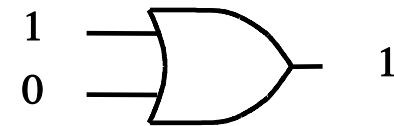


OR gate

x_1	x_2	f
0	0	0
0	1	1
1	0	1
1	1	1

4a. If $x=0$, then $\bar{x} = 1$


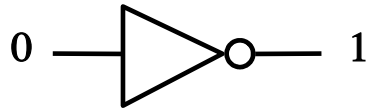


4b. If $x=1$, then $\bar{x} = 0$

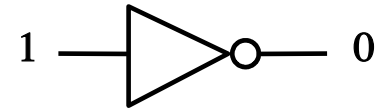

4a. If $x=0$, then $\bar{x} = 1$

4b. If $x=1$, then $\bar{x} = 0$

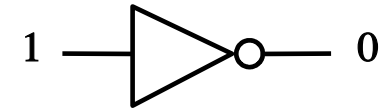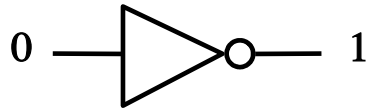

NOT gate

x	\bar{x}
0	1
1	0

NOT gate

x	\bar{x}
0	1
1	0

Single-Variable Theorems

$$5a. \quad \mathbf{x \cdot 0 = 0}$$

$$5b. \quad \mathbf{x + 1 = 1}$$

$$6a. \quad \mathbf{x \cdot 1 = x}$$

$$6b. \quad \mathbf{x + 0 = x}$$

$$7a. \quad \mathbf{x \cdot x = x}$$

$$7b. \quad \mathbf{x + x = x}$$

$$8a. \quad \mathbf{x \cdot \bar{x} = 0}$$

$$8b. \quad \mathbf{x + \bar{x} = 1}$$

$$9. \quad \mathbf{\overline{\bar{x}} = x}$$

$$5a. \quad \mathbf{x} \cdot \mathbf{0} = \mathbf{0}$$

$$5a. \quad x \cdot 0 = 0$$

The Boolean variable x can have only two possible values: 0 or 1. Let's look at each case separately.

$$5a. \quad x \cdot 0 = 0$$

The Boolean variable x can have only two possible values: 0 or 1. Let's look at each case separately.

i) If $x = 0$, then we have

$$0 \cdot 0 = 0$$

// axiom 1a

$$5a. \quad x \cdot 0 = 0$$

The Boolean variable x can have only two possible values: 0 or 1. Let's look at each case separately.

i) If $x = 0$, then we have

$$0 \cdot 0 = 0 \quad // \text{ axiom 1a}$$

ii) If $x = 1$, then we have

$$1 \cdot 0 = 0 \quad // \text{ axiom 3a}$$

5b. **$x + 1 = 1$**

$$\mathbf{5b. \quad x + 1 = 1}$$

The Boolean variable x can have only two possible values: 0 or 1. Let's look at each case separately.

i) If $x = 0$, then we have

$$\mathbf{0 + 1 = 1}$$

// axiom 3b

$$\mathbf{5b. \quad x + 1 = 1}$$

The Boolean variable x can have only two possible values: 0 or 1. Let's look at each case separately.

i) If $x = 0$, then we have

$$0 + 1 = 1 \quad // \text{ axiom 3b}$$

ii) If $x = 1$, then we have

$$1 + 1 = 1 \quad // \text{ axiom 1b}$$

$$\mathbf{6a. \quad x \cdot 1 = x}$$

The Boolean variable x can have only two possible values: 0 or 1. Let's look at each case separately.

i) If $x = 0$, then we have

$$0 \cdot 1 = 0 \quad // \text{ axiom 3a}$$

ii) If $x = 1$, then we have

$$1 \cdot 1 = 1 \quad // \text{ axiom 2a}$$

$$6a. \quad \boxed{x} \cdot 1 = \boxed{x}$$

The Boolean variable x can have only two possible values: 0 or 1. Let's look at each case separately.

i) If $x = 0$, then we have

$$\boxed{0} \cdot 1 = \boxed{0}$$

// axiom 3a

ii) If $x = 1$, then we have

$$\boxed{1} \cdot 1 = \boxed{1}$$

// axiom 2a

$$\mathbf{6b. \quad x + 0 = x}$$

The Boolean variable x can have only two possible values: 0 or 1. Let's look at each case separately.

i) If $x = 0$, then we have

$$0 + 0 = 0 \quad // \text{ axiom 2b}$$

ii) If $x = 1$, then we have

$$1 + 0 = 1 \quad // \text{ axiom 3b}$$

$$6b. \quad \boxed{x} + 0 = \boxed{x}$$

The Boolean variable x can have only two possible values: 0 or 1. Let's look at each case separately.

i) If $x = 0$, then we have

$$\boxed{0} + 0 = \boxed{0} \quad // \text{ axiom 2b}$$

ii) If $x = 1$, then we have

$$\boxed{1} + 0 = \boxed{1} \quad // \text{ axiom 3b}$$

$$\mathbf{7a. \quad x \cdot x = x}$$

i) If $x = 0$, then we have

$$0 \cdot 0 = 0$$

// axiom 1a

ii) If $x = 1$, then we have

$$1 \cdot 1 = 1$$

// axiom 2a

$$7a. \quad \boxed{x} \cdot \boxed{x} = \boxed{x}$$

i) If $x = 0$, then we have

$$\boxed{0} \cdot \boxed{0} = \boxed{0}$$

// axiom 1a

ii) If $x = 1$, then we have

$$\boxed{1} \cdot \boxed{1} = \boxed{1}$$

// axiom 2a

$$7b. \quad \mathbf{x + x = x}$$

i) If $x = 0$, then we have

$$0 + 0 = 0 \quad // \text{ axiom 2b}$$

ii) If $x = 1$, then we have

$$1 + 1 = 1 \quad // \text{ axiom 1b}$$

$$7b. \quad \boxed{x} + \boxed{x} = \boxed{x}$$

i) If $x = 0$, then we have

$$\boxed{0} + \boxed{0} = \boxed{0}$$

// axiom 2b

ii) If $x = 1$, then we have

$$\boxed{1} + \boxed{1} = \boxed{1}$$

// axiom 1b

$$8a. \quad \mathbf{x} \cdot \overline{\mathbf{x}} = \mathbf{0}$$

i) If $\mathbf{x} = \mathbf{0}$, then we have

$$\mathbf{0} \cdot \mathbf{1} = \mathbf{0} \quad // \text{ axiom 3a}$$

ii) If $\mathbf{x} = \mathbf{1}$, then we have

$$\mathbf{1} \cdot \mathbf{0} = \mathbf{0} \quad // \text{ axiom 3a}$$

$$8a. \quad x \cdot \overline{x} = 0$$

i) If $x = 0$, then we have

$$0 \cdot 1 = 0$$

// axiom 3a

ii) If $x = 1$, then we have

$$1 \cdot 0 = 0$$

// axiom 3a

$$\mathbf{8b.} \quad \mathbf{x + \bar{x} = 1}$$

i) If $x = 0$, then we have

$$\mathbf{0 + 1 = 1}$$

// axiom 3b

ii) If $x = 1$, then we have

$$\mathbf{1 + 0 = 1}$$

// axiom 3b

$$8b. \quad x + \bar{x} = 1$$

i) If $x = 0$, then we have

$$0 + 1 = 1$$

// axiom 3b

ii) If $x = 1$, then we have

$$1 + 0 = 1$$

// axiom 3b

$$9. \quad \overline{\overline{x}} = x$$

i) If $x = 0$, then we have

$$\overline{x} = 1 \quad // \text{ axiom 4a}$$

let $y = \overline{x} = 1$, then we have

$$\overline{y} = 0 \quad // \text{ axiom 4b}$$

Therefore,

$$\overline{\overline{x}} = x \quad (\text{when } x = 0)$$

$$9. \quad \overline{\overline{x}} = x$$

ii) If $x = 1$, then we have

$$\overline{x} = 0 \quad // \text{ axiom 4b}$$



let $y = \overline{x} = 0$, then we have

$$\overline{y} = 1 \quad // \text{ axiom 4a}$$



Therefore,

$$\overline{\overline{x}} = x \quad (\text{when } x = 1)$$



10a. $\mathbf{x \cdot y = y \cdot x}$

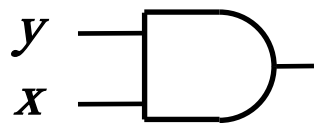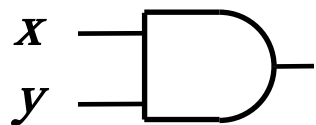

10b. $\mathbf{x + y = y + x}$

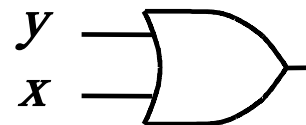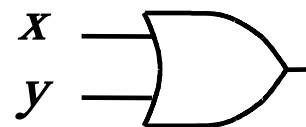



10a. $x \cdot y = y \cdot x$

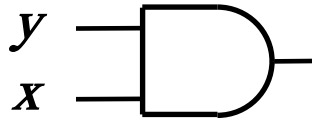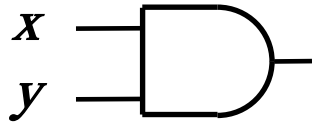

AND gate

x	y	f
0	0	0
0	1	0
1	0	0
1	1	1

10b. $x + y = y + x$

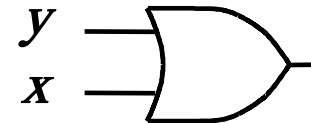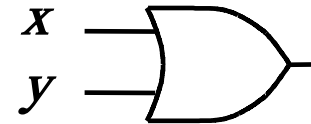

OR gate

x	y	f
0	0	0
0	1	1
1	0	1
1	1	1

The order of the inputs does not matter.

$$11a. \quad \mathbf{x} \cdot (\mathbf{y} \cdot \mathbf{z}) = (\mathbf{x} \cdot \mathbf{y}) \cdot \mathbf{z}$$

x	y	z	x	y · z	x · (y · z)
0	0	0			
0	0	1			
0	1	0			
0	1	1			
1	0	0			
1	0	1			
1	1	0			
1	1	1			

Truth table for the left-hand side

$$11a. \quad \mathbf{x} \cdot (\mathbf{y} \cdot \mathbf{z}) = (\mathbf{x} \cdot \mathbf{y}) \cdot \mathbf{z}$$

x	y	z	x	y · z	x·(y·z)
0	0	0	0	0	
0	0	1	0	0	
0	1	0	0	0	
0	1	1	0	1	
1	0	0	1	0	
1	0	1	1	0	
1	1	0	1	0	
1	1	1	1	1	

Truth table for the left-hand side

$$11a. \quad \mathbf{x} \cdot (\mathbf{y} \cdot \mathbf{z}) = (\mathbf{x} \cdot \mathbf{y}) \cdot \mathbf{z}$$

x	y	z	x	y · z	x·(y·z)
0	0	0	0	0	0
0	0	1	0	0	0
0	1	0	0	0	0
0	1	1	0	1	0
1	0	0	1	0	0
1	0	1	1	0	0
1	1	0	1	0	0
1	1	1	1	1	1

Truth table for the left-hand side

$$11a. \quad \mathbf{x} \cdot (\mathbf{y} \cdot \mathbf{z}) = (\mathbf{x} \cdot \mathbf{y}) \cdot \mathbf{z}$$

x	y	z	$x \cdot y$	z	$(x \cdot y) \cdot z$
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	0
0	1	1	0	1	0
1	0	0	0	0	0
1	0	1	0	1	0
1	1	0	1	0	0
1	1	1	1	1	1

Truth table for the right-hand side

11a. **$x \cdot (y \cdot z) = (x \cdot y) \cdot z$**

$x \cdot (y \cdot z)$
0
0
0
0
0
0
0
1

$(x \cdot y) \cdot z$
0
0
0
0
0
0
0
1

These two are identical, which concludes the proof.

11b. **$x + (y + z) = (x + y) + z$**

x	y	z	x	y + z	x+(y+z)
0	0	0			
0	0	1			
0	1	0			
0	1	1			
1	0	0			
1	0	1			
1	1	0			
1	1	1			

Truth table for the left-hand side

11b. $x + (y + z) = (x + y) + z$

x	y	z	x	y + z	x+(y+z)
0	0	0	0	0	
0	0	1	0	1	
0	1	0	0	1	
0	1	1	0	1	
1	0	0	1	0	
1	0	1	1	1	
1	1	0	1	1	
1	1	1	1	1	

Truth table for the left-hand side

11b. **$x + (y + z) = (x + y) + z$**

x	y	z	x	y + z	x+(y+z)
0	0	0	0	0	0
0	0	1	0	1	1
0	1	0	0	1	1
0	1	1	0	1	1
1	0	0	1	0	1
1	0	1	1	1	1
1	1	0	1	1	1
1	1	1	1	1	1

Truth table for the left-hand side

11b. **$x + (y + z) = (x + y) + z$**

x	y	z	x + y	z	(x+y)+z
0	0	0	0	0	0
0	0	1	0	1	1
0	1	0	1	0	1
0	1	1	1	1	1
1	0	0	1	0	1
1	0	1	1	1	1
1	1	0	1	0	1
1	1	1	1	1	1

Truth table for the right-hand side


11b. $\mathbf{x + (y + z) = (x + y) + z}$

$\mathbf{x+(y+z)}$
0
1
1
1
1
1
1
1
1

$\mathbf{(x+y)+z}$
0
1
1
1
1
1
1
1
1


These two are identical, which concludes the proof.

The Venn Diagram Representation

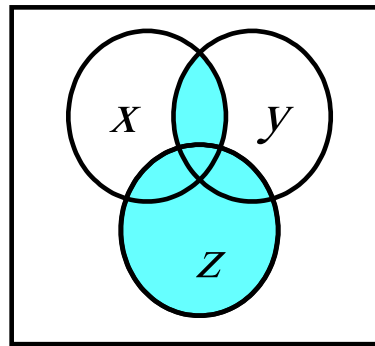

$$xy + z$$


Venn Diagram Basics

 


(a) Constant 1



(b) Constant 0

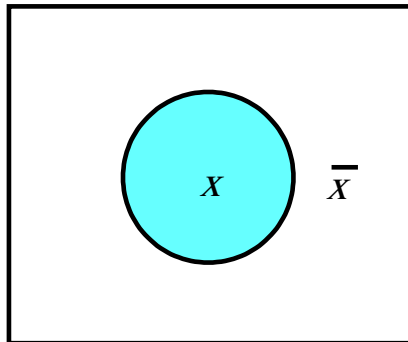


(c) Variable x

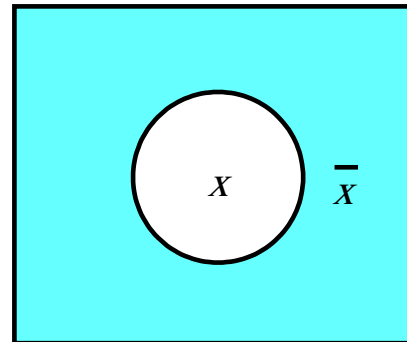


(d) \bar{x}


Venn Diagram Basics

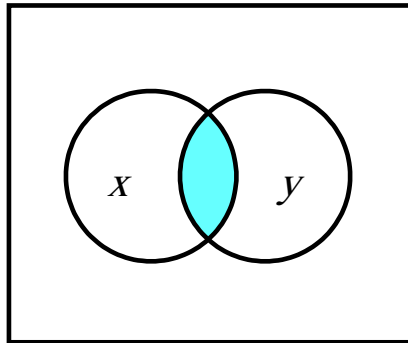


(e) $x y$

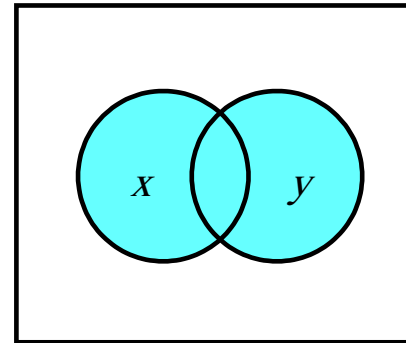

(f) $x + y$

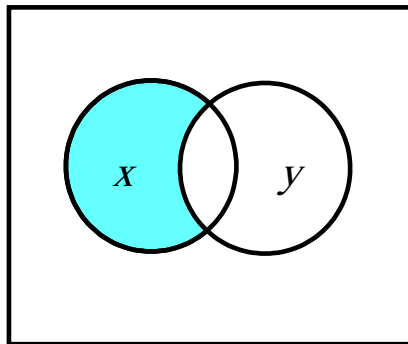

(g) $x \bar{y}$

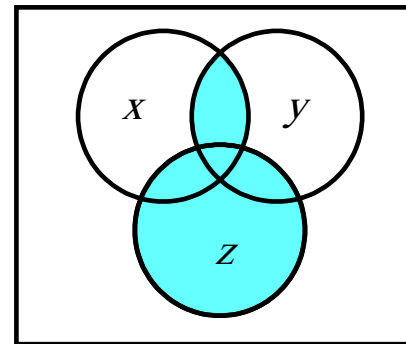

(h) $x y + z$


Let's Prove the Distributive Properties

$$12a. \quad \mathbf{x \cdot (y + z) = x \cdot y + x \cdot z}$$


$$12b. \quad \mathbf{x + y \cdot z = (x + y) \cdot (x + z)}$$

12a.

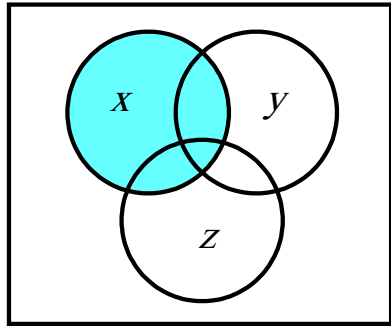
$$\mathbf{x \cdot (y + z) = x \cdot y + x \cdot z}$$




(a) x

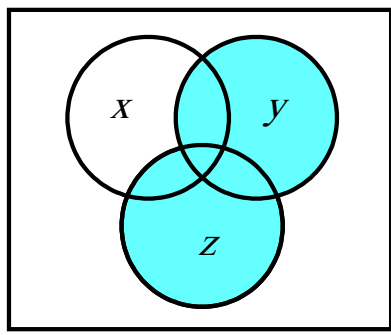


(b) $y + z$

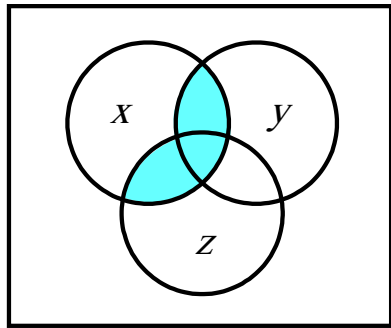


(c) $x \cdot (y + z)$

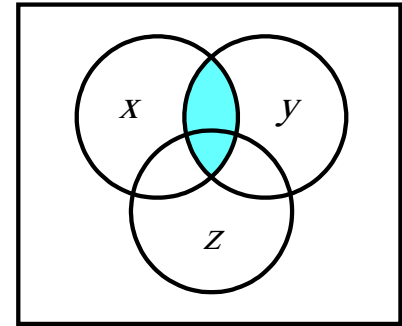

(d) $x \cdot y$

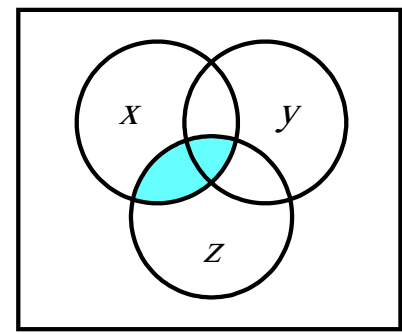


(e) $x \cdot z$

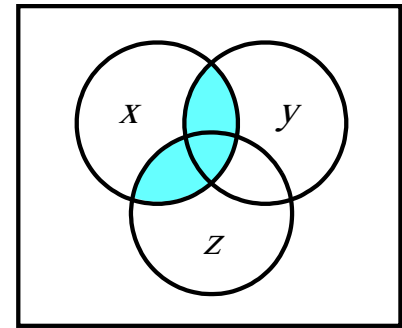


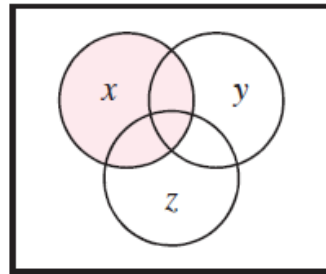(f) $x \cdot y + x \cdot z$


12b. **$x + y \cdot z = (x + y) \cdot (x + z)$**




(a) x

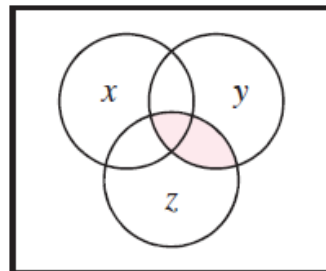


(b) $y \cdot z$

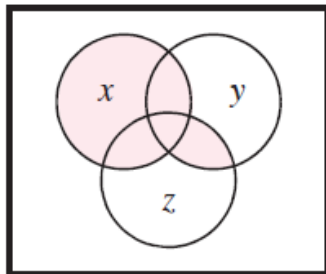


(c) $x + y \cdot z$

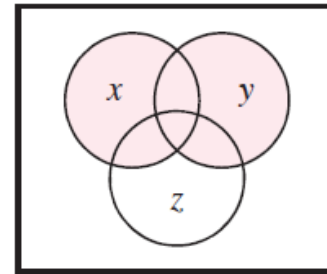

(d) $x + y$

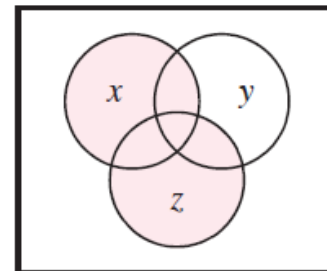

(e) $x + z$

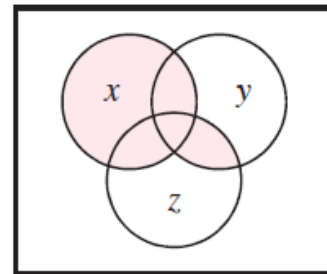

(f) $(x + y) \cdot (x + z)$

Try to prove these ones at home

$$13a. \quad \mathbf{x + x \cdot y = x}$$

$$13b. \quad \mathbf{x \cdot (x + y) = x}$$

$$14a. \quad \mathbf{x \cdot y + x \cdot \bar{y} = x}$$

$$14b. \quad \mathbf{(x + y) \cdot (x + \bar{y}) = x}$$

DeMorgan's Theorem

$$15a. \quad \overline{x \cdot y} = \bar{x} + \bar{y}$$

$$15b. \quad \overline{x + y} = \bar{x} \cdot \bar{y}$$


Proof of DeMorgan's theorem

$$15a. \quad \overline{x \cdot y} = \bar{x} + \bar{y}$$

Proof of DeMorgan's theorem

15a. $\overline{x \cdot y} = \bar{x} + \bar{y}$

x	y	$x \cdot y$	$\overline{x \cdot y}$	\bar{x}	\bar{y}	$\bar{x} + \bar{y}$
0	0					
0	1					
1	0					
1	1					



LHS RHS

Proof of DeMorgan's theorem

15a. $\overline{x \cdot y} = \bar{x} + \bar{y}$

x	y	$x \cdot y$	$\overline{x \cdot y}$	\bar{x}	\bar{y}	$\bar{x} + \bar{y}$
0	0	0	1			
0	1	0	1			
1	0	0	1			
1	1	1	0			

$\underbrace{\hspace{15em}}_{\text{LHS}} \qquad \underbrace{\hspace{15em}}_{\text{RHS}}$

Proof of DeMorgan's theorem

$$15a. \quad \overline{x \cdot y} = \bar{x} + \bar{y}$$

x	y	$x \cdot y$	$\overline{x \cdot y}$	\bar{x}	\bar{y}	$\bar{x} + \bar{y}$
0	0	0	1	1	1	
0	1	0	1	1	0	
1	0	0	1	0	1	
1	1	1	0	0	0	

$\underbrace{\hspace{15em}}_{\text{LHS}} \qquad \underbrace{\hspace{15em}}_{\text{RHS}}$

Proof of DeMorgan's theorem

$$15a. \quad \overline{x \cdot y} = \bar{x} + \bar{y}$$

x	y	$x \cdot y$	$\overline{x \cdot y}$	\bar{x}	\bar{y}	$\bar{x} + \bar{y}$
0	0	0	1	1	1	
0	1	0	1	1	0	
1	0	0	1	0	1	
1	1	1	0	0	0	

$\underbrace{\hspace{15em}}_{\text{LHS}} \qquad \underbrace{\hspace{15em}}_{\text{RHS}}$

Proof of DeMorgan's theorem

$$15a. \quad \overline{x \cdot y} = \bar{x} + \bar{y}$$

x	y	$x \cdot y$	$\overline{x \cdot y}$	\bar{x}	\bar{y}	$\bar{x} + \bar{y}$
0	0	0	1	1	1	1
0	1	0	1	1	0	1
1	0	0	1	0	1	1
1	1	1	0	0	0	0

$\underbrace{\hspace{15em}}_{\text{LHS}} \qquad \underbrace{\hspace{15em}}_{\text{RHS}}$

Proof of DeMorgan's theorem

$$15a. \quad \overline{x \cdot y} = \bar{x} + \bar{y}$$


x	y	$x \cdot y$	$\overline{x \cdot y}$	\bar{x}	\bar{y}	$\bar{x} + \bar{y}$
0	0	0	1	1	1	1
0	1	0	1	1	0	1
1	0	0	1	0	1	1
1	1	1	0	0	0	0

$\underbrace{\hspace{10em}}_{\text{LHS}} \qquad \underbrace{\hspace{10em}}_{\text{RHS}}$


These two columns are equal. Therefore, the theorem is true.

Alternative proof using Venn Diagrams

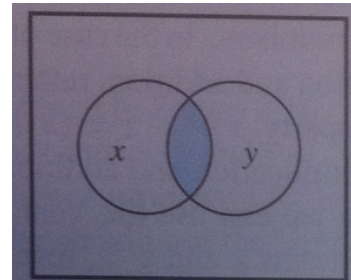
$$15a. \quad \overline{x \cdot y} = \bar{x} + \bar{y}$$




(a) $x \cdot y$

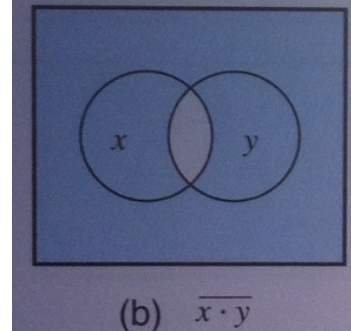


(b) $\overline{x \cdot y}$

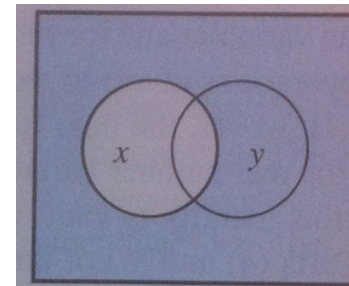

(c) \bar{x}

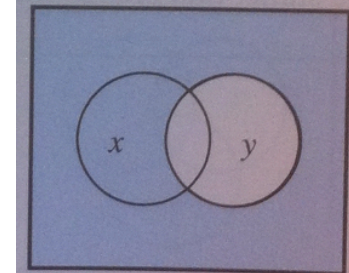

(d) \bar{y}

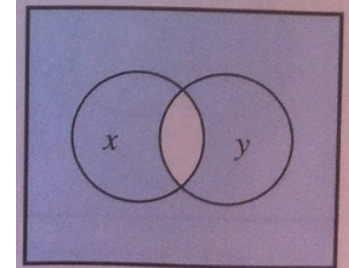

(e) $\bar{x} + \bar{y}$

Let's prove the other DeMorgan's theorem

$$15b. \quad \overline{x + y} = \bar{x} \cdot \bar{y}$$

Let's prove the other DeMorgan's theorem

$$15b. \quad \overline{x + y} = \bar{x} \cdot \bar{y}$$

These two columns are equal, so the theorem is true.

x	y	$x + y$	$\overline{x + y}$	\bar{x}	\bar{y}	$\bar{x} \cdot \bar{y}$
0	0	0	1	1	1	1
0	1	1	0	1	0	0
1	0	1	0	0	1	0
1	1	1	0	0	0	0

$\underbrace{\hspace{15em}}_{\text{LHS}} \qquad \underbrace{\hspace{15em}}_{\text{RHS}}$

DeMorgan's Theorem

Generalizes to more than 2 variables

$$\overline{\mathbf{x} \cdot \mathbf{y} \cdot \mathbf{z}} = \overline{\mathbf{x}} + \overline{\mathbf{y}} + \overline{\mathbf{z}}$$

$$\overline{\mathbf{x} + \mathbf{y} + \mathbf{z}} = \overline{\mathbf{x}} \cdot \overline{\mathbf{y}} \cdot \overline{\mathbf{z}}$$

DeMorgan's Theorem

Generalizes to more than 2 variables

$$\overline{a \cdot b \cdot c \cdot d} = \overline{a} + \overline{b} + \overline{c} + \overline{d}$$

$$\overline{a + b + c + d} = \overline{a} \cdot \overline{b} \cdot \overline{c} \cdot \overline{d}$$

Try to prove these ones at home

16a. $x + \bar{x} \cdot y = x + y$

16b. $x \cdot (\bar{x} + y) = x \cdot y$

17a. $x \cdot y + y \cdot z + \bar{x} \cdot z = x \cdot y + \bar{x} \cdot z$


17b. $(x+y) \cdot (y+z) \cdot (\bar{x}+z) = (x+y) \cdot (\bar{x}+z)$

Venn Diagram Example


Proof of Property 17a

$$17a. \quad x \cdot y + y \cdot z + \bar{x} \cdot z = x \cdot y + \bar{x} \cdot z$$


Left-Hand Side

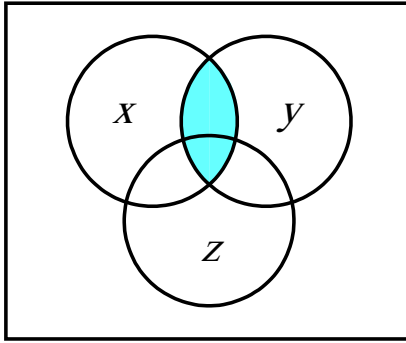


$$x y$$

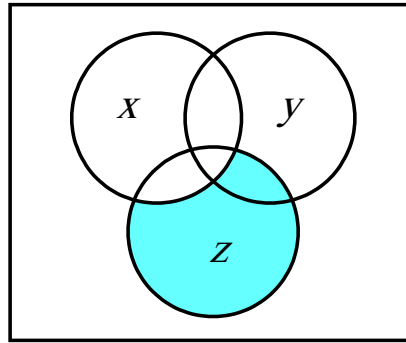

$$\bar{x} z$$

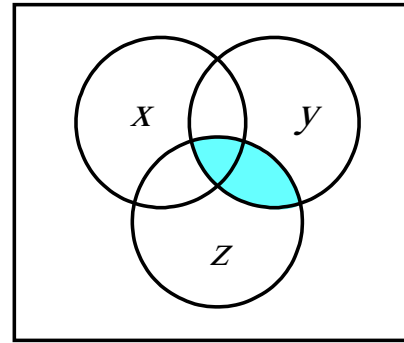


$$y z$$

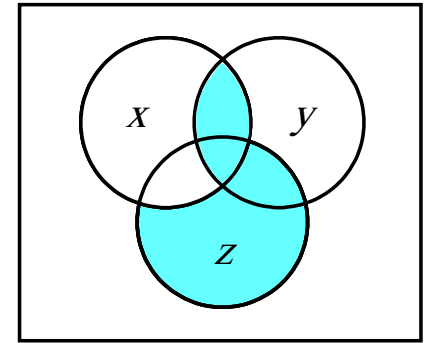


$$x y + \bar{x} z + y z$$


Left-Hand Side

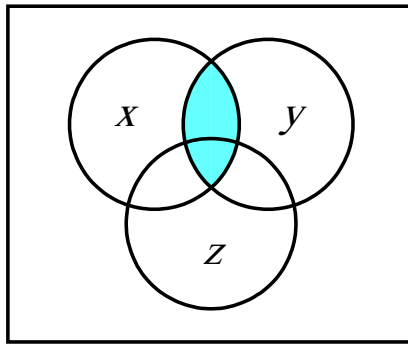


$$x y$$

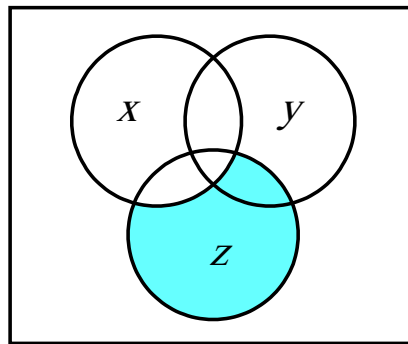

$$\bar{x} z$$

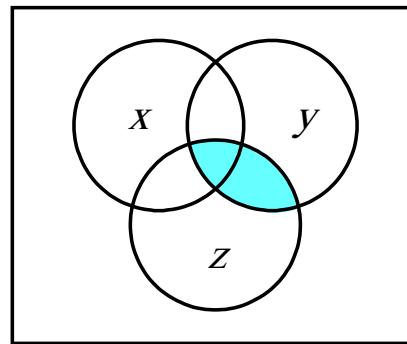


$$y z$$

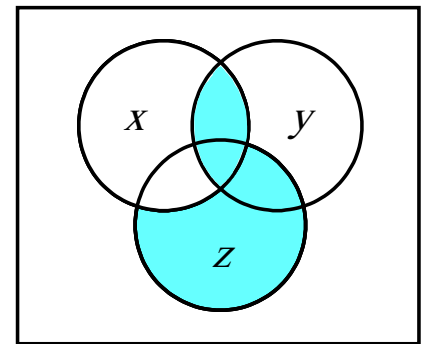


$$x y + \bar{x} z + y z$$


Right-Hand Side

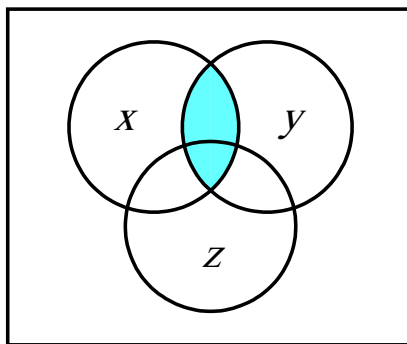

$$x y$$

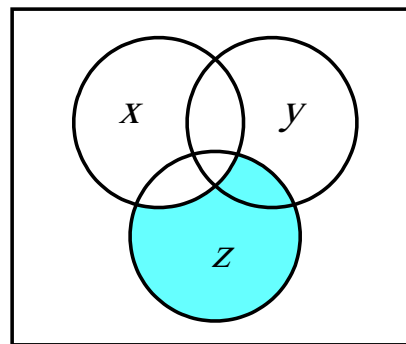


$$\bar{x} z$$

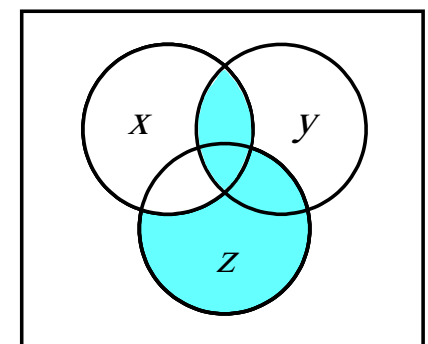


$$x y + \bar{x} z$$


Left-Hand Side

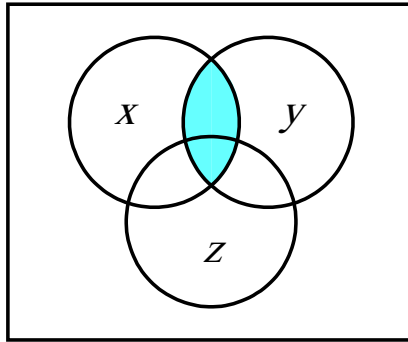

$$x y$$

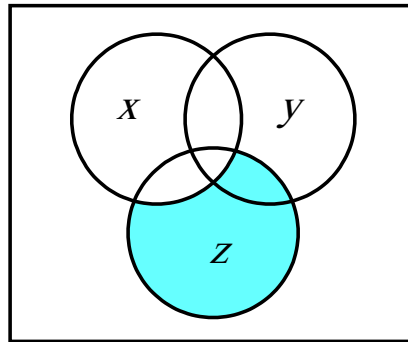


$$\bar{x} z$$

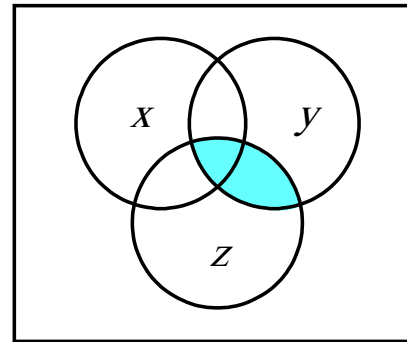


$$y z$$

These two are equal

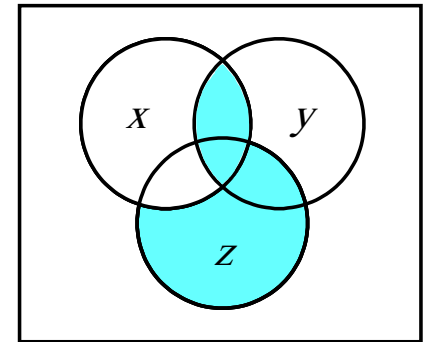


$$x y + \bar{x} z + y z$$


Right-Hand Side

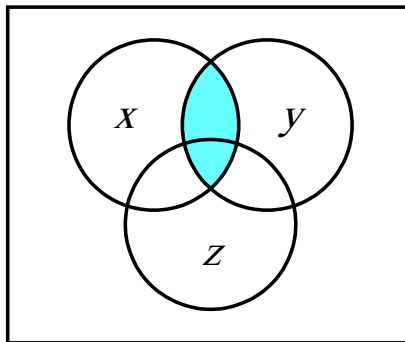

$$x y$$

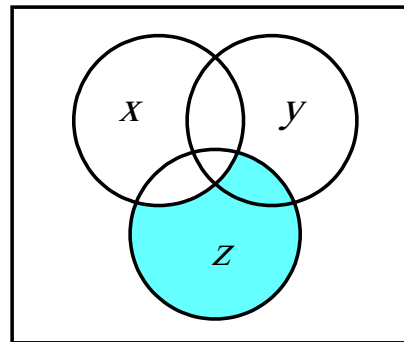

$$\bar{x} z$$

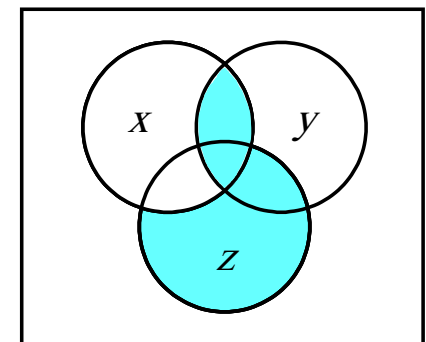

$$x y + \bar{x} z$$

Questions?

THE END