

CprE 281: Digital Logic

Instructor: Alexander Stoytchev

<http://www.ece.iastate.edu/~alexs/classes/>

Fast Adders

*CprE 281: Digital Logic
Iowa State University, Ames, IA
Copyright © Alexander Stoytchev*

Administrative Stuff

- **No HW is due next Monday**
- **HW 6 will be due on Monday Oct. 9.**

Administrative Stuff

- **Labs next week**
- **Mini-Project**
- **This is worth 3% of your grade (x2 labs)**
- **https://www.ece.iastate.edu/~alexs/classes/2023_Fall_281/labs/Project-Mini/**

Quick Review

The problems in which row are easier to calculate?

$$\begin{array}{r} - 82 \\ - 61 \\ \hline ?? \end{array}$$

$$\begin{array}{r} - 48 \\ - 26 \\ \hline ?? \end{array}$$

$$\begin{array}{r} - 32 \\ - 11 \\ \hline ?? \end{array}$$

$$\begin{array}{r} - 82 \\ - 64 \\ \hline ?? \end{array}$$

$$\begin{array}{r} - 48 \\ - 29 \\ \hline ?? \end{array}$$

$$\begin{array}{r} - 32 \\ - 13 \\ \hline ?? \end{array}$$

The problems in which row are easier to calculate?

$$\begin{array}{r} 82 \\ - 61 \\ \hline 21 \end{array}$$

$$\begin{array}{r} 48 \\ - 26 \\ \hline 22 \end{array}$$

$$\begin{array}{r} 32 \\ - 11 \\ \hline 21 \end{array}$$

Why?

$$\begin{array}{r} 82 \\ - 64 \\ \hline 18 \end{array}$$

$$\begin{array}{r} 48 \\ - 29 \\ \hline 19 \end{array}$$

$$\begin{array}{r} 32 \\ - 13 \\ \hline 19 \end{array}$$

Another Way to Do Subtraction

$$82 - 64 = 82 + 100 - 100 - 64$$

Another Way to Do Subtraction

$$\begin{aligned} 82 - 64 &= 82 + 100 - 100 - 64 \\ &= 82 + (100 - 64) - 100 \end{aligned}$$

Another Way to Do Subtraction

$$\begin{aligned} 82 - 64 &= 82 + 100 - 100 - 64 \\ &= 82 + (100 - 64) - 100 \\ &= 82 + (99 + 1 - 64) - 100 \end{aligned}$$

Another Way to Do Subtraction

$$\begin{aligned} 82 - 64 &= 82 + 100 - 100 - 64 \\ &= 82 + (100 - 64) - 100 \\ &= 82 + (99 + 1 - 64) - 100 \\ &= 82 + (99 - 64) + 1 - 100 \end{aligned}$$

Another Way to Do Subtraction

$$\begin{aligned} 82 - 64 &= 82 + 100 - 100 - 64 \\ &= 82 + (100 - 64) - 100 \\ &= 82 + (99 + 1 - 64) - 100 \end{aligned}$$

Does not require borrows

$$= 82 + (99 - 64) + 1 - 100$$

9's Complement

(subtract each digit from 9)

$$\begin{array}{r} 99 \\ - 64 \\ \hline 35 \end{array}$$

10's Complement

(subtract each digit from 9 and add 1 to the result)

$$\begin{array}{r} 99 \\ - 64 \\ \hline 35 + 1 = 36 \end{array}$$

Another Way to Do Subtraction

$$82 - 64 = 82 + (99 - 64) + 1 - 100$$

Another Way to Do Subtraction

9's complement

$$82 - 64 = 82 + (99 - 64) + 1 - 100$$

Another Way to Do Subtraction

9's complement

$$\begin{aligned} 82 - 64 &= 82 + (99 - 64) + 1 - 100 \\ &= 82 + 35 + 1 - 100 \end{aligned}$$

Another Way to Do Subtraction

$$\begin{aligned} 82 - 64 &= 82 + (99 - 64) + 1 - 100 \\ &= 82 + 35 + 1 - 100 \end{aligned}$$

9's complement

10's complement

Another Way to Do Subtraction

$$\begin{aligned} 82 - 64 &= 82 + (99 - 64) + 1 - 100 \\ &= 82 + 35 + 1 - 100 \\ &= 82 + 36 - 100 \end{aligned}$$

9's complement

10's complement

Another Way to Do Subtraction

$$\begin{aligned} 82 - 64 &= 82 + (99 - 64) + 1 - 100 && \text{9's complement} \\ &= 82 + 35 + 1 - 100 && \text{10's complement} \\ &= 82 + 36 - 100 && // \text{Add the first two.} \\ &= 118 - 100 \end{aligned}$$

Another Way to Do Subtraction

$$\begin{aligned} 82 - 64 &= 82 + (99 - 64) + 1 - 100 && \text{9's complement} \\ &= 82 + 35 + 1 - 100 && \text{10's complement} \\ &= 82 + 36 - 100 && // \text{Add the first two.} \\ &= 118 - 100 && // \text{Just delete the leading 1.} \\ &= 18 && // \text{No need to subtract 100.} \end{aligned}$$

Three Different Ways to Represent Negative Integer Numbers

- **Sign and magnitude**
- **1's complement**
- **2's complement**

Three Different Ways to Represent Negative Integer Numbers

- Sign and magnitude
- 1's complement
- 2's complement

only this method is used in modern computers

Interpretation of four-bit signed integers

$b_3 b_2 b_1 b_0$	Sign and magnitude	1's complement	2's complement
0111	+7	+7	+7
0110	+6	+6	+6
0101	+5	+5	+5
0100	+4	+4	+4
0011	+3	+3	+3
0010	+2	+2	+2
0001	+1	+1	+1
0000	+0	+0	+0
1000	-0	-7	-8
1001	-1	-6	-7
1010	-2	-5	-6
1011	-3	-4	-5
1100	-4	-3	-4
1101	-5	-2	-3
1110	-6	-1	-2
1111	-7	-0	-1

[Table 3.2 from the textbook]


1's Complement

1's complement


(subtract each digit from 1)

$$\begin{array}{r} 1 & 1 & 1 & 1 & 1 & 1 & 1 & 1 \\ - \\ 0 & 0 & 1 & 0 & 1 & 1 & 0 & 0 \\ \hline 1 & 1 & 0 & 1 & 0 & 0 & 1 & 1 \end{array}$$

 Circuit for negating a number stored in 1's complement representation



 Circuit for negating a number stored in 1's complement representation




2's Complement

2's complement representation (4-bit)

$b_3 b_2 b_1 b_0$	2's complement
0111	+7
0110	+6
0101	+5
0100	+4
0011	+3
0010	+2
0001	+1
0000	+0
1000	-8
1001	-7
1010	-6
1011	-5
1100	-4
1101	-3
1110	-2
1111	-1

The number circle for 2's complement

 

[Figure 3.11a from the textbook]

**Negate these numbers stored in
2's complement representation**

0 1 0 1

1 1 1 0

1 1 0 0

0 1 1 1

Negate these numbers stored in 2's complement representation

0 1 0 1

1 0 1 0

1 1 1 0

0 0 0 1

1 1 0 0

0 0 1 1

0 1 1 1

1 0 0 0

Invert all bits...

Negate these numbers stored in 2's complement representation

$$\begin{array}{r} 0101 \\ + 1010 \\ \hline 1011 \end{array}$$

$$\begin{array}{r} 1110 \\ + 0001 \\ \hline 0010 \end{array}$$

$$\begin{array}{r} 1100 \\ + 0011 \\ \hline 0100 \end{array}$$

$$\begin{array}{r} 0111 \\ + 1000 \\ \hline 1001 \end{array}$$

.. then add 1.

Negate these numbers stored in 2's complement representation

$$0101 = +5$$

$$\begin{array}{r} 1010 \\ + \quad 1 \\ \hline 1011 \end{array} = -5$$

$$1100 = -4$$

$$\begin{array}{r} 0011 \\ + \quad 1 \\ \hline 0100 \end{array} = +4$$


$$1110 = -2$$

$$\begin{array}{r} 0001 \\ + \quad 1 \\ \hline 0010 \end{array} = +2$$


$$0111 = +7$$

$$\begin{array}{r} 1000 \\ + \quad 1 \\ \hline 1001 \end{array} = -7$$

 Circuit #1 for negating a number stored in 2's complement representation



 Circuit #2 for negating a number stored in 2's complement representation



**Addition of two numbers stored
in 2's complement representation**

There are four cases to consider

- (+5) + (+2)
- (-5) + (+2)
- (+5) + (-2)
- (-5) + (-2)

There are four cases to consider

- $(+5) + (+2)$ positive plus positive
- $(-5) + (+2)$ negative plus positive
- $(+5) + (-2)$ positive plus negative
- $(-5) + (-2)$ negative plus negative

Positive plus positive

$$\begin{array}{r} (+5) \\ + (+2) \\ \hline (+7) \end{array} \quad \begin{array}{r} 0101 \\ + 0010 \\ \hline 0111 \end{array}$$

$b_3 b_2 b_1 b_0$	2's complement
0111	+7
0110	+6
0101	+5
0100	+4
0011	+3
0010	+2
0001	+1
0000	+0
1000	-8
1001	-7
1010	-6
1011	-5
1100	-4
1101	-3
1110	-2
1111	-1

[Figure 3.9 from the textbook]

Negative plus positive

$$\begin{array}{r} (-5) \\ + (+2) \\ \hline (-3) \end{array}$$

+ 1 0 1 1
+ 0 0 1 0

1 1 0 1

$b_3 b_2 b_1 b_0$	2's complement
0111	+7
0110	+6
0101	+5
0100	+4
0011	+3
0010	+2
0001	+1
0000	+0
1000	-8
1001	-7
1010	-6
1011	-5
1100	-4
1101	-3
1110	-2
1111	-1

[Figure 3.9 from the textbook]

Positive plus negative

$$\begin{array}{r} (+5) \\ + (-2) \\ \hline (+3) \end{array} \quad \begin{array}{r} 0101 \\ + 1110 \\ \hline 10011 \end{array}$$

↑
ignore

$b_3 b_2 b_1 b_0$	2's complement
0111	+7
0110	+6
0101	+5
0100	+4
0011	+3
0010	+2
0001	+1
0000	+0
1000	-8
1001	-7
1010	-6
1011	-5
1100	-4
1101	-3
1110	-2
1111	-1

[Figure 3.9 from the textbook]

Negative plus negative

$$\begin{array}{r}
 (-5) \quad \quad \quad \boxed{1\ 0\ 1\ 1} \\
 + (-2) \quad \quad \quad + \boxed{1\ 1\ 1\ 0} \\
 \hline
 (-7) \quad \quad \quad \boxed{1\ 1\ 0\ 0\ 1}
 \end{array}$$

↑
ignore

$b_3 b_2 b_1 b_0$	2's complement
0111	+7
0110	+6
0101	+5
0100	+4
0011	+3
0010	+2
0001	+1
0000	+0
1000	-8
1001	-7
1010	-6
1011	-5
1100	-4
1101	-3
1110	-2
1111	-1

[Figure 3.9 from the textbook]

**Subtraction of two numbers stored
in 2's complement representation**

There are four cases to consider

- $(+5) - (+2)$
- $(-5) - (+2)$
- $(+5) - (-2)$
- $(-5) - (-2)$

There are four cases to consider

- $(+5) - (+2)$ **positive minus positive**
- $(-5) - (+2)$ **negative minus positive**
- $(+5) - (-2)$ **positive minus negative**
- $(-5) - (-2)$ **negative minus negative**

There are four cases to consider

- $(+5) - (+2)$
- $(-5) - (+2)$
- $(+5) - (-2)$
- $(-5) - (-2)$

There are four cases to consider

- $(+5) - (+2) = (+5) + (-2)$
- $(-5) - (+2) = (-5) + (-2)$
- $(+5) - (-2) = (+5) + (+2)$
- $(-5) - (-2) = (-5) + (+2)$

There are four cases to consider

- $(+5) - (+2) = (+5) + (-2)$
- $(-5) - (+2) = (-5) + (-2)$
- $(+5) - (-2) = (+5) + (+2)$
- $(-5) - (-2) = (-5) + (+2)$

We can change subtraction into addition ...

There are four cases to consider

- $(+5) - (+2) = (+5) + (-2)$
- $(-5) - (+2) = (-5) + (-2)$
- $(+5) - (-2) = (+5) + (+2)$
- $(-5) - (-2) = (-5) + (+2)$

... if we negate the second number.

There are four cases to consider

- $(+5) - (+2) = (+5) + (-2)$
- $(-5) - (+2) = (-5) + (-2)$
- $(+5) - (-2) = (+5) + (+2)$
- $(-5) - (-2) = (-5) + (+2)$

These are the four addition cases
(arranged in a shuffled order)

Start with: Positive minus positive

$$\begin{array}{r} (+5) \\ - (+2) \\ \hline (+3) \end{array}$$

0 1 0 1
- 0 0 1 0

$b_3 b_2 b_1 b_0$	2's complement
0111	+7
0110	+6
0101	+5
0100	+4
0011	+3
0010	+2
0001	+1
0000	+0
1000	-8
1001	-7
1010	-6
1011	-5
1100	-4
1101	-3
1110	-2
1111	-1

[Figure 3.10 from the textbook]

Convert to: Positive plus negative

$$\begin{array}{r}
 (+5) \\
 - (+2) \\
 \hline
 (+3)
 \end{array}
 \quad
 \begin{array}{r}
 0101 \\
 - 0010 \\
 \hline
 \end{array}
 \quad
 \Rightarrow
 \quad
 \begin{array}{r}
 0101 \\
 + 1110 \\
 \hline
 10011
 \end{array}
 \quad
 \begin{array}{r}
 (+5) \\
 + (-2) \\
 \hline
 (+3)
 \end{array}$$

↑
ignore

$b_3 b_2 b_1 b_0$	2's complement
0111	+7
0110	+6
0101	+5
0100	+4
0011	+3
0010	+2
0001	+1
0000	+0
1000	-8
1001	-7
1010	-6
1011	-5
1100	-4
1101	-3
1110	-2
1111	-1

[Figure 3.10 from the textbook]

Convert to: Positive plus negative


$$\begin{array}{r}
 (+5) \\
 - (+2) \\
 \hline
 (+3)
 \end{array}
 \quad
 \begin{array}{r}
 0101 \\
 - 0010 \\
 \hline
 \end{array}
 \quad
 \Rightarrow
 \quad
 \begin{array}{r}
 0101 \\
 + 1110 \\
 \hline
 10011
 \end{array}
 \quad
 \begin{array}{r}
 (+5) \\
 + (-2) \\
 \hline
 (+3)
 \end{array}$$

↑
ignore


$b_3 b_2 b_1 b_0$	2's complement
0111	+7
0110	+6
0101	+5
0100	+4
0011	+3
0010	+2
0001	+1
0000	+0
1000	-8
1001	-7
1010	-6
1011	-5
1100	-4
1101	-3
1110	-2
1111	-1

[Figure 3.10 from the textbook]

 Graphical interpretation of four-bit 2's complement numbers



(a) The number circle

 

(b) Subtracting 2 by adding its 2's complement

[Figure 3.11 from the textbook]

Start with: Negative minus positive

$$\begin{array}{r} (-5) \\ - (+2) \\ \hline (-7) \end{array}$$

$\begin{array}{r} 1011 \\ - 0010 \\ \hline \end{array}$

$b_3 b_2 b_1 b_0$	2's complement
0111	+7
0110	+6
0101	+5
0100	+4
0011	+3
0010	+2
0001	+1
0000	+0
1000	-8
1001	-7
1010	-6
1011	-5
1100	-4
1101	-3
1110	-2
1111	-1

[Figure 3.10 from the textbook]

Convert to: Negative plus negative

$$\begin{array}{r}
 (-5) \\
 - (+2) \\
 \hline
 (-7)
 \end{array}
 \quad
 \begin{array}{r}
 1011 \\
 - 0010 \\
 \hline
 \end{array}
 \quad
 \xrightarrow{\hspace{1cm}}
 \quad
 \begin{array}{r}
 1011 \\
 + 1110 \\
 \hline
 11001
 \end{array}
 \quad
 \begin{array}{r}
 (-5) \\
 + (-2) \\
 \hline
 (-7)
 \end{array}$$

↑
ignore

$b_3 b_2 b_1 b_0$	2's complement
0111	+7
0110	+6
0101	+5
0100	+4
0011	+3
0010	+2
0001	+1
0000	+0
1000	-8
1001	-7
1010	-6
1011	-5
1100	-4
1101	-3
1110	-2
1111	-1

[Figure 3.10 from the textbook]

Start with: Positive minus negative

$$\begin{array}{r} (+5) \\ - (-2) \\ \hline (+7) \end{array}$$

0 1 0 1
- 1 1 1 0

$b_3 b_2 b_1 b_0$	2's complement
0111	+7
0110	+6
0101	+5
0100	+4
0011	+3
0010	+2
0001	+1
0000	+0
1000	-8
1001	-7
1010	-6
1011	-5
1100	-4
1101	-3
1110	-2
1111	-1

[Figure 3.10 from the textbook]

Convert to: Positive plus positive

$$\begin{array}{r}
 (+5) \\
 - (-2) \\
 \hline
 (+7)
 \end{array}
 \quad
 \begin{array}{c}
 \textcolor{red}{0\ 1\ 0\ 1} \\
 - \textcolor{yellow}{1\ 1\ 1\ 0} \\
 \hline
 \end{array}
 \quad
 \xrightarrow{\hspace{1cm}}
 \quad
 \begin{array}{r}
 (+5) \\
 + (+2) \\
 \hline
 (+7)
 \end{array}
 \quad
 \begin{array}{r}
 0\ 1\ 0\ 1 \\
 + \textcolor{green}{0\ 0\ 1\ 0} \\
 \hline
 0\ 1\ 1\ 1
 \end{array}$$

$b_3 b_2 b_1 b_0$	2's complement
0111	+7
0110	+6
0101	+5
0100	+4
0011	+3
0010	+2
0001	+1
0000	+0
1000	-8
1001	-7
1010	-6
1011	-5
1100	-4
1101	-3
1110	-2
1111	-1

[Figure 3.10 from the textbook]

Start with: Negative minus negative

$$\begin{array}{r}
 (-5) \\
 - (-2) \\
 \hline
 (-3)
 \end{array}
 \quad
 \begin{array}{r}
 \textcolor{red}{1} \textcolor{red}{0} \textcolor{red}{1} \textcolor{red}{1} \\
 - \textcolor{yellow}{1} \textcolor{yellow}{1} \textcolor{yellow}{1} \textcolor{yellow}{0} \\
 \hline
 \end{array}$$

$b_3 b_2 b_1 b_0$	2's complement
0111	+7
0110	+6
0101	+5
0100	+4
0011	+3
0010	+2
0001	+1
0000	+0
1000	-8
1001	-7
1010	-6
1011	-5
1100	-4
1101	-3
1110	-2
1111	-1

[Figure 3.10 from the textbook]

Convert to: Negative plus positive

$$\begin{array}{r}
 (-5) \\
 - (-2) \\
 \hline
 (-3)
 \end{array}
 \quad
 \begin{array}{r}
 \textcolor{red}{1} \textcolor{red}{0} \textcolor{red}{1} \textcolor{red}{1} \\
 - \textcolor{yellow}{1} \textcolor{yellow}{1} \textcolor{yellow}{1} \textcolor{yellow}{0} \\
 \hline
 \end{array}
 \quad
 \xrightarrow{\hspace{1cm}}
 \quad
 \begin{array}{r}
 \textcolor{red}{1} \textcolor{red}{0} \textcolor{red}{1} \textcolor{red}{1} \\
 + \textcolor{green}{0} \textcolor{green}{0} \textcolor{green}{1} \textcolor{green}{0} \\
 \hline
 \textcolor{blue}{1} \textcolor{blue}{1} \textcolor{blue}{0} \textcolor{blue}{1}
 \end{array}
 \quad
 \begin{array}{r}
 (-5) \\
 + (+2) \\
 \hline
 (-3)
 \end{array}$$


$b_3 b_2 b_1 b_0$	2's complement
0111	+7
0110	+6
0101	+5
0100	+4
0011	+3
0010	+2
0001	+1
0000	+0
1000	-8
1001	-7
1010	-6
1011	-5
1100	-4
1101	-3
1110	-2
1111	-1

[Figure 3.10 from the textbook]

Take Home Message

- Subtraction can be performed by simply negating the second number and adding it to the first, regardless of the signs of the two numbers.
- Thus, the same adder circuit can be used to perform both addition and subtraction !!!

Adder/subtractor unit

 


[Figure 3.12 from the textbook]

XOR Tricks


control	y	out
0	0	0
0	1	1
1	0	1
1	1	0

control

 

XOR as a repeater

control	y	out
0	0	0
0	1	1

 


XOR as a repeater

control	y	out
0	0	0
0	1	1

y ————— y


XOR as an inverter

control	y	out
1	0	1
1	1	0

 


XOR as an inverter

control	y	out
1	0	1
1	1	0

 


Addition: when control = 0

 


[Figure 3.12 from the textbook]

Addition: when control = 0

 


[Figure 3.12 from the textbook]

Addition: when control = 0

 


[Figure 3.12 from the textbook]

Subtraction: when control = 1

 


[Figure 3.12 from the textbook]

Subtraction: when control = 1

 


[Figure 3.12 from the textbook]

Subtraction: when control = 1

 

[Figure 3.12 from the textbook]

Subtraction: when control = 1

 


[Figure 3.12 from the textbook]


Addition Examples:

**all inputs and outputs are given in
2's complement representation**


Addition: $5 + 6 = 11$

 


Addition: $5 + 6 = 11$

 


Addition: $5 + 6 = 11$

 


Addition: $5 + 6 = 11$

 


Addition: $5 + 6 = 11$

 


Addition: $4 + (-7) = -3$

 

Addition: $4 + (-7) = -3$

 


Addition: $4 + (-7) = -3$

 


Subtraction Examples:
**all inputs and outputs are given in
2's complement representation**


Subtraction: $7 - 3 = 4$

 


Subtraction: $7 - 3 = 4$

 


Subtraction: $7 - 3 = 4$

 

Subtraction: $7 - 3 = 4$

 


Subtraction: $7 - 3 = 4$

 


Analogy: Another Way to Do Subtraction

$$\begin{aligned} 82 - 64 &= 82 + (99 - 64) + 1 - 100 && \text{9's complement} \\ &= 82 + 35 + 1 - 100 && \text{10's complement} \\ &= 82 + 36 - 100 && // \text{Add the first two.} \\ &= 118 - 100 && // \text{Just delete the leading 1.} \\ &= 18 && // \text{No need to subtract 100.} \end{aligned}$$


Subtraction: $(-2) - (-5) = 3$

 


Subtraction: $(-2) - (-5) = 3$

 

Subtraction: $(-2) - (-5) = 3$

 

Subtraction: $(-2) - (-5) = 3$

 

Overflow Detection

Examples of determination of overflow

$$\begin{array}{r} (+7) \\ + (+2) \\ \hline (+9) \end{array} \quad + \quad \begin{array}{r} 0111 \\ 0010 \\ \hline 1001 \end{array}$$

$$\begin{array}{r} (-7) \\ + (+2) \\ \hline (-5) \end{array} \quad + \quad \begin{array}{r} 1001 \\ 0010 \\ \hline 1011 \end{array}$$

$$\begin{array}{r} (+7) \\ + (-2) \\ \hline (+5) \end{array} \quad + \quad \begin{array}{r} 0111 \\ 1110 \\ \hline 10101 \end{array}$$

$$\begin{array}{r} (-7) \\ + (-2) \\ \hline (-9) \end{array} \quad + \quad \begin{array}{r} 1001 \\ 1110 \\ \hline 10111 \end{array}$$

[Figure 3.13 from the textbook]

Examples of determination of overflow

$$\begin{array}{r} (+7) \\ + (+2) \\ \hline (+9) \end{array} \quad + \quad \begin{array}{r} 0111 \\ 0010 \\ \hline 1001 \end{array}$$

$$\begin{array}{r} (-7) \\ + (+2) \\ \hline (-5) \end{array} \quad + \quad \begin{array}{r} 1001 \\ 0010 \\ \hline 1011 \end{array}$$

$$\begin{array}{r} (+7) \\ + (-2) \\ \hline (+5) \end{array} \quad + \quad \begin{array}{r} 0111 \\ 1110 \\ \hline 10101 \end{array}$$

$$\begin{array}{r} (-7) \\ + (-2) \\ \hline (-9) \end{array} \quad + \quad \begin{array}{r} 1001 \\ 1110 \\ \hline 10111 \end{array}$$

In 2's complement, both +9 and -9 are not representable with 4 bits.

[Figure 3.13 from the textbook]

Examples of determination of overflow

$$\begin{array}{r} 01100 \\ (+7) \\ + (+2) \\ \hline (+9) \end{array}$$

$$\begin{array}{r} 0111 \\ + 0010 \\ \hline 1001 \end{array}$$

$$\begin{array}{r} 00000 \\ (-7) \\ + (+2) \\ \hline (-5) \end{array}$$

$$\begin{array}{r} 1001 \\ + 0010 \\ \hline 1011 \end{array}$$

$$\begin{array}{r} 11100 \\ (+7) \\ + (-2) \\ \hline (+5) \end{array}$$

$$\begin{array}{r} 0111 \\ + 1110 \\ \hline 10101 \end{array}$$

$$\begin{array}{r} 10000 \\ (-7) \\ + (-2) \\ \hline (-9) \end{array}$$

$$\begin{array}{r} 1001 \\ + 1110 \\ \hline 10111 \end{array}$$

Include the carry bits: $c_4\ c_3\ c_2\ c_1\ c_0$

Examples of determination of overflow

$$\begin{array}{r} (+7) \\ + (+2) \\ \hline (+9) \end{array} \quad + \quad \begin{array}{r} \boxed{0} 1 1 0 0 \\ 0 1 1 1 \\ 0 0 1 0 \\ \hline 1 0 0 1 \end{array}$$

$$\begin{array}{r} (-7) \\ + (+2) \\ \hline (-5) \end{array} \quad + \quad \begin{array}{r} \boxed{0} 0 0 0 \\ 1 0 0 1 \\ 0 0 1 0 \\ \hline 1 0 1 1 \end{array}$$

$$\begin{array}{r} (+7) \\ + (-2) \\ \hline (+5) \end{array} \quad + \quad \begin{array}{r} \boxed{1} 1 1 0 0 \\ 0 1 1 1 \\ 1 1 1 0 \\ \hline 1 0 1 0 1 \end{array}$$

$$\begin{array}{r} (-7) \\ + (-2) \\ \hline (-9) \end{array} \quad + \quad \begin{array}{r} \boxed{1} 0 0 0 \\ 1 0 0 1 \\ 1 1 1 0 \\ \hline 1 0 1 1 1 \end{array}$$

Include the carry bits: $\boxed{c_4 c_3} c_2 c_1 c_0$

Examples of determination of overflow

$$\begin{array}{l} c_4 = 0 \\ c_3 = 1 \end{array}$$

$$\begin{array}{r} (+7) \\ + (+2) \\ \hline (+9) \end{array}$$

$$\begin{array}{r} \boxed{0} 1 1 0 0 \\ + \quad 0 1 1 1 \\ \hline 1 0 0 1 \end{array}$$

$$\begin{array}{r} (-7) \\ + (+2) \\ \hline (-5) \end{array}$$

$$\begin{array}{r} \boxed{0} 0 0 0 \\ + \quad 1 0 0 1 \\ \hline 1 0 1 1 \end{array}$$

$$\begin{array}{l} c_4 = 0 \\ c_3 = 0 \end{array}$$

$$\begin{array}{l} c_4 = 1 \\ c_3 = 1 \end{array}$$

$$\begin{array}{r} (+7) \\ + (-2) \\ \hline (+5) \end{array}$$

$$\begin{array}{r} \boxed{1} 1 1 0 0 \\ + \quad 0 1 1 1 \\ \hline 1 0 1 0 1 \end{array}$$

$$\begin{array}{r} (-7) \\ + (-2) \\ \hline (-9) \end{array}$$

$$\begin{array}{r} \boxed{1} 0 0 0 \\ + \quad 1 0 0 1 \\ \hline 1 0 1 1 1 \end{array}$$

$$\begin{array}{l} c_4 = 1 \\ c_3 = 0 \end{array}$$

Include the carry bits: $\boxed{c_4 \ c_3} \ c_2 \ c_1 \ c_0$

Examples of determination of overflow

$$\begin{array}{l} c_4 = 0 \\ c_3 = 1 \end{array}$$

$$\begin{array}{r} (+7) \\ + (+2) \\ \hline (+9) \end{array}$$

$$\begin{array}{r} \boxed{0} 1 1 0 0 \\ + \quad 0 1 1 1 \\ \hline 1 0 0 1 \end{array}$$

$$\begin{array}{r} (-7) \\ + (+2) \\ \hline (-5) \end{array}$$

$$\begin{array}{r} \boxed{0} 0 0 0 0 \\ + \quad 1 0 0 1 \\ \hline 1 0 1 1 \end{array}$$

$$\begin{array}{l} c_4 = 0 \\ c_3 = 0 \end{array}$$

$$\begin{array}{l} c_4 = 1 \\ c_3 = 1 \end{array}$$

$$\begin{array}{r} (+7) \\ + (-2) \\ \hline (+5) \end{array}$$

$$\begin{array}{r} \boxed{1} 1 1 0 0 \\ + \quad 0 1 1 1 \\ \hline 1 0 1 0 1 \end{array}$$

$$\begin{array}{r} (-7) \\ + (-2) \\ \hline (-9) \end{array}$$

$$\begin{array}{r} \boxed{1} 0 0 0 0 \\ + \quad 1 0 0 1 \\ \hline 1 0 1 1 1 \end{array}$$

$$\begin{array}{l} c_4 = 1 \\ c_3 = 0 \end{array}$$

Overflow occurs only in these two cases.

Examples of determination of overflow

$$\begin{aligned}c_4 &= 0 \\c_3 &= 1\end{aligned}$$

$$\begin{array}{r} (+7) \\ + (+2) \\ \hline (+9)\end{array}$$

$$\begin{array}{r} \boxed{0} 1 1 0 0 \\ + \quad 0 1 1 1 \\ \hline 1 0 0 1\end{array}$$

$$\begin{array}{r} (-7) \\ + (+2) \\ \hline (-5)\end{array}$$

$$\begin{array}{r} \boxed{0} 0 0 0 \\ + \quad 1 0 0 1 \\ \hline 1 0 1 1\end{array}$$

$$\begin{aligned}c_4 &= 0 \\c_3 &= 0\end{aligned}$$

$$\begin{aligned}c_4 &= 1 \\c_3 &= 1\end{aligned}$$

$$\begin{array}{r} (+7) \\ + (-2) \\ \hline (+5)\end{array}$$

$$\begin{array}{r} \boxed{1} 1 1 0 0 \\ + \quad 0 1 1 1 \\ \hline 1 0 1 0 1\end{array}$$

$$\begin{array}{r} (-7) \\ + (-2) \\ \hline (-9)\end{array}$$

$$\begin{array}{r} \boxed{1} 0 0 0 \\ + \quad 1 0 0 1 \\ \hline 1 0 1 1 1\end{array}$$

$$\begin{aligned}c_4 &= 1 \\c_3 &= 0\end{aligned}$$

$$\text{Overflow} = c_3 \bar{c}_4 + \bar{c}_3 c_4$$

Examples of determination of overflow

$$\begin{aligned}c_4 &= 0 \\c_3 &= 1\end{aligned}$$

$$\begin{array}{r} (+7) \\ + (+2) \\ \hline (+9)\end{array}$$

$$\begin{array}{r} \boxed{0} 1 1 0 0 \\ + \quad 0 1 1 1 \\ \hline 1 0 0 1\end{array}$$

$$\begin{array}{r} (-7) \\ + (+2) \\ \hline (-5)\end{array}$$

$$\begin{array}{r} \boxed{0} 0 0 0 \\ + \quad 1 0 0 1 \\ \hline 1 0 1 1\end{array}$$

$$\begin{aligned}c_4 &= 0 \\c_3 &= 0\end{aligned}$$

$$\begin{aligned}c_4 &= 1 \\c_3 &= 1\end{aligned}$$

$$\begin{array}{r} (+7) \\ + (-2) \\ \hline (+5)\end{array}$$

$$\begin{array}{r} \boxed{1} 1 1 0 0 \\ + \quad 0 1 1 1 \\ \hline 1 0 1 0 1\end{array}$$

$$\begin{array}{r} (-7) \\ + (-2) \\ \hline (-9)\end{array}$$

$$\begin{array}{r} \boxed{1} 0 0 0 \\ + \quad 1 0 0 1 \\ \hline 1 0 1 1 1\end{array}$$

$$\begin{aligned}c_4 &= 1 \\c_3 &= 0\end{aligned}$$

$$\text{Overflow} = \underbrace{c_3 \bar{c}_4 + \bar{c}_3 c_4}_{\text{XOR}}$$


Calculating overflow for 4-bit numbers with only three significant bits

$$\begin{aligned}\text{Overflow} &= c_3 \bar{c}_4 + \bar{c}_3 c_4 \\ &= c_3 \oplus c_4\end{aligned}$$


Calculating overflow for n-bit numbers with only n-1 significant bits

$$\text{Overflow} = c_{n-1} \oplus c_n$$

Detecting Overflow

 


Detecting Overflow (with one extra XOR)

 

Detecting Overflow (alternative method)


Used if you don't have access to the internal carries of the adder.

Detecting Overflow (with one extra XOR)

 


If the adder is implemented on a chip,
then this line is not available.
So the first method can't be used.

Overflow Detection: 4-bits

 


Overflow Detection: 5-bits

 


A ripple-carry adder

 
How long does it take to compute all sum bits and all carry bits?



 Delays through the modular implementation of the full-adder circuit




(a) Block diagram

 

 
(b) Detailed diagram

[Figure 3.4 from the textbook]

Delays through the modular implementation of the full-adder circuit




(a) Block diagram

 

 
(b) Detailed diagram

[Figure 3.4 from the textbook]

Delays through the modular implementation of the full-adder circuit




(a) Block diagram

 

 (b) Detailed diagram


[Figure 3.4 from the textbook]

How long does it take to compute all sum bits and all carry bits in this case?




It takes $3n$ gate delays?

Delays through the Full-Adder circuit

 


[Figure 3.3c from the textbook]

Delays through the Full-Adder circuit

 


[Figure 3.3c from the textbook]

Delays through the Full-Adder circuit

 

[Figure 3.3c from the textbook]

 How long does it take to compute all sum bits and all carry bits?



It takes $2n$ gate delays?

Can we perform addition even faster?


The goal is to evaluate very fast if the carry from the previous stage will be equal to 0 or 1.

Can we perform addition even faster?

The goal is to evaluate very fast if the carry from the previous stage will be equal to 0 or 1.


To accomplish this goal we will have to redesign the full-adder circuit yet again.

The Full-Adder Circuit

 

[Figure 3.3c from the textbook]

The Full-Adder Circuit

 

Decomposing the Carry Expression

$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

Decomposing the Carry Expression


$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

$$c_{i+1} = x_i y_i + (x_i + y_i) c_i$$

Decomposing the Carry Expression

$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$


$$c_{i+1} = x_i y_i + (x_i + y_i) c_i$$

 

Another Way to Draw the Full-Adder Circuit


$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

$$c_{i+1} = x_i y_i + (x_i + y_i)c_i$$

 


Another Way to Draw the Full-Adder Circuit

$$c_{i+1} = x_i y_i + (x_i + y_i)c_i$$

 

Another Way to Draw the Full-Adder Circuit
 
$$c_{i+1} = \underbrace{x_i y_i}_{g_i} + \underbrace{(x_i + y_i)c_i}_{p_i}$$




Another Way to Draw the Full-Adder Circuit


g - generate

p - propagate

 
$$c_{i+1} = \underbrace{x_i y_i}_{g_i} + \underbrace{(x_i + y_i)c_i}_{p_i}$$



 Yet Another Way to Draw It (Just Rotate It)




Now we can Build a Ripple-Carry Adder

 


[Figure 3.14 from the textbook]

Now we can Build a Ripple-Carry Adder

 


[Figure 3.14 from the textbook]

 2-bit ripple-carry adder: 5 gate delays (1+2+2)



 n -bit ripple-carry adder: $2n+1$ gate delays



n-bit Ripple-Carry Adder

- It takes 1 gate delay to generate all g_i and p_i signals
- +2 more gate delays to generate carry 1
- +2 more gate delay to generate carry 2
- ...
- +2 more gate delay to generate carry n
- Thus, the total delay through an n-bit ripple-carry adder is $2n+1$ gate delays!

n-bit Ripple-Carry Adder

- It takes 1 gate delay to generate all g_i and p_i signals
- +2 more gate delays to generate carry 1
- +2 more gate delay to generate carry 2
- ...
- +2 more gate delay to generate carry n
- Thus, the total delay through an n-bit ripple-carry adder is $2n+1$ gate delays!

This is slower by 1 than the original design?!

A carry-lookahead adder

Decomposing the Carry Expression

$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

Decomposing the Carry Expression

$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

$$c_{i+1} = \underbrace{x_i y_i}_{g_i} + \underbrace{(x_i + y_i)}_{p_i} c_i$$


Decomposing the Carry Expression

$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

$$c_{i+1} = \underbrace{x_i y_i}_{g_i} + \underbrace{(x_i + y_i)}_{p_i} c_i$$


(1 gate delay) (1 gate delay)

It takes 1 gate delay to compute all p_i signals

 

[Figure 3.14 from the textbook]

It takes 1 gate delay to compute all g_i signals

 

[Figure 3.14 from the textbook]

Decomposing the Carry Expression

$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

$$c_{i+1} = \underbrace{x_i y_i}_{g_i} + \underbrace{(x_i + y_i)}_{p_i} c_i$$

Decomposing the Carry Expression

$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

$$c_{i+1} = \underbrace{x_i y_i}_{g_i} + \underbrace{(x_i + y_i)}_{p_i} c_i$$

$$c_{i+1} = g_i + p_i c_i$$

Decomposing the Carry Expression

$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

$$c_{i+1} = \underbrace{x_i y_i}_{g_i} + \underbrace{(x_i + y_i)}_{p_i} c_i$$

$$c_{i+1} = g_i + p_i c_i$$

recursive
expansion of

$$c_{i+1} = g_i + p_i (g_{i-1} + p_{i-1} c_{i-1})$$

Decomposing the Carry Expression

$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$


$$c_{i+1} = \underbrace{x_i y_i}_{g_i} + \underbrace{(x_i + y_i)}_{p_i} c_i$$

$$c_{i+1} = g_i + p_i c_i$$

$$c_{i+1} = g_i + p_i(g_{i-1} + p_{i-1} c_{i-1})$$


$$c_{i+1} = g_i + p_i g_{i-1} + p_i p_{i-1} c_{i-1}$$

Now we can Build a Carry-Lookahead Adder

 

[Figure 3.15 from the textbook]

The first two stages of a carry-lookahead adder

 


[Figure 3.15 from the textbook]

Carry for the first stage

$$c_1 = g_0 + p_0 c_0$$


Carry for the first stage

 

Carry for the second stage

$$c_2 = g_1 + p_1 g_0 + p_1 p_0 c_0$$

Carry for the second stage

 

Carry for the first two stages

$$c_1 = g_0 + p_0 c_0$$

$$c_2 = g_1 + p_1 g_0 + p_1 p_0 c_0$$

Carry for the first two stages

$$c_1 = g_0 + p_0 c_0$$

$$c_2 = g_1 + \underline{p_1 g_0} + \underline{p_1 p_0 c_0}$$

Carry for the first two stages

$$c_1 = g_0 + p_0 c_0$$

$$c_2 = g_1 + \underline{p_1 g_0} + \underline{p_1 p_0 c_0}$$

$$= g_1 + p_1 (\underbrace{g_0 + p_0 c_0}_{c_1})$$

Carry for the first two stages


$$c_1 = g_0 + p_0 c_0$$

$$c_2 = g_1 + p_1 g_0 + p_1 p_0 c_0$$

$$= g_1 + p_1 \underbrace{(g_0 + p_0 c_0)}_{c_1}$$


$$= g_1 + p_1 c_1$$

The first two stages of a carry-lookahead adder

 


[Figure 3.15 from the textbook]


It takes 3 gate delays to generate c_1

 


It takes 3 gate delays to generate c_2

 

 
The first two stages of a carry-lookahead adder



It takes 4 gate delays to generate s_1

 

It takes 4 gate delays to generate s_2

 

N-bit Carry-Lookahead Adder

- It takes 1 gate delay to generate all g_i and p_i signals
- It takes 2 more gate delays to generate all carry signals
- It takes 1 more gate delay to generate all sum bits
- Thus, the total delay through an n-bit carry-lookahead adder is only 4 gate delays!

Expanding the Carry Expression

$$c_{i+1} = g_i + p_i c_i$$

$$c_1 = g_0 + p_0 c_0$$

$$c_2 = g_1 + p_1 g_0 + p_1 p_0 c_0$$

$$c_3 = g_2 + p_2 g_1 + p_2 p_1 g_0 + p_2 p_1 p_0 c_0$$

...

$$\begin{aligned} c_8 = & g_7 + p_7 g_6 + p_7 p_6 g_5 + p_7 p_6 p_5 g_4 \\ & + p_7 p_6 p_5 p_4 g_3 + p_7 p_6 p_5 p_4 p_3 g_2 \\ & + p_7 p_6 p_5 p_4 p_3 p_2 g_1 + p_7 p_6 p_5 p_4 p_3 p_2 p_1 g_0 \\ & + p_7 p_6 p_5 p_4 p_3 p_2 p_1 p_0 c_0 \end{aligned}$$

Expanding the Carry Expression

$$c_{i+1} = g_i + p_i c_i$$

$$c_1 = g_0 + p_0 c_0$$

$$c_2 = g_1 + p_1 g_0 + p_1 p_0 c_0$$

$$c_3 = g_2 + p_2 g_1 + p_2 p_1 g_0 + p_2 p_1 p_0 c_0$$

...


$$c_8 = g_7 + p_7 g_6 + p_7 p_6 g_5 + p_7 p_6 p_5 g_4$$

Even this takes
only 3 gate delays


$$\begin{aligned} &+ p_7 p_6 p_5 p_4 g_3 + p_7 p_6 p_5 p_4 p_3 g_2 \\ &+ p_7 p_6 p_5 p_4 p_3 p_2 g_1 + p_7 p_6 p_5 p_4 p_3 p_2 p_1 g_0 \\ &+ p_7 p_6 p_5 p_4 p_3 p_2 p_1 p_0 c_0 \end{aligned}$$

A **hierarchical** carry-lookahead adder
with ripple-carry between blocks

 
A hierarchical carry-lookahead adder with ripple-carry between blocks



 A hierarchical carry-lookahead adder with ripple-carry between blocks




 A hierarchical carry-lookahead adder with ripple-carry between blocks




A hierarchical carry-lookahead adder

A hierarchical carry-lookahead adder with ripple-carry between blocks

 


[Figure 3.16 from the textbook]

A hierarchical carry-lookahead adder

 


[Figure 3.17 from the textbook]


A hierarchical carry-lookahead adder

 

A hierarchical carry-lookahead adder

 

A hierarchical carry-lookahead adder

 

The Hierarchical Carry Expression

$$\begin{aligned}c_8 = & g_7 + p_7g_6 + p_7p_6g_5 + p_7p_6p_5g_4 \\& + p_7p_6p_5p_4g_3 + p_7p_6p_5p_4p_3g_2 \\& + p_7p_6p_5p_4p_3p_2g_1 + p_7p_6p_5p_4p_3p_2p_1g_0 \\& + p_7p_6p_5p_4p_3p_2p_1p_0c_0\end{aligned}$$

The Hierarchical Carry Expression

$$c_8 = g_7 + p_7g_6 + p_7p_6g_5 + p_7p_6p_5g_4 \\ + p_7p_6p_5p_4g_3 + p_7p_6p_5p_4p_3g_2 \\ + p_7p_6p_5p_4p_3p_2g_1 + p_7p_6p_5p_4p_3p_2p_1g_0 \\ + p_7p_6p_5p_4p_3p_2p_1p_0c_0$$

The Hierarchical Carry Expression

$$c_8 = \boxed{g_7 + p_7g_6 + p_7p_6g_5 + p_7p_6p_5g_4 + p_7p_6p_5p_4g_3 + p_7p_6p_5p_4p_3g_2 + p_7p_6p_5p_4p_3p_2g_1 + p_7p_6p_5p_4p_3p_2p_1g_0 + p_7p_6p_5p_4p_3p_2p_1p_0c_0}$$

G_0 → (The first seven terms)

P_0 → ($p_7p_6p_5p_4p_3p_2p_1p_0c_0$)

The Hierarchical Carry Expression

$$c_8 = \boxed{g_7 + p_7g_6 + p_7p_6g_5 + p_7p_6p_5g_4 + p_7p_6p_5p_4g_3 + p_7p_6p_5p_4p_3g_2 + p_7p_6p_5p_4p_3p_2g_1 + p_7p_6p_5p_4p_3p_2p_1g_0} + \boxed{p_7p_6p_5p_4p_3p_2p_1p_0c_0}$$

G_0 →

P_0 →

$$c_8 = G_0 + P_0 c_0$$

The Hierarchical Carry Expression

$$c_8 = \boxed{g_7 + p_7g_6 + p_7p_6g_5 + p_7p_6p_5g_4 + p_7p_6p_5p_4g_3 + p_7p_6p_5p_4p_3g_2 + p_7p_6p_5p_4p_3p_2g_1 + p_7p_6p_5p_4p_3p_2p_1g_0 + p_7p_6p_5p_4p_3p_2p_1p_0c_0}$$

3-gate delays

G_0 → (The first four terms)

P_0 → (The last term)

2-gate delays

$$c_8 = G_0 + P_0 c_0$$

The Hierarchical Carry Expression

$$c_8 = g_7 + p_7g_6 + p_7p_6g_5 + p_7p_6p_5g_4 + p_7p_6p_5p_4g_3 + p_7p_6p_5p_4p_3g_2 + p_7p_6p_5p_4p_3p_2g_1 + p_7p_6p_5p_4p_3p_2p_1g_0 + p_7p_6p_5p_4p_3p_2p_1p_0c_0$$

3-gate delays

G_0 → (blue box)

P_0 → (red box)

2-gate delays

$$c_8 = G_0 + P_0 c_0$$

3-gate 2-gate
delays delays

The Hierarchical Carry Expression

$$c_8 = g_7 + p_7g_6 + p_7p_6g_5 + p_7p_6p_5g_4 + p_7p_6p_5p_4g_3 + p_7p_6p_5p_4p_3g_2 + p_7p_6p_5p_4p_3p_2g_1 + p_7p_6p_5p_4p_3p_2p_1g_0 + p_7p_6p_5p_4p_3p_2p_1p_0c_0$$

3-gate delays

G_0 → (blue box)

P_0 → (red box)

2-gate delays

$$c_8 = G_0 + P_0 c_0$$

3-gate delays 3-gate delays

The Hierarchical Carry Expression

$$c_8 = g_7 + p_7g_6 + p_7p_6g_5 + p_7p_6p_5g_4 + p_7p_6p_5p_4g_3 + p_7p_6p_5p_4p_3g_2 + p_7p_6p_5p_4p_3p_2g_1 + p_7p_6p_5p_4p_3p_2p_1g_0 + p_7p_6p_5p_4p_3p_2p_1p_0c_0$$

3-gate delays

G_0 → (blue box)

P_0 → (red box)

2-gate delays

$$c_8 = G_0 + P_0 c_0$$

4-gate
delays

The Hierarchical Carry Expression

$$\begin{aligned}c_8 = & g_7 + p_7g_6 + p_7p_6g_5 + p_7p_6p_5g_4 \\& + p_7p_6p_5p_4g_3 + p_7p_6p_5p_4p_3g_2 \\& + p_7p_6p_5p_4p_3p_2g_1 + p_7p_6p_5p_4p_3p_2p_1g_0 \\& + p_7p_6p_5p_4p_3p_2p_1p_0c_0\end{aligned}$$

$$\begin{aligned}c_{16} = & g_{15} + p_{15}g_{14} + p_{15}p_{14}g_{13} + p_{15}p_{14}p_{13}g_{12} \\& + p_{15}p_{14}p_{13}p_{12}g_{11} + p_{15}p_{14}p_{13}p_{12}p_{11}g_{10} \\& + p_{15}p_{14}p_{13}p_{12}p_{11}p_{10}g_9 + p_{15}p_{14}p_{13}p_{12}p_{11}p_{10}p_9g_8 \\& + p_{15}p_{14}p_{13}p_{12}p_{11}p_{10}p_9p_8c_8\end{aligned}$$

The Hierarchical Carry Expression

$$\begin{aligned}c_8 = & g_7 + p_7g_6 + p_7p_6g_5 + p_7p_6p_5g_4 \\& + p_7p_6p_5p_4g_3 + p_7p_6p_5p_4p_3g_2 \\& + p_7p_6p_5p_4p_3p_2g_1 + p_7p_6p_5p_4p_3p_2p_1g_0 \\& + p_7p_6p_5p_4p_3p_2p_1p_0c_0\end{aligned}$$

The same expression, just add 8 to all subscripts

$$\begin{aligned}c_{16} = & g_{15} + p_{15}g_{14} + p_{15}p_{14}g_{13} + p_{15}p_{14}p_{13}g_{12} \\& + p_{15}p_{14}p_{13}p_{12}g_{11} + p_{15}p_{14}p_{13}p_{12}p_{11}g_{10} \\& + p_{15}p_{14}p_{13}p_{12}p_{11}p_{10}g_9 + p_{15}p_{14}p_{13}p_{12}p_{11}p_{10}p_9g_8 \\& + p_{15}p_{14}p_{13}p_{12}p_{11}p_{10}p_9p_8c_8\end{aligned}$$

The Hierarchical Carry Expression

$$c_8 = g_7 + p_7g_6 + p_7p_6g_5 + p_7p_6p_5g_4$$
$$+ p_7p_6p_5p_4g_3 + p_7p_6p_5p_4p_3g_2$$
$$+ p_7p_6p_5p_4p_3p_2g_1 + p_7p_6p_5p_4p_3p_2p_1g_0$$
$$+ p_7p_6p_5p_4p_3p_2p_1p_0c_0$$

3-gate delays

G_0

P_0

2-gate delays

$$c_{16} = g_{15} + p_{15}g_{14} + p_{15}p_{14}g_{13} + p_{15}p_{14}p_{13}g_{12}$$
$$+ p_{15}p_{14}p_{13}p_{12}g_{11} + p_{15}p_{14}p_{13}p_{12}p_{11}g_{10}$$
$$+ p_{15}p_{14}p_{13}p_{12}p_{11}p_{10}g_9 + p_{15}p_{14}p_{13}p_{12}p_{11}p_{10}p_9g_8$$
$$+ p_{15}p_{14}p_{13}p_{12}p_{11}p_{10}p_9p_8c_8$$

The Hierarchical Carry Expression

$$\begin{aligned}c_8 = & g_7 + p_7g_6 + p_7p_6g_5 + p_7p_6p_5g_4 \\& + p_7p_6p_5p_4g_3 + p_7p_6p_5p_4p_3g_2 \\& + p_7p_6p_5p_4p_3p_2g_1 + p_7p_6p_5p_4p_3p_2p_1g_0 \\& + p_7p_6p_5p_4p_3p_2p_1p_0c_0\end{aligned}$$

$$c_{16} = \boxed{\begin{aligned} & g_{15} + p_{15}g_{14} + p_{15}p_{14}g_{13} + p_{15}p_{14}p_{13}g_{12} \\ & + p_{15}p_{14}p_{13}p_{12}g_{11} + p_{15}p_{14}p_{13}p_{12}p_{11}g_{10} \\ & + p_{15}p_{14}p_{13}p_{12}p_{11}p_{10}g_9 + p_{15}p_{14}p_{13}p_{12}p_{11}p_{10}p_9g_8 \\ & + p_{15}p_{14}p_{13}p_{12}p_{11}p_{10}p_9p_8c_8 \end{aligned}}$$

3-gate delays

G_1 → $\boxed{+ p_{15}p_{14}p_{13}p_{12}p_{11}p_{10}p_9p_8c_8}$

P_1 → $\boxed{+ p_{15}p_{14}p_{13}p_{12}p_{11}p_{10}p_9p_8c_8}$

2-gate delays

The Hierarchical Carry Expression

$$c_8 = G_0 + P_0 c_0$$

The Hierarchical Carry Expression

$$c_8 = \textcircled{G_0} + P_0 c_0$$

3-gate delays

The Hierarchical Carry Expression

$$c_8 = \underbrace{G_0 + P_0 c_0}_{\text{4-gate delays}}$$

The Hierarchical Carry Expression

$$c_8 = G_0 + P_0 c_0$$

$$\begin{aligned}c_{16} &= G_1 + P_1 c_8 \\&= G_1 + P_1 G_0 + P_1 P_0 c_0\end{aligned}$$

The Hierarchical Carry Expression

$$c_8 = G_0 + P_0 c_0$$

3-gate delays

$$\begin{aligned} c_{16} &= G_1 + P_1 c_8 \\ &= G_1 + P_1 G_0 + P_1 P_0 c_0 \end{aligned}$$

3-gate delays

The Hierarchical Carry Expression

$$c_8 = G_0 + P_0 c_0$$

$$\begin{aligned}c_{16} &= G_1 + P_1 c_8 \\&= G_1 + P_1 \textcolor{blue}{G_0} + P_1 P_0 c_0\end{aligned}$$

3-gate delays

The Hierarchical Carry Expression

$$c_8 = G_0 + P_0 c_0$$

$$\begin{aligned}c_{16} &= G_1 + P_1 c_8 \\&= G_1 + \textcircled{P_1 G_0} + P_1 P_0 c_0\end{aligned}$$

4-gate delays

The Hierarchical Carry Expression

$$c_8 = G_0 + P_0 c_0$$

$$\begin{aligned}c_{16} &= G_1 + P_1 c_8 \\&= \textcircled{G_1 + P_1 G_0 + P_1 P_0 c_0}\end{aligned}$$

5-gate delays

The Hierarchical Carry Expression

$$c_8 = G_0 + P_0 c_0$$

$$\begin{aligned}c_{16} &= G_1 + P_1 c_8 \\&= G_1 + P_1 G_0 + P_1 P_0 c_0\end{aligned}$$

$$c_{24} = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 c_0$$

$$c_{32} = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 c_0$$

The Hierarchical Carry Expression


$$c_8 = G_0 + P_0 c_0 \quad \text{4-gate delays}$$

$$\begin{aligned} c_{16} &= G_1 + P_1 c_8 \\ &= G_1 + P_1 G_0 + P_1 P_0 c_0 \end{aligned} \quad \text{5-gate delays}$$

$$c_{24} = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 c_0 \quad \text{5-gate delays}$$


$$c_{32} = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 c_0 \quad \text{5-gate delays}$$

A hierarchical carry-lookahead adder

 

[Figure 3.17 from the textbook]

A hierarchical carry-lookahead adder

 

[Figure 3.17 from the textbook]


Total Gate Delay Through a Hierarchical Carry-Lookahead Adder

- The total delay is 8 gates:
 - 3 to generate all G_i and P_i signals
 - +2 to generate c_8 , c_{16} , c_{24} , and c_{32}
 - +2 to generate internal carries in the blocks
 - +1 to generate the sum bits (one extra XOR)


Total Gate Delay Through a Hierarchical Carry-Lookahead Adder

- The total delay is 8 gates:
 - 3 to generate all G_i and P_i signals
 - +2 to generate c_8 , c_{16} , c_{24} , and c_{32}
 - **+2 to generate internal carries in the blocks**
 - +1 to generate the sum bits (one extra XOR)

 2 more gate delays for the internal carries within a block




 
2 more gate delays for the internal carries within a block



Hierarchical CLA Adder Carry Logic

SECOND
LEVEL
HIERARCHY

  - C8 – 4 gate delays
- C16 – 5 gate delays
- C24 – 5 Gate delays
- C32 – 5 Gate delays





FIRST LEVEL HIERARCHY

Hierarchical CLA Critical Path

- C1 - 3 gate delays
- C9 - 6 gate delays
- C17 - 7 gate delays**
- C25 - 7 Gate delays

SECOND
LEVEL
HIERARCHY

  

Total Gate Delay Through a Hierarchical Carry-Lookahead Adder

- The total delay is **8 gates**:
 - 3 to generate all G_i and P_i signals
 - +2 to generate c_8 , c_{16} , c_{24} , and c_{32}
 - +2 to generate internal carries in the blocks
 - +1 to generate the sum bits (one extra XOR)

Questions?

THE END