

CprE 281: Digital Logic

Instructor: Alexander Stoytchev

<http://www.ece.iastate.edu/~alexs/classes/>

Multiplication

*CprE 281: Digital Logic
Iowa State University, Ames, IA
Copyright © Alexander Stoytchev*

Administrative Stuff

- **No HW is due today**
- **HW 6 will be due on Monday Oct. 9.**
- **Posted on the class web page.**


Administrative Stuff

- **Labs this week**
- **Mini-Project**
- **This is worth 3% of your grade (x2 labs)**
- **https://www.ece.iastate.edu/~alexs/classes/2023_Fall_281/labs/Project-Mini/**

Quick Review


A ripple-carry adder

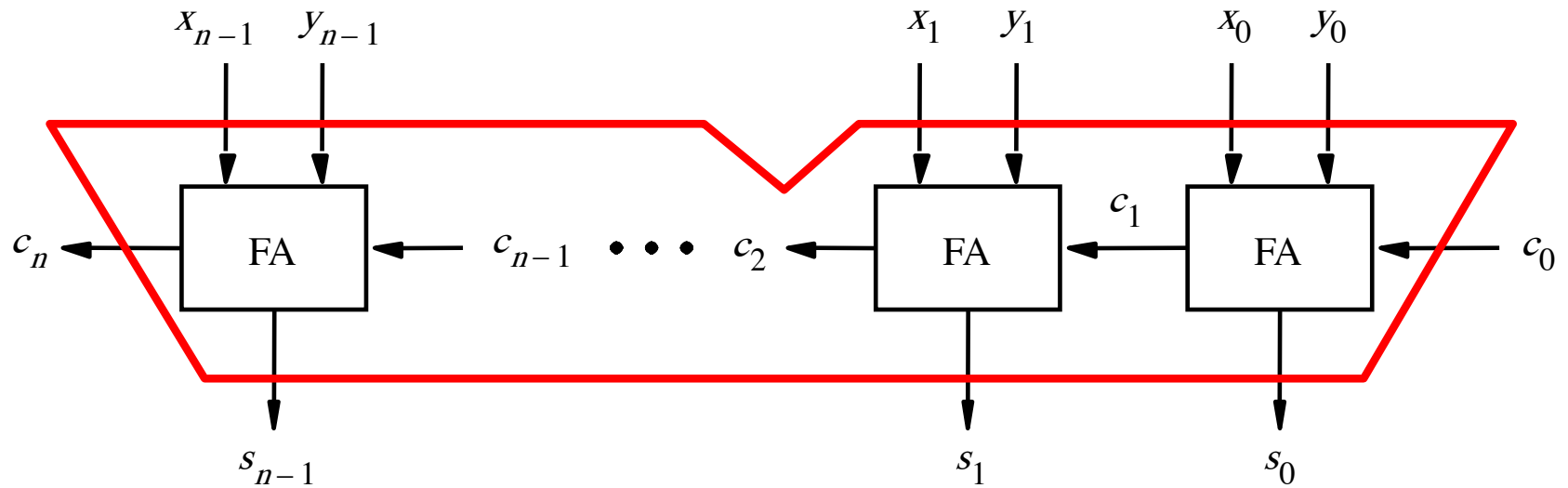How long does it take to compute all sum bits and all carry bits?




It takes $2n$ gate delays using a ripple-carry adder?

Delays through the Full-Adder circuit

 


The Full-Adder Circuit

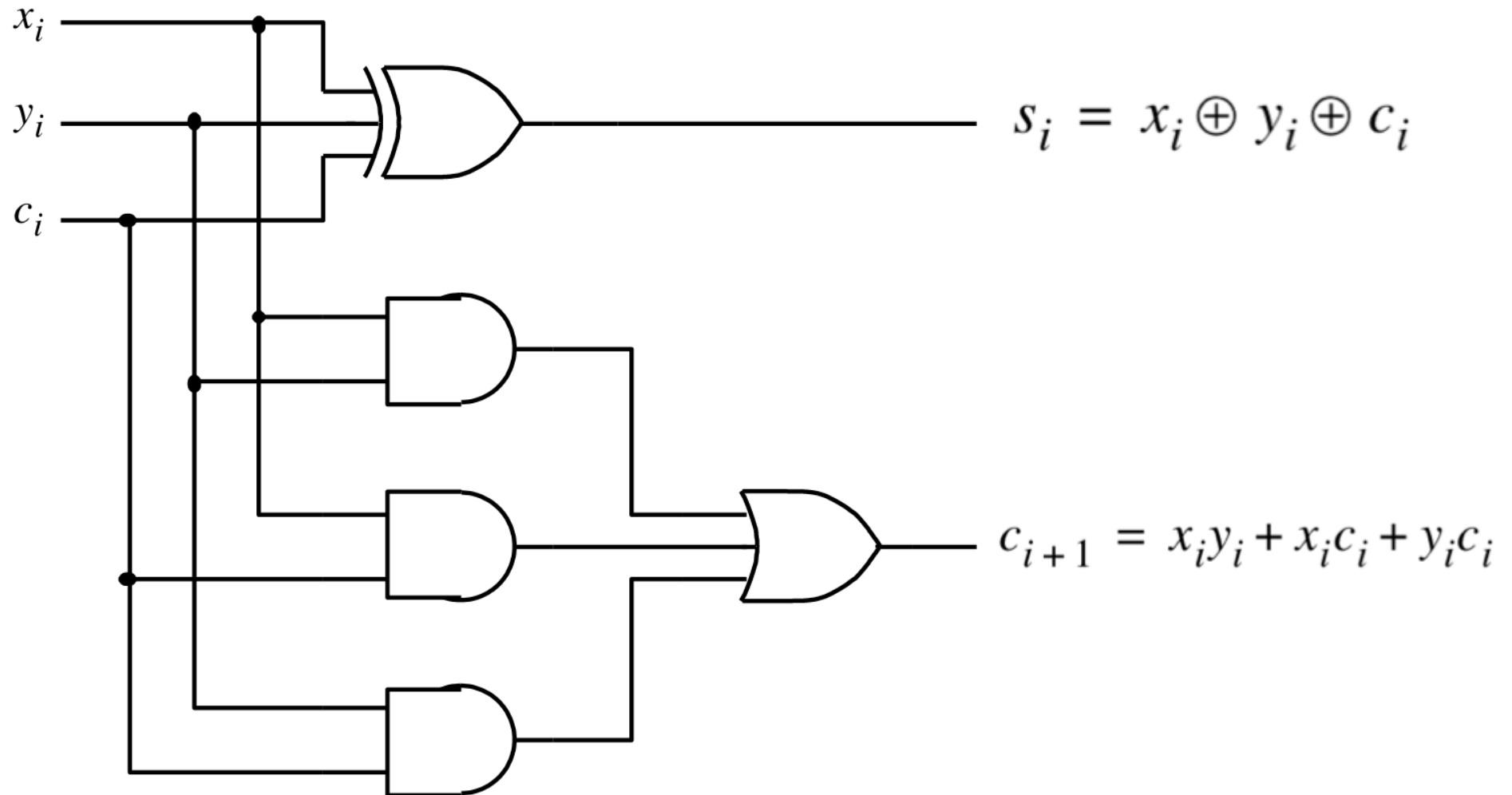


[Figure 3.3c from the textbook]

The Full-Adder Circuit

 

Let's take a closer look at this.

 Another Way to Draw the Full-Adder Circuit



Decomposing the Carry Expression

$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

Decomposing the Carry Expression


$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

$$c_{i+1} = x_i y_i + (x_i + y_i) c_i$$

Decomposing the Carry Expression

$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$


$$c_{i+1} = x_i y_i + (x_i + y_i) c_i$$

 

Another Way to Draw the Full-Adder Circuit


$$C_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

$$C_{i+1} = x_i y_i + (x_i + y_i) c_i$$

 


Another Way to Draw the Full-Adder Circuit

$$C_{i+1} = x_i y_i + (x_i + y_i)C_i$$

 


Another Way to Draw the Full-Adder Circuit
 
$$C_{i+1} = \underbrace{x_i y_i}_{g_i} + \underbrace{(x_i + y_i)}_{p_i} C_i$$




Another Way to Draw the Full-Adder Circuit

 
$$C_{i+1} = \underbrace{x_i y_i}_{g_i} + \underbrace{(x_i + y_i)}_{P_i} C_i$$



 Yet Another Way to Draw It (Just Rotate It)



Now we can Build a Ripple-Carry Adder

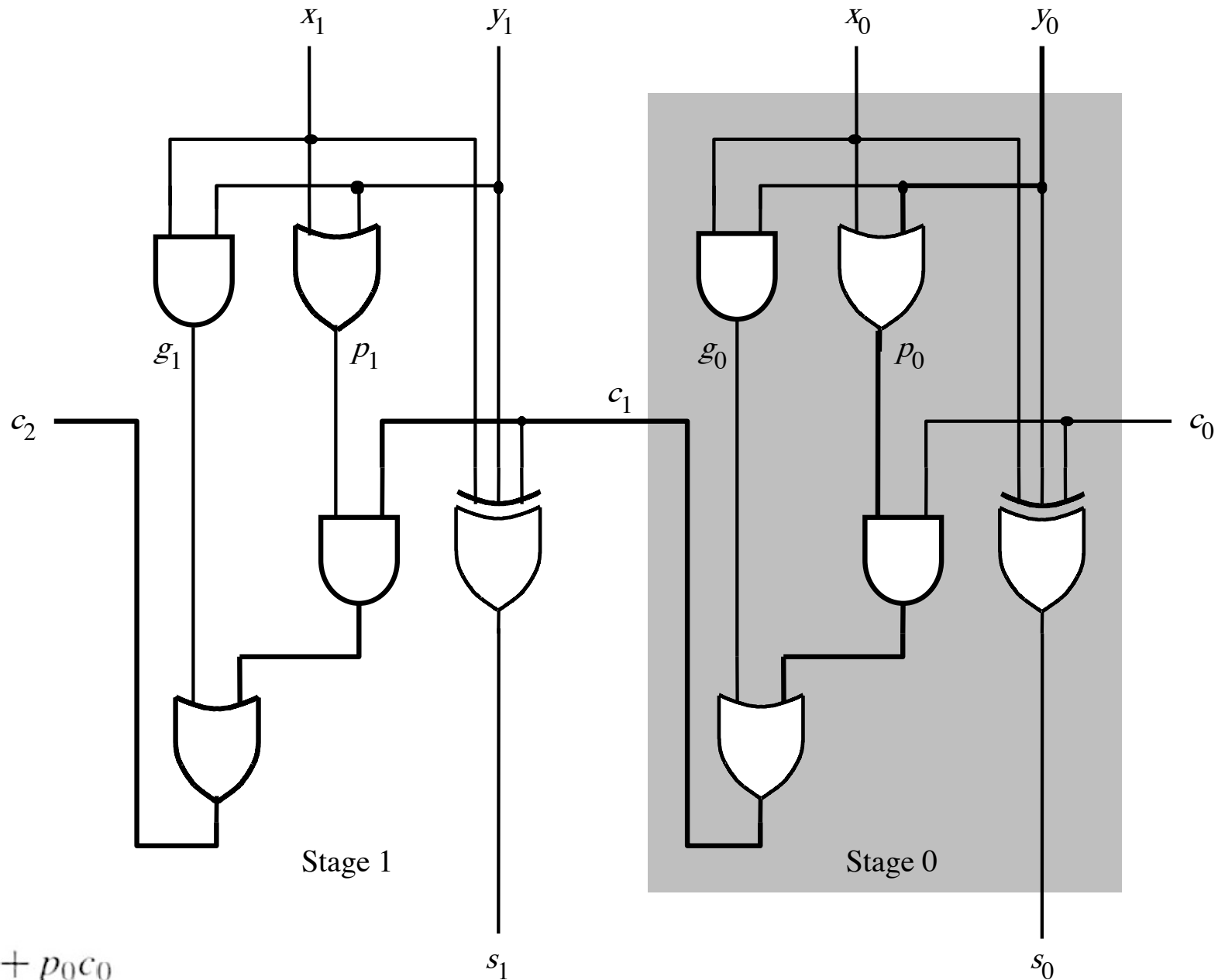


$$c_1 = g_0 + p_0 c_0$$

$$c_2 = g_1 + p_1 g_0 + p_1 p_0 c_0$$

[Figure 3.14 from the textbook]

Now we can Build a Ripple-Carry Adder

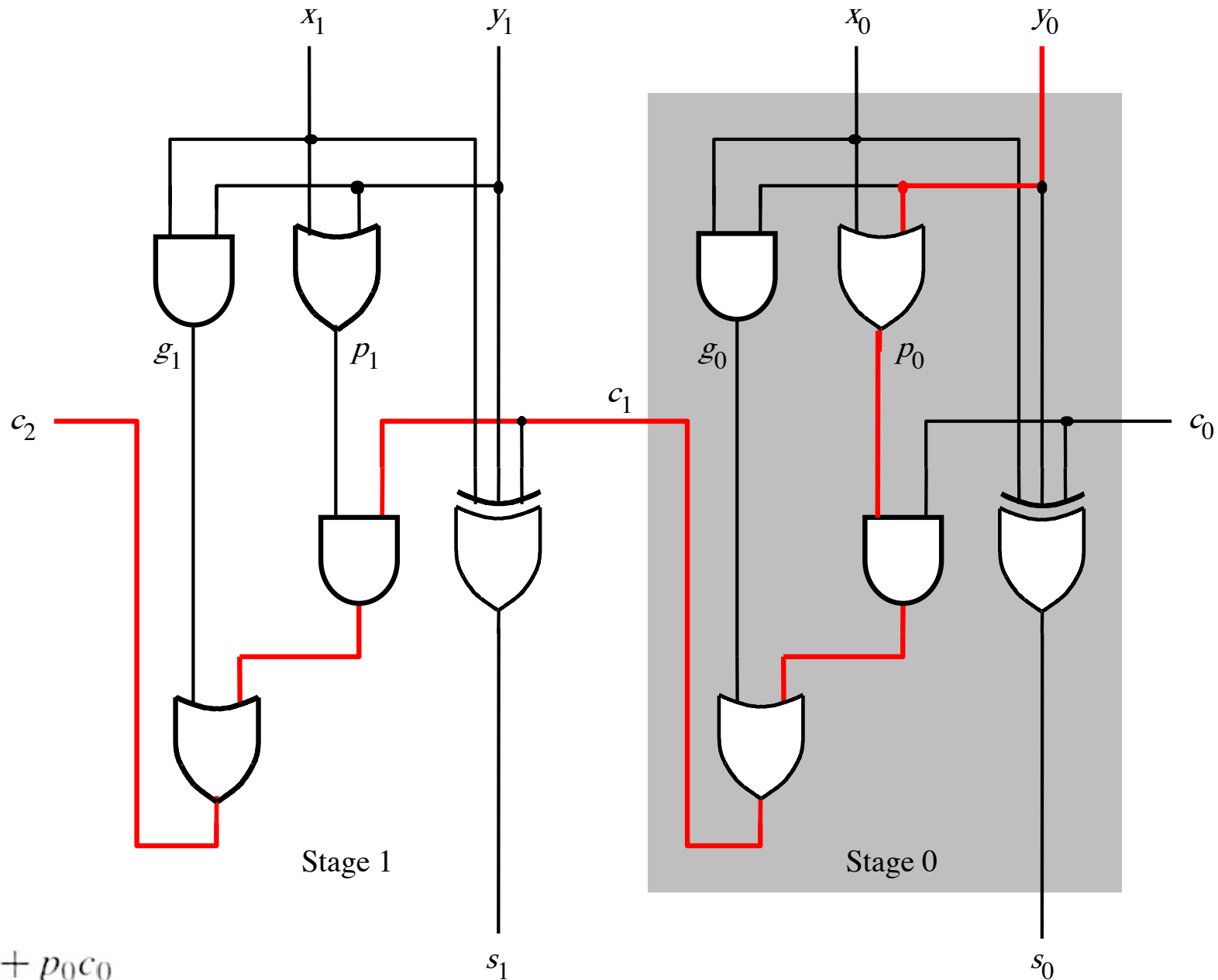


$$c_1 = g_0 + p_0 c_0$$


$$c_2 = g_1 + p_1 g_0 + p_1 p_0 c_0$$

[Figure 3.14 from the textbook]

The delay is 5 gates (1+2+2)

 

 n-bit ripple-carry adder: $2n+1$ gate delays



Decomposing the Carry Expression

$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

$$c_{i+1} = \underbrace{x_i y_i}_{g_i} + \underbrace{(x_i + y_i)}_{p_i} c_i$$

$$c_{i+1} = g_i + p_i c_i$$

$$c_{i+1} = g_i + p_i (g_{i-1} + p_{i-1} c_{i-1})$$


$$= g_i + p_i g_{i-1} + p_i p_{i-1} c_{i-1}$$

Carry for the first two stages

$$c_1 = g_0 + p_0 c_0$$

$$c_2 = g_1 + p_1 g_0 + p_1 p_0 c_0$$

 The first two stages of a carry-lookahead adder




$$c_1 = g_0 + p_0 c_0$$

$$c_2 = g_1 + p_1 g_0 + p_1 p_0 c_0$$

[Figure 3.15 from the textbook]


It takes 3 gate delays to generate c_1

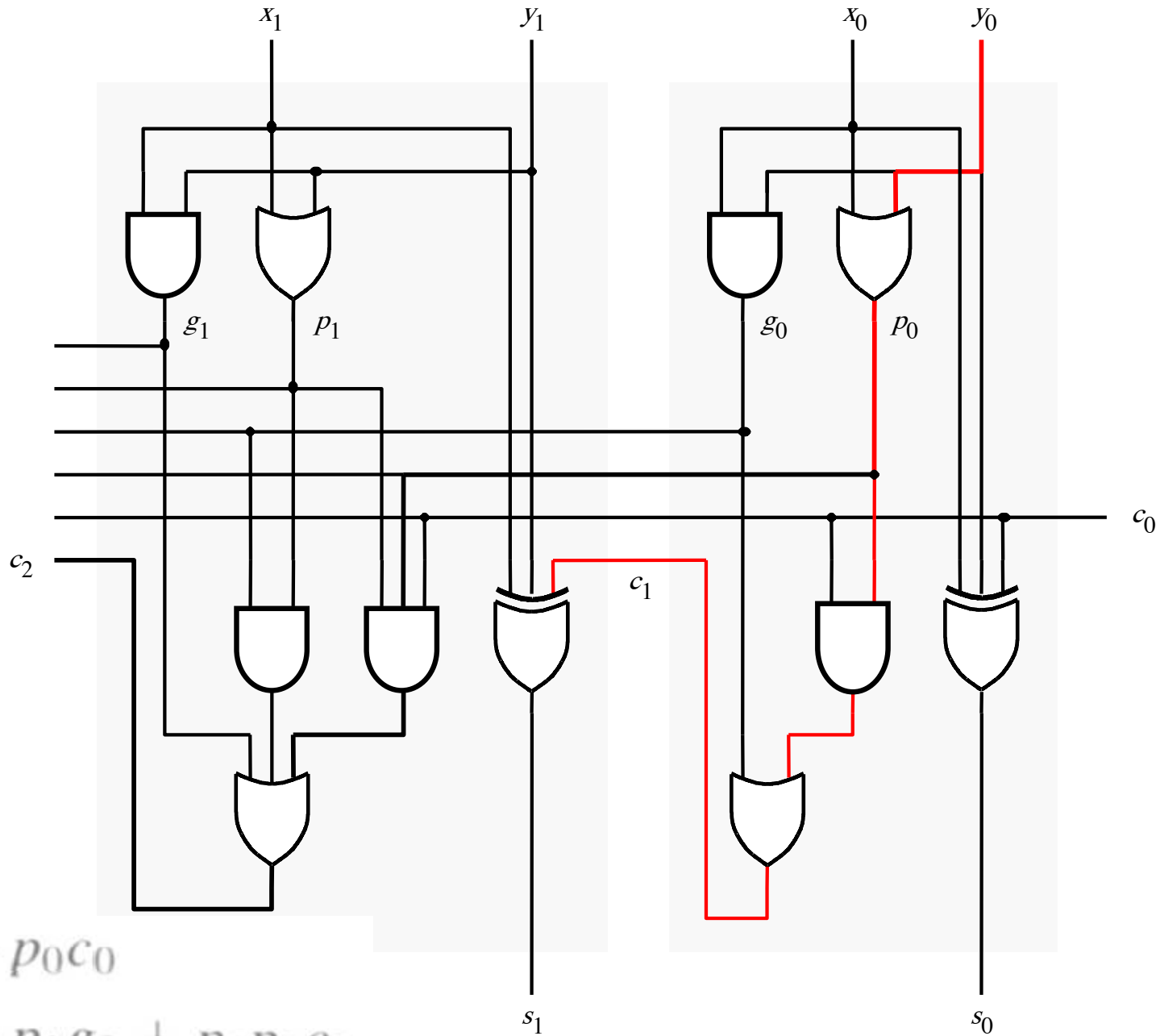

$$c_1 = g_0 + p_0 c_0$$

$$c_2 = g_1 + p_1 g_0 + p_1 p_0 c_0$$


It takes 3 gate delays to generate c_2

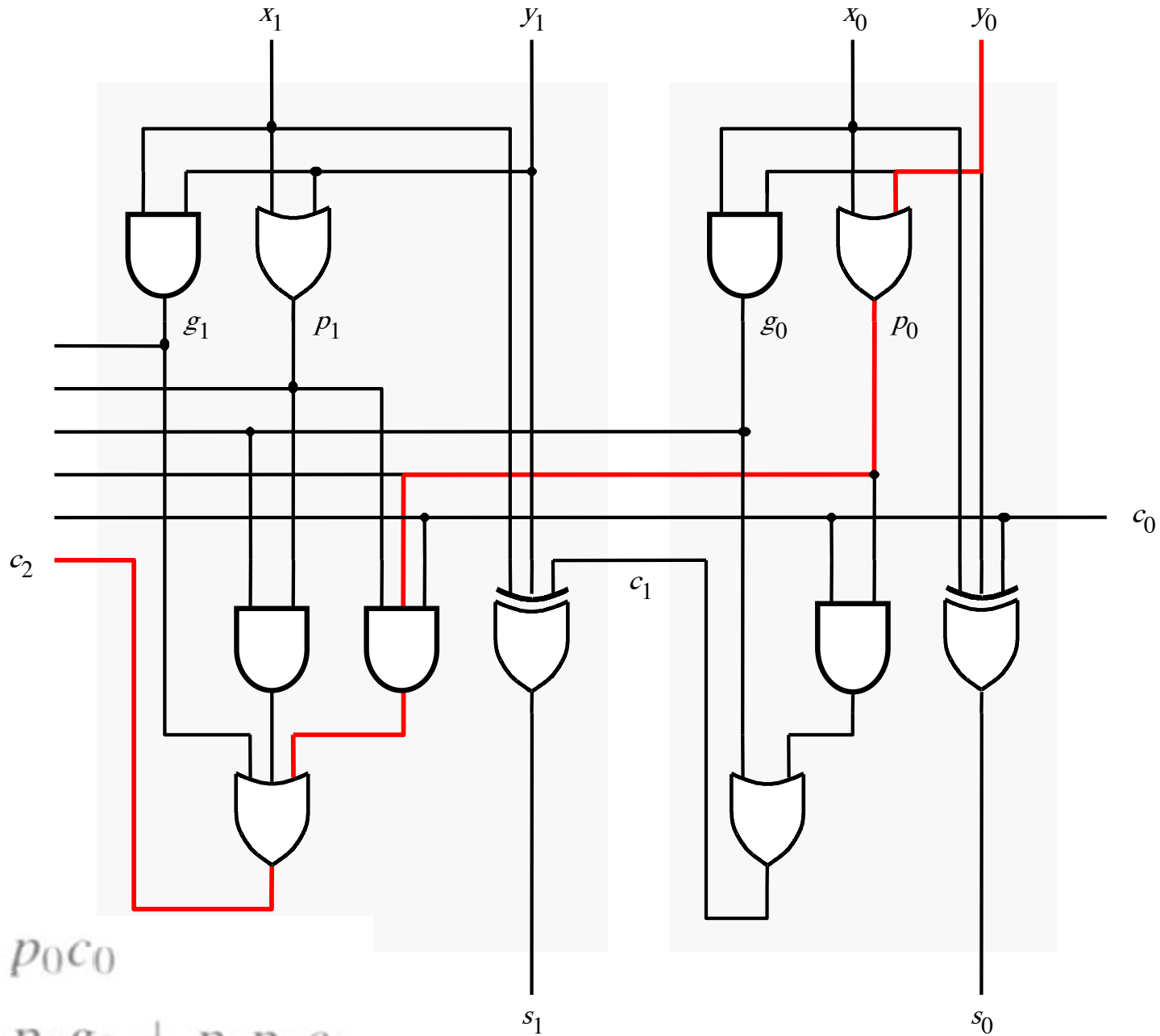


$$c_1 = g_0 + p_0 c_0$$

$$c_2 = g_1 + p_1 g_0 + p_1 p_0 c_0$$

 
The first two stages of a carry-lookahead adder



It takes 4 gate delays to generate s_1

 

It takes 4 gate delays to generate s_2

 

N-bit Carry-Lookahead Adder

- **It takes 3 gate delays to generate all carry signals**
- **It takes 1 more gate delay to generate all sum bits**
- **Thus, the total delay through an n-bit carry-lookahead adder is only 4 gate delays!**

Expanding the Carry Expression

$$c_{i+1} = g_i + p_i c_i$$

$$c_1 = g_0 + p_0 c_0$$

$$c_2 = g_1 + p_1 g_0 + p_1 p_0 c_0$$

$$c_3 = g_2 + p_2 g_1 + p_2 p_1 g_0 + p_2 p_1 p_0 c_0$$

...

$$\begin{aligned} c_8 = & g_7 + p_7 g_6 + p_7 p_6 g_5 + p_7 p_6 p_5 g_4 \\ & + p_7 p_6 p_5 p_4 g_3 + p_7 p_6 p_5 p_4 p_3 g_2 \\ & + p_7 p_6 p_5 p_4 p_3 p_2 g_1 + p_7 p_6 p_5 p_4 p_3 p_2 p_1 g_0 \\ & + p_7 p_6 p_5 p_4 p_3 p_2 p_1 p_0 c_0 \end{aligned}$$

Expanding the Carry Expression

$$c_{i+1} = g_i + p_i c_i$$

$$c_1 = g_0 + p_0 c_0$$

$$c_2 = g_1 + p_1 g_0 + p_1 p_0 c_0$$

$$c_3 = g_2 + p_2 g_1 + p_2 p_1 g_0 + p_2 p_1 p_0 c_0$$

...

$$c_8 = g_7 + p_7 g_6 + p_7 p_6 g_5 + p_7 p_6 p_5 g_4$$


Even this takes
only 3 gate delays

$$+ p_7 p_6 p_5 p_4 g_3 + p_7 p_6 p_5 p_4 p_3 g_2$$


$$+ p_7 p_6 p_5 p_4 p_3 p_2 g_1 + p_7 p_6 p_5 p_4 p_3 p_2 p_1 g_0$$

$$+ p_7 p_6 p_5 p_4 p_3 p_2 p_1 p_0 c_0$$

 
A hierarchical carry-lookahead adder with ripple-carry between blocks



 
A hierarchical carry-lookahead adder with ripple-carry between blocks



 
A hierarchical carry-lookahead adder with ripple-carry between blocks



 A hierarchical carry-lookahead adder with ripple-carry between blocks




A hierarchical carry-lookahead adder

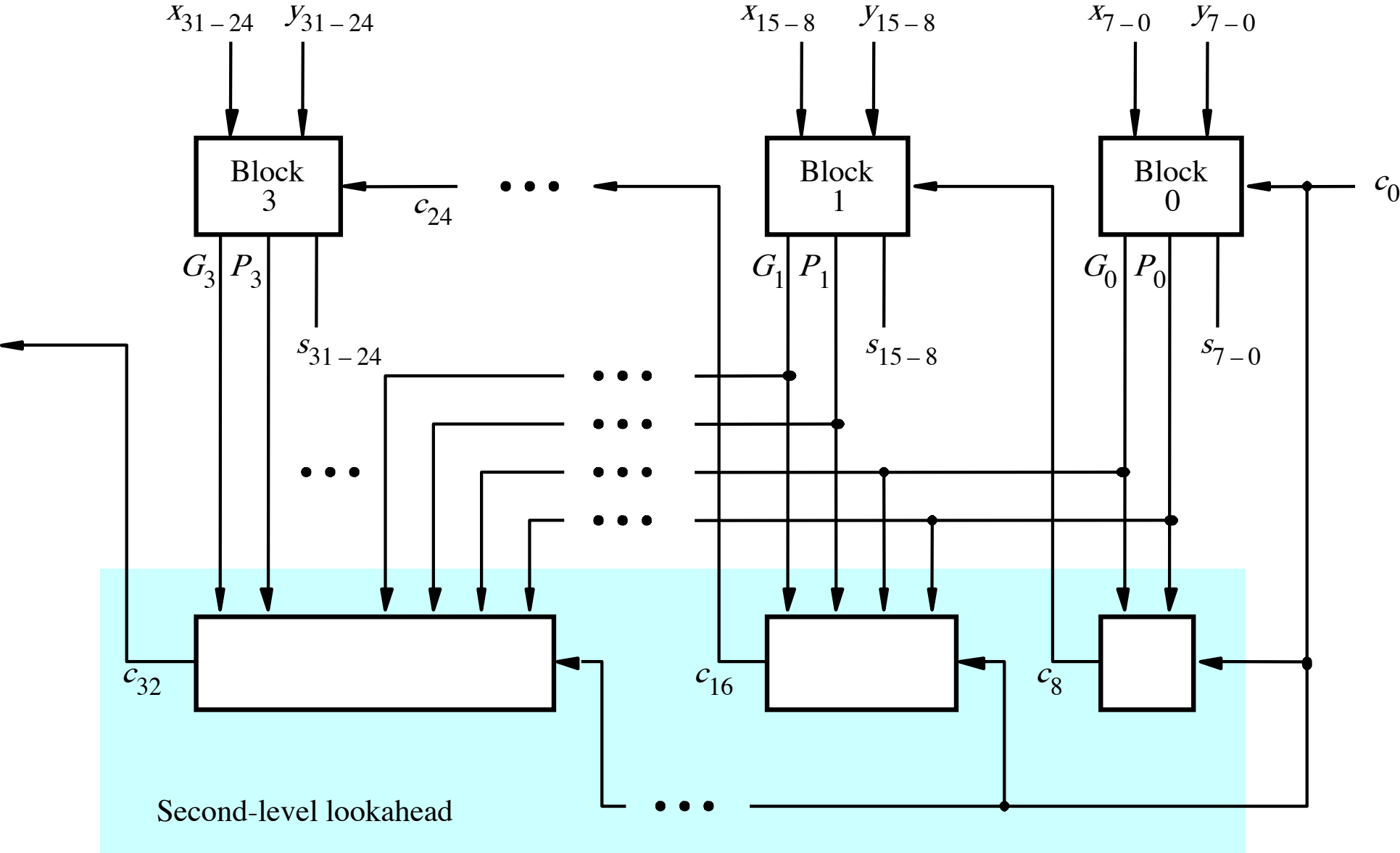


[Figure 3.17 from the textbook]

A hierarchical carry-lookahead adder

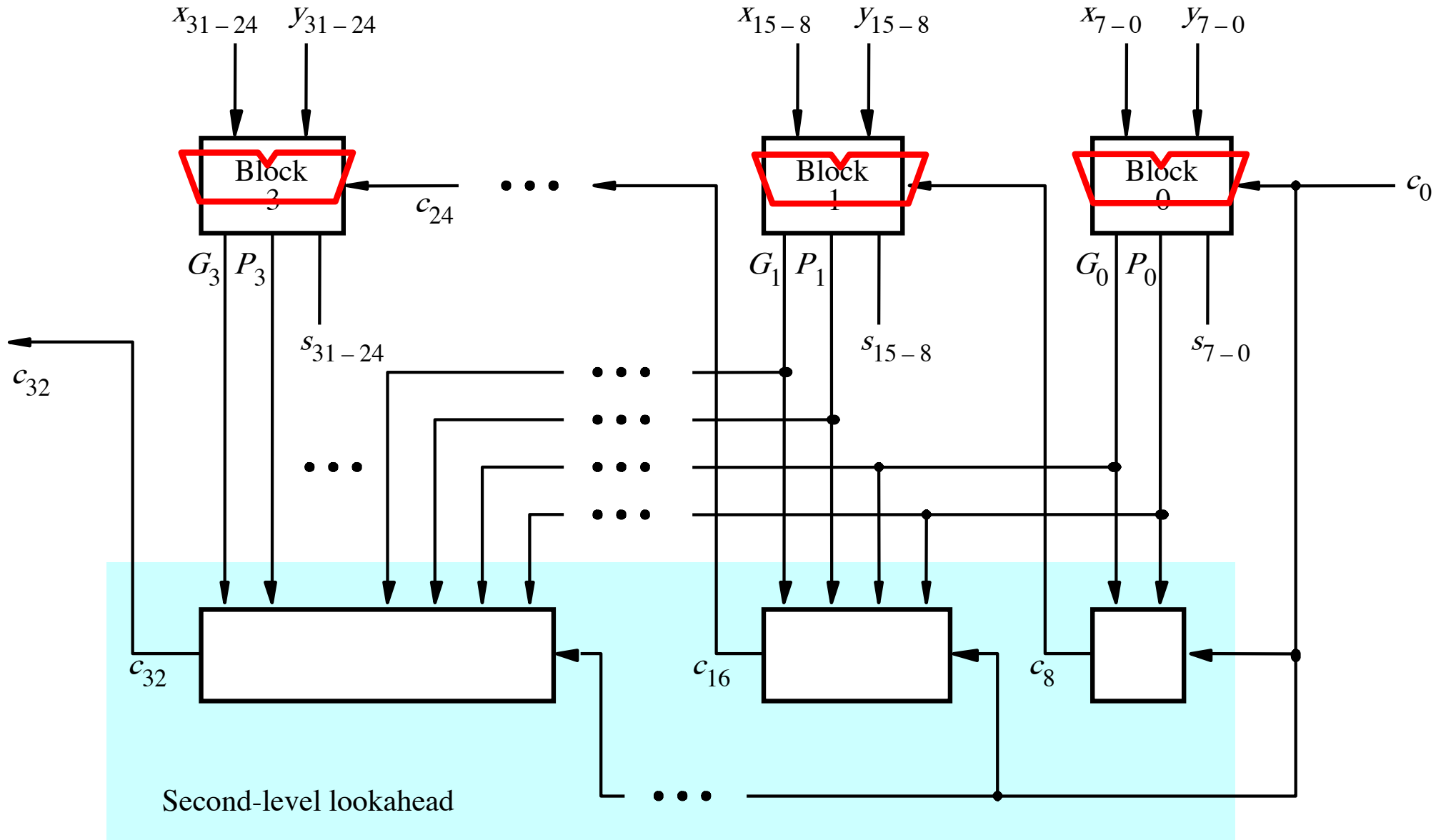

A hierarchical carry-lookahead adder

 

The Hierarchical Carry Expression

$$\begin{aligned}c_8 = & g_7 + p_7g_6 + p_7p_6g_5 + p_7p_6p_5g_4 \\ & + p_7p_6p_5p_4g_3 + p_7p_6p_5p_4p_3g_2 \\ & + p_7p_6p_5p_4p_3p_2g_1 + p_7p_6p_5p_4p_3p_2p_1g_0 \\ & + p_7p_6p_5p_4p_3p_2p_1p_0c_0\end{aligned}$$

The Hierarchical Carry Expression

$$\begin{aligned}c_8 = & g_7 + p_7g_6 + p_7p_6g_5 + p_7p_6p_5g_4 \\ & + p_7p_6p_5p_4g_3 + p_7p_6p_5p_4p_3g_2 \\ & + p_7p_6p_5p_4p_3p_2g_1 + p_7p_6p_5p_4p_3p_2p_1g_0 \\ & + p_7p_6p_5p_4p_3p_2p_1p_0c_0\end{aligned}$$

The Hierarchical Carry Expression

$$c_8 = g_7 + p_7g_6 + p_7p_6g_5 + p_7p_6p_5g_4$$
$$+ p_7p_6p_5p_4g_3 + p_7p_6p_5p_4p_3g_2$$
$$+ p_7p_6p_5p_4p_3p_2g_1 + p_7p_6p_5p_4p_3p_2p_1g_0$$
$$+ p_7p_6p_5p_4p_3p_2p_1p_0c_0$$

G_0 →

P_0 →

The Hierarchical Carry Expression

$$c_8 = g_7 + p_7g_6 + p_7p_6g_5 + p_7p_6p_5g_4 \\ + p_7p_6p_5p_4g_3 + p_7p_6p_5p_4p_3g_2 \\ + p_7p_6p_5p_4p_3p_2g_1 + p_7p_6p_5p_4p_3p_2p_1g_0 \\ + p_7p_6p_5p_4p_3p_2p_1p_0c_0$$

G_0 →

P_0 →

$$c_8 = G_0 + P_0c_0$$

The Hierarchical Carry Expression

$$\begin{aligned}c_8 = & g_7 + p_7g_6 + p_7p_6g_5 + p_7p_6p_5g_4 \\ & + p_7p_6p_5p_4g_3 + p_7p_6p_5p_4p_3g_2 \\ & + p_7p_6p_5p_4p_3p_2g_1 + p_7p_6p_5p_4p_3p_2p_1g_0 \\ & + p_7p_6p_5p_4p_3p_2p_1p_0c_0\end{aligned}$$

$$\begin{aligned}c_{16} = & g_{15} + p_{15}g_{14} + p_{15}p_{14}g_{13} + p_{15}p_{14}p_{13}g_{12} \\ & + p_{15}p_{14}p_{13}p_{12}g_{11} + p_{15}p_{14}p_{13}p_{12}p_{11}g_{10} \\ & + p_{15}p_{14}p_{13}p_{12}p_{11}p_{10}g_9 + p_{15}p_{14}p_{13}p_{12}p_{11}p_{10}p_9g_8 \\ & + p_{15}p_{14}p_{13}p_{12}p_{11}p_{10}p_9p_8c_8\end{aligned}$$

The Hierarchical Carry Expression

$$\begin{aligned}c_8 = & g_7 + p_7g_6 + p_7p_6g_5 + p_7p_6p_5g_4 \\ & + p_7p_6p_5p_4g_3 + p_7p_6p_5p_4p_3g_2 \\ & + p_7p_6p_5p_4p_3p_2g_1 + p_7p_6p_5p_4p_3p_2p_1g_0 \\ & + p_7p_6p_5p_4p_3p_2p_1p_0c_0\end{aligned}$$

The same expression, just add 8 to all subscripts

$$\begin{aligned}c_{16} = & g_{15} + p_{15}g_{14} + p_{15}p_{14}g_{13} + p_{15}p_{14}p_{13}g_{12} \\ & + p_{15}p_{14}p_{13}p_{12}g_{11} + p_{15}p_{14}p_{13}p_{12}p_{11}g_{10} \\ & + p_{15}p_{14}p_{13}p_{12}p_{11}p_{10}g_9 + p_{15}p_{14}p_{13}p_{12}p_{11}p_{10}p_9g_8 \\ & + p_{15}p_{14}p_{13}p_{12}p_{11}p_{10}p_9p_8c_8\end{aligned}$$

The Hierarchical Carry Expression

3-gate delays

$$\begin{aligned}
 c_8 = & g_7 + p_7g_6 + p_7p_6g_5 + p_7p_6p_5g_4 \\
 & + p_7p_6p_5p_4g_3 + p_7p_6p_5p_4p_3g_2 \\
 & + p_7p_6p_5p_4p_3p_2g_1 + p_7p_6p_5p_4p_3p_2p_1g_0 \\
 & + p_7p_6p_5p_4p_3p_2p_1p_0c_0
 \end{aligned}$$

G_0 points to the first four terms of the expression.

P_0 points to the term $p_7p_6p_5p_4p_3p_2p_1p_0c_0$.

2-gate delays

$$\begin{aligned}
 c_{16} = & g_{15} + p_{15}g_{14} + p_{15}p_{14}g_{13} + p_{15}p_{14}p_{13}g_{12} \\
 & + p_{15}p_{14}p_{13}p_{12}g_{11} + p_{15}p_{14}p_{13}p_{12}p_{11}g_{10} \\
 & + p_{15}p_{14}p_{13}p_{12}p_{11}p_{10}g_9 + p_{15}p_{14}p_{13}p_{12}p_{11}p_{10}p_9g_8 \\
 & + p_{15}p_{14}p_{13}p_{12}p_{11}p_{10}p_9p_8c_8
 \end{aligned}$$

The Hierarchical Carry Expression

$$\begin{aligned}
 c_8 = & g_7 + p_7g_6 + p_7p_6g_5 + p_7p_6p_5g_4 \\
 & + p_7p_6p_5p_4g_3 + p_7p_6p_5p_4p_3g_2 \\
 & + p_7p_6p_5p_4p_3p_2g_1 + p_7p_6p_5p_4p_3p_2p_1g_0 \\
 & + p_7p_6p_5p_4p_3p_2p_1p_0c_0
 \end{aligned}$$

3-gate delays

$$\begin{aligned}
 c_{16} = & g_{15} + p_{15}g_{14} + p_{15}p_{14}g_{13} + p_{15}p_{14}p_{13}g_{12} \\
 & + p_{15}p_{14}p_{13}p_{12}g_{11} + p_{15}p_{14}p_{13}p_{12}p_{11}g_{10} \\
 & + p_{15}p_{14}p_{13}p_{12}p_{11}p_{10}g_9 + p_{15}p_{14}p_{13}p_{12}p_{11}p_{10}p_9g_8 \\
 & + p_{15}p_{14}p_{13}p_{12}p_{11}p_{10}p_9p_8c_8
 \end{aligned}$$

G_1 →

P_1 →

2-gate delays

The Hierarchical Carry Expression

$$c_8 = G_0 + P_0 c_0$$

$$\begin{aligned} c_{16} &= G_1 + P_1 c_8 \\ &= G_1 + P_1 G_0 + P_1 P_0 c_0 \end{aligned}$$

$$c_{24} = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 c_0$$

$$c_{32} = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 c_0$$

The Hierarchical Carry Expression


$$c_8 = G_0 + P_0 c_0 \quad \text{4-gate delays}$$

$$\begin{aligned} c_{16} &= G_1 + P_1 c_8 && \text{5-gate delays} \\ &= G_1 + P_1 G_0 + P_1 P_0 c_0 \end{aligned}$$

$$c_{24} = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 c_0 \quad \text{5-gate delays}$$

$$c_{32} = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 c_0 \quad \text{5-gate delays}$$

A hierarchical carry-lookahead adder

 

[Figure 3.17 from the textbook]


Total Gate Delay Through a Hierarchical Carry-Lookahead Adder

- The total delay is 8 gates:
 - 3 to generate all G_i and P_i signals
 - +2 to generate c_8 , c_{16} , c_{24} , and c_{32}
 - +2 to generate internal carries in the blocks
 - +1 to generate the sum bits (one extra XOR)


Total Gate Delay Through a Hierarchical Carry-Lookahead Adder

- The total delay is 8 gates:
 - 3 to generate all G_i and P_i signals
 - +2 to generate c_8 , c_{16} , c_{24} , and c_{32}
 - +2 to generate internal carries in the blocks
 - +1 to generate the sum bits (one extra XOR)

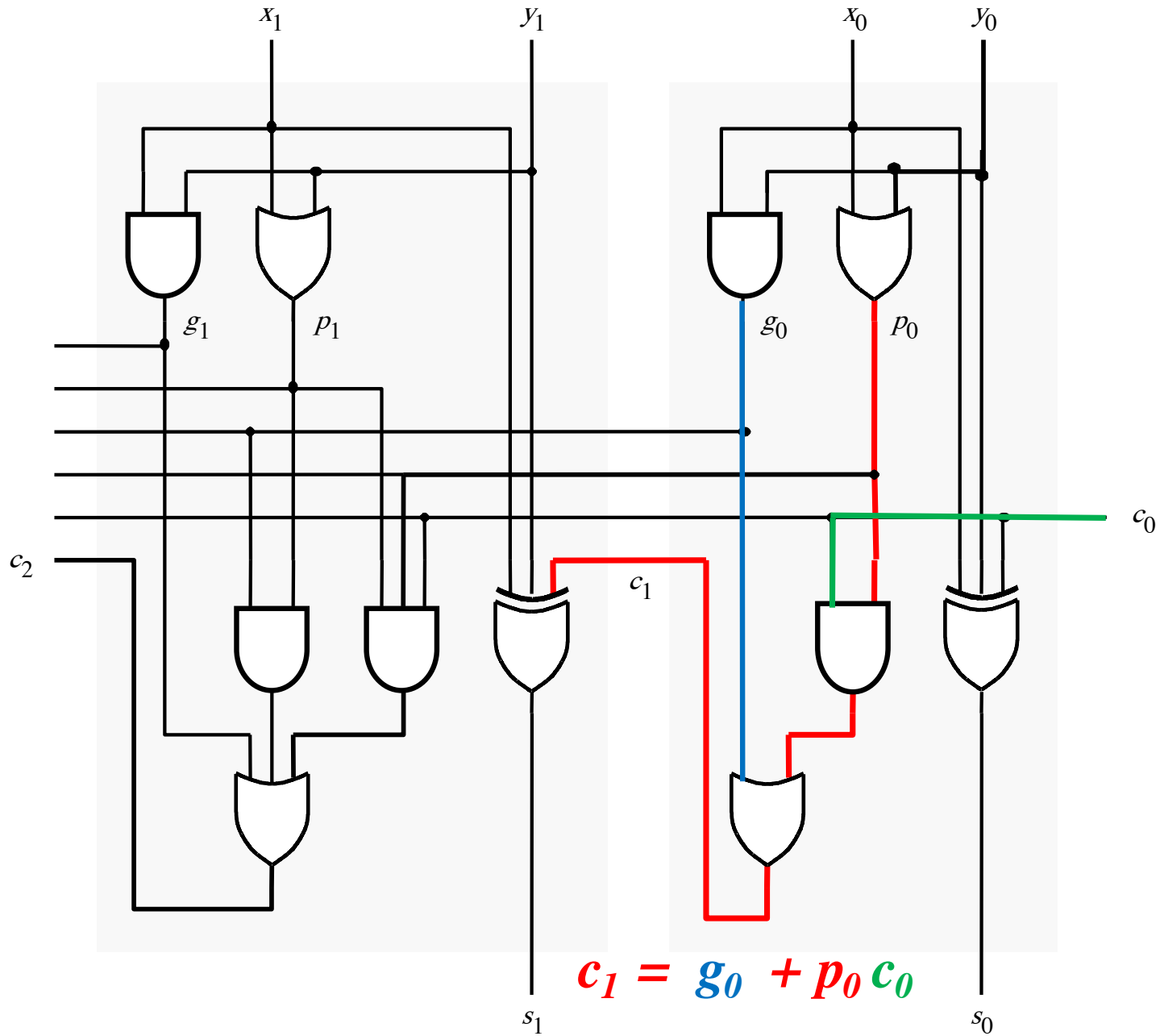2 more gate delays for the internal carries within a block




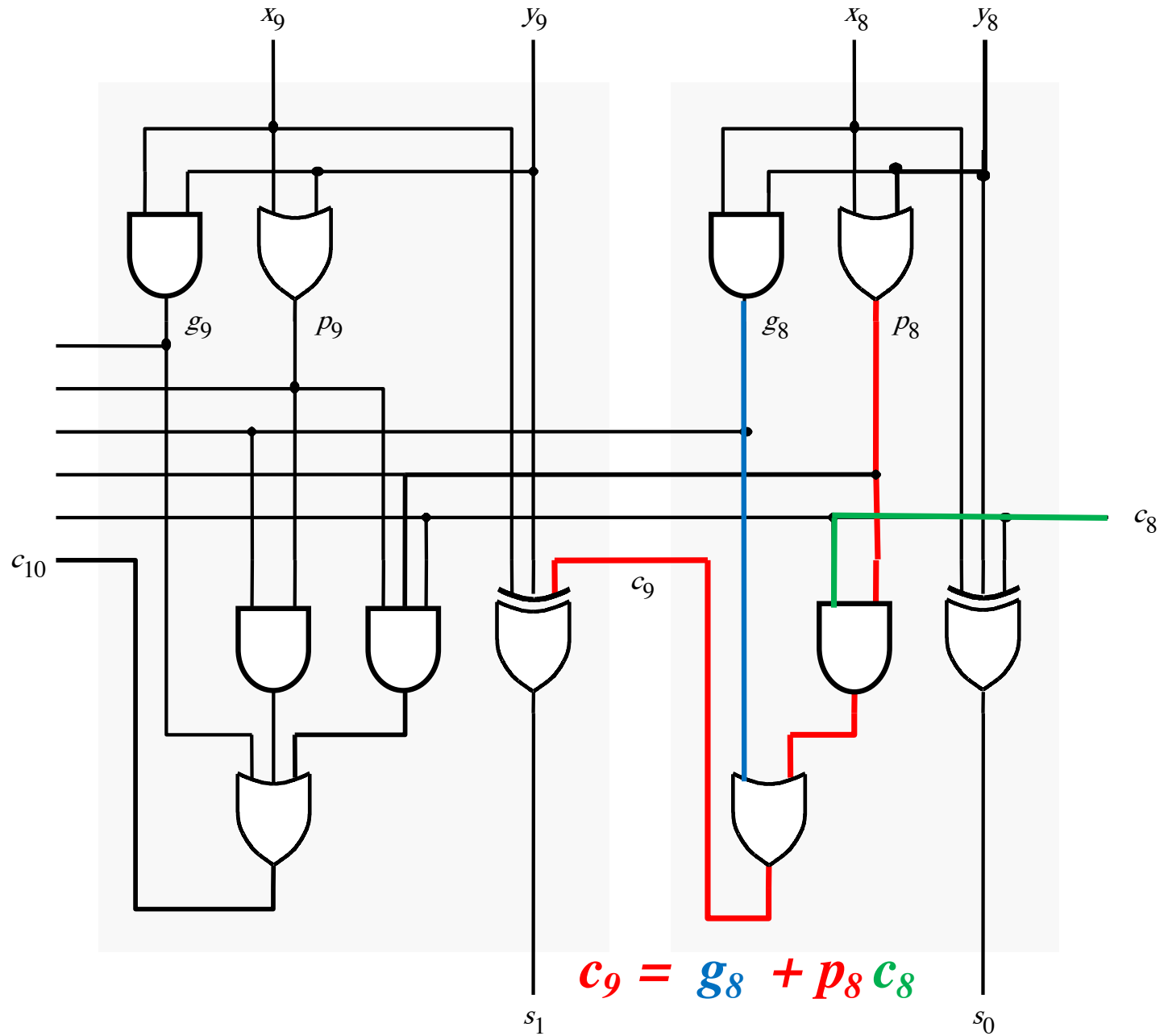
2 more gate delays for the internal carries within a block



Hierarchical CLA Adder Carry Logic

SECOND
LEVEL
HIERARCHY

 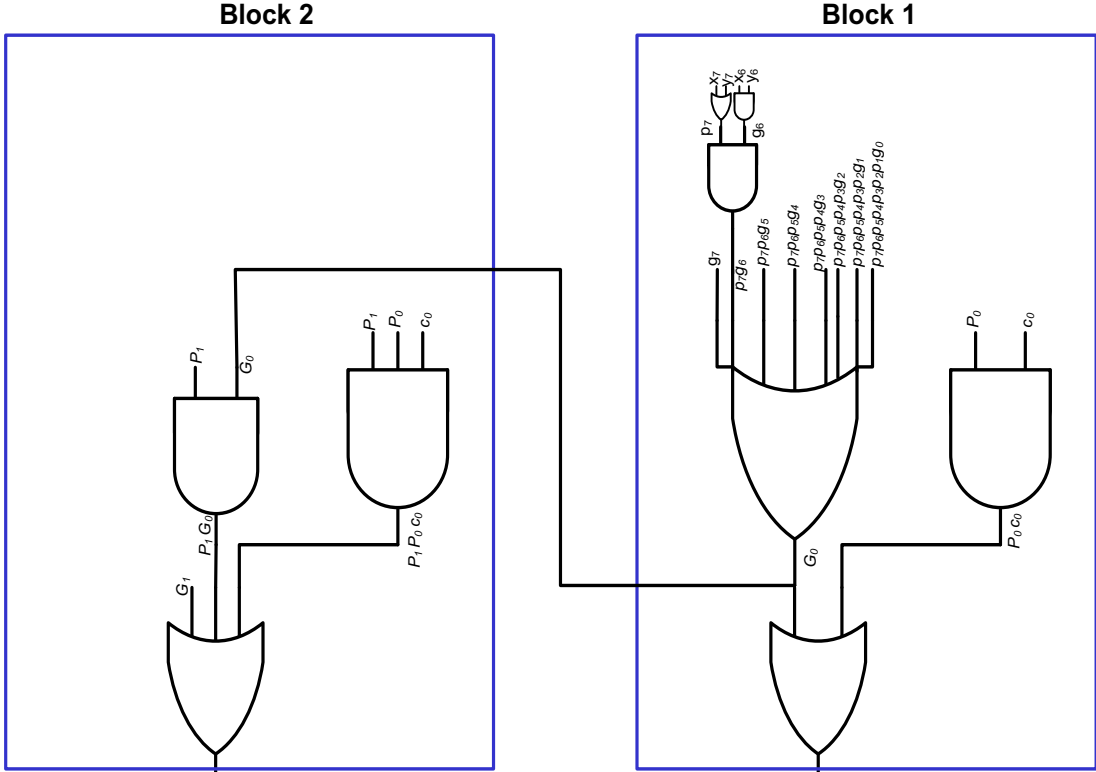- C8 – 4 gate delays
- C16 – 5 gate delays
- C24 – 5 Gate delays
- C32 – 5 Gate delays



FIRST LEVEL HIERARCHY

Hierarchical CLA Critical Path


SECOND
LEVEL
HIERARCHY

C1 - 3 gate delays

C9 - 6 gate delays

C17 - 7 gate delays

C25 - 7 Gate delays

 

FIRST LEVEL HIERARCHY

Total Gate Delay Through a Hierarchical Carry-Lookahead Adder

- The total delay is **8 gates**:
 - 3 to generate all G_i and P_i signals
 - +2 to generate c_8 , c_{16} , c_{24} , and c_{32}
 - +2 to generate internal carries in the blocks
 - +1 to generate the sum bits (one extra XOR)

Multiplication and division by 10 in the decimal system

Decimal Multiplication by 10

What happens when we multiply a number by 10?

$$4 \times 10 = ?$$

$$542 \times 10 = ?$$

$$1245 \times 10 = ?$$

Decimal Multiplication by 10

What happens when we multiply a number by 10?

$$4 \times 10 = 40$$

$$542 \times 10 = 5420$$

$$1245 \times 10 = 12450$$

Decimal Multiplication by 10

What happens when we multiply a number by 10?

$$4 \times 10 = 40$$

$$542 \times 10 = 5420$$

$$1245 \times 10 = 12450$$

You simply add a zero as the rightmost number

Decimal Division by 10

What happens when we divide a number by 10?

$$14 / 10 = ?$$

$$540 / 10 = ?$$

$$1240 / 10 = ?$$

Decimal Division by 10

What happens when we divide a number by 10?

$$14 / 10 = 1 \quad //\text{integer division}$$

$$540 / 10 = 54$$

$$1240 / 10 = 124$$

You simply delete the rightmost number

Multiplication and division by 2 in the binary system

Binary Multiplication by 2

What happens when we multiply a number by 2?

011 times 2 = ?

101 times 2 = ?

110011 times 2 = ?

Binary Multiplication by 2

What happens when we multiply a number by 2?

$$011 \text{ times } 2 = 0110$$

$$101 \text{ times } 2 = 1010$$

$$110011 \text{ times } 2 = 1100110$$

You simply add a zero as the rightmost number

Binary Multiplication by 4

What happens when we multiply a number by 4?

011 times 4 = ?

101 times 4 = ?

110011 times 4 = ?

Binary Multiplication by 4

What happens when we multiply a number by 4?

$$011 \text{ times } 4 = 01100$$

$$101 \text{ times } 4 = 10100$$

$$110011 \text{ times } 4 = 11001100$$

add two zeros in the last two bits and shift everything else to the left

Binary Multiplication by 2^N

What happens when we multiply a number by 2^N ?

011 times $2^N = 01100\dots0$ // add N zeros

101 times 4 = 10100...0 // add N zeros

110011 times 4 = 11001100...0 // add N zeros

Binary Division by 2

What happens when we divide a number by 2?

0110 divided by 2 = ?

1010 divides by 2 = ?

110011 divides by 2 = ?

Binary Division by 2

What happens when we divide a number by 2?

0110 divided by 2 = 011

1010 divides by 2 = 101

110011 divides by 2 = 11001

You simply delete the rightmost number

Multiplication of two unsigned binary numbers

Decimal Multiplication By Hand

$$\begin{array}{r} 5127 \\ \times 4265 \\ \hline 25635 \\ 307620 \\ 1025400 \\ 20508000 \\ \hline 21866655 \end{array}$$

Binary Multiplication By Hand

Multiplicand M	(14)	1 1 1 0
Multiplier Q	(11)	x 1 0 1 1
		<hr/>
		1 1 1 0
		1 1 1 0
		0 0 0 0
		1 1 1 0
		<hr/>
Product P	(154)	1 0 0 1 1 0 1 0

Binary Multiplication By Hand

Multiplicand M	(14)	1 1 1 0
Multiplier Q	(11)	× 1 0 1 1
		<hr/>
Partial product 0		1 1 1 0
		+ 1 1 1 0
		<hr/>
Partial product 1		1 0 1 0 1
		+ 0 0 0 0
		<hr/>
Partial product 2		0 1 0 1 0
		+ 1 1 1 0
		<hr/>
Product P	(154)	1 0 0 1 1 0 1 0

[Figure 3.34b from the textbook]

Binary Multiplication By Hand

					m_3	m_2	m_1	m_0	
					q_3	q_2	q_1	q_0	
					<hr/>				
Partial product 0					m_3q_0	m_2q_0	m_1q_0	m_0q_0	
					$+ m_3q_1$	m_2q_1	m_1q_1	m_0q_1	
					<hr/>				
Partial product 1					$PP1_5$	$PP1_4$	$PP1_3$	$PP1_2$	$PP1_1$
					$+ m_3q_2$	m_2q_2	m_1q_2	m_0q_2	
					<hr/>				
Partial product 2					$PP2_6$	$PP2_5$	$PP2_4$	$PP2_3$	$PP2_2$
					$+ m_3q_3$	m_2q_3	m_1q_3	m_0q_3	
					<hr/>				
Product P	p_7	p_6	p_5	p_4	p_3	p_2	p_1	p_0	

[Figure 3.34c from the textbook]

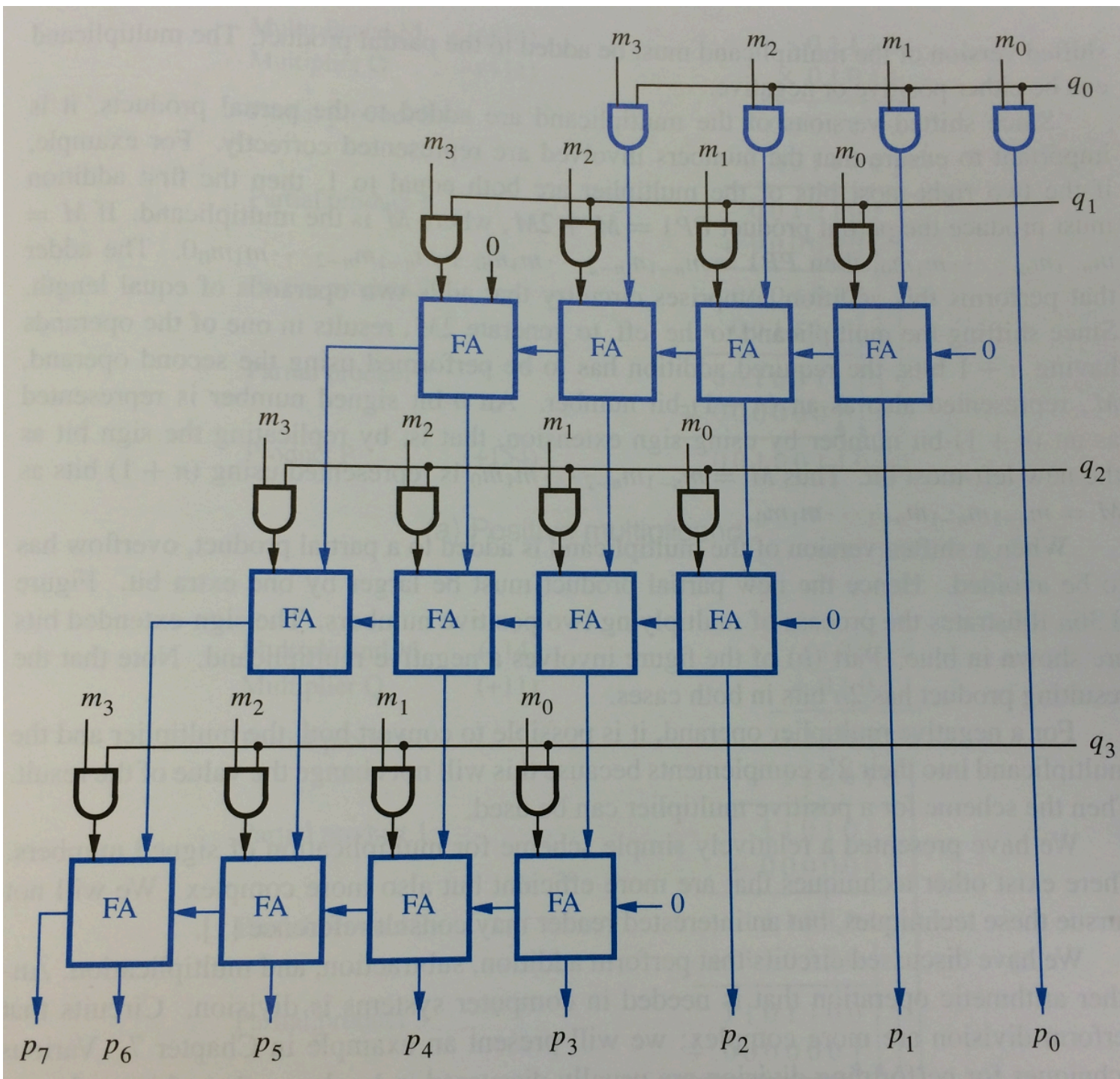


Figure 3.35. A 4x4 multiplier circuit.

Sign Extension

Sign extension for positive numbers

- If we want to represent the same positive number with more bits, we simply pad it on the left with zeros.

- For example:

0110	(+6 with 4-bits)
00110	(+6 with 5-bits)
000110	(+6 with 6-bits)

Sign extension for negative numbers

- If we want to represent the same negative number with more bits, we simply pad it on the left with ones.

- For example:

1011	(-5 with 4-bits)
11011	(-5 with 5-bits)
111011	(-5 with 6-bits)

Multiplication of two **signed** binary numbers

Positive Multiplicand Example

Multiplicand M	(+14)	0 1 1 1 0
Multiplier Q	(+11)	x 0 1 0 1 1
		<hr style="width: 20%; margin-left: auto; margin-right: 0;"/>
Partial product 0		0 0 0 1 1 1 0
		+ 0 0 1 1 1 0
		<hr style="width: 20%; margin-left: auto; margin-right: 0;"/>
Partial product 1		0 0 1 0 1 0 1
		+ 0 0 0 0 0 0
		<hr style="width: 20%; margin-left: auto; margin-right: 0;"/>
Partial product 2		0 0 0 1 0 1 0
		+ 0 0 1 1 1 0
		<hr style="width: 20%; margin-left: auto; margin-right: 0;"/>
Partial product 3		0 0 1 0 0 1 1
		+ 0 0 0 0 0 0
		<hr style="width: 20%; margin-left: auto; margin-right: 0;"/>
Product P	(+154)	0 0 1 0 0 1 1 0 1 0

[Figure 3.36a in the textbook]

Positive Multiplicand Example

Multiplicand M	(+14)		0 1 1 1 0
Multiplier Q	(+11)		x 0 1 0 1 1
Partial product 0			0 0 0 1 1 1 0
		add an extra bit to avoid overflow	+ 0 0 1 1 1 0
Partial product 1			0 0 1 0 1 0 1
			+ 0 0 0 0 0 0
Partial product 2			0 0 0 1 0 1 0
			+ 0 0 1 1 1 0
Partial product 3			0 0 1 0 0 1 1
			+ 0 0 0 0 0 0
Product P	(+154)		0 0 1 0 0 1 1 0 1 0

[Figure 3.36a in the textbook]

Negative Multiplicand Example

Multiplicand M (-14)

Multiplier Q (+11)


Partial product 0

Partial product 1

Partial product 2

Partial product 3

Product P (-154)

 

[Figure 3.36b in the textbook]

Negative Multiplicand Example

Multiplicand M	(-14)		1 0 0 1 0
Multiplier Q	(+11)		× 0 1 0 1 1
Partial product 0		add an extra bit to avoid overflow but now it is 1	$\begin{array}{r} 1110010 \\ + 110010 \\ \hline \end{array}$
Partial product 1			$\begin{array}{r} 1101011 \\ + 000000 \\ \hline \end{array}$
Partial product 2			$\begin{array}{r} 1110101 \\ + 110010 \\ \hline \end{array}$
Partial product 3			$\begin{array}{r} 1101100 \\ + 000000 \\ \hline \end{array}$
Product P	(-154)		1 1 0 1 1 0 0 1 1 0

[Figure 3.36b in the textbook]

What if the Multiplier is Negative?

- **Negate both numbers.**
- **This will make the multiplier positive.**
- **Then proceed as normal.**
- **This will not affect the result.**
- **Example: $5*(-4) = (-5)*(4) = -20$**


Arithmetic Comparison Circuits

Truth table for a one-bit digital comparator

Inputs		Outputs		
A	B	$A > B$	$A = B$	$A < B$
0	0	0	1	0
0	1	0	0	1
1	0	1	0	0
1	1	0	1	0

A one-bit digital comparator circuit


Inputs		Outputs		
A	B	$A > B$	$A = B$	$A < B$
0	0	0	1	0
0	1	0	0	1
1	0	1	0	0
1	1	0	1	0

 


Truth table for a two-bit digital comparator

Inputs				Outputs		
A_1	A_0	B_1	B_0	$A < B$	$A = B$	$A > B$
0	0	0	0	0	1	0
0	0	0	1	1	0	0
0	0	1	0	1	0	0
0	0	1	1	1	0	0
0	1	0	0	0	0	1
0	1	0	1	0	1	0
0	1	1	0	1	0	0
0	1	1	1	1	0	0
1	0	0	0	0	0	1
1	0	0	1	0	0	1
1	0	1	0	0	1	0
1	0	1	1	1	0	0
1	1	0	0	0	0	1
1	1	0	1	0	0	1
1	1	1	0	0	0	1
1	1	1	1	0	1	0

A two-bit digital comparator circuit

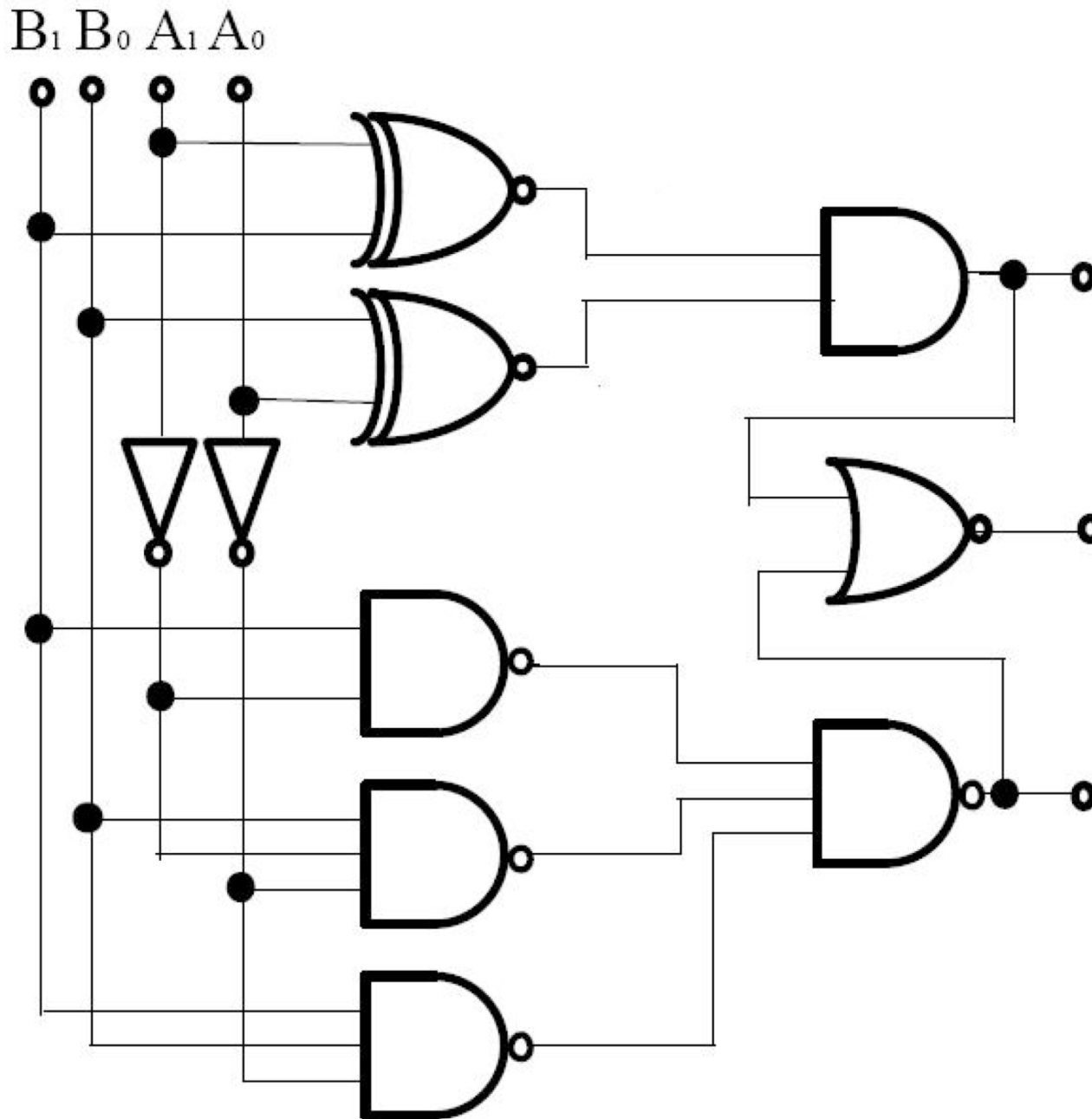


A four-bit comparator circuit

 


[Figure 4.22 from the textbook]

Another four-bit comparator circuit

 


[Figure 3.45 from the textbook]

Another four-bit comparator circuit

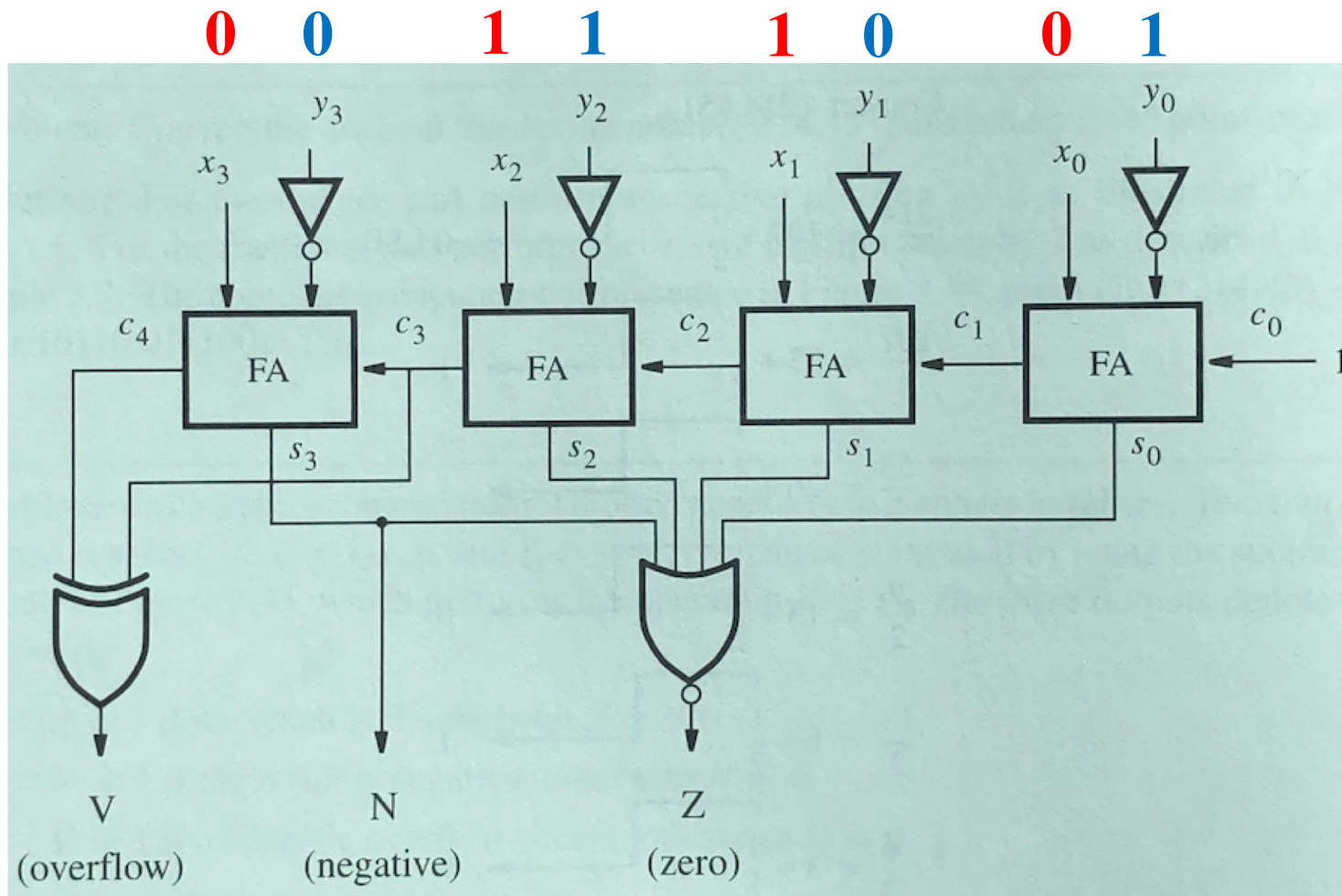


Compare 6 with 5 by subtraction (6-5).


Another four-bit comparator circuit

 


Another four-bit comparator circuit

 

Another four-bit comparator circuit

 

Another four-bit comparator circuit

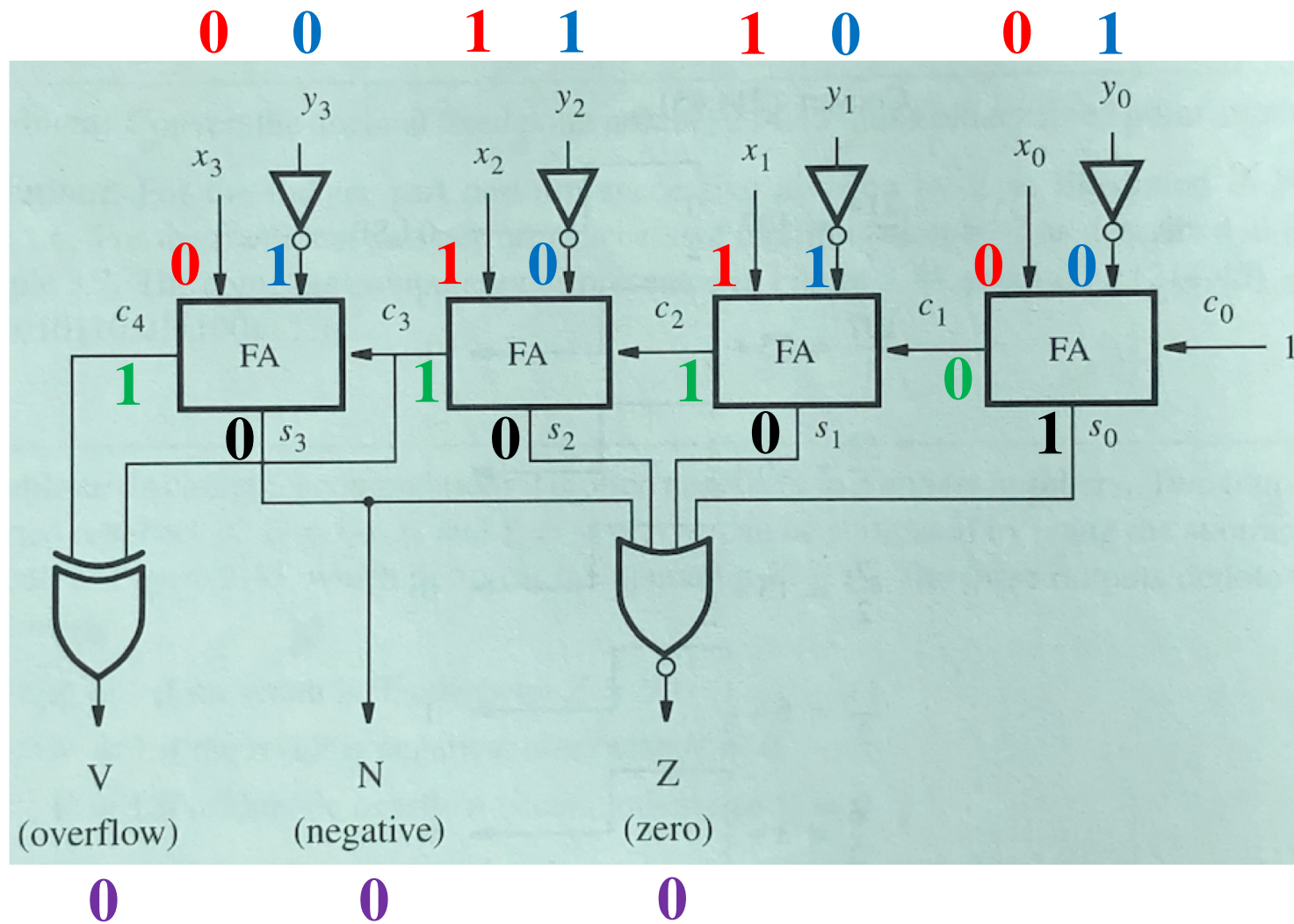

Binary Coded Decimal (BCD)

Table of Binary-Coded Decimal Digits

Decimal digit	BCD code
0	0000
1	0001
2	0010
3	0011
4	0100
5	0101
6	0110
7	0111
8	1000
9	1001

Addition of BCD digits

$$\begin{array}{r} X \\ + Y \\ \hline Z \end{array} \qquad \begin{array}{r} 0111 \\ + 0101 \\ \hline 1100 \end{array} \qquad \begin{array}{r} 7 \\ + 5 \\ \hline 12 \end{array}$$

Addition of BCD digits

$$\begin{array}{r} X \\ + Y \\ \hline Z \end{array} \qquad \begin{array}{r} 0111 \\ + 0101 \\ \hline 1100 \end{array} \qquad \begin{array}{r} 7 \\ + 5 \\ \hline 12 \end{array}$$

The result is greater than 9, which is not a valid BCD number

Addition of BCD digits

$$\begin{array}{r} X \\ + Y \\ \hline Z \end{array} \quad \begin{array}{r} 0111 \\ + 0101 \\ \hline 1100 \\ + 0110 \\ \hline 10010 \end{array} \quad \begin{array}{r} 7 \\ + 5 \\ \hline 12 \end{array}$$

carry \rightarrow 10010

$S = 2$


add 6 \leftarrow

Addition of BCD digits

X	1 0 0 0	8
+ Y	+ 1 0 0 1	+ 9
<hr/>	<hr/>	<hr/>
Z	1 0 0 0 1	17

Addition of BCD digits

X	1 0 0 0	8
+ Y	+ 1 0 0 1	+ 9
<hr/>	<hr/>	<hr/>
Z	1 0 0 0 1	17



The result is 1, but it should be 7

Addition of BCD digits

X	1 0 0 0	8
+ Y	+ 1 0 0 1	+ 9
<hr/>		
Z	1 0 0 0 1	17
	+ 0 1 1 0	
	<hr/>	
carry →	1 0 1 1 1	
	$\underbrace{\hspace{2em}}$	
	S = 7	

← add 6

Why add 6?

- **Think of BCD addition as a mod 16 operation**
- **Decimal addition is mod 10 operation**


BCD Arithmetic Rules

$$Z = X + Y$$

If $Z \leq 9$, then $S=Z$ and carry-out = 0

If $Z > 9$, then $S=Z+6$ and carry-out = 1

Block diagram for a one-digit BCD adder

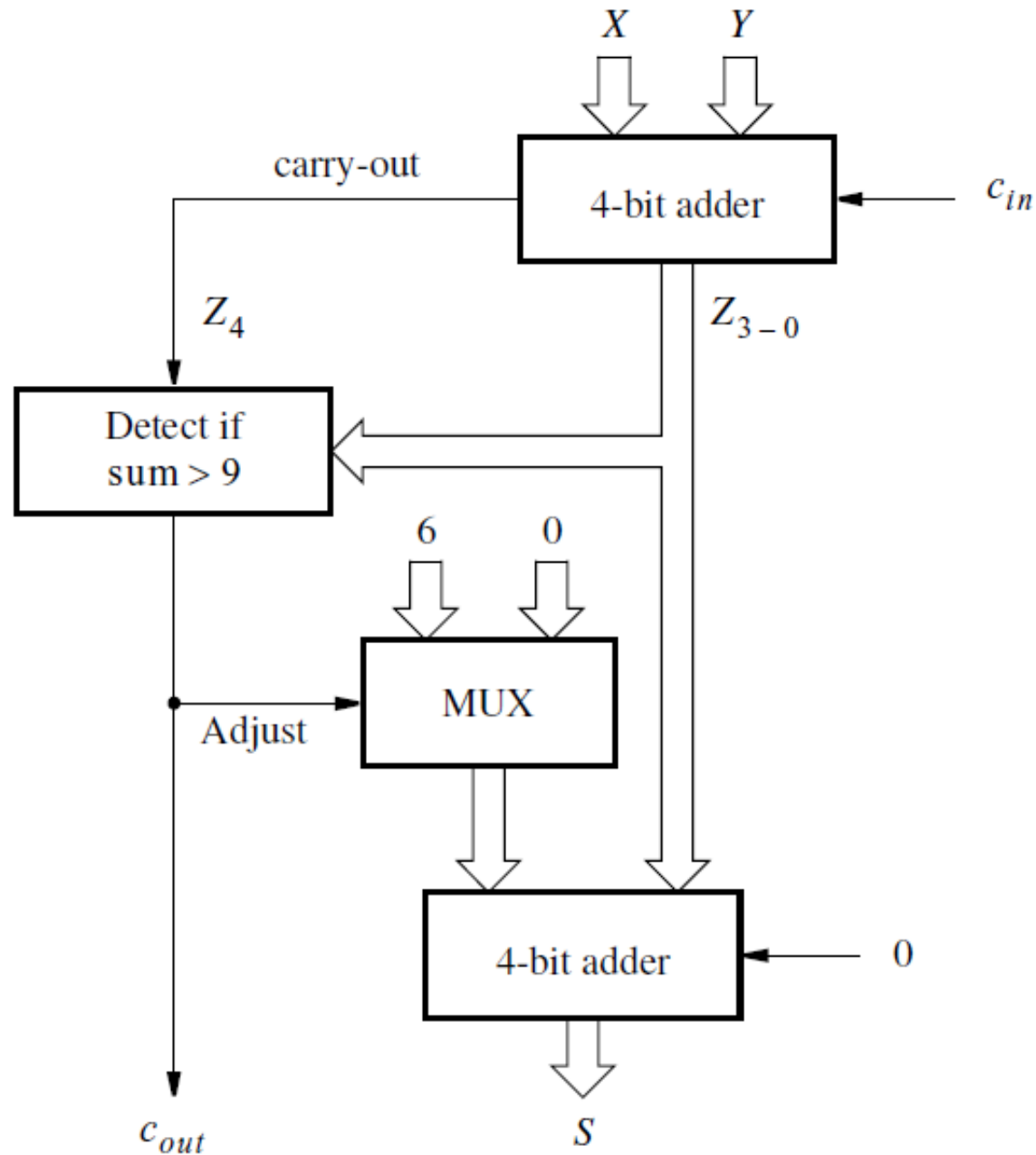

[Figure 3.39 in the textbook]

How to check if the number is > 9 ?

7 - 0111

8 - 1000

9 - 1001

10 - 1010

11 - 1011

12 - 1100


13 - 1101

14 - 1110

15 - 1111

A four-variable Karnaugh map

x1	x2	x3	x4		
0	0	0	0	m0	0
0	0	0	1	m1	0
0	0	1	0	m2	0
0	0	1	1	m3	0
0	1	0	0	m4	0
0	1	0	1	m5	0
0	1	1	0	m6	0
0	1	1	1	m7	0
1	0	0	0	m8	0
1	0	0	1	m9	0
1	0	1	0	m10	1
1	0	1	1	m11	1
1	1	0	0	m12	1
1	1	0	1	m13	1
1	1	1	0	m14	1
1	1	1	1	m15	1

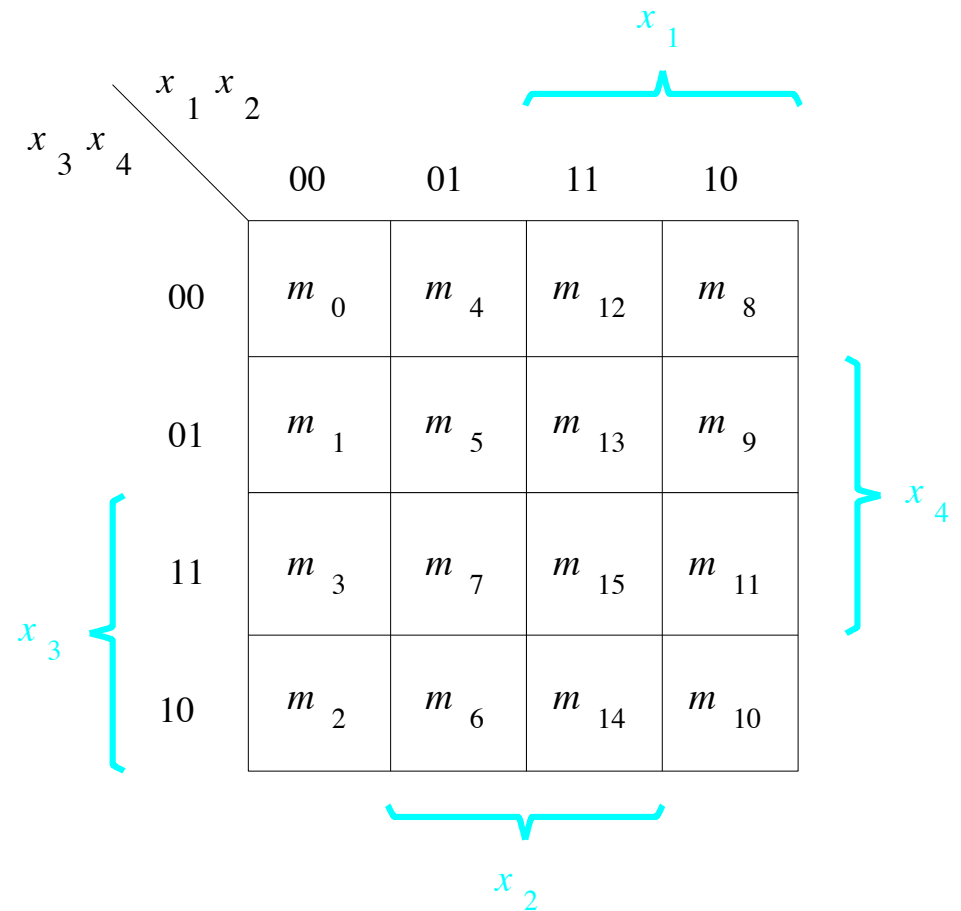

How to check if the number is > 9 ?

z3	z2	z1	z0		
0	0	0	0	m0	0
0	0	0	1	m1	0
0	0	1	0	m2	0
0	0	1	1	m3	0
0	1	0	0	m4	0
0	1	0	1	m5	0
0	1	1	0	m6	0
0	1	1	1	m7	0
1	0	0	0	m8	0
1	0	0	1	m9	0
1	0	1	0	m10	1
1	0	1	1	m11	1
1	1	0	0	m12	1
1	1	0	1	m13	1
1	1	1	0	m14	1
1	1	1	1	m15	1

		$z_3 z_2$			
		00	01	11	10
$z_1 z_0$	00	0	0	1	0
	01	0	0	1	0
	11	0	0	1	1
	10	0	0	1	1

How to check if the number is > 9 ?

z3	z2	z1	z0		
0	0	0	0	m0	0
0	0	0	1	m1	0
0	0	1	0	m2	0
0	0	1	1	m3	0
<hr/>					
0	1	0	0	m4	0
0	1	0	1	m5	0
0	1	1	0	m6	0
0	1	1	1	m7	0
<hr/>					
1	0	0	0	m8	0
1	0	0	1	m9	0
1	0	1	0	m10	1
1	0	1	1	m11	1
<hr/>					
1	1	0	0	m12	1
1	1	0	1	m13	1
1	1	1	0	m14	1
1	1	1	1	m15	1

		$z_3 z_2$			
		00	01	11	10
$z_1 z_0$	00	0	0	1	0
	01	0	0	1	0
	11	0	0	1	1
	10	0	0	1	1

$$f = z_3 z_2 + z_3 z_1$$

How to check if the number is > 9 ?

z3	z2	z1	z0		
0	0	0	0	m0	0
0	0	0	1	m1	0
0	0	1	0	m2	0
0	0	1	1	m3	0
<hr/>					
0	1	0	0	m4	0
0	1	0	1	m5	0
0	1	1	0	m6	0
0	1	1	1	m7	0
<hr/>					
1	0	0	0	m8	0
1	0	0	1	m9	0
1	0	1	0	m10	1
1	0	1	1	m11	1
<hr/>					
1	1	0	0	m12	1
1	1	0	1	m13	1
1	1	1	0	m14	1
1	1	1	1	m15	1

		$z_3 z_2$			
		00	01	11	10
$z_1 z_0$	00	0	0	1	0
	01	0	0	1	0
	11	0	0	1	1
	10	0	0	1	1

$$f = z_3 z_2 + z_3 z_1$$


In addition, also check if there was a carry

$$f = \text{carry-out} + z_3 z_2 + z_3 z_1$$

Verilog code for a one-digit BCD adder


```
module bcdadd(Cin, X, Y, S, Cout);  
    input Cin;  
    input [3:0] X, Y;  
    output reg [3:0] S;  
    output reg Cout;  
    reg [4:0] Z;  
  
    always@ (X, Y, Cin)  
    begin  
        Z = X + Y + Cin;  
        if (Z < 10)  
            {Cout, S} = Z;  
        else  
            {Cout, S} = Z + 6;  
    end  
  
endmodule
```

Circuit for a one-digit BCD adder

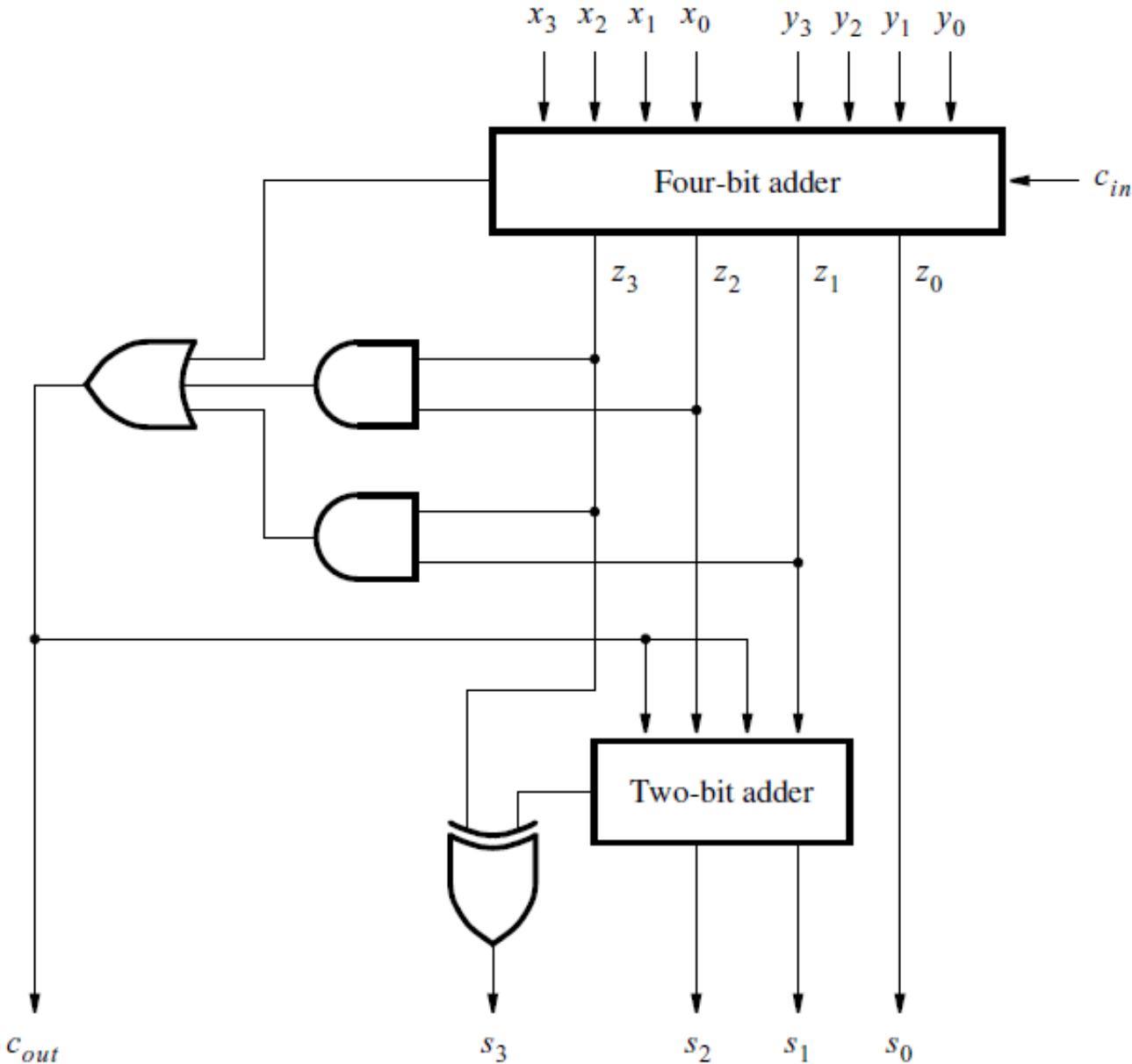


[Figure 3.41 in the textbook]

Circuit for a one-digit BCD adder

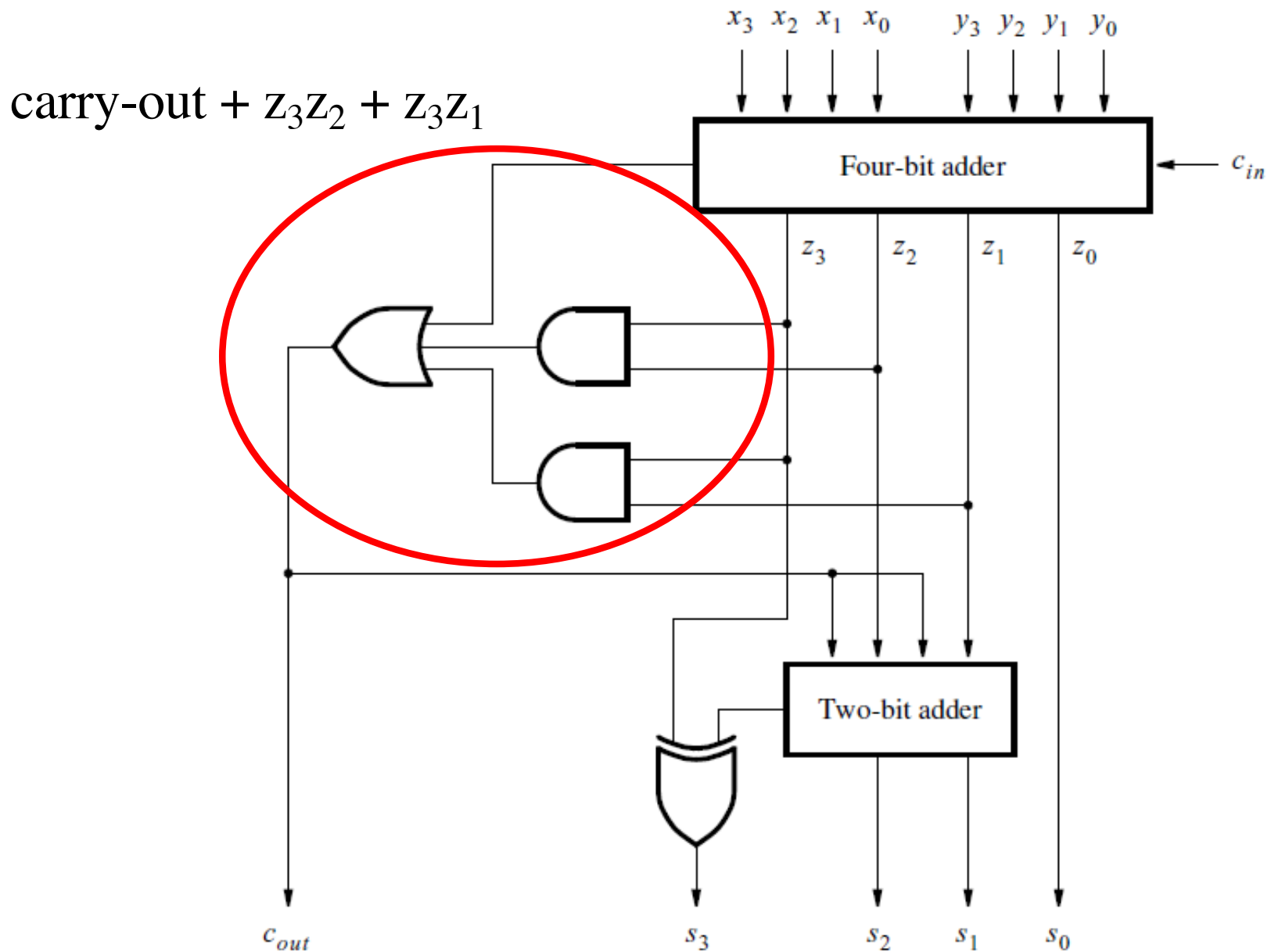


[Figure 3.41 in the textbook]

Circuit for a one-digit BCD adder

 


[Figure 3.41 in the textbook]

Circuit for a one-digit BCD adder

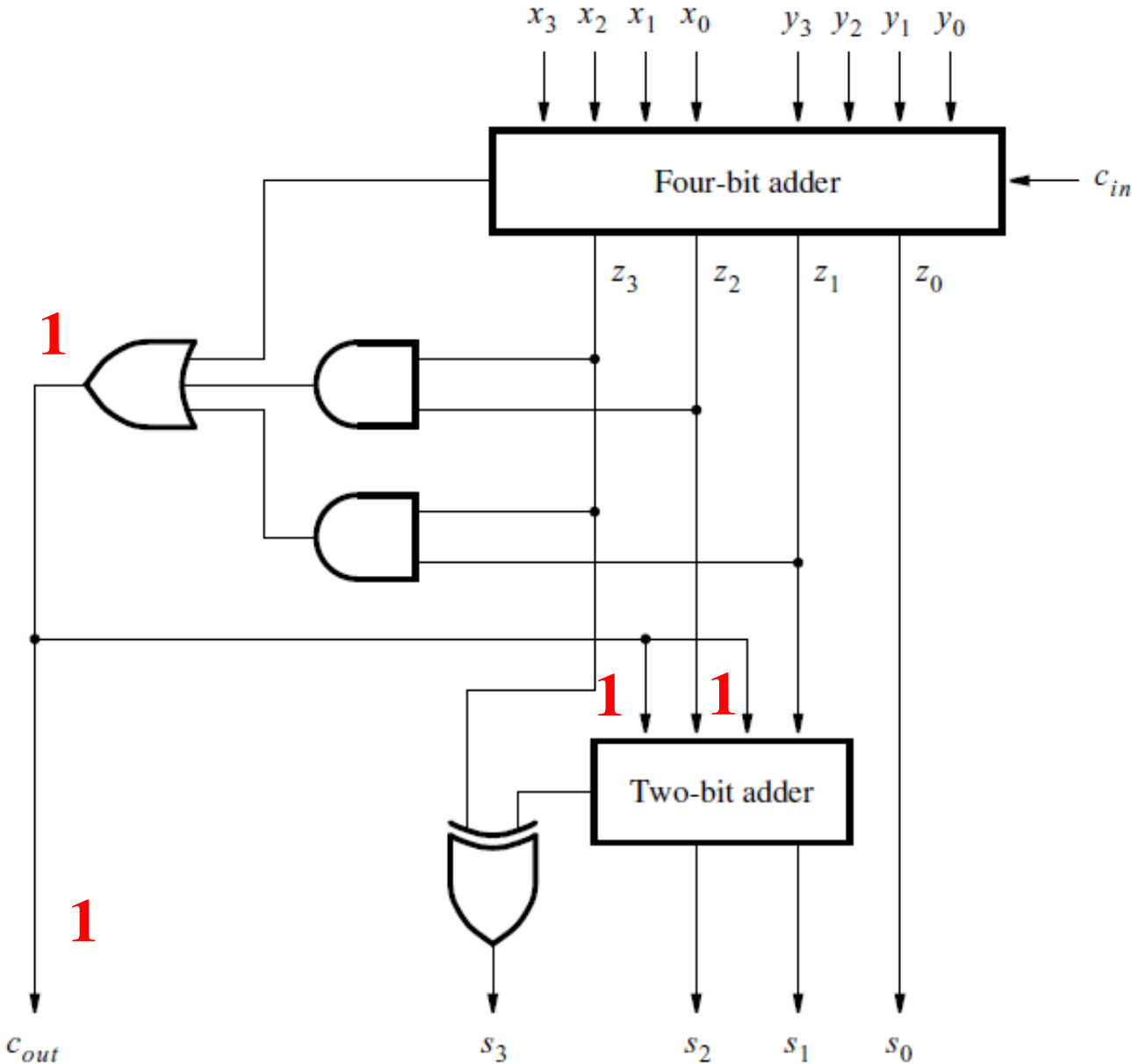


[Figure 3.41 in the textbook]

Circuit for a one-digit BCD adder

 


[Figure 3.41 in the textbook]

Circuit for a one-digit BCD adder

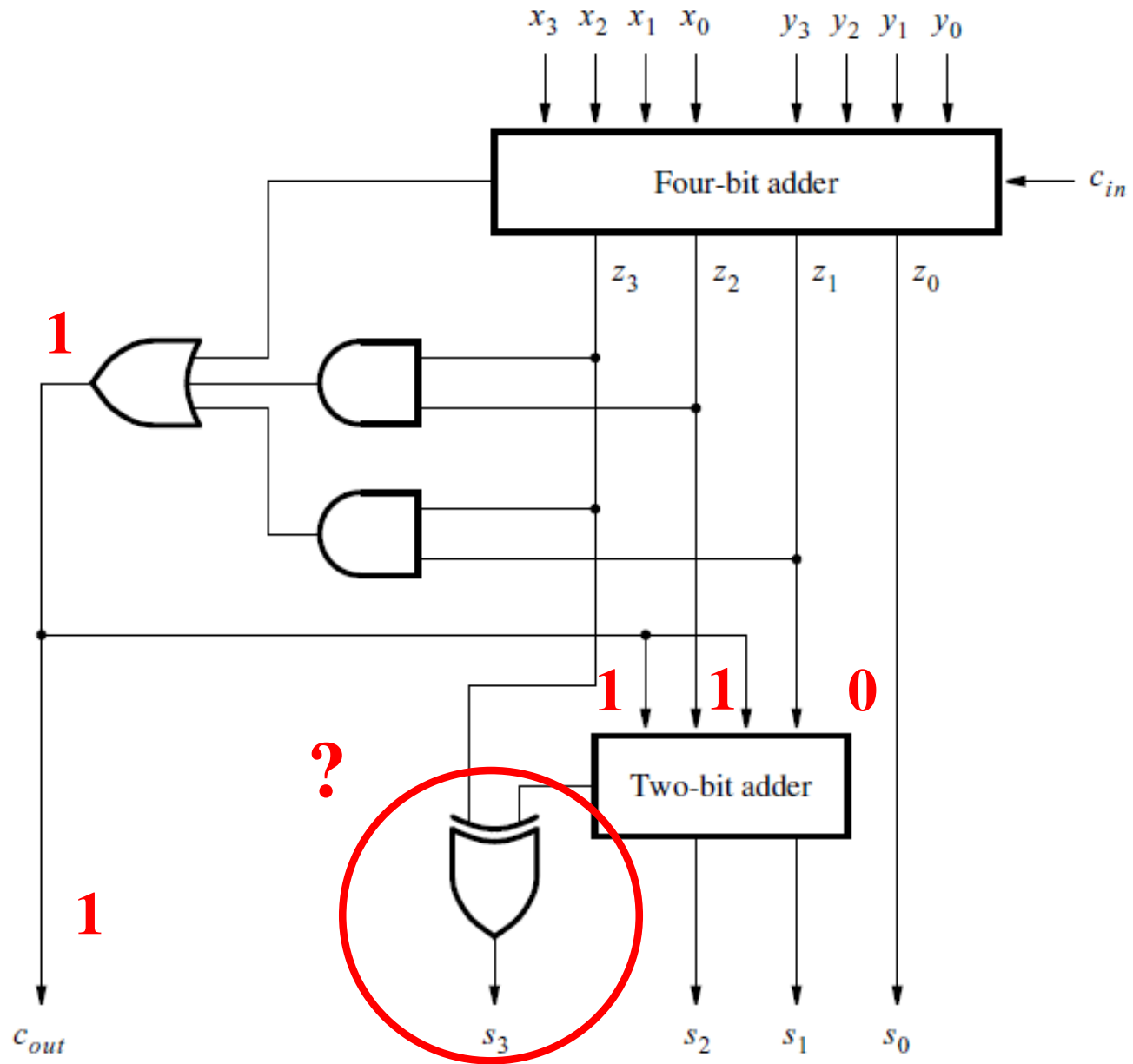


[Figure 3.41 in the textbook]

 
Simplification of the Full-Adder circuit when $x_i=0$



 
Simplification of the Full-Adder circuit when $x_i=0$



 
Simplification of the Full-Adder circuit when $x_i=0$



 
Simplification of the Full-Adder circuit when $x_i=0$



 
Simplification of the Full-Adder circuit when $x_i=0$



 Simplification of the Full-Adder circuit when $x_i=0$




 Simplification of the Full-Adder circuit when $x_i=0$




It reduces to a half-adder.

 Simplification of the Full-Adder circuit when $x_i=0$




But if we only need the sum bit ...

 Simplification of the Full-Adder circuit when $x_i=0$




... it reduces to an XOR.

Circuit for a one-digit BCD adder

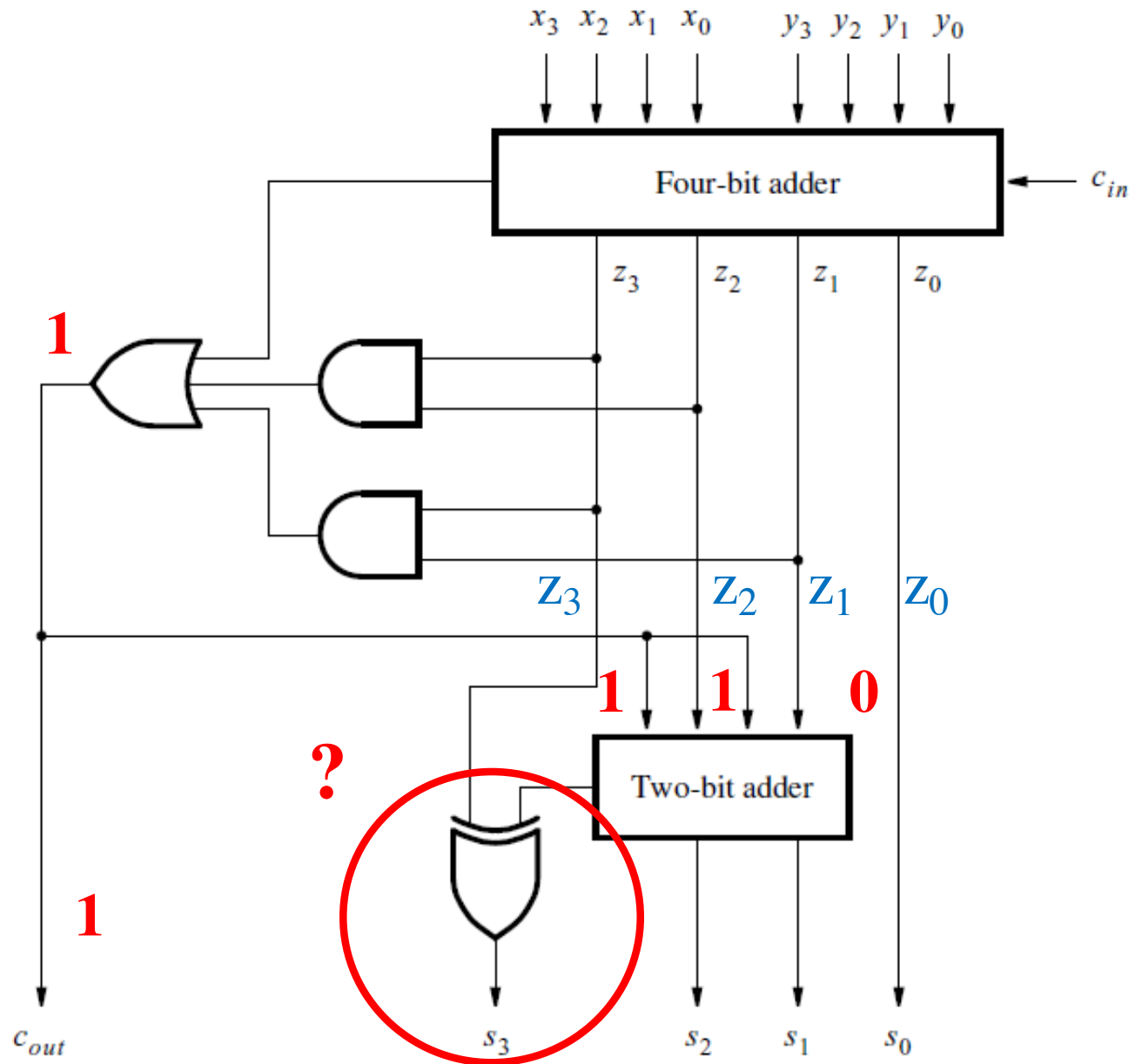


[Figure 3.41 in the textbook]

Circuit for a one-digit BCD adder

 

[Figure 3.41 in the textbook]

Circuit for a one-digit BCD adder

 

[Figure 3.41 in the textbook]

Questions?

THE END