

Instructions


Complete the questions below to the best of your ability. Do this on white paper. Once you are finished, upload a scanned PDF (just one file) of your work to canvas. **Also, please write the following on the first page: 1) your full name; 2) your student ID number; and 3) your lab section letter.**

Questions

- P1. (10 points) Define the following terms in no more than 2 sentences each.
- A. Verilog
 - B. Unicode
 - C. AND gate
 - D. Truth Table
 - E. Logic Circuit
- P2. (10 points) Answer the following in 4-5 sentences.
- A. What are the three basic logic gates?
 - B. What is a number system?
- P3. (10 points) Convert the following numbers to decimal:
- A. 1100011_2
 - B. 1101_2
 - C. 215_8
 - D. $25F_{16}$
 - E. $ACDC_{16}$
- P4. (10 points) Convert the following numbers to binary:
- A. 39
 - B. 435
 - C. 261
 - D. 134_8
 - E. $BAAD_{16}$
- P5. (10 points) Consider this array of bytes: [53_{16} 74_{16} 61_{16} 72_{16} 57_{16} 61_{16} 72_{16} 73_{16}].
- A. Convert each byte of the array to a binary number (e.g $32_{16} = 00110010_2$).
 - B. Convert each binary number to an ASCII character (Refer to section 1.5.3 on pages 14 – 16 in the textbook). What does it spell?

P6. (10 points) Consider the circuit below. Name the two inputs as A, and B. Name the output as F.

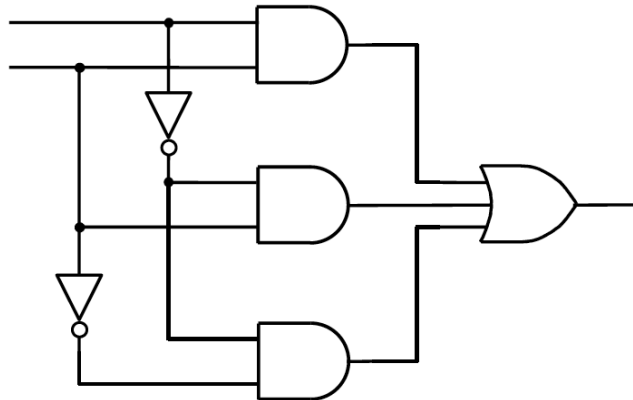- A. Write the logic expression for F.
- B. Draw the truth table for the circuit.



P7. (20 points) Consider the logic function $f(x, y) = (x + y) \cdot (\bar{x} + \bar{y})$

- A. (8 points) Draw the circuit diagram for $f(x, y)$.
- B. (8 points) Write the truth table for $f(x, y)$.
- C. (4 points) By looking at the truth table in (b), what observation can you make about $f(x, y)$.

P8. (20 points) Given the following logic expression:

$$F(x, y, z) = (x + \bar{y} + z) \cdot (\bar{x} + y + \bar{z}) \cdot (\bar{x} + z)$$

- A. (10 points) Draw the circuit diagram for $F(x, y, z)$.
- B. (10 points) Draw the truth table for $F(x, y, z)$.