

CprE 281: Digital Logic

Instructor: Alexander Stoytchev

<http://www.ece.iastate.edu/~alexs/classes/>

NAND and NOR Logic Networks

*CprE 281: Digital Logic
Iowa State University, Ames, IA
Copyright © Alexander Stoytchev*

Administrative Stuff

- **HW2 is due today, Sep 9 @ 10pm**
- **Please write clearly on the first page the following three things:**
 - **Your First and Last Name**
 - **Your Student ID Number**
 - **Your Lab Section Letter**
- **Submit on Canvas as *one* PDF file.**
- **Please orient your pages such that the text can be read without the need to rotate the page.**

Administrative Stuff

- **This week we will start with Lab2**
- **Read the lab assignment and do the prelab at home.**
- **Complete the prelab on paper before you go to the lab. Otherwise, you'll lose 20% of your grade for that lab.**

Quick Review

Minterms
(a set of basis functions)

The Four Basis Functions

x	y	f₀₀
0	0	1
0	1	0
1	0	0
1	1	0

$f_{00}(x, y)$

x	y	f₀₁
0	0	0
0	1	1
1	0	0
1	1	0

$f_{01}(x, y)$

x	y	f₁₀
0	0	0
0	1	0
1	0	1
1	1	0

$f_{10}(x, y)$

x	y	f₁₁
0	0	0
0	1	0
1	0	0
1	1	1

$f_{11}(x, y)$

The Four Basis Functions

x	y	f_{00}
0	0	1
0	1	0
1	0	0
1	1	0

$f_{00}(x, y)$

x	y	f_{01}
0	0	0
0	1	1
1	0	0
1	1	0

$f_{01}(x, y)$

x	y	f_{10}
0	0	0
0	1	0
1	0	1
1	1	0

$f_{10}(x, y)$

x	y	f_{11}
0	0	0
0	1	0
1	0	0
1	1	1

$f_{11}(x, y)$

The Four Basis Functions

x	y	$f_{00}(x, y)$	$f_{01}(x, y)$	$f_{10}(x, y)$	$f_{11}(x, y)$
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

The Four Basis Functions

x	y	$\bar{x}\bar{y}$	$\bar{x}y$	$x\bar{y}$	xy
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

Expressions for the minterms

$$m_0 = \bar{x} \bar{y}$$

$$m_1 = \bar{x} y$$

$$m_2 = x \bar{y}$$

$$m_3 = x y$$

Expressions for the minterms

$$0 \ 0 \quad m_0 = \bar{x} \bar{y}$$


$$0 \ 1 \quad m_1 = \bar{x} y$$

$$1 \ 0 \quad m_2 = x \bar{y}$$


$$1 \ 1 \quad m_3 = x y$$

The bars coincide
with the 0's
in the binary expansion
of the minterm sub-index


Circuits for the four basis functions

 


$$f_{00}(x, y) = \bar{x} \bar{y}$$

 

$$f_{01}(x, y) = \bar{x} y$$

 

$$f_{10}(x, y) = x \bar{y}$$

 

$$f_{11}(x, y) = x y$$

The Four Basis Functions

x	y	f ₀₀
0	0	1
0	1	0
1	0	0
1	1	0

$$f_{00}(x, y) = \bar{x} \bar{y}$$

x	y	f ₀₁
0	0	0
0	1	1
1	0	0
1	1	0

$$f_{01}(x, y) = \bar{x} y$$

x	y	f ₁₀
0	0	0
0	1	0
1	0	1
1	1	0

$$f_{10}(x, y) = x \bar{y}$$

x	y	f ₁₁
0	0	0
0	1	0
1	0	0
1	1	1

$$f_{11}(x, y) = x y$$

The Four Basis Functions (alternative names)

x	y	f ₀₀
0	0	1
0	1	0
1	0	0
1	1	0

$$f_{00}(x, y) = \bar{x} \bar{y}$$

m₀

x	y	f ₀₁
0	0	0
0	1	1
1	0	0
1	1	0

$$f_{01}(x, y) = \bar{x} y$$

m₁

x	y	f ₁₀
0	0	0
0	1	0
1	0	1
1	1	0

$$f_{10}(x, y) = x \bar{y}$$

m₂

x	y	f ₁₁
0	0	0
0	1	0
1	0	0
1	1	1

$$f_{11}(x, y) = x y$$

m₃

The Four Basis Functions (minterms)

x	y	m_0
0	0	1
0	1	0
1	0	0
1	1	0

$$f_{00}(x, y) = \bar{x} \bar{y}$$

m_0

x	y	m_1
0	0	0
0	1	1
1	0	0
1	1	0

$$f_{01}(x, y) = \bar{x} y$$

m_1

x	y	m_2
0	0	0
0	1	0
1	0	1
1	1	0

$$f_{10}(x, y) = x \bar{y}$$

m_2

x	y	m_3
0	0	0
0	1	0
1	0	0
1	1	1

$$f_{11}(x, y) = x y$$

m_3

Maxterms
(an alternative set of basis functions)

The Four Maxterms

x	y	M_0
0	0	0
0	1	1
1	0	1
1	1	1

$M_0(x, y)$

x	y	M_1
0	0	1
0	1	0
1	0	1
1	1	1

$M_1(x, y)$

x	y	M_2
0	0	1
0	1	1
1	0	0
1	1	1

$M_2(x, y)$

x	y	M_3
0	0	1
0	1	1
1	0	1
1	1	0

$M_3(x, y)$

The Four Maxterms

x	y	M_0
0	0	0
0	1	1
1	0	1
1	1	1

$M_0(x, y)$

x	y	M_1
0	0	1
0	1	0
1	0	1
1	1	1

$M_1(x, y)$

x	y	M_2
0	0	1
0	1	1
1	0	0
1	1	1

$M_2(x, y)$

x	y	M_3
0	0	1
0	1	1
1	0	1
1	1	0

$M_3(x, y)$

The Four Maxterms

x	y	$M_0(x, y)$	$M_1(x, y)$	$M_2(x, y)$	$M_3(x, y)$
0	0	0	1	1	1
0	1	1	0	1	1
1	0	1	1	0	1
1	1	1	1	1	0

The Four Maxterms

x	y		$x + y$	$x + \bar{y}$	$\bar{x} + y$	$\bar{x} + \bar{y}$
0	0		0	1	1	1
0	1		1	0	1	1
1	0		1	1	0	1
1	1		1	1	1	0

Expressions for the Maxterms

$$M_0 = x + y$$

$$M_1 = x + \bar{y}$$

$$M_2 = \bar{x} + y$$

$$M_3 = \bar{x} + \bar{y}$$

Expressions for the Maxterms

$$M_0 = x + y$$

$$M_1 = x + \bar{y}$$

$$M_2 = \bar{x} + y$$

$$M_3 = \bar{x} + \bar{y}$$

Note that these are now sums, not products.

Expressions for the Maxterms

$$0 \ 0 \quad M_0 = x + y$$


$$0 \ 1 \quad M_1 = x + \bar{y}$$

$$1 \ 0 \quad M_2 = \bar{x} + y$$


$$1 \ 1 \quad M_3 = \bar{x} + \bar{y}$$

The bars coincide
with the 1's
in the binary expansion
of the maxterm sub-index


Circuits for the four Maxterms

 


$$M_0(x, y) = x + y$$

 

$$M_1(x, y) = x + \bar{y}$$

 

$$M_2(x, y) = \bar{x} + y$$

 

$$M_3(x, y) = \bar{x} + \bar{y}$$

Minterms and Maxterms

Row number	x_1	x_2	Minterm	Maxterm
0	0	0	$m_0 = \bar{x}_1\bar{x}_2$	$M_0 = x_1 + x_2$
1	0	1	$m_1 = \bar{x}_1x_2$	$M_1 = x_1 + \bar{x}_2$
2	1	0	$m_2 = x_1\bar{x}_2$	$M_2 = \bar{x}_1 + x_2$
3	1	1	$m_3 = x_1x_2$	$M_3 = \bar{x}_1 + \bar{x}_2$

Minterms and Maxterms

Row number	x_1	x_2	Minterm	Maxterm
0	0	0	$m_0 = \bar{x}_1\bar{x}_2$	$M_0 = x_1 + x_2$
1	0	1	$m_1 = \bar{x}_1x_2$	$M_1 = x_1 + \bar{x}_2$
2	1	0	$m_2 = x_1\bar{x}_2$	$M_2 = \bar{x}_1 + x_2$
3	1	1	$m_3 = x_1x_2$	$M_3 = \bar{x}_1 + \bar{x}_2$

Use these for
Sum-of-Products
 Minimization
 (1's of the function)

Use these for
Product-of-Sums
 Minimization
 (0's of the function)

Sum-of-Products Form

(uses the **ones** of the function)

Sum-of-Products Form

Row number	x_1	x_2	Minterm	$f(x_1, x_2)$
0	0	0	$m_0 = \bar{x}_1\bar{x}_2$	1
1	0	1	$m_1 = \bar{x}_1x_2$	1
2	1	0	$m_2 = x_1\bar{x}_2$	0
3	1	1	$m_3 = x_1x_2$	1

Sum-of-Products Form

Row number	x_1	x_2	Minterm	$f(x_1, x_2)$
0	0	0	$m_0 = \bar{x}_1\bar{x}_2$	1
1	0	1	$m_1 = \bar{x}_1x_2$	1
2	1	0	$m_2 = x_1\bar{x}_2$	0
3	1	1	$m_3 = x_1x_2$	1

Sum-of-Products Form

Row number	x_1	x_2	Minterm	$f(x_1, x_2)$
0	0	0	$m_0 = \bar{x}_1\bar{x}_2$	1
1	0	1	$m_1 = \bar{x}_1x_2$	1
2	1	0	$m_2 = x_1\bar{x}_2$	0
3	1	1	$m_3 = x_1x_2$	1

$$\begin{aligned}f &= m_0 \cdot 1 + m_1 \cdot 1 + m_2 \cdot 0 + m_3 \cdot 1 \\&= m_0 + m_1 + m_3 \\&= \bar{x}_1\bar{x}_2 + \bar{x}_1x_2 + x_1x_2\end{aligned}$$

Product-of-Sums Form

(uses the **zeros** of the function)

Product-of-Sums Form

(for this logic function)

Row number	x_1	x_2	Maxterm	$f(x_1, x_2)$
0	0	0	$M_0 = x_1 + x_2$	0
1	0	1	$M_1 = x_1 + \bar{x}_2$	1
2	1	0	$M_2 = \bar{x}_1 + x_2$	0
3	1	1	$M_3 = \bar{x}_1 + \bar{x}_2$	1

Product-of-Sums Form (for this logic function)

Row number	x_1	x_2	Maxterm	$f(x_1, x_2)$
0	0	0	$M_0 = x_1 + x_2$	0
1	0	1	$M_1 = x_1 + \bar{x}_2$	1
2	1	0	$M_2 = \bar{x}_1 + x_2$	0
3	1	1	$M_3 = \bar{x}_1 + \bar{x}_2$	1

Product-of-Sums Form (for this logic function)

Row number	x_1	x_2	Maxterm	$f(x_1, x_2)$
0	0	0	$M_0 = x_1 + x_2$	0
1	0	1	$M_1 = x_1 + \bar{x}_2$	1
2	1	0	$M_2 = \bar{x}_1 + x_2$	0
3	1	1	$M_3 = \bar{x}_1 + \bar{x}_2$	1

$$f(x_1, x_2) = M_0 \cdot M_2 = (x_1 + x_2) \cdot (\bar{x}_1 + x_2)$$

Shorthand Notation

- **Sum-of-Products (SOP)**

$$f(x_1, x_2, x_3) = \sum (m_1, m_4, m_5, m_6)$$

or

$$f(x_1, x_2, x_3) = \sum m(1, 4, 5, 6)$$

- **Product-of-Sums (POS)**

$$f(x_1, x_2, x_3) = \Pi(M_0, M_2, M_3, M_7)$$

or

$$f(x_1, x_2, x_3) = \Pi M(0, 2, 3, 7)$$

Shorthand Notation for SOP

Row number	x_1	x_2	x_3	$f(x_1, x_2, x_3)$
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	0
4	1	0	0	1
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

$$f(x_1, x_2, x_3) = \sum (m_1, m_4, m_5, m_6)$$

or

$$f(x_1, x_2, x_3) = \sum m(1, 4, 5, 6)$$

Shorthand Notation

Row number	x_1	x_2	x_3	Minterm	Maxterm
0	0	0	0	$m_0 = \bar{x}_1\bar{x}_2\bar{x}_3$	$M_0 = x_1 + x_2 + x_3$
1	0	0	1	$m_1 = \bar{x}_1\bar{x}_2x_3$	$M_1 = x_1 + x_2 + \bar{x}_3$
2	0	1	0	$m_2 = \bar{x}_1x_2\bar{x}_3$	$M_2 = x_1 + \bar{x}_2 + x_3$
3	0	1	1	$m_3 = \bar{x}_1x_2x_3$	$M_3 = x_1 + \bar{x}_2 + \bar{x}_3$
4	1	0	0	$m_4 = x_1\bar{x}_2\bar{x}_3$	$M_4 = \bar{x}_1 + x_2 + x_3$
5	1	0	1	$m_5 = x_1\bar{x}_2x_3$	$M_5 = \bar{x}_1 + x_2 + \bar{x}_3$
6	1	1	0	$m_6 = x_1x_2\bar{x}_3$	$M_6 = \bar{x}_1 + \bar{x}_2 + x_3$
7	1	1	1	$m_7 = x_1x_2x_3$	$M_7 = \bar{x}_1 + \bar{x}_2 + \bar{x}_3$

$$f(x_1, x_2, x_3) = \sum (m_1, m_4, m_5, m_6)$$

$$f(x_1, x_2, x_3) = \sum m(1, 4, 5, 6)$$

Shorthand Notation for POS

Row number	x_1	x_2	x_3	$f(x_1, x_2, x_3)$
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	0
4	1	0	0	1
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

$$f(x_1, x_2, x_3) = \Pi(M_0, M_2, M_3, M_7)$$

or

$$f(x_1, x_2, x_3) = \Pi M(0, 2, 3, 7)$$

Shorthand Notation

Row number	x_1	x_2	x_3	Minterm	Maxterm
0	0	0	0	$m_0 = \bar{x}_1\bar{x}_2\bar{x}_3$	$M_0 = x_1 + x_2 + x_3$
1	0	0	1	$m_1 = \bar{x}_1\bar{x}_2x_3$	$M_1 = x_1 + x_2 + \bar{x}_3$
2	0	1	0	$m_2 = \bar{x}_1x_2\bar{x}_3$	$M_2 = x_1 + \bar{x}_2 + x_3$
3	0	1	1	$m_3 = \bar{x}_1x_2x_3$	$M_3 = x_1 + \bar{x}_2 + \bar{x}_3$
4	1	0	0	$m_4 = x_1\bar{x}_2\bar{x}_3$	$M_4 = \bar{x}_1 + x_2 + x_3$
5	1	0	1	$m_5 = x_1\bar{x}_2x_3$	$M_5 = \bar{x}_1 + x_2 + \bar{x}_3$
6	1	1	0	$m_6 = x_1x_2\bar{x}_3$	$M_6 = \bar{x}_1 + \bar{x}_2 + x_3$
7	1	1	1	$m_7 = x_1x_2x_3$	$M_7 = \bar{x}_1 + \bar{x}_2 + \bar{x}_3$

$$f(x_1, x_2, x_3) = \Pi(M_0, M_2, M_3, M_7)$$

$$f(x_1, x_2, x_3) = \Pi M(0, 2, 3, 7)$$


Shorthand Notation

Row number	x_1	x_2	x_3	Minterm	Maxterm
0	0	0	0	$m_0 = \bar{x}_1\bar{x}_2\bar{x}_3$	$M_0 = x_1 + x_2 + x_3$
1	0	0	1	$m_1 = \bar{x}_1\bar{x}_2x_3$	$M_1 = x_1 + x_2 + \bar{x}_3$
2	0	1	0	$m_2 = \bar{x}_1x_2\bar{x}_3$	$M_2 = x_1 + \bar{x}_2 + x_3$
3	0	1	1	$m_3 = \bar{x}_1x_2x_3$	$M_3 = x_1 + \bar{x}_2 + \bar{x}_3$
4	1	0	0	$m_4 = x_1\bar{x}_2\bar{x}_3$	$M_4 = \bar{x}_1 + x_2 + x_3$
5	1	0	1	$m_5 = x_1\bar{x}_2x_3$	$M_5 = \bar{x}_1 + x_2 + \bar{x}_3$
6	1	1	0	$m_6 = x_1x_2\bar{x}_3$	$M_6 = \bar{x}_1 + \bar{x}_2 + x_3$
7	1	1	1	$m_7 = x_1x_2x_3$	$M_7 = \bar{x}_1 + \bar{x}_2 + \bar{x}_3$


Notice that the red and the green are nicely separated and that they cover all possible rows (no gaps).

Two New Logic Gates


The Three Basic Logic Gates

 

NOT gate

 


AND gate

 


OR gate

NAND Gate

 



x_1	x_2	f
0	0	1
0	1	1
1	0	1
1	1	0

NOR Gate

 

x_1	x_2	f
0	0	1
0	1	0
1	0	0
1	1	0


AND vs NAND

  

x_1	x_2	f
0	0	0
0	1	0
1	0	0
1	1	1


x_1	x_2	f
0	0	1
0	1	1
1	0	1
1	1	0

AND followed by NOT = NAND

 


x_1	x_2	f
0	0	0
0	1	0
1	0	0
1	1	1

f
1
1
1
0

 


x_1	x_2	f
0	0	1
0	1	1
1	0	1
1	1	0

NAND followed by NOT = AND

 



x_1	x_2	f
0	0	1
0	1	1
1	0	1
1	1	0

f
0
0
0
1

 

x_1	x_2	f
0	0	0
0	1	0
1	0	0
1	1	1


OR vs NOR

  

x_1	x_2	f
0	0	0
0	1	1
1	0	1
1	1	1


x_1	x_2	f
0	0	1
0	1	0
1	0	0
1	1	0

OR followed by NOT = NOR

 


x_1	x_2	f
0	0	0
0	1	1
1	0	1
1	1	1

f
1
0
0
0

 


x_1	x_2	f
0	0	1
0	1	0
1	0	0
1	1	0

NOR followed by NOT = OR

 

x_1	x_2	f
0	0	1
0	1	0
1	0	0
1	1	0

f
0
1
1
1

 

x_1	x_2	f
0	0	0
0	1	1
1	0	1
1	1	1


Why do we need two more gates?

Why do we need two more gates?


They can be implemented with fewer transistors.

**They are simpler to implement,
but are they also useful?**

Building a NOT Gate with NAND

 


x	\bar{x}
0	1
1	0

 


x	x	f
0	0	1
0	1	1
1	0	1
1	1	0

Building a NOT Gate with NAND

 


x	\bar{x}
0	1
1	0

 


x	x	f
0	0	1
1	1	0

impossible combinations

Building a NOT Gate with NAND

 

x	\bar{x}
0	1
1	0


 


x	x	f
0	0	1
1	1	0

impossible combinations

Thus, the two truth tables are equal!

Building a NOT Gate with NAND

  

$$\overline{X \cdot X} = \bar{X}$$

Another way to think about this.


Building an AND gate with NAND gates

Desired AND Gate



$$Q = A \text{ AND } B$$

NAND Construction

 

$$= \text{NOT}(\text{NOT}(A \text{ AND } B))$$

Truth Table

Input A	Input B	Output Q
0	0	0
0	1	0
1	0	0
1	1	1


Building an OR gate with NAND gates

Desired OR Gate



$$Q = A \text{ OR } B$$

NAND Construction

 

$$= \text{NOT} [\text{NOT} (A \text{ AND } A) \text{ AND } \text{NOT} (B \text{ AND } B)]$$

Truth Table

Input A	Input B	Output Q
0	0	0
0	1	1
1	0	1
1	1	1

Implications

Implications

**Any Boolean function can be implemented
with only NAND gates!**


NOR gate with NAND gates

Desired NOR Gate



$$Q = \text{NOT}(A \text{ OR } B)$$

NAND Construction

 

$$= \text{NOT}\{ \text{NOT}[\text{NOT}(A \text{ AND } A) \text{ AND } \text{NOT}(B \text{ AND } B)] \}$$

Truth Table

Input A	Input B	Output Q
0	0	1
0	1	0
1	0	0
1	1	0


XOR gate with NAND gates

Desired XOR Gate



$$Q = A \text{ XOR } B$$

NAND Construction

 

$$= \text{NOT} [\text{NOT} \{ A \text{ AND } \text{NOT} (A \text{ AND } B) \} \text{ AND } \text{NOT} \{ B \text{ AND } \text{NOT} (A \text{ AND } B) \}]$$

Truth Table

Input A	Input B	Output Q
0	0	0
0	1	1
1	0	1
1	1	0


XNOR gate with NAND gates

Desired XNOR Gate



$$Q = \text{NOT}(A \text{ XOR } B)$$

NAND Construction

 


$$= \text{NOT}[\text{NOT}[\text{NOT}\{A \text{ AND } \text{NOT}(A \text{ AND } B)\} \text{ AND } \text{NOT}\{B \text{ AND } \text{NOT}(A \text{ AND } B)\}]]$$

Truth Table

Input A	Input B	Output Q
0	0	1
0	1	0
1	0	0
1	1	1

Building a NOT Gate with NOR

 


x	\bar{x}
0	1
1	0



x	x	f
0	0	1
0	1	0
1	0	0
1	1	0

Building a NOT Gate with NOR

 


x	\bar{x}
0	1
1	0



x	x	f
0	0	1
[Redacted]		
1	1	0

impossible combinations

Building a NOT Gate with NOR

 

x	\bar{x}
0	1
1	0




x	x	f
0	0	1
[Redacted]		
1	1	0

impossible combinations

Thus, the two truth tables are equal!

Building a NOT Gate with NOR

 

$$\overline{X + X} = \bar{X}$$


Another way to think about this.

Building an OR gate with NOR gates

Desired Gate



NOR Construction

 


Truth Table

Input A	Input B	Output Q
0	0	0
0	1	1
1	0	1
1	1	1

Let's build an AND gate with NOR gates

Let's build an AND gate with NOR gates

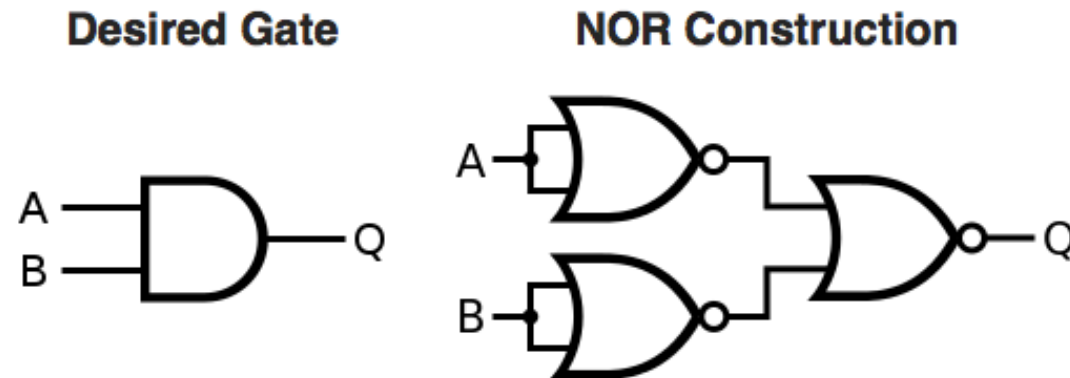

Truth Table

Input A	Input B	Output Q
0	0	0
0	1	0
1	0	0
1	1	1

Implications

Implications


**Any Boolean function can be implemented
with only NOR gates!**

NAND gate with NOR gates

Desired Gate




NOR Construction

 

Truth Table

Input A	Input B	Output Q
0	0	1
0	1	1
1	0	1
1	1	0

XOR gate with NOR gates

 

Truth Table


Input A	Input B	Output Q
0	0	0
0	1	1
1	0	1
1	1	0

XNOR gate with NOR gates

Desired XNOR Gate




NOR Construction

 


Truth Table


Input A	Input B	Output Q
0	0	1
0	1	0
1	0	0
1	1	1

The following examples came from this book

 


 


[Platt 2009]

 


[Platt 2009]

 


[Platt 2009]

 

[Platt 2009]

 


[Platt 2009]

 

[Platt 2009]


DeMorgan's Theorem Revisited

 DeMorgan's theorem (in terms of logic gates)



$$\overline{x \cdot y} = \overline{x} + \overline{y}$$

 
The other DeMorgan's theorem (in terms of logic gates)



$$\overline{x + y} = \overline{x} \cdot \overline{y}$$


Shortcut Notation

DeMorgan's theorem in terms of logic gates

 


(Theorem 15.a) $\overline{x \cdot y} = \overline{x} + \overline{y}$

DeMorgan's theorem in terms of logic gates


 


(Theorem 15.b) $\overline{x + y} = \overline{x} \overline{y}$




Two NOTs in a row

 

Two NOTs in a row

  


Two NOTs in a row

   


NAND-NAND Implementation of Sum-of-Products Expressions

NAND followed by NOT = AND

 

x_1	x_2	f
0	0	1
0	1	1
1	0	1
1	1	0

f
0
0
0
1

 


x_1	x_2	f
0	0	0
0	1	0
1	0	0
1	1	1

DeMorgan's Theorem


$$15a. \quad \overline{x \cdot y} = \bar{x} + \bar{y}$$

DeMorgan's Theorem

 
15a. $\overline{\mathbf{x} \cdot \mathbf{y}} = \overline{\mathbf{x}} + \overline{\mathbf{y}}$





=

 



Sum-Of-Products

 


Sum-Of-Products

  



Sum-Of-Products

  



Sum-Of-Products

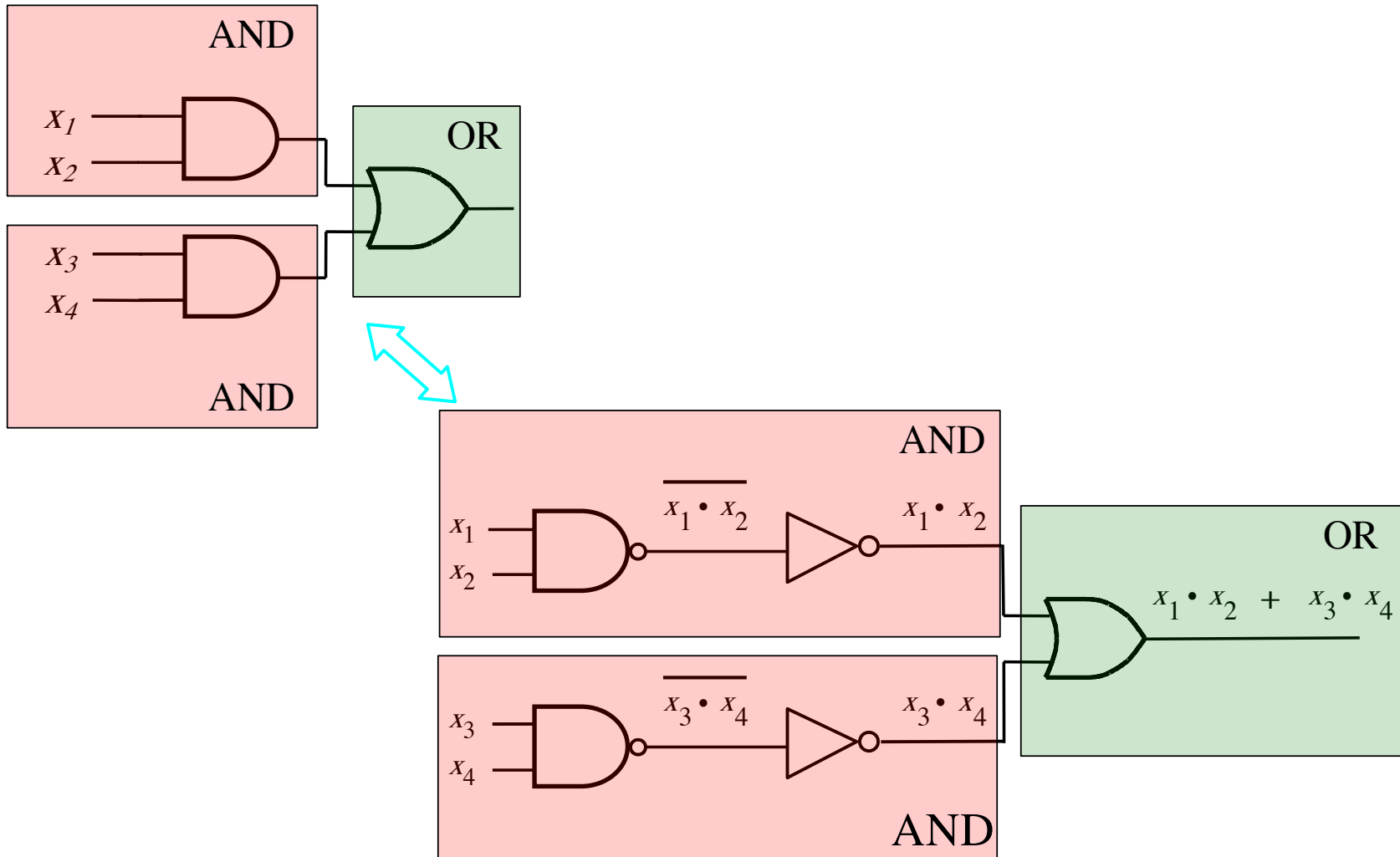



Sum-Of-Products

  


Sum-Of-Products

  

Sum-Of-Products

 
 


Sum-Of-Products

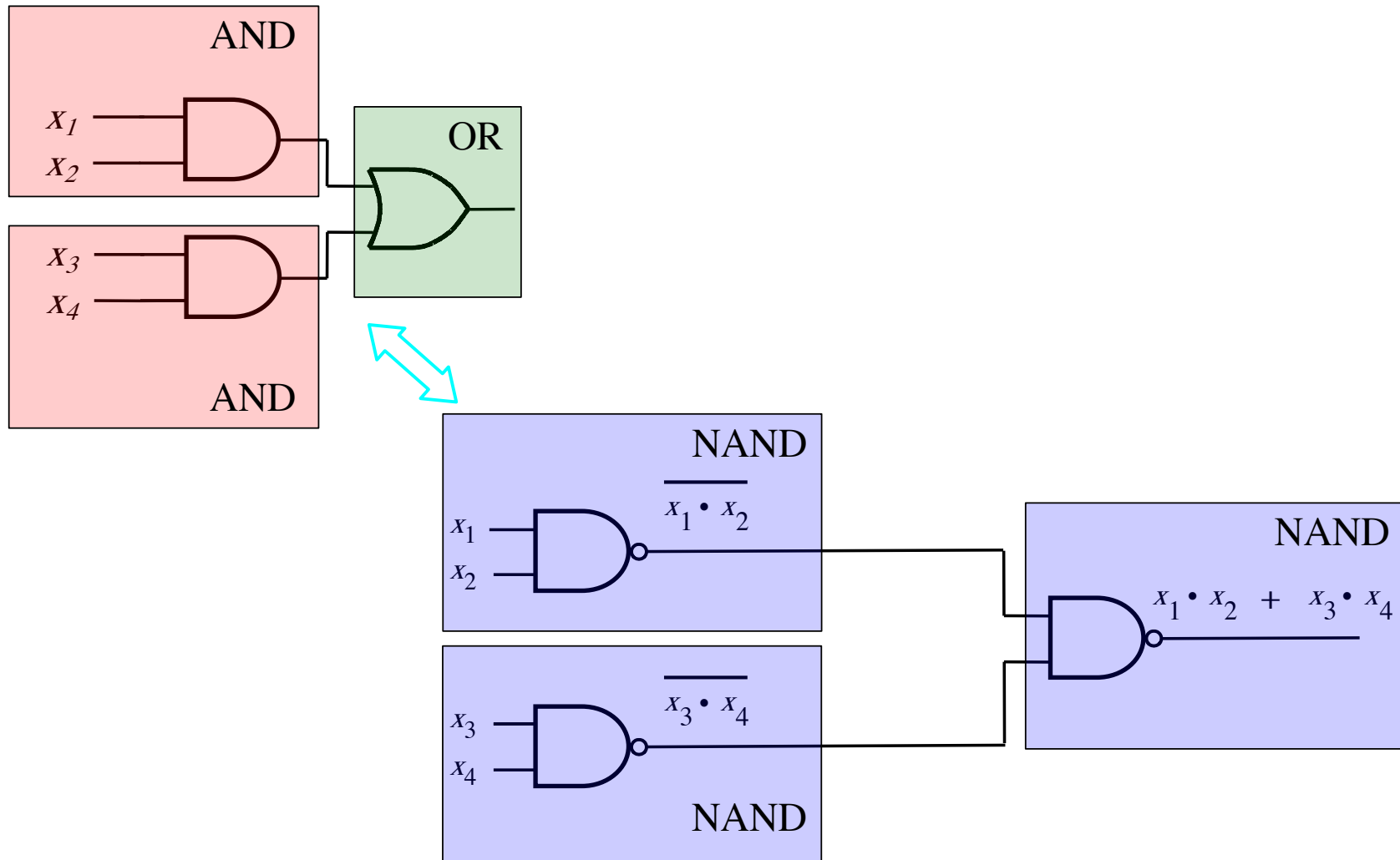


This circuit uses only NANDs

Sum-Of-Products


 
 


This circuit uses only NANDs

Another SOP Example

 

This circuit uses ANDs & OR

   


This circuit uses only NANDs

[Figure 2.27 from the textbook]


NOR-NOR Implementation of Product-of-Sums Expressions

NOR followed by NOT = OR

 

x_1	x_2	f
0	0	1
0	1	0
1	0	0
1	1	0

f
0
1
1
1

 


x_1	x_2	f
0	0	0
0	1	1
1	0	1
1	1	1

DeMorgan's Theorem


$$15b. \quad \overline{x + y} = \bar{x} \cdot \bar{y}$$

DeMorgan's Theorem


 
15b. $\overline{x + y} = \bar{x} \cdot \bar{y}$





Product-Of-Sums

 



Product-Of-Sums

  



Product-Of-Sums

  



Product-Of-Sums

  



Product-Of-Sums

  


Product-Of-Sums

  

Product-Of-Sums

 
 


Product-Of-Sums

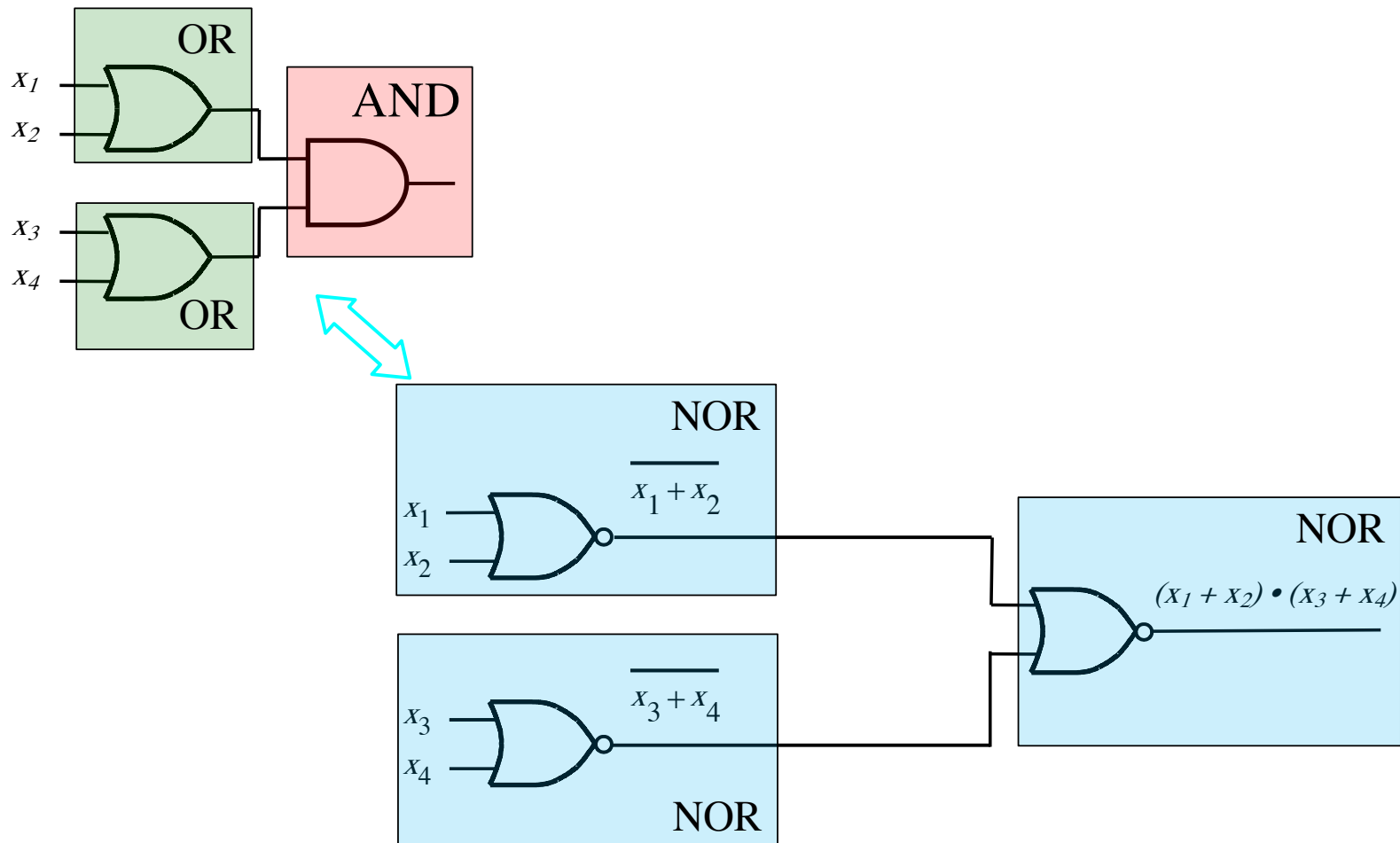




This circuit uses only NORs

Product-Of-Sums

  

This circuit uses only NORs

Another POS Example

   

This circuit uses ORs & AND

This circuit uses only NORs

[Figure 2.28 from the textbook]

Summary

- **Sum-of-Products (SOP) expressions are directly mappable to NAND-NAND implementation.**
- **Product-of-Sums (POS) expressions are directly mappable to NOR-NOR implementation.**
- **Going from SOP to NOR-NOR is not that easy.**
- **Similarly, converting from POS to NAND-NAND implementation requires extra work.**

Questions?

THE END