

# **CprE 281: Digital Logic**

**Instructor: Alexander Stoytchev**

**<http://www.ece.iastate.edu/~alexs/classes/>**

# Intro to Verilog

*CprE 281: Digital Logic  
Iowa State University, Ames, IA  
Copyright © Alexander Stoytchev*

# **Administrative Stuff**

- **HW3 is due on Monday Sep 16 @ 10pm**




# **Quick Review**

# The Three Basic Logic Gates

x	NOT
0	1
1	0


x	y	AND
0	0	0
0	1	0
1	0	0
1	1	1

x	y	OR
0	0	0
0	1	1
1	0	1
1	1	1

   


# **AND with Switches**

# AND Circuit

 


# AND Circuit

 




# AND Circuit

 


# AND Circuit

 


**NOT with Switches**

# NOT Circuit

 


# NOT Circuit

 


# **NAND with Switches**

# NAND Circuit

 


# NAND Circuit

 




# NAND Circuit

 


# NAND Circuit

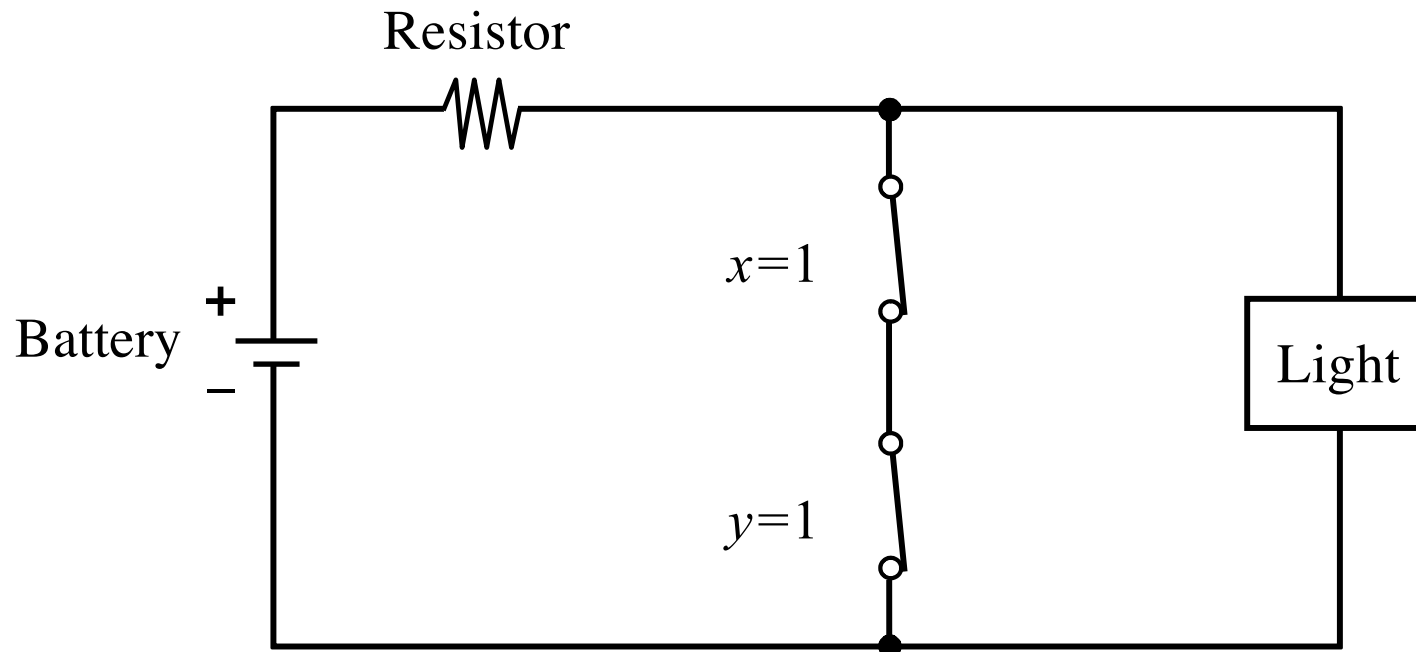


# **OR with Switches**


# OR Circuit

 


# OR Circuit

 

# OR Circuit

 


# OR Circuit

 


# **NOR with Switches**




# NOR Circuit

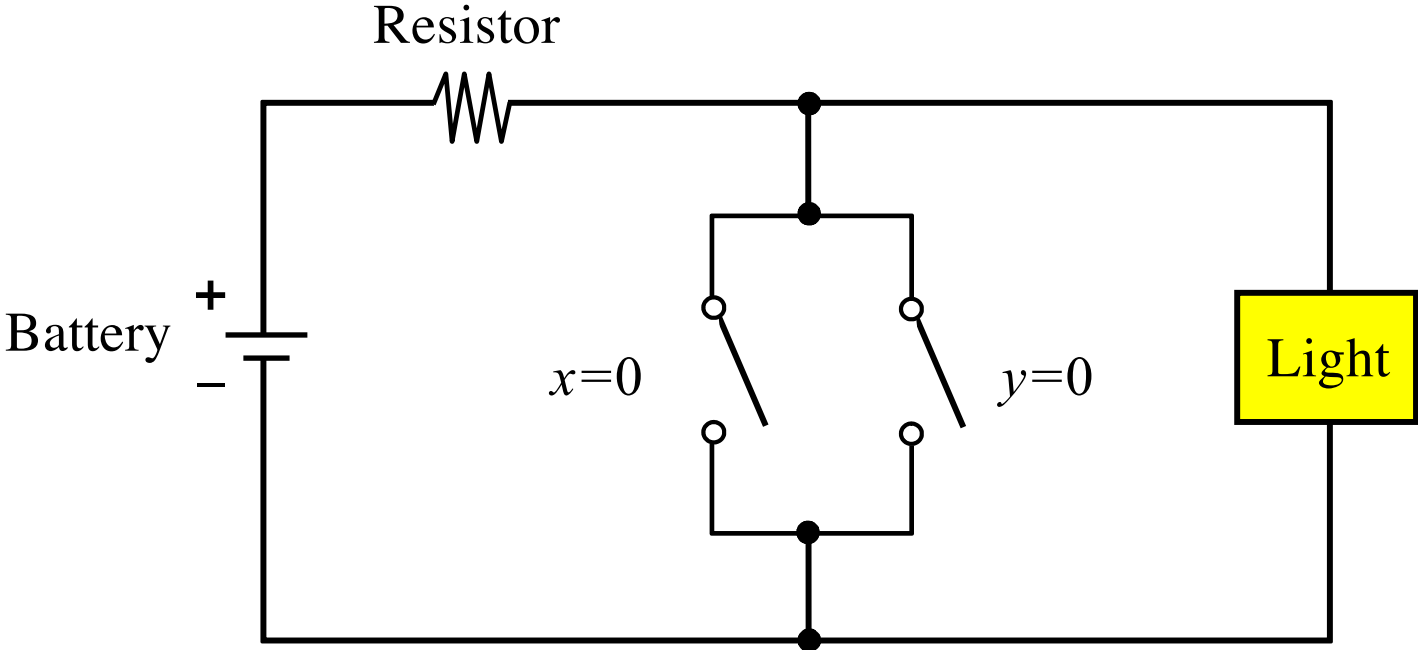


# NOR Circuit

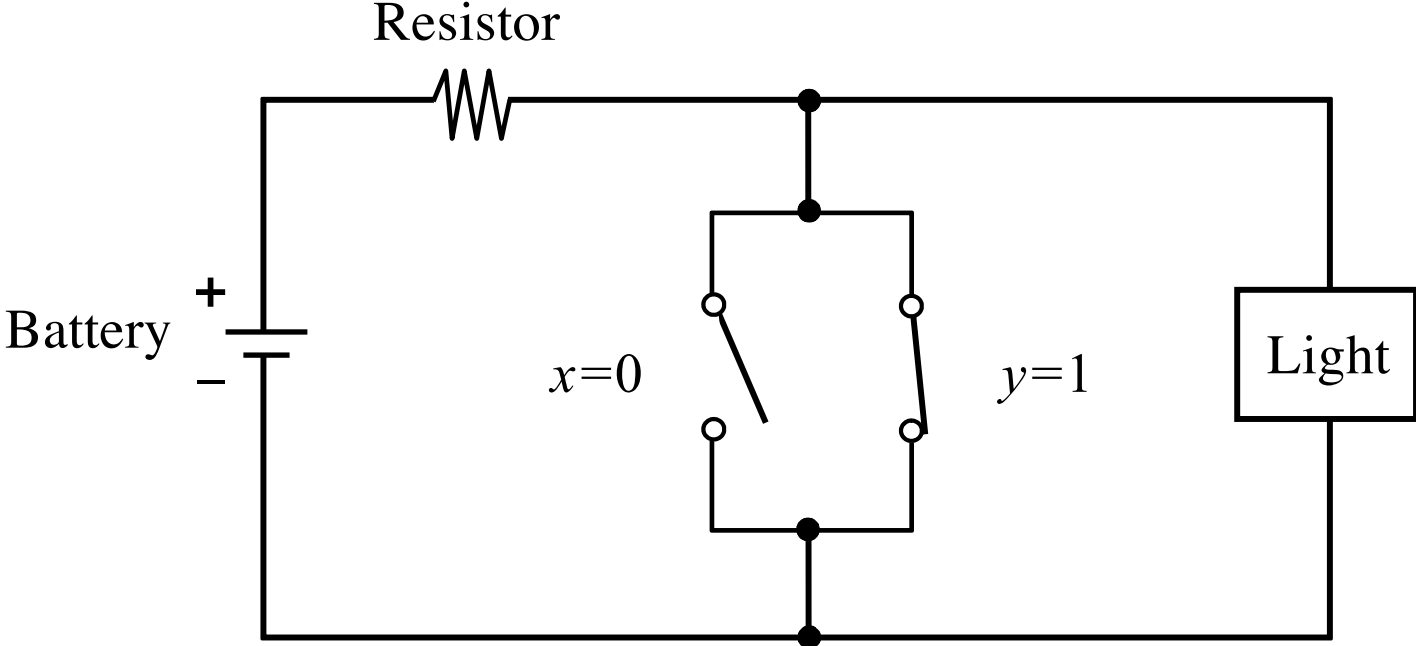

# NOR Circuit

 

# NOR Circuit



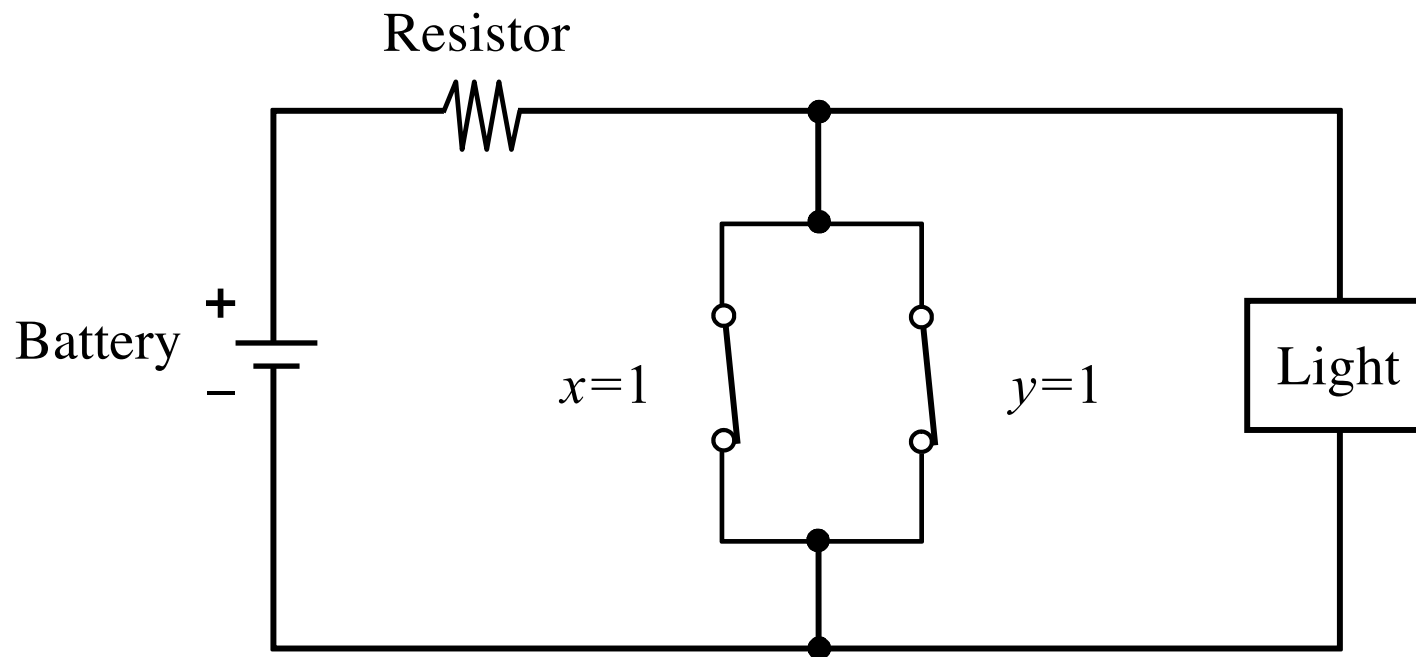


# The Three Basic Logic Gates

x	NOT
0	1
1	0

x	y	AND
0	0	0
0	1	0
1	0	0
1	1	1



x	y	OR
0	0	0
0	1	1
1	0	1
1	1	1

   

# NAND and NOR

x	y	NAND
0	0	1
0	1	1
1	0	1
1	1	0


x	y	NOR
0	0	1
0	1	0
1	0	0
1	1	0

  

# XOR and XNOR

x	y	XOR
0	0	0
0	1	1
1	0	1
1	1	0


x	y	XNOR
0	0	1
0	1	0
1	0	0
1	1	1

 


# **XNOR with Switches**




# XNOR Circuit

 


# XNOR Circuit

 

# XNOR Circuit

 


# XNOR Circuit

 


# **XOR with Switches**


# XOR Circuit

 

# XOR Circuit

 


# XOR Circuit

 




# XOR Circuit



 


# **7-Segment Display Example**


# 7-Segment Display

 


# Displaying Some Numbers

   

# Displaying Some Hexadecimal Numbers

 

# Display of numbers

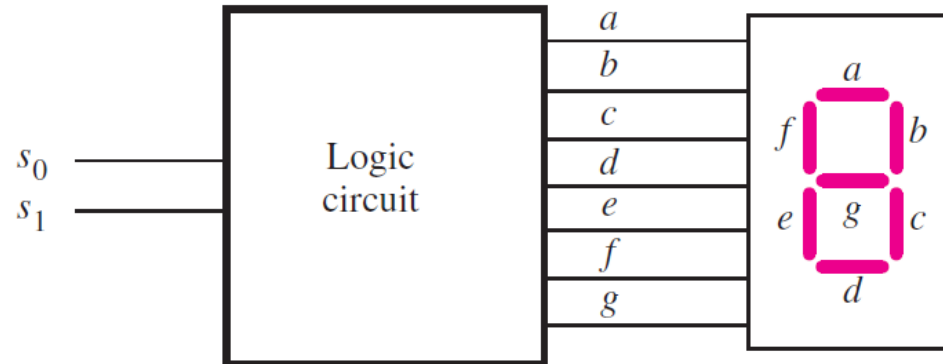

(a) Logic circuit and 7-segment display

	$s_1$	$s_0$	$a$	$b$	$c$	$d$	$e$	$f$	$g$
<b>0</b>	0	0	1	1	1	1	1	1	0
<b>1</b>	0	1	0	1	1	0	0	0	0
<b>2</b>	1	0	1	1	0	1	1	0	1

(b) Truth table

[ Figure 2.34 from the textbook ]

# Display of numbers

	$s_1$	$s_0$	$a$	$b$	$c$	$d$	$e$	$f$	$g$
0	0	0	1	1	1	1	1	1	0
1	0	1	0	1	1	0	0	0	0
2	1	0	1	1	0	1	1	0	1

# Display of numbers

	$s_1$	$s_0$	$a$	$b$	$c$	$d$	$e$	$f$	$g$
0	0	0	1	1	1	1	1	1	0
1	0	1	0	1	1	0	0	0	0
2	1	0	1	1	0	1	1	0	1

$$a = \overline{s_0}$$

$$c = \overline{s_1}$$

$$e = \overline{s_0}$$

$$g = s_1 \overline{s_0}$$

$$b = 1$$

$$d = \overline{s_0}$$

$$f = \overline{s_1} \overline{s_0}$$



# **Intro to Verilog**

# History


- **Created in 1983/1984**
- **Verilog-95 (IEEE standard 1364-1995)**
- **Verilog 2001 (IEEE Standard 1364-2001)**
- **Verilog 2005 (IEEE Standard 1364-2005)**
- **SystemVerilog**
- **SystemVerilog 2009 (IEEE Standard 1800-2009).**

# HDL

- **Hardware Description Language**
- **Verilog HDL**
- **VHDL**

# Verilog HDL $\neq$ VHDL

- **These are two different Languages!**
- **Verilog is closer to C**
- **VHDL is closer to Ada**

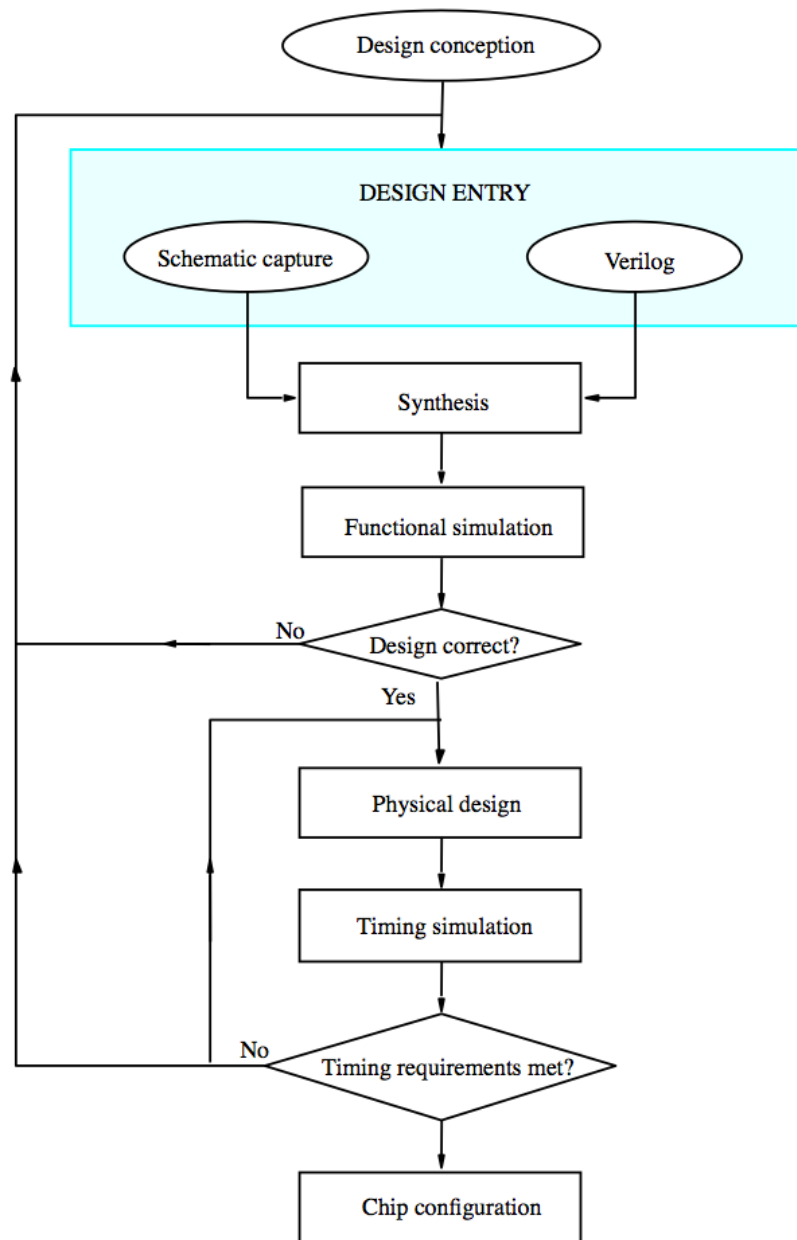


[ Figure 2.35 from the textbook ]


# Sample Verilog Program

```
module example1 (x1, x2, s, f);  
  input x1, x2, s;  
  output f;  
  
  not (k, s);  
  and (g, k, x1);  
  and (h, s, x2);  
  or (f, g, h);  
  
endmodule
```


# The Three Basic Logic Gates

 

NOT gate

 


AND gate

 

OR gate

You can build any circuit using only these three gates

# How to specify a NOT gate in Verilog

 


NOT gate




# How to specify a NOT gate in Verilog

we'll use the letter *y* for the output

 

NOT gate

# How to specify a NOT gate in Verilog

 


`not (y, x);`

NOT gate

Verilog code

# How to specify an AND gate in Verilog

 


`and (f, x1, x2);`

AND gate

Verilog code

# How to specify an OR gate in Verilog

 


OR gate

`or (f, x1, x2);`


Verilog code

# 3-input Logic Gates

 

3-input AND gate


and ( $f, x_1, x_2, x_3$ );

 


3-input OR gate

or ( $f, x_1, x_2, x_3$ );


# Other Logic Gates

 


NAND gate

 

NOR gate

 


XOR gate

 

XNOR gate


# Other Logic Gates

nand (f, x1, x2);

 


NAND gate


nor (f, x1, x2);

 

NOR gate

 

XOR gate

 

XNOR gate


xor (f, x1, x2);

xnor (f, x1, x2);

Verilog Code

Structural

Behavioral

 




# **Structural Verilog**


# **2-to-1 Multiplexer in Verilog (structural syntax)**

# 2-1 Multiplexer

 

[ Figure 2.36 from the textbook ]

# Verilog Code for a 2-1 Multiplexer

 


[ Figure 2.36 from the textbook ]

```
module example1 (x1, x2, s, f);  
  input x1, x2, s;  
  output f;  
  
  not (k, s);  
  and (g, k, x1);  
  and (h, s, x2);  
  or (f, g, h);  
  
endmodule
```

[ Figure 2.37 from the textbook ]

# Verilog Code for a 2-1 Multiplexer

 


```
module example1 (x1, x2, s, f);  
    input x1, x2, s;  
    output f;  
  
    not (k, s);  
    and (g, k, x1);  
    and (h, s, x2);  
    or (f, g, h);  
  
endmodule
```

[ Figure 2.36 from the textbook ]

[ Figure 2.37 from the textbook ]

# Verilog Code for a 2-1 Multiplexer

 


```
module example1 (x1, x2, s, f);  
  input x1, x2, s;  
  output f;  
  
  not (k, s);  
  and (g, k, x1);  
  and (h, s, x2);  
  or (f, g, h);  
  
endmodule
```

[ Figure 2.36 from the textbook ]

[ Figure 2.37 from the textbook ]

# Verilog Code for a 2-1 Multiplexer

 

```
module example1 (x1, x2, s, f);
    input x1, x2, s;
    output f;
```

```
    not (k, s);
```

```
    and (g, k, x1);
```

```
    and (h, s, x2);
```


```
    or (f, g, h);
```

```
endmodule
```

[ Figure 2.36 from the textbook ]

[ Figure 2.37 from the textbook ]

# Verilog Code for a 2-1 Multiplexer

 


```
module example1 (x1, x2, s, f);  
  input x1, x2, s;  
  output f;  
  
  not (k, s);  
  and (g, k, x1);  
  and (h, s, x2);  
  or (f, g, h);  
  
endmodule
```

[ Figure 2.36 from the textbook ]

[ Figure 2.37 from the textbook ]



# Verilog Code for a 2-1 Multiplexer

 


[ Figure 2.36 from the textbook ]

```
module example1 (x1, x2, s, f);  
    input x1, x2, s;  
    output f;  
  
    not (k, s);  
    and (g, k, x1);  
    and (h, s, x2);  
    or (f, g, h);  
  
endmodule
```

[ Figure 2.37 from the textbook ]

# Verilog Code for a 2-1 Multiplexer

 


[ Figure 2.36 from the textbook ]

```
module example1 (x1, x2, s, f);  
  input x1, x2, s;  
  output f;  
  
  not (k, s);  
  and (g, k, x1);  
  and (h, s, x2);  
  or (f, g, h);  
  
endmodule
```

[ Figure 2.37 from the textbook ]

# Verilog Code for a 2-1 Multiplexer

 


[ Figure 2.36 from the textbook ]

```
module example1 (x1, x2, s, f);  
  input x1, x2, s;  
  output f;  
  
  not (k, s);  
  and (g, k, x1);  
  and (h, s, x2);  
  or (f, g, h);  
  
endmodule
```

[ Figure 2.37 from the textbook ]

# Verilog Code for a 2-1 Multiplexer

 


```
module example1 (x1, x2, s, f);  
  input x1, x2, s;  
  output f;  
  
  not (k, s);  
  and (g, k, x1);  
  and (h, s, x2);  
  or (f, g, h);  
  
endmodule
```

[ Figure 2.36 from the textbook ]

[ Figure 2.37 from the textbook ]

# Verilog Code for a 2-1 Multiplexer

 


```
module example1 (x1, x2, s, f);  
  input x1, x2, s;  
  output f;  
  
  not (k, s);  
  and (g, k, x1);  
  and (h, s, x2);  
  or (f, g, h);  
  
endmodule
```

[ Figure 2.36 from the textbook ]

[ Figure 2.37 from the textbook ]

# Verilog Code for a 2-1 Multiplexer

 

```
module example1 (x1, x2, s, f);  
  input x1, x2, s;  
  output f;  
  
  not (k, s);  
  and (g, k, x1);  
  and (h, s, x2);  
  or (f, g, h);  
  
endmodule
```

[ Figure 2.36 from the textbook ]


[ Figure 2.37 from the textbook ]

# **Behavioral Verilog**


Verilog Code

Structural

Behavioral

 




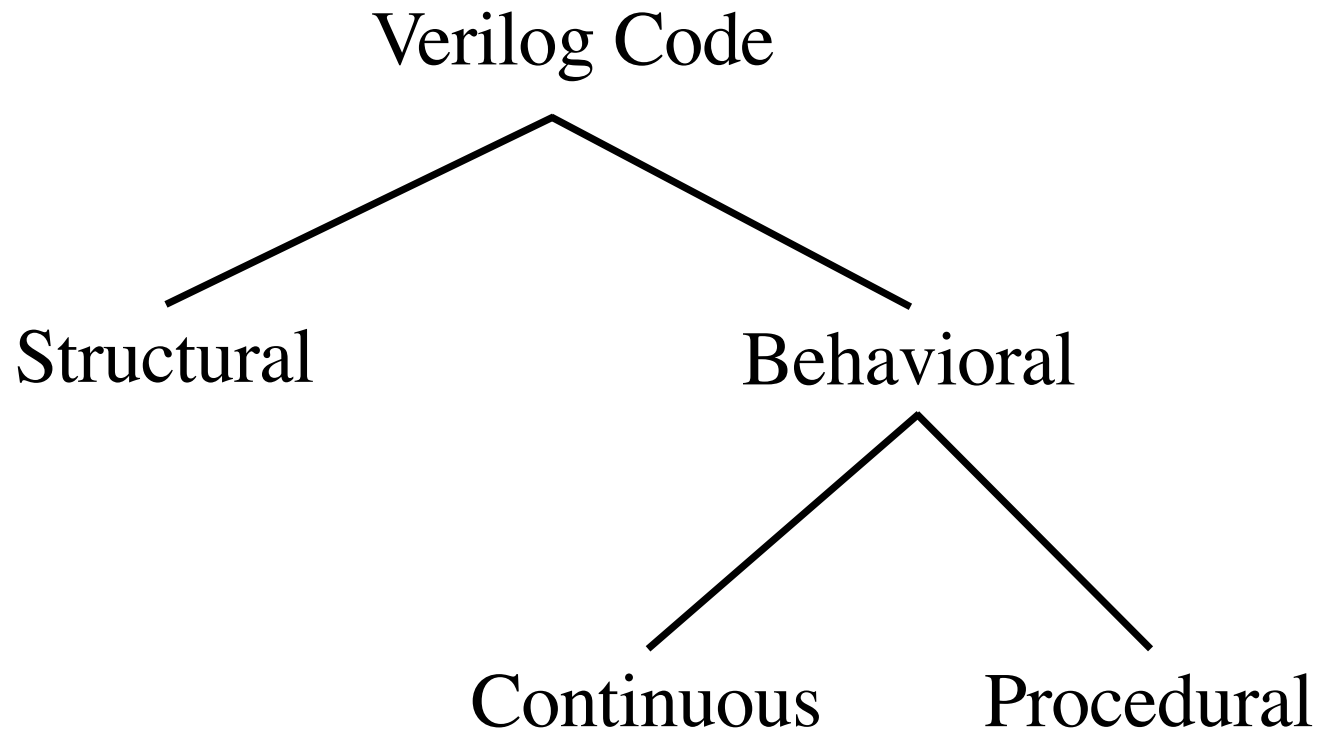

# **2-to-1 Multiplexer in Verilog (behavioral-continuous syntax)**

# Verilog Code for a 2-1 Multiplexer

 

// Behavioral-Continuous specification

```
module example3 (x1, x2, s, f);
```

```
  input x1, x2, s;
```

```
  output f;
```


```
  assign f = (~s & x1) | (s & x2);
```

```
endmodule
```

[ Figure 2.36 from the textbook ]

[ Figure 2.40 from the textbook ]

# Verilog Code for a 2-1 Multiplexer

 

[ Figure 2.36 from the textbook ]


```
// Behavioral-Continuous specification
module example3 (x1, x2, s, f);
    input x1, x2, s;
    output f;

    assign f = (~s & x1) | (s & x2);

endmodule
```

[ Figure 2.40 from the textbook ]

# Verilog Code for a 2-1 Multiplexer

 

```
// Behavioral-Continuous specification
module example3 (x1, x2, s, f);
    input x1, x2, s;
    output f;


    assign f = (~s & x1) | (s & x2);

endmodule
```

[ Figure 2.36 from the textbook ]

[ Figure 2.40 from the textbook ]

# Verilog Code for a 2-1 Multiplexer

 

// Behavioral-Continuous specification

```
module example3 (x1, x2, s, f);
```

```
  input x1, x2, s;
```

```
  output f;
```

```
  assign f = (~s & x1) | (s & x2);
```


```
endmodule
```

[ Figure 2.36 from the textbook ]

[ Figure 2.40 from the textbook ]

# **2-to-1 Multiplexor in Verilog (behavioral-procedural specification)**

# Verilog Code for a 2-1 Multiplexer

 

[ Figure 2.36 from the textbook ]

// Behavioral-Procedural specification

```
module example5 (x1, x2, s, f);
```

```
input x1, x2, s;
```

```
output f; 1
```

```
reg f;
```

```
always @(x1 or x2 or s)
```

```
if (s == 0)
```

```
    f = x1;
```

```
else
```


```
    f = x2;
```

```
endmodule
```

[ Figure 2.42 from the textbook ]



# Verilog Code for a 2-1 Multiplexer

 

[ Figure 2.36 from the textbook ]

// Behavioral-Procedural specification

```
module example5 (x1, x2, s, f);
```

```
input x1, x2, s;
```

```
output f; 1
```

```
reg f;
```

procedural statement

```
always @(x1 or x2 or s)
```

```
if (s == 0)
```

```
    f = x1;
```


```
else
```

```
    f = x2;
```

```
endmodule
```

[ Figure 2.42 from the textbook ]

# Verilog Code for a 2-1 Multiplexer

 

The always block is executed only when one of the signals in the sensitivity list has changed its value.

[ Figure 2.36 from the textbook ]

// Behavioral-Procedural specification

```
module example5 (x1, x2, s, f);
```

```
input x1, x2, s;
```

```
output f; 1
```

```
reg f;
```

sensitivity list

```
always @(x1 or x2 or s)
```

```
if (s == 0)
```

```
    f = x1;
```


```
else
```

```
    f = x2;
```

```
endmodule
```

[ Figure 2.42 from the textbook ]

# Verilog Code for a 2-1 Multiplexer

 

reg: does not need to be computed all the time.  
It stores a value until you write to it a new value.

[ Figure 2.36 from the textbook ]

// Behavioral-Procedural specification


```
module example5 (x1, x2, s, f);
  input x1, x2, s;
  output f; 1 of type register
  reg f; (can store a value)
```

```
  always @(x1 or x2 or s)
    if (s == 0)
      f = x1;
    else
      f = x2;
```

```
endmodule
```

[ Figure 2.42 from the textbook ]

# Verilog Code for a 2-1 Multiplexer

 

Because the signal  $f$  is updated inside a procedural statement (i.e., inside an always block) it must be declared of type `reg`. This is required so it can hold its value until the next time the always block is executed, which will happen only when one of the signals on the sensitivity list has changed its value.

[ Figure 2.36 from the textbook ]

// Behavioral-Procedural specification


```
module example5 (x1, x2, s, f);
  input x1, x2, s;
  output f; 1 of type register
  reg f; (can store a value)
```

```
  always @(x1 or x2 or s)
    if (s == 0)
      f = x1;
    else
      f = x2;
```

```
endmodule
```

[ Figure 2.42 from the textbook ]

# Verilog Code for a 2-1 Multiplexer

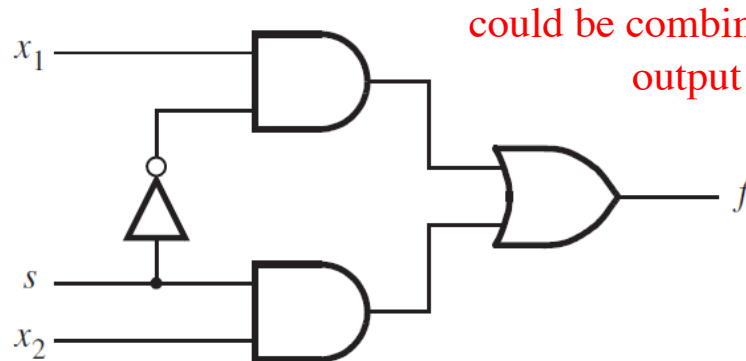

// Behavioral-Procedural specification

```
module example5 (x1, x2, s, f);
```

```
input x1, x2, s;
```

```
output f;
```

```
reg f;
```

```
always @(x1 or x2 or s)
```

```
if (s == 0)
```

```
    f = x1;
```

```
else
```

```
    f = x2;
```

```
endmodule
```

[ Figure 2.36 from the textbook ]

[ Figure 2.42 from the textbook ]

# Verilog Code for a 2-1 Multiplexer

A 2-to-1 Multiplexer has:

- one output  $f$
- two inputs:  $x_1$  and  $x_2$
- It also has another input line  $s$
- If  $s=0$ , then the output is equal to  $x_1$
- If  $s=1$ , then the output is equal to  $x_2$

// Behavioral-Procedural specification

```
module example5 (x1, x2, s, f);  
  input x1, x2, s;  
  output f;   
  reg f;  
  
  always @(x1 or x2 or s)  
    if (s == 0)  
      f = x1;  
    else  
      f = x2;  
  
endmodule
```

# Verilog Code for a 2-1 Multiplexer

A 2-to-1 Multiplexer has:

- one output  $f$
  - two inputs:  $x_1$  and  $x_2$
  - It also has another input line  $s$
- If  $s=0$ , then the output is equal to  $x_1$
  - If  $s=1$ , then the output is equal to  $x_2$

// Behavioral-Procedural specification

```
module example5 (x1, x2, s, f);  
  input x1, x2, s;  
  output f;  
  reg f;
```

```
  always @(x1 or x2 or s)  
    if (s == 0)  
      f = x1;  
    else  
      f = x2;
```

```
endmodule
```

# always@ syntax

always @(x,y)

always @(x or y)

always @(\*)

always @\*



# always@ syntax

always @(x,y)


always @(x or y)

always @(\*)

always @\*

Leave it to the Verilog compiler to figure out which signals appear in the always block and add them to the sensitivity list.

# Verilog Code for a 2-1 Multiplexer

 

[ Figure 2.36 from the textbook ]

// Behavioral-Procedural specification

```
module example5 (input x1, x2, s, output reg f);
```

```
    always @(x1, x2, s)
```

```
        if (s == 0)
```

```
            f = x1;
```

```
        else
```

```
            f = x2;
```

```
endmodule
```

[ Figure 2.43 from the textbook ]

# **Structural v.s. Behavioral**

# Verilog Code: Structural v.s. Behavioral

```
// Structural specification
module example1 (x1, x2, s, f);
    input x1, x2, s;
    output f;

    not (k, s);
    and (g, k, x1);
    and (h, s, x2);
    or (f, g, h);

endmodule
```

[ Figure 2.37 from the textbook ]

```
// Behavioral-Continuous specification
module example3 (x1, x2, s, f);
    input x1, x2, s;
    output f;

    assign f = (~s & x1) | (s & x2);

endmodule
```

[ Figure 2.40 from the textbook ]

# Verilog Code: Structural v.s. Behavioral

```
// Structural specification
module example1 (x1, x2, s, f);
    input x1, x2, s;
    output f;

    not (k, s);
    and (g, k, x1);
    and (h, s, x2);
    or (f, g, h);

endmodule
```

[ Figure 2.37 from the textbook ]

```
// Behavioral-Procedural specification
module example5 (x1, x2, s, f);
    input x1, x2, s;
    output f;
    reg f;

    always @(x1 or x2 or s)
        if (s == 0)
            f = x1;
        else
            f = x2;

endmodule
```

[ Figure 2.42 from the textbook ]

# Behavioral Verilog: Continuous v.s. Procedural

```
// Behavioral-Continuous specification
module example3 (x1, x2, s, f);
    input x1, x2, s;
    output f;

    assign f = (~s & x1) | (s & x2);

endmodule
```

[ Figure 2.40 from the textbook ]


```
// Behavioral-Procedural specification
module example5 (x1, x2, s, f);
    input x1, x2, s;
    output f;
    reg f;

    always @(x1 or x2 or s)
        if (s == 0)
            f = x1;
        else
            f = x2;

endmodule
```

[ Figure 2.42 from the textbook ]


# Verilog Code

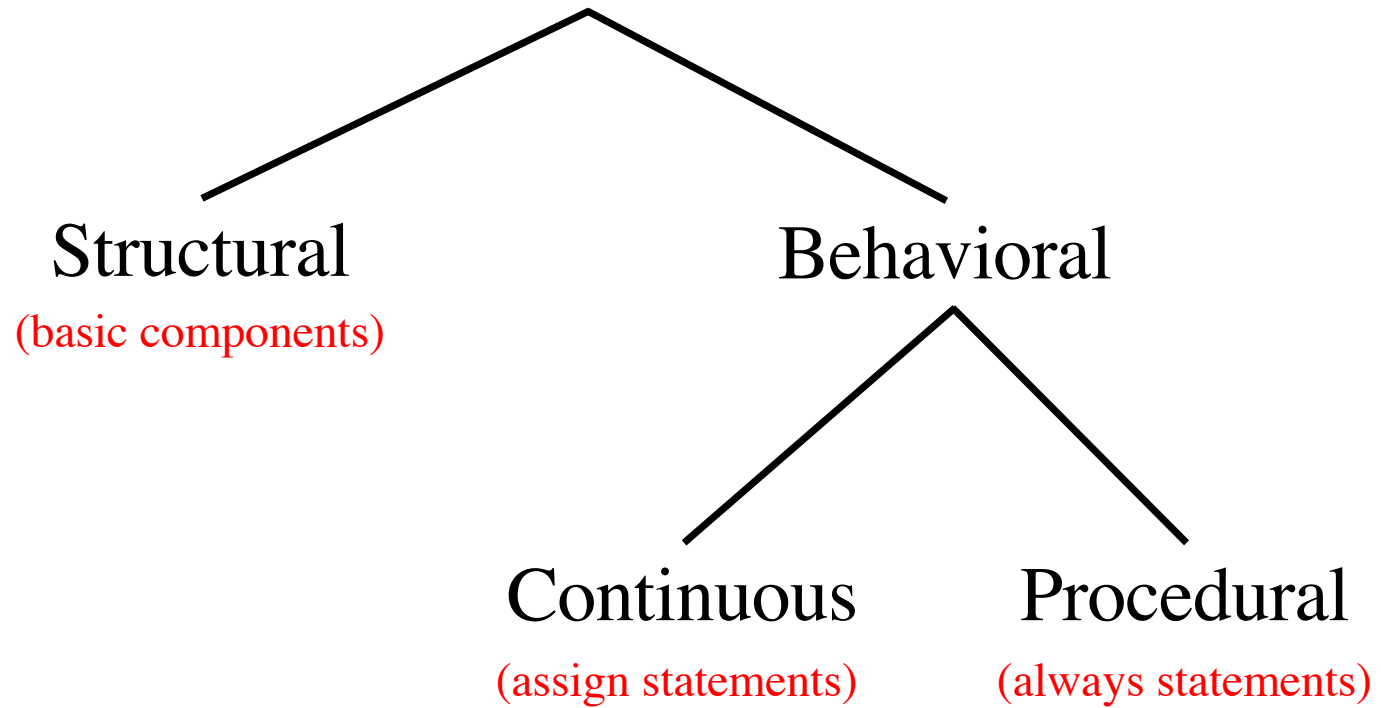

# **Another Example**




# Let's Write the Code for This Circuit

 

[ Figure 2.39 from the textbook ]

# Structural Verilog

 


```
module example2 (x1, x2, x3, x4, f, g, h);  
  input x1, x2, x3, x4;  
  output f, g, h;  
  
  and (z1, x1, x3);  
  and (z2, x2, x4);  
  or (g, z1, z2);  
  or (z3, x1, ~x3);  
  or (z4, ~x2, x4);  
  and (h, z3, z4);  
  or (f, g, h);  
  
endmodule
```

[ Figure 2.39 from the textbook ]

[ Figure 2.38 from the textbook ]

# Structural Verilog

 


```
module example2 (x1, x2, x3, x4, f, g, h);  
    input x1, x2, x3, x4;  
    output f, g, h;  
  
    and (z1, x1, x3);  
    and (z2, x2, x4);  
    or (g, z1, z2);  
    or (z3, x1, ~x3);  
    or (z4, ~x2, x4);  
    and (h, z3, z4);  
    or (f, g, h);  
  
endmodule
```

[ Figure 2.39 from the textbook ]

[ Figure 2.38 from the textbook ]

# Behavioral Verilog

 

```
module example4 (x1, x2, x3, x4, f, g, h);  
  input x1, x2, x3, x4;  
  output f, g, h;
```

```
  assign g = (x1 & x3) | (x2 & x4);  
  assign h = (x1 | ~x3) & (~x2 | x4);  
  assign f = g | h;
```

```
endmodule
```

[ Figure 2.39 from the textbook ]

[ Figure 2.41 from the textbook ]

# Structural v.s. Behavioral

```
module example2 (x1, x2, x3, x4, f, g, h);  
  input x1, x2, x3, x4;  
  output f, g, h;  
  
  and (z1, x1, x3);  
  and (z2, x2, x4);  
  or (g, z1, z2);  
  or (z3, x1, ~x3);  
  or (z4, ~x2, x4);  
  and (h, z3, z4);  
  or (f, g, h);  
  
endmodule
```


// structural

```
module example4 (x1, x2, x3, x4, f, g, h);  
  input x1, x2, x3, x4;  
  output f, g, h;  
  
  assign g = (x1 & x3) | (x2 & x4);  
  assign h = (x1 | ~x3) & (~x2 | x4);  
  assign f = g | h;  
  
endmodule
```

// behavioral-continuous

**Yet Another Example**

# A logic circuit with two modules

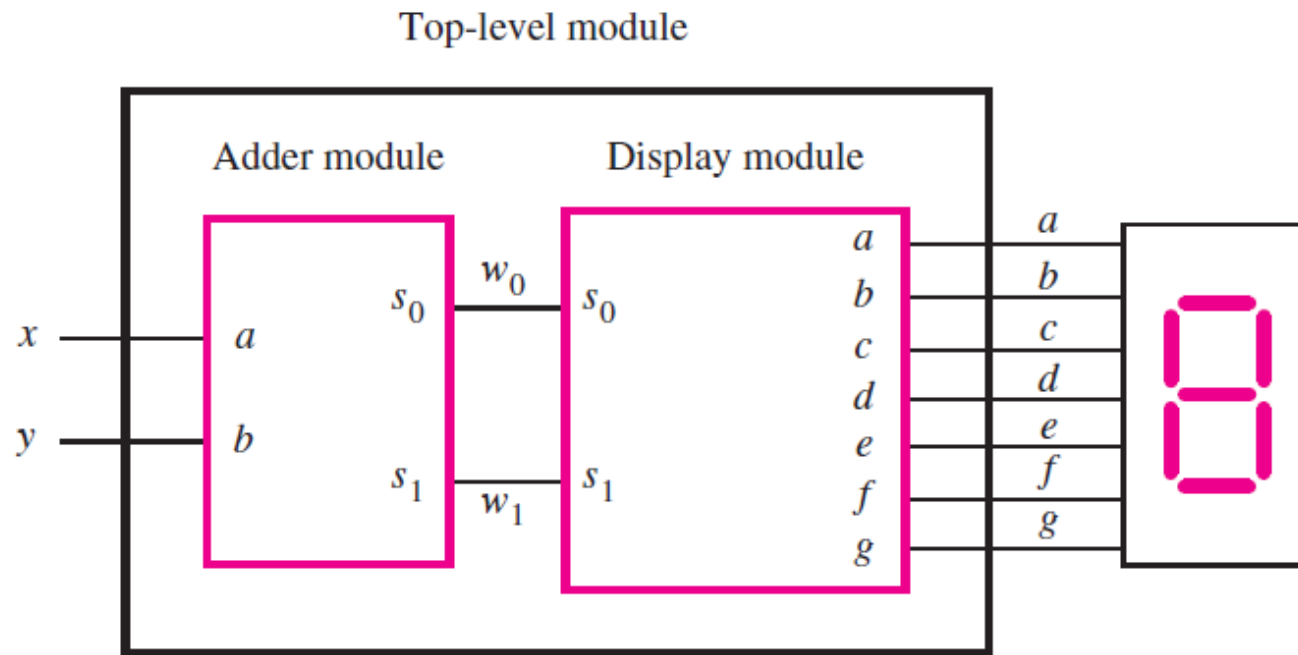

[ Figure 2.44 from the textbook ]


# The adder module

$a$	$0$	$0$	$1$	$1$
$+b$	$+0$	$+1$	$+0$	$+1$
$s_1 s_0$	$0 0$	$0 1$	$0 1$	$1 0$

(a) Evaluation of  $S = a + b$

$a$	$b$	$s_1$	$s_0$
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0


(b) Truth table

 

(c) Logic network



# The adder module

 

```
// An adder module
module adder (a, b, s1, s0);
  input a, b;
  output s1, s0;

  assign s1 = a & b;
  assign s0 = a ^ b;

endmodule
```

# The display module

	$s_1$	$s_0$	$a$	$b$	$c$	$d$	$e$	$f$	$g$
0	0	0	1	1	1	1	1	1	0
1	0	1	0	1	1	0	0	0	0
2	1	0	1	1	0	1	1	0	1

$$a = \overline{s_0}$$

$$c = \overline{s_1}$$

$$e = \overline{s_0}$$

$$g = s_1 \overline{s_0}$$

$$b = 1$$

$$d = \overline{s_0}$$

$$f = \overline{s_1} \overline{s_0}$$

# The display module

$$a = \overline{s_0}$$

$$b = 1$$

$$c = \overline{s_1}$$

$$d = \overline{s_0}$$

$$e = \overline{s_0}$$

$$f = \overline{s_1} \overline{s_0}$$

$$g = s_1 \overline{s_0}$$

// A module for driving a 7-segment display

**module** display (s1, s0, a, b, c, d, e, f, g);

**input** s1, s0;

**output** a, b, c, d, e, f, g;

**assign** a = ~s0;

**assign** b = 1;

**assign** c = ~s1;

**assign** d = ~s0;

**assign** e = ~s0;

**assign** f = ~s1 & ~s0;


**assign** g = s1 & ~s0;

**endmodule**

[ Figure 2.46 from the textbook ]

# Putting it all together

Top-level module

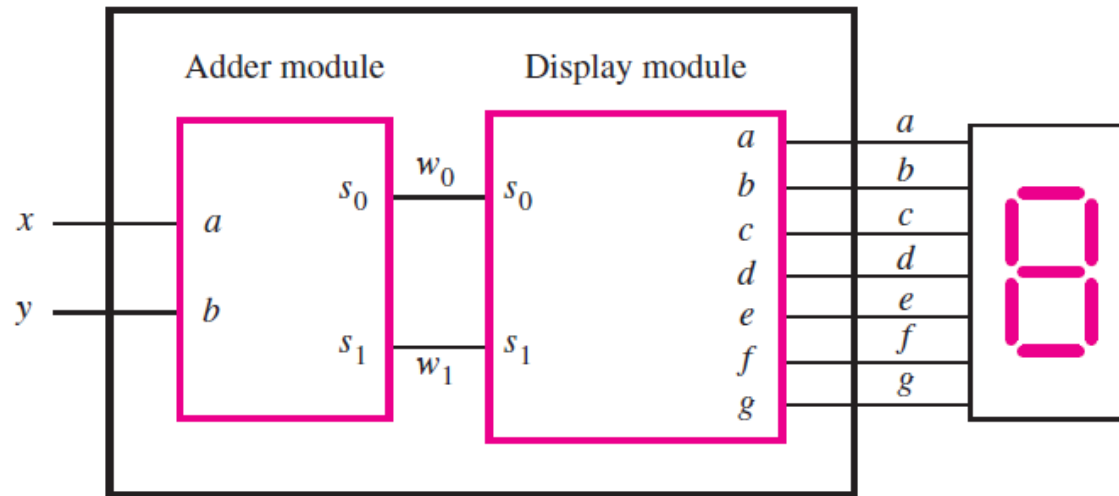

```
// An adder module
```

```
module adder (a, b, s1, s0)
```

```
  input a, b;
```

```
  output s1, s0;
```

```
  assign s1 = a & b;
```

```
  assign s0 = a ^ b;
```

```
endmodule
```

```
// A module for driving a 7-segment display
```

```
module display (s1, s0, a, b, c, d, e, f, g);
```

```
  input s1, s0;
```

```
  output a, b, c, d, e, f, g;
```

```
  assign a = ~s0;
```

```
  assign b = 1;
```

```
  assign c = ~s1;
```

```
  assign d = ~s0;
```

```
  assign e = ~s0;
```

```
  assign f = ~s1 & ~s0;
```

```
  assign g = s1 & ~s0;
```

```
endmodule
```

```
module adder_display (x, y, a, b, c, d, e, f, g);
```

```
  input x, y;
```

```
  output a, b, c, d, e, f, g;
```

```
  wire w1, w0;
```


```
  adder U1 (x, y, w1, w0);
```

```
  display U2 (w1, w0, a, b, c, d, e, f, g);
```

```
endmodule
```

# Putting it all together

Top-level module

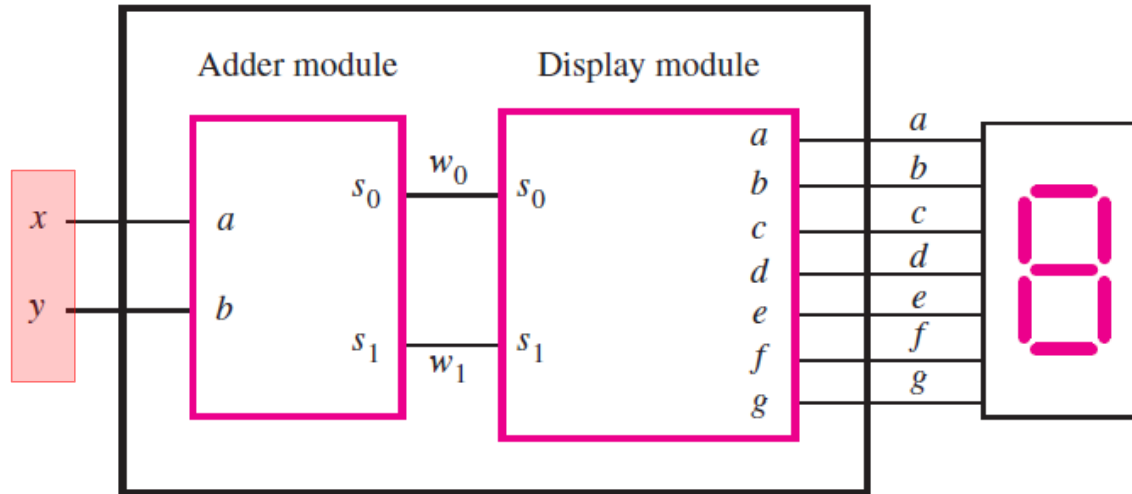

```
// An adder module
```

```
module adder (a, b, s1, s0)
```

```
  input a, b;
```

```
  output s1, s0;
```

```
  assign s1 = a & b;
```

```
  assign s0 = a ^ b;
```

```
endmodule
```

```
// A module for driving a 7-segment display
```

```
module display (s1, s0, a, b, c, d, e, f, g);
```

```
  input s1, s0;
```

```
  output a, b, c, d, e, f, g;
```

```
  assign a = ~s0;
```

```
  assign b = 1;
```

```
  assign c = ~s1;
```

```
  assign d = ~s0;
```

```
  assign e = ~s0;
```

```
  assign f = ~s1 & ~s0;
```

```
  assign g = s1 & ~s0;
```

```
endmodule
```

```
module adder_display (x, y, a, b, c, d, e, f, g);
```

```
  input x, y;
```

```
  output a, b, c, d, e, f, g;
```

```
  wire w1, w0;
```


```
  adder U1 (x, y, w1, w0);
```

```
  display U2 (w1, w0, a, b, c, d, e, f, g);
```

```
endmodule
```

# Putting it all together

Top-level module

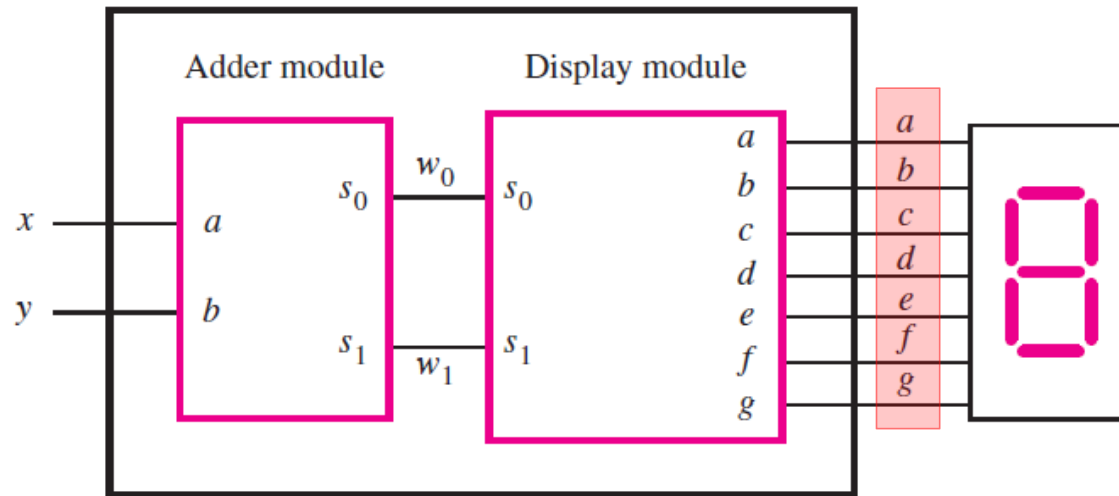

```
// An adder module
```

```
module adder (a, b, s1, s0)
```

```
  input a, b;
```

```
  output s1, s0;
```

```
  assign s1 = a & b;
```

```
  assign s0 = a ^ b;
```

```
endmodule
```

```
// A module for driving a 7-segment display
```

```
module display (s1, s0, a, b, c, d, e, f, g);
```

```
  input s1, s0;
```

```
  output a, b, c, d, e, f, g;
```

```
  assign a = ~s0;
```

```
  assign b = 1;
```

```
  assign c = ~s1;
```

```
  assign d = ~s0;
```

```
  assign e = ~s0;
```

```
  assign f = ~s1 & ~s0;
```

```
  assign g = s1 & ~s0;
```

```
endmodule
```

```
module adder_display (x, y, a, b, c, d, e, f, g);
```

```
  input x, y;
```

```
  output a, b, c, d, e, f, g;
```

```
  wire w1, w0;
```


```
  adder U1 (x, y, w1, w0);
```

```
  display U2 (w1, w0, a, b, c, d, e, f, g);
```

```
endmodule
```

# Putting it all together

Top-level module

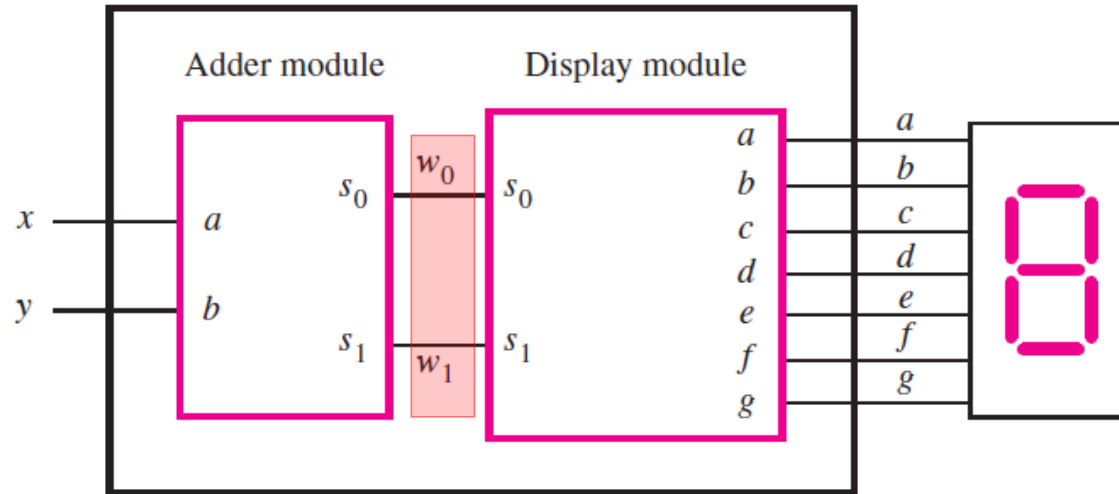

```
// An adder module
```

```
module adder (a, b, s1, s0)
```

```
  input a, b;
```

```
  output s1, s0;
```

```
  assign s1 = a & b;
```

```
  assign s0 = a ^ b;
```

```
endmodule
```

```
// A module for driving a 7-segment display
```

```
module display (s1, s0, a, b, c, d, e, f, g);
```

```
  input s1, s0;
```

```
  output a, b, c, d, e, f, g;
```

```
  assign a = ~s0;
```

```
  assign b = 1;
```

```
  assign c = ~s1;
```

```
  assign d = ~s0;
```

```
  assign e = ~s0;
```

```
  assign f = ~s1 & ~s0;
```

```
  assign g = s1 & ~s0;
```

```
endmodule
```

```
module adder_display (x, y, a, b, c, d, e, f, g);
```

```
  input x, y;
```

```
  output a, b, c, d, e, f, g;
```

```
  wire w1, w0; variables of type wire  
(neither input nor output)
```


```
  adder U1 (x, y, w1, w0);
```

```
  display U2 (w1, w0, a, b, c, d, e, f, g);
```

```
endmodule
```

# Putting it all together

Top-level module

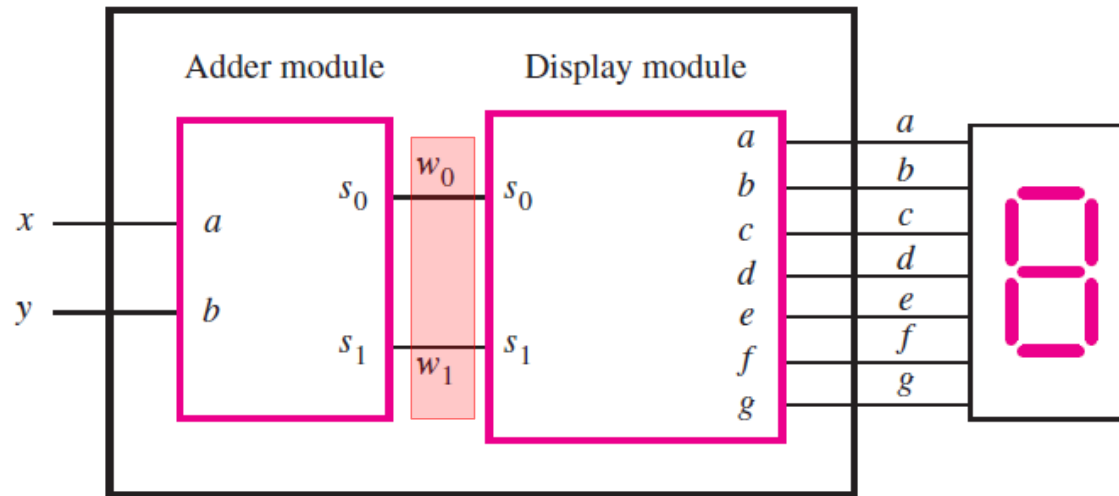

// An adder module

```
module adder (a, b, s1, s0)
```

```
  input a, b;
```

```
  output s1, s0;
```

```
  assign s1 = a & b;
```

```
  assign s0 = a ^ b;
```

```
endmodule
```

// A module for driving a 7-segment display

```
module display (s1, s0, a, b, c, d, e, f, g);
```

```
  input s1, s0;
```

```
  output a, b, c, d, e, f, g;
```

```
  assign a = ~s0;
```

```
  assign b = 1;
```

```
  assign c = ~s1;
```

```
  assign d = ~s0;
```

```
  assign e = ~s0;
```

```
  assign f = ~s1 & ~s0;
```

```
  assign g = s1 & ~s0;
```

```
endmodule
```

```
module adder_display (x, y, a, b, c, d, e, f, g);
```

```
  input x, y;
```

```
  output a, b, c, d, e, f, g;
```

```
  wire w1, w0; must be computed  
all the time, unlike reg
```

```
  adder U1 (x, y, w1, w0);
```


```
  display U2 (w1, w0, a, b, c, d, e, f, g);
```

```
endmodule
```



# Putting it all together

Top-level module

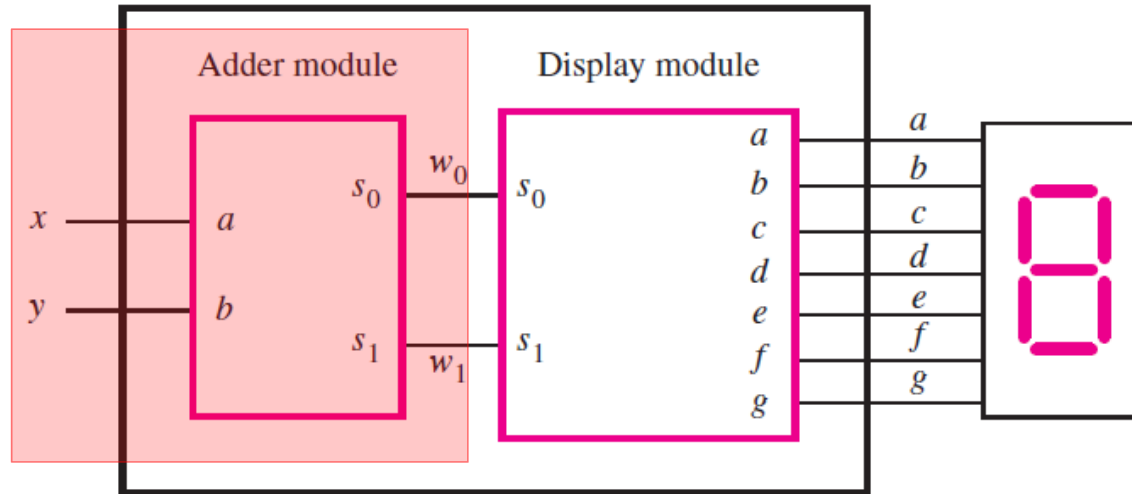

```
// An adder module
```

```
module adder (a, b, s1, s0)
```

```
  input a, b;
```

```
  output s1, s0;
```

```
  assign s1 = a & b;
```

```
  assign s0 = a ^ b;
```

```
endmodule
```

```
// A module for driving a 7-segment display
```

```
module display (s1, s0, a, b, c, d, e, f, g);
```

```
  input s1, s0;
```

```
  output a, b, c, d, e, f, g;
```

```
  assign a = ~s0;
```

```
  assign b = 1;
```

```
  assign c = ~s1;
```

```
  assign d = ~s0;
```

```
  assign e = ~s0;
```

```
  assign f = ~s1 & ~s0;
```

```
  assign g = s1 & ~s0;
```

```
endmodule
```

```
module adder_display (x, y, a, b, c, d, e, f, g);
```

```
  input x, y;
```

```
  output a, b, c, d, e, f, g;
```

```
  wire w1, w0;
```


```
  adder U1 (x, y, w1, w0);
```

```
  display U2 (w1, w0, a, b, c, d, e, f, g);
```

```
endmodule
```

# Putting it all together

Top-level module

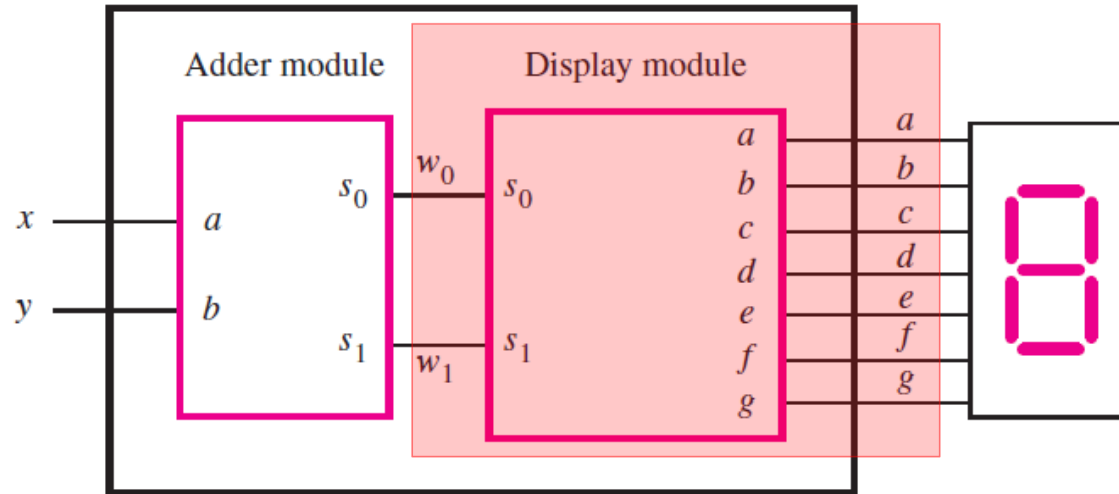

```
// An adder module
```

```
module adder (a, b, s1, s0)
```

```
  input a, b;
```

```
  output s1, s0;
```

```
  assign s1 = a & b;
```

```
  assign s0 = a ^ b;
```

```
endmodule
```

```
// A module for driving a 7-segment display
```

```
module display (s1, s0, a, b, c, d, e, f, g);
```

```
  input s1, s0;
```

```
  output a, b, c, d, e, f, g;
```

```
  assign a = ~s0;
```

```
  assign b = 1;
```

```
  assign c = ~s1;
```

```
  assign d = ~s0;
```

```
  assign e = ~s0;
```

```
  assign f = ~s1 & ~s0;
```

```
  assign g = s1 & ~s0;
```

```
endmodule
```

```
module adder_display (x, y, a, b, c, d, e, f, g);
```

```
  input x, y;
```

```
  output a, b, c, d, e, f, g;
```

```
  wire w1, w0;
```

```
  adder U1 (x, y, w1, w0);
```

```
  display U2 (w1, w0, a, b, c, d, e, f, g);
```

```
endmodule
```

**Questions?**

**THE END**