

CprE 2810: Digital Logic

Instructor: Alexander Stoytchev

<http://www.ece.iastate.edu/~alexs/classes/>

Examples of Solved Problems

*CprE 281: Digital Logic
Iowa State University, Ames, IA
Copyright © Alexander Stoytchev*

Administrative Stuff

- **HW4 is due today**

Administrative Stuff

- **HW5 is out**
- **It is due on Monday Sep 30 @ 10pm.**
- **It is posted on the class web page**
- **I also sent you an e-mail with the link.**
- **You can use this as a preparation for the exam.**

Administrative Stuff

- **Midterm Exam #1**
- **When: Friday Sep 27.**
- **What: Chapter 1 and Chapter 2 plus number systems**
- **The exam will be closed book but open notes
(you can bring up to 3 pages of handwritten notes).**
- **It will be in this room.**
- **Review session: This Wednesday during lecture**

Topics for the Midterm Exam

- **Binary Numbers**
- **Octal Numbers**
- **Hexadecimal Numbers**
- **Conversion between the different number systems**
- **Truth Tables**
- **Boolean Algebra**
- **Logic Gates**
- **Circuit Synthesis with AND, OR, NOT**
- **Circuit Synthesis with NAND, NOR**
- **Converting an AND/OR/NOT circuit to NAND circuit**
- **Converting an AND/OR/NOT circuit to NOR circuit**
- **SOP and POS expressions**

Topics for the Midterm Exam

- **Mapping a Circuit to Verilog code**
- **Mapping Verilog code to a circuit**
- **Multiplexers**
- **Venn Diagrams**
- **K-maps for 2, 3, and 4 variables**
- **Minimization of Boolean expressions using theorems**
- **Minimization of Boolean expressions with K-maps**

- **Incompletely specified functions (with don't cares)**
- **Functions with multiple outputs**
- **Something from Star Wars**

**All possible Boolean functions
with two input variables**

**There are 16 possible Boolean functions
with two input variables**

There are 16 possible Boolean functions with two input variables

x	y	F_0	F_1	F_2	F_3	F_4	F_5	F_6	F_7	F_8	F_9	F_{10}	F_{11}	F_{12}	F_{13}	F_{14}	F_{15}
0	0	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
0	1	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	0	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	1	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1



constant 0



constant 1

**There are 16 possible Boolean functions
with two input variables**

x	y	F_0	F_1	F_2	F_3	F_4	F_5	F_6	F_7	F_8	F_9	F_{10}	F_{11}	F_{12}	F_{13}	F_{14}	F_{15}
0	0	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
0	1	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	0	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	1	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1



NOR(x, y)



OR(x, y)

There are 16 possible Boolean functions with two input variables

x	y	F_0	F_1	F_2	F_3	F_4	F_5	F_6	F_7	F_8	F_9	F_{10}	F_{11}	F_{12}	F_{13}	F_{14}	F_{15}
0	0	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
0	1	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	0	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	1	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1

$$m_1 = \bar{x} \bar{y}$$

$$M_1 = x + \bar{y}$$

There are 16 possible Boolean functions with two input variables

x	y	F_0	F_1	F_2	F_3	F_4	F_5	F_6	F_7	F_8	F_9	F_{10}	F_{11}	F_{12}	F_{13}	F_{14}	F_{15}
0	0	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
0	1	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	0	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	1	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1



NOT(x)



x

There are 16 possible Boolean functions with two input variables

x	y	F ₀	F ₁	F ₂	F ₃	F ₄	F ₅	F ₆	F ₇	F ₈	F ₉	F ₁₀	F ₁₁	F ₁₂	F ₁₃	F ₁₄	F ₁₅
0	0	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
0	1	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	0	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	1	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1

$$m_2 = x \bar{y}$$

$$M_2 = \bar{x} + y$$

**There are 16 possible Boolean functions
with two input variables**

x	y	F_0	F_1	F_2	F_3	F_4	F_5	F_6	F_7	F_8	F_9	F_{10}	F_{11}	F_{12}	F_{13}	F_{14}	F_{15}
0	0	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
0	1	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	0	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	1	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1



NOT(y)




y

There are 16 possible Boolean functions with two input variables

x	y	F_0	F_1	F_2	F_3	F_4	F_5	F_6	F_7	F_8	F_9	F_{10}	F_{11}	F_{12}	F_{13}	F_{14}	F_{15}
0	0	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
0	1	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	0	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	1	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1




XOR(x, y)

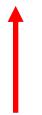

XNOR(x, y)

**There are 16 possible Boolean functions
with two input variables**

x	y	F_0	F_1	F_2	F_3	F_4	F_5	F_6	F_7	F_8	F_9	F_{10}	F_{11}	F_{12}	F_{13}	F_{14}	F_{15}
0	0	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
0	1	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	0	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	1	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1

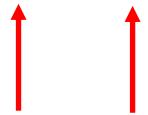

NAND(x, y) AND(x, y)

There are 16 possible Boolean functions with two input variables

x	y	F_0	F_1	F_2	F_3	F_4	F_5	F_6	F_7	F_8	F_9	F_{10}	F_{11}	F_{12}	F_{13}	F_{14}	F_{15}
0	0	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
0	1	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	0	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	1	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1

0 NOR m_1 \bar{x} m_2 \bar{y} XOR NAND AND XNOR y M_2 x M_1 OR 1

There are 16 possible Boolean functions with two input variables

x	y	F_0	F_1	F_2	F_3	F_4	F_5	F_6	F_7	F_8	F_9	F_{10}	F_{11}	F_{12}	F_{13}	F_{14}	F_{15}
0	0	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
0	1	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	0	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	1	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1

$0 \quad m_0 \quad m_1 \quad \bar{x} \quad m_2 \quad \bar{y} \quad \text{XOR} \quad M_3 \quad m_3 \quad \text{XNOR} \quad y \quad M_2 \quad x \quad M_1 \quad M_0 \quad 1$

There are 16 possible Boolean functions with two input variables

x	y	F_0	F_1	F_2	F_3	F_4	F_5	F_6	F_7	F_8	F_9	F_{10}	F_{11}	F_{12}	F_{13}	F_{14}	F_{15}
0	0	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
0	1	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	0	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	1	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1

0 m_0 m_1 \bar{x} m_2 \bar{y} $m_1 + m_2$ M_3 m_3 $M_1 \bullet M_2$ y M_2 x M_1 M_0 1





There are 16 possible Boolean functions with two input variables

x	y	F_0	F_1	F_2	F_3	F_4	F_5	F_6	F_7	F_8	F_9	F_{10}	F_{11}	F_{12}	F_{13}	F_{14}	F_{15}
0	0	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
0	1	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	0	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	1	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1

0 m_0 m_1 $m_0 + m_1$ m_2 $m_0 + m_2$ $m_1 + m_2$ M_3 m_3 $M_1 \bullet M_2$ $M_0 \bullet M_2$ M_2 $M_0 \bullet M_1$ M_1 M_0 1

**K-Maps for all 16 possible functions
with two input variables**

K-Maps for the 16 functions

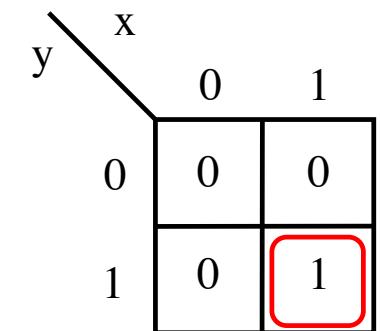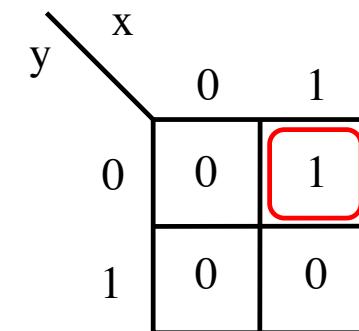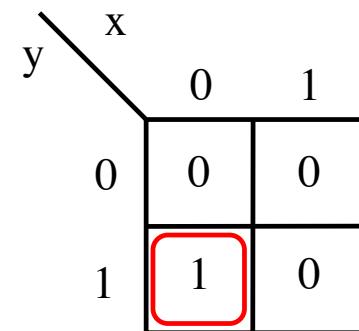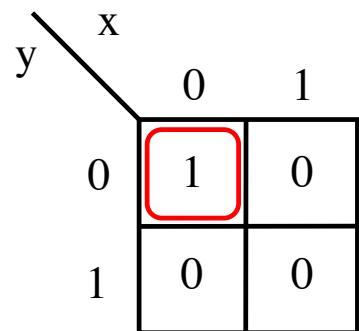

$\bar{x} \quad \bar{y}$

$\bar{x} y$

$x \bar{y}$

$x y$


F_1

F_2

F_4


F_8

K-Maps for the 16 functions

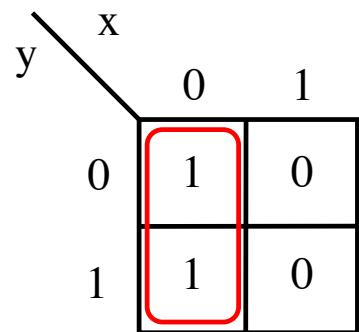


\bar{x}

F_3

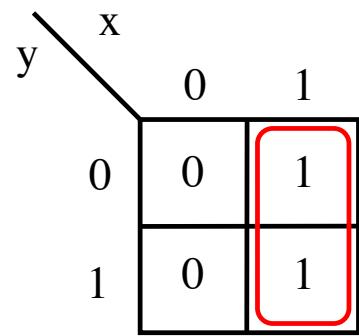


x

F_{12}

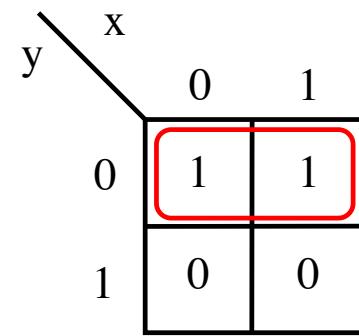

\bar{y}


F_5

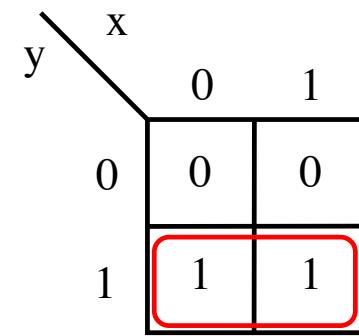

y


F_{10}

K-Maps for the 16 functions

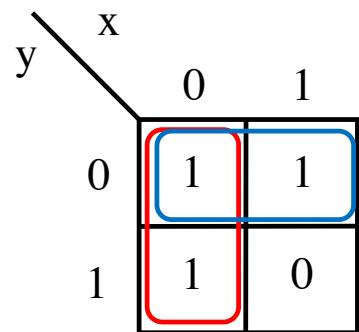


$$\overline{x} + \overline{y}$$

F_7

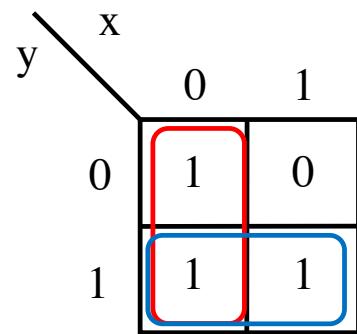


$$\overline{x} + y$$

F_{11}

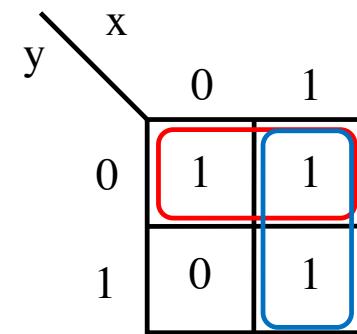

$$x + \overline{y}$$


F_{13}

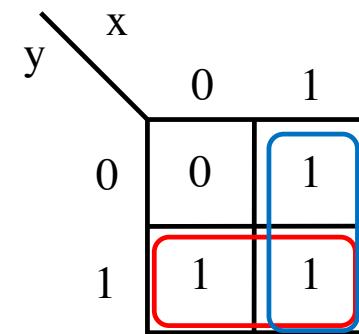

$$x + y$$


F_{14}

K-Maps for the 16 functions

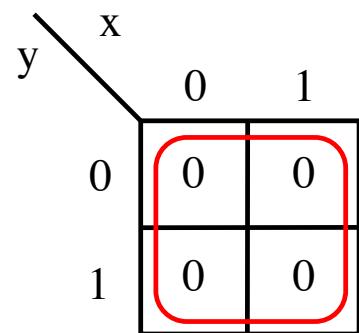

constant 0

F_0

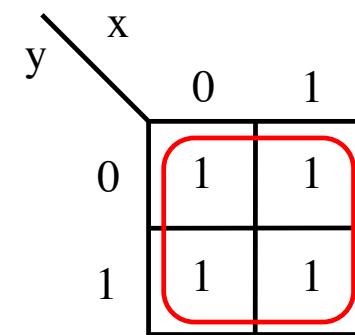

constant 1

F_{15}

**These are not valid groupings,
but they correspond to XOR and XNOR**

A Karnaugh map for two variables x and y. The x-axis is labeled 'x' and the y-axis is labeled 'y'. The map shows the following values:

	0	1
0	0	1
1	1	0


The cells (0,0) and (1,1) are highlighted with red diagonal lines, indicating they belong to the same group.

A Karnaugh map for two variables x and y. The x-axis is labeled 'x' and the y-axis is labeled 'y'. The map shows the following values:

	0	1
0	1	0
1	0	1

The cells (0,0) and (1,1) are highlighted with red diagonal lines, indicating they belong to the same group.

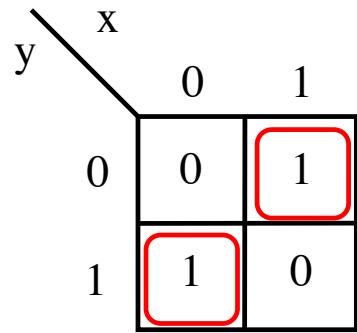**These are not valid groupings,
but they correspond to XOR and XNOR**




A truth table for the XOR function F_6 . The horizontal axis is labeled x and the vertical axis is labeled y , both with values 0 and 1. The table shows the output for all four combinations of x and y : (0,0) is 0, (0,1) is 1, (1,0) is 1, and (1,1) is 0. The cells containing 1 are highlighted with red boxes.

	x	0	1
y	0	0	1
0	1		
1		0	

XOR(x, y)

F_6

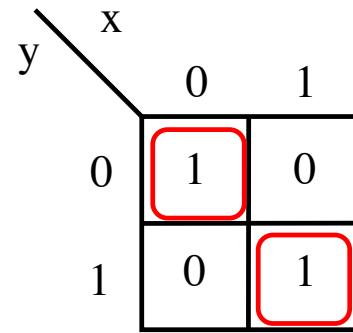

A truth table for the XNOR function F_9 . The horizontal axis is labeled x and the vertical axis is labeled y , both with values 0 and 1. The table shows the output for all four combinations of x and y : (0,0) is 1, (0,1) is 0, (1,0) is 0, and (1,1) is 1. The cells containing 1 are highlighted with red boxes.

	x	0	1
y	0	1	0
0	1		
1		0	1


XNOR(x, y)

F_9

The Link Between Truth Tables and Venn Diagrams


Place the minterms on the Venn diagram

A	B	
0	0	m_0
0	1	m_1
1	0	m_2
1	1	m_3

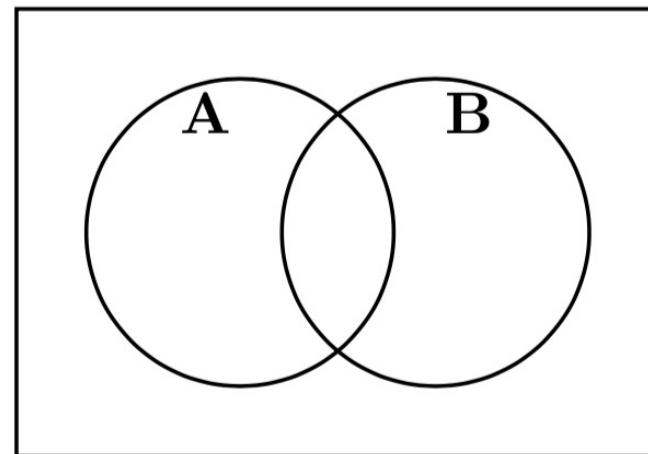


Place the minterms on the Venn diagram

A	B	
0	0	m_0
0	1	m_1
1	0	m_2
1	1	m_3

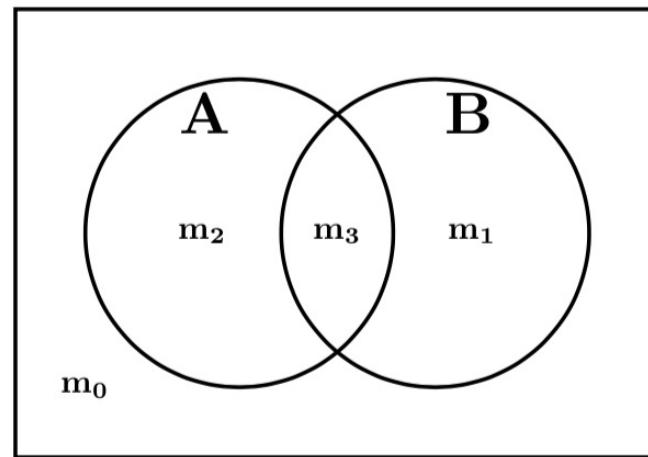


Color the Venn diagram for XOR

A	B	F
0	0	0
0	1	1
1	0	1
1	1	0

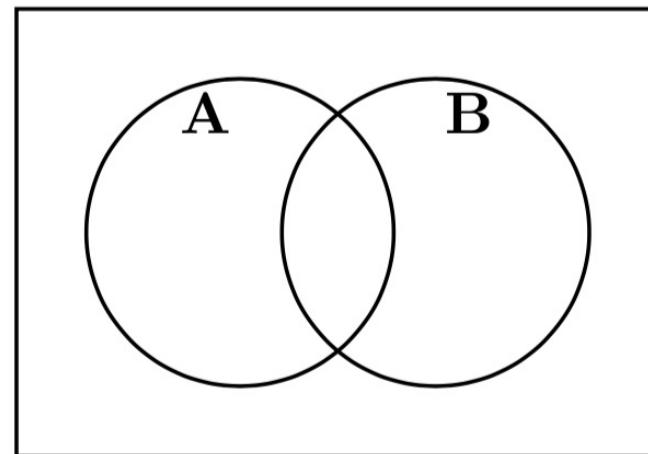


Color the Venn diagram for XOR

A	B	F
0	0	0
0	1	1
1	0	1
1	1	0

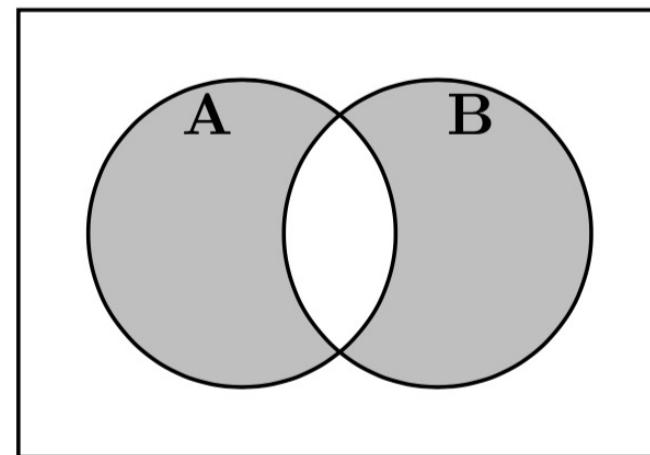

Color the Venn diagram for XOR


	A	B	F
m ₀	0	0	0
m ₁	0	1	1
m ₂	1	0	1
m ₃	1	1	0

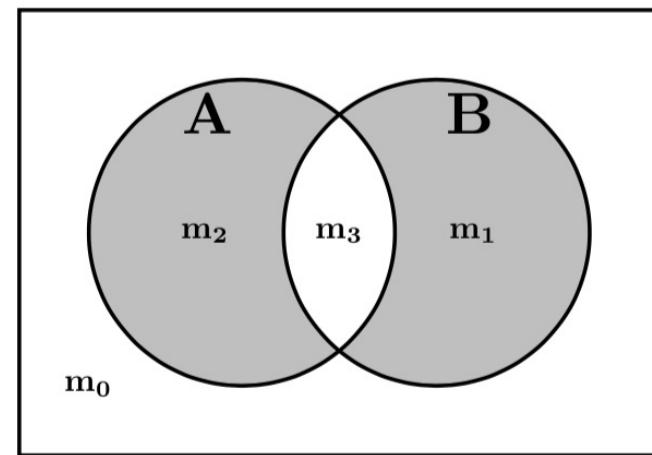

$$F = \overline{A} \overline{B} + A \overline{B}$$


Place the minterms on the Venn diagram

A	B	C	
0	0	0	m_0
0	0	1	m_1
0	1	0	m_2
0	1	1	m_3
1	0	0	m_4
1	0	1	m_5
1	1	0	m_6
1	1	1	m_7

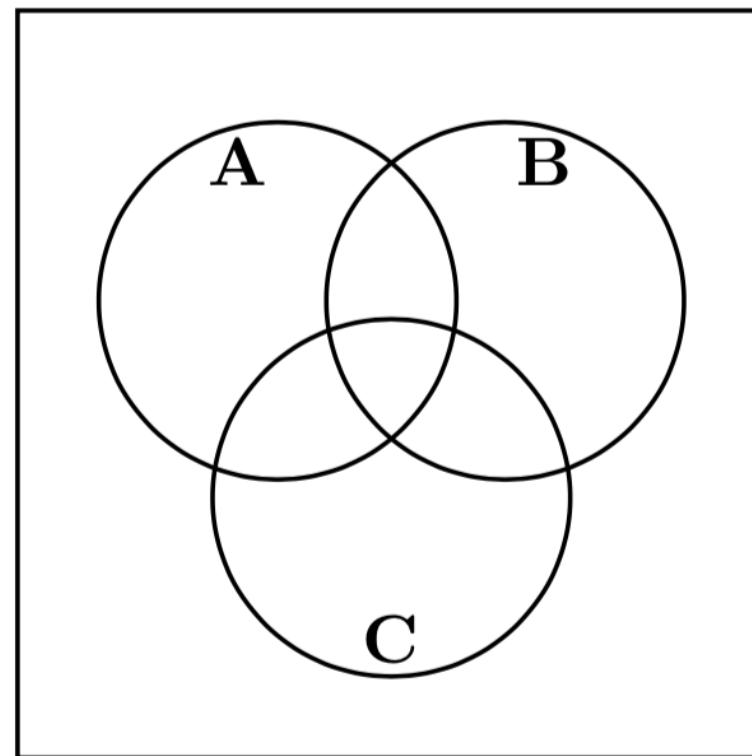


Place the minterms on the Venn diagram

A	B	C	
0	0	0	m_0
0	0	1	m_1
0	1	0	m_2
0	1	1	m_3
1	0	0	m_4
1	0	1	m_5
1	1	0	m_6
1	1	1	m_7

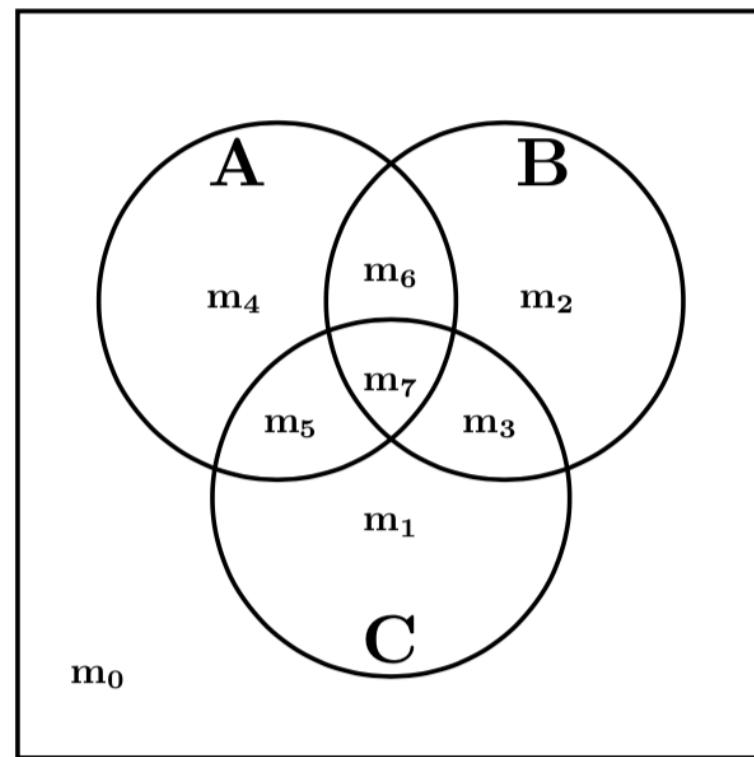


Color the Venn diagram for this function

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1

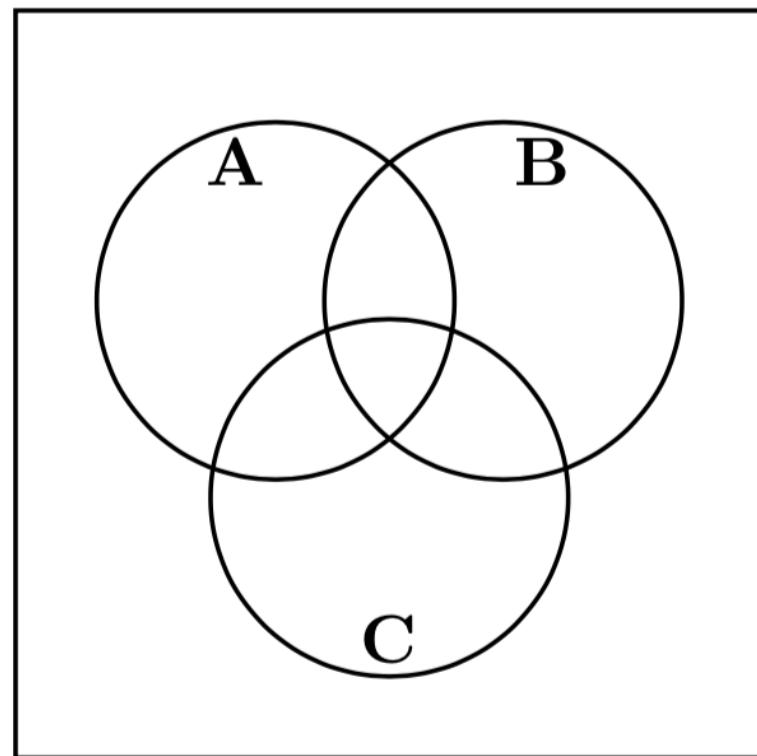


Color the Venn diagram for this function

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1

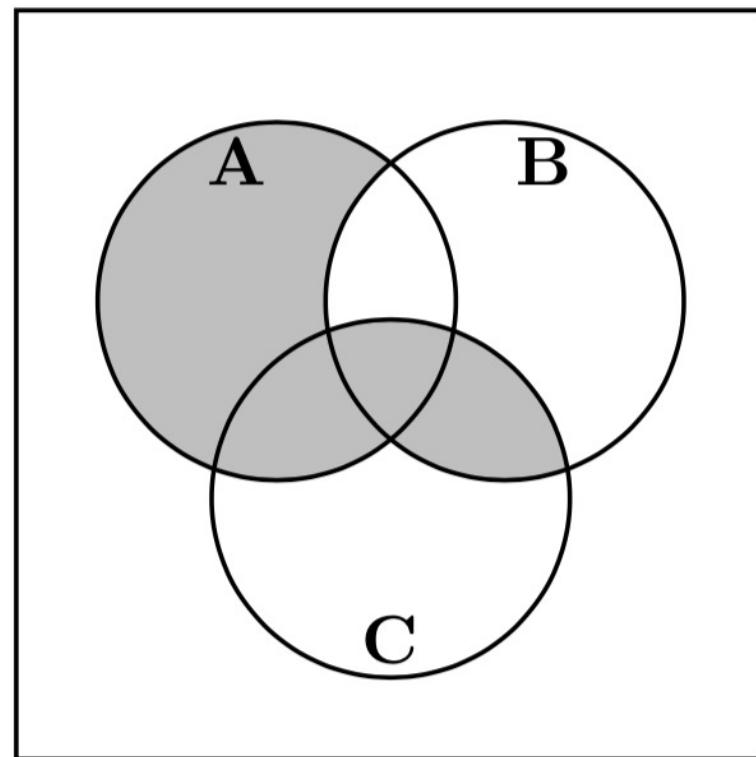


Place the minterms on the Venn diagram

	A	B	C	F
m ₀	0	0	0	0
m ₁	0	0	1	0
m ₂	0	1	0	0
m ₃	0	1	1	1
m ₄	1	0	0	1
m ₅	1	0	1	1
m ₆	1	1	0	0
m ₇	1	1	1	1

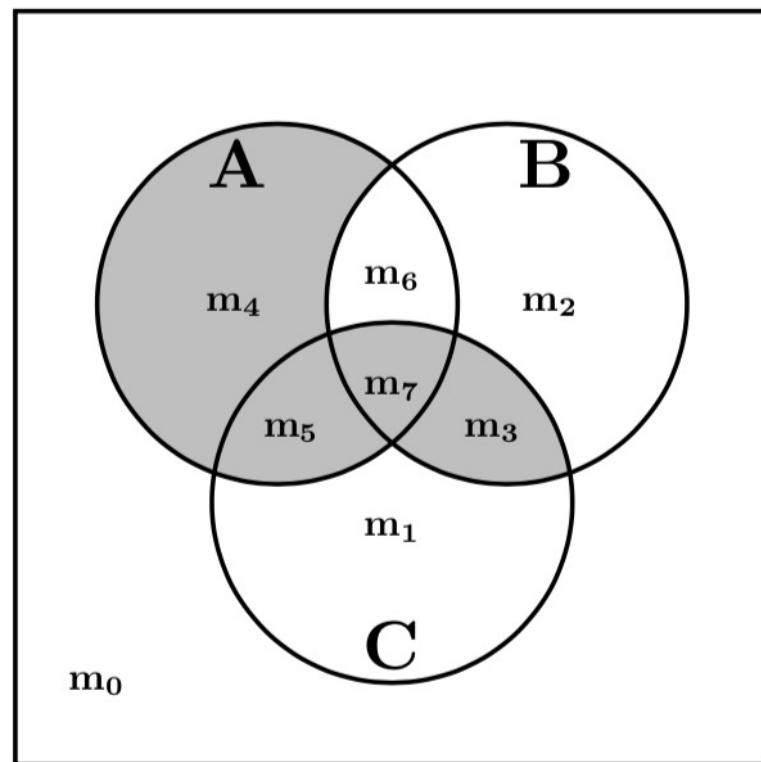


Color the Venn diagram for this function

A	B	C	F
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

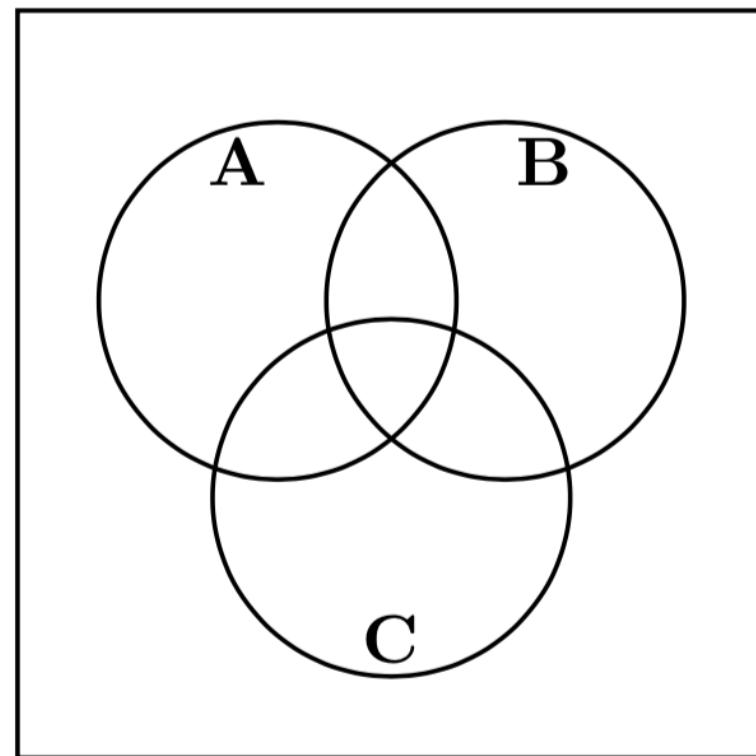


Color the Venn diagram for this function

A	B	C	F
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

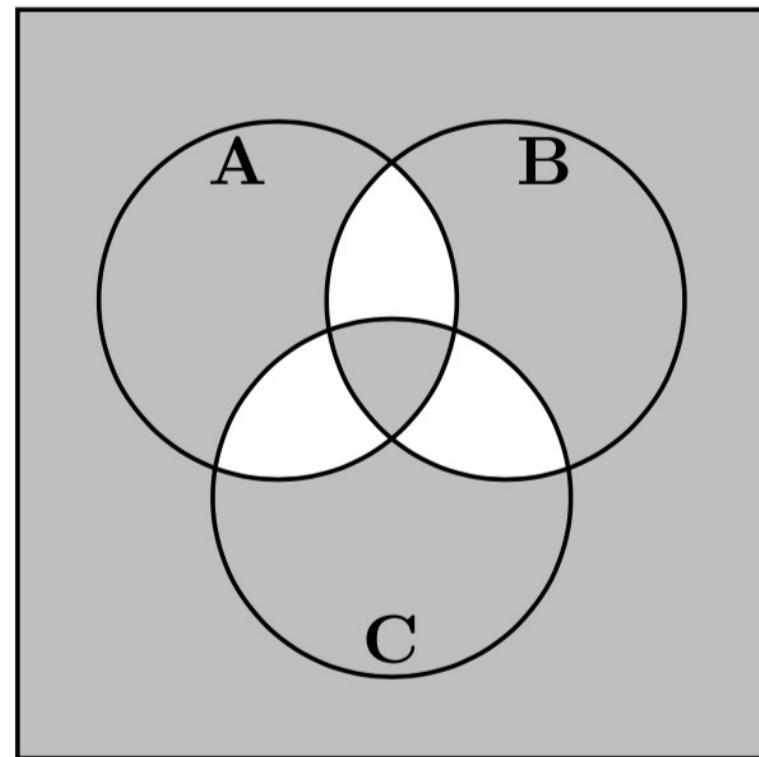


Place the minterms on the Venn diagram


	A	B	C	F
m ₀	0	0	0	1
m ₁	0	0	1	1
m ₂	0	1	0	1
m ₃	0	1	1	0
m ₄	1	0	0	1
m ₅	1	0	1	0
m ₆	1	1	0	0
m ₇	1	1	1	1

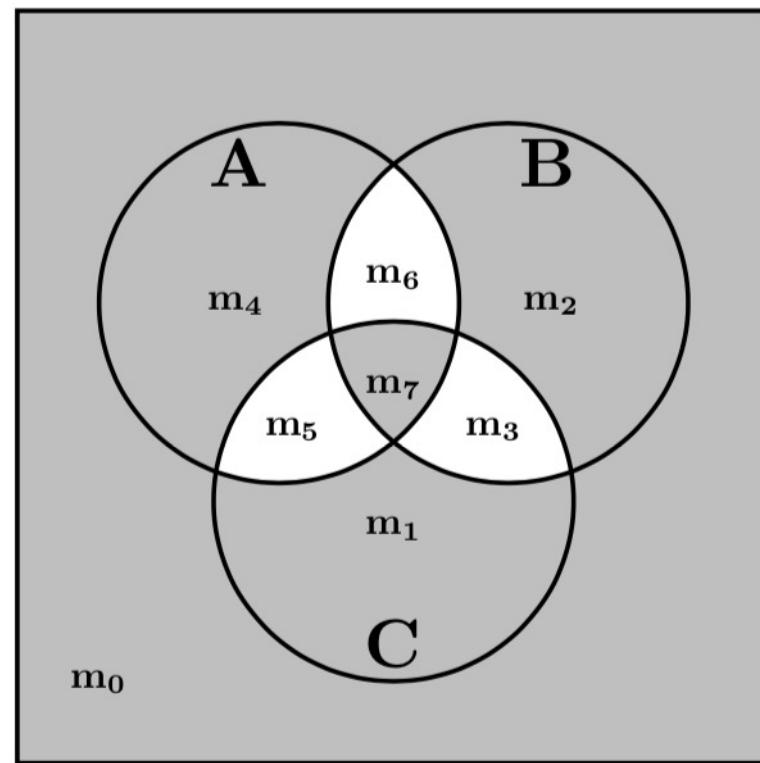

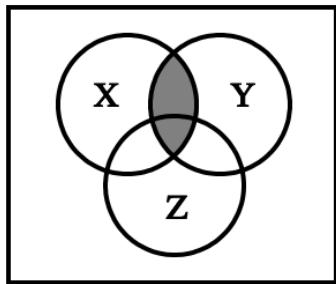
Write the expression that is represented by each of the three Venn diagrams:



(A)

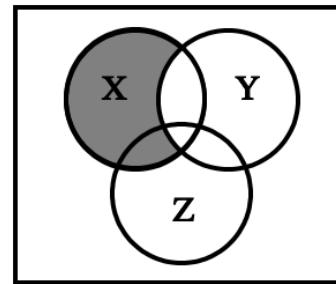


(B)

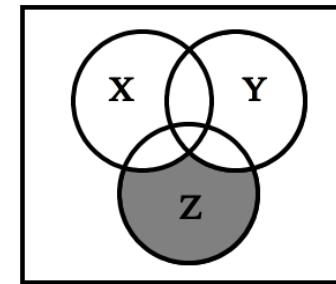


(C)

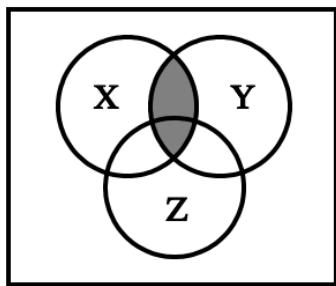
Write the expression that is represented by each of the three Venn diagrams:



(A)

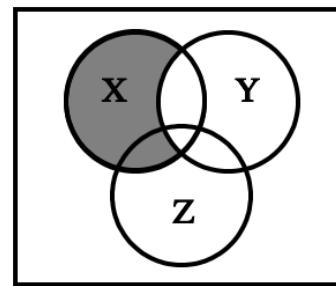

(B)

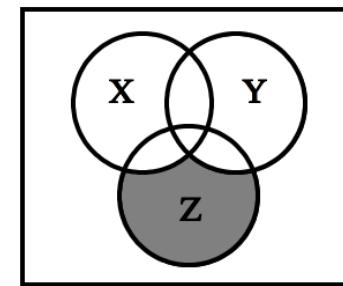

(C)

$X \cap Y$

$X \cap \overline{Y}$

$\overline{X} \cap \overline{Y} \cap Z$

Example 1

Determine if the following equation is valid

$$\bar{x}_1\bar{x}_3 + x_2x_3 + x_1\bar{x}_2 = \bar{x}_1x_2 + x_1x_3 + \bar{x}_2\bar{x}_3$$

$$\bar{x}_1\bar{x}_3 + x_2x_3 + x_1\bar{x}_2 \stackrel{?}{=} \bar{x}_1x_2 + x_1x_3 + \bar{x}_2\bar{x}_3$$

$$\bar{x}_1\bar{x}_3 + x_2x_3 + x_1\bar{x}_2 = \bar{x}_1x_2 + x_1x_3 + \bar{x}_2\bar{x}_3$$

?

LHS RHS

Left-Hand Side (LHS)

Row number	x_1	x_2	x_3	$\bar{x}_1 \bar{x}_3$	$x_2 x_3$	$x_1 \bar{x}_2$	f
0	0	0	0				
1	0	0	1				
2	0	1	0				
3	0	1	1				
4	1	0	0				
5	1	0	1				
6	1	1	0				
7	1	1	1				

Left-Hand Side (LHS)

Row number	x_1	x_2	x_3	$\bar{x}_1 \bar{x}_3$	$x_2 x_3$	$x_1 \bar{x}_2$	f
0	0	0	0	1	0	0	
1	0	0	1	0	0	0	
2	0	1	0	1	0	0	
3	0	1	1	0	1	0	
4	1	0	0	0	0	1	
5	1	0	1	0	0	1	
6	1	1	0	0	0	0	
7	1	1	1	0	1	0	

Left-Hand Side (LHS)

Row number	x_1	x_2	x_3	$\bar{x}_1 \bar{x}_3$	$x_2 x_3$	$x_1 \bar{x}_2$	f
0	0	0	0	1	0	0	1
1	0	0	1	0	0	0	0
2	0	1	0	1	0	0	1
3	0	1	1	0	1	0	1
4	1	0	0	0	0	1	1
5	1	0	1	0	0	1	1
6	1	1	0	0	0	0	0
7	1	1	1	0	1	0	1

Right-Hand Side (RHS)

Row number	x_1	x_2	x_3	\bar{x}_1x_2	x_1x_3	$\bar{x}_2 \bar{x}_3$	f
0	0	0	0				
1	0	0	1				
2	0	1	0				
3	0	1	1				
4	1	0	0				
5	1	0	1				
6	1	1	0				
7	1	1	1				

Right-Hand Side (RHS)

Row number	x_1	x_2	x_3	$\bar{x}_1 \bar{x}_2$	$x_1 x_3$	$\bar{x}_2 \bar{x}_3$	f
0	0	0	0	0	0	1	
1	0	0	1	0	0	0	
2	0	1	0	1	0	0	
3	0	1	1	1	0	0	
4	1	0	0	0	0	1	
5	1	0	1	0	1	0	
6	1	1	0	0	0	0	
7	1	1	1	0	1	0	

Right-Hand Side (RHS)

Row number	x_1	x_2	x_3	$\bar{x}_1 \bar{x}_2$	$x_1 x_3$	$\bar{x}_2 \bar{x}_3$	f
0	0	0	0	0	0	1	1
1	0	0	1	0	0	0	0
2	0	1	0	1	0	0	1
3	0	1	1	1	0	0	1
4	1	0	0	0	0	1	1
5	1	0	1	0	1	0	1
6	1	1	0	0	0	0	0
7	1	1	1	0	1	0	1

$$\overbrace{\bar{x}_1\bar{x}_3 + x_2x_3 + x_1\bar{x}_2}^{\text{LHS}} = \overbrace{\bar{x}_1x_2 + x_1x_3 + \bar{x}_2\bar{x}_3}^{\text{RHS}}$$

?

f	f
1	1
0	0
1	1
1	1
1	1
1	1
0	0
1	1

They are equal.

Example 2

Design the minimum-cost product-of-sums expression for the function

$$f(x_1, x_2, x_3) = \sum m(0, 2, 4, 5, 6, 7)$$

Minterms and Maxterms (with three variables)

Row number	x_1	x_2	x_3	Minterm	Maxterm
0	0	0	0	$m_0 = \bar{x}_1 \bar{x}_2 \bar{x}_3$	$M_0 = x_1 + x_2 + x_3$
1	0	0	1	$m_1 = \bar{x}_1 \bar{x}_2 x_3$	$M_1 = x_1 + x_2 + \bar{x}_3$
2	0	1	0	$m_2 = \bar{x}_1 x_2 \bar{x}_3$	$M_2 = x_1 + \bar{x}_2 + x_3$
3	0	1	1	$m_3 = \bar{x}_1 x_2 x_3$	$M_3 = x_1 + \bar{x}_2 + \bar{x}_3$
4	1	0	0	$m_4 = x_1 \bar{x}_2 \bar{x}_3$	$M_4 = \bar{x}_1 + x_2 + x_3$
5	1	0	1	$m_5 = x_1 \bar{x}_2 x_3$	$M_5 = \bar{x}_1 + x_2 + \bar{x}_3$
6	1	1	0	$m_6 = x_1 x_2 \bar{x}_3$	$M_6 = \bar{x}_1 + \bar{x}_2 + x_3$
7	1	1	1	$m_7 = x_1 x_2 x_3$	$M_7 = \bar{x}_1 + \bar{x}_2 + \bar{x}_3$

[Figure 2.22 from the textbook]

Minterms and Maxterms (with three variables)

Row number	x_1	x_2	x_3	Minterm	Maxterm
0	0	0	0	$m_0 = \bar{x}_1 \bar{x}_2 \bar{x}_3$	$M_0 = x_1 + x_2 + x_3$
1	0	0	1	$m_1 = \bar{x}_1 \bar{x}_2 x_3$	$M_1 = x_1 + x_2 + \bar{x}_3$
2	0	1	0	$m_2 = \bar{x}_1 x_2 \bar{x}_3$	$M_2 = x_1 + \bar{x}_2 + x_3$
3	0	1	1	$m_3 = \bar{x}_1 x_2 x_3$	$M_3 = x_1 + \bar{x}_2 + \bar{x}_3$
4	1	0	0	$m_4 = x_1 \bar{x}_2 \bar{x}_3$	$M_4 = \bar{x}_1 + x_2 + x_3$
5	1	0	1	$m_5 = x_1 \bar{x}_2 x_3$	$M_5 = \bar{x}_1 + x_2 + \bar{x}_3$
6	1	1	0	$m_6 = x_1 x_2 \bar{x}_3$	$M_6 = \bar{x}_1 + \bar{x}_2 + x_3$
7	1	1	1	$m_7 = x_1 x_2 x_3$	$M_7 = \bar{x}_1 + \bar{x}_2 + \bar{x}_3$

The function is
1 for these rows

Minterms and Maxterms (with three variables)

Row number	x_1	x_2	x_3	Minterm	Maxterm
0	0	0	0	$m_0 = \bar{x}_1 \bar{x}_2 \bar{x}_3$	$M_0 = x_1 + x_2 + x_3$
1	0	0	1	$m_1 = \bar{x}_1 \bar{x}_2 x_3$	$M_1 = x_1 + x_2 + \bar{x}_3$
2	0	1	0	$m_2 = \bar{x}_1 x_2 \bar{x}_3$	$M_2 = x_1 + \bar{x}_2 + x_3$
3	0	1	1	$m_3 = \bar{x}_1 x_2 x_3$	$M_3 = x_1 + \bar{x}_2 + \bar{x}_3$
4	1	0	0	$m_4 = x_1 \bar{x}_2 \bar{x}_3$	$M_4 = \bar{x}_1 + x_2 + x_3$
5	1	0	1	$m_5 = x_1 \bar{x}_2 x_3$	$M_5 = \bar{x}_1 + x_2 + \bar{x}_3$
6	1	1	0	$m_6 = x_1 x_2 \bar{x}_3$	$M_6 = \bar{x}_1 + \bar{x}_2 + x_3$
7	1	1	1	$m_7 = x_1 x_2 x_3$	$M_7 = \bar{x}_1 + \bar{x}_2 + \bar{x}_3$

The function is
1 for these rows

The function is
0 for these rows

Two different ways to specify the same function f of three variables

$$f(x_1, x_2, x_3) = \sum m(0, 2, 4, 5, 6, 7)$$

$$f(x_1, x_2, x_3) = \prod M(1, 3)$$

Two different ways to specify the same function f of three variables

$$f(x_1, x_2, x_3) = \sum m(0, 2, 4, 5, 6, 7)$$

$$f(x_1, x_2, x_3) = \prod M(1, 3)$$

$$= M_1 \bullet M_3$$

$$= (x_1 + x_2 + \bar{x}_3) \bullet (x_1 + \bar{x}_2 + \bar{x}_3)$$

The Minimum POS Expression

$$\begin{aligned}f(x_1, x_2, x_3) &= (x_1 + x_2 + \overline{x}_3) \bullet (x_1 + \overline{x}_2 + \overline{x}_3) \\&= (x_1 + \overline{x}_3 + x_2) \bullet (x_1 + \overline{x}_3 + \overline{x}_2) \\&= (x_1 + \overline{x}_3)\end{aligned}$$


Hint: Use the following Boolean Algebra theorem

14b. $(x + y) \bullet (x + \overline{y}) = x$

Alternative Solution Using K-Maps

x_1	x_2	x_3	
0	0	0	m_0
0	0	1	m_1
0	1	0	m_2
0	1	1	m_3
1	0	0	m_4
1	0	1	m_5
1	1	0	m_6
1	1	1	m_7

(a) Truth table

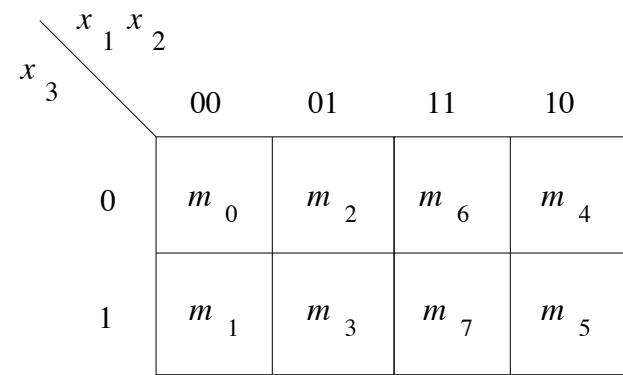


(b) Karnaugh map

Alternative Solution Using K-Maps

x_1	x_2	x_3	
0	0	0	m_0
0	0	1	m_1
0	1	0	m_2
0	1	1	m_3
1	0	0	m_4
1	0	1	m_5
1	1	0	m_6
1	1	1	m_7

(a) Truth table

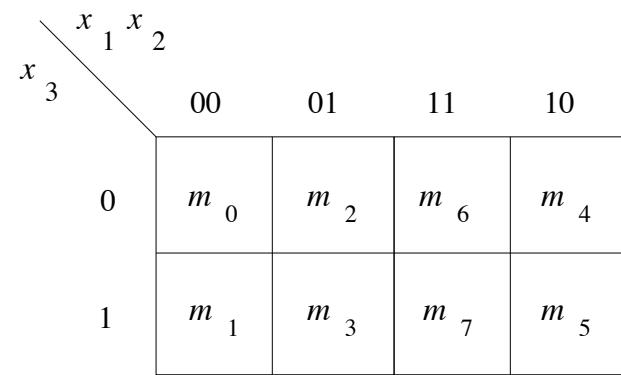


(b) Karnaugh map

Alternative Solution Using K-Maps

x_1	x_2	x_3	
0	0	0	m_0
0	0	1	m_1
0	1	0	m_2
0	1	1	m_3
1	0	0	m_4
1	0	1	m_5
1	1	0	m_6
1	1	1	m_7

(a) Truth table

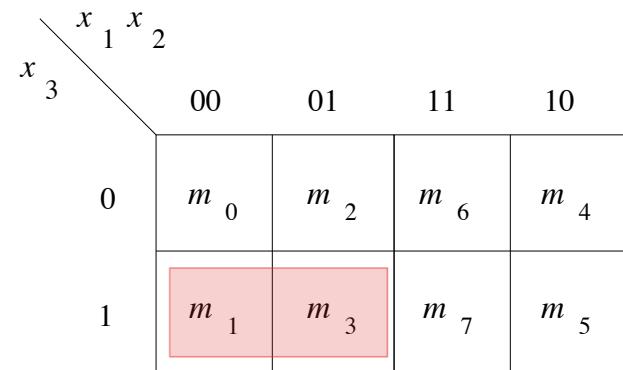

(b) Karnaugh map

Alternative Solution Using K-Maps


		x_1x_2	00	01	11	10	
		x_3	0	m_0	m_2	m_6	m_4
		1	m_1	m_3	m_7	m_5	

Alternative Solution Using K-Maps

A Karnaugh map for two variables x_1 and x_2 . The columns are labeled x_1x_2 with values 00, 01, 11, and 10. The rows are labeled x_3 with values 0 and 1. The map shows the following values:

		00	01	11	10	
		0	1	1	1	1
		1	0	0	1	1

Alternative Solution Using K-Maps

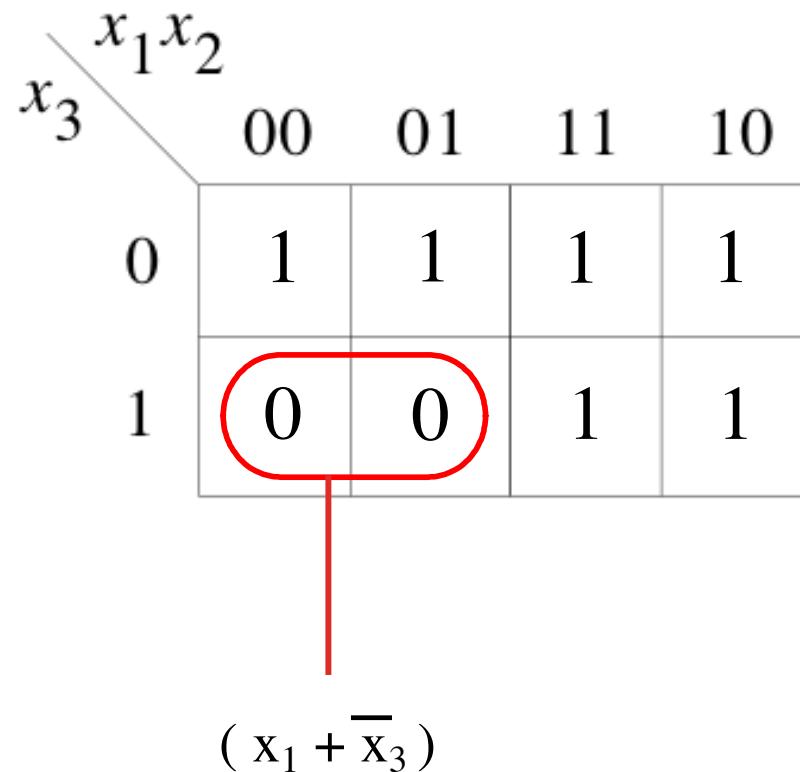

Example 3

Problem: A circuit that controls a given digital system has three inputs: x_1 , x_2 , and x_3 . It has to recognize three different conditions:

- Condition *A* is true if x_3 is true and either x_1 is true or x_2 is false
- Condition *B* is true if x_1 is true and either x_2 or x_3 is false
- Condition *C* is true if x_2 is true and either x_1 is true or x_3 is false

The control circuit must produce an output of 1 if at least two of the conditions *A*, *B*, and *C* are true. Design the simplest circuit that can be used for this purpose.

Condition A

Condition *A* is true if x_3 is true and either x_1 is true or x_2 is false

Condition A

Condition A is true if x_3 is true and either x_1 is true or x_2 is false

$$A = x_3(x_1 + \bar{x}_2) = x_3x_1 + x_3\bar{x}_2$$

Condition B

Condition *B* is true if x_1 is true and either x_2 or x_3 is false

Condition B

Condition B is true if x_1 is true and either x_2 or x_3 is false

$$B = x_1(\bar{x}_2 + \bar{x}_3) = x_1\bar{x}_2 + x_1\bar{x}_3$$

Condition C

Condition C is true if x_2 is true and either x_1 is true or x_3 is false

Condition C

Condition C is true if x_2 is true and either x_1 is true or x_3 is false

$$C = x_2(x_1 + \bar{x}_3) = x_2x_1 + x_2\bar{x}_3$$

The output of the circuit can be expressed as

$$f = AB + AC + BC$$

$$\begin{aligned}AB &= (x_3x_1 + x_3\bar{x}_2)(x_1\bar{x}_2 + x_1\bar{x}_3) \\&= x_3x_1x_1\bar{x}_2 + x_3x_1x_1\bar{x}_3 + x_3\bar{x}_2x_1\bar{x}_2 + x_3\bar{x}_2x_1\bar{x}_3 \\&= x_3x_1\bar{x}_2 + 0 + x_3\bar{x}_2x_1 + 0 \\&= x_1\bar{x}_2x_3\end{aligned}$$

The output of the circuit can be expressed as

$$f = AB + \boxed{AC} + BC$$

$$\begin{aligned} AC &= (x_3x_1 + x_3\bar{x}_2)(x_2x_1 + x_2\bar{x}_3) \\ &= x_3x_1x_2x_1 + x_3x_1x_2\bar{x}_3 + x_3\bar{x}_2x_2x_1 + x_3\bar{x}_2x_2\bar{x}_3 \\ &= x_3x_1x_2 + 0 + 0 + 0 \\ &= x_1x_2x_3 \end{aligned}$$

The output of the circuit can be expressed as

$$f = AB + AC + BC$$

$$\begin{aligned}BC &= (x_1\bar{x}_2 + x_1\bar{x}_3)(x_2x_1 + x_2\bar{x}_3) \\&= x_1\bar{x}_2x_2x_1 + x_1\bar{x}_2x_2\bar{x}_3 + x_1\bar{x}_3x_2x_1 + x_1\bar{x}_3x_2\bar{x}_3 \\&= 0 + 0 + x_1\bar{x}_3x_2 + x_1\bar{x}_3x_2 \\&= x_1x_2\bar{x}_3\end{aligned}$$


Finally, we get

$$\begin{aligned}f &= x_1\bar{x}_2x_3 + x_1x_2x_3 + x_1x_2\bar{x}_3 \\&= x_1(\bar{x}_2 + x_2)x_3 + x_1x_2(x_3 + \bar{x}_3) \\&= x_1x_3 + x_1x_2 \\&= x_1(x_3 + x_2)\end{aligned}$$

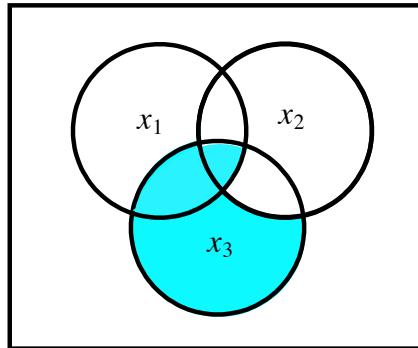Example 4


Solve the previous problem using Venn diagrams.

Venn Diagrams (find the areas that are shaded at least two times)




(a) Function A :

$$x_3x_1 + x_3\bar{x}_2$$

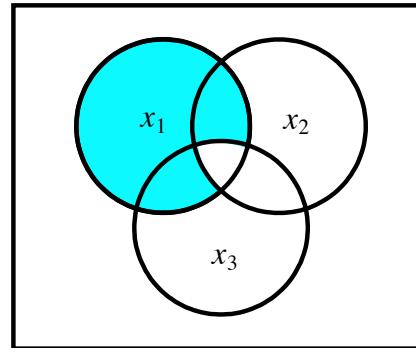


(b) Function B

$$x_1\bar{x}_2 + x_1\bar{x}_3$$

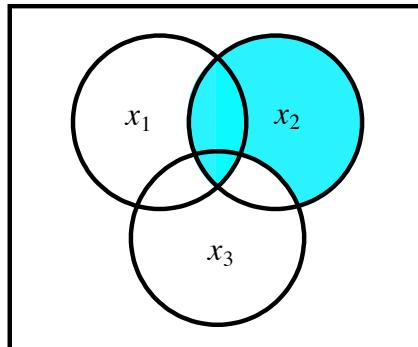

(c) Function C

$$x_2x_1 + x_2\bar{x}_3$$

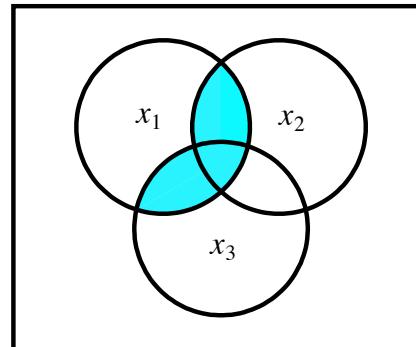

(d) Function f

$$x_1(x_3 + x_2)$$

[Figure 2.66 from the textbook]


Example 5

**Design the minimum-cost SOP and POS
expression for the function**

$$f(x_1, x_2, x_3, x_4) = \sum m(4, 6, 8, 10, 11, 12, 15) + D(3, 5, 7, 9)$$


Let's Use a K-Map
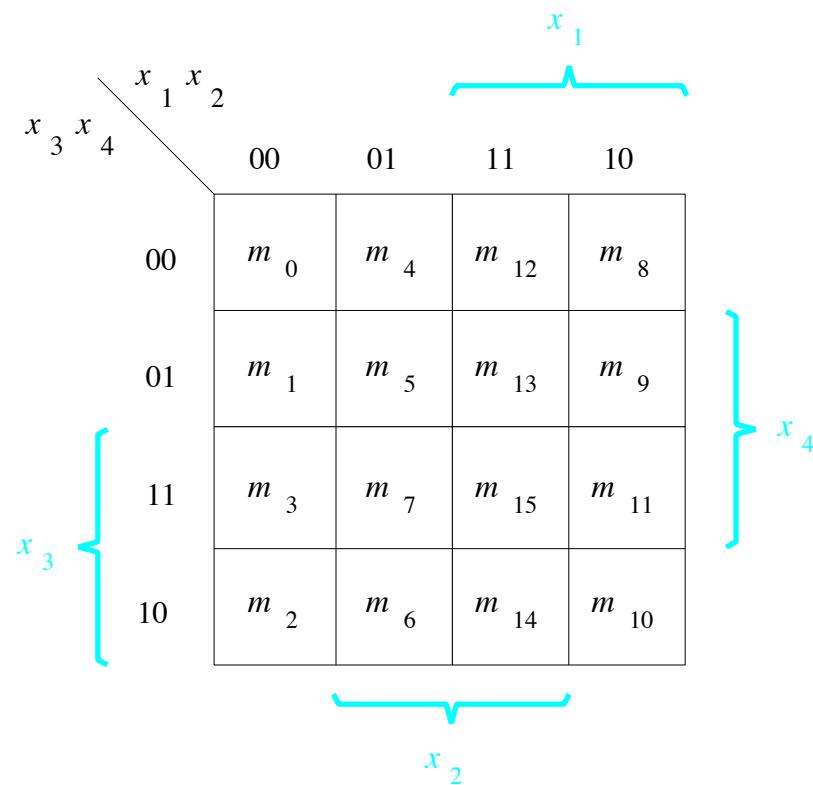
$$f(x_1, x_2, x_3, x_4) = \sum m(4, 6, 8, 10, 11, 12, 15) + D(3, 5, 7, 9)$$




Let's Use a K-Map
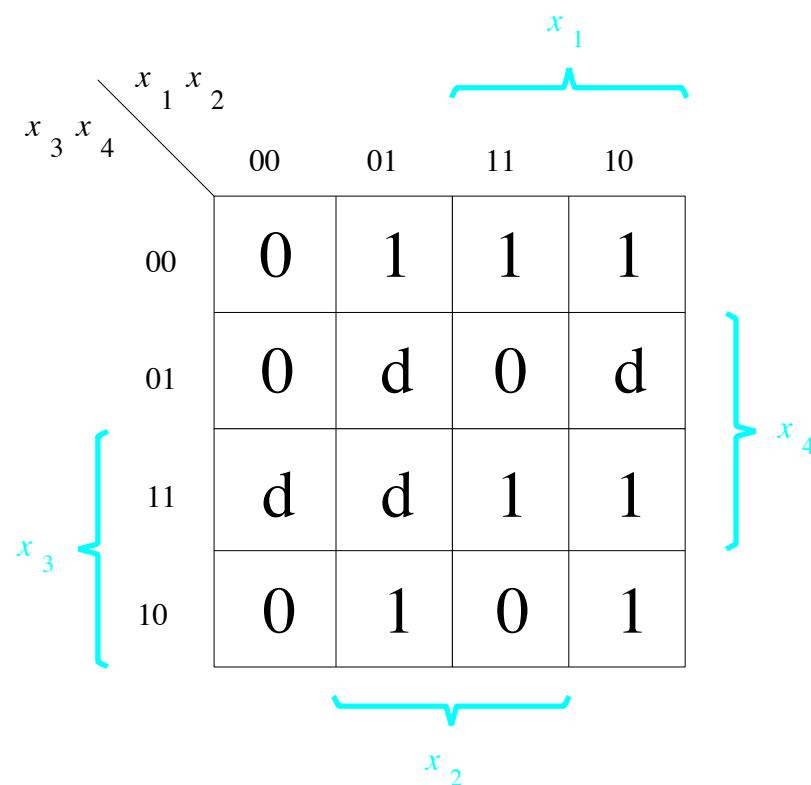
$$f(x_1, x_2, x_3, x_4) = \sum m(4, 6, 8, 10, 11, 12, 15) + D(3, 5, 7, 9)$$




Let's Use a K-Map
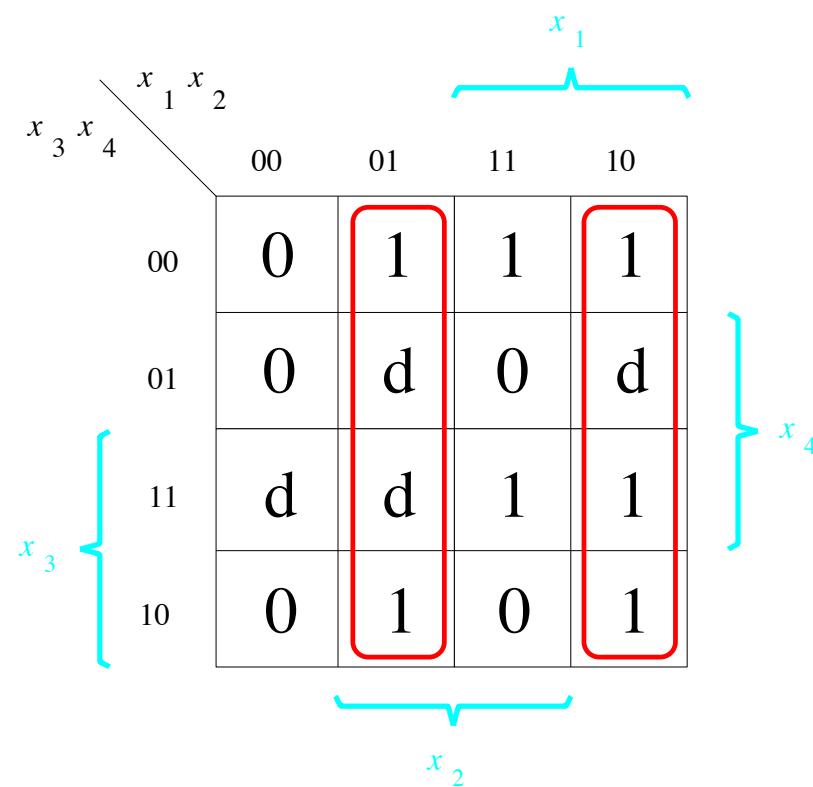
$$f(x_1, x_2, x_3, x_4) = \sum m(4, 6, 8, 10, 11, 12, 15) + D(3, 5, 7, 9)$$




Let's Use a K-Map
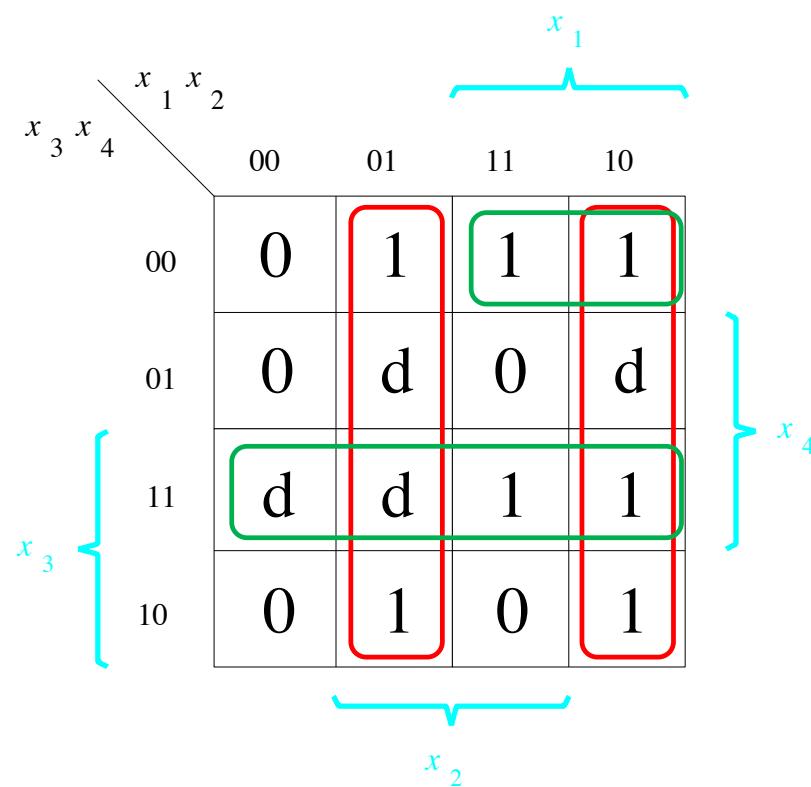
$$f(x_1, x_2, x_3, x_4) = \sum m(4, 6, 8, 10, 11, 12, 15) + D(3, 5, 7, 9)$$





Let's Use a K-Map
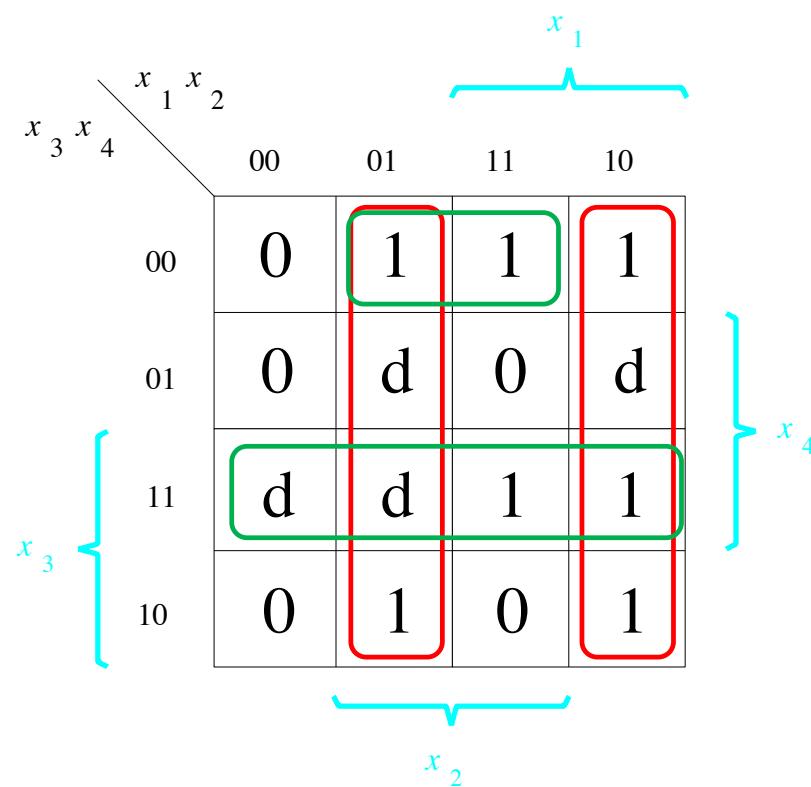
$$f(x_1, x_2, x_3, x_4) = \sum m(4, 6, 8, 10, 11, 12, 15) + D(3, 5, 7, 9)$$




Two Alternative Solutions
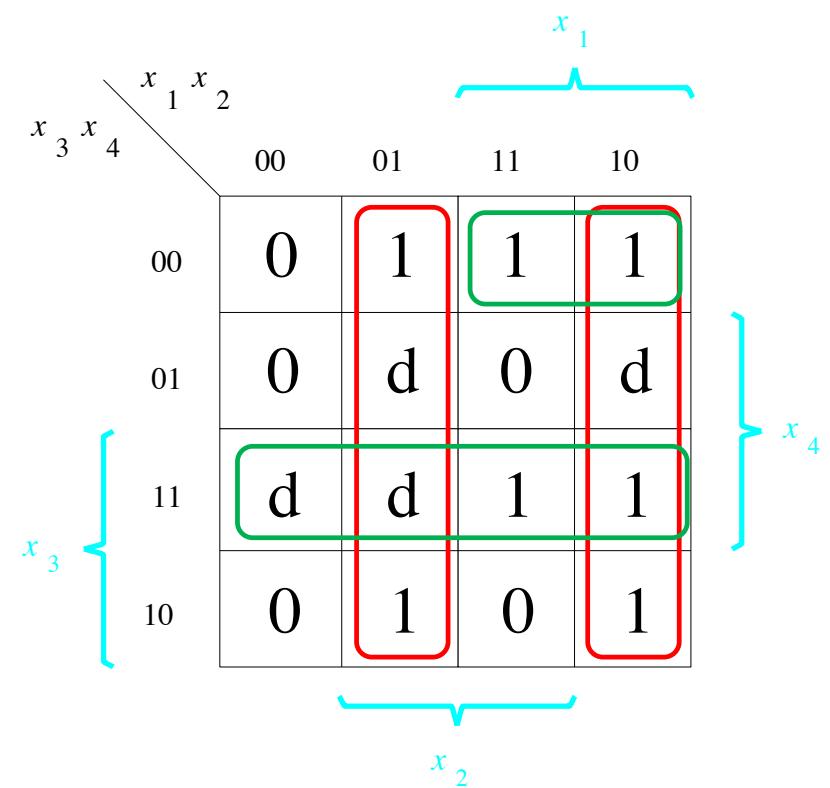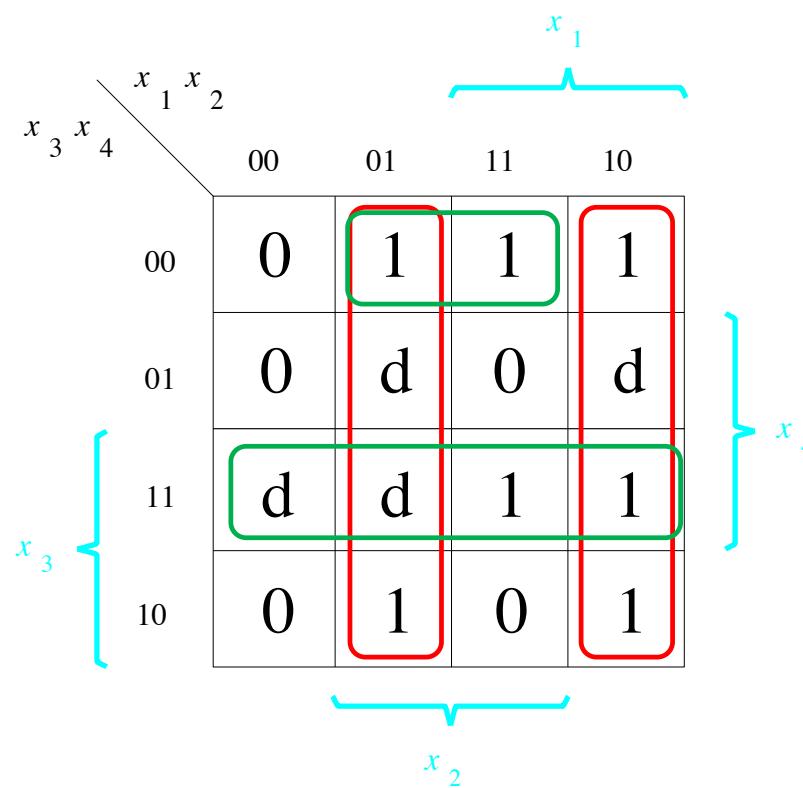
$$f(x_1, x_2, x_3, x_4) = \sum m(4, 6, 8, 10, 11, 12, 15) + D(3, 5, 7, 9)$$



The SOP Expression

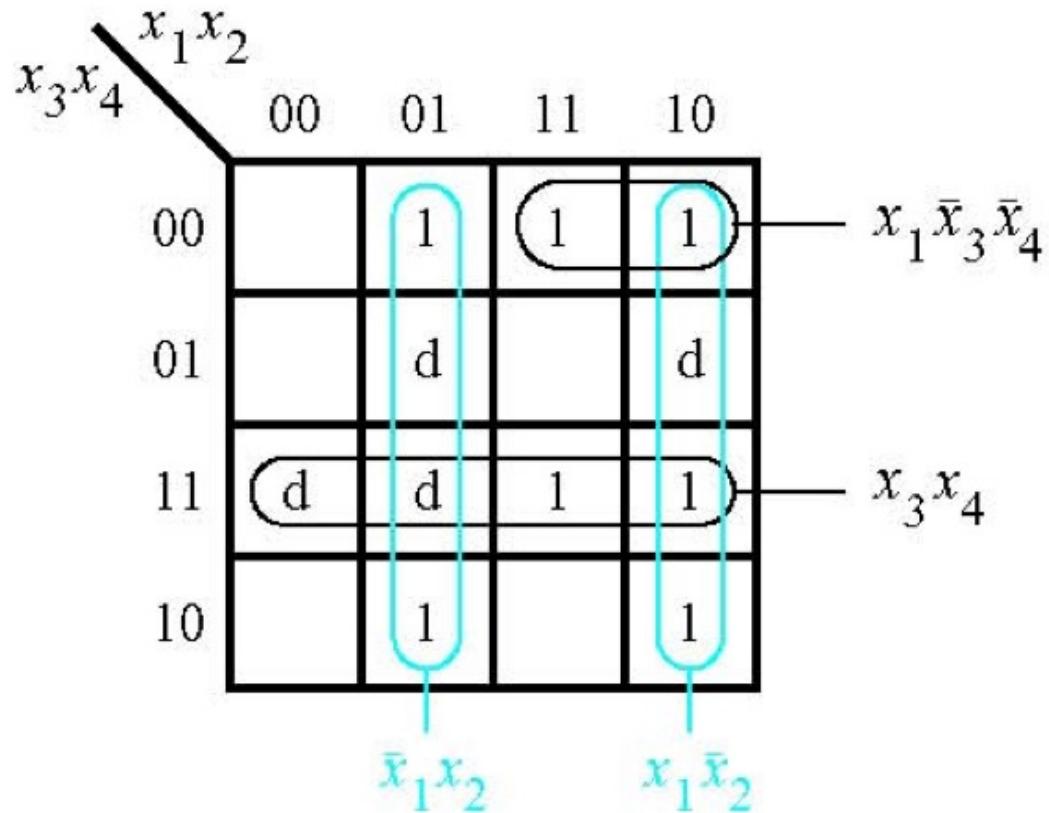


$$f = \overline{x_1} \ x_2 + x_1 \ \overline{x_2} + x_1 \ \overline{x_3} \ \overline{x_4} + x_3 \ x_4$$

[Figure 2.67a from the textbook]

What about the POS Expression?
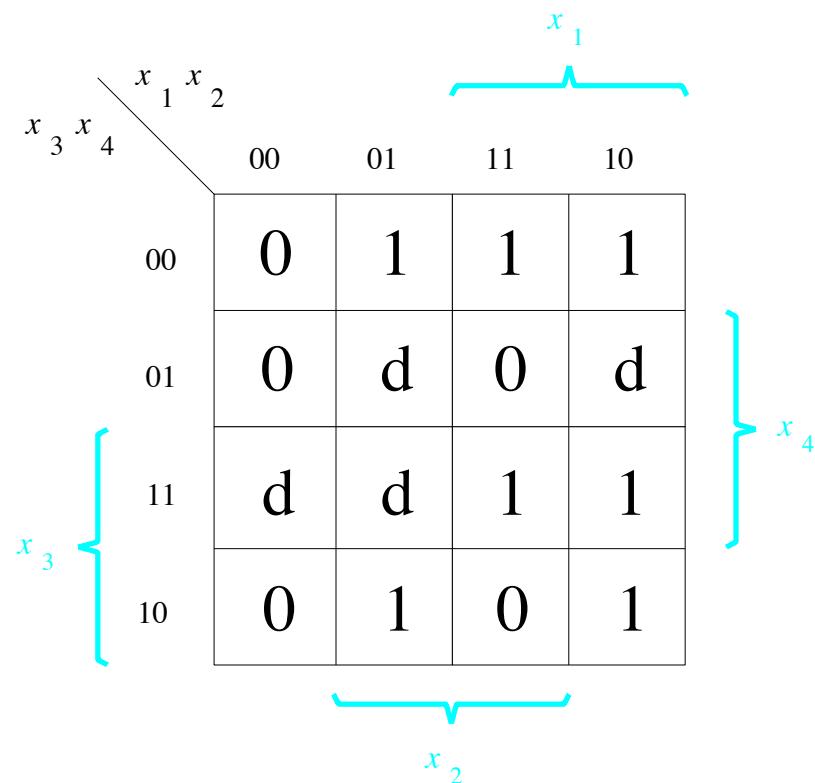
$$f(x_1, x_2, x_3, x_4) = \sum m(4, 6, 8, 10, 11, 12, 15) + D(3, 5, 7, 9)$$



A Karnaugh map for four variables x_1, x_2, x_3, x_4 . The columns are labeled 00, 01, 11, and 10. The rows are labeled 00, 01, 11, and 10. The map shows the following values:


00	0	1	1	1
01	0	d	0	d
11	d	d	1	1
10	0	1	0	1

Annotations with curly braces and arrows indicate the minterms and don't care terms:


- A brace on the left side groups rows 01 and 11, labeled x_3 .
- A brace at the top groups columns 00 and 01, labeled $x_1 x_2$.
- A brace on the right side groups columns 11 and 10, labeled x_4 .
- An arrow points from the top center to the value '1' in the cell (11, 10), labeled x_1 .
- An arrow points from the bottom center to the value '0' in the cell (10, 10), labeled x_2 .

What about the POS Expression?
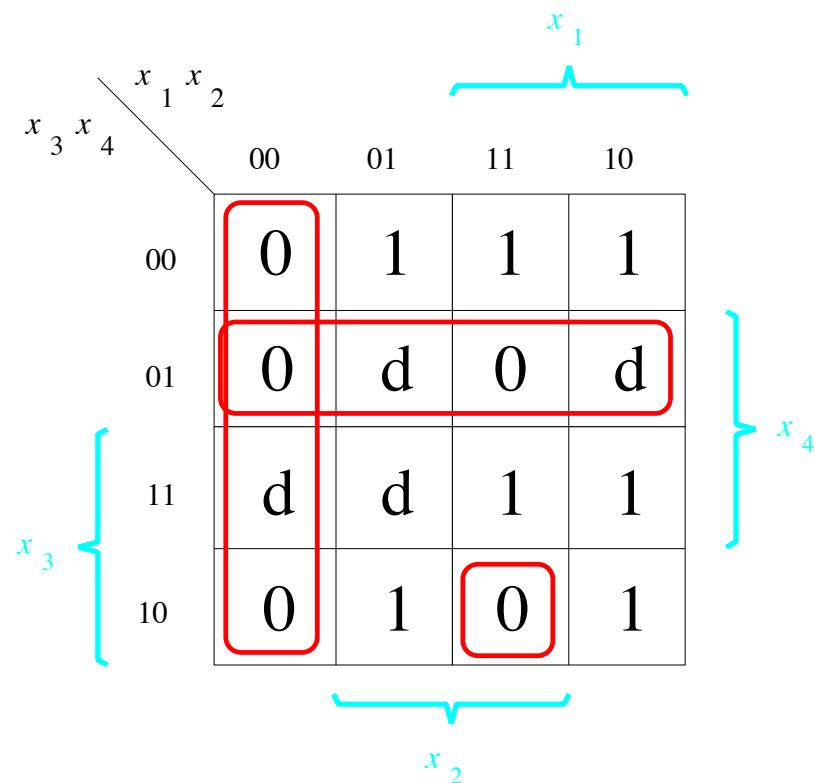
$$f(x_1, x_2, x_3, x_4) = \sum m(4, 6, 8, 10, 11, 12, 15) + D(3, 5, 7, 9)$$



The POS Expression

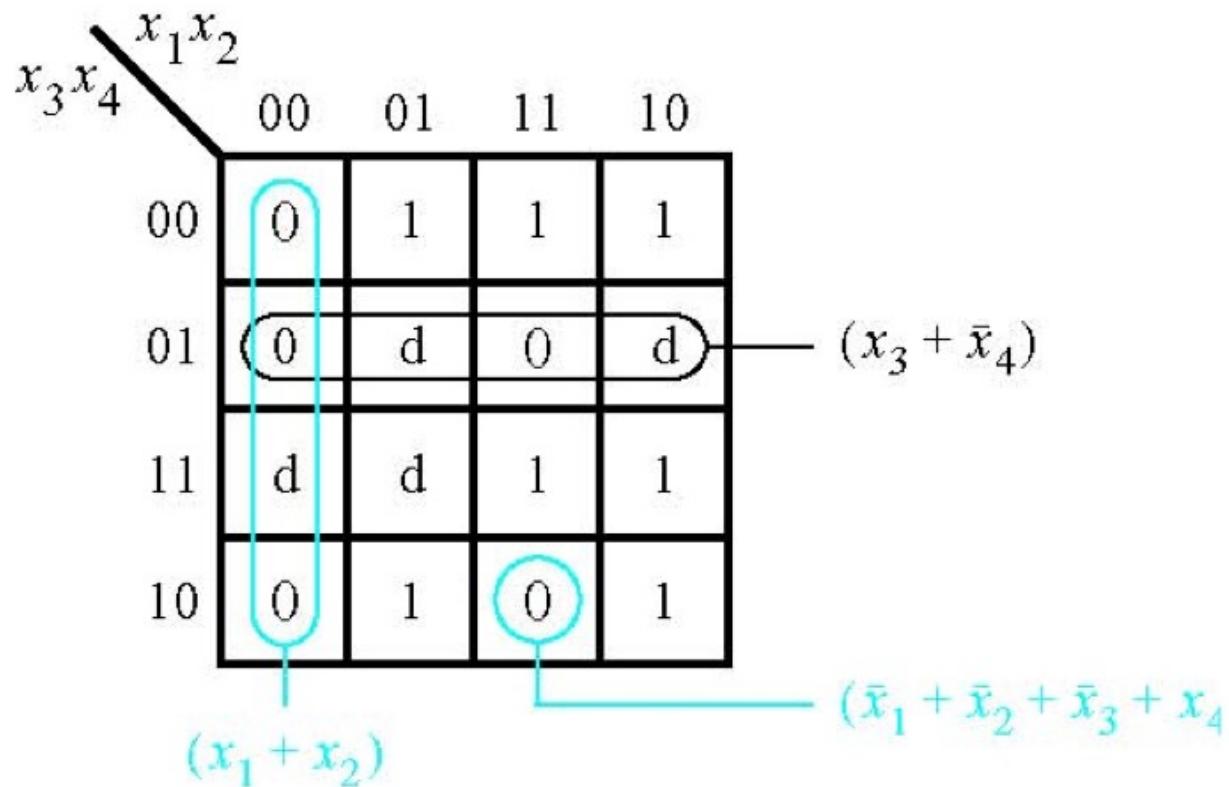

$$f = (x_1 + x_2) \bullet (x_3 + \bar{x}_4) \bullet (\bar{x}_1 + \bar{x}_2 + \bar{x}_3 + x_4)$$

[Figure 2.67b from the textbook]

Example 6

Use K-maps to find the minimum-cost SOP and POS expression for the function


$$f(x_1, \dots, x_4) = \bar{x}_1\bar{x}_3\bar{x}_4 + x_3x_4 + \bar{x}_1\bar{x}_2x_4 + x_1x_2\bar{x}_3x_4$$

assuming that there are also don't-cares defined as $D = \sum(9, 12, 14)$.

Let's map the expression to the K-Map

$$f(x_1, \dots, x_4) = \bar{x}_1\bar{x}_3\bar{x}_4 + x_3x_4 + \bar{x}_1\bar{x}_2x_4 + x_1x_2\bar{x}_3x_4$$


$$D = \sum(9, 12, 14).$$

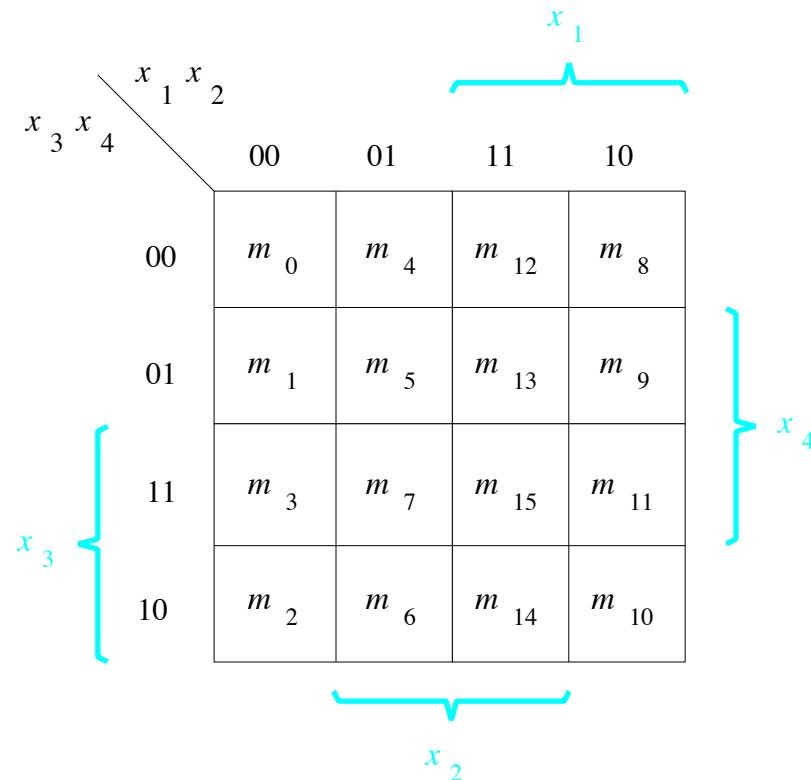

Let's map the expression to the K-Map


$$f(x_1, \dots, x_4) = \bar{x}_1\bar{x}_3\bar{x}_4 + x_3x_4 + \bar{x}_1\bar{x}_2x_4 + x_1x_2\bar{x}_3x_4$$

$$D = \sum(9, 12, 14).$$

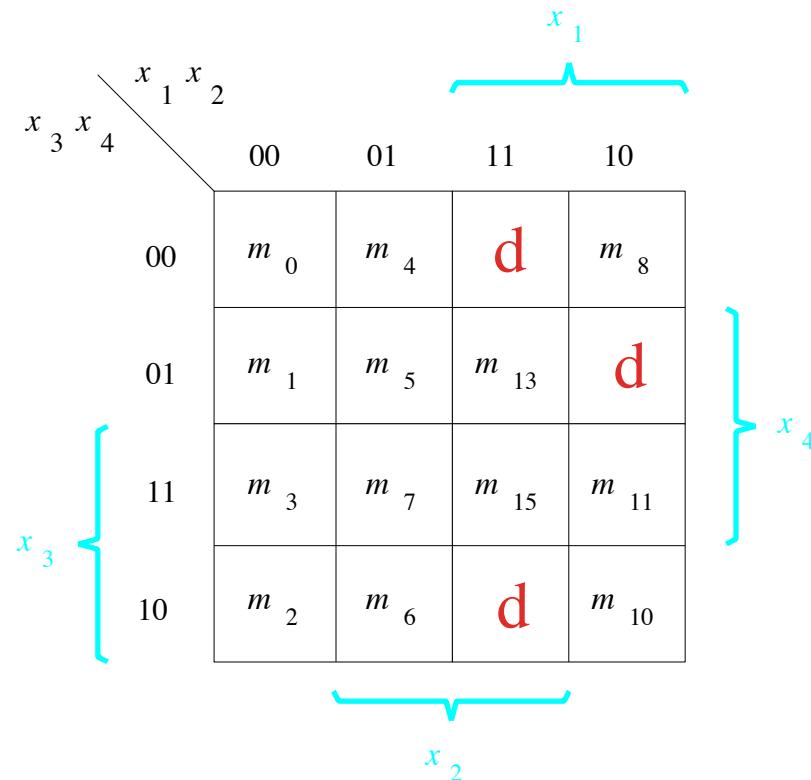


Let's map the expression to the K-Map
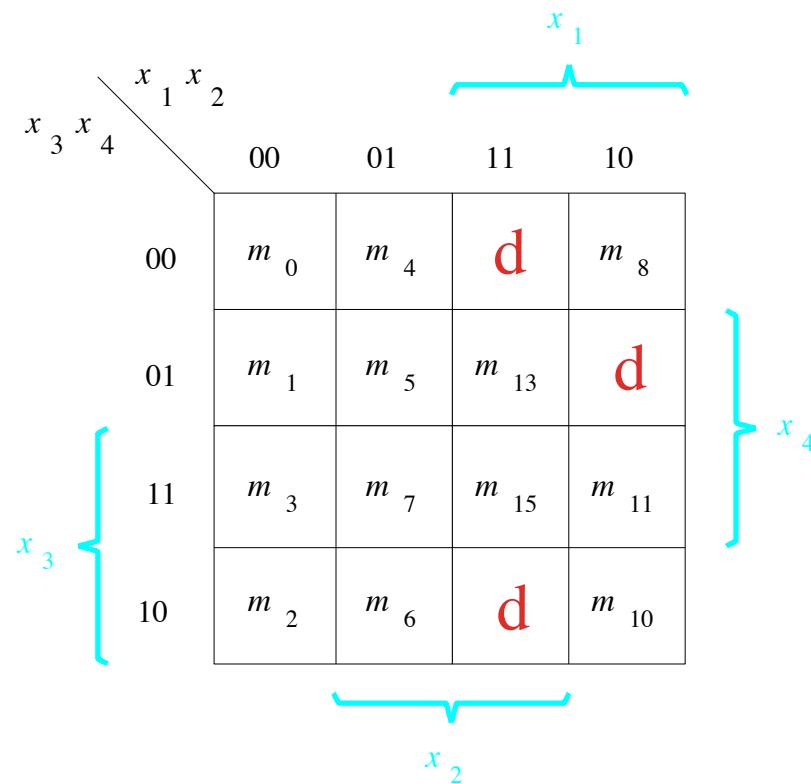
$$f(x_1, \dots, x_4) = \bar{x}_1\bar{x}_3\bar{x}_4 + x_3x_4 + \bar{x}_1\bar{x}_2x_4 + x_1x_2\bar{x}_3x_4$$




Let's map the expression to the K-Map
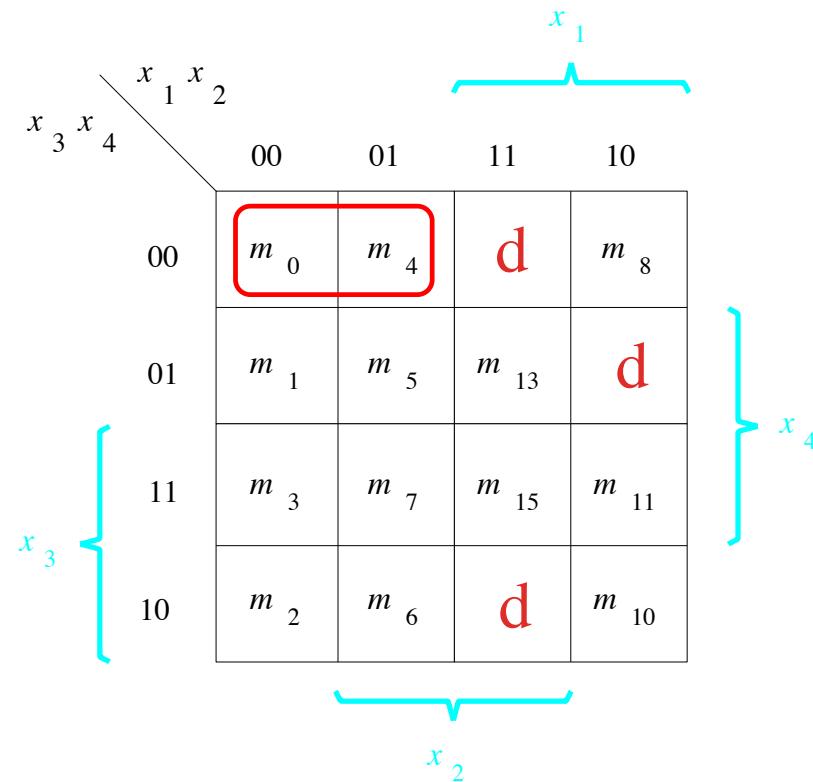
$$f(x_1, \dots, x_4) = \boxed{\bar{x}_1 \bar{x}_3 \bar{x}_4} + x_3 x_4 + \bar{x}_1 \bar{x}_2 x_4 + x_1 x_2 \bar{x}_3 x_4$$




Let's map the expression to the K-Map
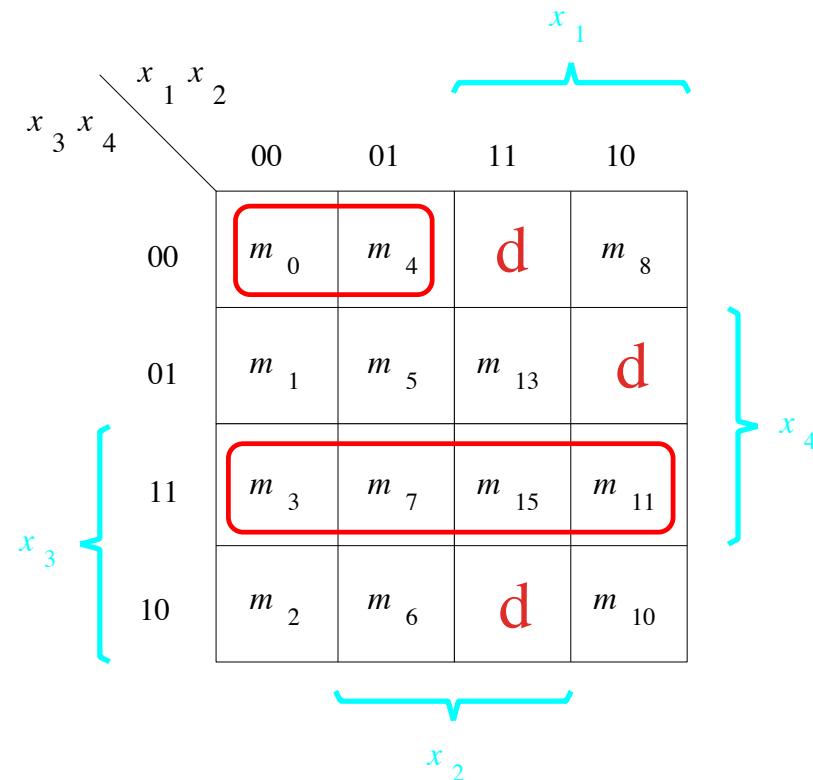
$$f(x_1, \dots, x_4) = \bar{x}_1 \bar{x}_3 \bar{x}_4 + \boxed{x_3 x_4} + \bar{x}_1 \bar{x}_2 x_4 + x_1 x_2 \bar{x}_3 x_4$$




Let's map the expression to the K-Map
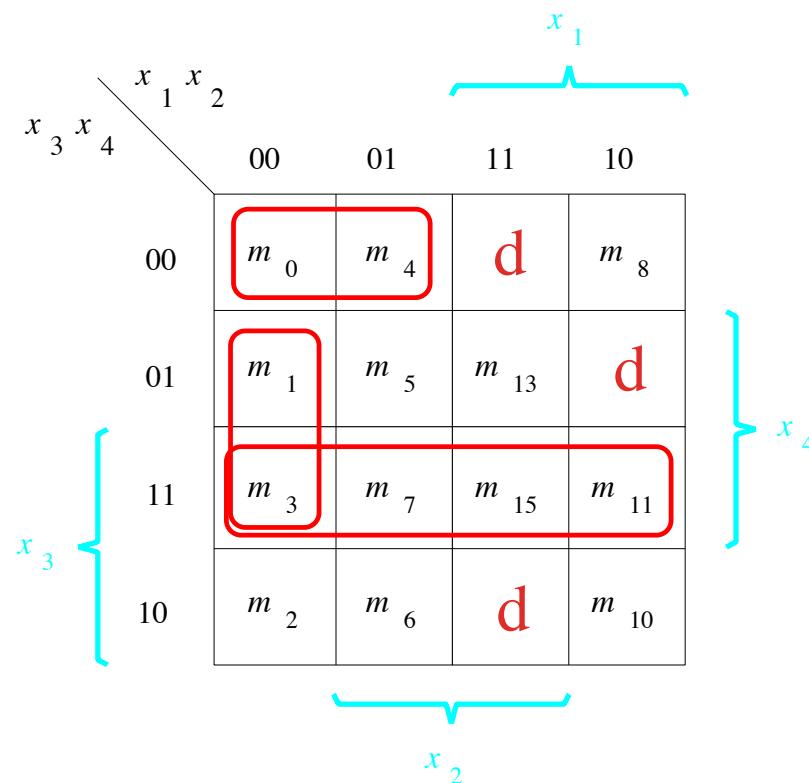
$$f(x_1, \dots, x_4) = \bar{x}_1 \bar{x}_3 \bar{x}_4 + x_3 x_4 + \boxed{\bar{x}_1 \bar{x}_2 x_4} + x_1 x_2 \bar{x}_3 x_4$$




Let's map the expression to the K-Map
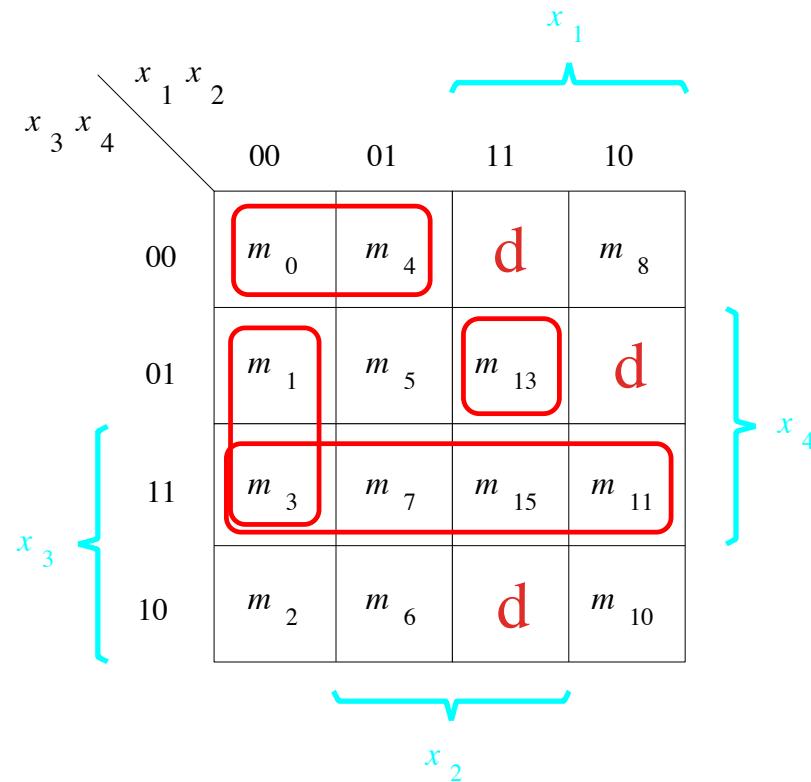
$$f(x_1, \dots, x_4) = \bar{x}_1\bar{x}_3\bar{x}_4 + x_3x_4 + \bar{x}_1\bar{x}_2x_4 + \boxed{x_1x_2\bar{x}_3x_4}$$




Let's map the expression to the K-Map
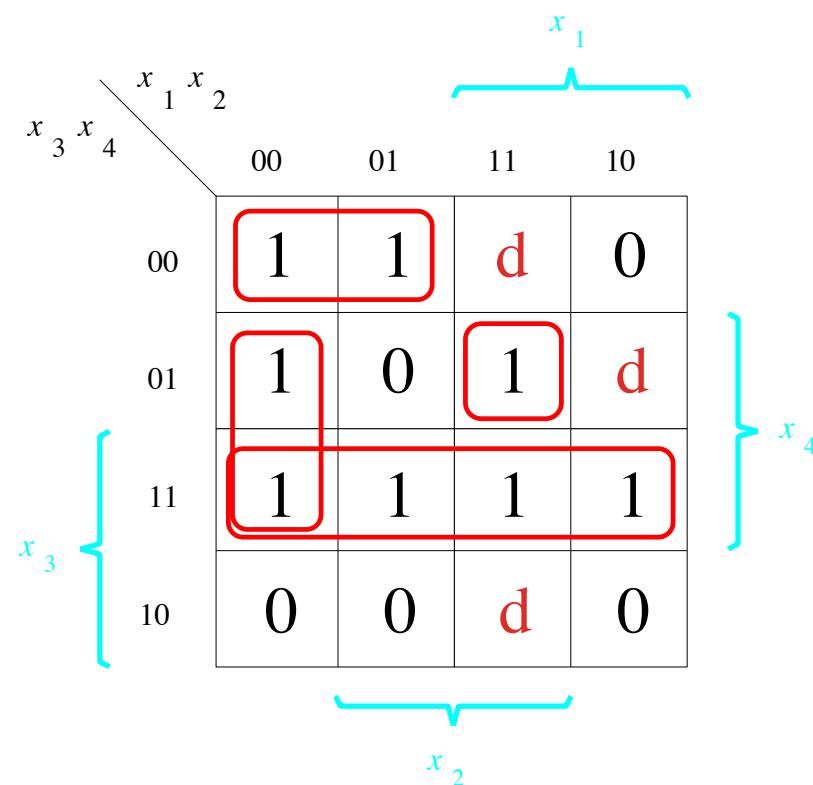
$$f(x_1, \dots, x_4) = \bar{x}_1\bar{x}_3\bar{x}_4 + x_3x_4 + \bar{x}_1\bar{x}_2x_4 + x_1x_2\bar{x}_3x_4$$




Let's map the expression to the K-Map
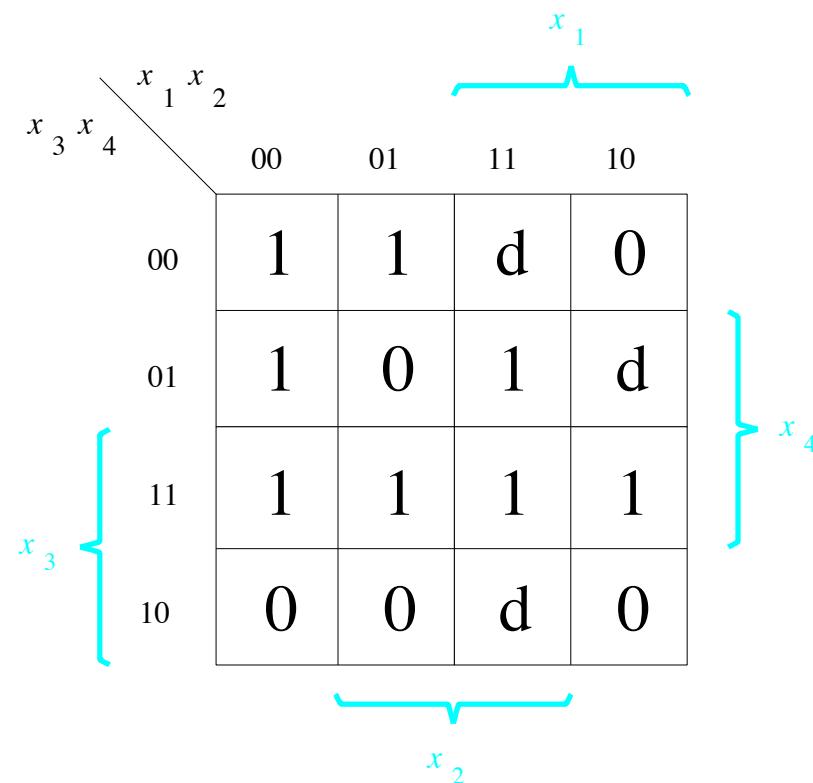
$$f(x_1, \dots, x_4) = \bar{x}_1\bar{x}_3\bar{x}_4 + x_3x_4 + \bar{x}_1\bar{x}_2x_4 + x_1x_2\bar{x}_3x_4$$




Let's map the expression to the K-Map
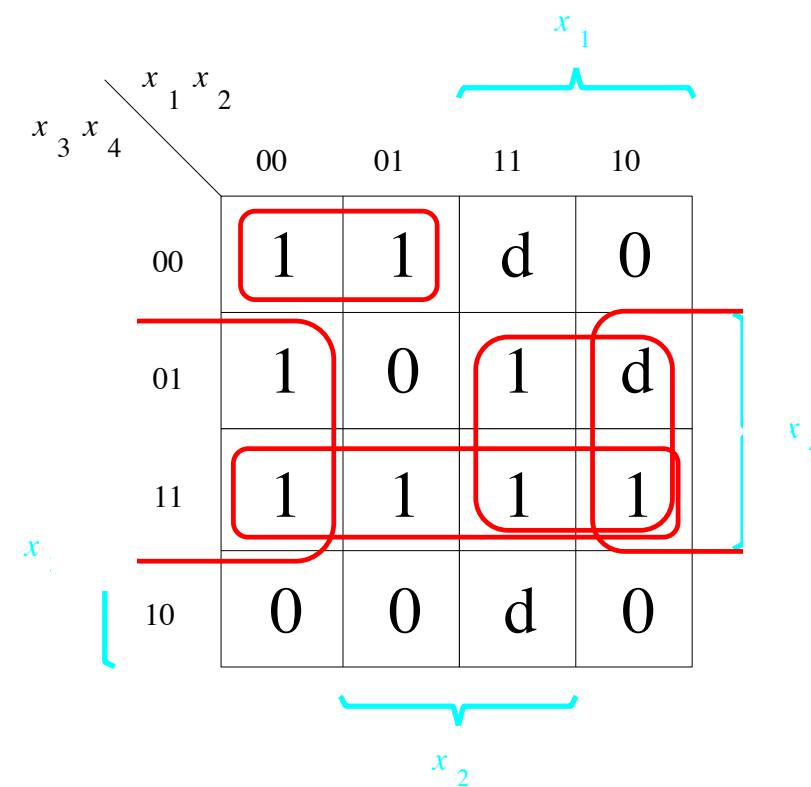
$$f(x_1, \dots, x_4) = \bar{x}_1\bar{x}_3\bar{x}_4 + x_3x_4 + \bar{x}_1\bar{x}_2x_4 + x_1x_2\bar{x}_3x_4$$



The SOP Expression

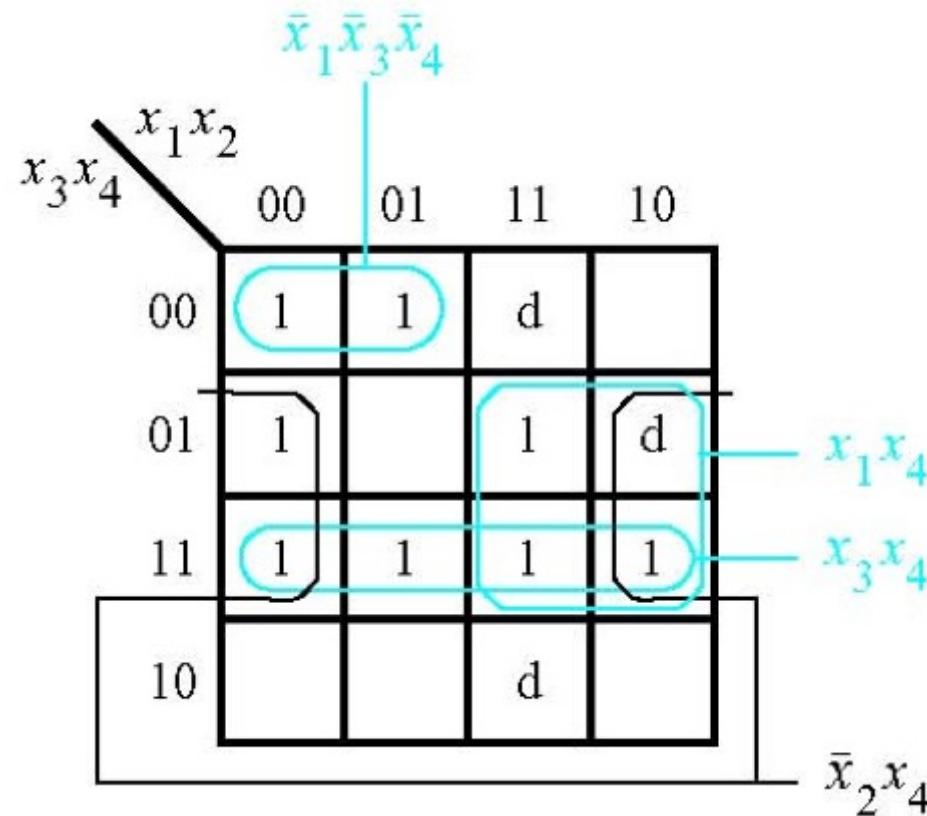
$$f(x_1, \dots, x_4) = \bar{x}_1\bar{x}_3\bar{x}_4 + x_3x_4 + \bar{x}_1\bar{x}_2x_4 + x_1x_2\bar{x}_3x_4$$




$$f = x_3x_4 + \bar{x}_1\bar{x}_3\bar{x}_4 + \bar{x}_2x_4 + x_1x_4$$

[Figure 2.68a from the textbook]


What about the POS Expression?

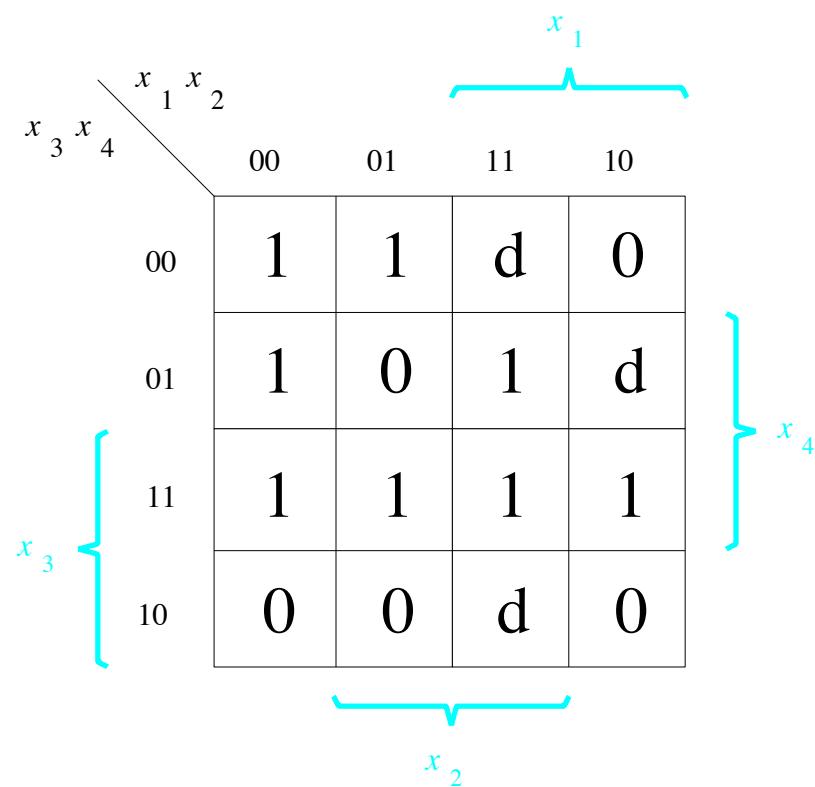

What about the POS Expression?

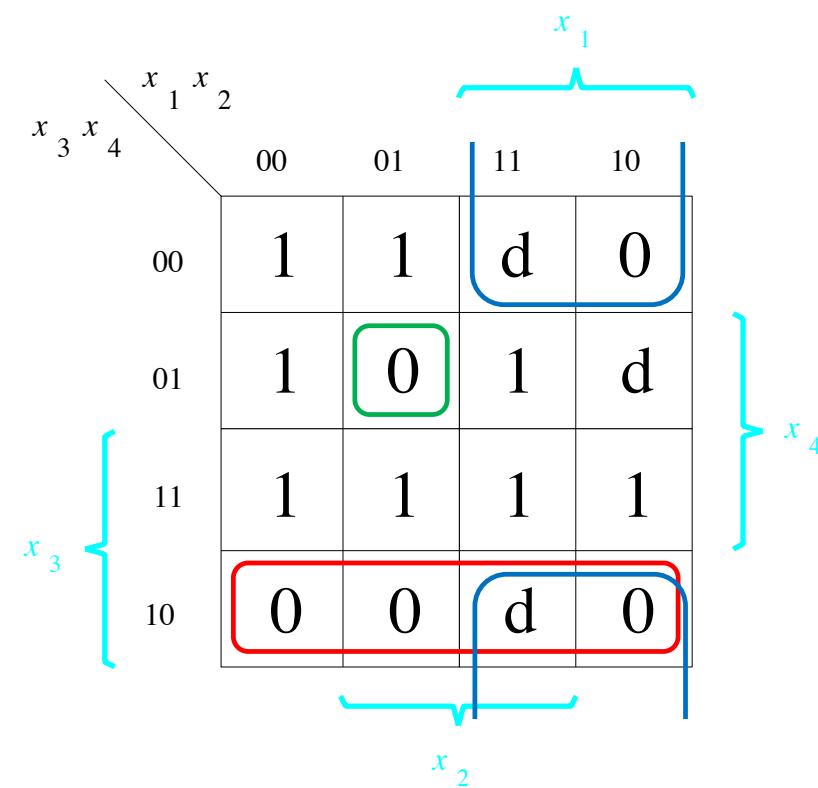

The POS Expression

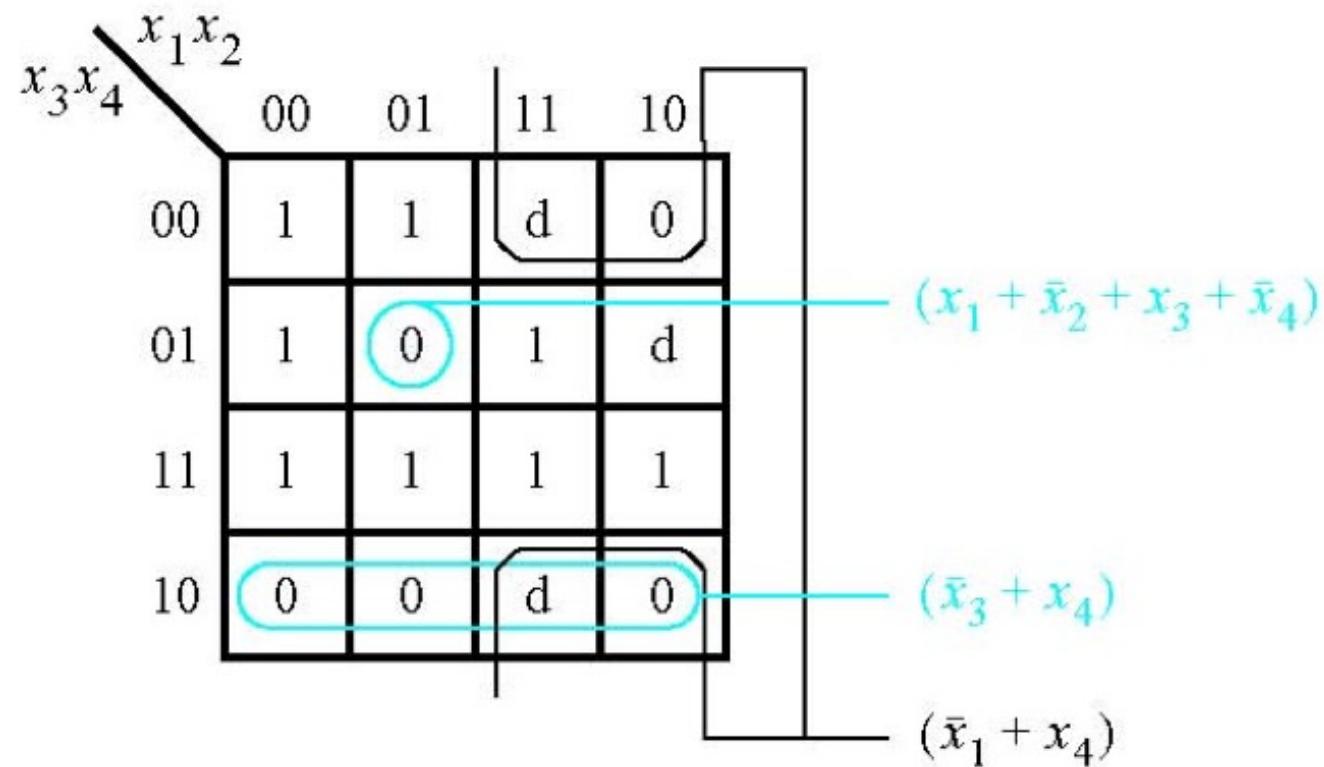

$$f = (\bar{x}_3 + x_4)(\bar{x}_1 + x_4)(x_1 + \bar{x}_2 + x_3 + \bar{x}_4)$$

[Figure 2.68b from the textbook]

Example 7

Derive the minimum-cost SOP expression for

$$f = s_3(\bar{s}_1 + \bar{s}_2) + s_1s_2$$

**First, expand the expression
using property 12a**

$$f = s_3(\bar{s}_1 + \bar{s}_2) + s_1s_2$$


$$f = \bar{s}_1s_3 + \bar{s}_2s_3 + s_1s_2$$

Construct the K-Map for this expression

$$f = \bar{s}_1 s_3 + \bar{s}_2 s_3 + s_1 s_2$$

s_1	s_2	s_3	
0	0	0	m_0
0	0	1	m_1
0	1	0	m_2
0	1	1	m_3
1	0	0	m_4
1	0	1	m_5
1	1	0	m_6
1	1	1	m_7

(a) Truth table

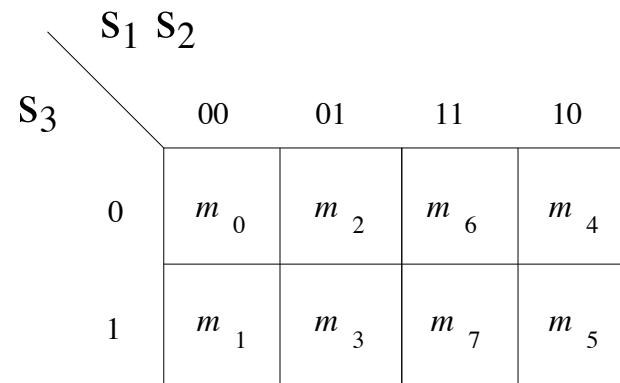


(b) Karnaugh map

Construct the K-Map for this expression

$$f = \boxed{\bar{s}_1 s_3} + \bar{s}_2 s_3 + s_1 s_2$$

s_1	s_2	s_3	
0	0	0	m_0
0	0	1	m_1
0	1	0	m_2
0	1	1	m_3
1	0	0	m_4
1	0	1	m_5
1	1	0	m_6
1	1	1	m_7

(a) Truth table

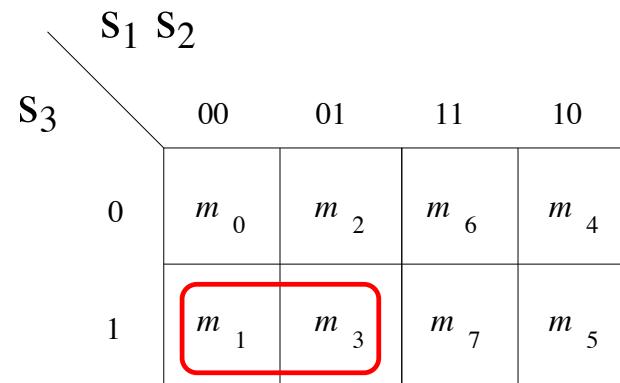


(b) Karnaugh map

Construct the K-Map for this expression

$$f = \bar{s}_1 s_3 + \boxed{\bar{s}_2 s_3} + s_1 s_2$$

s_1	s_2	s_3	
0	0	0	m_0
0	0	1	m_1
0	1	0	m_2
0	1	1	m_3
1	0	0	m_4
1	0	1	m_5
1	1	0	m_6
1	1	1	m_7

(a) Truth table

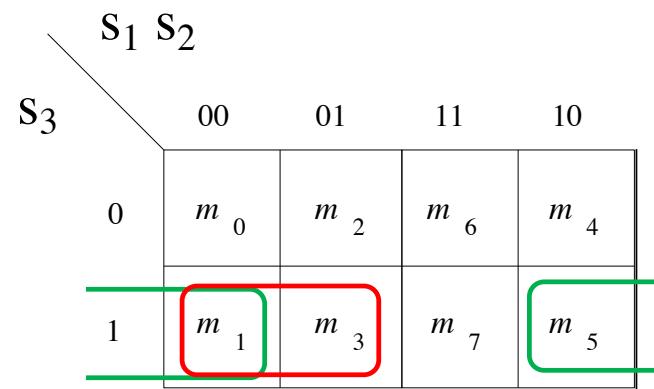


(b) Karnaugh map

Construct the K-Map for this expression

$$f = \bar{s}_1 s_3 + \bar{s}_2 s_3 + \boxed{s_1 s_2}$$

s_1	s_2	s_3	
0	0	0	m_0
0	0	1	m_1
0	1	0	m_2
0	1	1	m_3
1	0	0	m_4
1	0	1	m_5
1	1	0	m_6
1	1	1	m_7

(a) Truth table

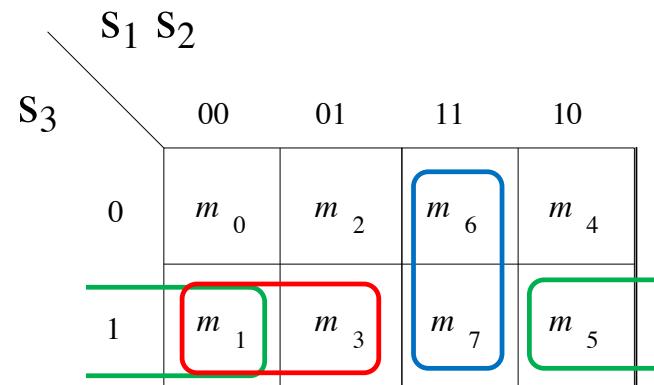


(b) Karnaugh map

Construct the K-Map for this expression

$$f = \bar{s}_1 s_3 + \bar{s}_2 s_3 + s_1 s_2$$

s_1	s_2	s_3	
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

(a) Truth table

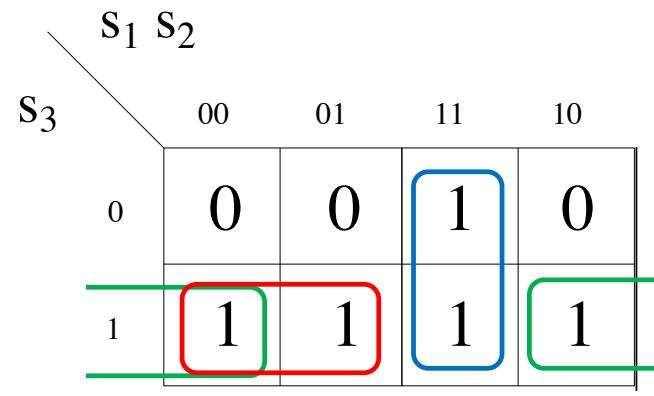


(b) Karnaugh map

Construct the K-Map for this expression

$$f = \bar{s}_1 s_3 + \bar{s}_2 s_3 + s_1 s_2$$

s_1	s_2	s_3	
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

(a) Truth table

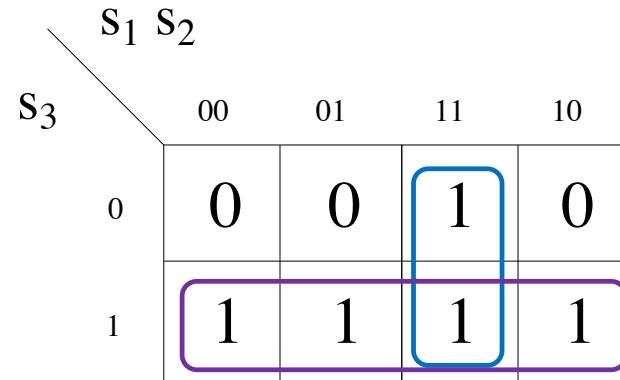


(b) Karnaugh map

Simplified Expression: $f = s_3 + s_1 s_2$

Construct the K-Map for this expression


$$f = \bar{s}_1 s_3 + \bar{s}_2 s_3 + s_1 s_2$$

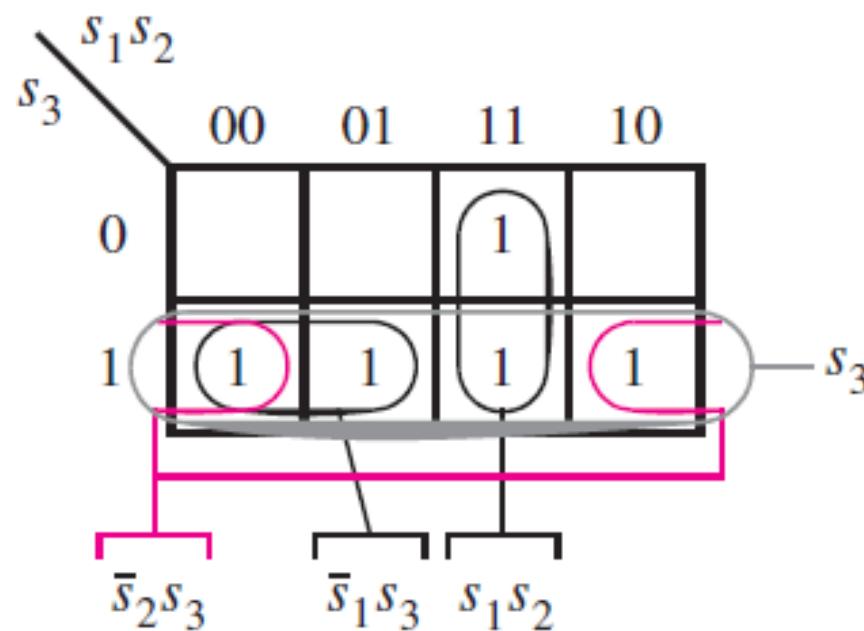

[Figure 2.69 from the textbook]

Construct the K-Map for this expression
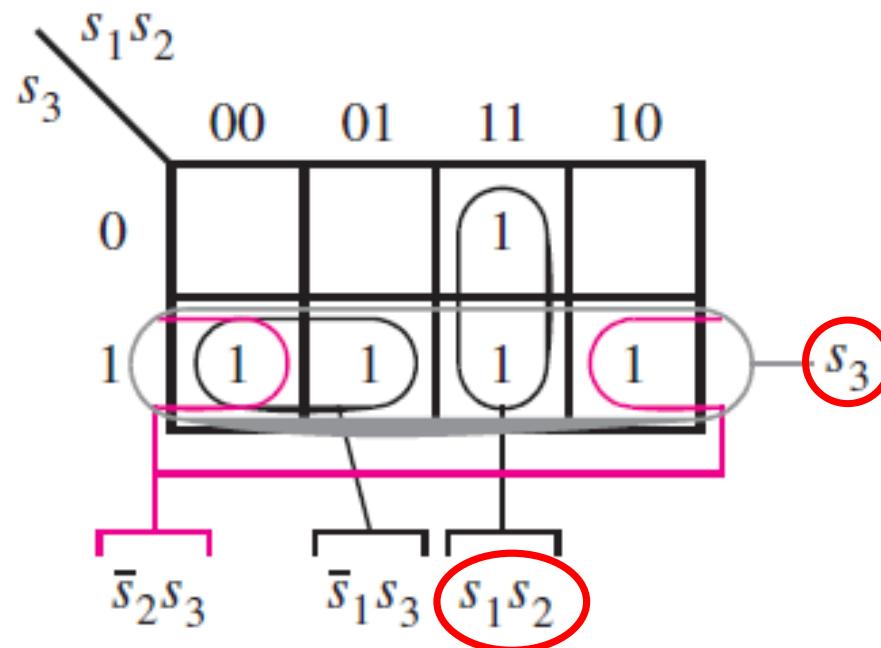
$$f = \bar{s}_1 s_3 + \bar{s}_2 s_3 + s_1 s_2$$




Simplified Expression: $f = s_3 + s_1 s_2$

[Figure 2.69 from the textbook]

Example 8


Write the Verilog code for the following circuit ...

Logic Circuit

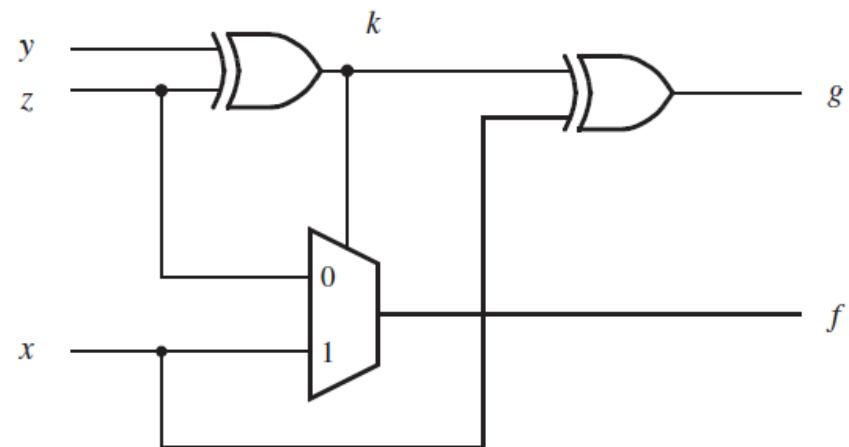


[Figure 2.70 from the textbook]

Circuit for 2-1 Multiplexer

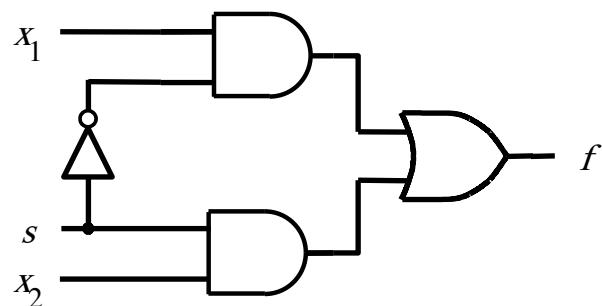

(b) Circuit

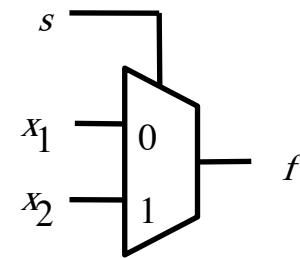


(c) Graphical symbol

$$f(s, x_1, x_2) = \bar{s}x_1 + s x_2$$

[Figure 2.33b-c from the textbook]

Logic Circuit vs Verilog Code

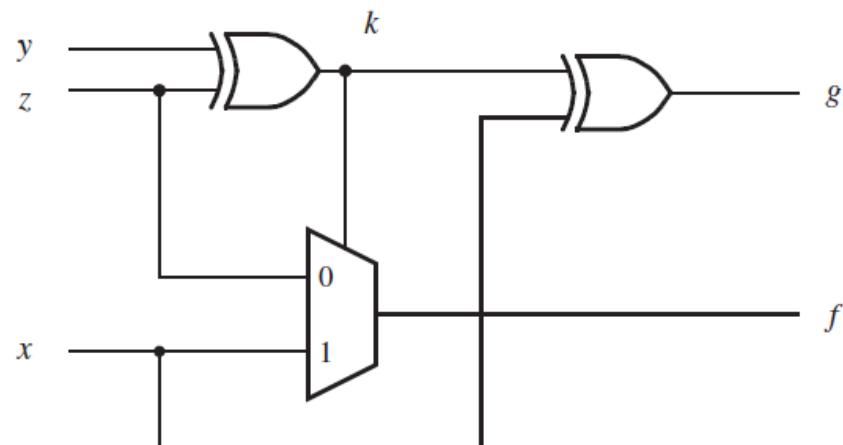

[Figure 2.70 from the textbook]

```
module f_g (x, y, z, f, g);
  input x, y, z;
  output f, g;
  wire k;

  assign k = y ^ z;
  assign g = k ^ x;
  assign f = (~k & z) | (k & x);


endmodule
```

[Figure 2.71 from the textbook]

Example 9


Write the Verilog code for the following circuit ...

The Logic Circuit for this Example

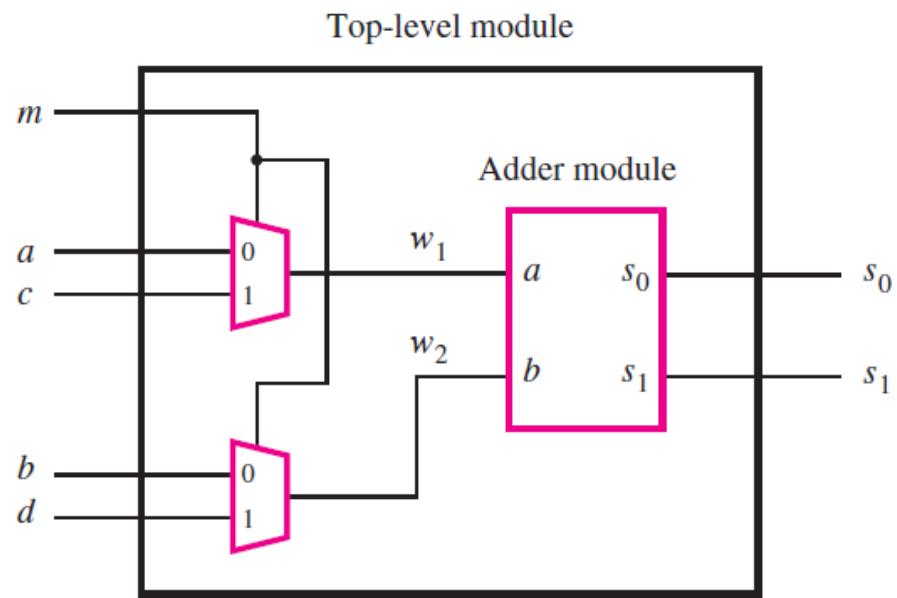


[Figure 2.72 from the textbook]

Circuit for 2-1 Multiplexer

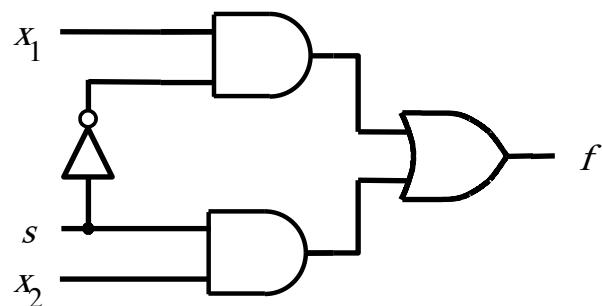

(b) Circuit

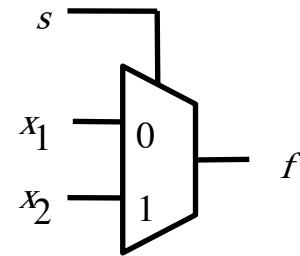


(c) Graphical symbol

$$f(s, x_1, x_2) = \bar{s}x_1 + s x_2$$


[Figure 2.33b-c from the textbook]

Addition of Binary Numbers

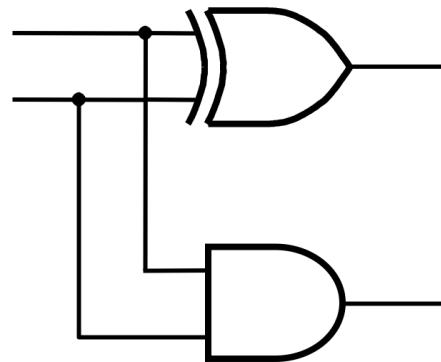

a	b	s ₁	s ₀
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

Logic Circuit vs Verilog Code

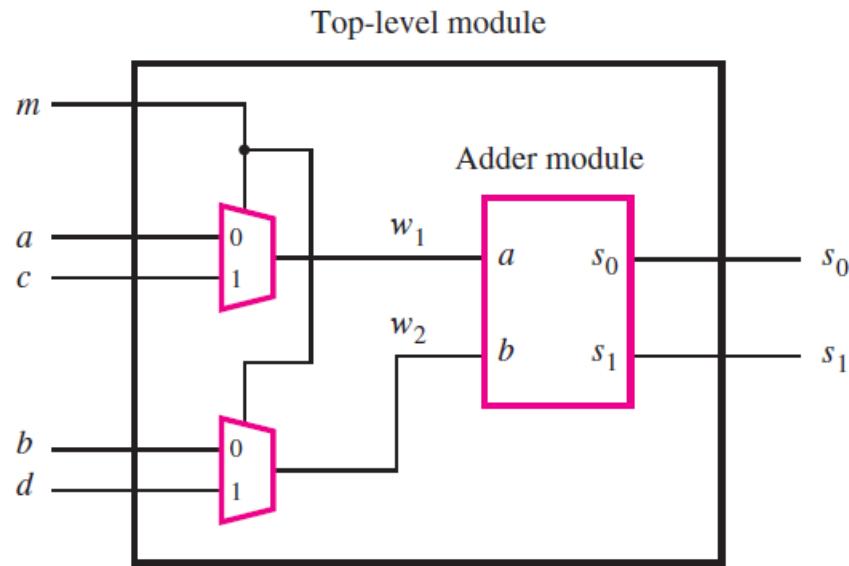

```
module shared (a, b, c, d, m, s1, s0);
    input a, b, c, d, m;
    output s1, s0;
    wire w1, w2;
    mux2to1 U1 (a, c, m, w1);
    mux2to1 U2 (b, d, m, w2);
    adder U3 (w1, w2, s1, s0);
endmodule
```


```
module mux2to1 (x1, x2, s, f);
    input x1, x2, s;
    output f;
    assign f = (~s & x1) | (s & x2);
endmodule
```

```
module adder (a, b, s1, s0);
    input a, b;
    output s1, s0;
    assign s1 = a & b;
    assign s0 = a ^ b;
endmodule
```

[Figure 2.73 from the textbook]


Some material form Appendix B

Programmable Logic Array (PLA)

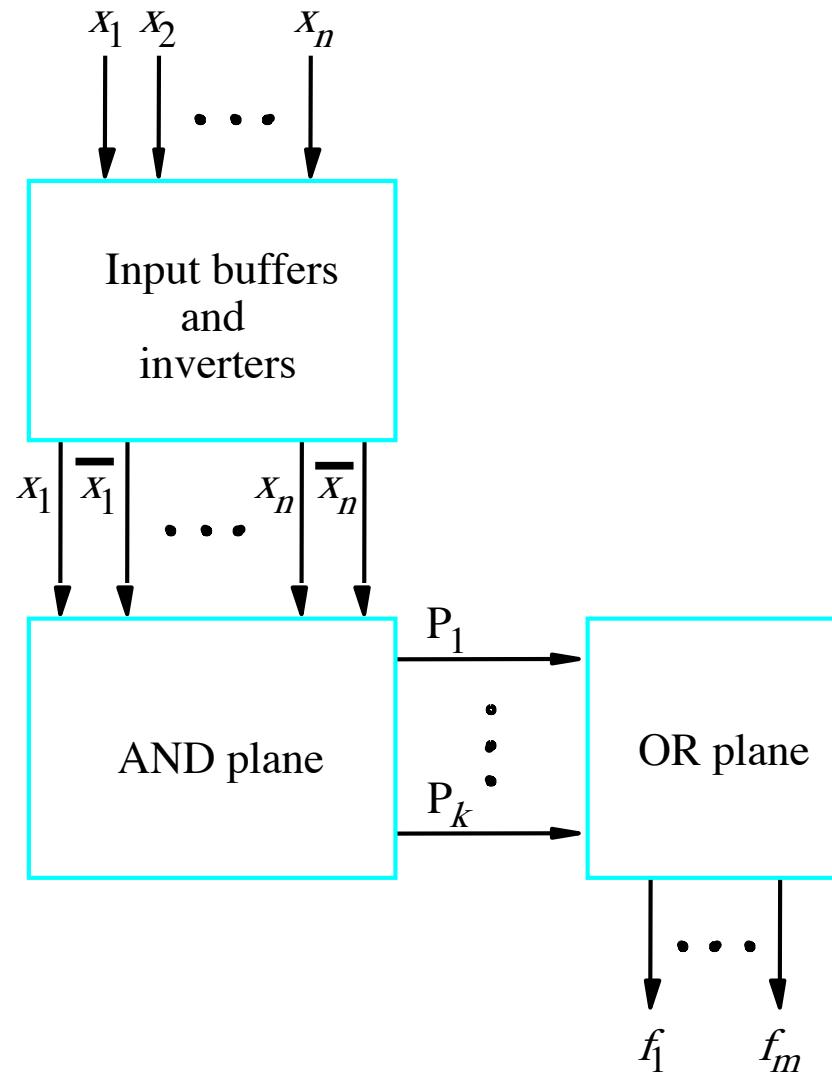


[Figure B.25 from textbook]

Gate-Level Diagram of a PLA

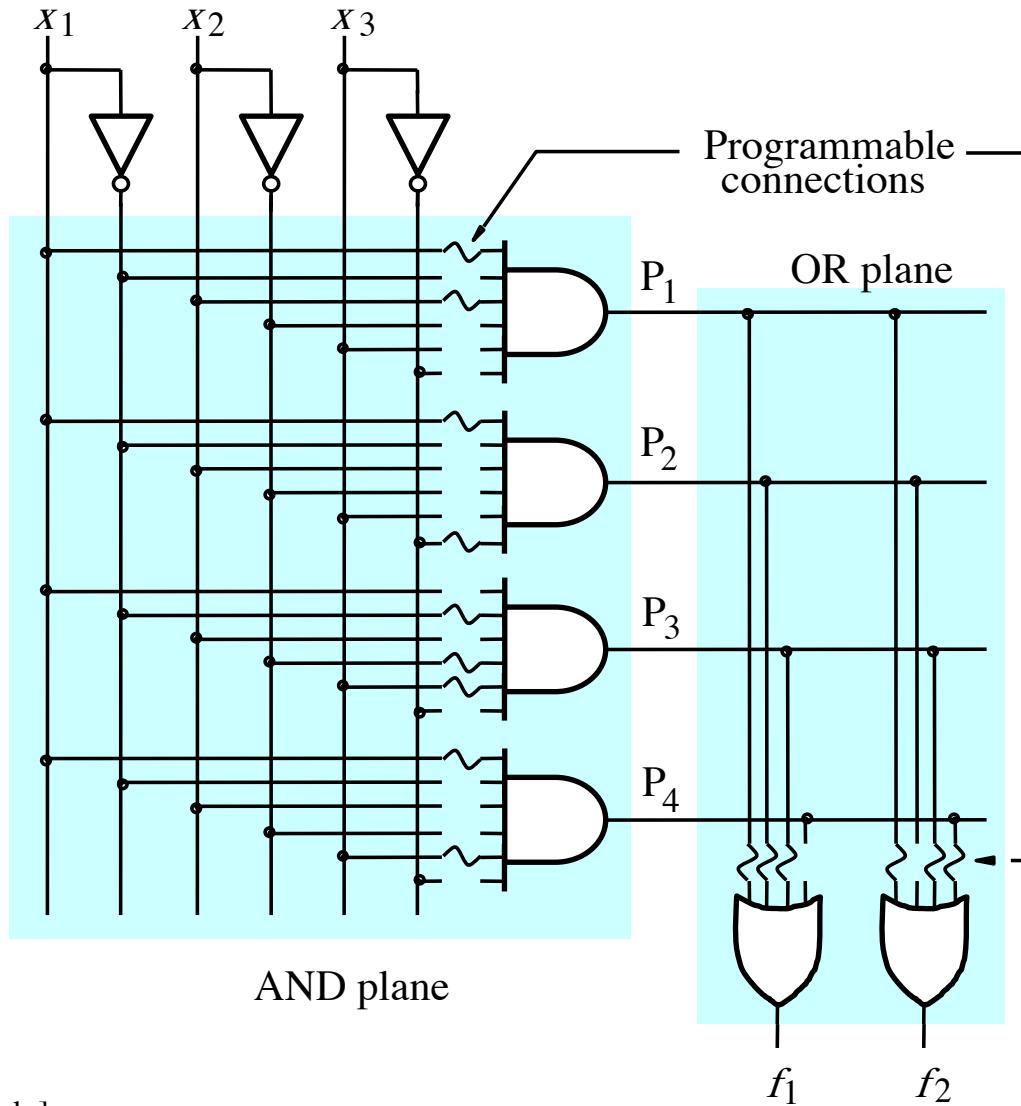


[Figure B.26 from textbook]

Customary Schematic for PLA

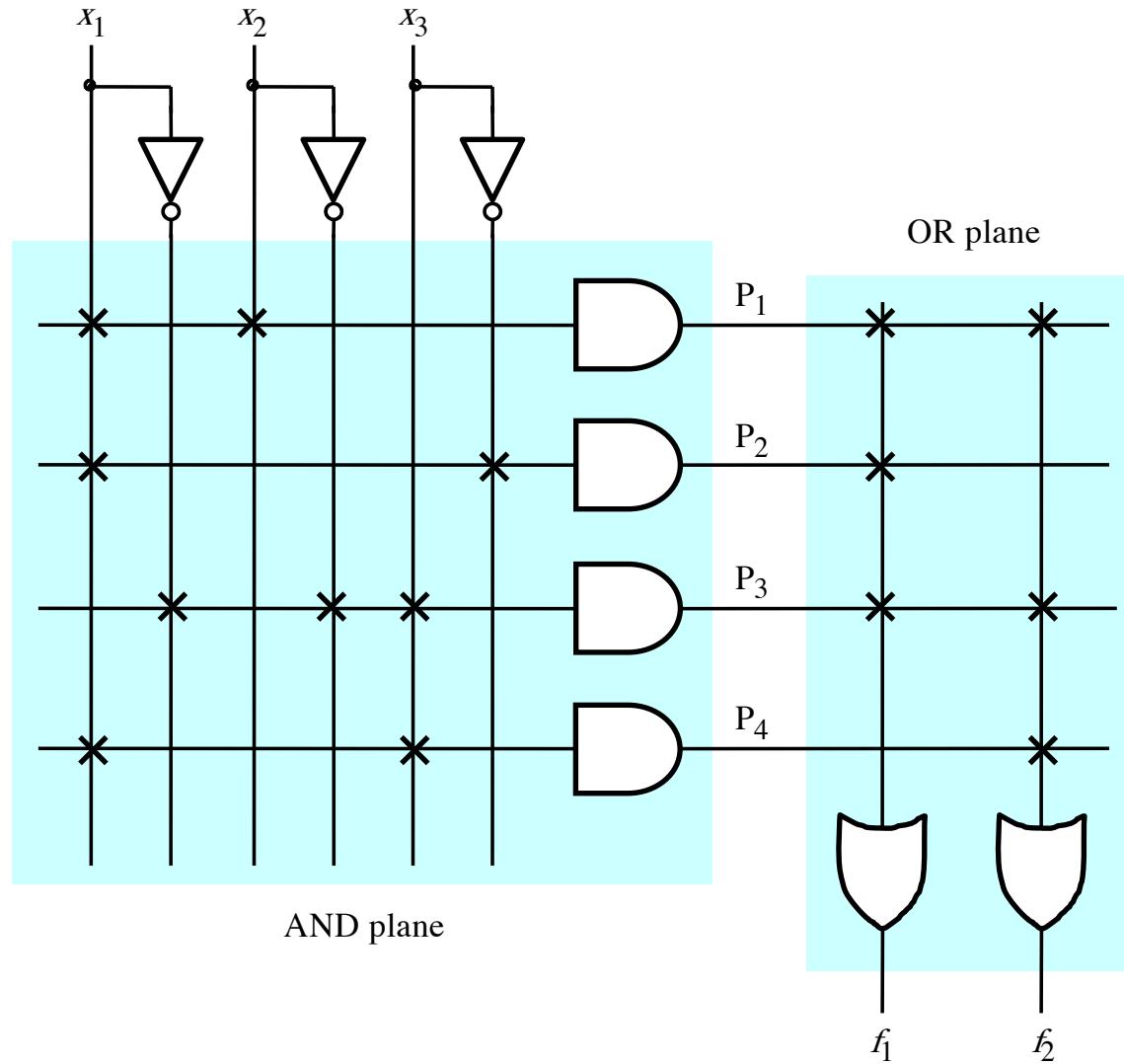


[Figure B.27 from textbook]

Programmable Array Logic (PAL)

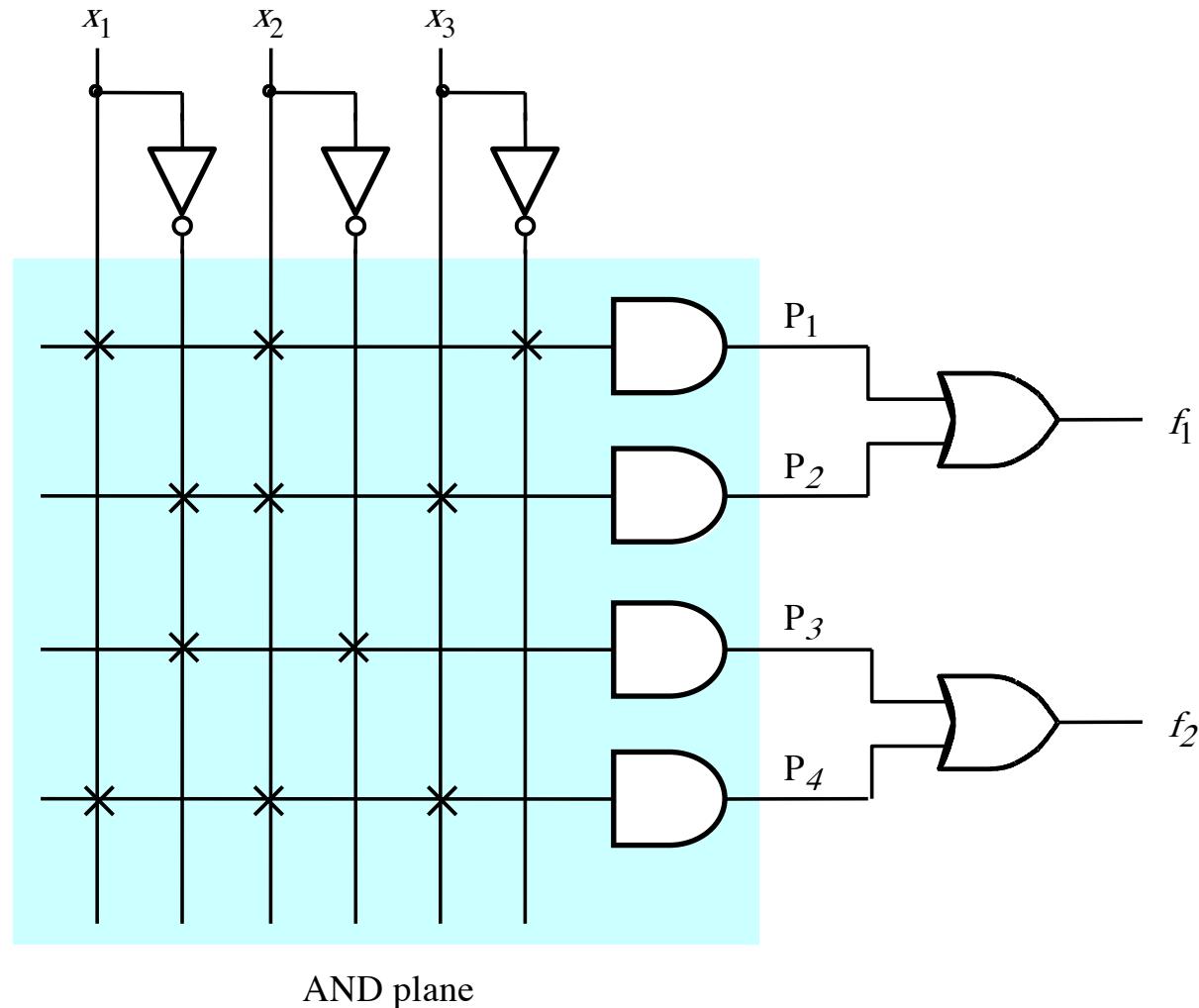

[Figure B.28 from textbook]

Programmable Array Logic (PAL)

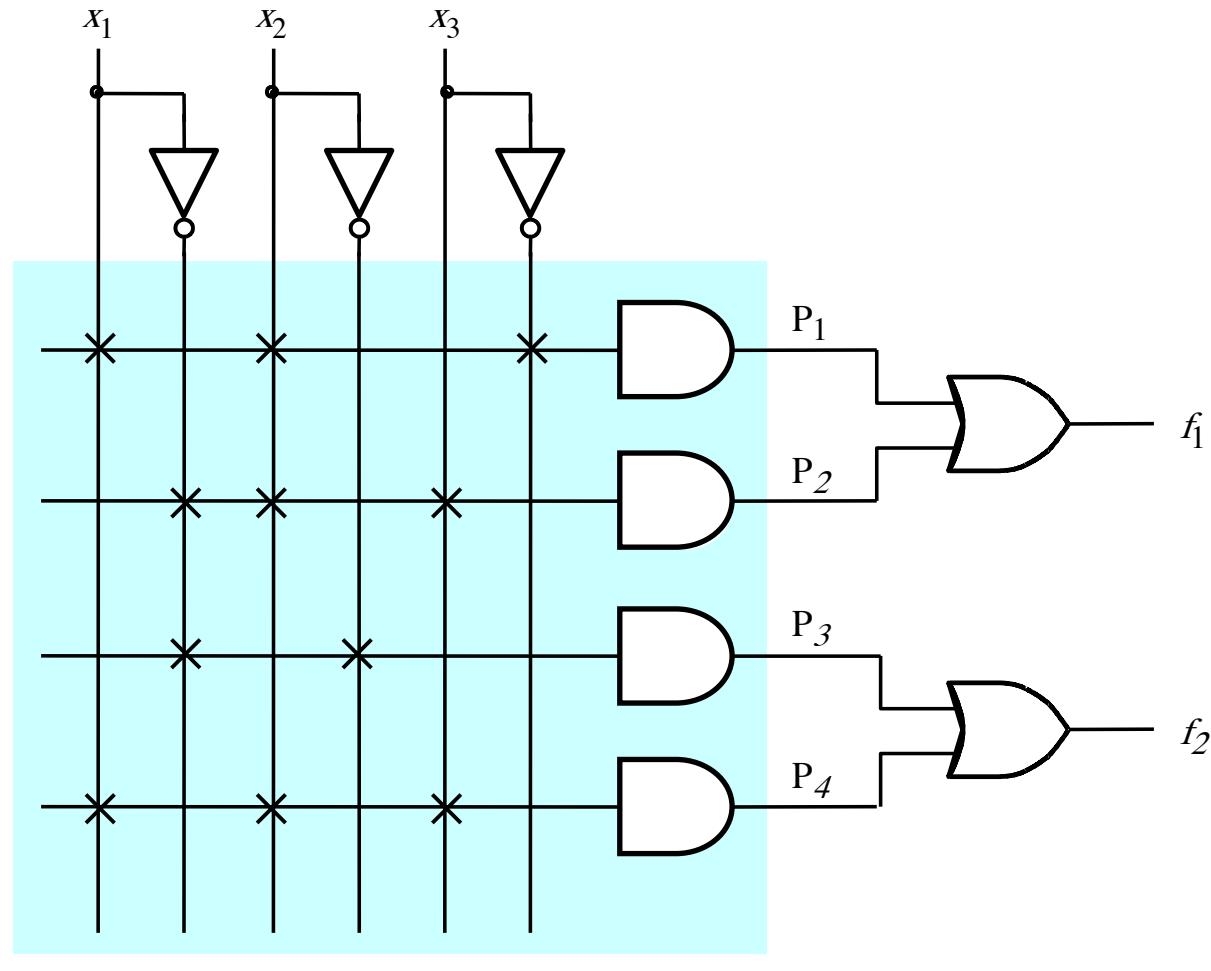

AND plane

Only the AND plane is programmable.
The OR plane is fixed.

[Figure B.28 from textbook]

Questions?

THE END