

CprE 2810: Digital Logic

Instructor: Alexander Stoytchev

<http://www.ece.iastate.edu/~alexs/classes/>

Addition of Unsigned Numbers

*CprE 281: Digital Logic
Iowa State University, Ames, IA
Copyright © Alexander Stoytchev*

Administrative Stuff

- **We are now starting with Chapter 3**

Administrative Stuff

- **HW5 is due today @ 10 pm**

Administrative Stuff

- **No homework due next week**
- **HW6 will be due on Monday, Oct 14**

Quick Review


Number Systems

$$N = d_n B^n + d_{n-1} B^{n-1} + \cdots + d_1 B^1 + d_0 B^0$$


Number Systems

$$N = d_n B^n + d_{n-1} B^{n-1} + \dots + d_1 B^1 + d_0 B^0$$

n-th digit
(most significant)



0-th digit
(least significant)



Number Systems

The diagram shows the expansion of a number N in base B . The formula is $N = d_n B^n + d_{n-1} B^{n-1} + \dots + d_1 B^1 + d_0 B^0$. Red arrows point from the labels 'base' and 'power' to the B and B^n terms respectively. Another red arrow points from 'n-th digit (most significant)' to the d_n term. A final red arrow points from '0-th digit (least significant)' to the d_0 term.

base

power

$$N = d_n B^n + d_{n-1} B^{n-1} + \dots + d_1 B^1 + d_0 B^0$$

n-th digit
(most significant)

0-th digit
(least significant)

The Decimal System

$$524_{10} = 5 \times 10^2 + 2 \times 10^1 + 4 \times 10^0$$

The Decimal System

$$\begin{aligned}524_{10} &= 5 \times 10^2 + 2 \times 10^1 + 4 \times 10^0 \\ &= 5 \times 100 + 2 \times 10 + 4 \times 1 \\ &= 500 + 20 + 4 \\ &= 524_{10}\end{aligned}$$


Another Way to Look at This

| | | |
|---|---|---|
| 5 | 2 | 4 |
|---|---|---|

Another Way to Look at This

| | | | |
|--|--------|--------|--------|
| | 10^2 | 10^1 | 10^0 |
| | 5 | 2 | 4 |

Another Way to Look at This

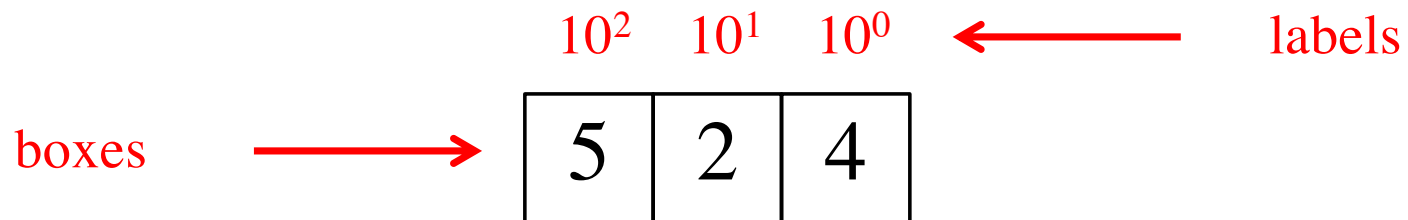

Each box can contain only one digit and has only one label. From right to left, the labels are increasing powers of the base, starting from 0.

Base 7

$$524_7 = 5 \times 7^2 + 2 \times 7^1 + 4 \times 7^0$$

Base 7

base

power

$$524_7 = 5 \times 7^2 + 2 \times 7^1 + 4 \times 7^0$$

most significant digit

least significant digit

Base 7

$$\begin{aligned}524_7 &= 5 \times 7^2 + 2 \times 7^1 + 4 \times 7^0 \\ &= 5 \times 49 + 2 \times 7 + 4 \times 1 \\ &= 245 + 14 + 4 \\ &= 263_{10}\end{aligned}$$

Another Way to Look at This

$$\begin{array}{ccc} 7^2 & 7^1 & 7^0 \\ \boxed{5} & \boxed{2} & \boxed{4} \end{array} = \begin{array}{ccc} 10^2 & 10^1 & 10^0 \\ \boxed{2} & \boxed{6} & \boxed{3} \end{array}$$

Binary Numbers (Base 2)

$$1001_2 = 1 \times 2^3 + 0 \times 2^2 + 0 \times 2^1 + 1 \times 2^0$$

Binary Numbers (Base 2)

base power

$$1001_2 = 1 \times 2^3 + 0 \times 2^2 + 0 \times 2^1 + 1 \times 2^0$$

most significant bit least significant bit

Binary Numbers (Base 2)

$$\begin{aligned} 1001_2 &= 1 \times 2^3 + 0 \times 2^2 + 0 \times 2^1 + 1 \times 2^0 = \\ &= 1 \times 8 + 0 \times 4 + 0 \times 2 + 1 \times 1 = \\ &= 8 + 0 + 0 + 1 = \\ &= 9_{10} \end{aligned}$$

Another Example

$$\begin{aligned} 11101_2 &= 1 \times 2^4 + 1 \times 2^3 + 1 \times 2^2 + 0 \times 2^1 + 1 \times 2^0 = \\ &= 1 \times 16 + 1 \times 8 + 1 \times 4 + 0 \times 2 + 1 \times 1 = \\ &= 16 + 8 + 4 + 0 + 1 = 29_{10} \end{aligned}$$

Powers of 2

$$2^{10} = 1024$$

$$2^9 = 512$$

$$2^8 = 256$$

$$2^7 = 128$$

$$2^6 = 64$$

$$2^5 = 32$$

$$2^4 = 16$$

$$2^3 = 8$$

$$2^2 = 4$$

$$2^1 = 2$$

$$2^0 = 1$$


What is the value of this binary number?

- **0 0 1 0 1 1 0 0**
- **0 0 1 0 1 1 0 0**
- **$0*2^7 + 0*2^6 + 1*2^5 + 0*2^4 + 1*2^3 + 1*2^2 + 0*2^1 + 0*2^0$**
- **$0*128 + 0*64 + 1*32 + 0*16 + 1*8 + 1*4 + 0*2 + 0*1$**
- **$0*128 + 0*64 + 1*32 + 0*16 + 1*8 + 1*4 + 0*2 + 0*1$**
- **$32 + 8 + 4 = 44$ (in decimal)**

Another Way to Look at This

| | | | | | | | |
|-------|-------|-------|-------|-------|-------|-------|-------|
| 2^7 | 2^6 | 2^5 | 2^4 | 2^3 | 2^2 | 2^1 | 2^0 |
| 0 | 0 | 1 | 0 | 1 | 1 | 0 | 0 |

Another Way to Look at This

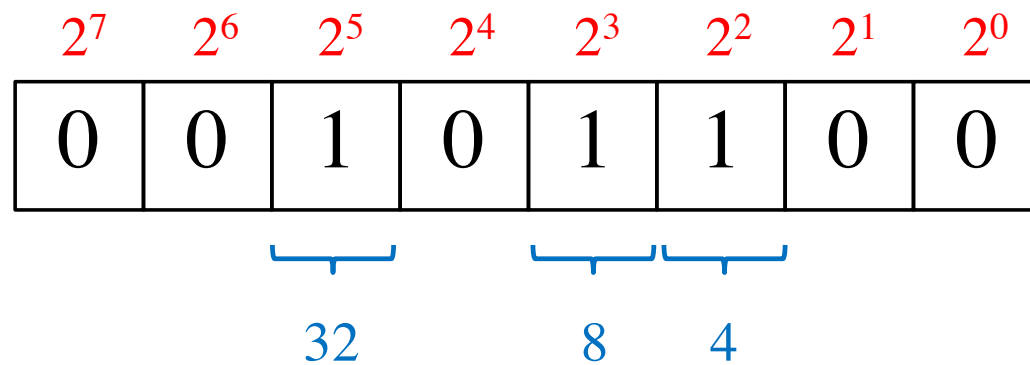

Signed v.s. Unsigned Numbers

Signed v.s. Unsigned Numbers



positive
and
negative
integers



only
positive
integers

Signed v.s. Unsigned Numbers

positive
and
negative
integers

and zero

only
positive
integers

and zero

Two Different Types of Binary Numbers

Unsigned numbers

- All bits jointly represent a positive integer.
- Negative numbers cannot be represented this way.

Signed numbers

- The left-most bit represents the sign of the number.
- If that bit is 0, then the number is positive.
- If that bit is 1, then the number is negative.
- The magnitude of the largest number that can be represented in this way is twice smaller than the largest number in the unsigned representation.

Two Different Types of Binary Numbers

Unsigned numbers

- All bits jointly represent a positive integer.
- Negative numbers cannot be represented this way.

**There are 3 different ways
to represent signed numbers.**

Signed numbers

They will be introduced next time.

- The left-most bit represents the sign of the number.
- If that bit is 0, then the number is positive.
- If that bit is 1, then the number is negative.
- The magnitude of the largest number that can be represented in this way is twice smaller than the largest number in the unsigned representation.

Unsigned Representation

| | | | | | | | |
|-------|-------|-------|-------|-------|-------|-------|-------|
| 2^7 | 2^6 | 2^5 | 2^4 | 2^3 | 2^2 | 2^1 | 2^0 |
| 0 | 0 | 1 | 0 | 1 | 1 | 0 | 0 |

This represents + 44.

Unsigned Representation

| | | | | | | | |
|-------|-------|-------|-------|-------|-------|-------|-------|
| 2^7 | 2^6 | 2^5 | 2^4 | 2^3 | 2^2 | 2^1 | 2^0 |
| 1 | 0 | 1 | 0 | 1 | 1 | 0 | 0 |

This represents + 172.

Signed Representation (using the left-most bit as the sign)

| sign | 2^6 | 2^5 | 2^4 | 2^3 | 2^2 | 2^1 | 2^0 |
|------|-------|-------|-------|-------|-------|-------|-------|
| 0 | 0 | 1 | 0 | 1 | 1 | 0 | 0 |

This represents + 44.

Signed Representation (using the left-most bit as the sign)

| | | | | | | | |
|------|-------|-------|-------|-------|-------|-------|-------|
| sign | 2^6 | 2^5 | 2^4 | 2^3 | 2^2 | 2^1 | 2^0 |
| 1 | 0 | 1 | 0 | 1 | 1 | 0 | 0 |

This represents -44 .

**Today's Lecture is About
Addition of **Unsigned** Numbers**

Important Clarification:

There are two types of addition

- Addition of Boolean variables, e.g.,

$$x + y \quad \text{where } x, y \in \{0, 1\}$$

- Addition of n-bit Binary numbers, e.g.,

$$x_4x_3x_2x_1x_0 + y_4y_3y_2y_1y_0 \quad \text{where each } x_k, y_k \in \{0, 1\}$$

Important Clarification: There are two types of addition

- **Addition of Boolean variables, e.g.,**


$$1 + 0 = 1$$

- **Addition of n-bit Binary numbers, e.g.,**


$$00101 + 00110 = 01011$$

Important Clarification: There are two types of addition

- Addition of Boolean variables, e.g.,

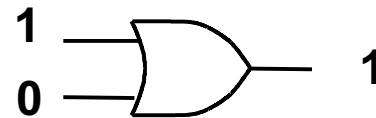


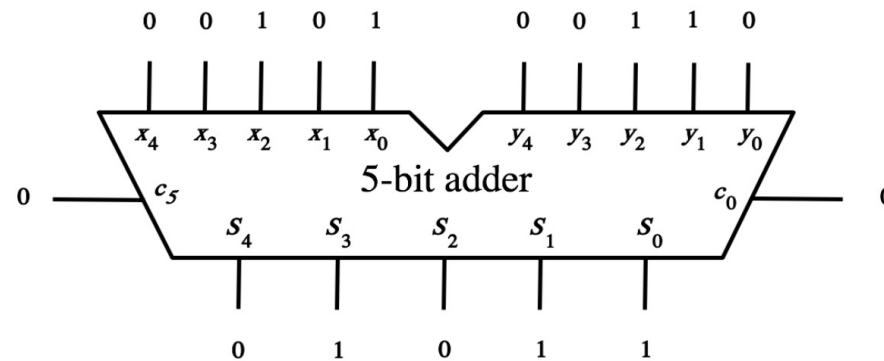- Addition of n-bit Binary numbers, e.g.,




Important Clarification: There are two types of addition

- Addition of Boolean variables, e.g.,

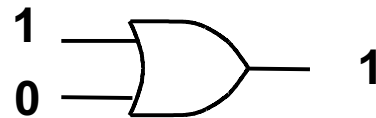

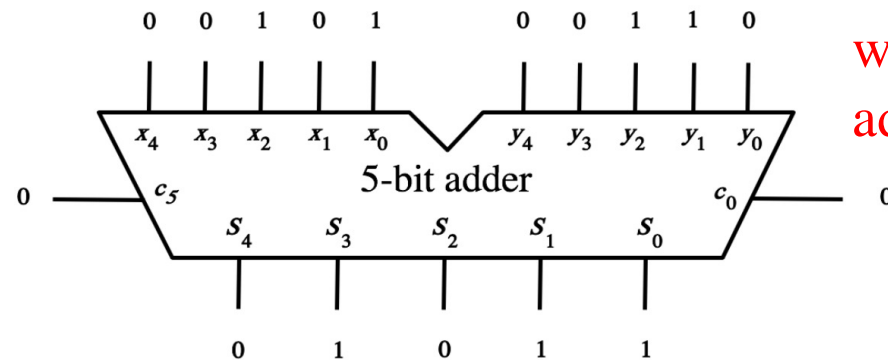- Addition of n-bit Binary numbers, e.g.,



we will derive this
adder circuit today

Important Clarification: There are two types of addition

- **Addition of Boolean variables, e.g.,**


$$1 + 1 = 1 \quad (\text{according to the rules of Boolean algebra})$$

- **Addition of n-bit Binary numbers, e.g.,**

$$1 + 1 = 10 \quad (\text{because in decimal } 1 + 1 = 2)$$


Addition of 1-bit Unsigned Numbers

Addition of two 1-bit numbers

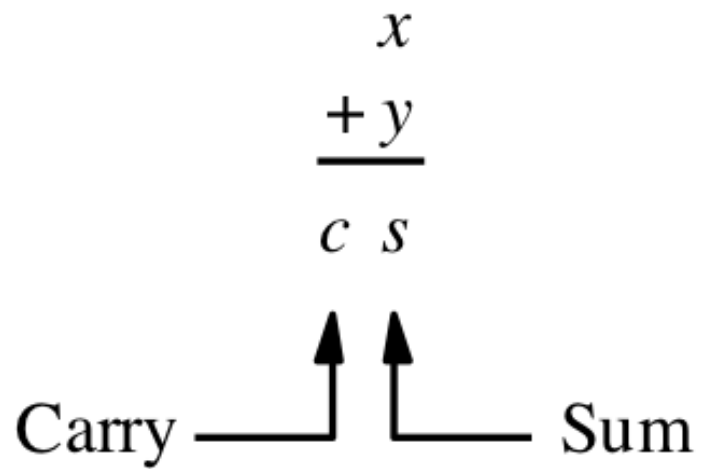

[Figure 3.1a from the textbook]

Addition of two 1-bit numbers (there are four possible cases)

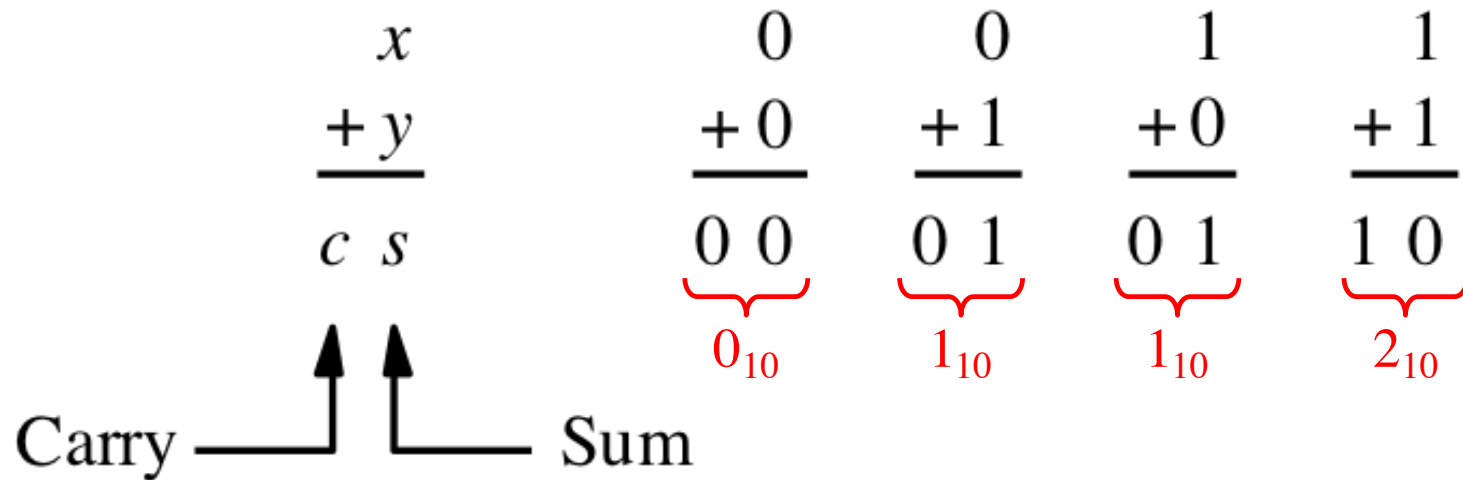

[Figure 3.1a from the textbook]

Addition of two 1-bit numbers (the truth table)

| x | y | Carry c | Sum s |
|-----|-----|--------------|------------|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 0 |

[Figure 3.1b from the textbook]

Addition of two 1-bit numbers

| | | | | |
|--------|-----------|-----------|-----------|-----------|
| x | 0 | 0 | 1 | 1 |
| $+y$ | <u>+0</u> | <u>+1</u> | <u>+0</u> | <u>+1</u> |
| $c\ s$ | 0 0 | 0 1 | 0 1 | 1 0 |

[Figure 2.12 from the textbook]

Addition of two 1-bit numbers

| | | | | |
|--------|-----------|-----------|-----------|-----------|
| x | 0 | 0 | 1 | 1 |
| $+y$ | <u>+0</u> | <u>+1</u> | <u>+0</u> | <u>+1</u> |
| $c\ s$ | 0 0 | 0 1 | 0 1 | 1 0 |

| x | y | c | s |
|-----|-----|-----|-----|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 0 |

Addition of two 1-bit numbers

| | | | | |
|--------|-----------|-----------|-----------|-----------|
| x | 0 | 0 | 1 | 1 |
| $+y$ | <u>+0</u> | <u>+1</u> | <u>+0</u> | <u>+1</u> |
| $c\ s$ | 0 0 | 0 1 | 0 1 | 1 0 |

| x | y | c | s |
|-----|-----|-----|-----|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 0 |

Addition of two 1-bit numbers

| | | | | |
|--------|-----------|-----------|-----------|-----------|
| x | 0 | 0 | 1 | 1 |
| $+y$ | <u>+0</u> | <u>+1</u> | <u>+0</u> | <u>+1</u> |
| $c\ s$ | 0 0 | 0 1 | 0 1 | 1 0 |

| x | y | c | s |
|-----|-----|-----|-----|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 0 |

Addition of two 1-bit numbers

| | | | | |
|--------|-----------|-----------|-----------|-----------|
| x | 0 | 0 | 1 | 1 |
| $+y$ | <u>+0</u> | <u>+1</u> | <u>+0</u> | <u>+1</u> |
| $c\ s$ | 0 0 | 0 1 | 0 1 | 1 0 |

| x | y | c | s |
|-----|-----|-----|-----|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 0 |

Addition of two 1-bit numbers

| | | | | |
|------------------------|-----------|-----------|-----------|-----------|
| x | 0 | 0 | 1 | 1 |
| <u>$+y$</u> | <u>+0</u> | <u>+1</u> | <u>+0</u> | <u>+1</u> |
| $c\ s$ | 0 0 | 0 1 | 0 1 | 1 0 |

| x | y | c | s |
|-----|-----|-----|-----|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 0 |

Addition of two 1-bit numbers

| | | | | |
|------------------------|-----------|-----------|-----------|-----------|
| x | 0 | 0 | 1 | 1 |
| <u>$+y$</u> | <u>+0</u> | <u>+1</u> | <u>+0</u> | <u>+1</u> |
| $c\ s$ | 0 0 | 0 1 | 0 1 | 1 0 |

| x | y | c | s |
|-----|-----|-----|-----|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 0 |

Addition of two 1-bit numbers

| | | | | |
|--------|-----------|-----------|-----------|-----------|
| x | 0 | 0 | 1 | 1 |
| $+y$ | <u>+0</u> | <u>+1</u> | <u>+0</u> | <u>+1</u> |
| $c\ s$ | 0 0 | 0 1 | 0 1 | 1 0 |

| x | y | c | s |
|-----|-----|-----|-----|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 0 |

Addition of two 1-bit numbers

$$\begin{array}{r} x \\ + y \\ \hline c \quad s \end{array} \quad \begin{array}{r} 0 \\ + 0 \\ \hline 0 \quad 0 \end{array} \quad \begin{array}{r} 0 \\ + 1 \\ \hline 0 \quad 1 \end{array} \quad \begin{array}{r} 1 \\ + 0 \\ \hline 0 \quad 1 \end{array} \quad \begin{array}{r} 1 \\ + 1 \\ \hline 1 \quad 0 \end{array}$$

| x | y | c | s |
|-----|-----|-----|-----|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 0 |

Addition of two 1-bit numbers

$$\begin{array}{r} x \\ + y \\ \hline c \quad s \end{array} \quad \begin{array}{r} 0 \\ + 0 \\ \hline 0 \quad 0 \end{array} \quad \begin{array}{r} 0 \\ + 1 \\ \hline 0 \quad 1 \end{array} \quad \begin{array}{r} 1 \\ + 0 \\ \hline 0 \quad 1 \end{array} \quad \begin{array}{r} 1 \\ + 1 \\ \hline 1 \quad 0 \end{array}$$

| x | y | c | s |
|-----|-----|-----|-----|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 0 |

Addition of two 1-bit numbers

| | | | | |
|--------|-----------|-----------|-----------|-----------|
| x | 0 | 0 | 1 | 1 |
| $+y$ | <u>+0</u> | <u>+1</u> | <u>+0</u> | <u>+1</u> |
| $c\ s$ | 0 0 | 0 1 | 0 1 | 1 0 |

| x | y | c | s |
|-----|-----|-----|-----|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 0 |

Addition of two 1-bit numbers

$$\begin{array}{r} x \\ + y \\ \hline c \quad s \end{array} \quad \begin{array}{r} 0 \\ + 0 \\ \hline 0 \quad 0 \end{array} \quad \begin{array}{r} 0 \\ + 1 \\ \hline 0 \quad 1 \end{array} \quad \begin{array}{r} 1 \\ + 0 \\ \hline 0 \quad 1 \end{array} \quad \begin{array}{r} 1 \\ + 1 \\ \hline 1 \quad 0 \end{array}$$

| x | y | c | s |
|-----|-----|-----|-----|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 0 |

Addition of two 1-bit numbers

$$\begin{array}{r} x \\ + y \\ \hline c \quad s \end{array} \quad \begin{array}{r} 0 \\ + 0 \\ \hline 0 \quad 0 \end{array} \quad \begin{array}{r} 0 \\ + 1 \\ \hline 0 \quad 1 \end{array} \quad \begin{array}{r} 1 \\ + 0 \\ \hline 0 \quad 1 \end{array} \quad \begin{array}{r} 1 \\ + 1 \\ \hline 1 \quad 0 \end{array}$$

| x | y | c | s |
|-----|-----|-----|-----|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 0 |

Addition of two 1-bit numbers

| | | | | |
|--------|-----------|-----------|-----------|-----------|
| x | 0 | 0 | 1 | 1 |
| $+y$ | <u>+0</u> | <u>+1</u> | <u>+0</u> | <u>+1</u> |
| $c\ s$ | 0 0 | 0 1 | 0 1 | 1 0 |

| x | y | c | s |
|-----|-----|-----|-----|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 0 |

Addition of two 1-bit numbers

| x | y | c | s |
|-----|-----|-----|-----|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 0 |

Addition of two 1-bit numbers

| x | y | | c | | s | | | |
|-----|-----|---|-----|---|-----|---|---|----------|
| 0 | + | 0 | = | 0 | | 0 | = | 0_{10} |
| 0 | + | 1 | = | 0 | | 1 | = | 1_{10} |
| 1 | + | 0 | = | 0 | | 1 | = | 1_{10} |
| 1 | + | 1 | = | 1 | | 0 | = | 2_{10} |

Addition of two 1-bit numbers

| x | y | c | s |
|-----|-----|-----|-----|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 0 |

Addition of two 1-bit numbers

AND

| <i>x</i> | <i>y</i> | <i>c</i> | <i>s</i> |
|----------|----------|----------|----------|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 0 |

Addition of two 1-bit numbers

| x | y | c | s |
|-----|-----|-----|-----|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 0 |

Addition of two 1-bit numbers

| x | y | c | s |
|-----|-----|-----|-----|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 0 |

?

Addition of two 1-bit numbers


XOR

| x | y | c | s |
|-----|-----|-----|-----|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 0 |

Addition of two 1-bit numbers


| x | y | c | s |
|-----|-----|-----|-----|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 0 |

Addition of two 1-bit numbers

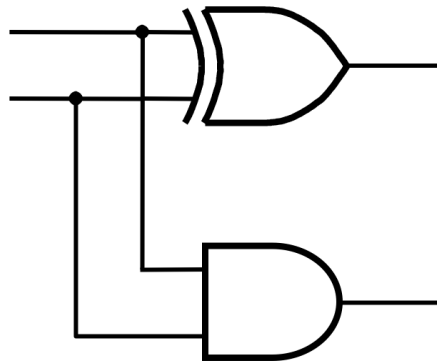


| x | y | c | s |
|-----|-----|-----|-----|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 0 |

Addition of two 1-bit numbers

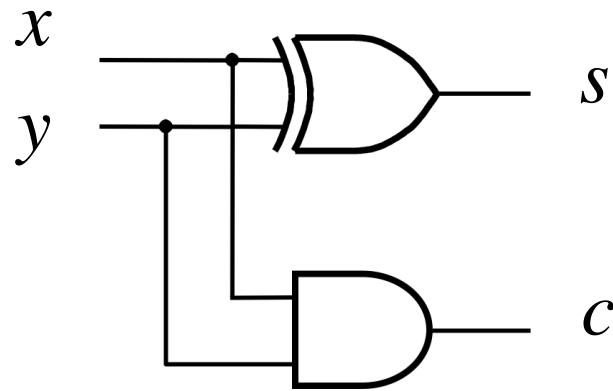


| x | y | c | s |
|-----|-----|-----|-----|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 0 |

Addition of two 1-bit numbers (the logic circuit)

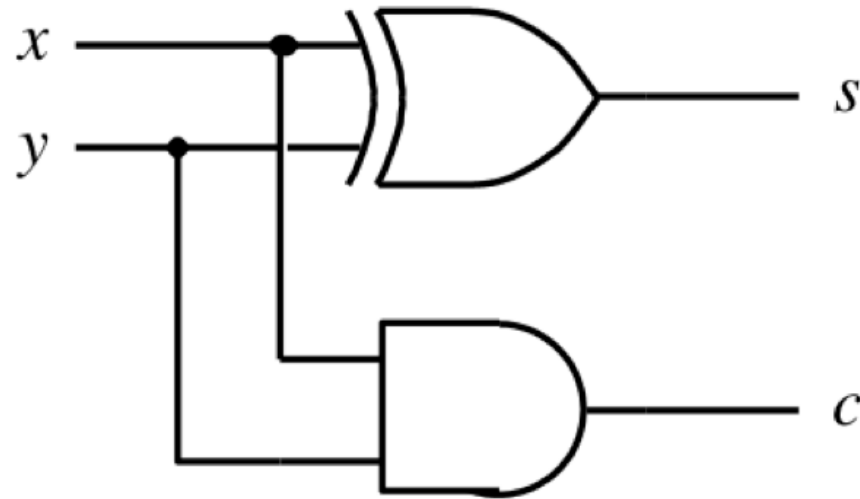


[Figure 3.1c from the textbook]

The Half-Adder

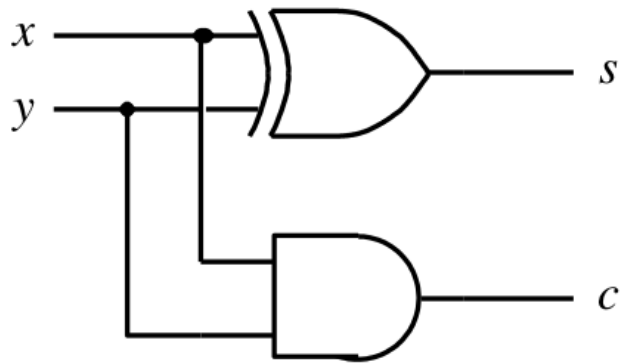

(c) Circuit

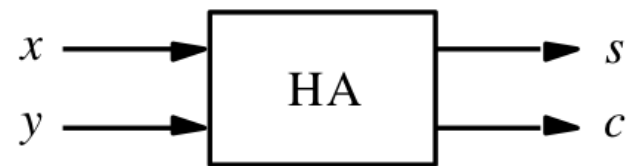

(d) Graphical symbol

Addition of Multibit Unsigned Numbers

Analogy with addition in base 10

$$\begin{array}{r} + \quad \quad \quad x_2 \quad x_1 \quad x_0 \\ \quad \quad \quad y_2 \quad y_1 \quad y_0 \\ \hline \quad \quad \quad s_2 \quad s_1 \quad s_0 \end{array}$$

Analogy with addition in base 10

$$\begin{array}{r} + \quad 3 \quad 8 \quad 9 \\ \quad 1 \quad 5 \quad 7 \\ \hline \quad 5 \quad 4 \quad 6 \end{array}$$

Analogy with addition in base 10

| | | | | |
|-------|---|-------|---|---|
| carry | 0 | 1 | 1 | 0 |
| | | 3 | 8 | 9 |
| + | | 1 | 5 | 7 |
| | | <hr/> | | |
| | | 5 | 4 | 6 |

Analogy with addition in base 10

$$\begin{array}{rcccc} & C_3 & C_2 & C_1 & C_0 \\ + & & X_2 & X_1 & X_0 \\ & & Y_2 & Y_1 & Y_0 \\ \hline & & S_2 & S_1 & S_0 \end{array}$$

Analogy with addition in base 10

$$\begin{array}{rcccc} & C_3 & C_2 & C_1 & C_0 \\ + & & X_2 & X_1 & X_0 \\ & & Y_2 & Y_1 & Y_0 \\ \hline & & S_2 & S_1 & S_0 \end{array}$$

given these
3 inputs

compute these
2 outputs

Analogy with addition in base 10

$$\begin{array}{rcccc} & C_3 & C_2 & C_1 & C_0 \\ + & & X_2 & X_1 & X_0 \\ & & Y_2 & Y_1 & Y_0 \\ \hline & & S_2 & S_1 & S_0 \end{array}$$

Analogy with addition in base 10

$$\begin{array}{r} \\ \\ \\ \\ \hline \end{array} \begin{array}{cccc} C_3 & C_2 & C_1 & C_0 \\ X_2 & X_1 & X_0 & \\ Y_2 & Y_1 & Y_0 & \\ S_2 & S_1 & S_0 & \end{array}$$

The diagram illustrates the analogy between addition in base 10 and a carry propagation process. It shows a vertical stack of variables: C_3 (red box), C_2 (blue box), X_2 (blue box), Y_2 (blue box), a horizontal line, S_2 (red box), S_1 , and S_0 . A plus sign is positioned to the left of the stack. The variables C_2 , X_2 , and Y_2 are grouped together in a light blue vertical box, representing the carry-in to the second stage. The variables C_3 and S_2 are highlighted in red boxes, representing the carry-out from the second stage and the carry-in to the third stage, respectively. The variables C_1 , C_0 , X_1 , X_0 , Y_1 , Y_0 , S_1 , and S_0 are in black text.

Addition of multibit numbers

Generated carries \longrightarrow 1 1 1 0

$$\begin{array}{r}
 X = x_4x_3x_2x_1x_0 \quad 01111 \quad (15)_{10} \\
 + Y = y_4y_3y_2y_1y_0 \quad + 01010 \quad + (10)_{10} \\
 \hline
 S = s_4s_3s_2s_1s_0 \quad 11001 \quad (25)_{10}
 \end{array}$$

Bit position i

[Figure 3.2 from the textbook]

Problem Statement and Truth Table


| | | | |
|-----|-----------|-------|-----|
| ... | c_{i+1} | c_i | ... |
| ... | ... | x_i | ... |
| ... | ... | y_i | ... |
| ... | ... | s_i | ... |

| c_i | x_i | y_i | c_{i+1} | s_i |
|-------|-------|-------|-----------|-------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 1 | 1 |

[Figure 3.2b from the textbook]

[Figure 3.3a from the textbook]

Problem Statement and Truth Table

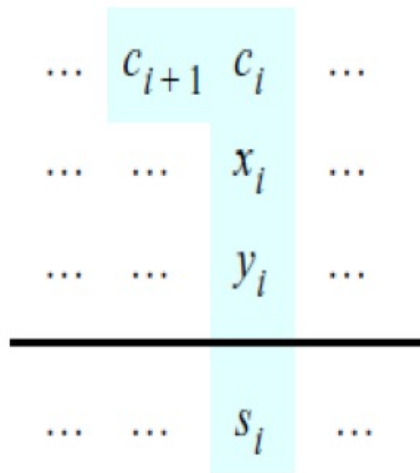

| c_i | x_i | y_i | c_{i+1} | s_i |
|-------|-------|-------|-----------|-------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 1 | 1 |

[Figure 3.2b from the textbook]

[Figure 3.3a from the textbook]

Let's fill-in the two K-maps

| c_i | x_i | y_i | c_{i+1} | s_i |
|-------|-------|-------|-----------|-------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 1 | 1 |

$x_i y_i$

| c_i | 00 | 01 | 11 | 10 |
|-------|----|----|----|----|
| 0 | | | | |
| 1 | | | | |

$s_i =$

$x_i y_i$

| c_i | 00 | 01 | 11 | 10 |
|-------|----|----|----|----|
| 0 | | | | |
| 1 | | | | |


$c_{i+1} =$

[Figure 3.3a-b from the textbook]


Let's fill-in the two K-maps

Note that the textbook switched to the other way to draw a K-Map

| c_i | x_i | y_i | c_{i+1} | s_i |
|-------|-------|-------|-----------|-------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 1 | 1 |

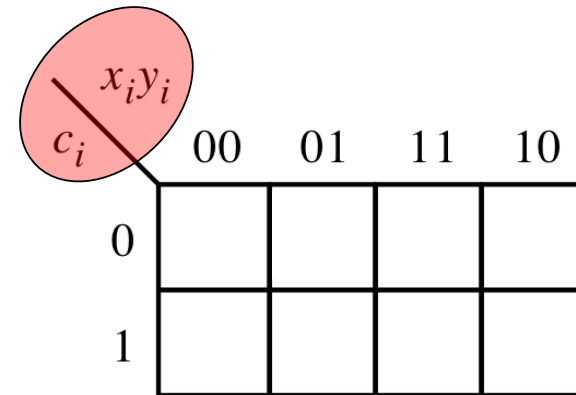

$s_i =$

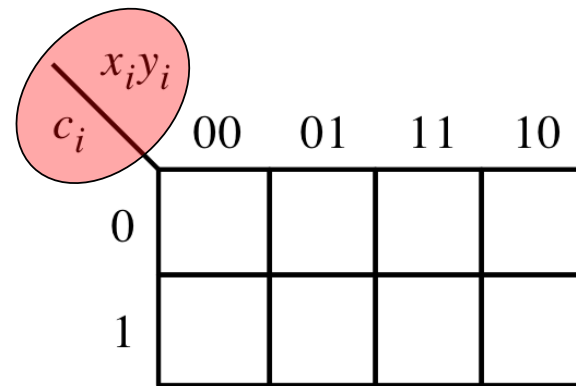


$c_{i+1} =$

[Figure 3.3a-b from the textbook]


Let's fill-in the two K-maps

Note that the textbook switched to the other way to draw a K-Map

| c_i | x_i | y_i | c_{i+1} | s_i |
|-------|-------|-------|-----------|-------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 1 | 1 |

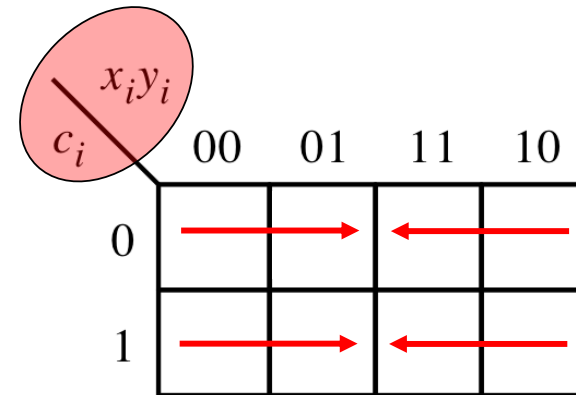

$s_i =$

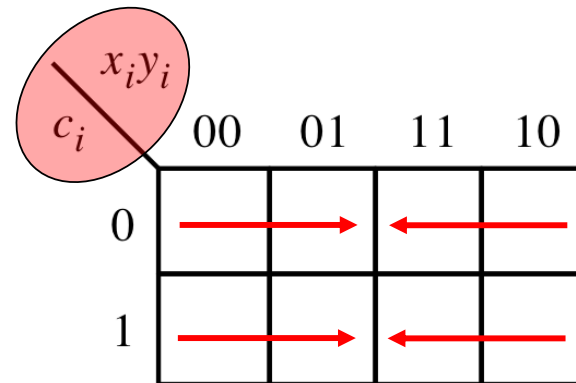

$c_{i+1} =$

[Figure 3.3a-b from the textbook]

Let's fill-in the two K-maps

| c_i | x_i | y_i | c_{i+1} | s_i |
|-------|-------|-------|-----------|-------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 1 | 1 |

| $c_i \backslash x_i y_i$ | 00 | 01 | 11 | 10 |
|--------------------------|----|----|----|----|
| 0 | | 1 | | 1 |
| 1 | 1 | | 1 | |

$$s_i = x_i \oplus y_i \oplus c_i$$

| $c_i \backslash x_i y_i$ | 00 | 01 | 11 | 10 |
|--------------------------|----|----|----|----|
| 0 | | | 1 | |
| 1 | | 1 | 1 | 1 |

$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

[Figure 3.3a-b from the textbook]

Let's fill-in the two K-maps

| c_i | x_i | y_i | c_{i+1} | s_i |
|-------|-------|-------|-----------|-------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 1 | 1 |

| | | | | | |
|-------|-----------|----|----|----|----|
| | $x_i y_i$ | | | | |
| c_i | | 00 | 01 | 11 | 10 |
| 0 | | | 1 | | 1 |
| 1 | | 1 | | 1 | |

3-input XOR


$$s_i = x_i \oplus y_i \oplus c_i$$

| | | | | | |
|-------|-----------|----|----|----|----|
| | $x_i y_i$ | | | | |
| c_i | | 00 | 01 | 11 | 10 |
| 0 | | | | 1 | |
| 1 | | | 1 | 1 | 1 |

$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$


[Figure 3.3a-b from the textbook]

The circuit for the two expressions

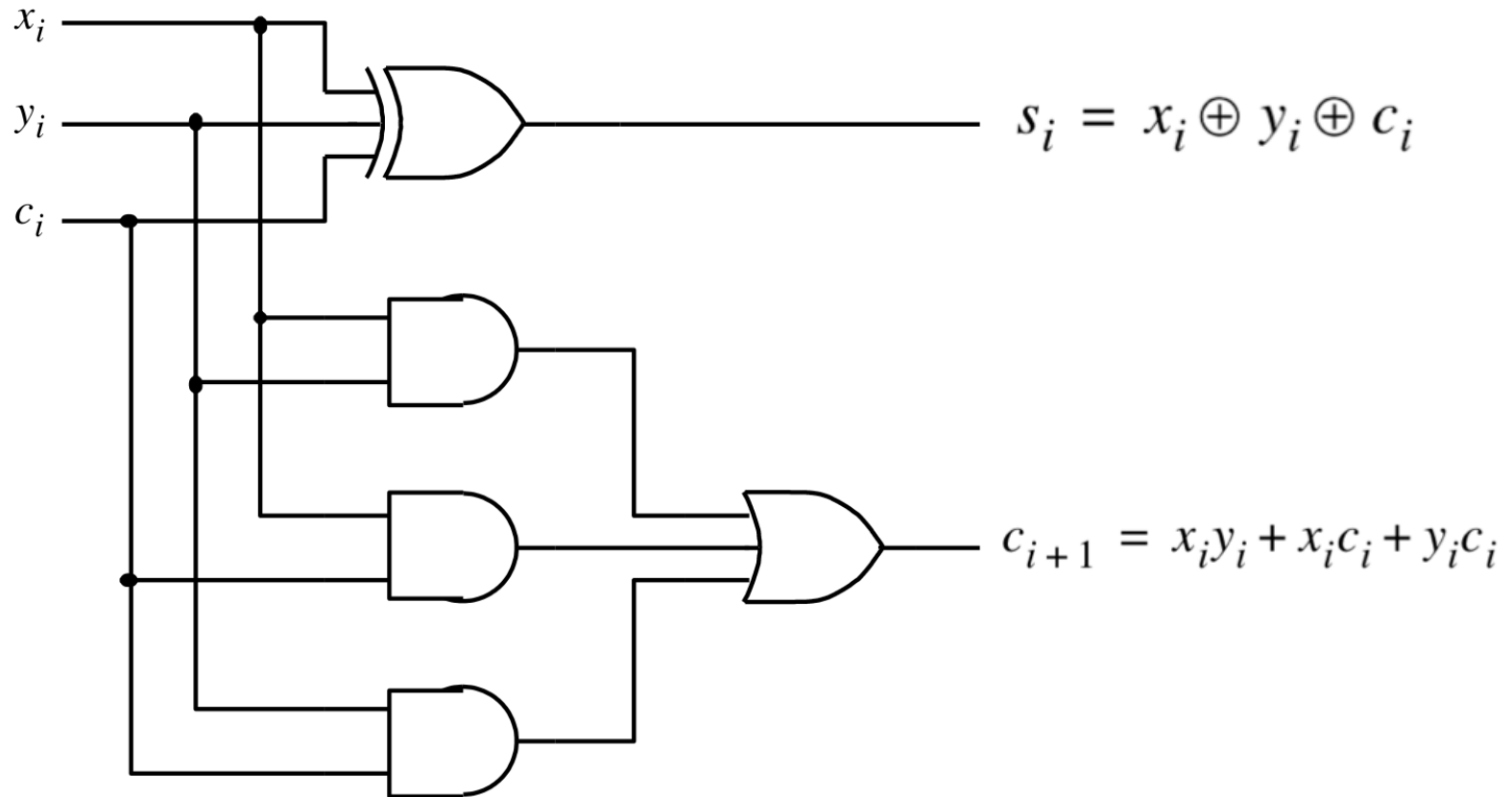


[Figure 3.3c from the textbook]

This is called the Full-Adder

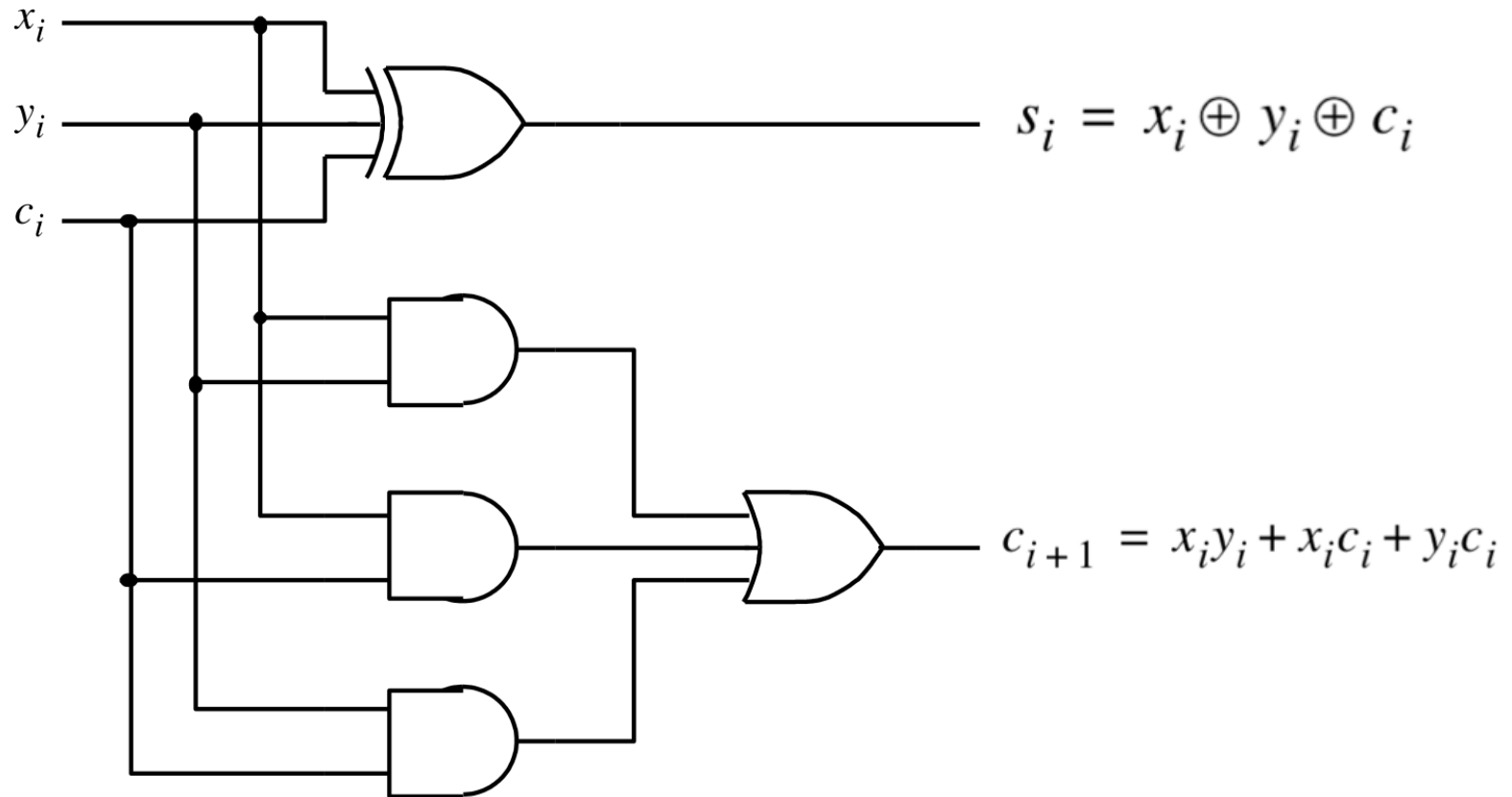

[Figure 3.3c from the textbook]

This is called the Full-Adder

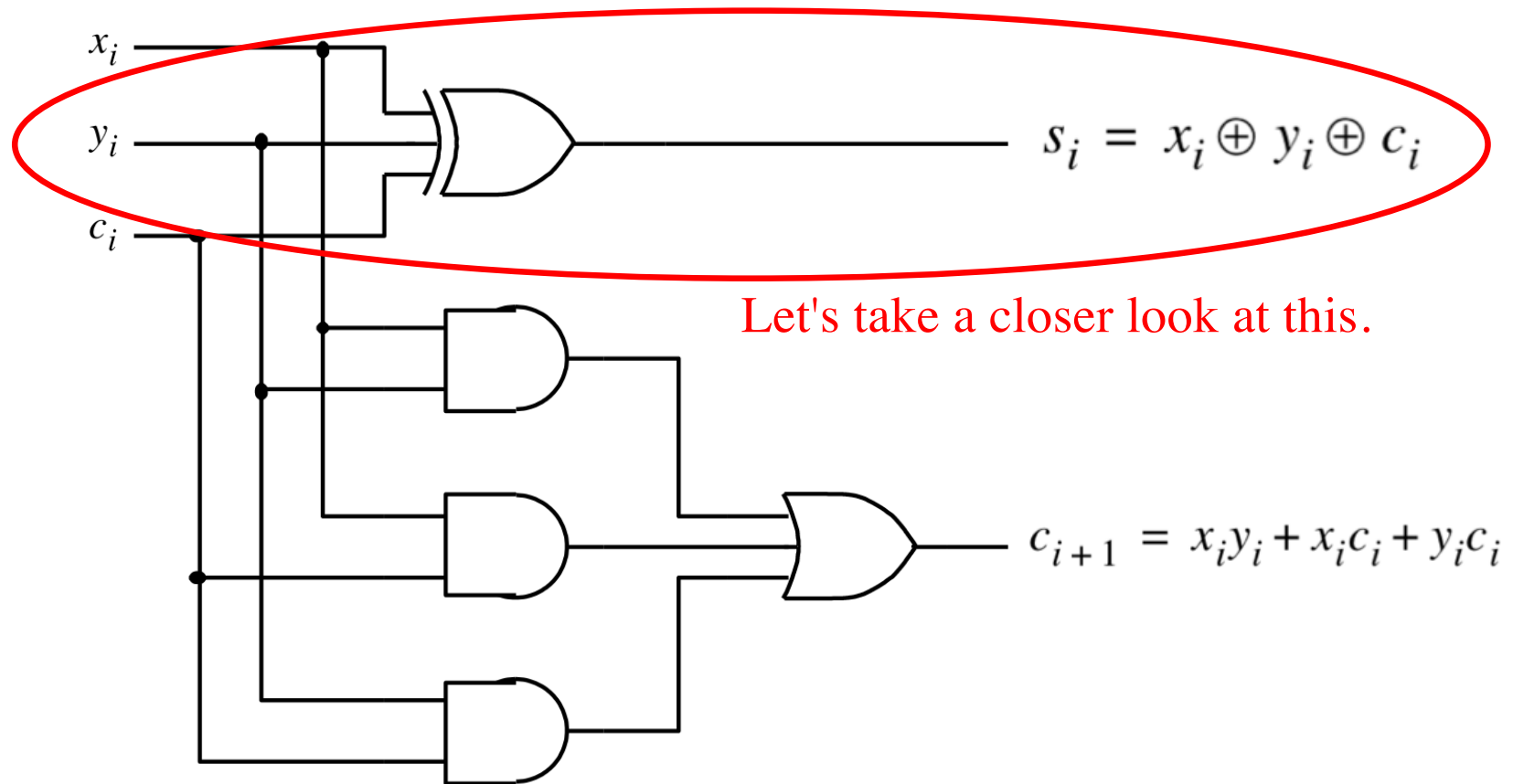

[Figure 3.3c from the textbook]

XOR Magic

$$s_i = \bar{x}_i y_i \bar{c}_i + x_i \bar{y}_i \bar{c}_i + \bar{x}_i \bar{y}_i c_i + x_i y_i c_i$$

| c_i \ $x_i y_i$ | 00 | 01 | 11 | 10 |
|-------------------|----|----|----|----|
| 0 | | 1 | | 1 |
| 1 | 1 | | 1 | |

$$s_i = x_i \oplus y_i \oplus c_i$$

XOR Magic

$$s_i = \bar{x}_i y_i \bar{c}_i + x_i \bar{y}_i \bar{c}_i + \bar{x}_i \bar{y}_i c_i + x_i y_i c_i$$

| c_i | $x_i y_i$ | 00 | 01 | 11 | 10 |
|-------|-----------|----|----|----|----|
| 0 | | | 1 | | 1 |
| 1 | | 1 | | 1 | |

$$s_i = x_i \oplus y_i \oplus c_i$$

XOR Magic

$$s_i = \bar{x}_i y_i \bar{c}_i + x_i \bar{y}_i \bar{c}_i + \bar{x}_i \bar{y}_i c_i + x_i y_i c_i$$

$$s_i = (\bar{x}_i y_i + x_i \bar{y}_i) \bar{c}_i + (\bar{x}_i \bar{y}_i + x_i y_i) c_i$$

$$= (x_i \oplus y_i) \bar{c}_i + \overline{(x_i \oplus y_i)} c_i$$

$$= (x_i \oplus y_i) \oplus c_i$$

XOR Magic

$$s_i = \bar{x}_i y_i \bar{c}_i + x_i \bar{y}_i \bar{c}_i + \bar{x}_i \bar{y}_i c_i + x_i y_i c_i$$

Can you prove this?

$$\begin{aligned} s_i &= (\bar{x}_i y_i + x_i \bar{y}_i) \bar{c}_i + (\bar{x}_i \bar{y}_i + x_i y_i) c_i \\ &= (x_i \oplus y_i) \bar{c}_i + \overline{(x_i \oplus y_i)} c_i \\ &= (x_i \oplus y_i) \oplus c_i \end{aligned}$$

XOR Magic

$$\overline{x_i} \overline{y_i} + x_i y_i = \overline{x_i \oplus y_i}$$

XOR Magic

$$\overline{x_i} \overline{y_i} + x_i y_i = \overline{x_i \oplus y_i}$$

XNOR

XOR Magic

$$\overline{x_i} \overline{y_i} + x_i y_i = \overline{x_i \oplus y_i}$$

XOR

XOR Magic

$$\overline{x_i} \overline{y_i} + x_i y_i = \overline{x_i \oplus y_i}$$

XNOR


XOR Magic

$$\overline{x_i} \overline{y_i} + x_i y_i = \overline{x_i \oplus y_i}$$

You can also prove this using the theorems of Boolean algebra.

Try that at home.



The Full-Adder Circuit

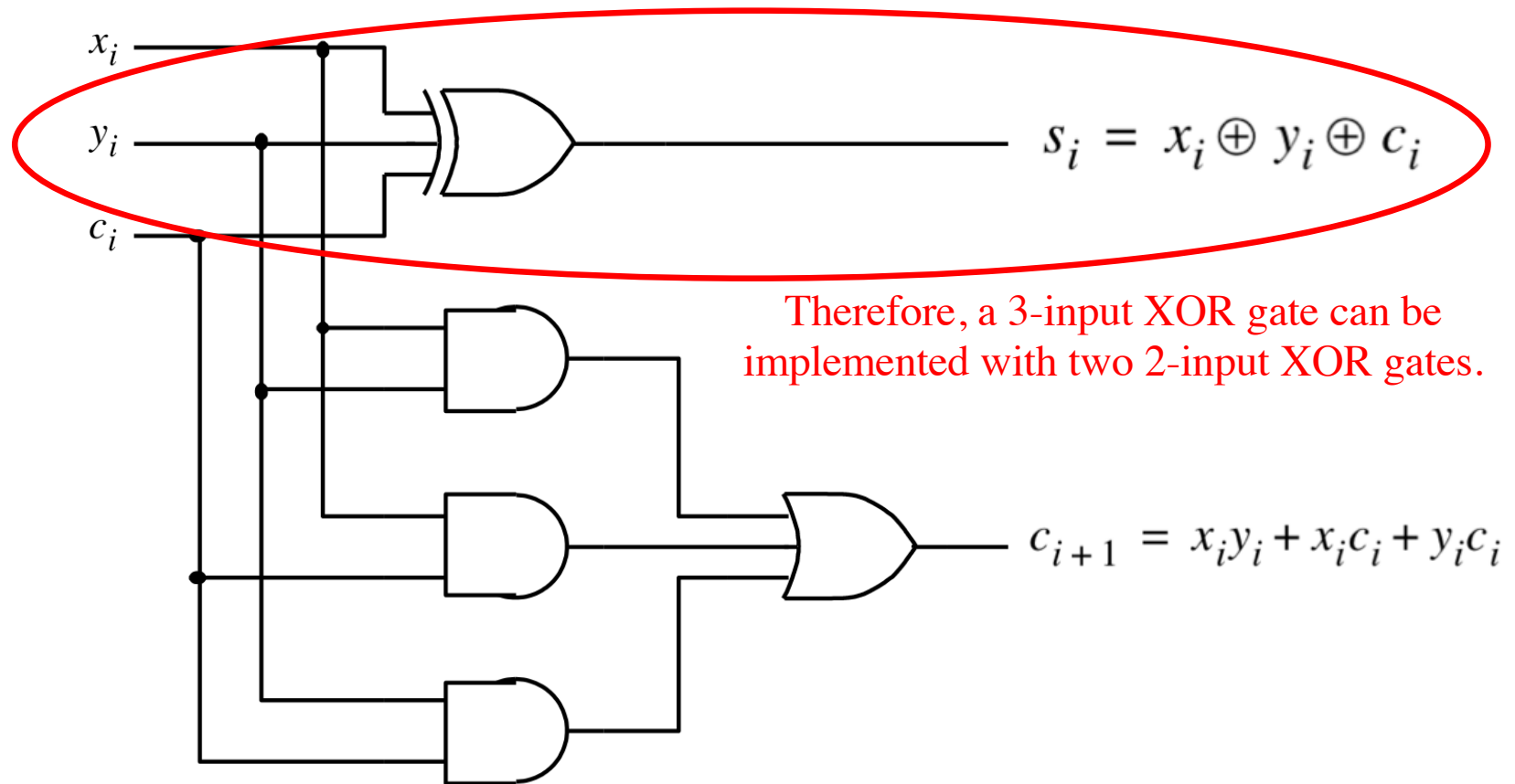


[Figure 3.3c from the textbook]

s_i can be implemented in two different ways

$$s_i = x_i \oplus y_i \oplus c_i$$

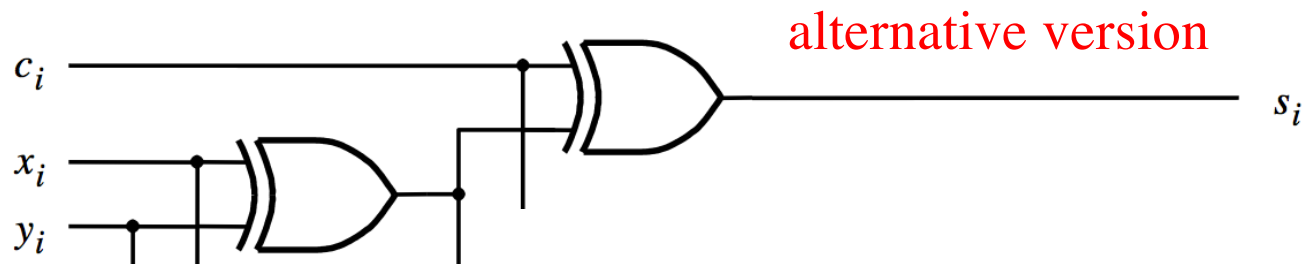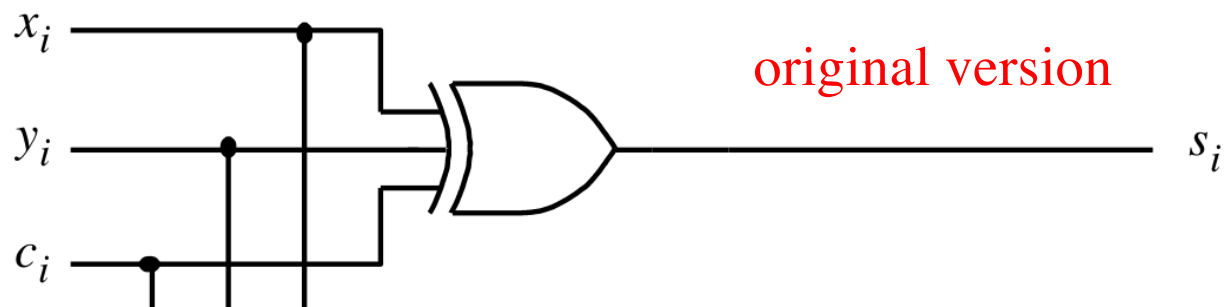


The Full-Adder Circuit (alternative drawing)

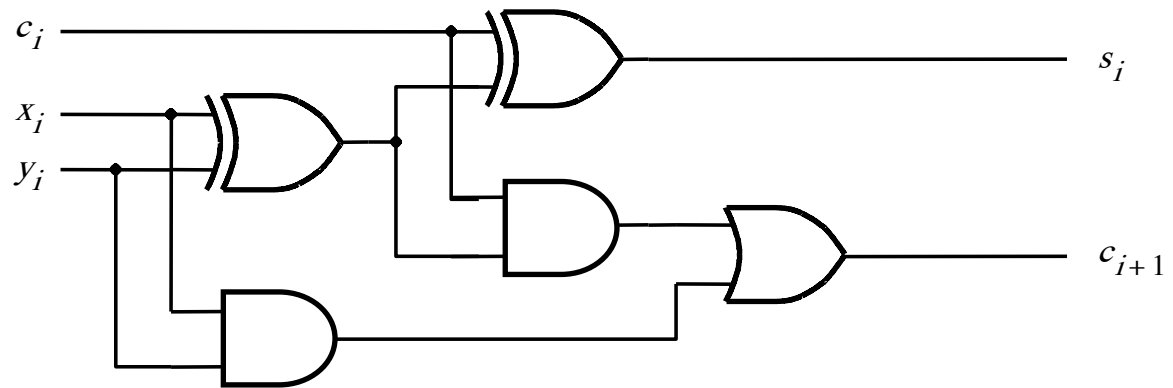


[Figure 3.4b from the textbook]

The Full-Adder Circuit (alternative drawing)

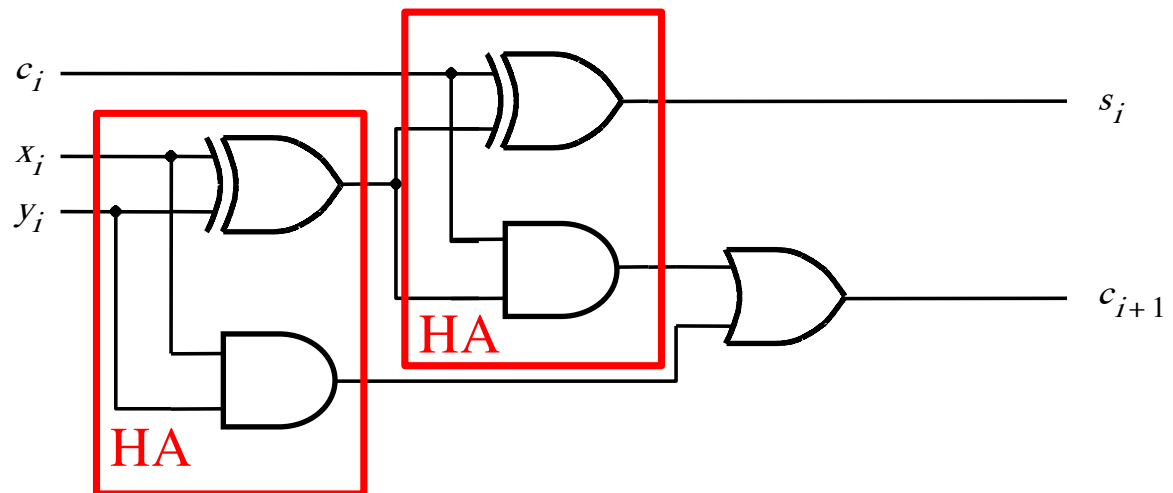


[Figure 3.4b from the textbook]

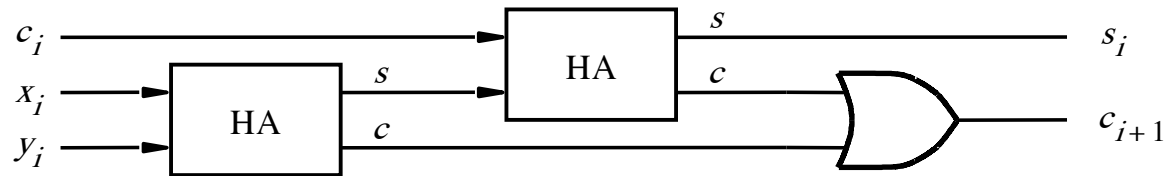The Full-Adder Circuit (alternative drawing)




(a) Block diagram

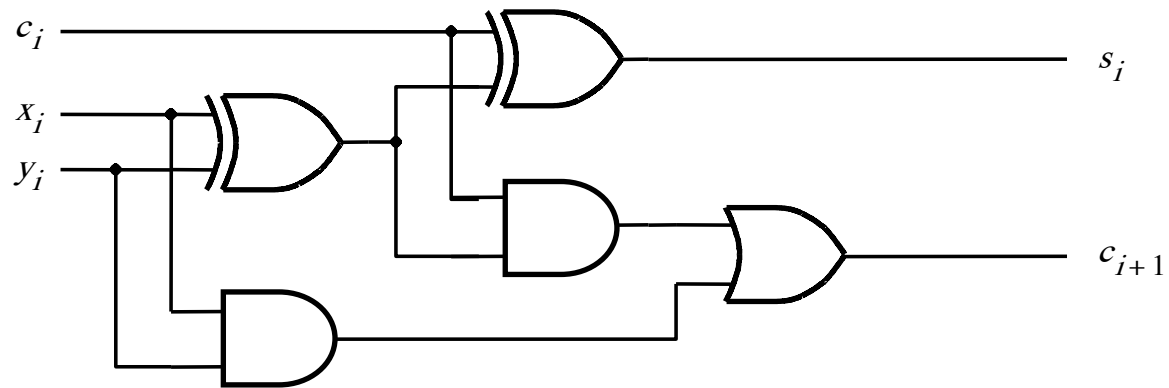

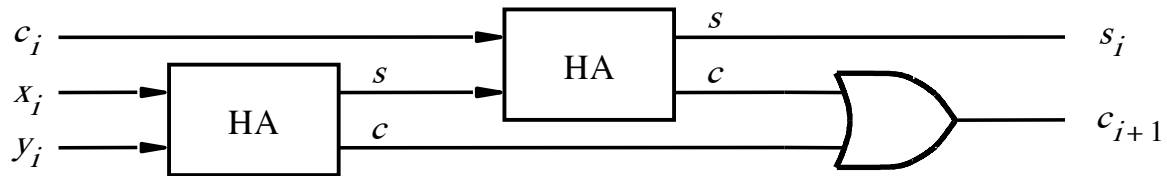
(b) Detailed diagram

[Figure 3.4 from the textbook]

The Full-Adder Circuit (alternative drawing)




(a) Block diagram

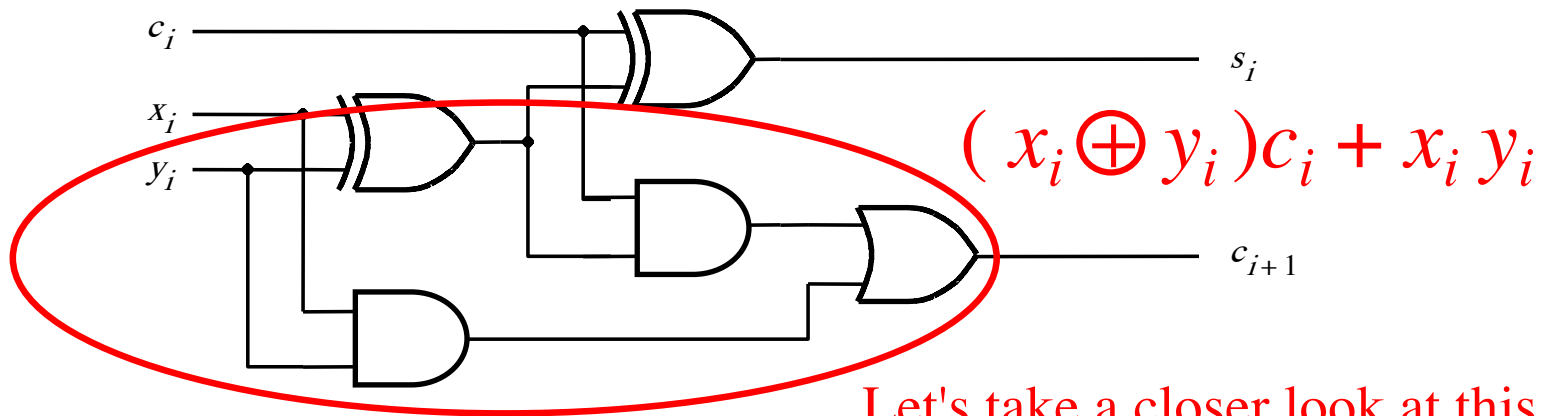

Let's take a closer look at this.

(b) Detailed diagram

The Full-Adder Circuit

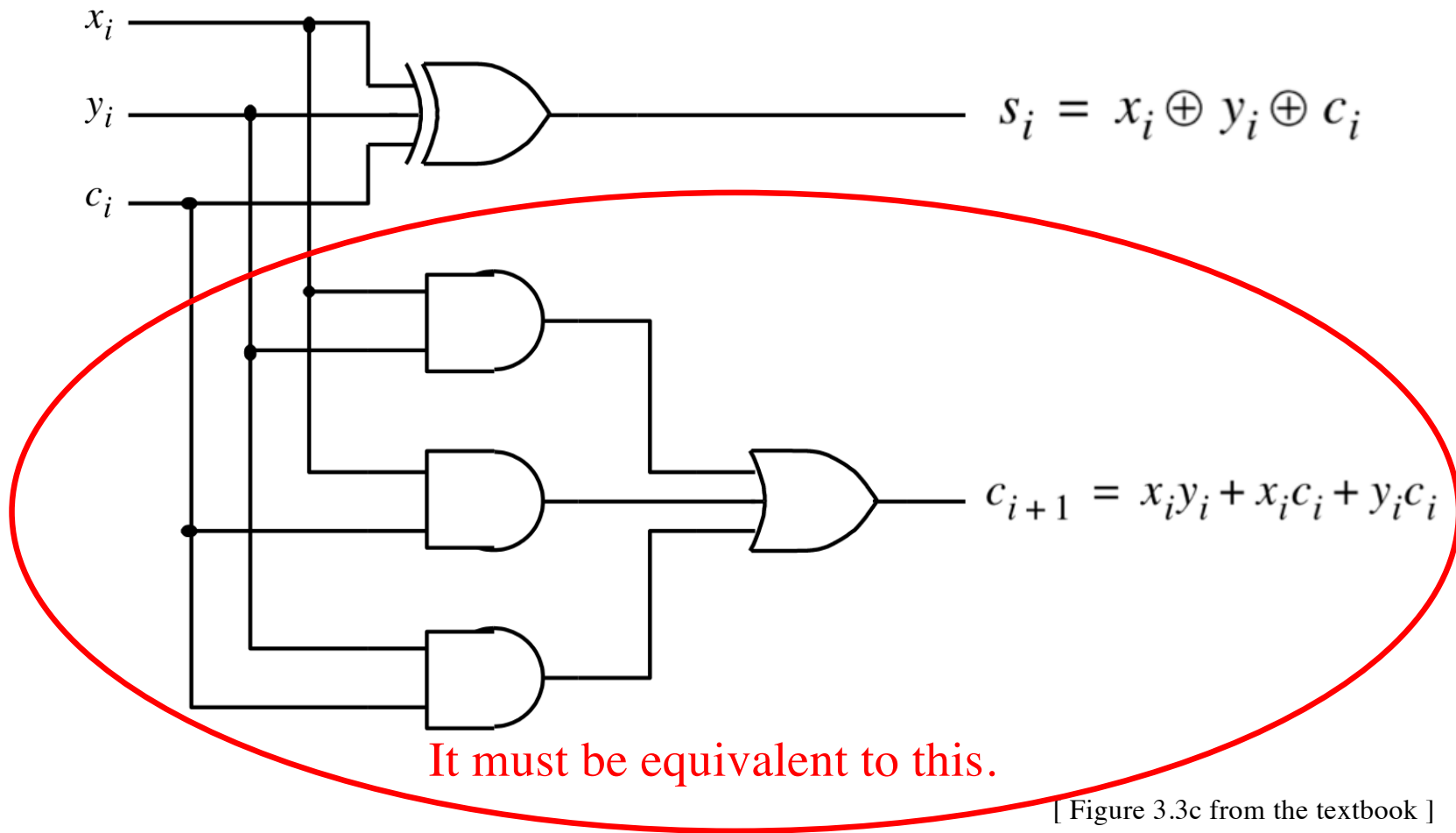

[Figure 3.3c from the textbook]

Let's Prove This

$$(x_i \oplus y_i)c_i + x_i y_i \stackrel{?}{=} x_i y_i + x_i c_i + c_i y_i$$

Let's Prove This

$$(x_i \oplus y_i)c_i + x_i y_i =$$

Let's Prove This

$$(x_i \oplus y_i)c_i + x_i y_i = (\bar{x}_i y_i + x_i \bar{y}_i)c_i + x_i y_i$$

Let's Prove This

$$\begin{aligned}(x_i \oplus y_i)c_i + x_i y_i &= (\bar{x}_i y_i + x_i \bar{y}_i)c_i + x_i y_i \\ &= \bar{x}_i y_i c_i + x_i \bar{y}_i c_i + x_i y_i + x_i y_i\end{aligned}$$

double
this term

Let's Prove This

$$\begin{aligned}(x_i \oplus y_i)c_i + x_i y_i &= (\bar{x}_i y_i + x_i \bar{y}_i)c_i + x_i y_i \\ &= \boxed{\bar{x}_i y_i c_i} + \boxed{x_i \bar{y}_i c_i} + \boxed{x_i y_i} + \boxed{x_i y_i}\end{aligned}$$

Let's Prove This

$$\begin{aligned}(x_i \oplus y_i)c_i + x_i y_i &= (\bar{x}_i y_i + x_i \bar{y}_i)c_i + x_i y_i \\ &= \boxed{\bar{x}_i y_i c_i} + \boxed{x_i \bar{y}_i c_i} + \boxed{x_i y_i} + \boxed{x_i y_i} \\ &= (\bar{x}_i c_i + x_i) y_i + x_i (\bar{y}_i c_i + y_i)\end{aligned}$$

Let's Prove This

$$\begin{aligned}(x_i \oplus y_i)c_i + x_i y_i &= (\bar{x}_i y_i + x_i \bar{y}_i)c_i + x_i y_i \\ &= \bar{x}_i y_i c_i + x_i \bar{y}_i c_i + x_i y_i + x_i y_i \\ &= (\bar{x}_i c_i + x_i) y_i + x_i (\bar{y}_i c_i + y_i) \\ &= (c_i + x_i) y_i + x_i (c_i + y_i)\end{aligned}$$

use Theorem 16a twice

Let's Prove This

$$\begin{aligned}(x_i \oplus y_i)c_i + x_i y_i &= (\overline{x_i} y_i + x_i \overline{y_i})c_i + x_i y_i \\ &= \overline{x_i} y_i c_i + x_i \overline{y_i} c_i + x_i y_i + x_i y_i \\ &= (\overline{x_i} c_i + x_i) y_i + x_i (\overline{y_i} c_i + y_i) \\ &= (c_i + x_i) y_i + x_i (c_i + y_i) \\ &= c_i y_i + x_i y_i + x_i c_i + x_i y_i\end{aligned}$$

Let's Prove This



$$\begin{aligned}(x_i \oplus y_i)c_i + x_i y_i &= (\bar{x}_i y_i + x_i \bar{y}_i)c_i + x_i y_i \\ &= \bar{x}_i y_i c_i + x_i \bar{y}_i c_i + x_i y_i + x_i y_i \\ &= (\bar{x}_i c_i + x_i) y_i + x_i (\bar{y}_i c_i + y_i) \\ &= (c_i + x_i) y_i + x_i (c_i + y_i) \\ &= c_i y_i + x_i y_i + x_i c_i + x_i y_i\end{aligned}$$

remove one copy of
this doubled term


Let's Prove This

$$\begin{aligned}(x_i \oplus y_i)c_i + x_i y_i &= (\overline{x_i} y_i + x_i \overline{y_i})c_i + x_i y_i \\ &= \overline{x_i} y_i c_i + x_i \overline{y_i} c_i + x_i y_i + x_i y_i \\ &= (\overline{x_i} c_i + x_i) y_i + x_i (\overline{y_i} c_i + y_i) \\ &= (c_i + x_i) y_i + x_i (c_i + y_i) \\ &= c_i y_i + x_i y_i + x_i c_i + x_i y_i \\ &= c_i y_i + x_i y_i + x_i c_i\end{aligned}$$


Therefore, these circuits are equivalent

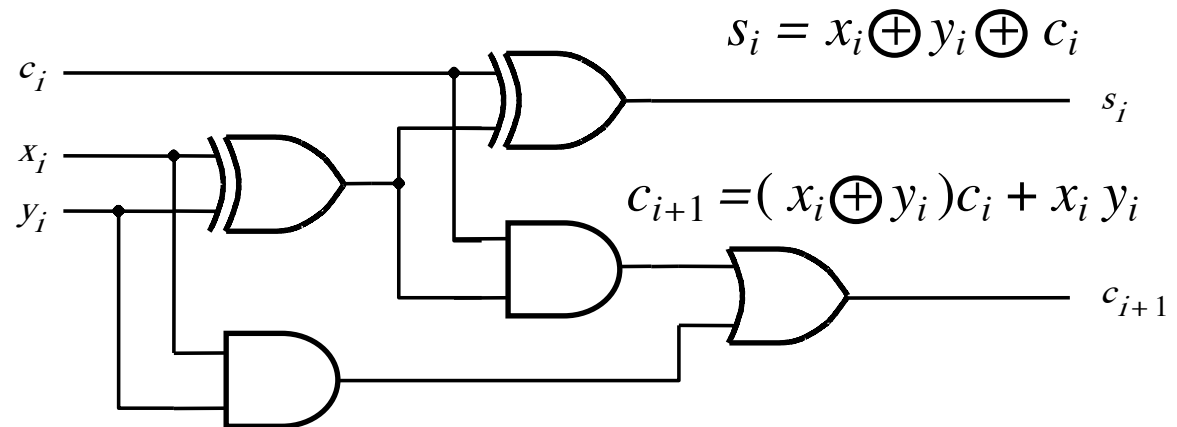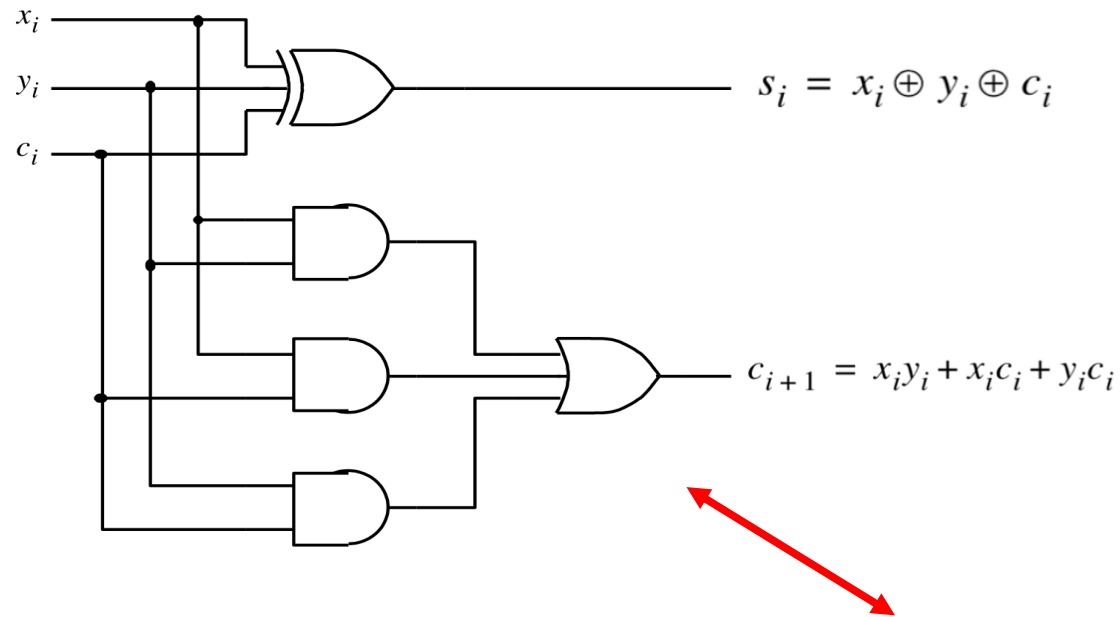


The Full-Adder Abstraction

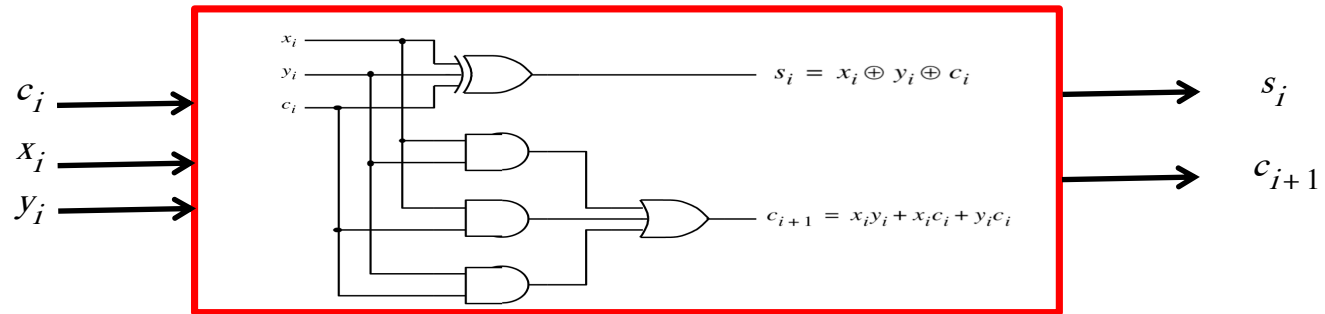


The Full-Adder Abstraction

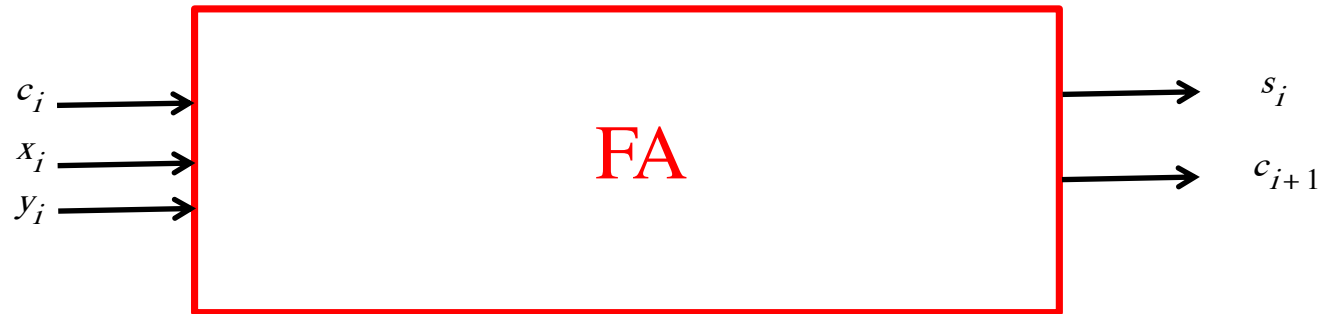


The Full-Adder Abstraction

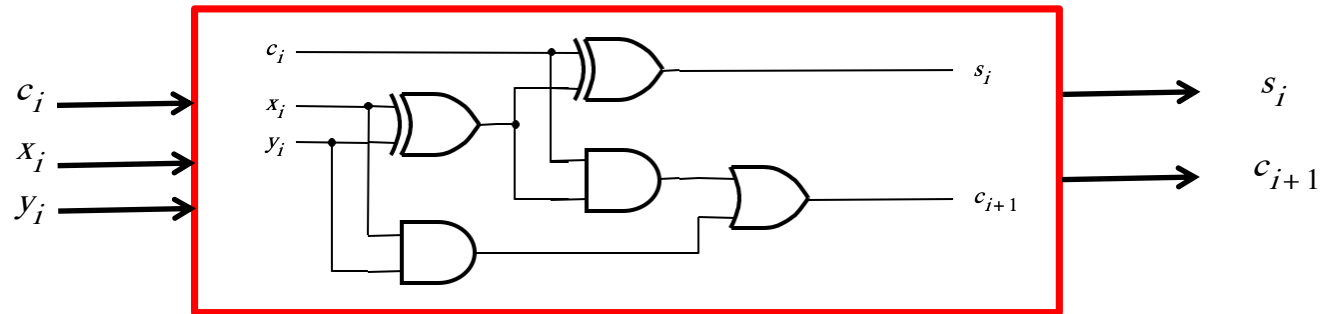


The Full-Adder Abstraction

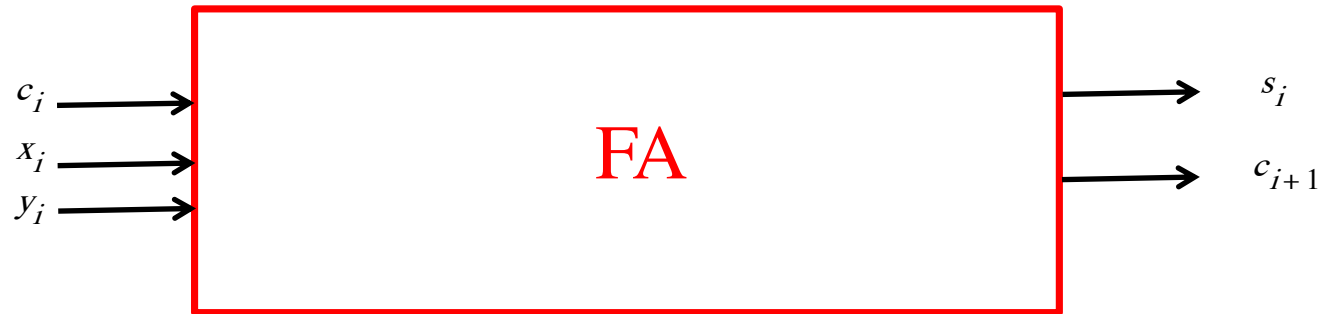


The Full-Adder Abstraction

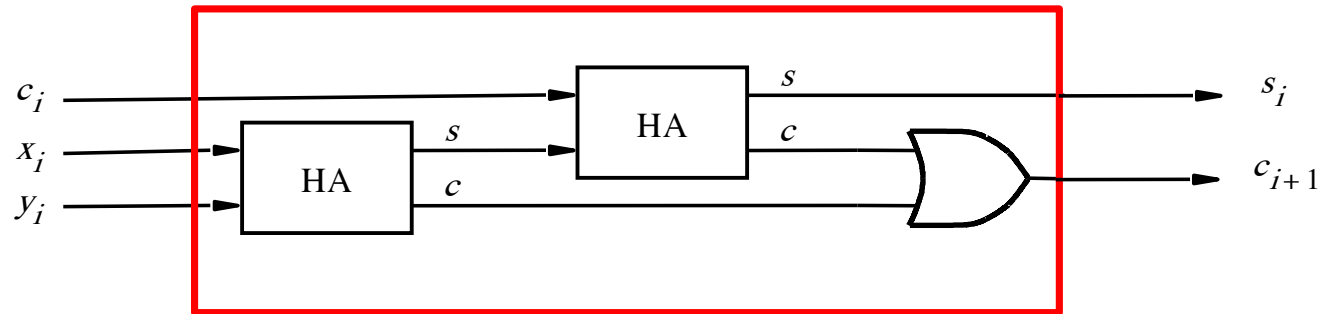


The Full-Adder Abstraction

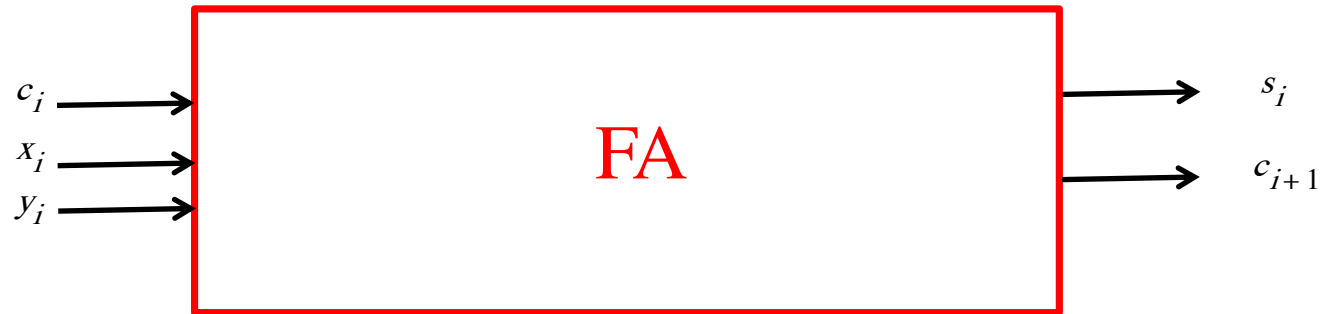

We can place the arrows anywhere

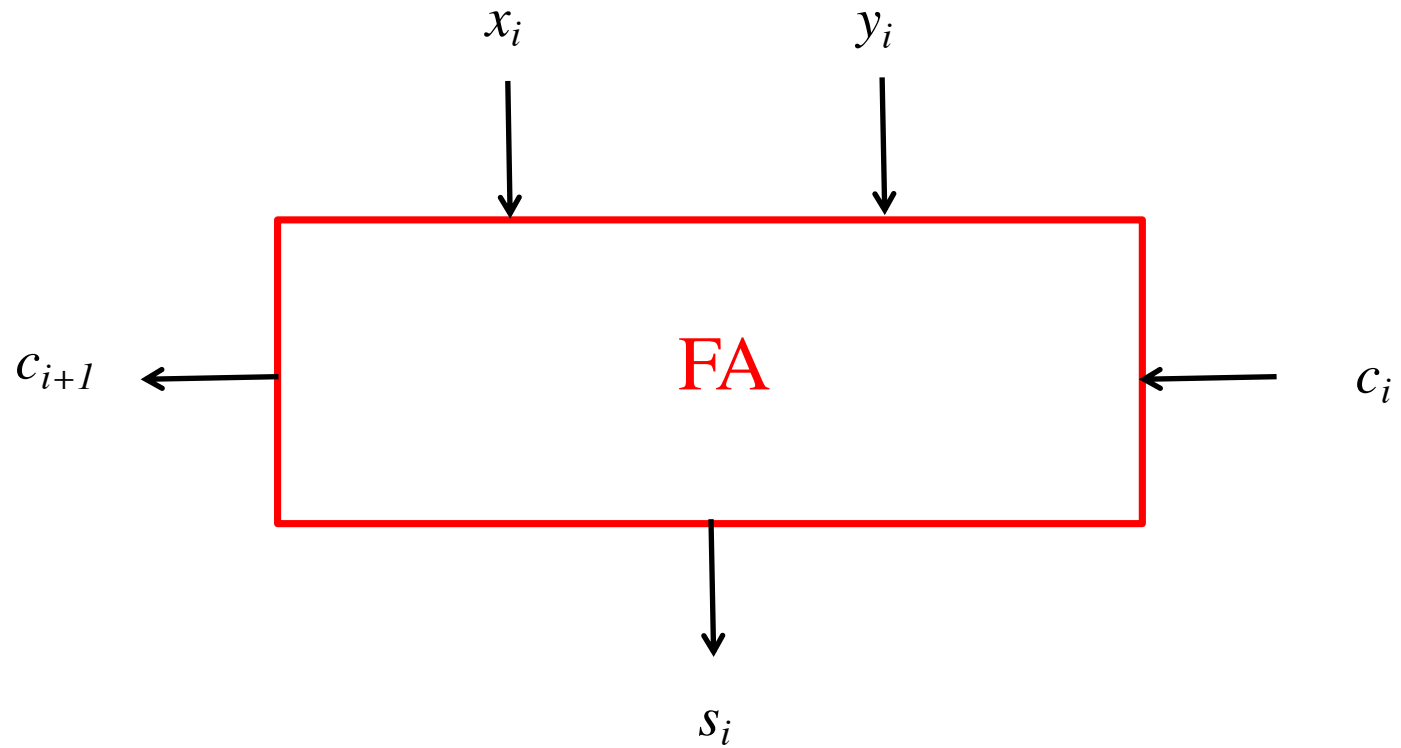


n -bit ripple-carry adder

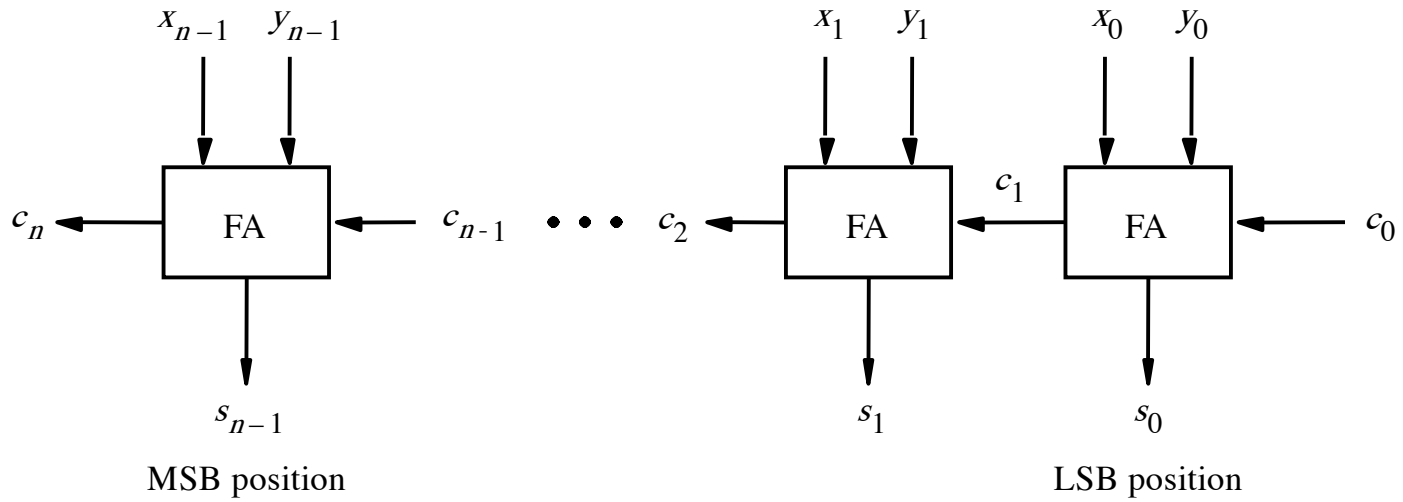


[Figure 3.5 from the textbook]


n -bit ripple-carry adder abstraction

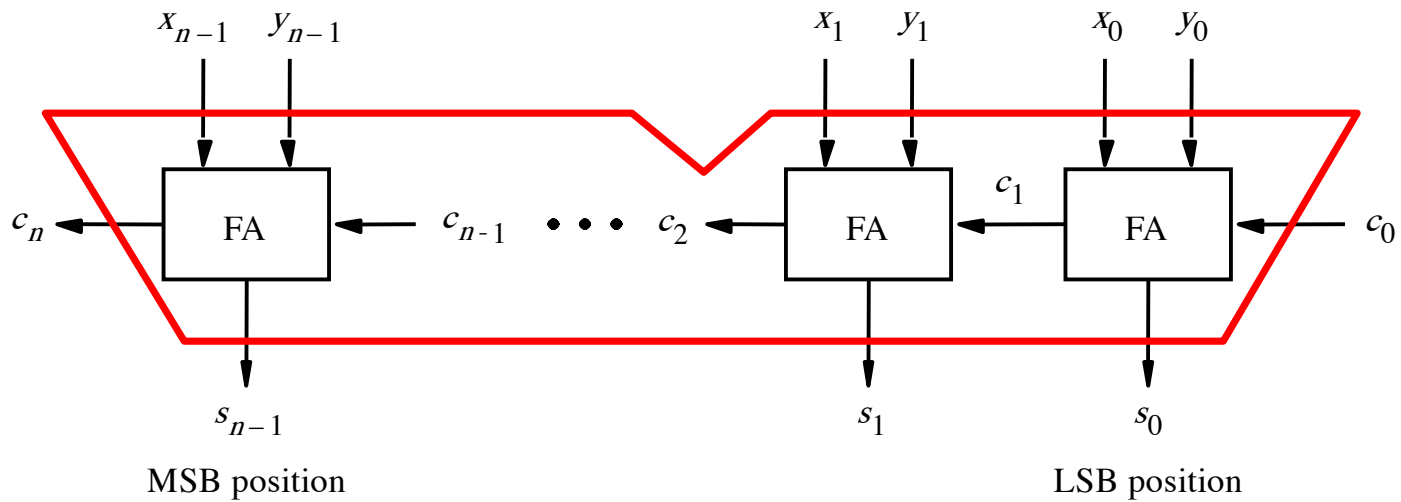


n-bit ripple-carry adder abstraction

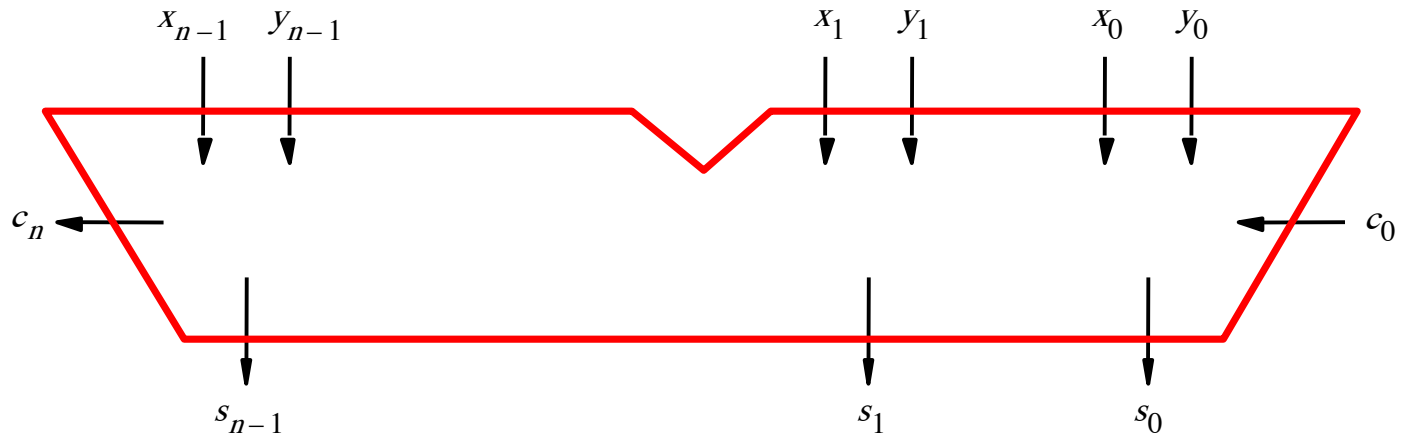

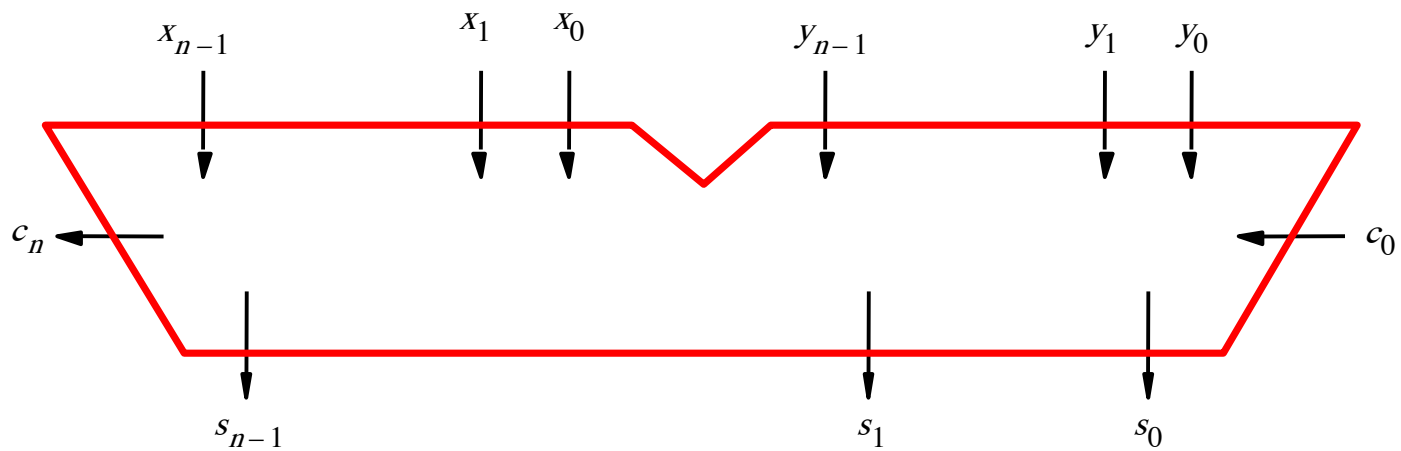
The x and y lines are typically grouped together for better visualization, but the underlying logic remains the same



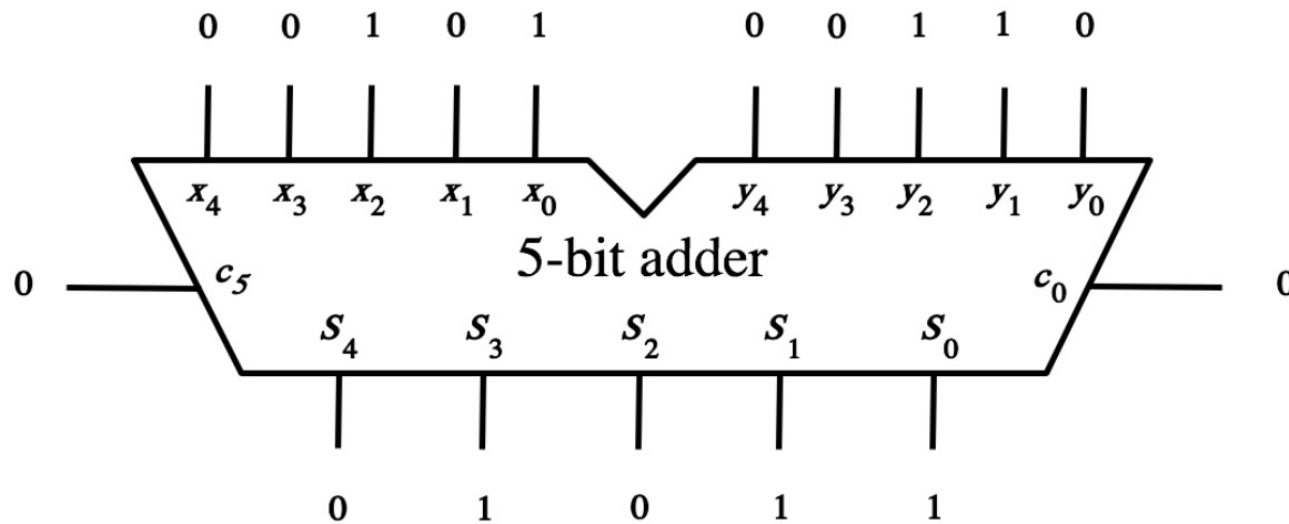Example: Computing 5+6 using a 5-bit adder



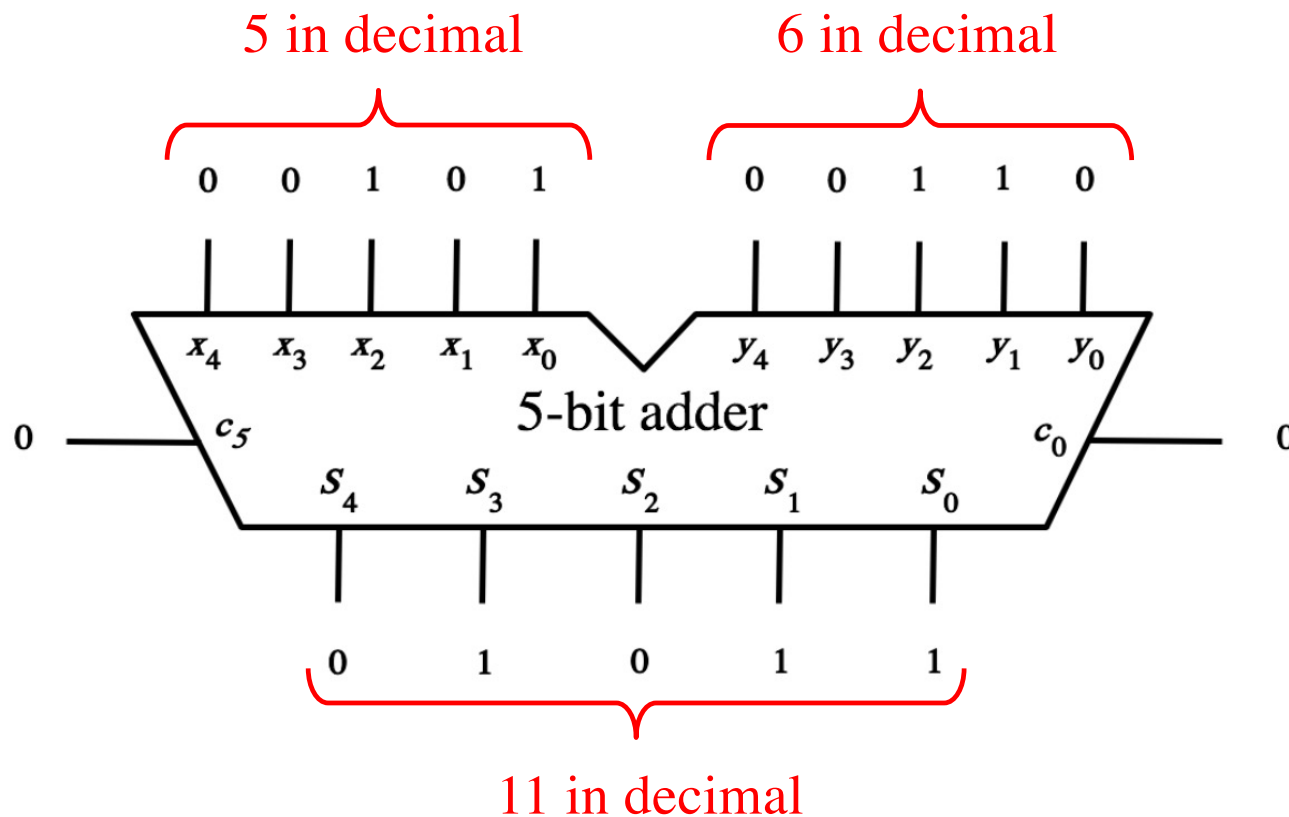Example: Computing 5+6 using a 5-bit adder




Design Example:


Create a circuit that multiplies a number by 3

How to Get 3A from A?


- $3A = A + A + A$
- $3A = (A+A) + A$
- $3A = 2A + A$

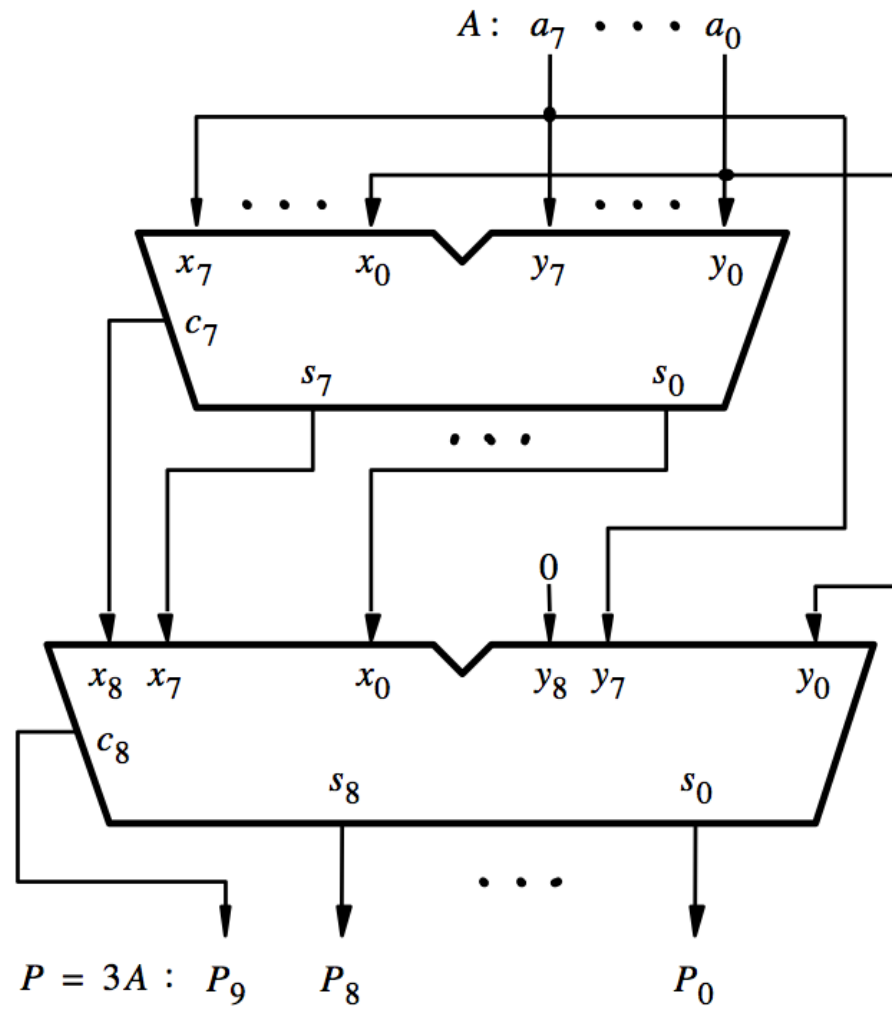


[Figure 3.6a from the textbook]

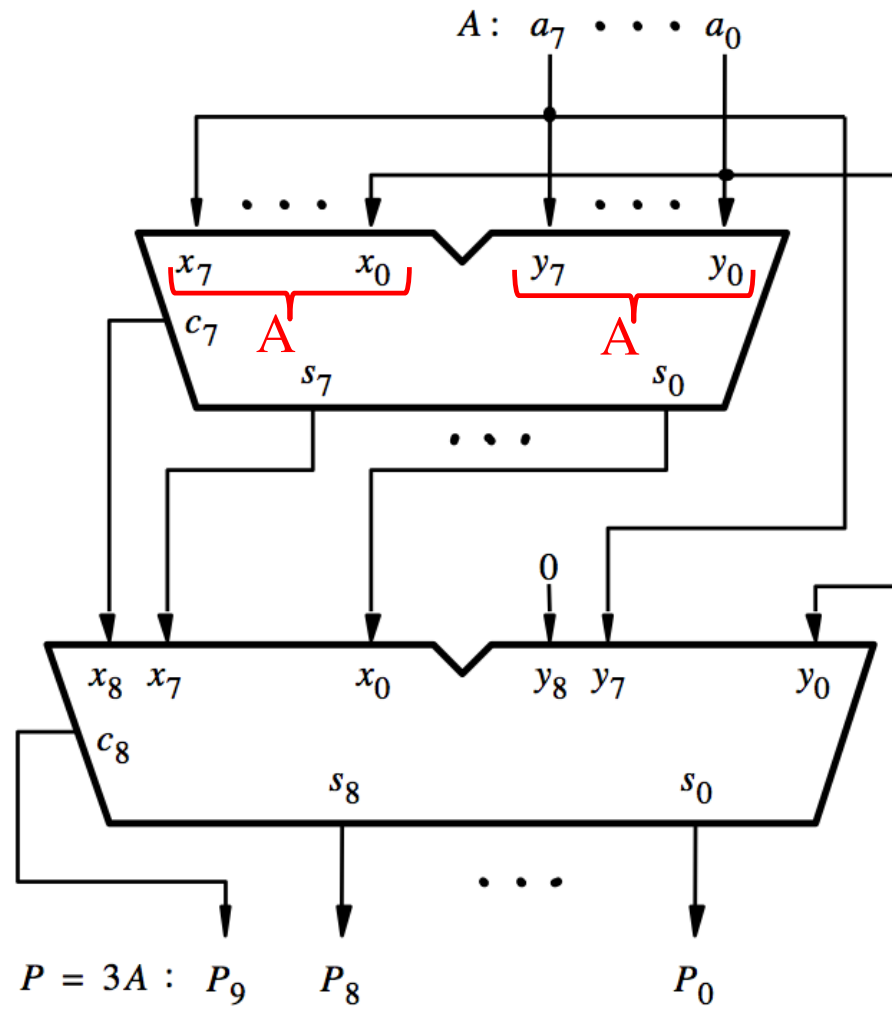


[Figure 3.6a from the textbook]

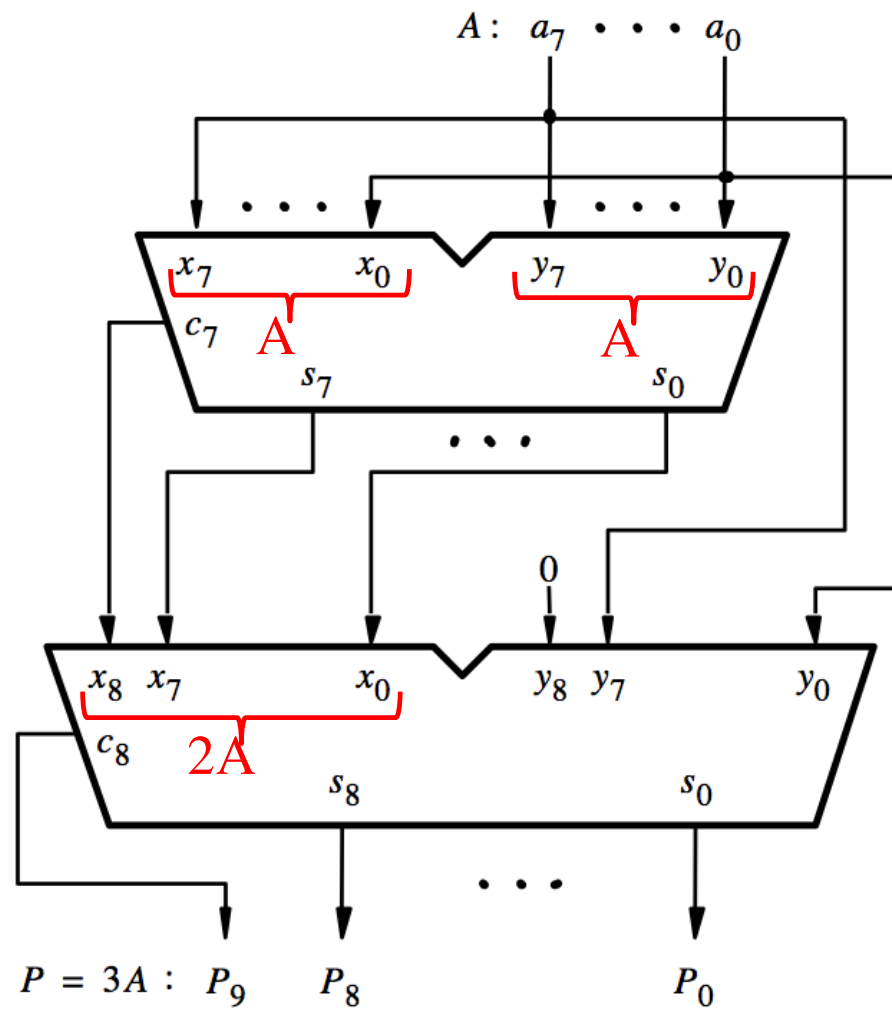

[Figure 3.6a from the textbook]

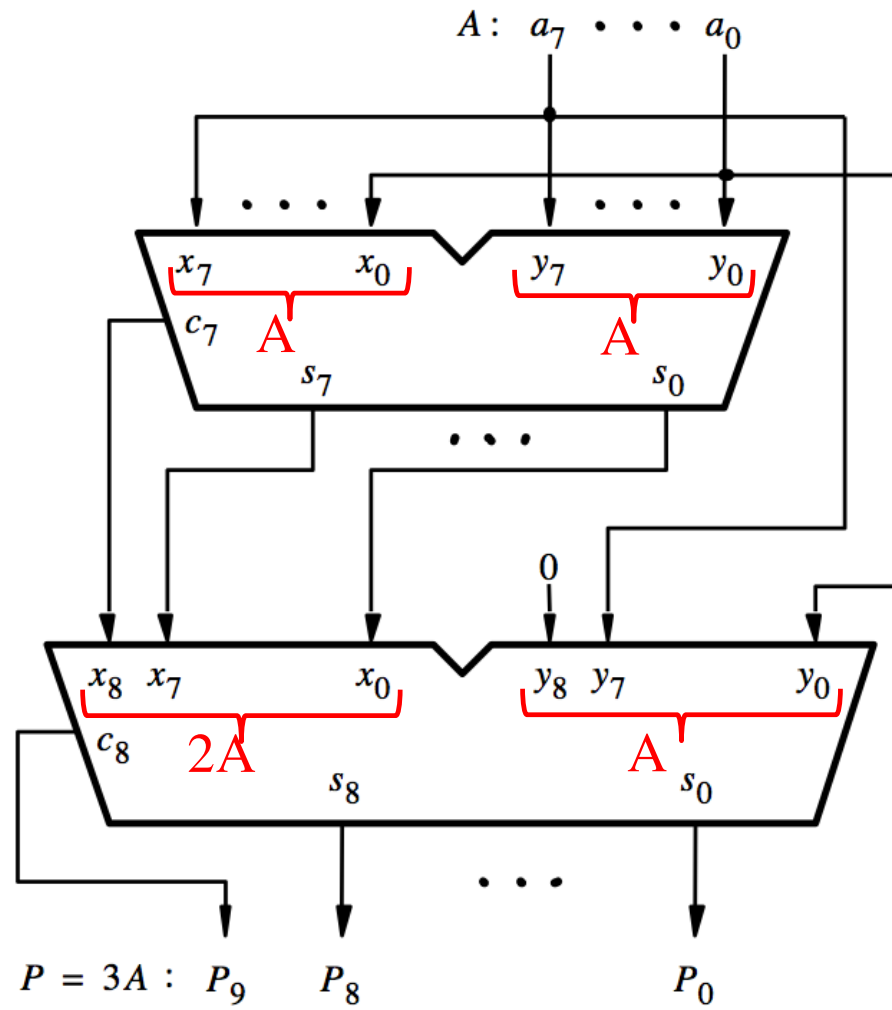

[Figure 3.6a from the textbook]

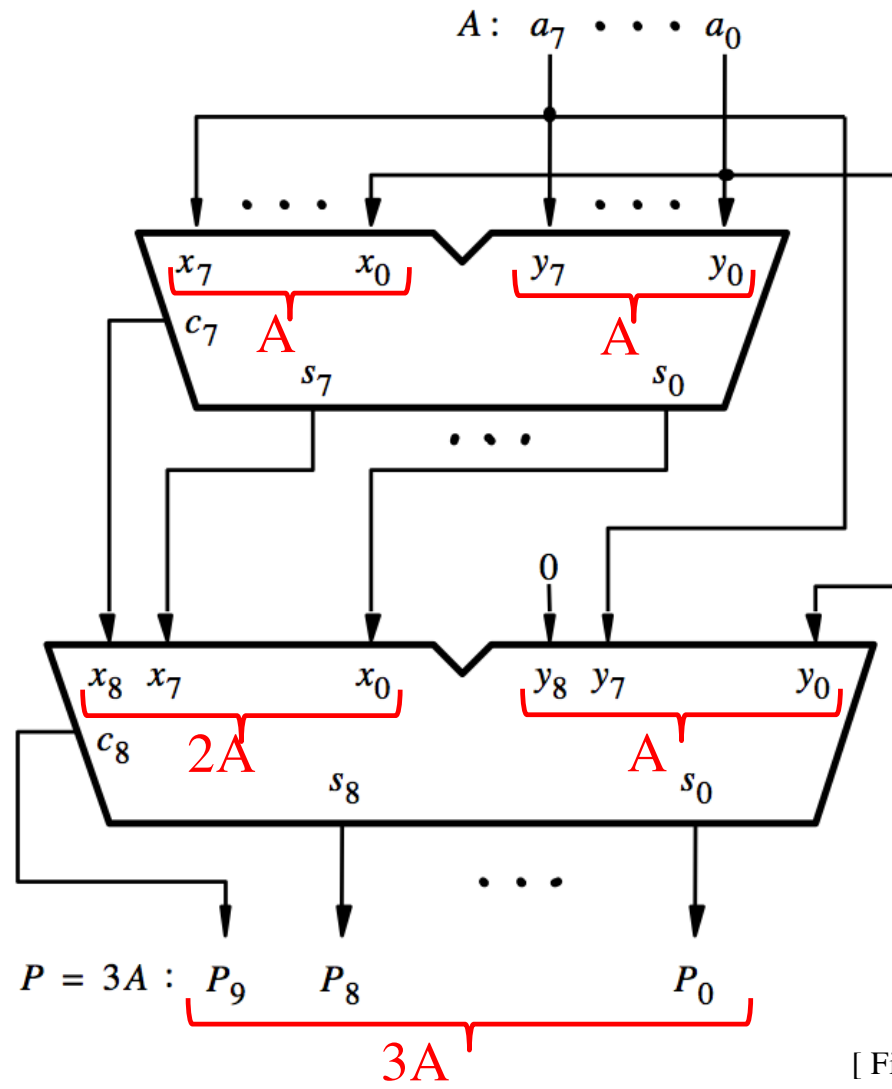

[Figure 3.6a from the textbook]

Decimal Multiplication by 10

What happens when we multiply a number by 10?

$$4 \times 10 = ?$$

$$542 \times 10 = ?$$

$$1245 \times 10 = ?$$

Decimal Multiplication by 10

What happens when we multiply a number by 10?

$$4 \times 10 = 40$$

$$542 \times 10 = 5420$$

$$1245 \times 10 = 12450$$

Decimal Multiplication by 10

What happens when we multiply a number by 10?

$$4 \times 10 = 40$$

$$542 \times 10 = 5420$$

$$1245 \times 10 = 12450$$

You simply add a zero as the rightmost number

Binary Multiplication by 2

What happens when we multiply a number by 2?

011 times 2 = ?

101 times 2 = ?

110011 times 2 = ?

Binary Multiplication by 2

What happens when we multiply a number by 2?

$$011 \text{ times } 2 = 0110$$

$$101 \text{ times } 2 = 1010$$

$$110011 \text{ times } 2 = 1100110$$

Binary Multiplication by 2


What happens when we multiply a number by 2?

$$011 \text{ times } 2 = 011\mathbf{0}$$


$$101 \text{ times } 2 = 101\mathbf{0}$$

$$110011 \text{ times } 2 = 110011\mathbf{0}$$


You simply add a zero as the rightmost number

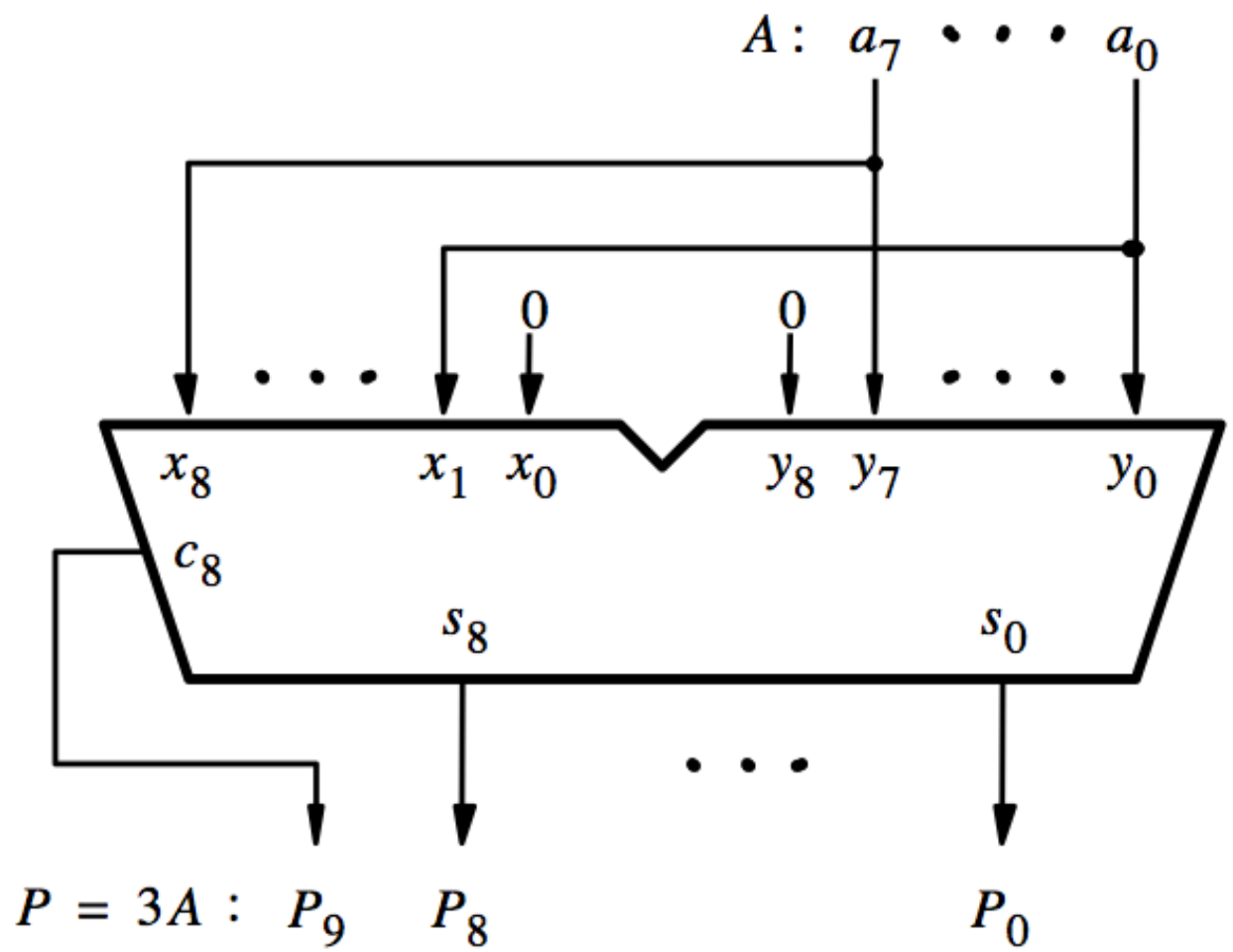

[Figure 3.6b from the textbook]

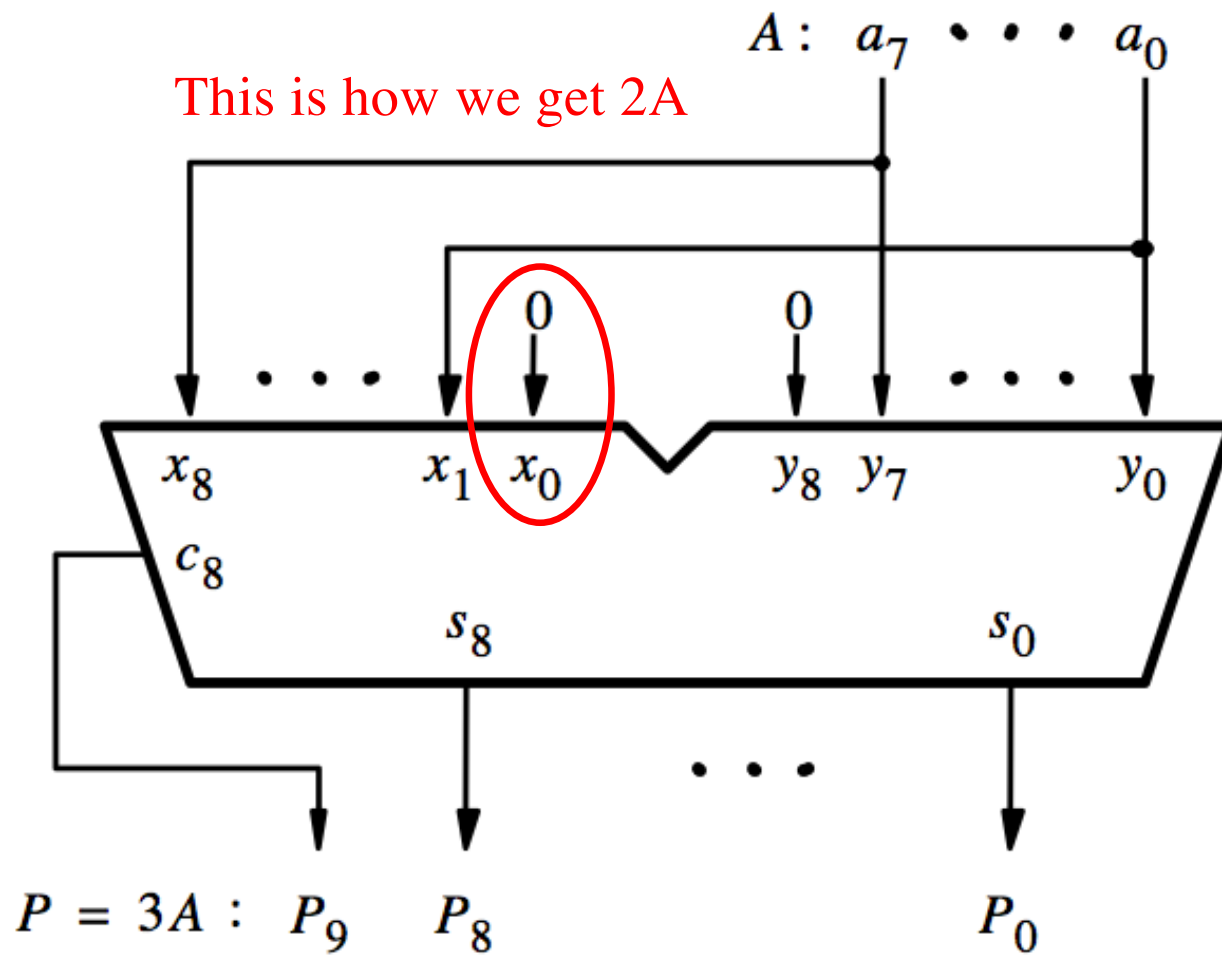

[Figure 3.6b from the textbook]

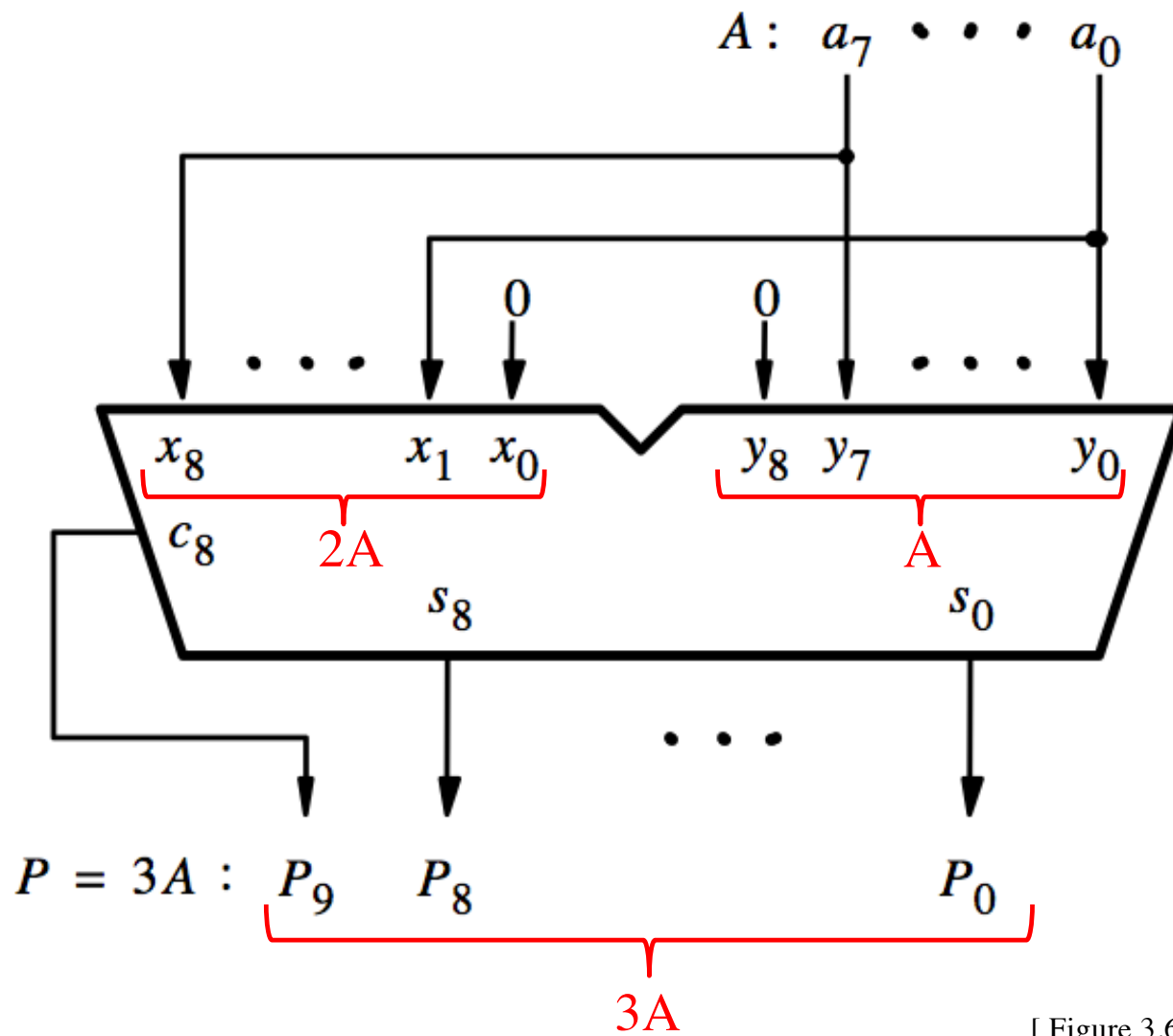

[Figure 3.6b from the textbook]

Questions?

THE END