

CprE 281: Digital Logic

Instructor: Alexander Stoytchev

<http://www.ece.iastate.edu/~alexs/classes/>

Fast Adders

*CprE 281: Digital Logic
Iowa State University, Ames, IA
Copyright © Alexander Stoytchev*

Administrative Stuff

- **No HW is due next Monday**
- **HW 6 will is due on Monday Oct. 14 @ 10 pm.**

Administrative Stuff

- Labs next week
- Mini-Project
- This is worth 3% of your grade (x2 labs)
- https://www.ece.iastate.edu/~alexs/classes/2024_Fall_2810/labs/Project-Mini/

Three Different Ways to Represent Negative Integer Numbers

- **Sign and magnitude**
- **1's complement**
- **2's complement**

Three Different Ways to Represent Negative Integer Numbers

- Sign and magnitude
- 1's complement
- 2's complement

only this method is used
in modern computers

Interpretation of four-bit signed integers

$b_3b_2b_1b_0$	Sign and magnitude	1's complement	2's complement
0111	+7	+7	+7
0110	+6	+6	+6
0101	+5	+5	+5
0100	+4	+4	+4
0011	+3	+3	+3
0010	+2	+2	+2
0001	+1	+1	+1
0000	+0	+0	+0
1000	-0	-7	-8
1001	-1	-6	-7
1010	-2	-5	-6
1011	-3	-4	-5
1100	-4	-3	-4
1101	-5	-2	-3
1110	-6	-1	-2
1111	-7	-0	-1

[Table 3.2 from the textbook]

Interpretation of four-bit signed integers

$b_3b_2b_1b_0$	Sign and magnitude	1's complement	2's complement
0111	+7	+7	+7
0110	+6	+6	+6
0101	+5	+5	+5
0100	+4	+4	+4
0011	+3	+3	+3
0010	+2	+2	+2
0001	+1	+1	+1
0000	+0	+0	+0
1000	-0	-7	-8
1001	-1	-6	-7
1010	-2	-5	-6
1011	-3	-4	-5
1100	-4	-3	-4
1101	-5	-2	-3
1110	-6	-1	-2
1111	-7	-0	-1

Note that each table includes both positive and negative integers.


[Table 3.2 from the textbook]

1's Complement


1' s complement
(subtract each digit from 1)

$$\begin{array}{r} 1 1 1 1 1 1 1 \\ - 0 0 1 0 1 1 0 0 \\ \hline 1 1 0 1 0 0 1 1 \end{array}$$

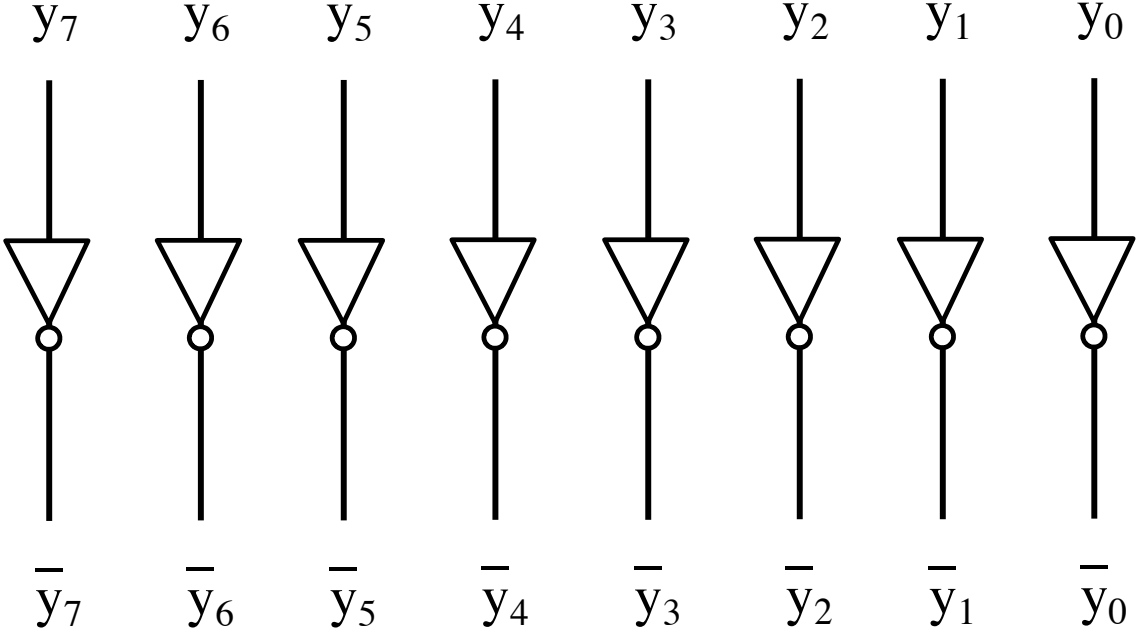Circuit for negating a number stored in 1's complement representation



 Circuit for negating a number stored in 1's complement representation




2's Complement

2's complement representation (4-bit)

$b_3b_2b_1b_0$	2's complement
0111	+7
0110	+6
0101	+5
0100	+4
0011	+3
0010	+2
0001	+1
0000	+0
1000	-8
1001	-7
1010	-6
1011	-5
1100	-4
1101	-3
1110	-2
1111	-1

The number circle for 2's complement

 

[Figure 3.11a from the textbook]

**Negate these numbers stored in
2's complement representation**

0 1 0 1

1 1 1 0

1 1 0 0

0 1 1 1

Negate these numbers stored in 2's complement representation

0 1 0 1

1 0 1 0

1 1 1 0

0 0 0 1

1 1 0 0

0 0 1 1

0 1 1 1

1 0 0 0

Invert all bits...

Negate these numbers stored in 2's complement representation

$$\begin{array}{r} 0101 \\ + 1010 \\ \hline 1011 \end{array}$$

$$\begin{array}{r} 1110 \\ + 0001 \\ \hline 0010 \end{array}$$

$$\begin{array}{r} 1100 \\ + 0011 \\ \hline 0100 \end{array}$$

$$\begin{array}{r} 0111 \\ + 1000 \\ \hline 1001 \end{array}$$

.. then add 1.

Negate these numbers stored in 2's complement representation


$$\begin{array}{r} 0101 = +5 \\ + 1010 \\ \hline 1011 = -5 \end{array}$$

$$\begin{array}{r} 1110 = -2 \\ + 0001 \\ \hline 0010 = +2 \end{array}$$


$$\begin{array}{r} 1100 = -4 \\ + 0011 \\ \hline 0100 = +4 \end{array}$$

$$\begin{array}{r} 0111 = +7 \\ + 1000 \\ \hline 1001 = -7 \end{array}$$

 Circuit #1 for negating a number stored in 2's complement representation



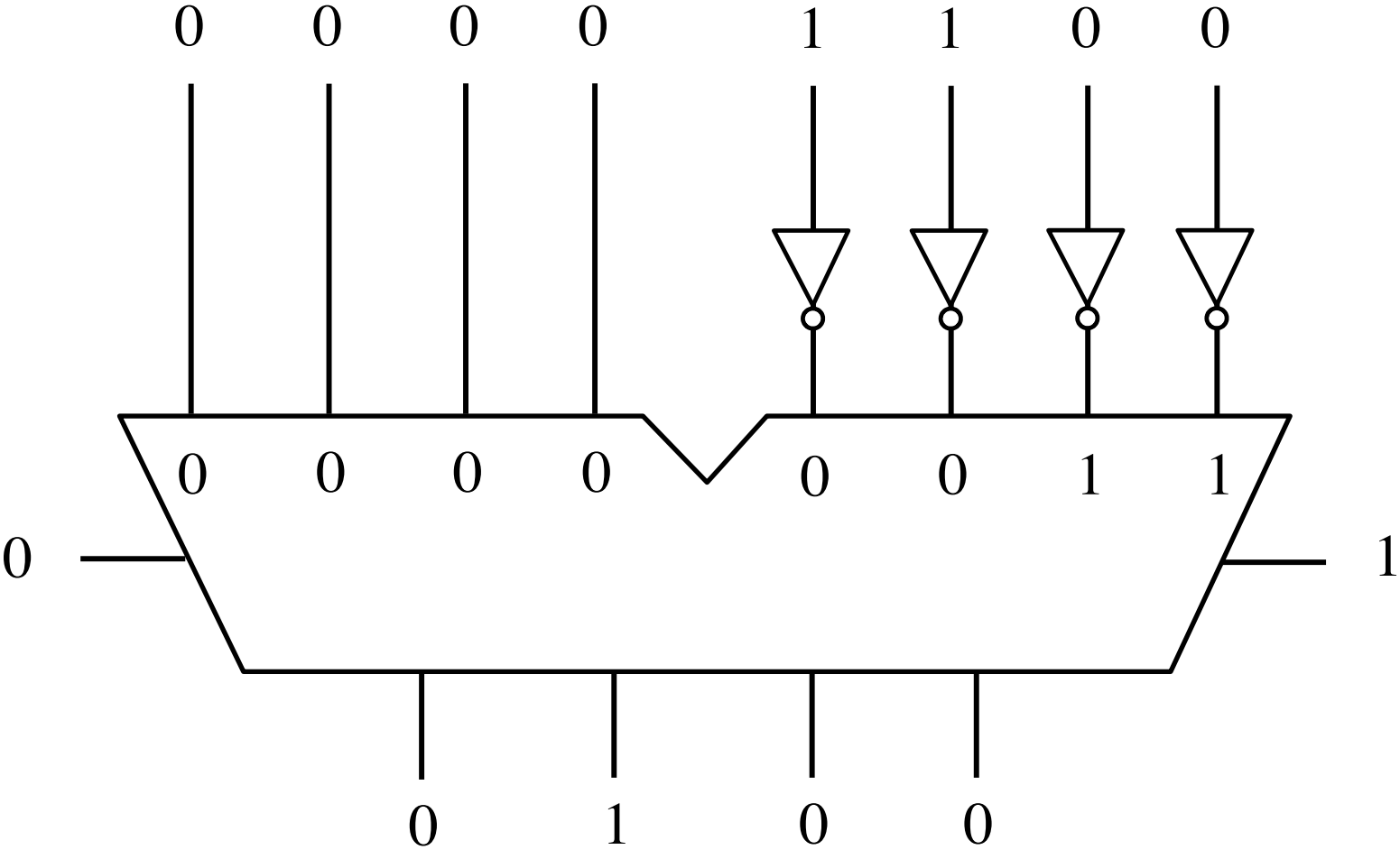Circuit #2 for negating a number stored in 2's complement representation



**Addition of two numbers stored
in 2's complement representation**

There are four cases to consider

- $(+5) + (+2)$

- $(-5) + (+2)$

- $(+5) + (-2)$

- $(-5) + (-2)$

There are four cases to consider

- $(+5) + (+2)$ **positive plus positive**
- $(-5) + (+2)$ **negative plus positive**
- $(+5) + (-2)$ **positive plus negative**
- $(-5) + (-2)$ **negative plus negative**

Positive plus positive

$$\begin{array}{r}
 (+5) \\
 + (+2) \\
 \hline
 (+7)
 \end{array}
 \qquad
 \begin{array}{r}
 0101 \\
 + 0010 \\
 \hline
 0111
 \end{array}$$

$b_3b_2b_1b_0$	2's complement
0111	+7
0110	+6
0101	+5
0100	+4
0011	+3
0010	+2
0001	+1
0000	+0
1000	-8
1001	-7
1010	-6
1011	-5
1100	-4
1101	-3
1110	-2
1111	-1

[Figure 3.9 from the textbook]

Negative plus positive


$$\begin{array}{r}
 (-5) \\
 + (+2) \\
 \hline
 (-3)
 \end{array}
 \qquad
 \begin{array}{r}
 1011 \\
 + 0010 \\
 \hline
 1101
 \end{array}$$

$b_3b_2b_1b_0$	2's complement
0111	+7
0110	+6
0101	+5
0100	+4
0011	+3
0010	+2
0001	+1
0000	+0
1000	-8
1001	-7
1010	-6
1011	-5
1100	-4
1101	-3
1110	-2
1111	-1

[Figure 3.9 from the textbook]

Positive plus negative

$$\begin{array}{r}
 (+5) \quad \quad 0101 \\
 + (-2) \quad \quad 1110 \\
 \hline
 (+3) \quad \quad 10011
 \end{array}$$



 ignore

$b_3b_2b_1b_0$	2's complement
0111	+7
0110	+6
0101	+5
0100	+4
0011	+3
0010	+2
0001	+1
0000	+0
1000	-8
1001	-7
1010	-6
1011	-5
1100	-4
1110	-2
1111	-1

[Figure 3.9 from the textbook]

Negative plus negative

$$\begin{array}{r}
 (-5) \\
 + (-2) \\
 \hline
 (-7)
 \end{array}
 \qquad
 \begin{array}{r}
 1011 \\
 + 1110 \\
 \hline
 11001
 \end{array}$$

↑
ignore

$b_3b_2b_1b_0$	2's complement
0111	+7
0110	+6
0101	+5
0100	+4
0011	+3
0010	+2
0001	+1
0000	+0
1000	-8
1001	-7
1010	-6
1011	-5
1100	-4
1101	-3
1110	-2
1111	-1

[Figure 3.9 from the textbook]

**Subtraction of two numbers stored
in 2's complement representation**

There are four cases to consider

- $(+5) - (+2)$ positive minus positive
- $(-5) - (+2)$ negative minus positive
- $(+5) - (-2)$ positive minus negative
- $(-5) - (-2)$ negative minus negative

There are four cases to consider

- $(+5) - (+2)$

- $(-5) - (+2)$

- $(+5) - (-2)$

- $(-5) - (-2)$

There are four cases to consider

- $(+5) - (+2) = (+5) + (-2)$

- $(-5) - (+2) = (-5) + (-2)$

- $(+5) - (-2) = (+5) + (+2)$

- $(-5) - (-2) = (-5) + (+2)$

There are four cases to consider

- $(+5) - (+2) = (+5) + (-2)$

- $(-5) - (+2) = (-5) + (-2)$

- $(+5) - (-2) = (+5) + (+2)$

- $(-5) - (-2) = (-5) + (+2)$

We can change subtraction into addition ...

There are four cases to consider

- $(+5) - (+2) = (+5) + (-2)$

- $(-5) - (+2) = (-5) + (-2)$

- $(+5) - (-2) = (+5) + (+2)$

- $(-5) - (-2) = (-5) + (+2)$

... if we negate the second number.

There are four cases to consider

- $(+5) - (+2) = (+5) + (-2)$

- $(-5) - (+2) = (-5) + (-2)$

- $(+5) - (-2) = (+5) + (+2)$

- $(-5) - (-2) = (-5) + (+2)$

These are the four addition cases
(arranged in a shuffled order)

Start with: Positive minus positive


$$\begin{array}{r}
 (+5) \\
 - (+2) \\
 \hline
 (+3)
 \end{array}
 \quad
 \begin{array}{r}
 \underline{0101} \\
 - \underline{0010} \\
 \hline
 \hline
 \end{array}$$

$b_3b_2b_1b_0$	2's complement
0111	+7
0110	+6
0101	+5
0100	+4
0011	+3
0010	+2
0001	+1
0000	+0
1000	-8
1001	-7
1010	-6
1011	-5
1100	-4
1101	-3
1110	-2
1111	-1

[Figure 3.10 from the textbook]

Convert to: Positive plus negative

$$\begin{array}{r}
 (+5) \\
 - (+2) \\
 \hline
 (+3)
 \end{array}
 \quad
 \begin{array}{r}
 \color{red}{0101} \\
 - \color{yellow}{0010} \\
 \hline
 \end{array}
 \quad
 \Rightarrow
 \quad
 \begin{array}{r}
 0101 \\
 + 1110 \\
 \hline
 10011
 \end{array}
 \quad
 \begin{array}{r}
 (+5) \\
 + (-2) \\
 \hline
 (+3)
 \end{array}$$




$b_3b_2b_1b_0$	2's complement
0111	+7
0110	+6
0101	+5
0100	+4
0011	+3
0010	+2
0001	+1
0000	+0
1000	-8
1001	-7
1010	-6
1011	-5
1100	-4
1101	-3
1110	-2
1111	-1

[Figure 3.10 from the textbook]

Convert to: Positive plus negative


$$\begin{array}{r}
 (+5) \\
 - (+2) \\
 \hline
 (+3)
 \end{array}
 \quad
 \begin{array}{r}
 0101 \\
 - 0010 \\
 \hline
 \end{array}
 \quad
 \Rightarrow
 \quad
 \begin{array}{r}
 0101 \\
 + 1110 \\
 \hline
 10011
 \end{array}
 \quad
 \begin{array}{r}
 (+5) \\
 + (-2) \\
 \hline
 (+3)
 \end{array}$$



$b_3b_2b_1b_0$	2's complement
0111	+7
0110	+6
0101	+5
0100	+4
0011	+3
0010	+2
0001	+1
0000	+0
1000	-8
1001	-7
1010	-6
1011	-5
1100	-4
1101	-3
1110	-2
1111	-1

[Figure 3.10 from the textbook]

 Graphical interpretation of four-bit 2's complement numbers



(a) The number circle

(b) Subtracting 2 by adding its 2's complement

[Figure 3.11 from the textbook]


Start with: Negative minus positive

$$\begin{array}{r}
 (-5) \\
 - (+2) \\
 \hline
 (-7)
 \end{array}
 \qquad
 \begin{array}{r}
 \color{red}{1011} \\
 - \color{yellow}{0010} \\
 \hline
 \end{array}$$

$b_3b_2b_1b_0$	2's complement
0111	+7
0110	+6
0101	+5
0100	+4
0011	+3
0010	+2
0001	+1
0000	+0
1000	-8
1001	-7
1010	-6
1011	-5
1100	-4
1101	-3
1110	-2
1111	-1

[Figure 3.10 from the textbook]

Convert to: Negative plus negative

 

$b_3b_2b_1b_0$	2's complement
0111	+7
0110	+6
0101	+5
0100	+4
0011	+3
0010	+2
0001	+1
0000	+0
1000	-8
1001	-7
1010	-6
1011	-5
1100	-4
1101	-3
1110	-2
1111	-1

[Figure 3.10 from the textbook]

Start with: Positive minus negative

$$\begin{array}{r}
 (+5) \quad \quad \underline{0101} \\
 - (-2) \quad \underline{1110} \\
 \hline
 (+7)
 \end{array}$$

$b_3b_2b_1b_0$	2's complement
0111	+7
0110	+6
0101	+5
0100	+4
0011	+3
0010	+2
0001	+1
0000	+0
1000	-8
1001	-7
1010	-6
1011	-5
1100	-4
1101	-3
1110	-2
1111	-1

[Figure 3.10 from the textbook]

Convert to: Positive plus positive

$$\begin{array}{r}
 (+5) \\
 - (-2) \\
 \hline
 (+7)
 \end{array}
 \quad
 \begin{array}{r}
 \color{red}{0101} \\
 - \color{yellow}{1110} \\
 \hline
 \end{array}
 \quad
 \Rightarrow
 \quad
 \begin{array}{r}
 \color{red}{0101} \\
 + \color{green}{0010} \\
 \hline
 \color{blue}{0111}
 \end{array}
 \quad
 \begin{array}{r}
 (+5) \\
 + (+2) \\
 \hline
 (+7)
 \end{array}$$

$b_3b_2b_1b_0$	2's complement
0111	+7
0110	+6
0101	+5
0100	+4
0011	+3
0010	+2
0001	+1
0000	+0
1000	-8
1001	-7
1010	-6
1011	-5
1100	-4
1101	-3
1110	-2
1111	-1

[Figure 3.10 from the textbook]

Start with: Negative minus negative

$$\begin{array}{r}
 (-5) \\
 - (-2) \\
 \hline
 (-3)
 \end{array}
 \qquad
 \begin{array}{r}
 \color{red}{1011} \\
 - \color{yellow}{1110} \\
 \hline
 \end{array}$$

$b_3b_2b_1b_0$	2's complement
0111	+7
0110	+6
0101	+5
0100	+4
0011	+3
0010	+2
0001	+1
0000	+0
1000	-8
1001	-7
1010	-6
1011	-5
1100	-4
1101	-3
1110	-2
1111	-1

[Figure 3.10 from the textbook]

Convert to: Negative plus positive

$$\begin{array}{r}
 (-5) \\
 - (-2) \\
 \hline
 (-3)
 \end{array}
 \quad
 \begin{array}{r}
 1011 \\
 - 1110 \\
 \hline
 \end{array}
 \quad
 \Rightarrow
 \quad
 \begin{array}{r}
 1011 \\
 + 0010 \\
 \hline
 1101
 \end{array}
 \quad
 \begin{array}{r}
 (-5) \\
 + (+2) \\
 \hline
 (-3)
 \end{array}$$


$b_3b_2b_1b_0$	2's complement
0111	+7
0110	+6
0101	+5
0100	+4
0011	+3
0010	+2
0001	+1
0000	+0
1000	-8
1001	-7
1010	-6
1011	-5
1100	-4
1101	-3
1110	-2
1111	-1

[Figure 3.10 from the textbook]

Take Home Message

- **Subtraction can be performed by simply negating the second number and adding it to the first, regardless of the signs of the two numbers.**
- **Thus, the same adder circuit can be used to perform both addition and subtraction !!!**


Adder/subtractor unit

 

[Figure 3.12 from the textbook]



XOR Tricks

control	y	out
0	0	0
0	1	1
1	0	1
1	1	0

  


XOR as a repeater

control	y	out
0	0	0
0	1	1




XOR as a repeater

control	y	out
0	0	0
0	1	1




XOR as an inverter

control	y	out
1	0	1
1	1	0

 


XOR as an inverter

control	y	out
1	0	1
1	1	0

 


Addition: when control = 0

 


[Figure 3.12 from the textbook]

Addition: when control = 0

 


[Figure 3.12 from the textbook]

Addition: when control = 0

 


[Figure 3.12 from the textbook]

Subtraction: when control = 1

 


[Figure 3.12 from the textbook]

Subtraction: when control = 1

 


[Figure 3.12 from the textbook]

Subtraction: when control = 1

 

[Figure 3.12 from the textbook]

Subtraction: when control = 1

 


[Figure 3.12 from the textbook]


Addition Examples:

**all inputs and outputs are given in
2's complement representation**


Addition: 5 + 6 = 11

 


Addition: **5** + **6** = **11**

 


Addition: **5** + **6** = **11**

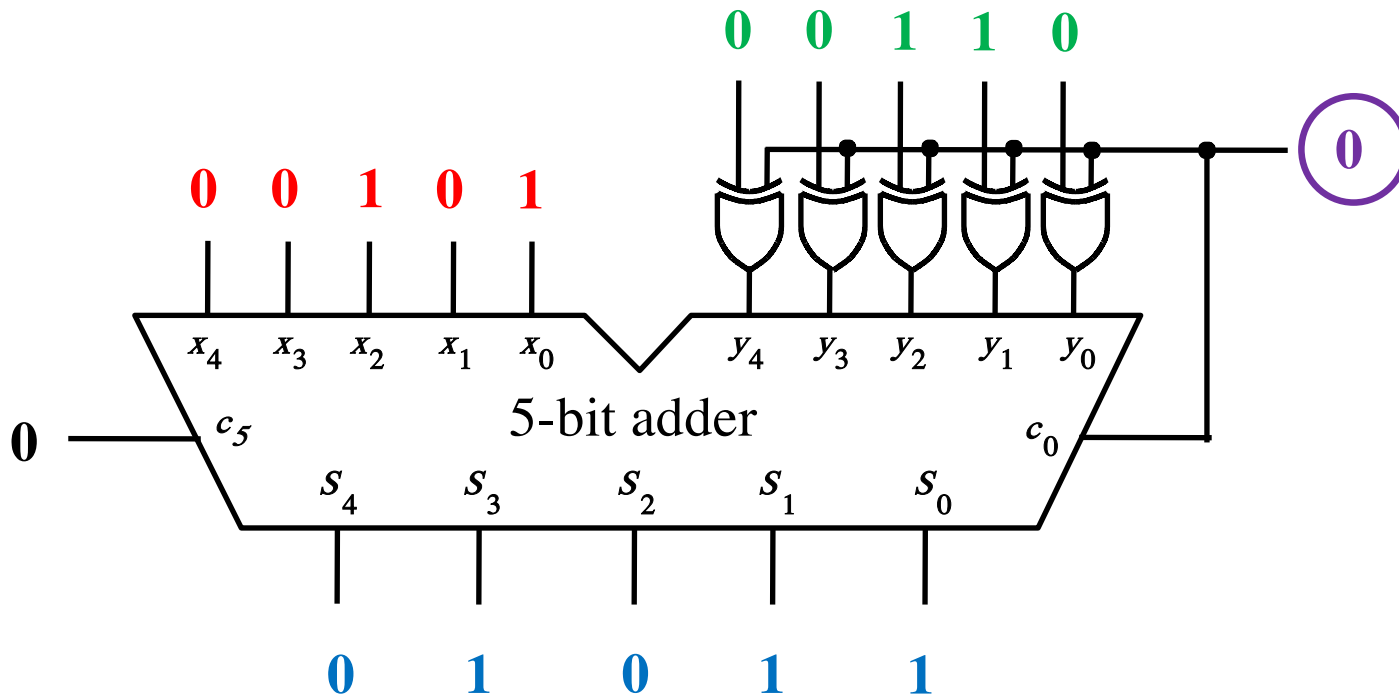

Addition: **5** + **6** = **11**

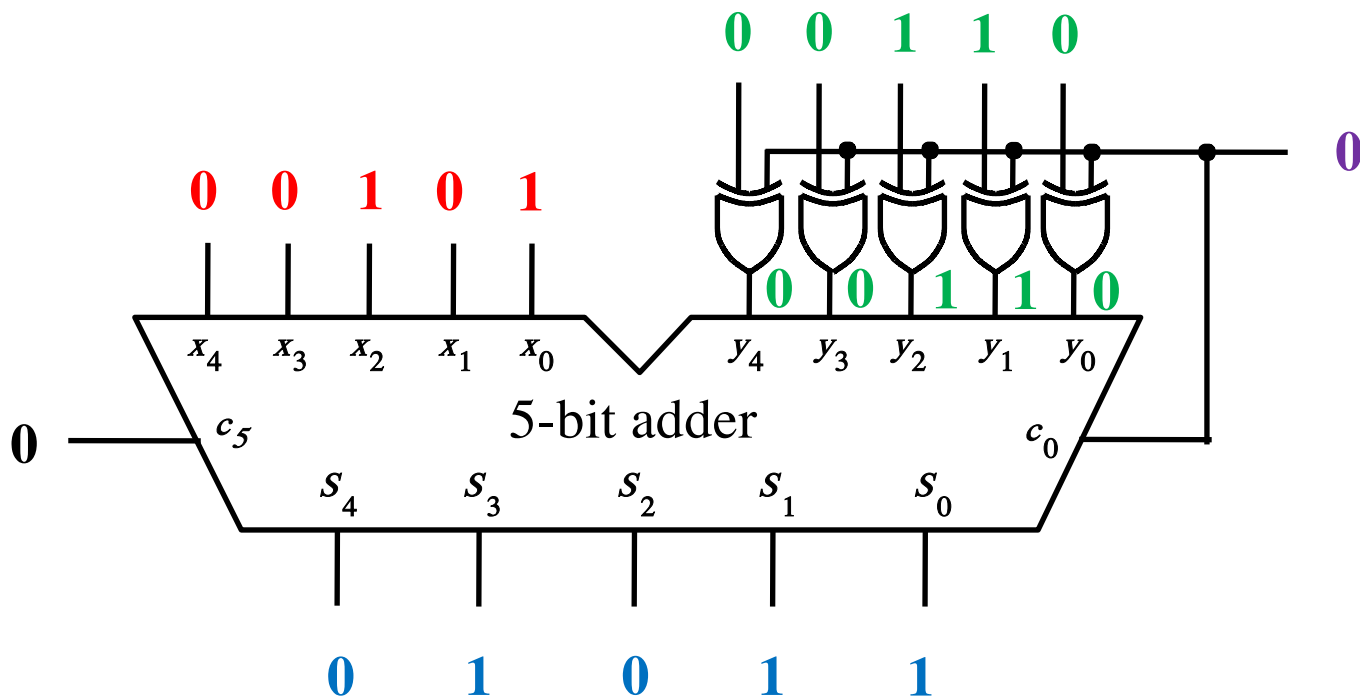


Addition: **5** + **6** = **11**

 


$$\begin{array}{r} \\ + \\ \\ \hline \end{array}$$


Addition: $4 + (-7) = -3$

 

Addition: $4 + (-7) = -3$

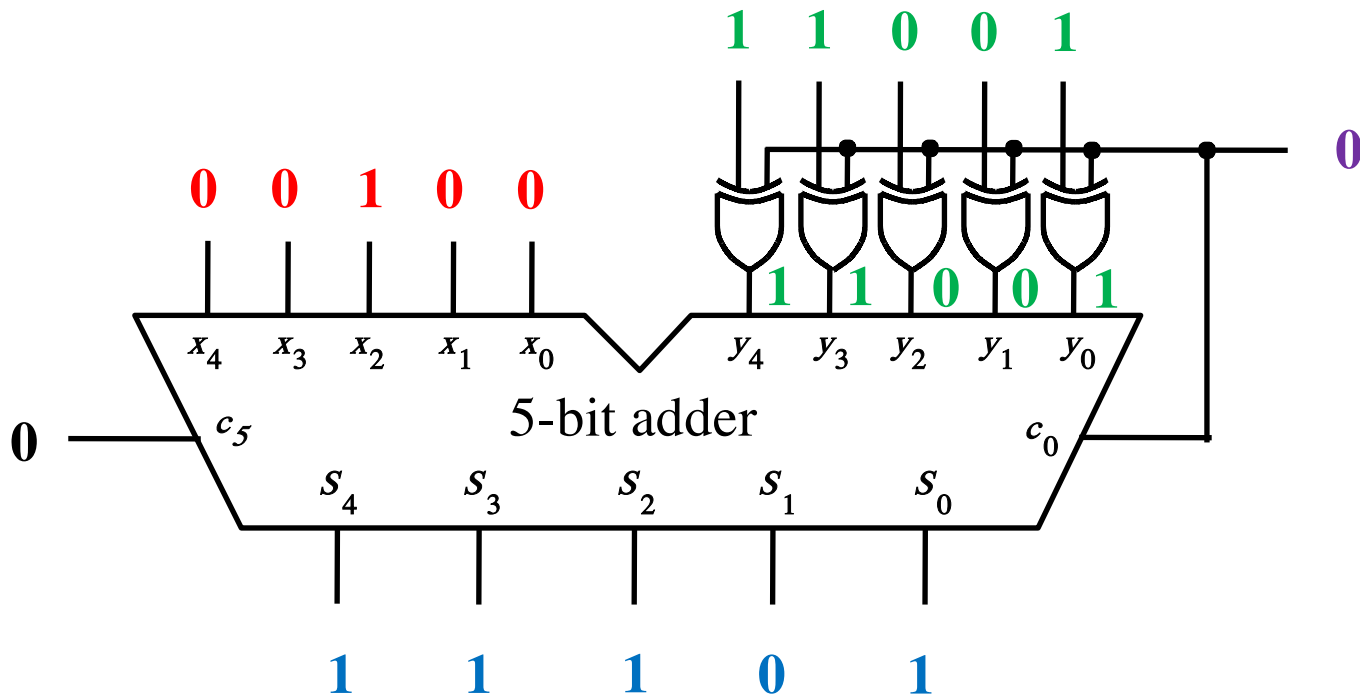


Addition: $4 + (-7) = -3$

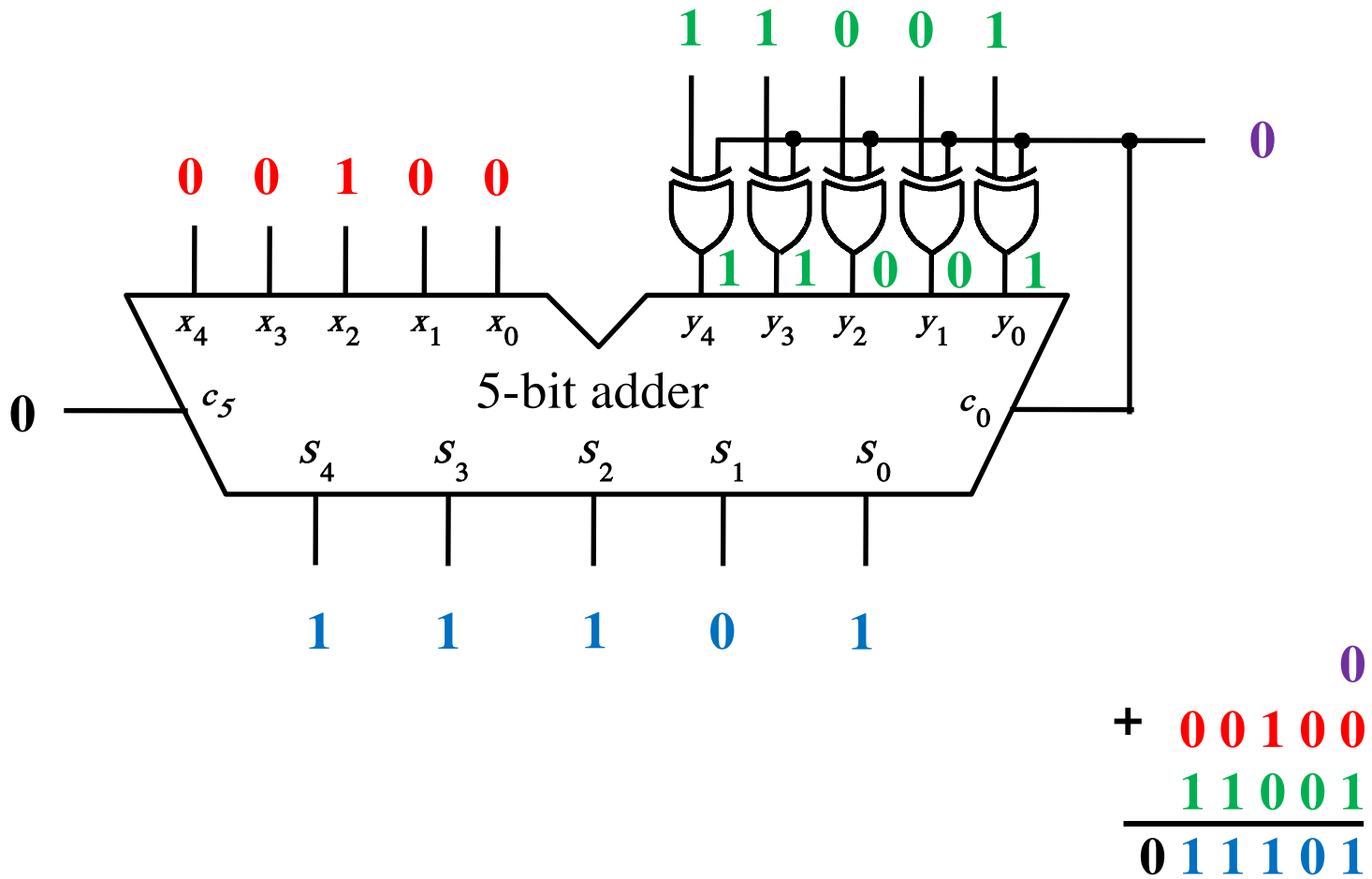


Subtraction Examples:

**all inputs and outputs are given in
2's complement representation**


Subtraction: 7 - 3 = 4

 


Subtraction: **7** - **3** = **4**

 


Subtraction: **7** - **3** = **4**

 

Subtraction: **7** - **3** = **4**

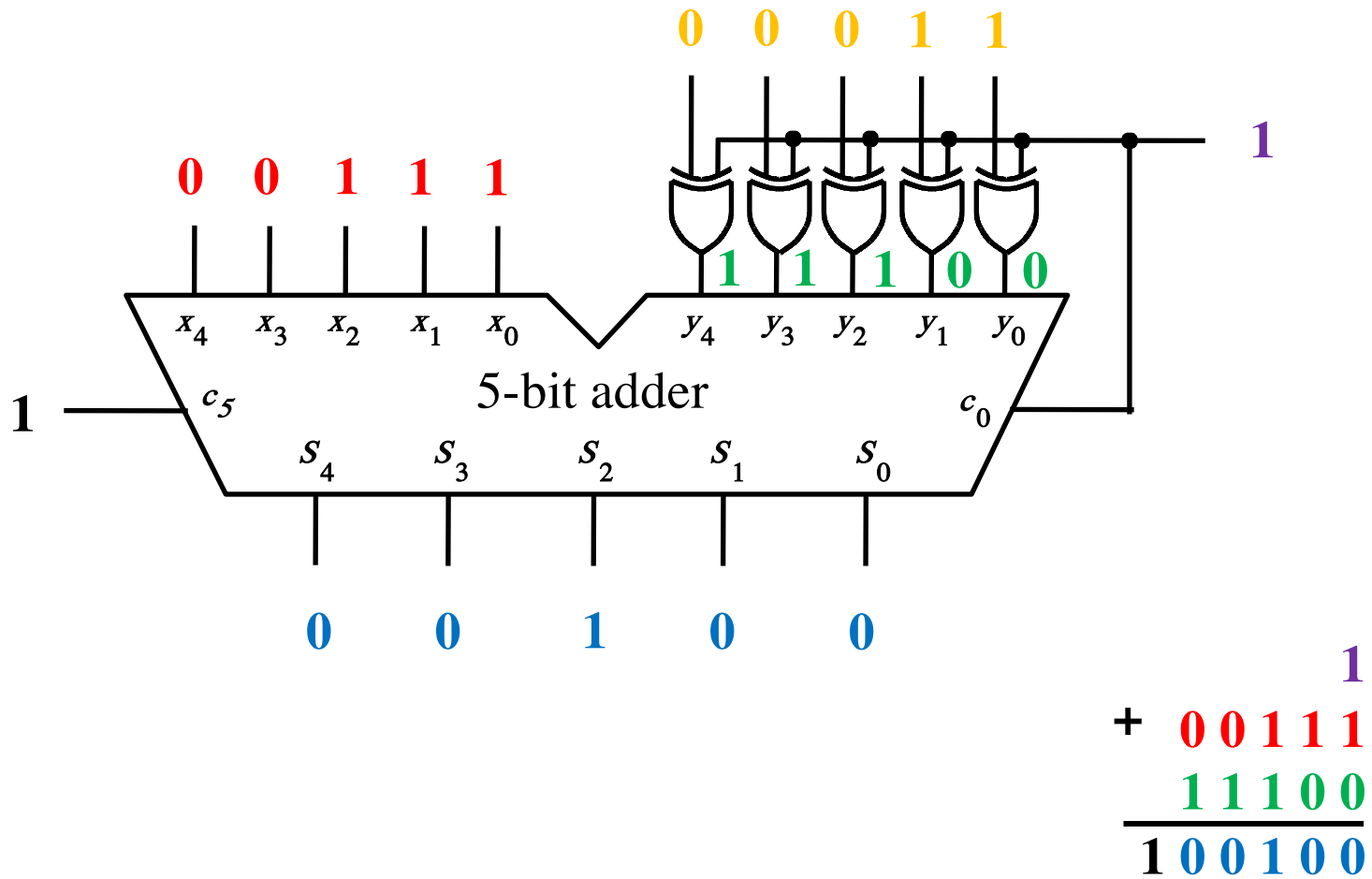

Subtraction: **7** - **3** = **4**

 


						1
					+	00111
						11100
					-----	100100
					Ignore	(1)00100


Analogy: Another Way to Do Subtraction

$$\begin{aligned} 82 - 64 &= 82 + \overset{\text{9's complement}}{(99 - 64)} + 1 - 100 \\ &= 82 + \underset{\text{10's complement}}{(35 + 1)} - 100 \\ &= 82 + 36 - 100 \quad // \text{ Add the first two.} \\ &= 118 - 100 \quad // \text{ Just delete the leading 1.} \\ &= 18 \quad // \text{ No need to subtract 100.} \end{aligned}$$


Subtraction: $(-2) - (-5) = 3$

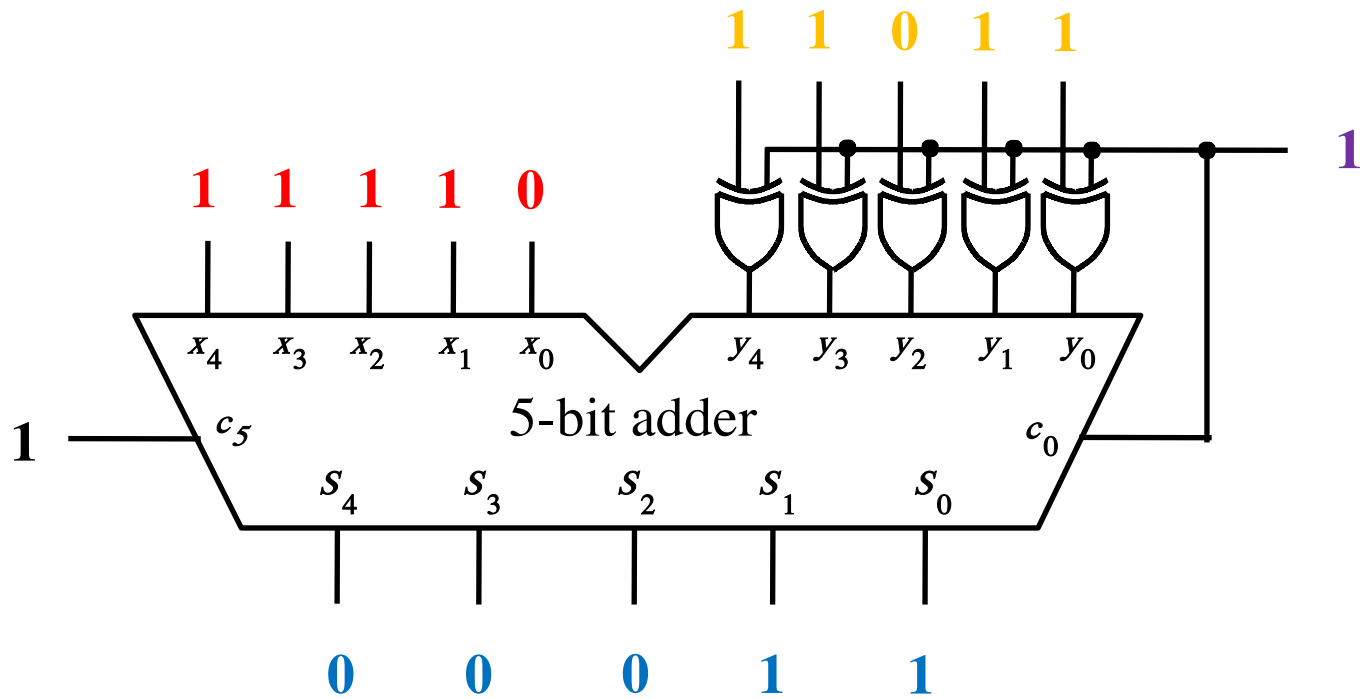


Subtraction: $(-2) - (-5) = 3$

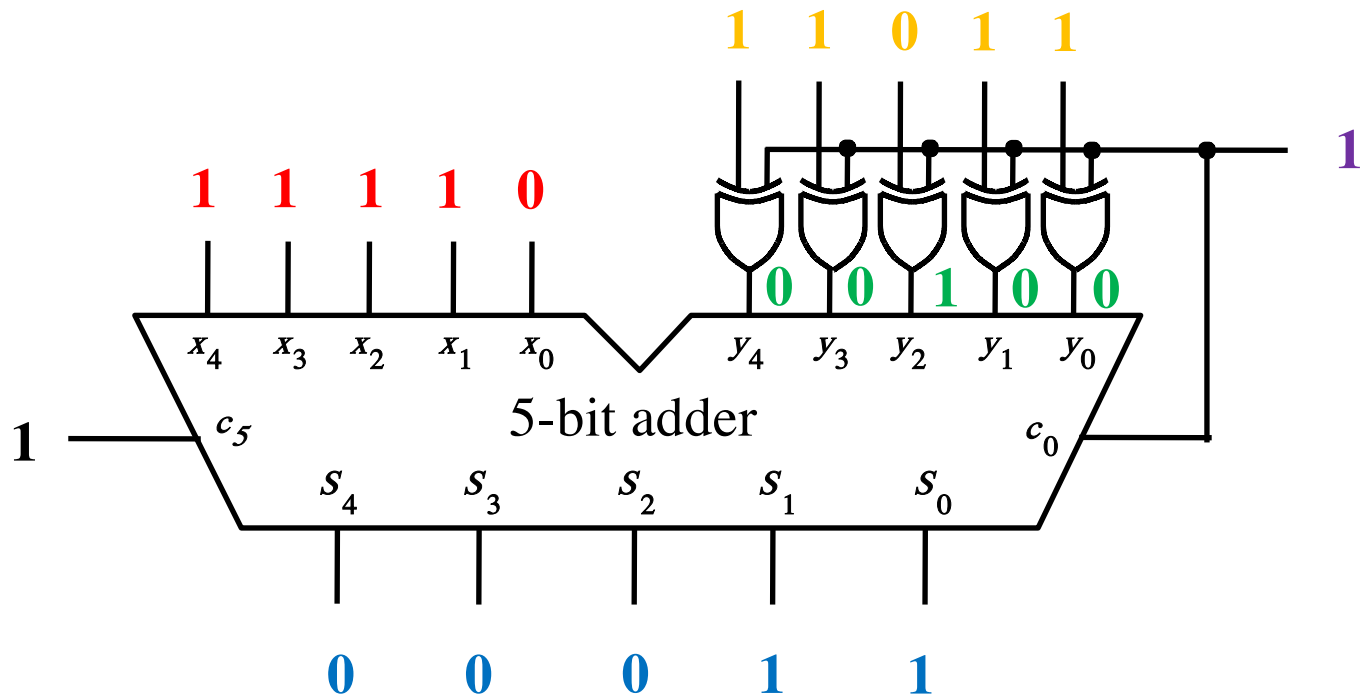

Subtraction: $(-2) - (-5) = 3$

 

Subtraction: $(-2) - (-5) = 3$

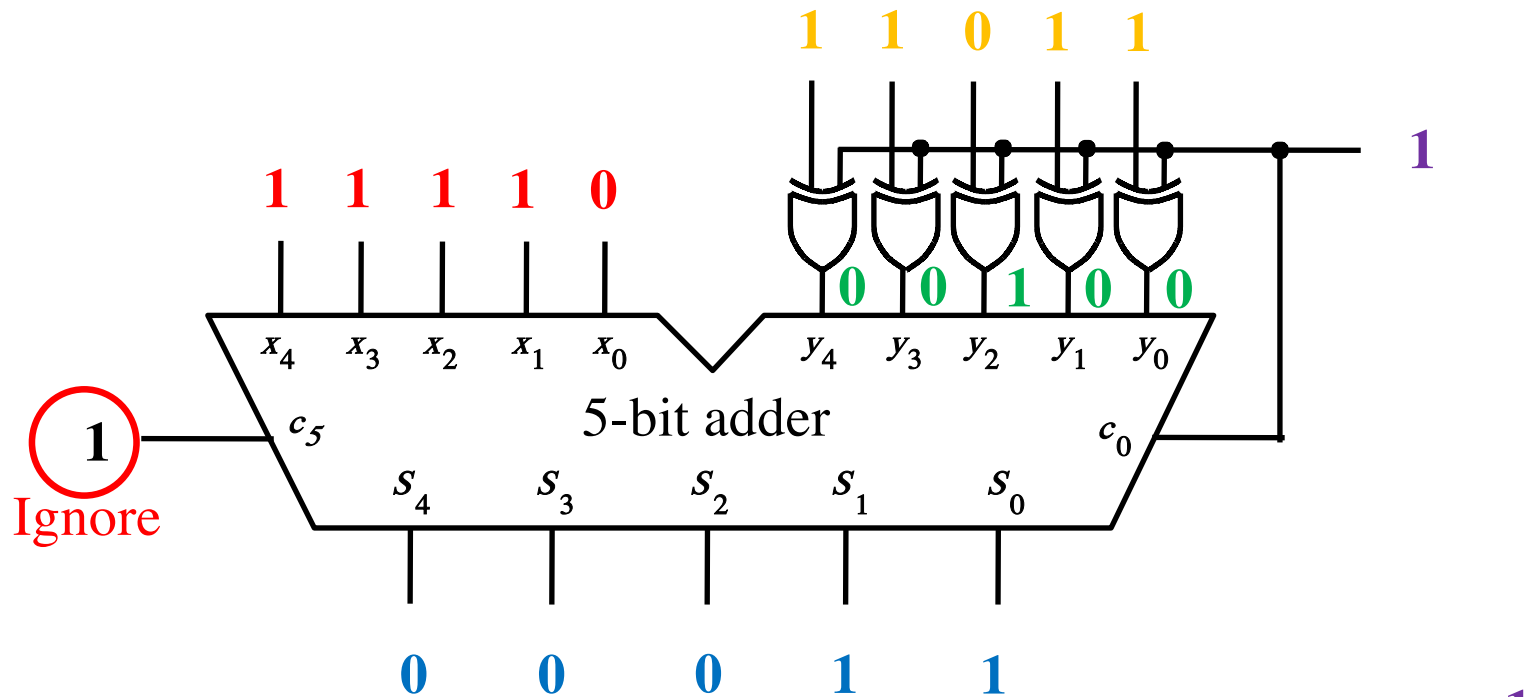

$$\begin{array}{r} \\ + \\ \\ \hline \\ \text{Ignore} \end{array}$$

Overflow Detection

Examples of determination of overflow

$$\begin{array}{r}
 (+7) \\
 + (+2) \\
 \hline
 (+9)
 \end{array}
 \quad + \quad
 \begin{array}{r}
 0111 \\
 0010 \\
 \hline
 1001
 \end{array}
 \qquad
 \begin{array}{r}
 (-7) \\
 + (+2) \\
 \hline
 (-5)
 \end{array}
 \quad + \quad
 \begin{array}{r}
 1001 \\
 0010 \\
 \hline
 1011
 \end{array}$$

$$\begin{array}{r}
 (+7) \\
 + (-2) \\
 \hline
 (+5)
 \end{array}
 \quad + \quad
 \begin{array}{r}
 0111 \\
 1110 \\
 \hline
 10101
 \end{array}
 \qquad
 \begin{array}{r}
 (-7) \\
 + (-2) \\
 \hline
 (-9)
 \end{array}
 \quad + \quad
 \begin{array}{r}
 1001 \\
 1110 \\
 \hline
 10111
 \end{array}$$

[Figure 3.13 from the textbook]

Examples of determination of overflow

(+ 7)	+	0 1 1 1	+	(- 7)	+	1 0 0 1
+ (+ 2)		0 0 1 0		+ (+ 2)		0 0 1 0
		1 0 0 1				1 0 1 1
(+ 9)				(- 5)		

(+ 7)	+	0 1 1 1	+	(- 7)	+	1 0 0 1
+ (- 2)		1 1 1 0		+ (- 2)		1 1 1 0
		1 0 1 0 1				1 0 1 1 1
(+ 5)				(- 9)		

In 2's complement, both +9 and -9 are not representable with 4 bits.

[Figure 3.13 from the textbook]

Examples of determination of overflow

$$\begin{array}{r}
 (+7) \quad 01100 \\
 + (+2) \quad 0111 \\
 \hline
 (+9) \quad 10010
 \end{array}$$

$$\begin{array}{r}
 (-7) \quad 00000 \\
 + (+2) \quad 1001 \\
 \hline
 (-5) \quad 1011
 \end{array}$$

$$\begin{array}{r}
 (+7) \quad 11100 \\
 + (-2) \quad 0111 \\
 \hline
 (+5) \quad 10101
 \end{array}$$

$$\begin{array}{r}
 (-7) \quad 10000 \\
 + (-2) \quad 1001 \\
 \hline
 (-9) \quad 10111
 \end{array}$$

Include the carry bits: $c_4 c_3 c_2 c_1 c_0$

Examples of determination of overflow

$$\begin{array}{r}
 (+7) \quad \boxed{01}100 \\
 + (+2) \quad 0111 \\
 \hline
 (+9) \quad 1001
 \end{array}$$

$$\begin{array}{r}
 (-7) \quad \boxed{00}000 \\
 + (+2) \quad 1001 \\
 \hline
 (-5) \quad 1011
 \end{array}$$

$$\begin{array}{r}
 (+7) \quad \boxed{11}100 \\
 + (-2) \quad 0111 \\
 \hline
 (+5) \quad 10101
 \end{array}$$

$$\begin{array}{r}
 (-7) \quad \boxed{10}000 \\
 + (-2) \quad 1001 \\
 \hline
 (-9) \quad 10111
 \end{array}$$

Include the carry bits: $\boxed{c_4 c_3} c_2 c_1 c_0$

Examples of determination of overflow

$$c_4 = 0$$

$$c_3 = 1$$

$$\begin{array}{r}
 (+7) \\
 + (+2) \\
 \hline
 (+9)
 \end{array}
 \quad + \quad
 \begin{array}{r}
 \boxed{01}100 \\
 0111 \\
 \hline
 0010 \\
 \hline
 1001
 \end{array}$$

$$\begin{array}{r}
 (-7) \\
 + (+2) \\
 \hline
 (-5)
 \end{array}
 \quad + \quad
 \begin{array}{r}
 \boxed{00}000 \\
 1001 \\
 \hline
 0010 \\
 \hline
 1011
 \end{array}
 \quad
 \begin{array}{l}
 c_4 = 0 \\
 c_3 = 0
 \end{array}$$

$$c_4 = 1$$

$$c_3 = 1$$

$$\begin{array}{r}
 (+7) \\
 + (-2) \\
 \hline
 (+5)
 \end{array}
 \quad + \quad
 \begin{array}{r}
 \boxed{11}100 \\
 0111 \\
 \hline
 1110 \\
 \hline
 10101
 \end{array}$$

$$\begin{array}{r}
 (-7) \\
 + (-2) \\
 \hline
 (-9)
 \end{array}
 \quad + \quad
 \begin{array}{r}
 \boxed{10}000 \\
 1001 \\
 \hline
 1110 \\
 \hline
 10111
 \end{array}
 \quad
 \begin{array}{l}
 c_4 = 1 \\
 c_3 = 0
 \end{array}$$

Include the carry bits: $\boxed{c_4 c_3} c_2 c_1 c_0$

Examples of determination of overflow

$$\begin{matrix} c_4 = 0 \\ c_3 = 1 \end{matrix}$$

$$\begin{array}{r} (+7) \\ + (+2) \\ \hline (+9) \end{array} \quad + \quad \begin{array}{r} \boxed{01}100 \\ 0111 \\ \hline 0010 \\ \hline 1001 \end{array}$$

$$\begin{array}{r} (-7) \\ + (+2) \\ \hline (-5) \end{array} \quad + \quad \begin{array}{r} \boxed{00}000 \\ 1001 \\ \hline 0010 \\ \hline 1011 \end{array}$$

$$\begin{matrix} c_4 = 0 \\ c_3 = 0 \end{matrix}$$

$$\begin{matrix} c_4 = 1 \\ c_3 = 1 \end{matrix}$$

$$\begin{array}{r} (+7) \\ + (-2) \\ \hline (+5) \end{array} \quad + \quad \begin{array}{r} \boxed{11}100 \\ 0111 \\ \hline 1110 \\ \hline 10101 \end{array}$$

$$\begin{array}{r} (-7) \\ + (-2) \\ \hline (-9) \end{array} \quad + \quad \begin{array}{r} \boxed{10}000 \\ 1001 \\ \hline 1110 \\ \hline 10111 \end{array}$$

$$\begin{matrix} c_4 = 1 \\ c_3 = 0 \end{matrix}$$

Overflow occurs only in these two cases.

Examples of determination of overflow

$$\begin{matrix} c_4 = 0 \\ c_3 = 1 \end{matrix}$$

$$\begin{array}{r} (+7) \\ + (+2) \\ \hline (+9) \end{array} \quad + \quad \begin{array}{r} \boxed{01}100 \\ 0111 \\ \hline 0010 \\ \hline 1001 \end{array}$$

$$\begin{array}{r} (-7) \\ + (+2) \\ \hline (-5) \end{array} \quad + \quad \begin{array}{r} \boxed{00}000 \\ 1001 \\ \hline 0010 \\ \hline 1011 \end{array}$$

$$\begin{matrix} c_4 = 0 \\ c_3 = 0 \end{matrix}$$

$$\begin{matrix} c_4 = 1 \\ c_3 = 1 \end{matrix}$$

$$\begin{array}{r} (+7) \\ + (-2) \\ \hline (+5) \end{array} \quad + \quad \begin{array}{r} \boxed{11}100 \\ 0111 \\ \hline 1110 \\ \hline 10101 \end{array}$$

$$\begin{array}{r} (-7) \\ + (-2) \\ \hline (-9) \end{array} \quad + \quad \begin{array}{r} \boxed{10}000 \\ 1001 \\ \hline 1110 \\ \hline 10111 \end{array}$$

$$\begin{matrix} c_4 = 1 \\ c_3 = 0 \end{matrix}$$

$$\text{Overflow} = c_3 \bar{c}_4 + \bar{c}_3 c_4$$

Examples of determination of overflow

$$\begin{matrix} c_4 = 0 \\ c_3 = 1 \end{matrix}$$

$$\begin{array}{r} (+7) \\ + (+2) \\ \hline (+9) \end{array} \quad + \quad \begin{array}{r} \boxed{01}100 \\ 0111 \\ \hline 0010 \\ \hline 1001 \end{array}$$

$$\begin{array}{r} (-7) \\ + (+2) \\ \hline (-5) \end{array} \quad + \quad \begin{array}{r} \boxed{00}000 \\ 1001 \\ \hline 0010 \\ \hline 1011 \end{array}$$

$$\begin{matrix} c_4 = 0 \\ c_3 = 0 \end{matrix}$$

$$\begin{matrix} c_4 = 1 \\ c_3 = 1 \end{matrix}$$

$$\begin{array}{r} (+7) \\ + (-2) \\ \hline (+5) \end{array} \quad + \quad \begin{array}{r} \boxed{11}100 \\ 0111 \\ \hline 1110 \\ \hline 10101 \end{array}$$

$$\begin{array}{r} (-7) \\ + (-2) \\ \hline (-9) \end{array} \quad + \quad \begin{array}{r} \boxed{10}000 \\ 1001 \\ \hline 1110 \\ \hline 10111 \end{array}$$

$$\begin{matrix} c_4 = 1 \\ c_3 = 0 \end{matrix}$$

$$\text{Overflow} = \underbrace{c_3 \bar{c}_4 + \bar{c}_3 c_4}_{\text{XOR}}$$


Calculating overflow for 4-bit numbers with only three significant bits

$$\begin{aligned}\text{Overflow} &= c_3 \bar{c}_4 + \bar{c}_3 c_4 \\ &= c_3 \oplus c_4\end{aligned}$$


Calculating overflow for n-bit numbers with only n-1 significant bits

$$\text{Overflow} = c_{n-1} \oplus c_n$$

Detecting Overflow

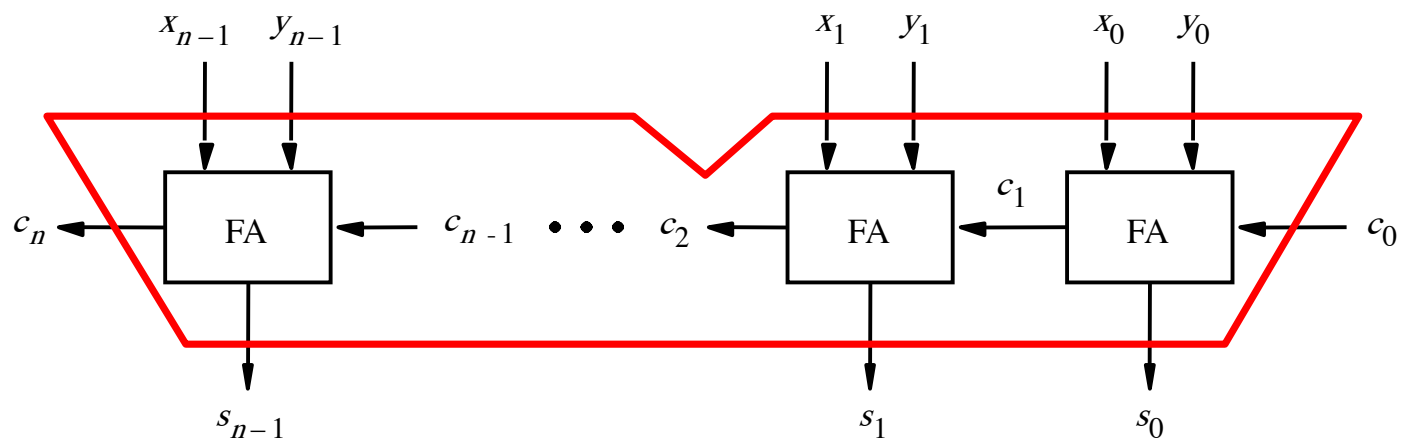

Detecting Overflow (with one extra XOR)

 


Detecting Overflow

(alternative method)


Used if you don't have access to the internal carries of the adder.

Detecting Overflow (with one extra XOR)

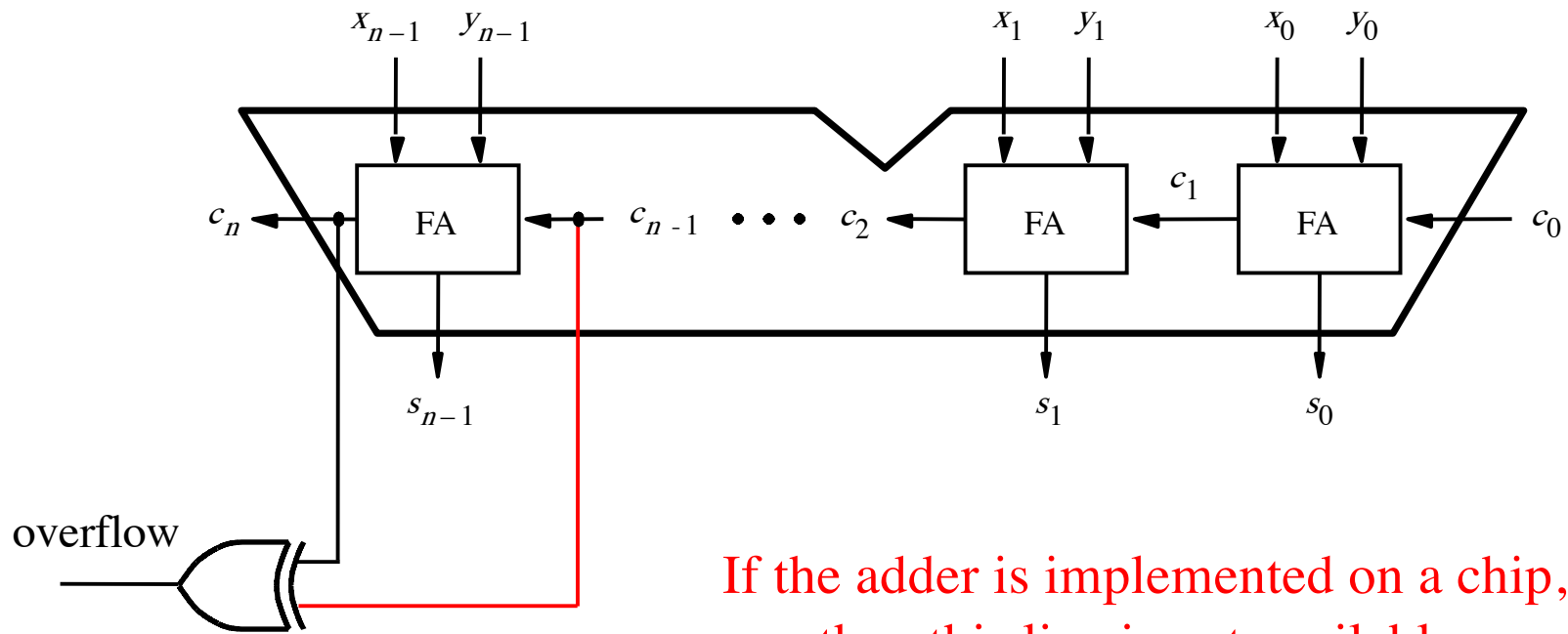


If the adder is implemented on a chip,
then this line is not available.
So the first method can't be used.

Overflow Detection: 4-bits

 


Overflow Detection: 5-bits

 


A ripple-carry adder

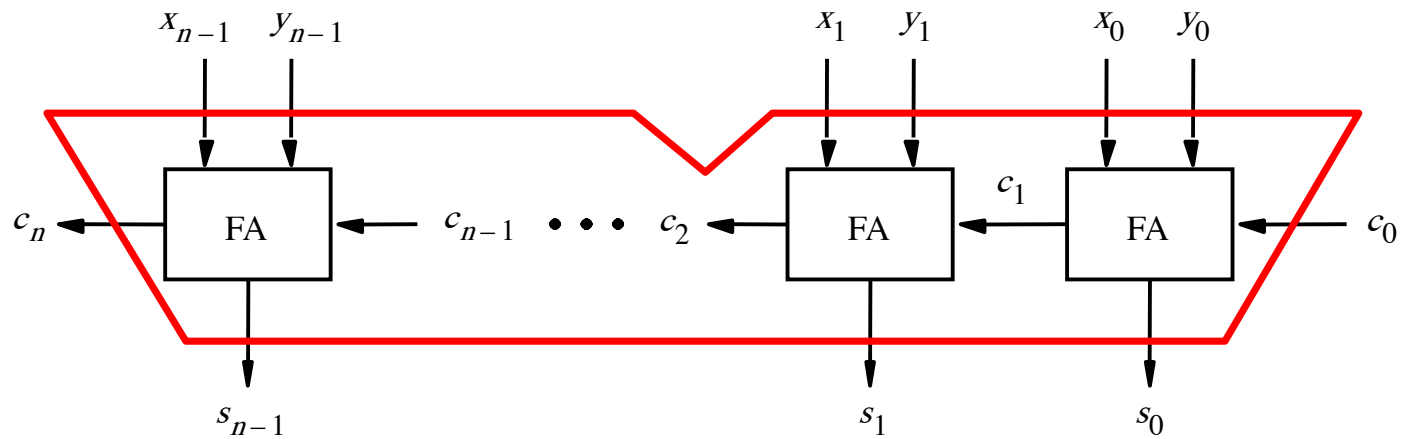
How long does it take to compute all sum bits and all carry bits?



 Delays through the modular implementation of the full-adder circuit




(a) Block diagram

 

 
(b) Detailed diagram

[Figure 3.4 from the textbook]

Delays through the modular implementation of the full-adder circuit




(a) Block diagram

 

 
(b) Detailed diagram

[Figure 3.4 from the textbook]

Delays through the modular implementation of the full-adder circuit




(a) Block diagram

 

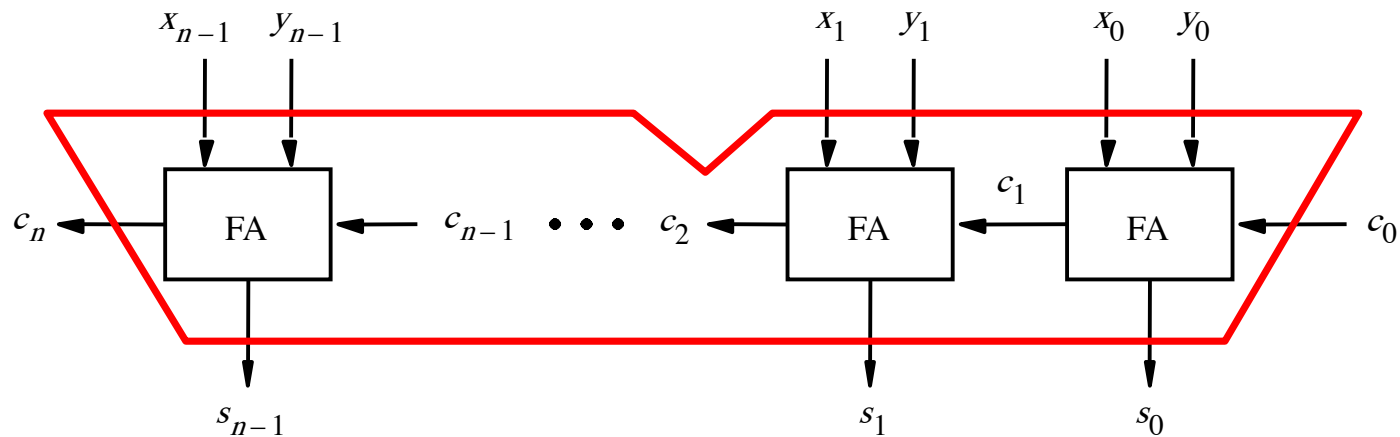(b) Detailed diagram


[Figure 3.4 from the textbook]

How long does it take to compute all sum bits and all carry bits in this case?




It takes $3n$ gate delays?

Delays through the Full-Adder circuit

 


[Figure 3.3c from the textbook]

Delays through the Full-Adder circuit

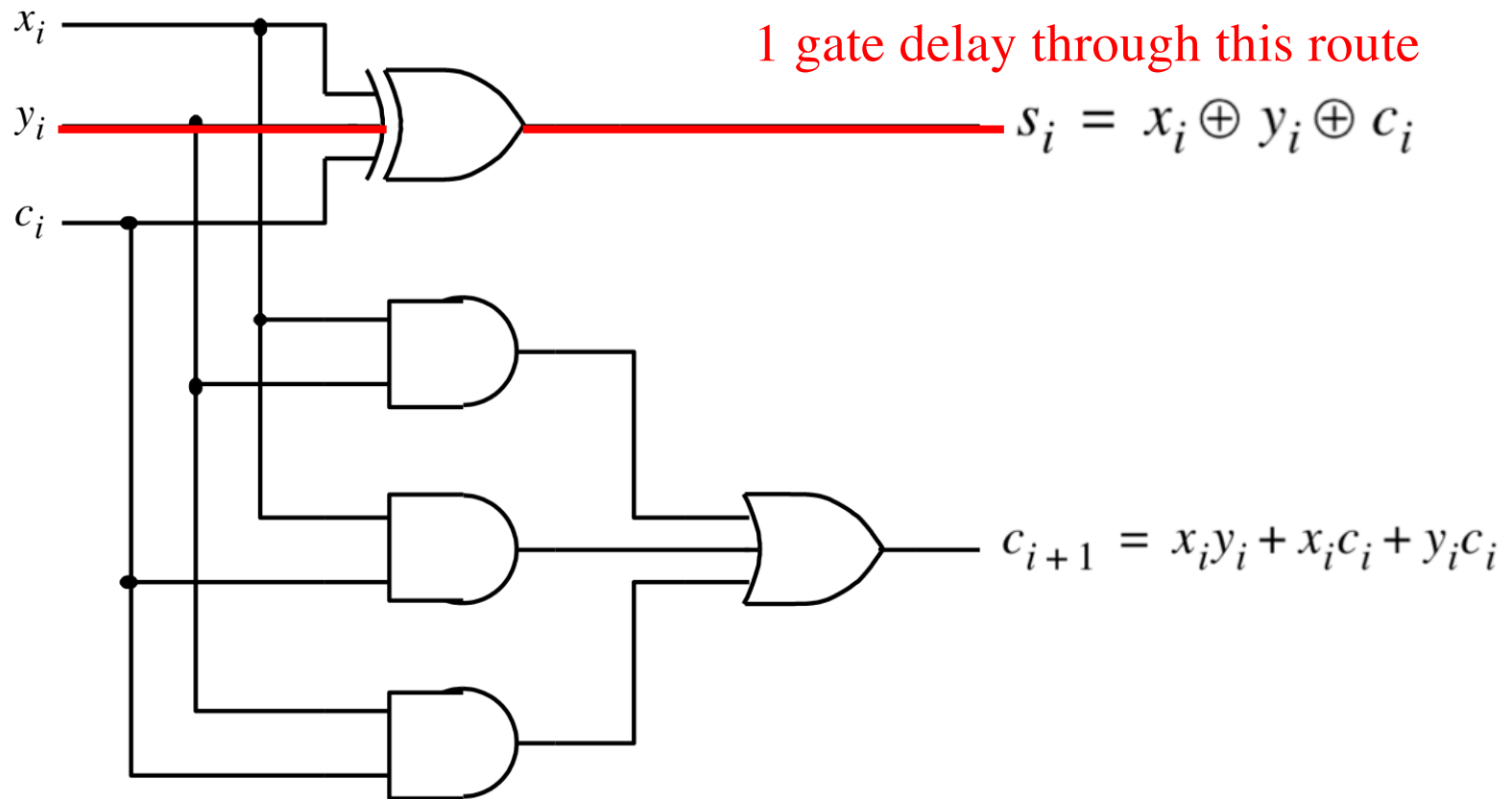


[Figure 3.3c from the textbook]

Delays through the Full-Adder circuit

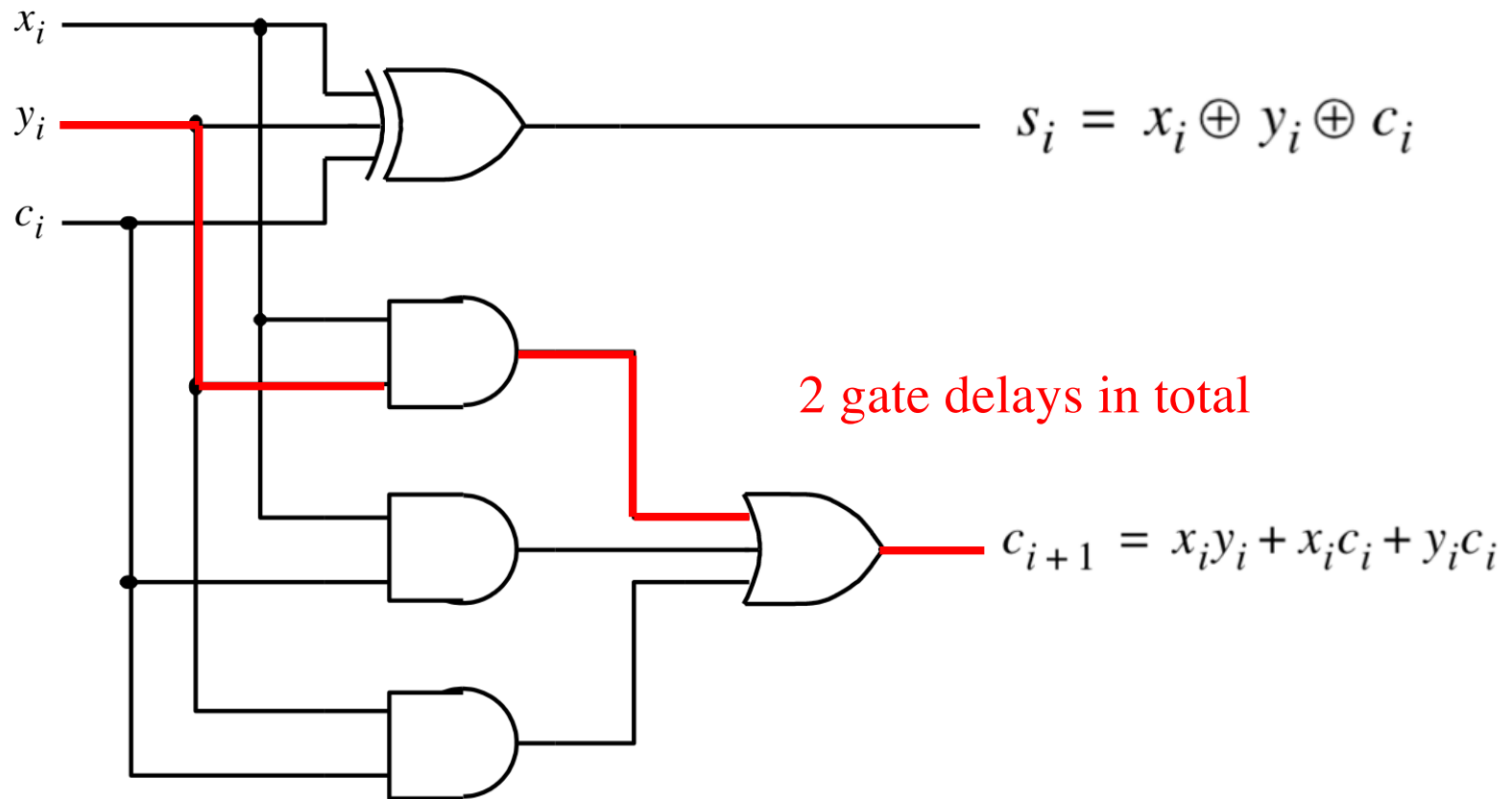

[Figure 3.3c from the textbook]

 How long does it take to compute all sum bits and all carry bits?



It takes $2n$ gate delays?

Can we perform addition even faster?


The goal is to evaluate very fast if the carry from the previous stage will be equal to 0 or 1.

Can we perform addition even faster?

The goal is to evaluate very fast if the carry from the previous stage will be equal to 0 or 1.


To accomplish this goal we will have to redesign the full-adder circuit yet again.

The Full-Adder Circuit

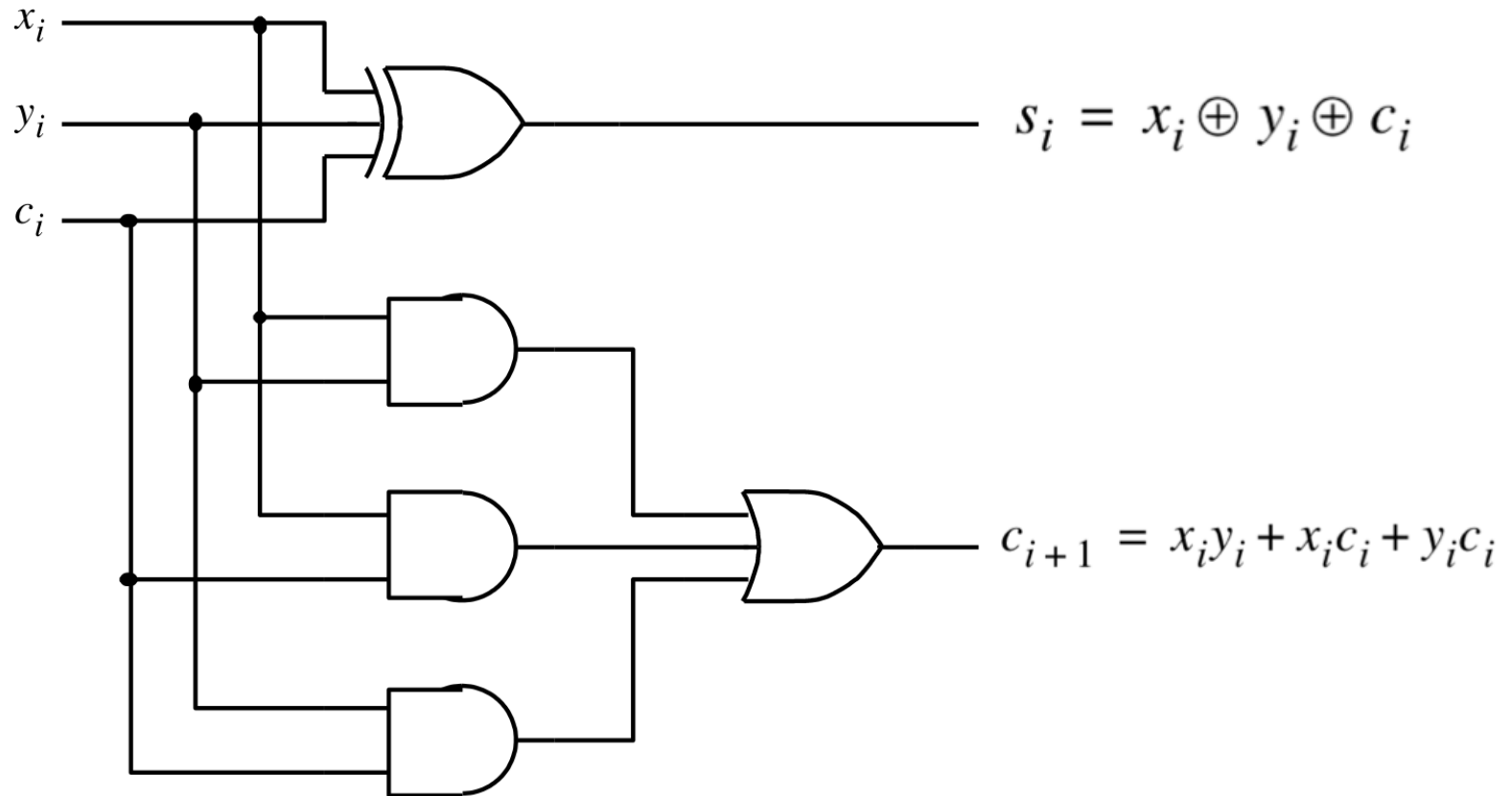

[Figure 3.3c from the textbook]

The Full-Adder Circuit

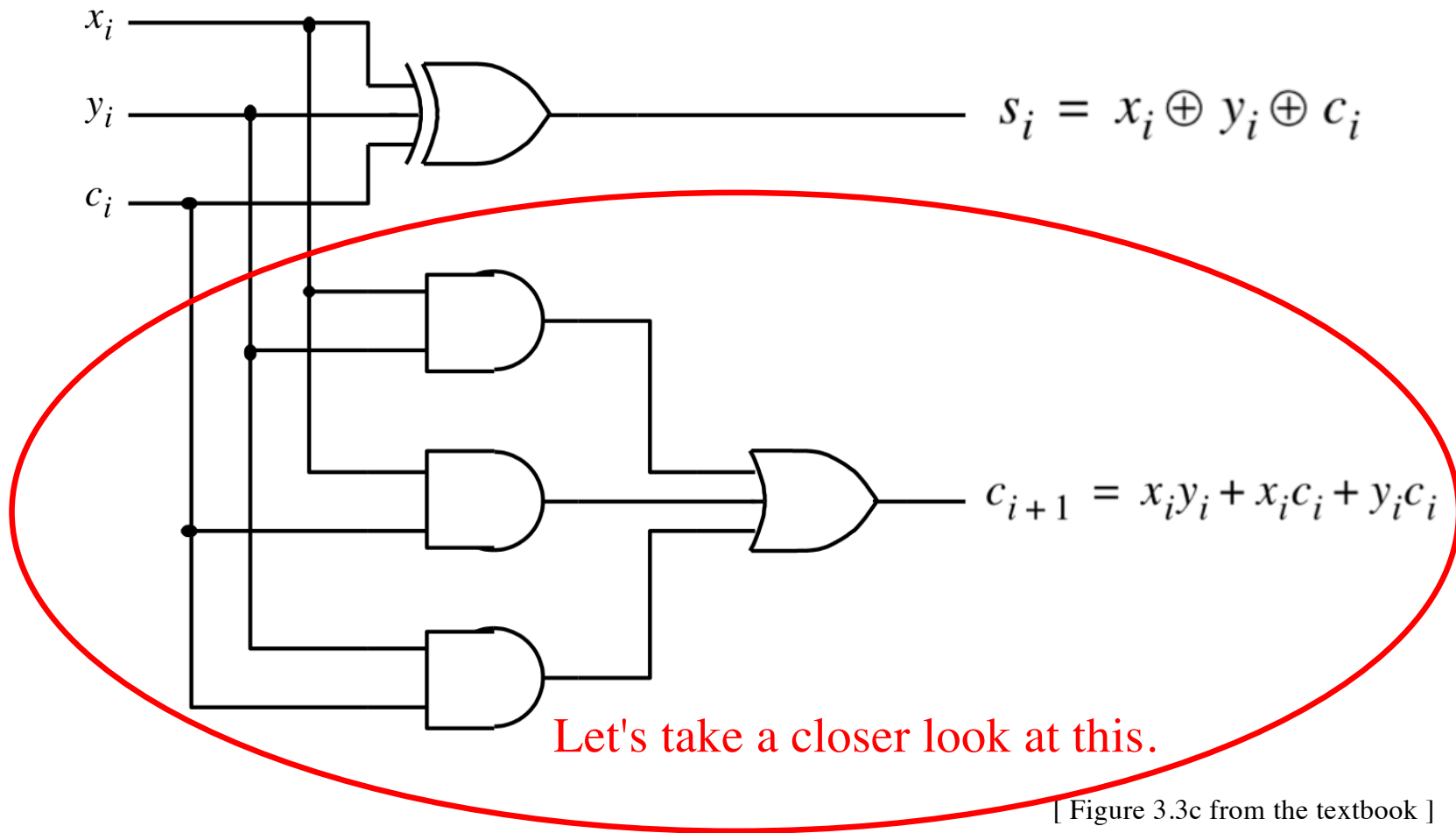

[Figure 3.3c from the textbook]

Decomposing the Carry Expression

$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

Decomposing the Carry Expression


$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

$$c_{i+1} = x_i y_i + (x_i + y_i)c_i$$

Decomposing the Carry Expression

$$C_{i+1} = x_i y_i + x_i c_i + y_i c_i$$


$$C_{i+1} = x_i y_i + (x_i + y_i) c_i$$

 

Another Way to Draw the Full-Adder Circuit


$$C_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

$$C_{i+1} = x_i y_i + (x_i + y_i) c_i$$

 


Another Way to Draw the Full-Adder Circuit

$$C_{i+1} = x_i y_i + (x_i + y_i)c_i$$

 

Another Way to Draw the Full-Adder Circuit
 
$$C_{i+1} = \underbrace{x_i y_i}_{g_i} + \underbrace{(x_i + y_i)}_{p_i} c_i$$




Another Way to Draw the Full-Adder Circuit


g - generate

p - propagate

 
$$C_{i+1} = \underbrace{x_i y_i}_{g_i} + \underbrace{(x_i + y_i)}_{p_i} C_i$$



 Yet Another Way to Draw It (Just Rotate It)



Now we can Build a Ripple-Carry Adder

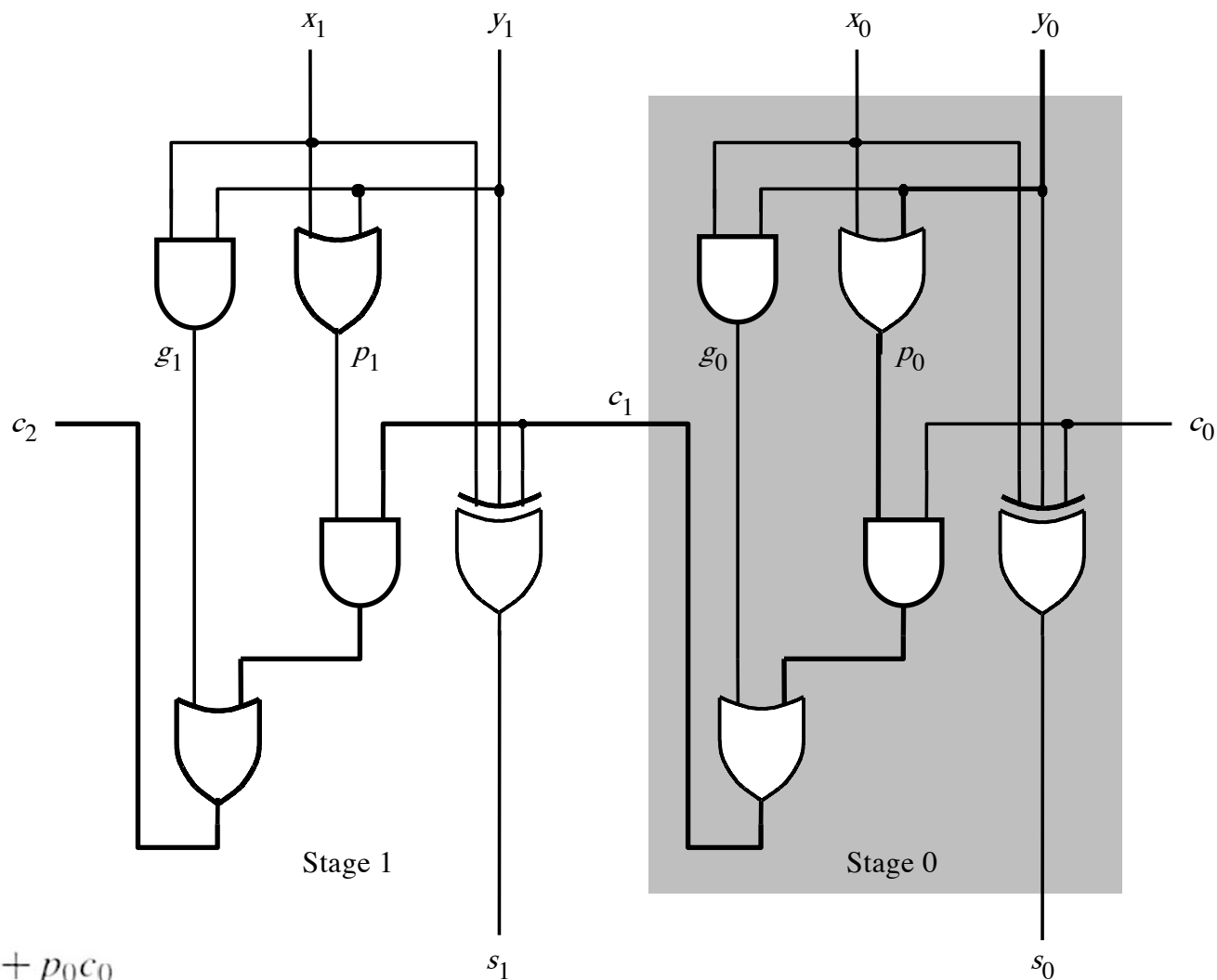


$$c_1 = g_0 + p_0 c_0$$

$$c_2 = g_1 + p_1 g_0 + p_1 p_0 c_0$$

[Figure 3.14 from the textbook]

Now we can Build a Ripple-Carry Adder

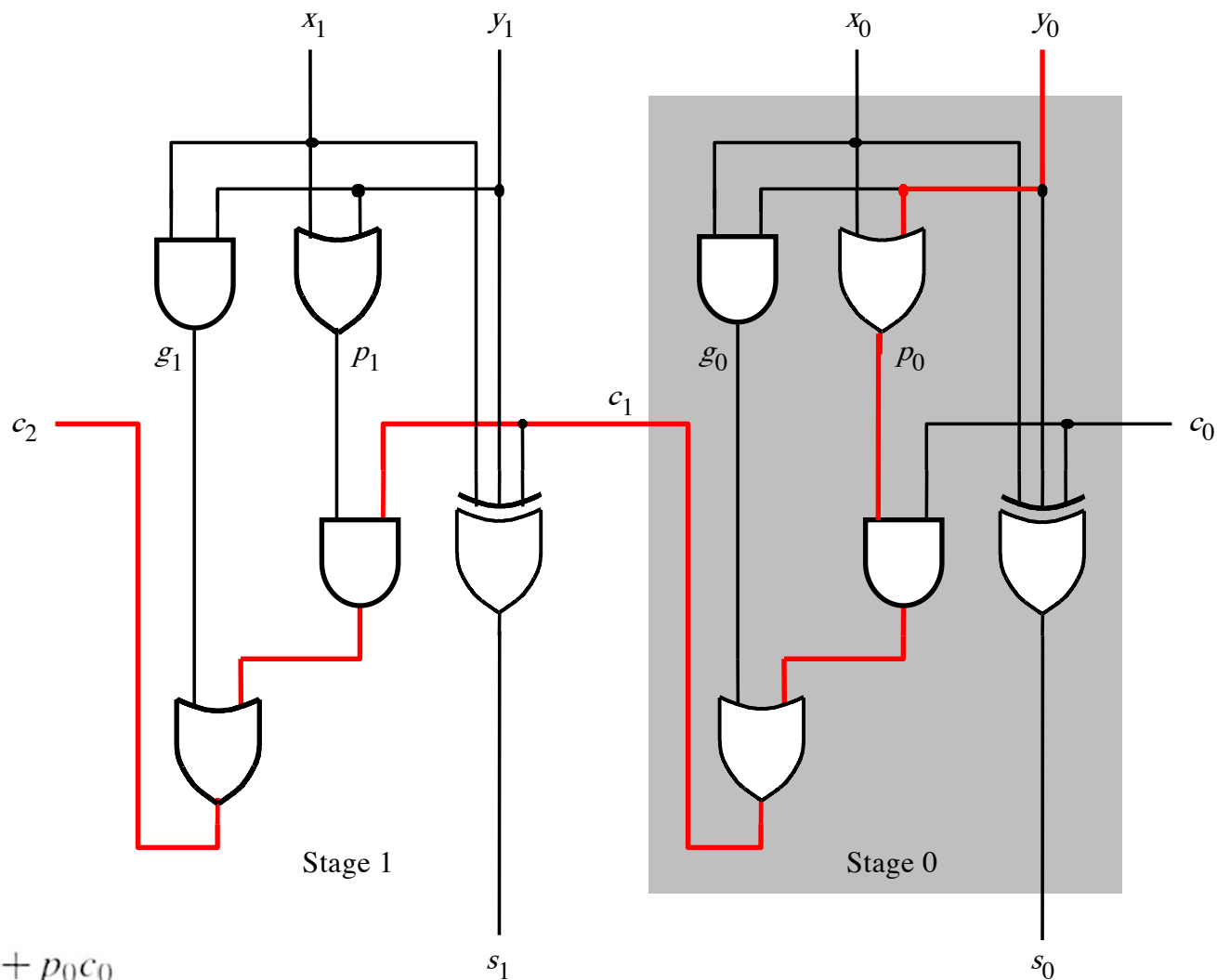


$$c_1 = g_0 + p_0 c_0$$


$$c_2 = g_1 + p_1 g_0 + p_1 p_0 c_0$$

[Figure 3.14 from the textbook]

 2-bit ripple-carry adder: 5 gate delays (1+2+2)



 n-bit ripple-carry adder: $2n+1$ gate delays



n-bit Ripple-Carry Adder

- **It takes 1 gate delay to generate all g_i and p_i signals**
- **+2 more gate delays to generate carry 1**
- **+2 more gate delay to generate carry 2**
- **...**
- **+2 more gate delay to generate carry n**
- **Thus, the total delay through an n-bit ripple-carry adder is $2n+1$ gate delays!**

n-bit Ripple-Carry Adder

- It takes 1 gate delay to generate all g_i and p_i signals
- +2 more gate delays to generate carry 1
- +2 more gate delay to generate carry 2
- ...
- +2 more gate delay to generate carry n
- Thus, the total delay through an n-bit ripple-carry adder is $2n+1$ gate delays!

This is slower by 1 than the original design?!

A carry-lookahead adder

Decomposing the Carry Expression

$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

Decomposing the Carry Expression

$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

$$c_{i+1} = \underbrace{x_i y_i}_{g_i} + \underbrace{(x_i + y_i)}_{p_i} c_i$$


Decomposing the Carry Expression

$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

$$c_{i+1} = \underbrace{x_i y_i}_{g_i} + \underbrace{(x_i + y_i)}_{p_i} c_i$$


(1 gate delay) (1 gate delay)

It takes 1 gate delay to compute all p_i signals

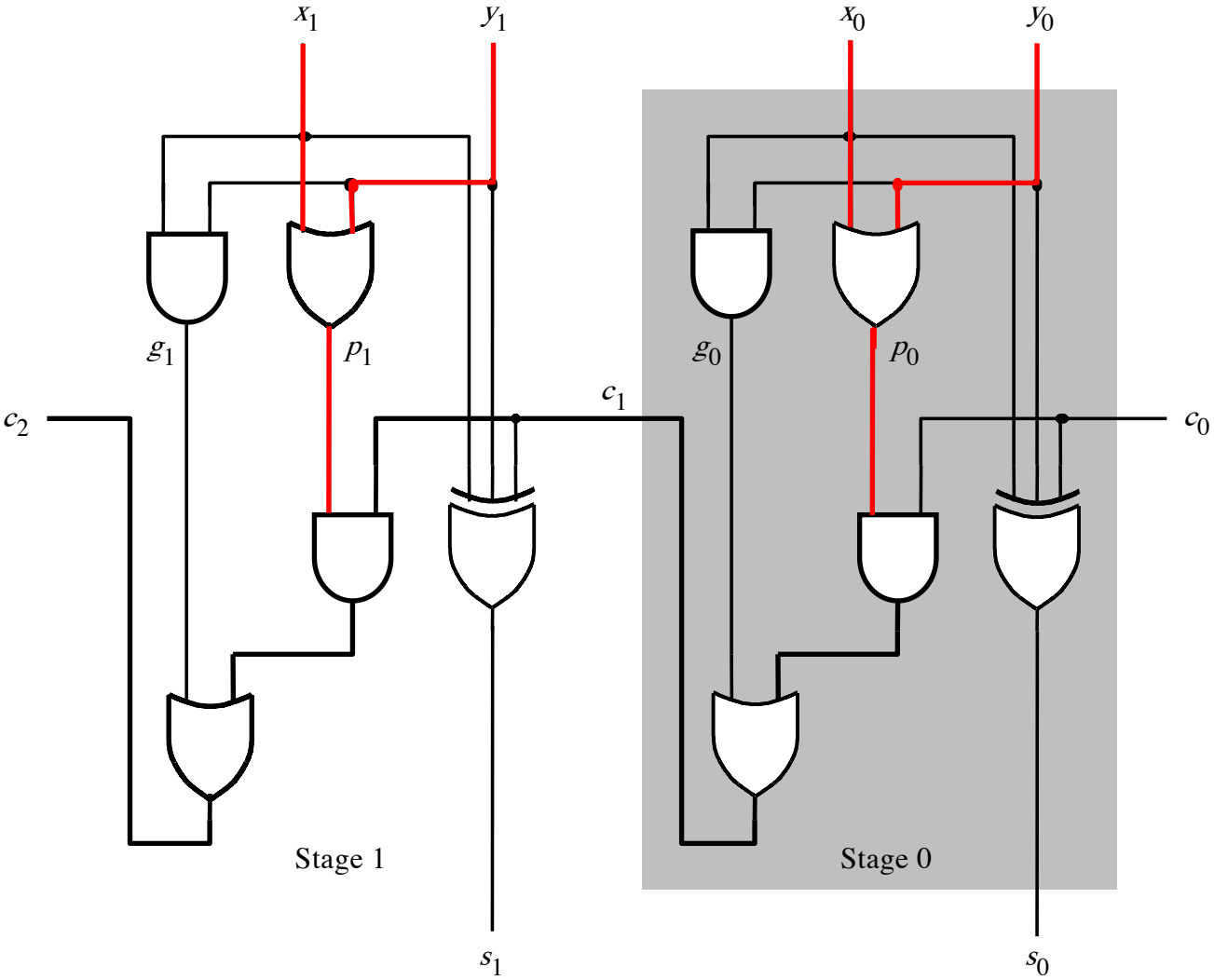

[Figure 3.14 from the textbook]

It takes 1 gate delay to compute all g_i signals

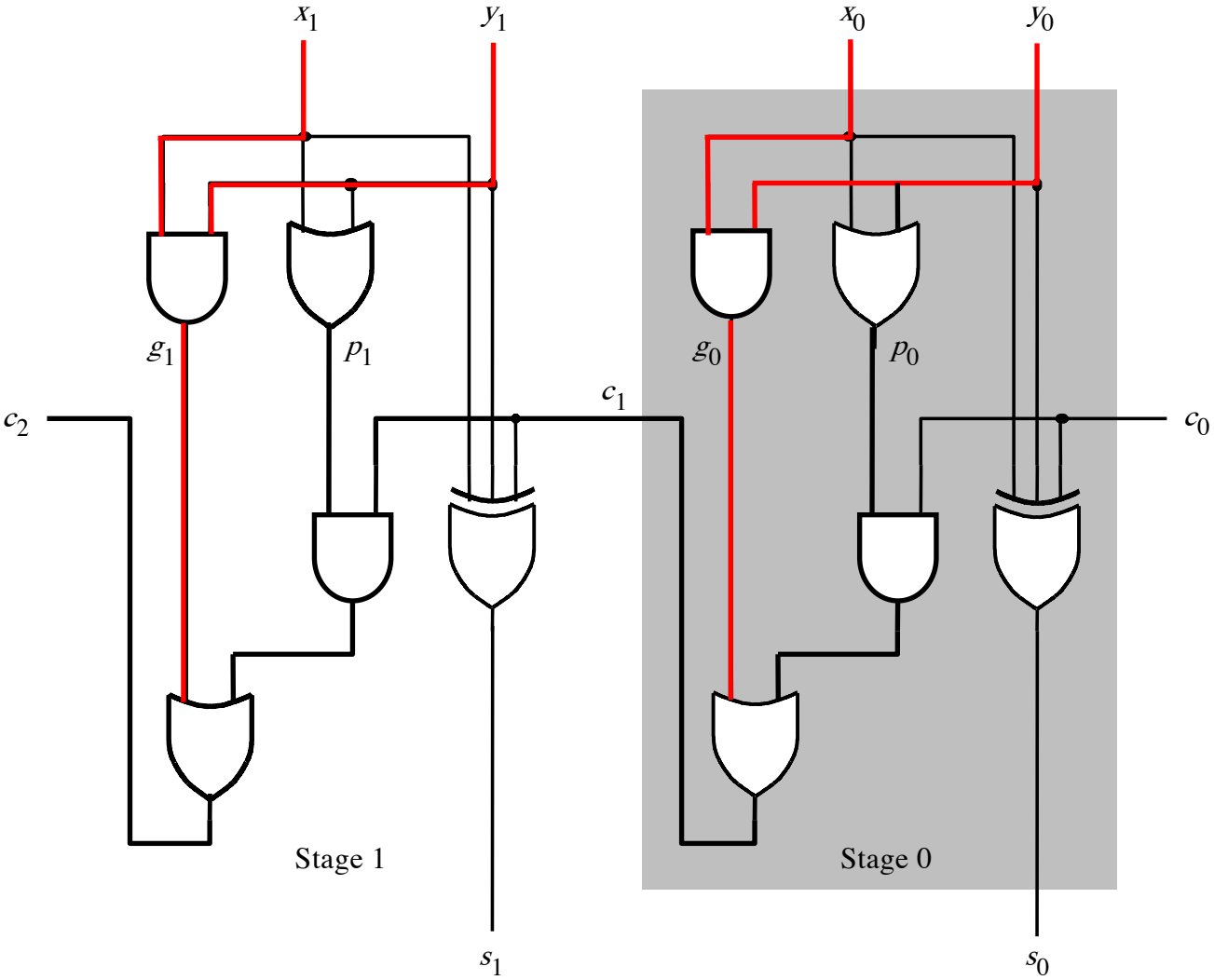

[Figure 3.14 from the textbook]

Decomposing the Carry Expression

$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

$$c_{i+1} = \underbrace{x_i y_i}_{g_i} + \underbrace{(x_i + y_i)}_{p_i} c_i$$

Decomposing the Carry Expression

$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

$$c_{i+1} = \underbrace{x_i y_i}_{g_i} + \underbrace{(x_i + y_i)}_{p_i} c_i$$

$$c_{i+1} = g_i + p_i c_i$$

Decomposing the Carry Expression

$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

$$c_{i+1} = \underbrace{x_i y_i}_{g_i} + \underbrace{(x_i + y_i)}_{p_i} c_i$$

$$c_{i+1} = g_i + p_i c_i$$

recursive
expansion of
 c_i

$$c_{i+1} = g_i + p_i (g_{i-1} + p_{i-1} c_{i-1})$$

Decomposing the Carry Expression

$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$


$$c_{i+1} = \underbrace{x_i y_i}_{g_i} + \underbrace{(x_i + y_i)}_{p_i} c_i$$

$$c_{i+1} = g_i + p_i c_i$$

$$c_{i+1} = g_i + p_i (g_{i-1} + p_{i-1} c_{i-1})$$


$$c_{i+1} = g_i + p_i g_{i-1} + p_i p_{i-1} c_{i-1}$$

Now we can Build a **Carry-Lookahead Adder**

 

[Figure 3.15 from the textbook]

The first two stages of a carry-lookahead adder

 


[Figure 3.15 from the textbook]

Carry for the first stage

$$c_1 = g_0 + p_0 c_0$$


Carry for the first stage

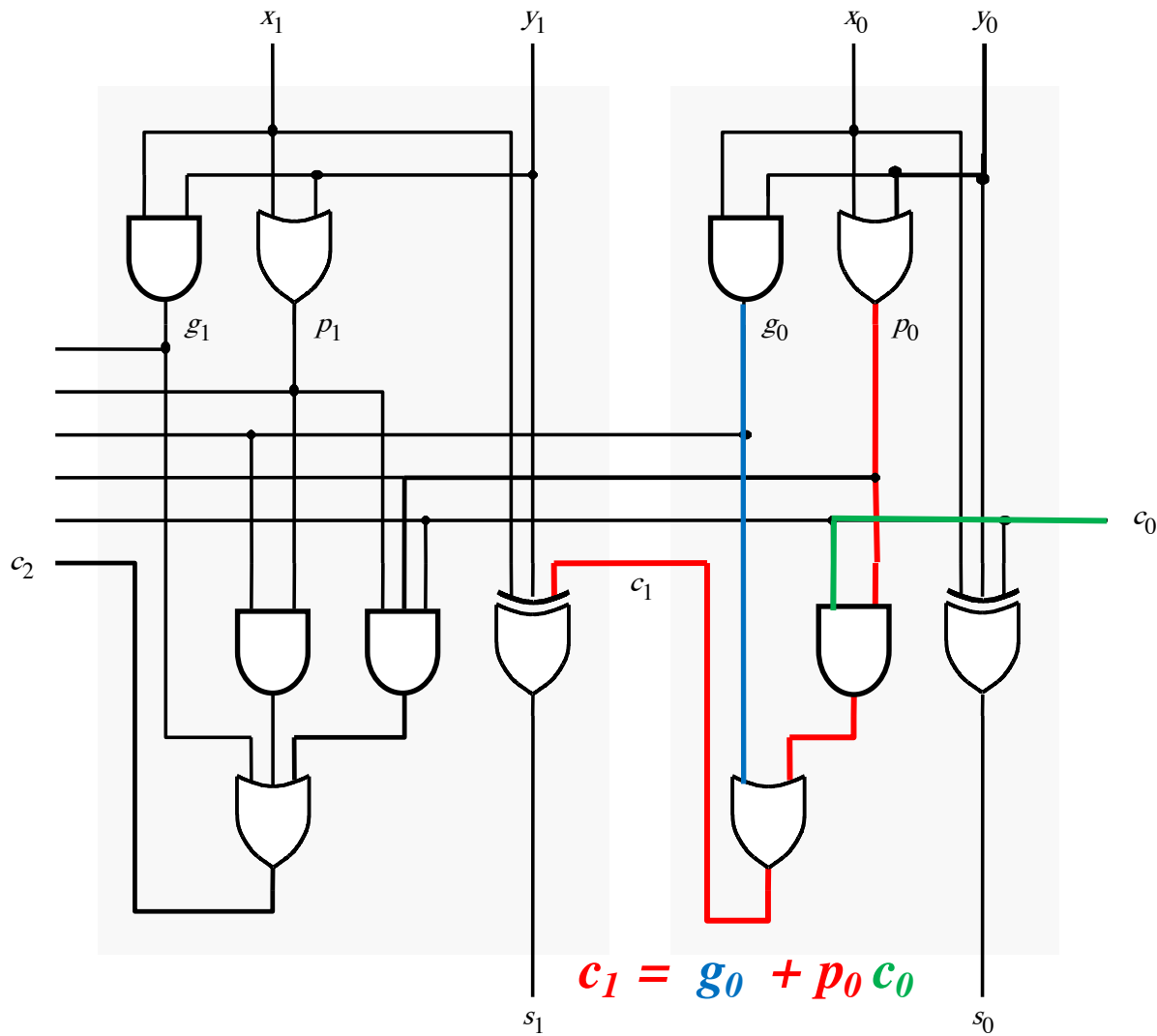

Carry for the second stage

$$c_2 = g_1 + p_1g_0 + p_1p_0c_0$$

Carry for the second stage

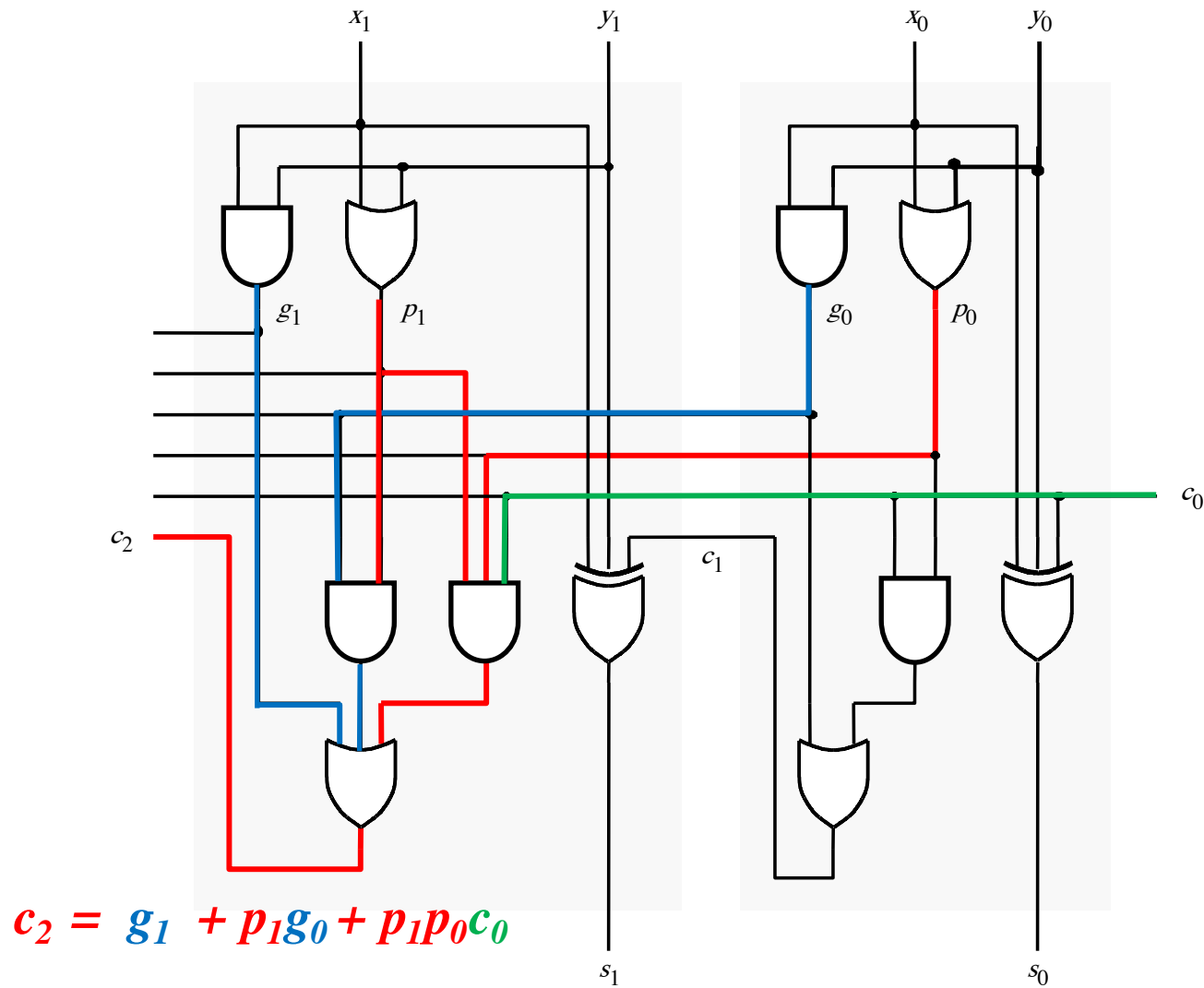

Carry for the first two stages

$$c_1 = g_0 + p_0 c_0$$

$$c_2 = g_1 + p_1 g_0 + p_1 p_0 c_0$$

Carry for the first two stages

$$c_1 = g_0 + p_0 c_0$$

$$c_2 = g_1 + \underline{p_1} g_0 + \underline{p_1 p_0} c_0$$

Carry for the first two stages

$$c_1 = g_0 + p_0 c_0$$

$$c_2 = g_1 + \underline{p_1} g_0 + \underline{p_1 p_0} c_0$$

$$= g_1 + p_1 \underbrace{(g_0 + p_0 c_0)}_{c_1}$$

Carry for the first two stages


$$c_1 = g_0 + p_0 c_0$$

$$c_2 = g_1 + p_1 g_0 + p_1 p_0 c_0$$

$$= g_1 + p_1 \underbrace{(g_0 + p_0 c_0)}_{c_1}$$


$$= g_1 + p_1 c_1$$

The first two stages of a carry-lookahead adder

 


[Figure 3.15 from the textbook]


It takes 3 gate delays to generate c_1

 


It takes 3 gate delays to generate c_2

 

 
The first two stages of a carry-lookahead adder



It takes 4 gate delays to generate s_1

 

It takes 4 gate delays to generate s_2

 

N-bit Carry-Lookahead Adder

- **It takes 1 gate delay to generate all g_i and p_i signals**
- **It takes 2 more gate delays to generate all carry signals**
- **It takes 1 more gate delay to generate all sum bits**
- **Thus, the total delay through an n-bit carry-lookahead adder is only 4 gate delays!**

N-bit Carry-Lookahead Adder

- It takes 1 gate delay to generate all g_i and p_i signals
- It takes 2 more gate delays to generate all carry signals
- It takes 1 more gate delay to generate all sum bits
- Thus, the total delay through an n-bit carry-lookahead adder is **only 4 gate delays!**

Expanding the Carry Expression

$$c_{i+1} = g_i + p_i c_i$$

$$c_1 = g_0 + p_0 c_0$$

$$c_2 = g_1 + p_1 g_0 + p_1 p_0 c_0$$

$$c_3 = g_2 + p_2 g_1 + p_2 p_1 g_0 + p_2 p_1 p_0 c_0$$

...

$$\begin{aligned} c_8 = & g_7 + p_7 g_6 + p_7 p_6 g_5 + p_7 p_6 p_5 g_4 \\ & + p_7 p_6 p_5 p_4 g_3 + p_7 p_6 p_5 p_4 p_3 g_2 \\ & + p_7 p_6 p_5 p_4 p_3 p_2 g_1 + p_7 p_6 p_5 p_4 p_3 p_2 p_1 g_0 \\ & + p_7 p_6 p_5 p_4 p_3 p_2 p_1 p_0 c_0 \end{aligned}$$

Expanding the Carry Expression

$$c_{i+1} = g_i + p_i c_i$$

$$c_1 = g_0 + p_0 c_0$$

$$c_2 = g_1 + p_1 g_0 + p_1 p_0 c_0$$

$$c_3 = g_2 + p_2 g_1 + p_2 p_1 g_0 + p_2 p_1 p_0 c_0$$

...

$$c_8 = g_7 + p_7 g_6 + p_7 p_6 g_5 + p_7 p_6 p_5 g_4$$

Even this takes

only 3 gate delays


$$+ p_7 p_6 p_5 p_4 g_3 + p_7 p_6 p_5 p_4 p_3 g_2$$

$$+ p_7 p_6 p_5 p_4 p_3 p_2 g_1 + p_7 p_6 p_5 p_4 p_3 p_2 p_1 g_0$$


$$+ p_7 p_6 p_5 p_4 p_3 p_2 p_1 p_0 c_0$$

**A hierarchical carry-lookahead adder
with ripple-carry between blocks**

 
A hierarchical carry-lookahead adder with ripple-carry between blocks



 A hierarchical carry-lookahead adder with ripple-carry between blocks




 A hierarchical carry-lookahead adder with ripple-carry between blocks




A hierarchical carry-lookahead adder

A hierarchical carry-lookahead adder with ripple-carry between blocks

 


[Figure 3.16 from the textbook]

A hierarchical carry-lookahead adder

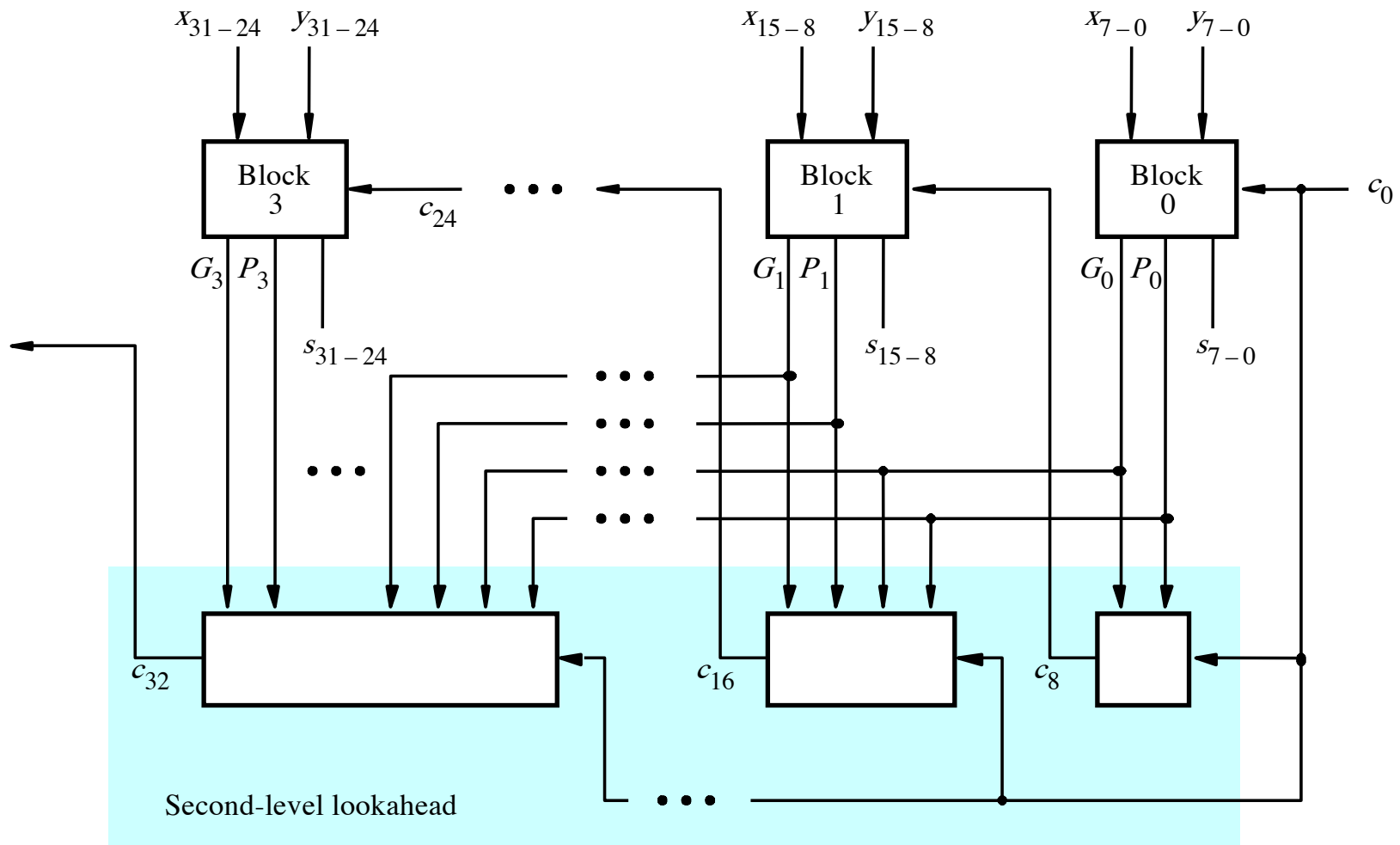


[Figure 3.17 from the textbook]


A hierarchical carry-lookahead adder

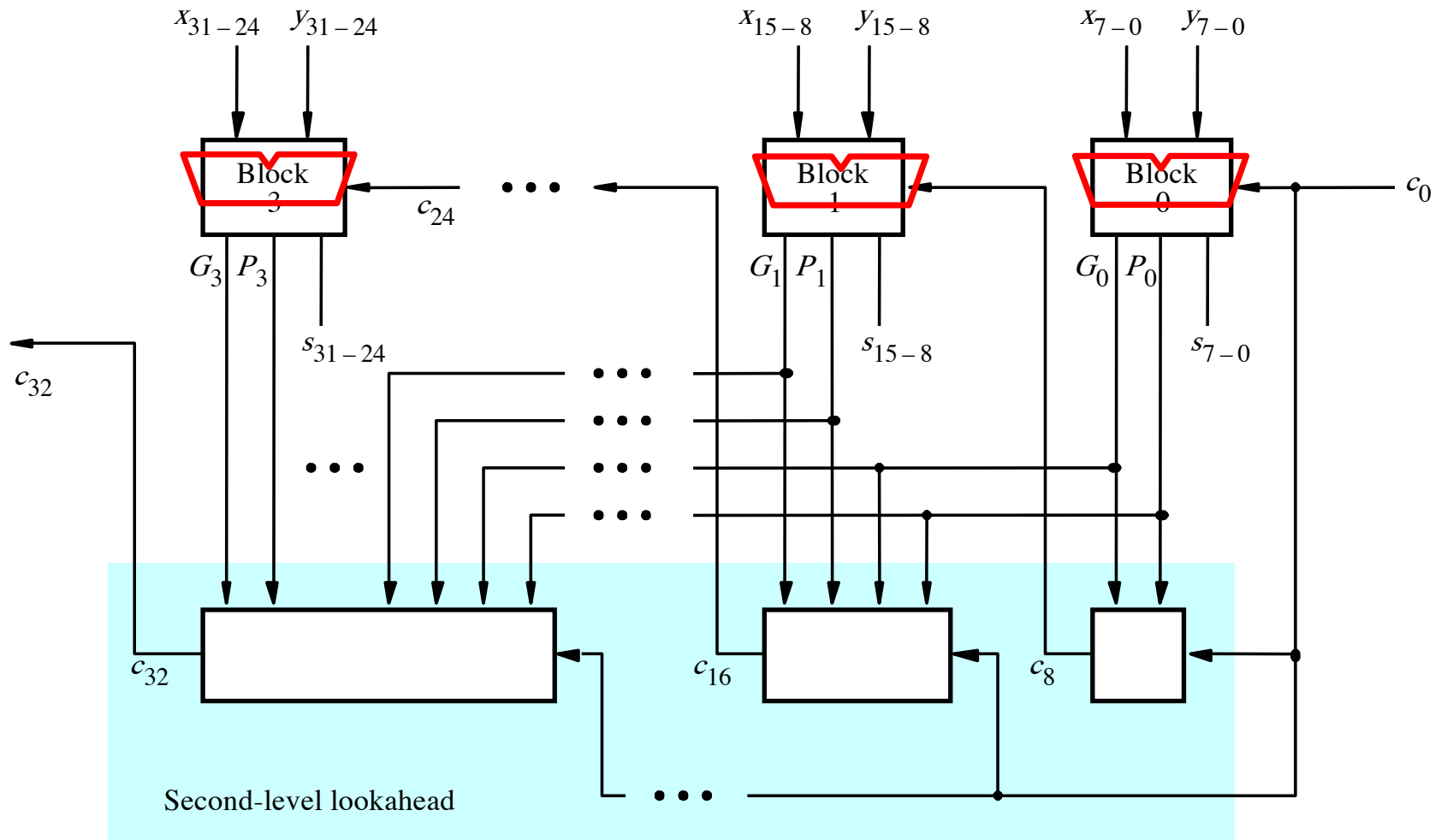

A hierarchical carry-lookahead adder

 

A hierarchical carry-lookahead adder

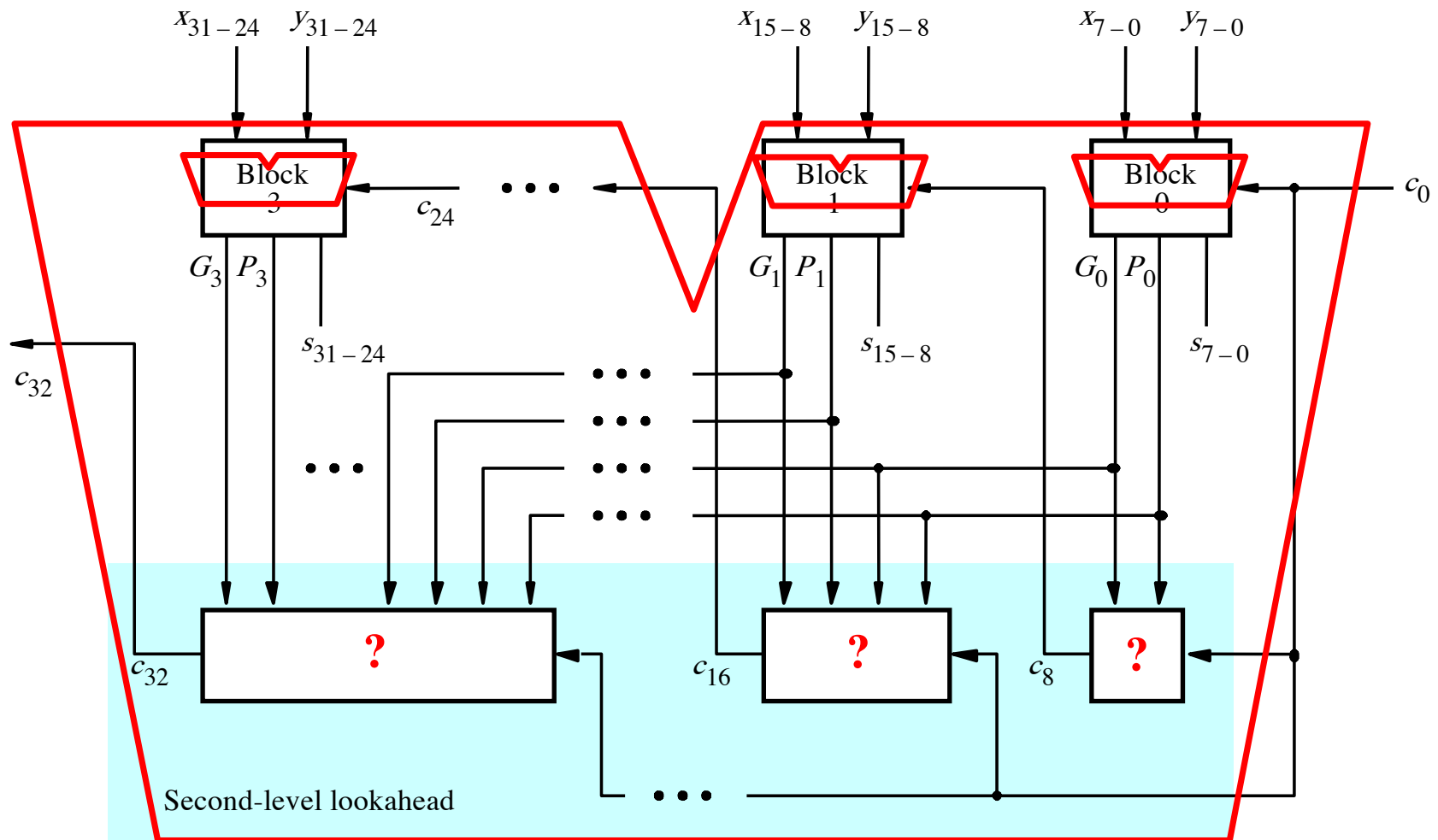

The Hierarchical Carry Expression

$$\begin{aligned}c_8 = & g_7 + p_7g_6 + p_7p_6g_5 + p_7p_6p_5g_4 \\ & + p_7p_6p_5p_4g_3 + p_7p_6p_5p_4p_3g_2 \\ & + p_7p_6p_5p_4p_3p_2g_1 + p_7p_6p_5p_4p_3p_2p_1g_0 \\ & + p_7p_6p_5p_4p_3p_2p_1p_0c_0\end{aligned}$$

The Hierarchical Carry Expression

$$\begin{aligned} c_8 = & g_7 + p_7g_6 + p_7p_6g_5 + p_7p_6p_5g_4 \\ & + p_7p_6p_5p_4g_3 + p_7p_6p_5p_4p_3g_2 \\ & + p_7p_6p_5p_4p_3p_2g_1 + p_7p_6p_5p_4p_3p_2p_1g_0 \\ & + p_7p_6p_5p_4p_3p_2p_1p_0c_0 \end{aligned}$$

The Hierarchical Carry Expression

$$c_8 = g_7 + p_7g_6 + p_7p_6g_5 + p_7p_6p_5g_4 \\ + p_7p_6p_5p_4g_3 + p_7p_6p_5p_4p_3g_2 \\ + p_7p_6p_5p_4p_3p_2g_1 + p_7p_6p_5p_4p_3p_2p_1g_0 \\ + p_7p_6p_5p_4p_3p_2p_1p_0c_0$$

G_0 →

P_0 →

The Hierarchical Carry Expression

$$c_8 = g_7 + p_7g_6 + p_7p_6g_5 + p_7p_6p_5g_4 \\ + p_7p_6p_5p_4g_3 + p_7p_6p_5p_4p_3g_2 \\ + p_7p_6p_5p_4p_3p_2g_1 + p_7p_6p_5p_4p_3p_2p_1g_0 \\ + p_7p_6p_5p_4p_3p_2p_1p_0c_0$$

G_0 →

P_0 →

$$c_8 = G_0 + P_0c_0$$

The Hierarchical Carry Expression

3-gate delays

$$c_8 = g_7 + p_7g_6 + p_7p_6g_5 + p_7p_6p_5g_4 \\ + p_7p_6p_5p_4g_3 + p_7p_6p_5p_4p_3g_2 \\ + p_7p_6p_5p_4p_3p_2g_1 + p_7p_6p_5p_4p_3p_2p_1g_0 \\ + p_7p_6p_5p_4p_3p_2p_1p_0c_0$$

G_0 →

P_0 →

2-gate delays

$$c_8 = G_0 + P_0c_0$$

The Hierarchical Carry Expression

3-gate delays

$$\begin{aligned}
 c_8 = & g_7 + p_7g_6 + p_7p_6g_5 + p_7p_6p_5g_4 \\
 & + p_7p_6p_5p_4g_3 + p_7p_6p_5p_4p_3g_2 \\
 & + p_7p_6p_5p_4p_3p_2g_1 + p_7p_6p_5p_4p_3p_2p_1g_0 \\
 & + p_7p_6p_5p_4p_3p_2p_1p_0c_0
 \end{aligned}$$

G_0 points to the first four terms of the expression.
 P_0 points to the product term $p_7p_6p_5p_4p_3p_2p_1p_0$.
 The product term is labeled as 2-gate delays.

$$c_8 = \underbrace{G_0}_{\substack{\text{3-gate} \\ \text{delays}}} + \underbrace{P_0}_{\substack{\text{2-gate} \\ \text{delays}}} c_0$$

The Hierarchical Carry Expression

3-gate delays

$$\begin{aligned}
 c_8 = & g_7 + p_7g_6 + p_7p_6g_5 + p_7p_6p_5g_4 \\
 & + p_7p_6p_5p_4g_3 + p_7p_6p_5p_4p_3g_2 \\
 & + p_7p_6p_5p_4p_3p_2g_1 + p_7p_6p_5p_4p_3p_2p_1g_0 \\
 & + p_7p_6p_5p_4p_3p_2p_1p_0c_0
 \end{aligned}$$

G_0 points to the first four terms of the expression.

P_0 points to the term $p_7p_6p_5p_4p_3p_2p_1p_0c_0$.

2-gate delays

$$c_8 = \underbrace{G_0}_{\substack{\text{3-gate} \\ \text{delays}}} + \underbrace{P_0 c_0}_{\substack{\text{3-gate} \\ \text{delays}}}$$

The Hierarchical Carry Expression

3-gate delays

$$c_8 = g_7 + p_7g_6 + p_7p_6g_5 + p_7p_6p_5g_4$$
$$+ p_7p_6p_5p_4g_3 + p_7p_6p_5p_4p_3g_2$$
$$+ p_7p_6p_5p_4p_3p_2g_1 + p_7p_6p_5p_4p_3p_2p_1g_0$$
$$+ p_7p_6p_5p_4p_3p_2p_1p_0c_0$$

G_0 points to the first four terms of the expression.

P_0 points to the term $p_7p_6p_5p_4p_3p_2p_1p_0c_0$.

2-gate delays

$$c_8 = G_0 + P_0c_0$$

4-gate delays

The Hierarchical Carry Expression

$$\begin{aligned}c_8 = & g_7 + p_7g_6 + p_7p_6g_5 + p_7p_6p_5g_4 \\ & + p_7p_6p_5p_4g_3 + p_7p_6p_5p_4p_3g_2 \\ & + p_7p_6p_5p_4p_3p_2g_1 + p_7p_6p_5p_4p_3p_2p_1g_0 \\ & + p_7p_6p_5p_4p_3p_2p_1p_0c_0\end{aligned}$$

$$\begin{aligned}c_{16} = & g_{15} + p_{15}g_{14} + p_{15}p_{14}g_{13} + p_{15}p_{14}p_{13}g_{12} \\ & + p_{15}p_{14}p_{13}p_{12}g_{11} + p_{15}p_{14}p_{13}p_{12}p_{11}g_{10} \\ & + p_{15}p_{14}p_{13}p_{12}p_{11}p_{10}g_9 + p_{15}p_{14}p_{13}p_{12}p_{11}p_{10}p_9g_8 \\ & + p_{15}p_{14}p_{13}p_{12}p_{11}p_{10}p_9p_8c_8\end{aligned}$$

The Hierarchical Carry Expression

$$\begin{aligned}c_8 = & g_7 + p_7g_6 + p_7p_6g_5 + p_7p_6p_5g_4 \\ & + p_7p_6p_5p_4g_3 + p_7p_6p_5p_4p_3g_2 \\ & + p_7p_6p_5p_4p_3p_2g_1 + p_7p_6p_5p_4p_3p_2p_1g_0 \\ & + p_7p_6p_5p_4p_3p_2p_1p_0c_0\end{aligned}$$

The same expression, just add 8 to all subscripts

$$\begin{aligned}c_{16} = & g_{15} + p_{15}g_{14} + p_{15}p_{14}g_{13} + p_{15}p_{14}p_{13}g_{12} \\ & + p_{15}p_{14}p_{13}p_{12}g_{11} + p_{15}p_{14}p_{13}p_{12}p_{11}g_{10} \\ & + p_{15}p_{14}p_{13}p_{12}p_{11}p_{10}g_9 + p_{15}p_{14}p_{13}p_{12}p_{11}p_{10}p_9g_8 \\ & + p_{15}p_{14}p_{13}p_{12}p_{11}p_{10}p_9p_8c_8\end{aligned}$$

The Hierarchical Carry Expression

3-gate delays

$$\begin{aligned}
 c_8 = & g_7 + p_7g_6 + p_7p_6g_5 + p_7p_6p_5g_4 \\
 & + p_7p_6p_5p_4g_3 + p_7p_6p_5p_4p_3g_2 \\
 & + p_7p_6p_5p_4p_3p_2g_1 + p_7p_6p_5p_4p_3p_2p_1g_0 \\
 & + p_7p_6p_5p_4p_3p_2p_1p_0c_0
 \end{aligned}$$

G_0 points to the first four terms of the expression.

P_0 points to the last term of the expression, which is highlighted with a red box and labeled "2-gate delays".

$$\begin{aligned}
 c_{16} = & g_{15} + p_{15}g_{14} + p_{15}p_{14}g_{13} + p_{15}p_{14}p_{13}g_{12} \\
 & + p_{15}p_{14}p_{13}p_{12}g_{11} + p_{15}p_{14}p_{13}p_{12}p_{11}g_{10} \\
 & + p_{15}p_{14}p_{13}p_{12}p_{11}p_{10}g_9 + p_{15}p_{14}p_{13}p_{12}p_{11}p_{10}p_9g_8 \\
 & + p_{15}p_{14}p_{13}p_{12}p_{11}p_{10}p_9p_8c_8
 \end{aligned}$$

The Hierarchical Carry Expression

$$\begin{aligned}
 c_8 = & g_7 + p_7g_6 + p_7p_6g_5 + p_7p_6p_5g_4 \\
 & + p_7p_6p_5p_4g_3 + p_7p_6p_5p_4p_3g_2 \\
 & + p_7p_6p_5p_4p_3p_2g_1 + p_7p_6p_5p_4p_3p_2p_1g_0 \\
 & + p_7p_6p_5p_4p_3p_2p_1p_0c_0
 \end{aligned}$$

3-gate delays

$$\begin{aligned}
 c_{16} = & g_{15} + p_{15}g_{14} + p_{15}p_{14}g_{13} + p_{15}p_{14}p_{13}g_{12} \\
 & + p_{15}p_{14}p_{13}p_{12}g_{11} + p_{15}p_{14}p_{13}p_{12}p_{11}g_{10} \\
 & + p_{15}p_{14}p_{13}p_{12}p_{11}p_{10}g_9 + p_{15}p_{14}p_{13}p_{12}p_{11}p_{10}p_9g_8 \\
 & + p_{15}p_{14}p_{13}p_{12}p_{11}p_{10}p_9p_8c_8
 \end{aligned}$$

G_1 →

P_1 →

2-gate delays

The Hierarchical Carry Expression

$$c_8 = G_0 + P_0 c_0$$

The Hierarchical Carry Expression

$$c_8 = \textcircled{G_0} + P_0 c_0$$

3-gate delays

The Hierarchical Carry Expression

$$c_8 = G_0 + P_0 c_0$$

2-gate delays

The Hierarchical Carry Expression

$$c_8 = G_0 + P_0 c_0$$

3-gate delays

The Hierarchical Carry Expression

$$c_8 = G_0 + P_0 c_0$$

4-gate delays

The Hierarchical Carry Expression

$$c_8 = G_0 + P_0 c_0$$

$$\begin{aligned} c_{16} &= G_1 + P_1 c_8 \\ &= G_1 + P_1 G_0 + P_1 P_0 c_0 \end{aligned}$$

The Hierarchical Carry Expression

$$c_8 = \textcircled{G_0} + P_0 c_0$$

3-gate delays

$$\begin{aligned} c_{16} &= G_1 + P_1 c_8 \\ &= G_1 + P_1 \textcircled{G_0} + P_1 P_0 c_0 \end{aligned}$$

3-gate delays

The Hierarchical Carry Expression

$$c_8 = \textcircled{G_0} + P_0 c_0$$

3-gate delays

$$\begin{aligned} c_{16} &= G_1 + P_1 c_8 \\ &= \textcircled{G_1} + P_1 G_0 + P_1 P_0 c_0 \end{aligned}$$

3-gate delays

The Hierarchical Carry Expression

$$c_8 = G_0 + P_0 c_0$$

$$\begin{aligned} c_{16} &= G_1 + P_1 c_8 \\ &= G_1 + P_1 \underbrace{G_0}_{\text{3-gate delays}} + P_1 P_0 c_0 \end{aligned}$$

3-gate delays

The Hierarchical Carry Expression

$$c_8 = G_0 + P_0 c_0$$

$$\begin{aligned} c_{16} &= G_1 + P_1 c_8 \\ &= G_1 + \underbrace{P_1}_{\text{2-gate delays}} G_0 + P_1 P_0 c_0 \end{aligned}$$

2-gate delays

The Hierarchical Carry Expression

$$c_8 = G_0 + P_0 c_0$$

$$\begin{aligned} c_{16} &= G_1 + P_1 c_8 \\ &= G_1 + P_1 G_0 + P_1 P_0 c_0 \end{aligned}$$

4-gate delays

The Hierarchical Carry Expression

$$c_8 = G_0 + P_0 c_0$$

$$\begin{aligned} c_{16} &= G_1 + P_1 c_8 \\ &= G_1 + P_1 G_0 + \underbrace{P_1}_{\text{2-gate delays}} P_0 c_0 \end{aligned}$$

The Hierarchical Carry Expression

$$c_8 = G_0 + P_0 c_0$$

$$\begin{aligned} c_{16} &= G_1 + P_1 c_8 \\ &= G_1 + P_1 G_0 + P_1 P_0 c_0 \end{aligned}$$

2-gate delays

The Hierarchical Carry Expression

$$c_8 = G_0 + P_0 c_0$$

$$\begin{aligned} c_{16} &= G_1 + P_1 c_8 \\ &= G_1 + P_1 G_0 + \underbrace{P_1 P_0 c_0}_{\text{3-gate delays}} \end{aligned}$$

The Hierarchical Carry Expression

$$c_8 = G_0 + P_0 c_0$$

$$\begin{aligned} c_{16} &= G_1 + P_1 c_8 \\ &= G_1 + P_1 G_0 + P_1 P_0 c_0 \end{aligned}$$

5-gate delays

The Hierarchical Carry Expression

$$c_8 = G_0 + P_0 c_0$$

$$\begin{aligned} c_{16} &= G_1 + P_1 c_8 \\ &= G_1 + P_1 G_0 + P_1 P_0 c_0 \end{aligned}$$

$$c_{24} = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 c_0$$

$$c_{32} = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 c_0$$

The Hierarchical Carry Expression


$$c_8 = G_0 + P_0 c_0 \quad \text{4-gate delays}$$

$$\begin{aligned} c_{16} &= G_1 + P_1 c_8 && \text{5-gate delays} \\ &= G_1 + P_1 G_0 + P_1 P_0 c_0 \end{aligned}$$

$$c_{24} = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 c_0 \quad \text{5-gate delays}$$


$$c_{32} = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 c_0 \quad \text{5-gate delays}$$

A hierarchical carry-lookahead adder

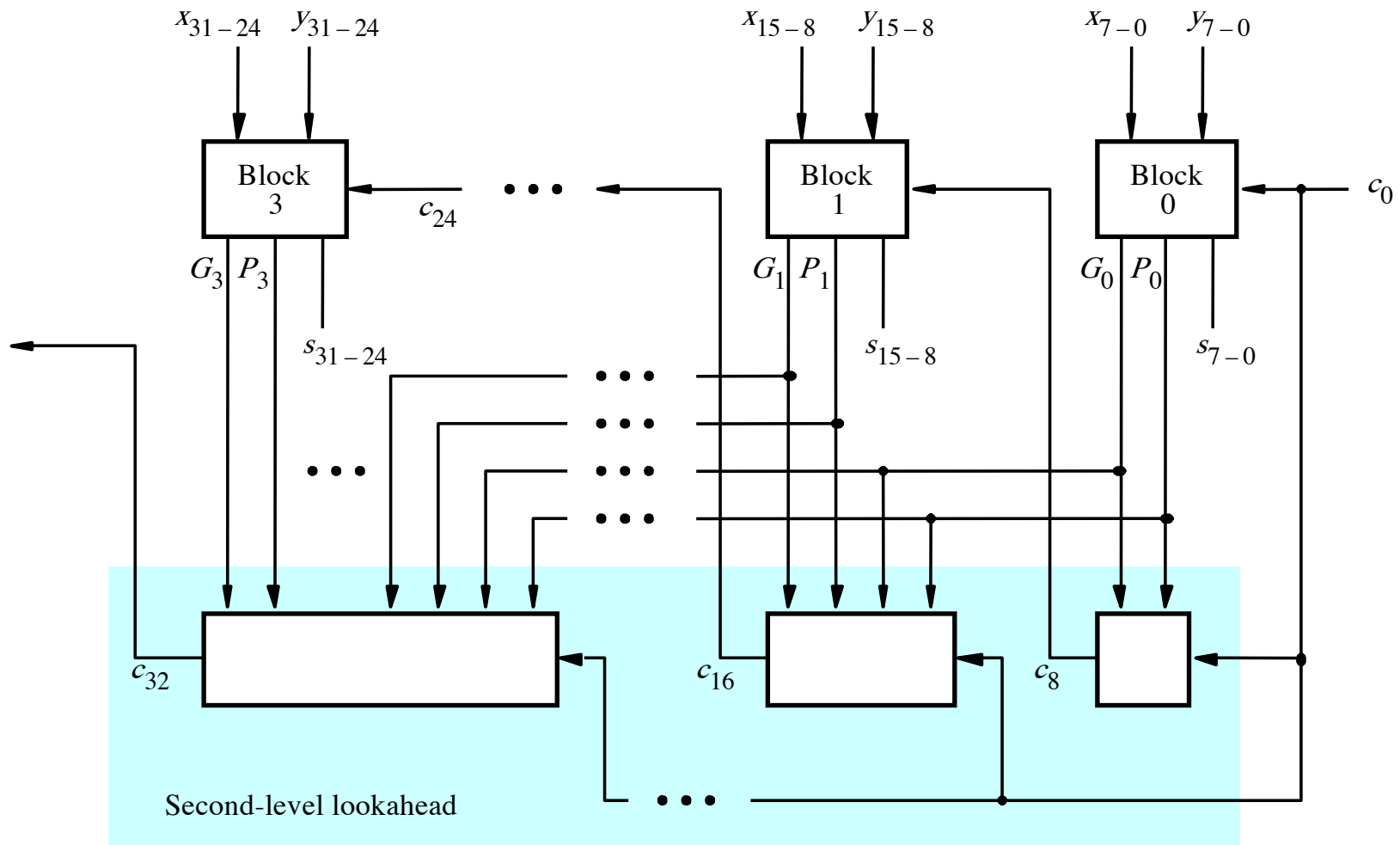

[Figure 3.17 from the textbook]

A hierarchical carry-lookahead adder

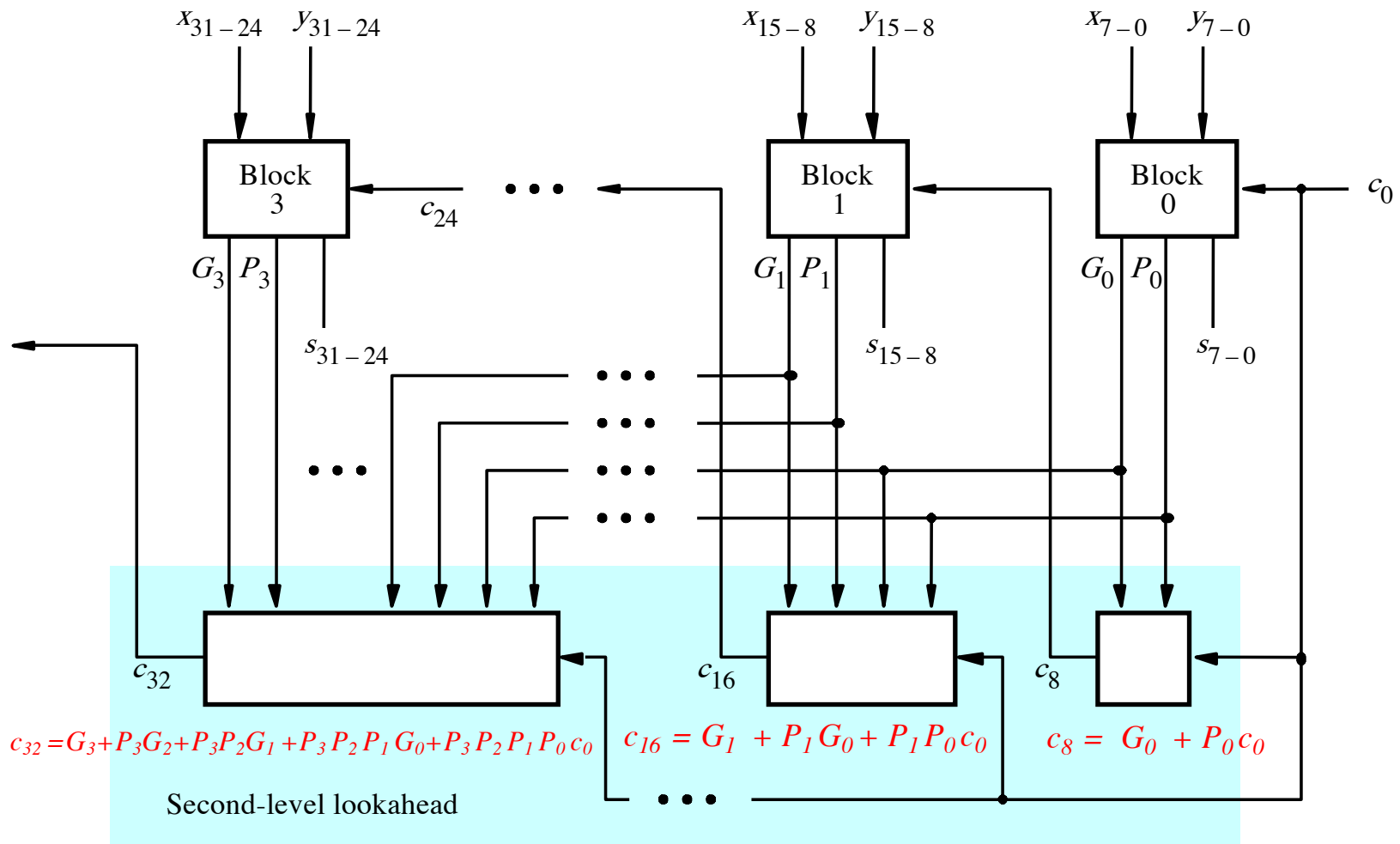

[Figure 3.17 from the textbook]


Total Gate Delay Through a Hierarchical Carry-Lookahead Adder

- The total delay is 8 gates:
 - 3 to generate all G_i and P_i signals
 - +2 to generate c_8 , c_{16} , c_{24} , and c_{32}
 - +2 to generate internal carries in the blocks
 - +1 to generate the sum bits (one extra XOR)


Total Gate Delay Through a Hierarchical Carry-Lookahead Adder

- The total delay is 8 gates:
 - 3 to generate all G_i and P_i signals
 - +2 to generate c_8 , c_{16} , c_{24} , and c_{32}
 - **+2 to generate internal carries in the blocks**
 - +1 to generate the sum bits (one extra XOR)

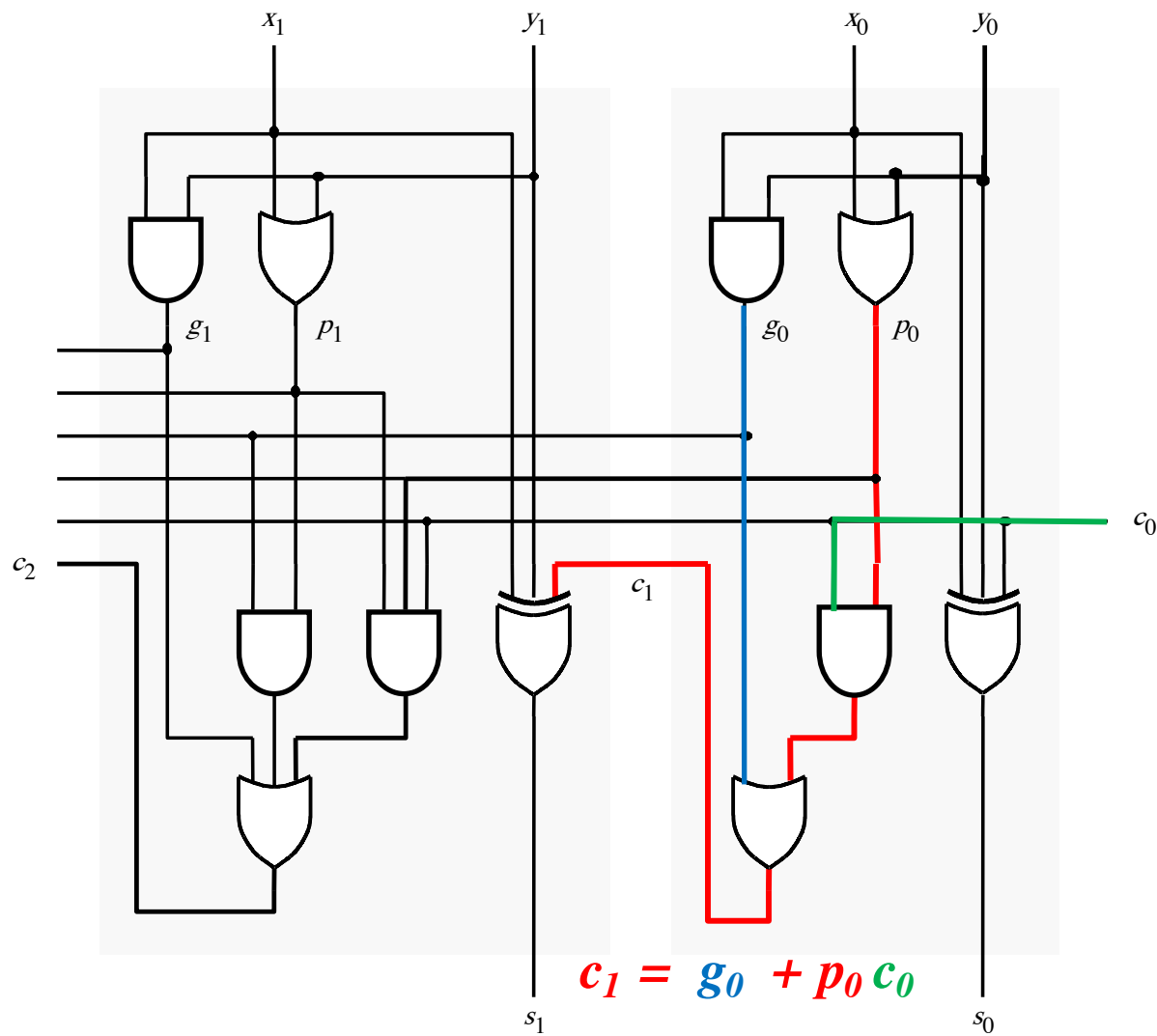2 more gate delays for the internal carries within a block




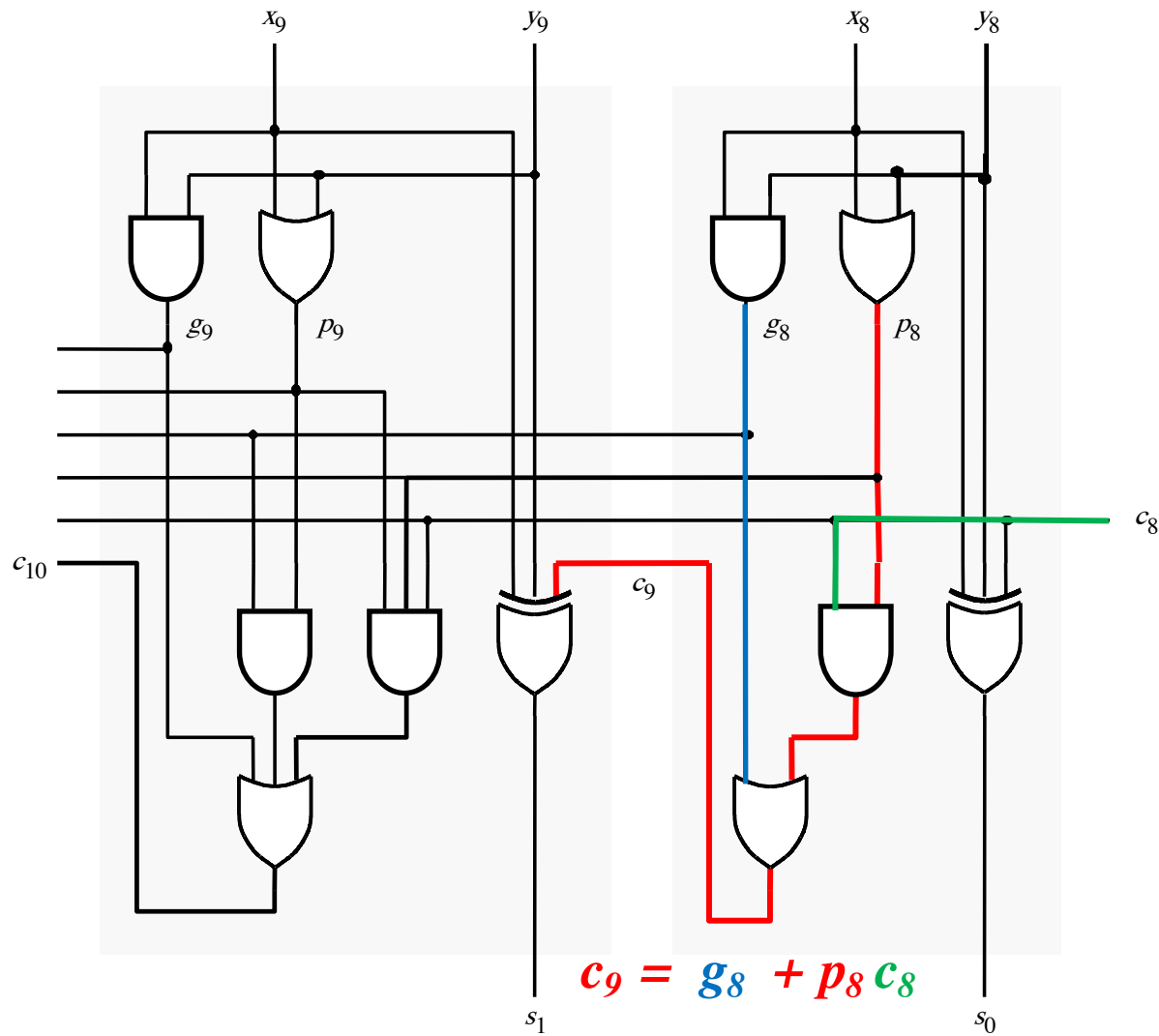
2 more gate delays for the internal carries within a block



Hierarchical Carry- Lookahead Adder (Carry Logic)

- C8** – 4 gate delays
- C16** – 5 gate delays
- C24** – 5 Gate delays
- C32** – 5 Gate delays

SECOND
LEVEL
HIERARCHY

  

FIRST LEVEL HIERARCHY

Hierarchical Carry-Lookahead Adder (Critical Path)


SECOND LEVEL HIERARCHY

C1 - 3 gate delays

C9 - 6 gate delays

C17 - 7 gate delays

C25 - 7 Gate delays

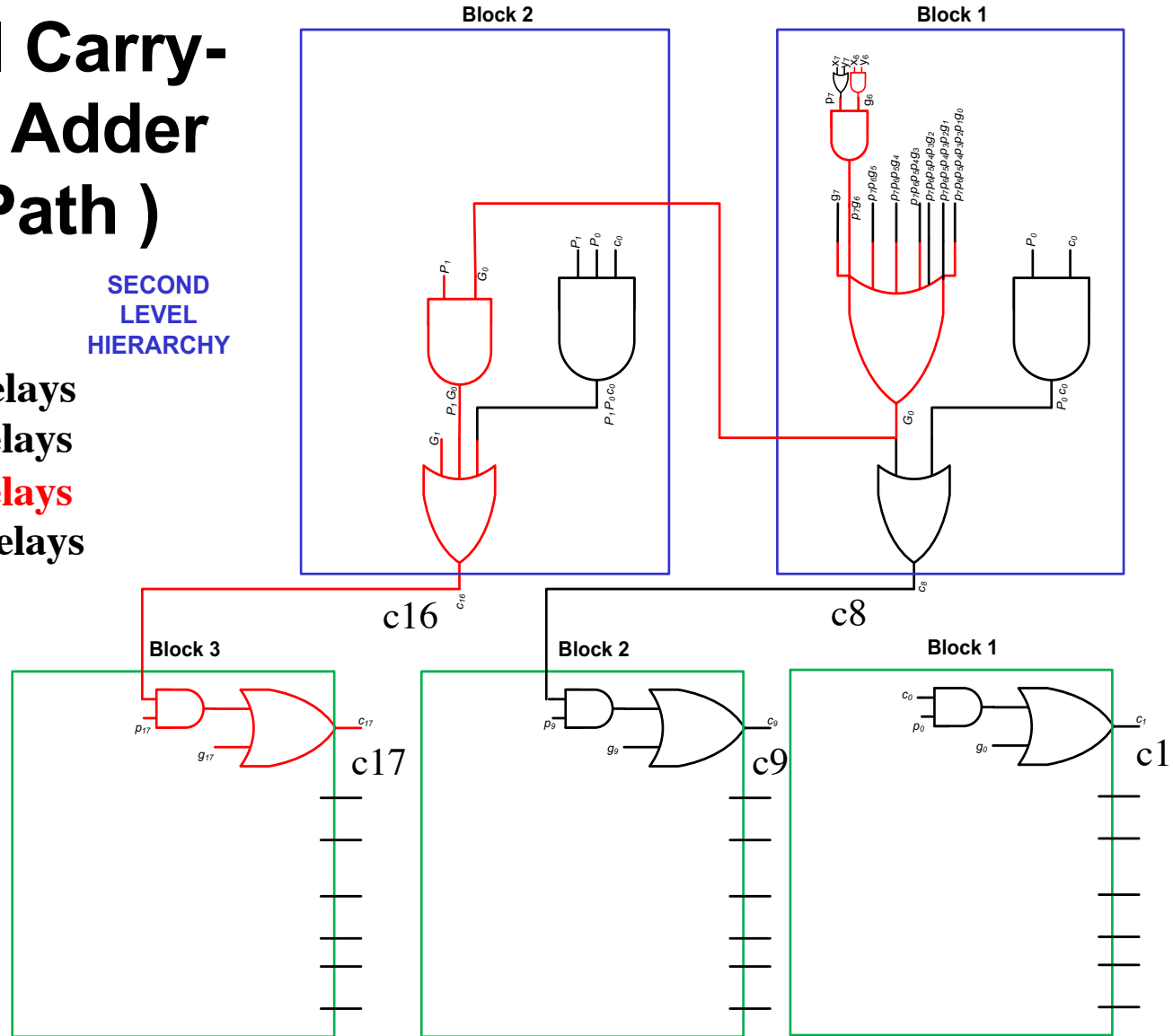

FIRST LEVEL HIERARCHY

Total Gate Delay Through a Hierarchical Carry-Lookahead Adder

- The total delay is **8 gates**:
 - 3 to generate all G_i and P_i signals
 - +2 to generate c_8 , c_{16} , c_{24} , and c_{32}
 - +2 to generate internal carries in the blocks
 - +1 to generate the sum bits (one extra XOR)

Questions?

THE END