

CprE 2810: Digital Logic

Instructor: Alexander Stoytchev

<http://www.ece.iastate.edu/~alexs/classes/>

Multiplexers

*CprE 281: Digital Logic
Iowa State University, Ames, IA
Copyright © Alexander Stoytchev*

Administrative Stuff


- **HW 6 is due on Monday Oct 14 @ 10pm**
- **HW 7 is due on Monday Oct 21 @ 10pm**
- **Next week: Lab 6**
- **Midterm progress report grades are due next week**

2-to-1 Multiplexer

2-to-1 Multiplexer (Definition)

- **Has two inputs: x_1 and x_2**
- **Also has another input line s**
- **If $s=0$, then the output is equal to x_1**
- **If $s=1$, then the output is equal to x_2**

Graphical Symbol for a 2-to-1 Multiplexer

 


[Figure 2.33c from the textbook]

Analogy: Railroad Switch




http://en.wikipedia.org/wiki/Railroad_switch

Analogy: Railroad Switch

 

Analogy: Railroad Switch

 

This is not a perfect analogy because the trains can go in either direction, while the multiplexer would only allow them to go from top to bottom.

http://en.wikipedia.org/wiki/Railroad_switch]

Truth Table for a 2-to-1 Multiplexer

s x_1 x_2	$f(s, x_1, x_2)$
0 0 0	0
0 0 1	0
0 1 0	1
0 1 1	1
1 0 0	0
1 0 1	1
1 1 0	0
1 1 1	1

[Figure 2.33a from the textbook]

Let's Derive the SOP form

$s \ x_1 \ x_2$	$f(s, x_1, x_2)$
0 0 0	0
0 0 1	0
0 1 0	1
0 1 1	1
1 0 0	0
1 0 1	1
1 1 0	0
1 1 1	1

Let's Derive the SOP form

$s \ x_1 \ x_2$	$f(s, x_1, x_2)$
0 0 0	0
0 0 1	0
0 1 0	1
0 1 1	1
1 0 0	0
1 0 1	1
1 1 0	0
1 1 1	1

Let's Derive the SOP form

$s \ x_1 \ x_2$	$f(s, x_1, x_2)$
0 0 0	0
0 0 1	0
0 1 0	1
0 1 1	1
1 0 0	0
1 0 1	1
1 1 0	0
1 1 1	1

Where should we
put the negation signs?

$s \ x_1 \ x_2$

$s \ x_1 \ x_2$

$s \ x_1 \ x_2$

$s \ x_1 \ x_2$

Let's Derive the SOP form

$s \ x_1 \ x_2$	$f(s, x_1, x_2)$	
0 0 0	0	
0 0 1	0	
0 1 0	1	$\bar{s} \ x_1 \ \bar{x}_2$
0 1 1	1	$\bar{s} \ x_1 \ x_2$
1 0 0	0	
1 0 1	1	$s \ \bar{x}_1 \ x_2$
1 1 0	0	
1 1 1	1	$s \ x_1 \ x_2$

Let's Derive the SOP form

$s \ x_1 \ x_2$	$f(s, x_1, x_2)$	
0 0 0	0	
0 0 1	0	
0 1 0	1	$\bar{s} x_1 \bar{x}_2$
0 1 1	1	$\bar{s} x_1 x_2$
1 0 0	0	
1 0 1	1	$s \bar{x}_1 x_2$
1 1 0	0	
1 1 1	1	$s x_1 x_2$

$$f(s, x_1, x_2) = \bar{s} x_1 \bar{x}_2 + \bar{s} x_1 x_2 + s \bar{x}_1 x_2 + s x_1 x_2$$

Let's simplify this expression

$$f(s, x_1, x_2) = \bar{s} x_1 \bar{x}_2 + \bar{s} x_1 x_2 + s \bar{x}_1 x_2 + s x_1 x_2$$

Let's simplify this expression

$$f(s, x_1, x_2) = \bar{s} x_1 \bar{x}_2 + \bar{s} x_1 x_2 + s \bar{x}_1 x_2 + s x_1 x_2$$

$$f(s, x_1, x_2) = \bar{s} x_1 (\bar{x}_2 + x_2) + s (\bar{x}_1 + x_1) x_2$$


Let's simplify this expression

$$f(s, x_1, x_2) = \bar{s} x_1 \bar{x}_2 + \bar{s} x_1 x_2 + s \bar{x}_1 x_2 + s x_1 x_2$$


$$f(s, x_1, x_2) = \bar{s} x_1 (\bar{x}_2 + x_2) + s (\bar{x}_1 + x_1) x_2$$

$$f(s, x_1, x_2) = \bar{s} x_1 + s x_2$$

Circuit for 2-1 Multiplexer

 


(b) Circuit

 

 
(c) Graphical symbol

$$f(s, x_1, x_2) = \bar{s}x_1 + sx_2$$


Analysis of the 2-to-1 Multiplexer (when the input $s=0$)



 
Analysis of the 2-to-1 Multiplexer (when the input $s=1$)



 Analysis of the 2-to-1 Multiplexer (when the input $s=0$)



 Analysis of the 2-to-1 Multiplexer (when the input $s=1$)



More Compact Truth-Table Representation

$s \ x_1 \ x_2$	$f(s, x_1, x_2)$
0 0 0	0
0 0 1	0
0 1 0	1
0 1 1	1
1 0 0	0
1 0 1	1
1 1 0	0
1 1 1	1

(a) Truth table


s	$f(s, x_1, x_2)$
0	x_1
1	x_2

4-to-1 Multiplexer

4-to-1 Multiplexer (Definition)

- Has four inputs: w_0 , w_1 , w_2 , w_3
- Also has two select lines: s_1 and s_0
- If $s_1=0$ and $s_0=0$, then the output f is equal to w_0
- If $s_1=0$ and $s_0=1$, then the output f is equal to w_1
- If $s_1=1$ and $s_0=0$, then the output f is equal to w_2
- If $s_1=1$ and $s_0=1$, then the output f is equal to w_3

Graphical Symbol and Truth Table

 

(a) Graphic symbol

s_1	s_0	f
0	0	w_0
0	1	w_1
1	0	w_2
1	1	w_3

(b) Truth table

The long-form truth table

The long-form truth table

$S_1 S_0$	$I_3 I_2 I_1 I_0$	F	$S_1 S_0$	$I_3 I_2 I_1 I_0$	F	$S_1 S_0$	$I_3 I_2 I_1 I_0$	F	$S_1 S_0$	$I_3 I_2 I_1 I_0$	F
0 0	0 0 0 0	0	0 1	0 0 0 0	0	1 0	0 0 0 0	0	1 1	0 0 0 0	0
	0 0 0 1	1		0 0 0 1	0		0 0 0 1	0		0 0 0 1	0
	0 0 1 0	0		0 0 1 0	1		0 0 1 0	0		0 0 1 0	0
	0 0 1 1	1		0 0 1 1	1		0 0 1 1	0		0 0 1 1	0
	0 1 0 0	0		0 1 0 0	0		0 1 0 0	1		0 1 0 0	0
	0 1 0 1	1		0 1 0 1	0		0 1 0 1	1		0 1 0 1	0
	0 1 1 0	0		0 1 1 0	1		0 1 1 0	1		0 1 1 0	0
	0 1 1 1	1		0 1 1 1	1		0 1 1 1	1		0 1 1 1	0
	1 0 0 0	0		1 0 0 0	0		1 0 0 0	0		1 0 0 0	1
	1 0 0 1	1		1 0 0 1	0		1 0 0 1	0		1 0 0 1	1
	1 0 1 0	0		1 0 1 0	1		1 0 1 0	0		1 0 1 0	1
	1 0 1 1	1		1 0 1 1	1		1 0 1 1	0		1 0 1 1	1
	1 1 0 0	0		1 1 0 0	0		1 1 0 0	1		1 1 0 0	1
	1 1 0 1	1		1 1 0 1	0		1 1 0 1	1		1 1 0 1	1
	1 1 1 0	0		1 1 1 0	1		1 1 1 0	1		1 1 1 0	1
	1 1 1 1	1		1 1 1 1	1		1 1 1 1	1		1 1 1 1	1

[<http://www.absoluteastronomy.com/topics/Multiplexer>]

The long-form truth table

$S_1 S_0$	I_3	I_2	I_1	I_0	F	$S_1 S_0$	I_3	I_2	I_1	I_0	F	$S_1 S_0$	I_3	I_2	I_1	I_0	F	$S_1 S_0$	I_3	I_2	I_1	I_0	F
0 0	0	0	0	0	0	0 1	0	0	0	0	0	1 0	0	0	0	0	0	1 1	0	0	0	0	0
	0	0	0	1	1		0	0	0	1	0		0	0	0	1	0		0	0	0	1	0
	0	0	1	0	0		0	0	1	0	1		0	0	1	0	0		0	0	1	0	0
	0	0	1	1	1		0	0	1	1	1		0	0	1	1	0		0	0	1	1	0
	0	1	0	0	0		0	1	0	0	0		0	1	0	0	1		0	1	0	0	0
	0	1	0	1	1		0	1	0	1	0		0	1	0	1	1		0	1	0	1	0
	0	1	1	0	0		0	1	1	0	1		0	1	1	0	1		0	1	1	0	0
	0	1	1	1	1		0	1	1	1	1		0	1	1	1	1		0	1	1	1	0
	1	0	0	0	0		1	0	0	0	0		1	0	0	0	0		1	0	0	0	1
	1	0	0	1	1		1	0	0	1	0		1	0	0	1	0		1	0	0	1	1
	1	0	1	0	0		1	0	1	0	1		1	0	1	0	0		1	0	1	0	1
	1	0	1	1	1		1	0	1	1	1		1	0	1	1	0		1	0	1	1	1
	1	1	0	0	0		1	1	0	0	0		1	1	0	0	1		1	1	0	0	1
	1	1	0	1	1		1	1	0	1	0		1	1	0	1	1		1	1	0	1	1
	1	1	1	0	0		1	1	1	0	1		1	1	1	0	1		1	1	1	0	1
	1	1	1	1	1		1	1	1	1	1		1	1	1	1	1		1	1	1	1	1

identical

[<http://www.absoluteastronomy.com/topics/Multiplexer>]

The long-form truth table

$S_1 S_0$	I_3	I_2	I_1	I_0	F	$S_1 S_0$	I_3	I_2	I_1	I_0	F	$S_1 S_0$	I_3	I_2	I_1	I_0	F	$S_1 S_0$	I_3	I_2	I_1	I_0	F
0 0	0	0	0	0	0	0 1	0	0	0	0	0	1 0	0	0	0	0	0	1 1	0	0	0	0	0
	0	0	0	1	1		0	0	0	1	0		0	0	0	1	0		0	0	0	1	0
	0	0	1	0	0		0	0	1	0	1		0	0	1	0	0		0	0	1	0	0
	0	0	1	1	1		0	0	1	1	1		0	0	1	1	0		0	0	1	1	0
	0	1	0	0	0		0	1	0	0	0		0	1	0	0	1		0	1	0	0	0
	0	1	0	1	1		0	1	0	1	0		0	1	0	1	1		0	1	0	1	0
	0	1	1	0	0		0	1	1	0	1		0	1	1	0	1		0	1	1	0	0
	0	1	1	1	1		0	1	1	1	1		0	1	1	1	1		0	1	1	1	0
	1	0	0	0	0		1	0	0	0	0		1	0	0	0	0		1	0	0	0	1
	1	0	0	1	1		1	0	0	1	0		1	0	0	1	0		1	0	0	1	1
	1	0	1	0	0		1	0	1	0	1		1	0	1	0	0		1	0	1	0	1
	1	0	1	1	1		1	0	1	1	1		1	0	1	1	0		1	0	1	1	1
	1	1	0	0	0		1	1	0	0	0		1	1	0	0	1		1	1	0	0	1
	1	1	0	1	1		1	1	0	1	0		1	1	0	1	1		1	1	0	1	1
	1	1	1	0	0		1	1	1	0	1		1	1	1	0	1		1	1	1	0	1
	1	1	1	1	1		1	1	1	1	1		1	1	1	1	1		1	1	1	1	1

identical

[<http://www.absoluteastronomy.com/topics/Multiplexer>]

The long-form truth table

$S_1 S_0$	$I_3 I_2 I_1 I_0$	F	$S_1 S_0$	$I_3 I_2 I_1 I_0$	F	$S_1 S_0$	$I_3 I_2 I_1 I_0$	F	$S_1 S_0$	$I_3 I_2 I_1 I_0$	F
0 0	0 0 0 0	0	0 1	0 0 0 0	0	1 0	0 0 0 0	0	1 1	0 0 0 0	0
	0 0 0 1	1		0 0 0 1	0		0 0 0 1	0		0 0 0 1	0
	0 0 1 0	0		0 0 1 0	1		0 0 1 0	0		0 0 1 0	0
	0 0 1 1	1		0 0 1 1	1		0 0 1 1	0		0 0 1 1	0
	0 1 0 0	0		0 1 0 0	0		0 1 0 0	1		0 1 0 0	0
	0 1 0 1	1		0 1 0 1	0		0 1 0 1	1		0 1 0 1	0
	0 1 1 0	0		0 1 1 0	1		0 1 1 0	1		0 1 1 0	0
	0 1 1 1	1		0 1 1 1	1		0 1 1 1	1		0 1 1 1	0
	1 0 0 0	0		1 0 0 0	0		1 0 0 0	0		1 0 0 0	1
	1 0 0 1	1		1 0 0 1	0		1 0 0 1	0		1 0 0 1	1
	1 0 1 0	0		1 0 1 0	1		1 0 1 0	0		1 0 1 0	1
	1 0 1 1	1		1 0 1 1	1		1 0 1 1	0		1 0 1 1	1
	1 1 0 0	0		1 1 0 0	0		1 1 0 0	1		1 1 0 0	1
	1 1 0 1	1		1 1 0 1	0		1 1 0 1	1		1 1 0 1	1
	1 1 1 0	0		1 1 1 0	1		1 1 1 0	1		1 1 1 0	1
	1 1 1 1	1		1 1 1 1	1		1 1 1 1	1		1 1 1 1	1

identical


[<http://www.absoluteastronomy.com/topics/Multiplexer>]

The long-form truth table

$S_1 S_0$	$I_3 I_2 I_1 I_0$	F	$S_1 S_0$	$I_3 I_2 I_1 I_0$	F	$S_1 S_0$	$I_3 I_2 I_1 I_0$	F	$S_1 S_0$	$I_3 I_2 I_1 I_0$	F
0 0	0 0 0 0	0	0 1	0 0 0 0	0	1 0	0 0 0 0	0	1 1	0 0 0 0	0
	0 0 0 1	1		0 0 0 1	0		0 0 0 1	0		0 0 0 1	0
	0 0 1 0	0		0 0 1 0	1		0 0 1 0	0		0 0 1 0	0
	0 0 1 1	1		0 0 1 1	1		0 0 1 1	0		0 0 1 1	0
	0 1 0 0	0		0 1 0 0	0		0 1 0 0	1		0 1 0 0	0
	0 1 0 1	1		0 1 0 1	0		0 1 0 1	1		0 1 0 1	0
	0 1 1 0	0		0 1 1 0	1		0 1 1 0	1		0 1 1 0	0
	0 1 1 1	1		0 1 1 1	1		0 1 1 1	1		0 1 1 1	0
	1 0 0 0	0		1 0 0 0	0		1 0 0 0	0		1 0 0 0	1
	1 0 0 1	1		1 0 0 1	0		1 0 0 1	0		1 0 0 1	1
	1 0 1 0	0		1 0 1 0	1		1 0 1 0	0		1 0 1 0	1
	1 0 1 1	1		1 0 1 1	1		1 0 1 1	0		1 0 1 1	1
	1 1 0 0	0		1 1 0 0	0		1 1 0 0	1		1 1 0 0	1
	1 1 0 1	1		1 1 0 1	0		1 1 0 1	1		1 1 0 1	1
	1 1 1 0	0		1 1 1 0	1		1 1 1 0	1		1 1 1 0	1
	1 1 1 1	1		1 1 1 1	1		1 1 1 1	1		1 1 1 1	1

identical

Graphical Symbol and Truth Table

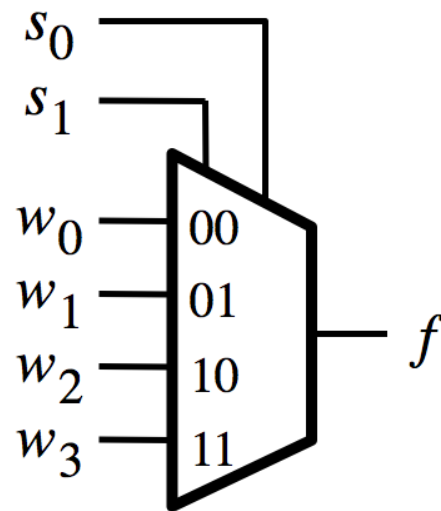


(a) Graphic symbol

s_1	s_0	f
0	0	w_0
0	1	w_1
1	0	w_2
1	1	w_3

(b) Truth table


4-to-1 Multiplexer (SOP circuit)

 


$$f = \overline{s_1} \overline{s_0} w_0 + \overline{s_1} s_0 w_1 + s_1 \overline{s_0} w_2 + s_1 s_0 w_3$$

[Figure 4.2c from the textbook]

 
Analysis of the 4-to-1 Multiplexer ($s_1=0$ and $s_0=0$)



 
Analysis of the 4-to-1 Multiplexer ($s_1=0$ and $s_0=0$)



 
Analysis of the 4-to-1 Multiplexer ($s_1=0$ and $s_0=0$)



 
Analysis of the 4-to-1 Multiplexer ($s_1=0$ and $s_0=0$)



 
Analysis of the 4-to-1 Multiplexer ($s_1=0$ and $s_0=1$)



 
Analysis of the 4-to-1 Multiplexer ($s_1=1$ and $s_0=0$)



 
Analysis of the 4-to-1 Multiplexer ($s_1=1$ and $s_0=1$)



 
Analysis of the 4-to-1 Multiplexer ($s_1=0$ and $s_0=0$)



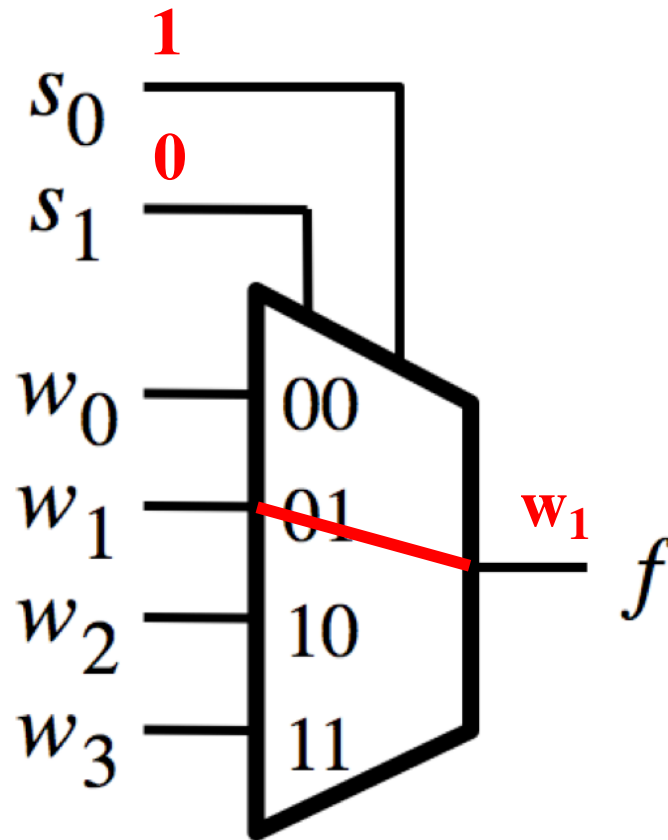
Analysis of the 4-to-1 Multiplexer ($s_1=0$ and $s_0=1$)



 
Analysis of the 4-to-1 Multiplexer ($s_1=1$ and $s_0=0$)



 Analysis of the 4-to-1 Multiplexer ($s_1=1$ and $s_0=1$)



Using three 2-to-1 multiplexers to build one 4-to-1 multiplexer

 




[Figure 4.3 from the textbook]

Analogy: Railroad Switches





http://en.wikipedia.org/wiki/Railroad_switch]

Analogy: Railroad Switches

   


http://en.wikipedia.org/wiki/Railroad_switch

Analogy: Railroad Switches

  

S_0


 
these two
switches are
controlled
together




S_1

http://en.wikipedia.org/wiki/Railroad_switch]

  
Using three 2-to-1 multiplexers to build one 4-to-1 multiplexer



 
Using three 2-to-1 multiplexers to build one 4-to-1 multiplexer



 
Using three 2-to-1 multiplexers to build one 4-to-1 multiplexer



 
Using three 2-to-1 multiplexers to build one 4-to-1 multiplexer



 That is different from the SOP form of the 4-to-1 multiplexer shown below, which uses fewer gates




Analysis of the Hierarchical Implementation ($s_1=0$ and $s_0=0$)

 


[Figure 4.3 from the textbook]

Analysis of the Hierarchical Implementation ($s_1=0$ and $s_0=1$)

 


[Figure 4.3 from the textbook]

Analysis of the Hierarchical Implementation ($s_1=1$ and $s_0=0$)

 

[Figure 4.3 from the textbook]


Analysis of the Hierarchical Implementation ($s_1=1$ and $s_0=1$)

 

[Figure 4.3 from the textbook]


16-to-1 Multiplexer

16-1 Multiplexer

 


[Figure 4.4 from the textbook]


16-1 Multiplexer

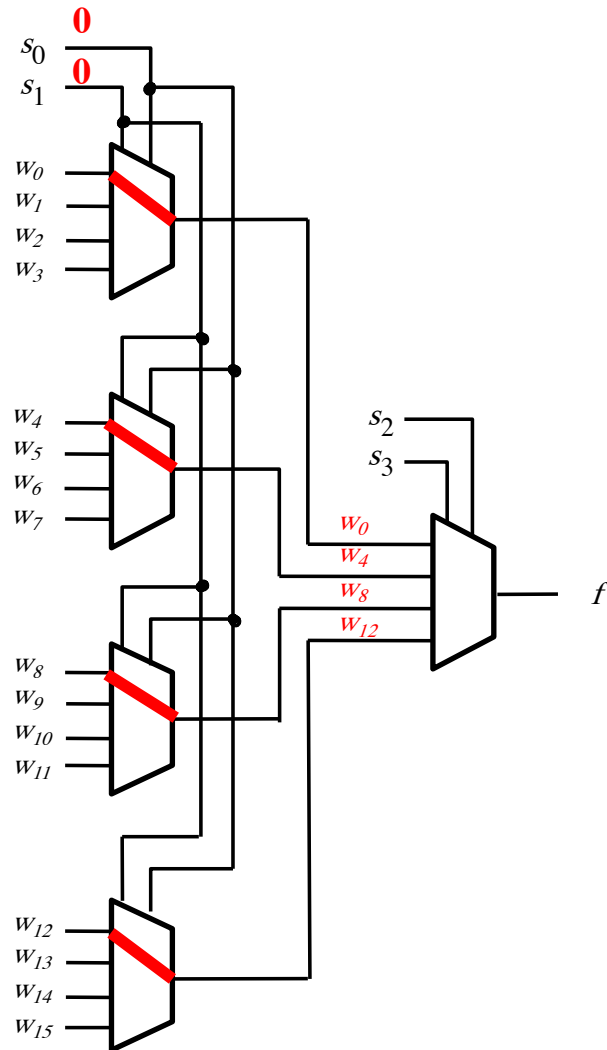


16-1 Multiplexer

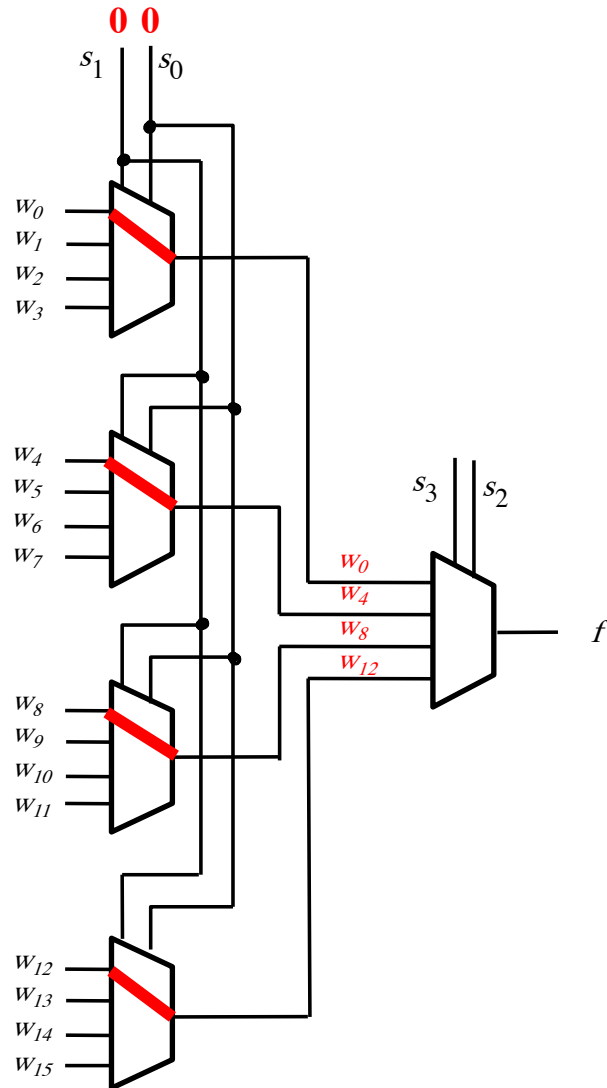


16-1 Multiplexer

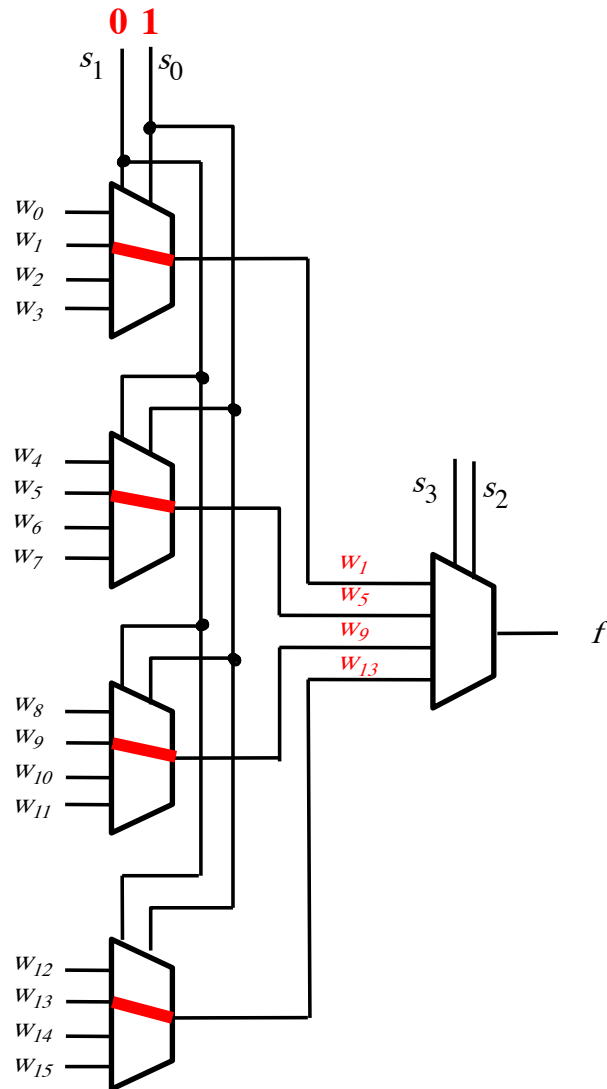


16-1 Multiplexer

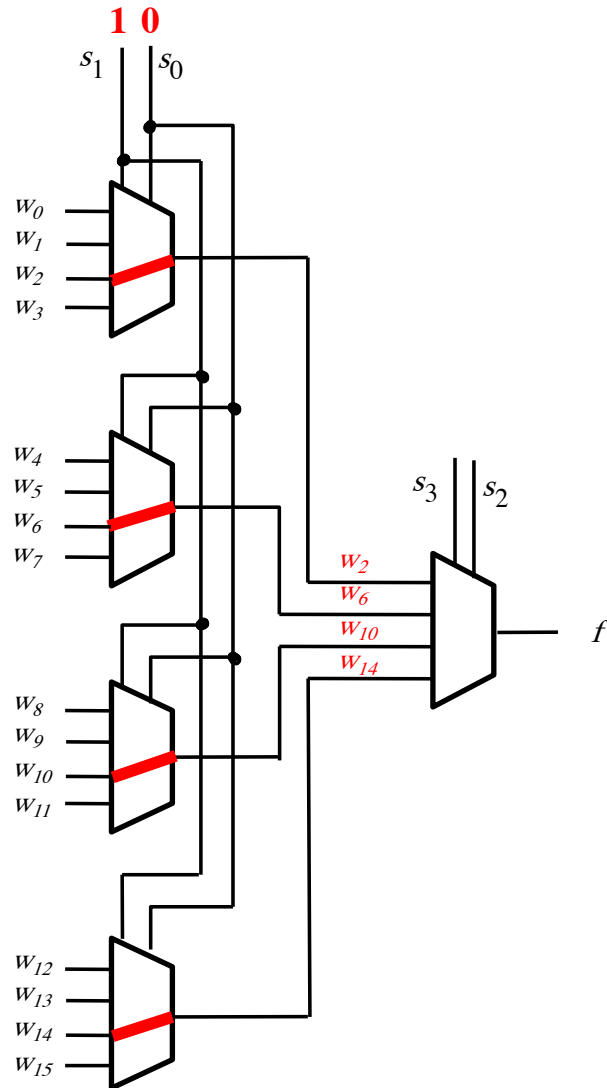


16-1 Multiplexer

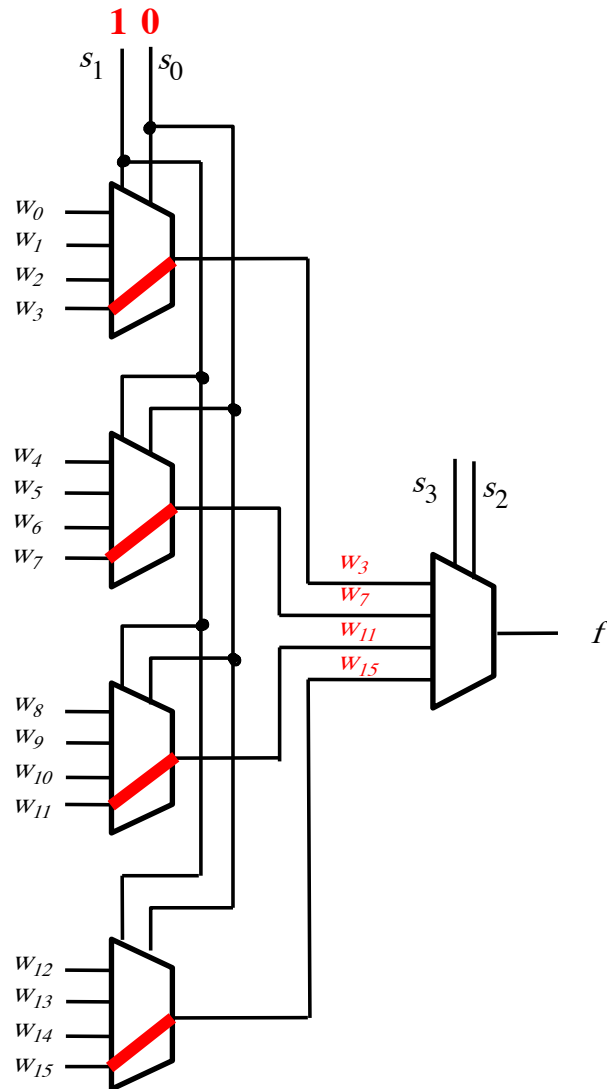


16-1 Multiplexer

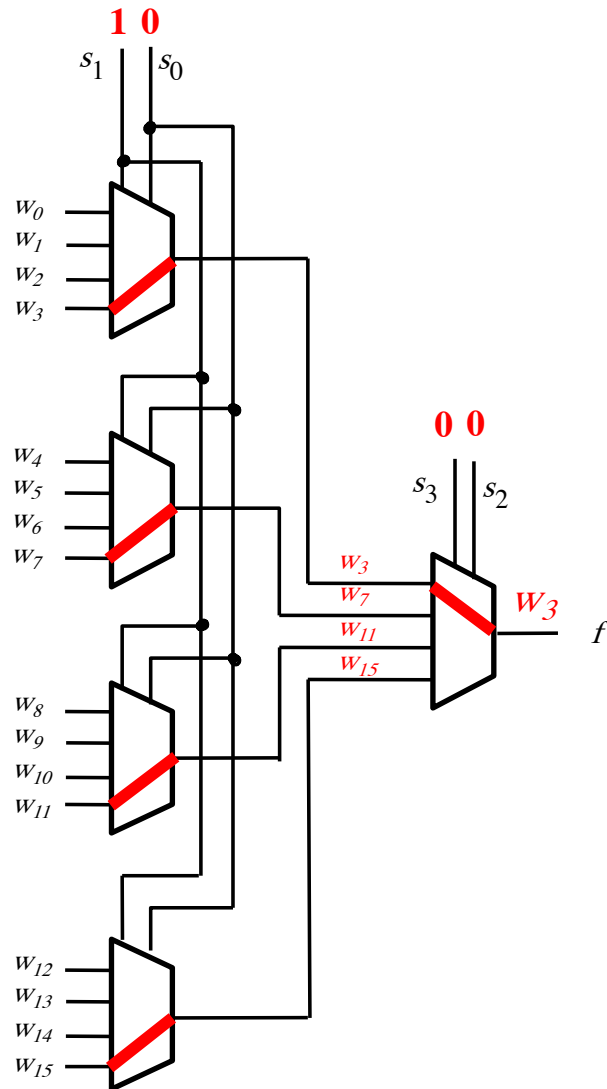


16-1 Multiplexer

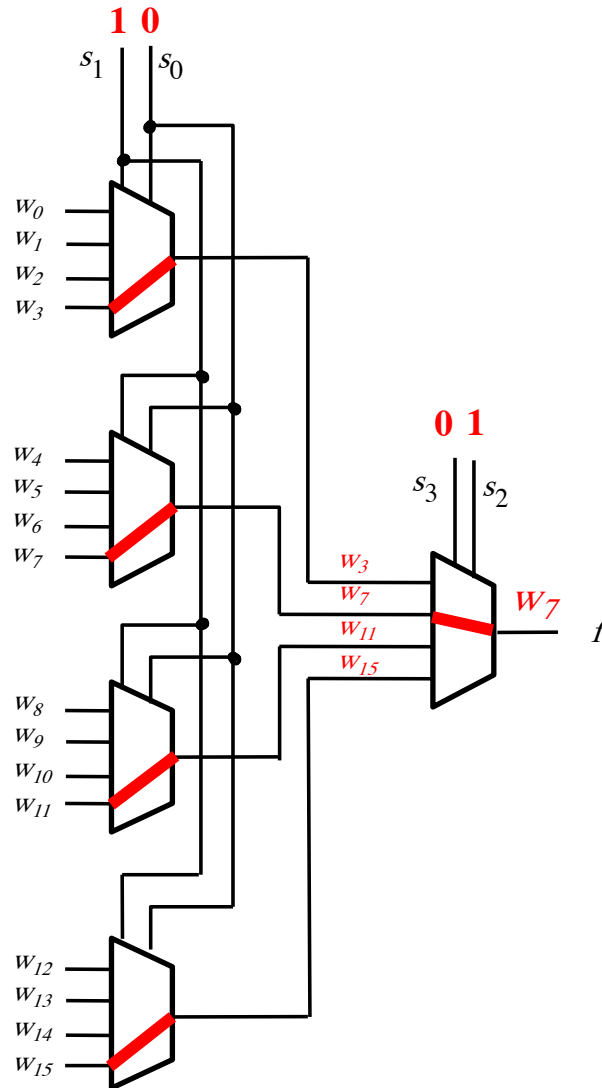

16-1 Multiplexer

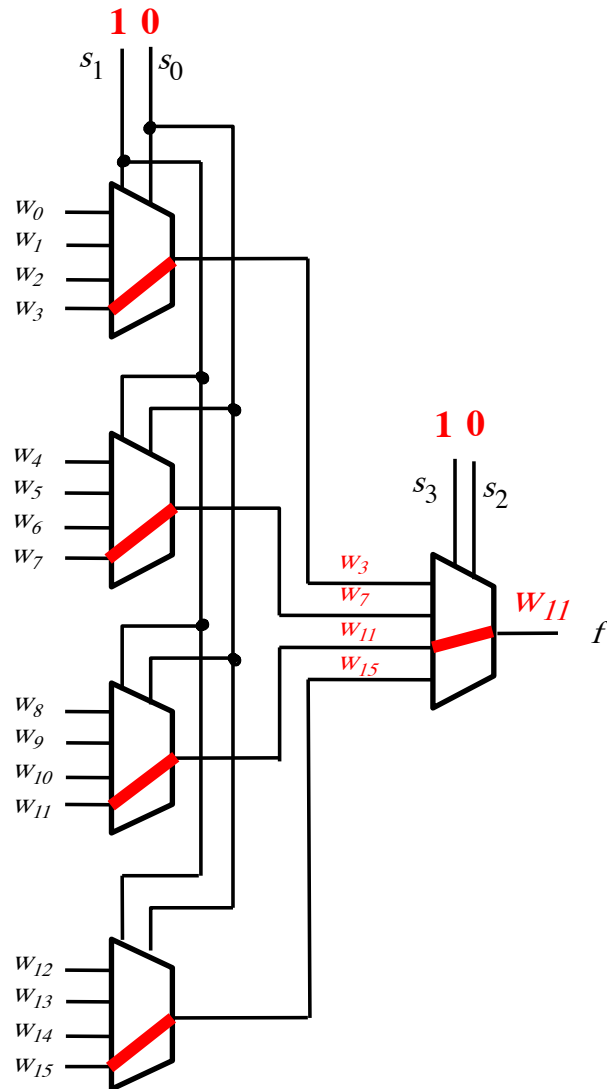

16-1 Multiplexer

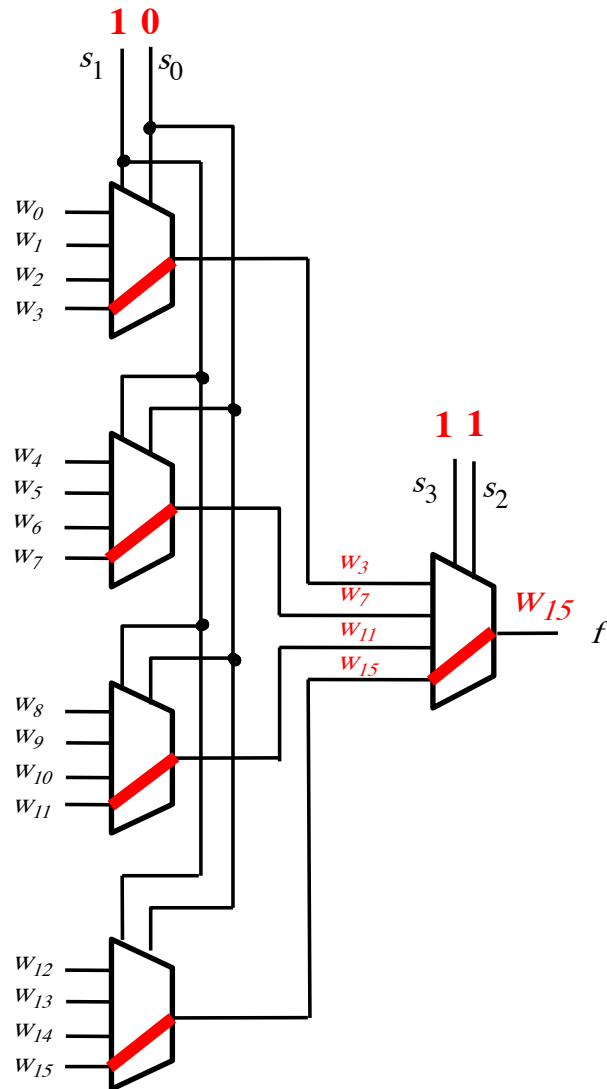





[<http://upload.wikimedia.org/wikipedia/commons/2/26/SunsetTracksCrop.JPG>]

Multiplexers Are Special


The Three Basic Logic Gates

 

NOT gate

 


AND gate

 


OR gate

Truth Table for NOT

 


x	\bar{x}
0	1
1	0

Truth Table for AND

 


x_1	x_2	$x_1 \cdot x_2$
0	0	0
0	1	0
1	0	0
1	1	1

Truth Table for OR

 


x_1	x_2	$x_1 + x_2$
0	0	0
0	1	1
1	0	1
1	1	1



Building an AND Gate with 4-to-1 Mux

 

x_1	x_2	$x_1 \cdot x_2$
0	0	0
0	1	0
1	0	0
1	1	1

 


Building an AND Gate with 4-to-1 Mux

  

These two are the same.


Building an AND Gate with 4-to-1 Mux

 


These two are the same.

And so are these two.


Building an OR Gate with 4-to-1 Mux

 


x_1	x_2	$x_1 + x_2$
0	0	0
0	1	1
1	0	1
1	1	1

 

Building an OR Gate with 4-to-1 Mux

 


x_1	x_2	$x_1 + x_2$
0	0	0
0	1	1
1	0	1
1	1	1

 


These two are the same.

Building an OR Gate with 4-to-1 Mux

 


x_1	x_2	$x_1 + x_2$
0	0	0
0	1	1
1	0	1
1	1	1

 


These two are the same.

And so are these two.


Building a NOT Gate with 4-to-1 Mux

 


x	\bar{x}
0	1
1	0

 

Building a NOT Gate with 4-to-1 Mux

 


x	y	f
0	0	1
0	1	1
1	0	0
1	1	0

 


Introduce a dummy variable y .


Building a NOT Gate with 4-to-1 Mux

 


x	y	f
0	0	1
0	1	1
1	0	0
1	1	0

 

Building a NOT Gate with 4-to-1 Mux

 


x	y	f
0	0	1
0	1	1
1	0	0
1	1	0


 


Now set y to either 0 or 1 (both will work). Why?

Building a NOT Gate with 4-to-1 Mux

 

x	\bar{x}
0	1
1	0

  


Two alternative solutions.


Implications

**Any Boolean function can be implemented
using only 4-to-1 multiplexers!**


Building an AND Gate with **2-to-1** Mux

 


x_1	x_2	$x_1 \cdot x_2$
0	0	0
0	1	0
1	0	0
1	1	1

 


Building an AND Gate with 2-to-1 Mux

 

x_1	x_2	$x_1 \cdot x_2$
0	0	0
0	1	0
1	0	0
1	1	1

 


Building an AND Gate with 2-to-1 Mux

 


x_1	x_2	$x_1 \cdot x_2$
0	0	0
0	1	0
1	0	0
1	1	1

 
Red annotations: A vertical red line is drawn between the x_2 and $x_1 \cdot x_2$ columns. A horizontal red line is drawn between the second and third rows. Red brackets on the right group the output values: the first two rows (0, 0) are grouped and labeled 0 ; the last two rows (0, 1) are grouped and labeled x_2 .




Building an OR Gate with 2-to-1 Mux

 


x_1	x_2	$x_1 + x_2$
0	0	0
0	1	1
1	0	1
1	1	1

 


Building an OR Gate with 2-to-1 Mux

 

x_1	x_2	$x_1 + x_2$
0	0	0
0	1	1
1	0	1
1	1	1

 


Building an OR Gate with 2-to-1 Mux

 


x_1	x_2	$x_1 + x_2$
0	0	0
0	1	1
1	0	1
1	1	1

 
Red annotations: A vertical red line is drawn between the x_1 and x_2 columns. A horizontal red line is drawn between the second and third rows. Red curly braces on the right group the output values: the first two rows (0 and 1) are grouped and labeled x_2 , and the last two rows (1 and 1) are grouped and labeled 1.




Building a NOT Gate with 2-to-1 Mux

 


x	\bar{x}
0	1
1	0

 

Building a NOT Gate with 2-to-1 Mux

 


x	\bar{x}
0	1
1	0

 


Implications

**Any Boolean function can be implemented
using only 2-to-1 multiplexers!**


AND

 


OR

 


NOT

 


AND

 


OR

 


NOT

 


AND

 

OR

 


NOT

 



Switch Circuit

2 x 2 Crossbar switch

 


[Figure 4.5a from the textbook]

2 x 2 Crossbar switch

  


Implementation of a 2 x 2 crossbar switch with multiplexers

 


[Figure 4.5b from the textbook]

Implementation of a 2 x 2 crossbar switch with multiplexers

 


[Figure 4.5b from the textbook]

Implementation of a 2 x 2 crossbar switch with multiplexers

 


[Figure 4.5b from the textbook]

Implementation of a 2 x 2 crossbar switch with multiplexers

 



[Figure 4.5b from the textbook]

Implementation of a 2 x 2 crossbar switch with multiplexers

 


[Figure 4.5b from the textbook]

  Implementation of a 2 x 2 crossbar switch with multiplexers



 Implementation of a 2 x 2 crossbar switch with multiplexers




Synthesis of Logic Circuits Using Multiplexers

Synthesis of Logic Circuits Using Multiplexers

**Note: This method is NOT the same as simply replacing each logic gate with a multiplexer!
It is a lot more efficient.**

The XOR Logic Gate

 


(a) Two switches that control a light

x	y	L
0	0	0
0	1	1
1	0	1
1	1	0

(b) Truth table


The XOR Logic Gate

 

(a) Two switches that control a light

x	y	L
0	0	0
0	1	1
1	0	1
1	1	0

(b) Truth table

 


(c) Logic network



(d) XOR gate symbol

Implementation of a logic function with a 4-to-1 multiplexer

w_1	w_2	f
0	0	0
0	1	1
1	0	1
1	1	0

 


[Figure 4.6a from the textbook]

Implementation of the same logic function with a 2-to-1 multiplexer

w_1	w_2	f
0	0	0
0	1	1
1	0	1
1	1	0


w_1	f
0	w_2
1	$\overline{w_2}$

(b) Modified truth table

 


 (c) Circuit


Implementation of the XOR Logic Gate with a 2-to-1 multiplexer and one NOT



 
Implementation of the XOR Logic Gate with a 2-to-1 multiplexer and one NOT





 
Implementation of the XOR Logic Gate with a 2-to-1 multiplexer and one NOT



 These two circuits are equivalent
(the wires of the bottom AND gate are flipped)



   **In other words,
all four of these are equivalent!**



Implementation of another logic function

w_1	w_2	w_3	f
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1


[Figure 4.7 from the textbook]

Implementation of another logic function

w_1	w_2	w_3	f
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

[Figure 4.7 from the textbook]

Implementation of another logic function

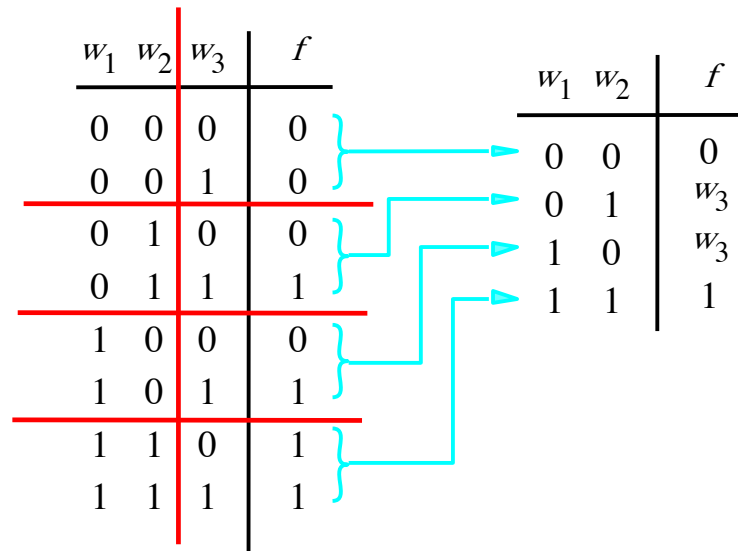


[Figure 4.7 from the textbook]

Implementation of another logic function

w_1	w_2	w_3	f
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

w_1	w_2	f
0	0	0
0	1	w_3
1	0	w_3
1	1	1

 

[Figure 4.7 from the textbook]

Another Example (3-input XOR)

Implementation of 3-input XOR with 2-to-1 Multiplexers

w_1	w_2	w_3	f
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

[Figure 4.8a from the textbook]

Implementation of 3-input XOR with 2-to-1 Multiplexers


w_1	w_2	w_3	f
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Red annotations in the original image: A red vertical line is drawn between the w_1 column and the w_2, w_3 columns. A red horizontal line is drawn between the $w_1 = 0$ rows and the $w_1 = 1$ rows. A red curly brace on the right side of the first four rows is labeled $w_2 \oplus w_3$. A red curly brace on the right side of the last four rows is labeled $\overline{w_2 \oplus w_3}$.

Implementation of 3-input XOR with 2-to-1 Multiplexers

w_1	w_2	w_3	f
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

(a) Truth table

 


(b) Circuit

Implementation of 3-input XOR with 2-to-1 Multiplexers

w_1	w_2	w_3	f
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

(a) Truth table

 

(b) Circuit

Implementation of 3-input XOR with a 4-to-1 Multiplexer

w_1	w_2	w_3	f
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

[Figure 4.9a from the textbook]

Implementation of 3-input XOR with a 4-to-1 Multiplexer

w_1	w_2	w_3	f
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

[Figure 4.9a from the textbook]

Implementation of 3-input XOR with a 4-to-1 Multiplexer


w_1	w_2	w_3	f
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

[Figure 4.9a from the textbook]

Implementation of 3-input XOR with a 4-to-1 Multiplexer

w_1	w_2	w_3	f
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

(a) Truth table

 

(b) Circuit

Multiplexor Synthesis Using Shannon's Expansion

Three-input majority function

w_1	w_2	w_3	f
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

[Figure 4.10a from the textbook]

Three-input majority function

w_1	w_2	w_3	f
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

w_1	f
0	
1	

[Figure 4.10a from the textbook]

Three-input majority function

w_1	w_2	w_3	f
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

w_1	f
0	$w_2 w_3$
1	$w_2 + w_3$

[Figure 4.10a from the textbook]


Three-input majority function

w_1	w_2	w_3	f
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

w_1	f
0	$w_2 w_3$
1	$w_2 + w_3$

The diagram shows a truth table for the three-input majority function. The first table lists all combinations of inputs w_1, w_2, w_3 and the output f . Red brackets group the rows where $w_1=0$ and $w_1=1$. Red arrows point from these groups to a second, simplified truth table. In the second table, for $w_1=0$, the output f is $w_2 w_3$. For $w_1=1$, the output f is $w_2 + w_3$.

(b) Truth table

 


(b) Circuit

[Figure 4.10a from the textbook]

Three-input majority function

$$f = \bar{w}_1 w_2 w_3 + w_1 \bar{w}_2 w_3 + w_1 w_2 \bar{w}_3 + w_1 w_2 w_3$$
 
$$\begin{aligned} f &= \bar{w}_1 (w_2 w_3) + w_1 (\bar{w}_2 w_3 + w_2 \bar{w}_3 + w_2 w_3) \\ &= \bar{w}_1 (w_2 w_3) + w_1 (w_2 + w_3) \end{aligned}$$



Shannon's Expansion Theorem

Any Boolean function $f(w_1, \dots, w_n)$ can be rewritten in the form:

$$f(w_1, w_2, \dots, w_n) = \bar{w}_1 \cdot f(0, w_2, \dots, w_n) + w_1 \cdot f(1, w_2, \dots, w_n)$$

Shannon's Expansion Theorem

Any Boolean function $f(w_1, \dots, w_n)$ can be rewritten in the form:

$$f(w_1, w_2, \dots, w_n) = \bar{w}_1 \cdot f(0, w_2, \dots, w_n) + w_1 \cdot f(1, w_2, \dots, w_n)$$

$$f = \bar{w}_1 f_{\bar{w}_1} + w_1 f_{w_1}$$

Shannon's Expansion Theorem

Any Boolean function $f(w_1, \dots, w_n)$ can be rewritten in the form:

$$f(w_1, w_2, \dots, w_n) = \bar{w}_1 \cdot f(0, w_2, \dots, w_n) + w_1 \cdot f(1, w_2, \dots, w_n)$$

$$f = \bar{w}_1 f_{\bar{w}_1} + w_1 f_{w_1}$$

cofactor

cofactor

Shannon's Expansion Theorem (Example)

$$f(w_1, w_2, w_3) = w_1w_2 + w_1w_3 + w_2w_3$$

Shannon's Expansion Theorem (Example)

$$f(w_1, w_2, w_3) = w_1w_2 + w_1w_3 + w_2w_3$$

$$f(w_1, w_2, w_3) = w_1w_2 + w_1w_3 + w_2w_3 (\overline{w_1} + w_1)$$

Shannon's Expansion Theorem (Example)

$$f(w_1, w_2, w_3) = w_1 w_2 + w_1 w_3 + w_2 w_3$$

$$f(w_1, w_2, w_3) = w_1 w_2 + w_1 w_3 + w_2 w_3 (\bar{w}_1 + w_1)$$


$$\begin{aligned} f &= \bar{w}_1(0 \cdot w_2 + 0 \cdot w_3 + w_2 w_3) + w_1(1 \cdot w_2 + 1 \cdot w_3 + w_2 w_3) \\ &= \bar{w}_1(w_2 w_3) + w_1(w_2 + w_3) \end{aligned}$$

Shannon's Expansion Theorem (Example)

$$f(w_1, w_2, w_3) = w_1w_2 + w_1w_3 + w_2w_3$$

$$f(w_1, w_2, w_3) = w_1w_2 + w_1w_3 + w_2w_3 (\bar{w}_1 + w_1)$$
 
$$\begin{aligned} f &= \bar{w}_1(0 \cdot w_2 + 0 \cdot w_3 + w_2w_3) + w_1(1 \cdot w_2 + 1 \cdot w_3 + w_2w_3) \\ &= \bar{w}_1(w_2w_3) + w_1(w_2 + w_3) \end{aligned}$$



Another Example

Factor and implement the following function with a 2-to-1 multiplexer


$$f = \bar{w}_1 \bar{w}_3 + w_1 w_2 + w_1 w_3$$

Factor and implement the following function with a 2-to-1 multiplexer

$$f = \bar{w}_1 \bar{w}_3 + w_1 w_2 + w_1 w_3$$

$$\begin{aligned} f &= \bar{w}_1 f_{\bar{w}_1} + w_1 f_{w_1} \\ &= \bar{w}_1 (\bar{w}_3) + w_1 (w_2 + w_3) \end{aligned}$$

 Factor and implement the following function with a 2-to-1 multiplexer



$$\begin{aligned} f &= \bar{w}_1 f_{\bar{w}_1} + w_1 f_{w_1} \\ &= \bar{w}_1 (\bar{w}_3) + w_1 (w_2 + w_3) \end{aligned}$$

[Figure 4.11a from the textbook]

Shannon's Expansion Theorem (In terms of more than one variable)

$$f(w_1, \dots, w_n) = \bar{w}_1 \bar{w}_2 \cdot f(0, 0, w_3, \dots, w_n) + \bar{w}_1 w_2 \cdot f(0, 1, w_3, \dots, w_n) \\ + w_1 \bar{w}_2 \cdot f(1, 0, w_3, \dots, w_n) + w_1 w_2 \cdot f(1, 1, w_3, \dots, w_n)$$

This form is suitable for implementation with a 4x1 multiplexer.

Factor and implement the following function with a 4-to-1 multiplexer

$$f = \bar{w}_1 \bar{w}_3 + w_1 w_2 + w_1 w_3$$

Factor and implement the following function with a 4-to-1 multiplexer

$$f = \bar{w}_1 \bar{w}_3 + w_1 w_2 + w_1 w_3$$

$$= \bar{w}_1 (\bar{w}_2 + w_2) \bar{w}_3 + w_1 w_2 + w_1 (\bar{w}_2 + w_2) w_3$$

Factor and implement the following function with a 4-to-1 multiplexer

$$f = \overline{w_1} \overline{w_3} + w_1 w_2 + w_1 w_3$$

$$= \overline{w_1} (\overline{w_2} + w_2) \overline{w_3} + w_1 w_2 + w_1 (\overline{w_2} + w_2) w_3$$

$$= \overline{w_1} \overline{w_2} \overline{w_3} + \overline{w_1} w_2 \overline{w_3} + w_1 w_2 + w_1 \overline{w_2} w_3 + w_1 w_2 w_3$$

$$= \overline{w_1} \overline{w_2} \overline{w_3} + \overline{w_1} w_2 \overline{w_3} + w_1 \overline{w_2} w_3 + w_1 w_2 (1 + w_3)$$

$$= \overline{w_1} \overline{w_2} (\overline{w_3}) + \overline{w_1} w_2 (\overline{w_3}) + w_1 \overline{w_2} (w_3) + w_1 w_2 (1)$$

Factor and implement the following function with a 4-to-1 multiplexer

$$f = \overline{w_1} \overline{w_3} + w_1 w_2 + w_1 w_3$$

$$= \overline{w_1} (\overline{w_2} + w_2) \overline{w_3} + w_1 w_2 + w_1 (\overline{w_2} + w_2) w_3$$

$$= \overline{w_1} \overline{w_2} \overline{w_3} + \overline{w_1} w_2 \overline{w_3} + w_1 w_2 + w_1 \overline{w_2} w_3 + w_1 w_2 w_3$$

$$= \overline{w_1} \overline{w_2} \overline{w_3} + \overline{w_1} w_2 \overline{w_3} + w_1 \overline{w_2} w_3 + w_1 w_2 (1 + w_3)$$

$$= \overline{w_1} \overline{w_2} (\overline{w_3}) + \overline{w_1} w_2 (\overline{w_3}) + w_1 \overline{w_2} (w_3) + w_1 w_2 (1)$$


these are the 4 cofactors

Factor and implement the following function with a 4-to-1 multiplexer

$$f = \bar{w}_1\bar{w}_3 + w_1w_2 + w_1w_3$$

$$\begin{aligned} f &= \bar{w}_1\bar{w}_2f_{\bar{w}_1\bar{w}_2} + \bar{w}_1w_2f_{\bar{w}_1w_2} + w_1\bar{w}_2f_{w_1\bar{w}_2} + w_1w_2f_{w_1w_2} \\ &= \bar{w}_1\bar{w}_2(\bar{w}_3) + \bar{w}_1w_2(\bar{w}_3) + w_1\bar{w}_2(w_3) + w_1w_2(1) \end{aligned}$$

 Factor and implement the following function with a 4-to-1 multiplexer



$$\begin{aligned}
 f &= \bar{w}_1 \bar{w}_2 f_{\bar{w}_1 \bar{w}_2} + \bar{w}_1 w_2 f_{\bar{w}_1 w_2} + w_1 \bar{w}_2 f_{w_1 \bar{w}_2} + w_1 w_2 f_{w_1 w_2} \\
 &= \bar{w}_1 \bar{w}_2 (\bar{w}_3) + \bar{w}_1 w_2 (\bar{w}_3) + w_1 \bar{w}_2 (w_3) + w_1 w_2 (1)
 \end{aligned}$$

[Figure 4.11b from the textbook]

Yet Another Example

Factor and implement the following function using only 2-to-1 multiplexers

$$f = w_1 w_2 + w_1 w_3 + w_2 w_3$$

Factor and implement the following function using only 2-to-1 multiplexers

$$f = w_1w_2 + w_1w_3 + w_2w_3$$

$$\begin{aligned} f &= \bar{w}_1(w_2w_3) + w_1(w_2 + w_3 + w_2w_3) \\ &= \bar{w}_1(w_2w_3) + w_1(w_2 + w_3) \end{aligned}$$

Factor and implement the following function using only 2-to-1 multiplexers


$$f = w_1 w_2 + w_1 w_3 + w_2 w_3$$

$$f = \bar{w}_1 (w_2 w_3) + w_1 (w_2 + w_3 + w_2 w_3)$$

$$= \bar{w}_1 \underbrace{(w_2 w_3)}_g + w_1 \underbrace{(w_2 + w_3)}_h$$

$$g = w_2 w_3 \quad h = w_2 + w_3$$

 Factor and implement the following function using only 2-to-1 multiplexers



$$f = \bar{w}_1(w_2w_3) + w_1(w_2 + w_3 + w_2w_3)$$

$$= \bar{w}_1(\underbrace{w_2w_3}_g) + w_1(\underbrace{w_2 + w_3}_h)$$

$$g = w_2w_3 \quad h = w_2 + w_3$$

Factor and implement the following function using only 2-to-1 multiplexers

$$g = w_2 w_3$$

$$h = w_2 + w_3$$

Factor and implement the following function using only 2-to-1 multiplexers

$$g = w_2 w_3$$





$$g = \bar{w}_2(0) + w_2(w_3)$$

$$h = w_2 + w_3$$



$$h = \bar{w}_2(w_3) + w_2(1)$$

  
Factor and implement the following function using only 2-to-1 multiplexers




$$g = \bar{w}_2(0) + w_2(w_3)$$

$$h = \bar{w}_2(w_3) + w_2(1)$$

 
Finally, we are ready to draw the circuit



 Finally, we are ready to draw the circuit



Finally, we are ready to draw the circuit

 

[Figure 4.12 from the textbook]

Questions?

THE END