

# **CprE 2810: Digital Logic**

**Instructor: Alexander Stoytchev**

**<http://www.ece.iastate.edu/~alexs/classes/>**

# D Flip-Flops


*CprE 2810: Digital Logic  
Iowa State University, Ames, IA  
Copyright © Alexander Stoytchev*

# **Administrative Stuff**


- **Homework 7 is due today**
- **Homework 8 is due on Monday Oct 28 @ 10pm.**

# **Quick Review**


# A simple memory element with NOT Gates

 


# A simple memory element with NOT Gates

 

# A simple memory element with NOT Gates

 


# A simple memory element with NOT Gates

 


The circuit will stay in this state indefinitely.




# A simple memory element with NOT Gates

 

# A simple memory element with NOT Gates

 

# A simple memory element with NOT Gates

 



The circuit will stay in this state indefinitely.

# A Strange Loop




[<http://animalsiadmire.blogspot.com/2011/07/stupid-snake-eating-itself.html>]

  
**This circuit can be in two possible states**



 **This circuit can be in two possible states**





used to store a 1

 


used to store a 0

  **This circuit can be in two possible states**



 
# A simple memory element with NAND Gates






# A simple memory element with NOR Gates

 


# Basic Latch


# A simple memory element with NOR Gates

 


# A simple memory element with NOR Gates

 

# A simple memory element with NOR Gates


 


# A memory element with NOR gates

 

[ Figure 5.3 from the textbook ]


# Two Different Ways to Draw the Same Circuit

  

[ Figure 5.3 & 5.4 from the textbook ]
 
# Circuit and Characteristic Table for the Basic Latch

Note that  $Q_a$  and  $Q_b$  are inverses of each other!




(a) Circuit

S	R	$Q_a$	$Q_b$	
0	0	0/1	1/0	(no change)
0	1	0	1	
1	0	1	0	
1	1	0	0	

(b) Characteristic table


 
# SR Latch: Circuit and Characteristic Table




(a) Circuit

S	R	$Q_a$	$Q_b$	
0	0	0/1	1/0	(no change)
0	1	0	1	
1	0	1	0	
1	1	0	0	<b>(Undesirable)</b>

(b) Truth table

[ Figure 5.4a,b from the textbook ]

## NOR Gate

 

## NOR Gate Truth table

$x_1$	$x_2$	f
0	0	1
0	1	0
1	0	0
1	1	0


# Oscillations and Undesirable States

- When  $S=1$  and  $R=1$  both outputs of the latch are equal to 0, i.e.,  $Q_a=0$  and  $Q_b=0$ .
- Thus, the two outputs are no longer complements of each other.
- This is undesirable as many of the circuits that we will build later with these latches rely on the assumption that the two outputs are always complements of each other.
- (This is obviously not the case for the basic latch, but we will patch it later to eliminate this problem).

# Oscillations and Undesirable States

- An even bigger problem occurs when we transition **from  $S=R=1$  to  $S=R=0$** .
- When  $S=R=1$  we have  $Q_a=Q_b=0$ . After the transition to  $S=R=0$ , however, we get  $Q_a=Q_b=1$ , which would immediately cause  $Q_a=Q_b=0$ , and so on.
- If the gate delays and the wire lengths are identical, then this oscillation will continue forever.
- In practice, the oscillation dies down and the output settles into either  $Q_a=1$  and  $Q_b=0$  or  $Q_a=0$  and  $Q_b=1$ .
- The problem is that **we can't predict** which one of these two it will settle into.

 
# Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit

S	R	$Q_a$	$Q_b$
0	0	0/1	1/0 (no change)
0	1	0	1
1	0	1	0
1	1	0	0

(b) Characteristic table

 


(c) Timing diagram

→ Time

[ Figure 5.4 from the textbook ]

 
# Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit

S	R	$Q_a$	$Q_b$	
0	0	0/1	1/0	(no change)
0	1	0	1	
1	0	1	0	
1	1	0	0	

(b) Characteristic table

 


(c) Timing diagram

→ Time

[ Figure 5.4 from the textbook ]

 
# Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit


S	R	$Q_a$	$Q_b$
0	0	0/1	1/0 (no change)
0	1	0	1
1	0	1	0
1	1	0	0

(b) Characteristic table

 

(c) Timing diagram

 
# Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit


S	R	$Q_a$	$Q_b$
0	0	0/1	1/0 (no change)
0	1	0	1
1	0	1	0
1	1	0	0

(b) Characteristic table

 

(c) Timing diagram

 
# Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit

S	R	Q <sub>a</sub>	Q <sub>b</sub>	
0	0	0/1	1/0	(no change)
0	1	0	1	
1	0	1	0	
1	1	0	0	


(b) Characteristic table

 

(c) Timing diagram



 
# Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit


S	R	Q <sub>a</sub>	Q <sub>b</sub>	
0	0	0/1	1/0	(no change)
0	1	0	1	
1	0	1	0	
1	1	0	0	

(b) Characteristic table

 

(c) Timing diagram

 
# Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit


S	R	Q <sub>a</sub>	Q <sub>b</sub>	
0	0	0/1	1/0	(no change)
0	1	0	1	
1	0	1	0	
1	1	0	0	

(b) Characteristic table

 

(c) Timing diagram
 
# Timing Diagram for the Basic Latch with NOR Gates




(a) Circuit

S	R	Q <sub>a</sub>	Q <sub>b</sub>
0	0	0/1	1/0
0	1	0	1
1	0	1	0
1	1	0	0


(no change)

(b) Characteristic table

 

(c) Timing diagram

 
# Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit


S	R	Q <sub>a</sub>	Q <sub>b</sub>	
0	0	0/1	1/0	(no change)
0	1	0	1	
1	0	1	0	
1	1	0	0	

(b) Characteristic table

 

(c) Timing diagram

 
# Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit


S	R	Q <sub>a</sub>	Q <sub>b</sub>	
0	0	0/1	1/0	(no change)
0	1	0	1	
1	0	1	0	
1	1	0	0	

(b) Characteristic table

 

(c) Timing diagram

 
# Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit

S	R	Q <sub>a</sub>	Q <sub>b</sub>	
0	0	0/1	1/0	(no change)
0	1	0	1	
1	0	1	0	
1	1	0	0	


(b) Characteristic table

 

(c) Timing diagram

For a brief moment the latch goes through the undesirable state  $Q_a=0$  and  $Q_b=0$ .

 
# Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit

S	R	Q <sub>a</sub>	Q <sub>b</sub>	
0	0	0/1	1/0	(no change)
0	1	0	1	
1	0	1	0	
1	1	0	0	


(b) Characteristic table

 

(c) Timing diagram

But these zeros loop around ...

 
# Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit

S	R	Q <sub>a</sub>	Q <sub>b</sub>	
0	0	0/1	1/0	(no change)
0	1	0	1	
1	0	1	0	
1	1	0	0	

(b) Characteristic table

 


(c) Timing diagram

... and set it to Q<sub>a</sub>=1 and Q<sub>b</sub>=0.



 
# Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit

S	R	Q <sub>a</sub>	Q <sub>b</sub>	
0	0	0/1	1/0	(no change)
0	1	0	1	
1	0	1	0	
1	1	0	0	


(b) Characteristic table

 

(c) Timing diagram

The new values also loop around ...

 
# Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit

S	R	Q <sub>a</sub>	Q <sub>b</sub>	
0	0	0/1	1/0	(no change)
0	1	0	1	
1	0	1	0	
1	1	0	0	

(b) Characteristic table

 


(c) Timing diagram

... but they leave the outputs the same.



 
# Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit

S	R	$Q_a$	$Q_b$	
0	0	0/1	1/0	(no change)
0	1	0	1	
1	0	1	0	
1	1	0	0	

(b) Characteristic table

 


(c) Timing diagram

→ Time

[ Figure 5.4 from the textbook ]
 
# Timing Diagram for the Basic Latch with NOR Gates




(a) Circuit

S	R	Q <sub>a</sub>	Q <sub>b</sub>
0	0	0/1	1/0
0	1	0	1
1	0	1	0
1	1	0	0


(no change)

(b) Characteristic table

 

(c) Timing diagram
 
# Timing Diagram for the Basic Latch with NOR Gates




(a) Circuit

S	R	$Q_a$	$Q_b$
0	0	0/1	1/0
0	1	0	1
1	0	1	0
1	1	0	0


(no change)

(b) Characteristic table

 

(c) Timing diagram

 
# Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit


S	R	Q <sub>a</sub>	Q <sub>b</sub>	
0	0	0/1	1/0	(no change)
0	1	0	1	
1	0	1	0	
1	1	0	0	

(b) Characteristic table

 

(c) Timing diagram

 
# Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit

S	R	$Q_a$	$Q_b$	
0	0	0/1	1/0	(no change)
0	1	0	1	
1	0	1	0	
1	1	0	0	

(b) Characteristic table

 


(c) Timing diagram

For a brief moment the latch goes through the undesirable state  $Q_a=0$  and  $Q_b=0$ .



 
# Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit

S	R	Q <sub>a</sub>	Q <sub>b</sub>	
0	0	0/1	1/0	(no change)
0	1	0	1	
1	0	1	0	
1	1	0	0	


(b) Characteristic table

 

(c) Timing diagram

But these zeros loop around ...

 
# Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit

S	R	Q <sub>a</sub>	Q <sub>b</sub>	
0	0	0/1	1/0	(no change)
0	1	0	1	
1	0	1	0	
1	1	0	0	


(b) Characteristic table

 

(c) Timing diagram

... and set it to Q<sub>a</sub>=0 and Q<sub>b</sub>=1.

 
# Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit

S	R	$Q_a$	$Q_b$	
0	0	0/1	1/0	(no change)
0	1	0	1	
1	0	1	0	
1	1	0	0	


(b) Characteristic table

 

(c) Timing diagram

The new values also loop around ...

 
# Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit

S	R	$Q_a$	$Q_b$	
0	0	0/1	1/0	(no change)
0	1	0	1	
1	0	1	0	
1	1	0	0	

(b) Characteristic table

 


(c) Timing diagram

... but they leave the outputs the same.



 
# Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit

S	R	$Q_a$	$Q_b$
0	0	0/1	1/0 (no change)
0	1	0	1
1	0	1	0
1	1	0	0

(b) Characteristic table

 


(c) Timing diagram

→ Time

[ Figure 5.4 from the textbook ]

 
# Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit

S	R	$Q_a$	$Q_b$
0	0	0/1	1/0 (no change)
0	1	0	1
1	0	1	0
1	1	0	0

(b) Characteristic table

 


(c) Timing diagram

→ Time

[ Figure 5.4 from the textbook ]

 
# Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit

S	R	$Q_a$	$Q_b$	
0	0	0/1	1/0	(no change)
0	1	0	1	
1	0	1	0	
1	1	0	0	

(b) Characteristic table

 

A transition from  $S=R=1$  to  $S=R=0$  causes oscillations of the two output values  $Q_a$  and  $Q_b$ .

(c) Timing diagram


→ Time

[ Figure 5.4 from the textbook ]




# **Basic Latch with NAND Gates**

 
# Circuit for the Basic Latch with NAND Gates



## Basic Latch (with NOR Gates)

 


## Basic Latch (with NAND Gates)

 

Notice that in the NAND case the two inputs are swapped and negated.


The labels of the outputs are the same in both cases.

## Basic Latch (with NOR Gates)

 


SR Latch

## Basic Latch (with NAND Gates)

 

$\bar{S}\bar{R}$  Latch

# Circuit and Characteristic Table

 

(a) Circuit


$\bar{S}$	$\bar{R}$	$Q_a$	$Q_b$
0	0	1	1
0	1	1	0
1	0	0	1
1	1	0/1	1/0 (no change)

(b) Characteristic table (version 1)

S	R	$Q_a$	$Q_b$
0	0	0/1	1/0 (no change)
0	1	0	1
1	0	1	0
1	1	1	1

(c) Characteristic table (version 2)


## NAND Gate

 

## NAND Gate Truth table


$x_1$	$x_2$	f
0	0	1
0	1	1
1	0	1
1	1	0

## Basic Latch (with NOR Gates)

 


S	R	$Q_a$	$Q_b$
0	0	0/1	1/0 (no change)
0	1	0	1
1	0	1	0
1	1	0	0

## Basic Latch (with NAND Gates)

 


S	R	$Q_a$	$Q_b$
0	0	0/1	1/0 (no change)
0	1	0	1
1	0	1	0
1	1	1	1

## Basic Latch (with NOR Gates)

 


S	R	$Q_a$	$Q_b$	
0	0	0/1	1/0	(no change) <b>Latch</b>
0	1	0	1	<b>Reset</b>
1	0	1	0	<b>Set</b>
1	1	0	0	<b>Undesirable</b>

## Basic Latch (with NAND Gates)

 


S	R	$Q_a$	$Q_b$	
0	0	0/1	1/0	(no change) <b>Latch</b>
0	1	0	1	<b>Reset</b>
1	0	1	0	<b>Set</b>
1	1	1	1	<b>Undesirable</b>

## Basic Latch (with NOR Gates)

 

S	R	$Q_a$	$Q_b$	
0	0	0/1	1/0	(no change) Latch
0	1	0	1	Reset
1	0	1	0	Set
1	1	0	0	Undesirable

## Basic Latch (with NAND Gates)

 

S	R	$Q_a$	$Q_b$	
0	0	0/1	1/0	(no change) Latch
0	1	0	1	Reset
1	0	1	0	Set
1	1	1	1	Undesirable

The two characteristic tables are the same  
(except for the last row, which is the undesirable configuration).



# Oscillations and Undesirable States


- **The basic latch with NAND gates also suffers from oscillation problems, similar to the basic latch implemented with NOR gates.**
- **Try to do this analysis on your own.**

# **Gated SR Latch**

# Motivation


- **The basic latch changes its state when the input signals change**
- **It is hard to control when these input signals will change and thus it is hard to know when the latch may change its state.**
- **We want to have something like an Enable input.**
- **In this case it is called the “Clock” input because it is desirable for the state changes to be synchronized.**

# Circuit Diagram for the Gated SR Latch

 


[ Figure 5.5a from the textbook ]

# Circuit Diagram for the Gated SR Latch

 


This is the “gate”  
of the gated latch

# Circuit Diagram for the Gated SR Latch

 


This is the “snake”  
of the gated latch

# Circuit Diagram for the Gated SR Latch

 

The outputs are complements of each other
 
# Circuit Diagram and Characteristic Table for the Gated SR Latch




Clk	S	R	$Q(t + 1)$
0	x	x	$Q(t)$ (no change)
1	0	0	$Q(t)$ (no change)
1	0	1	0
1	1	0	1
1	1	1	x

[ Figure 5.5a-b from the textbook ]



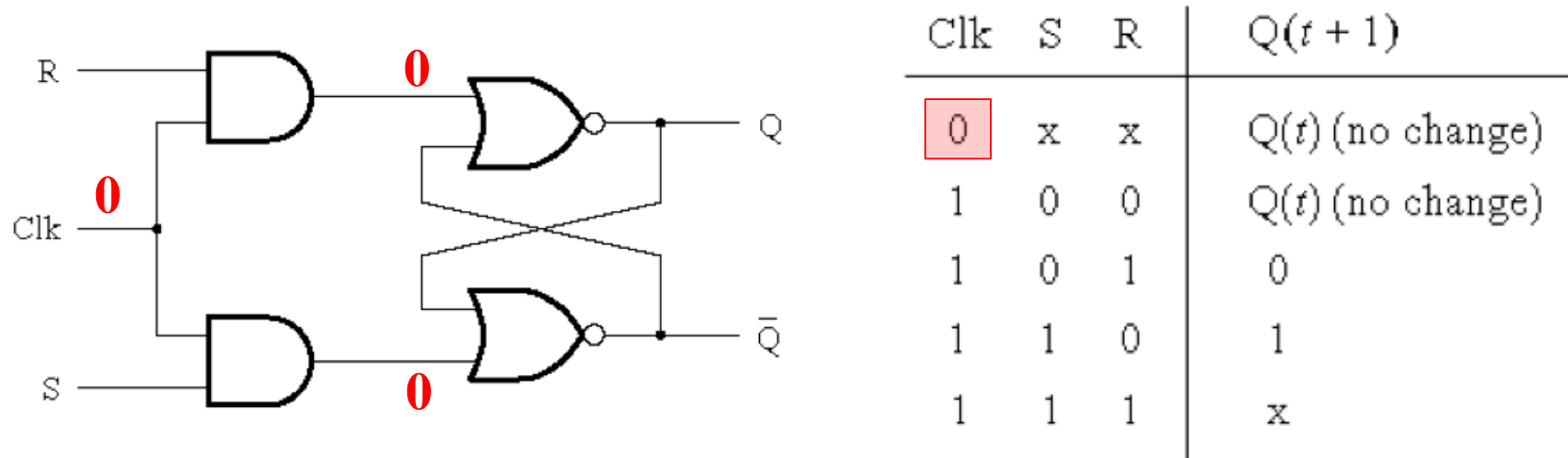
# Circuit Diagram and Characteristic Table for the Gated SR Latch



When Clk = 0 this circuit holds the previous output values, regardless of the current inputs S and R because S' and R' are 0.

 
# Circuit Diagram and Characteristic Table for the Gated SR Latch



Clk	S	R	Q(t + 1)
0	x	x	Q(t) (no change)
1	0	0	Q(t) (no change)
1	0	1	0
1	1	0	1
1	1	1	x



When Clk = 1 this circuit behaves like a basic latch.
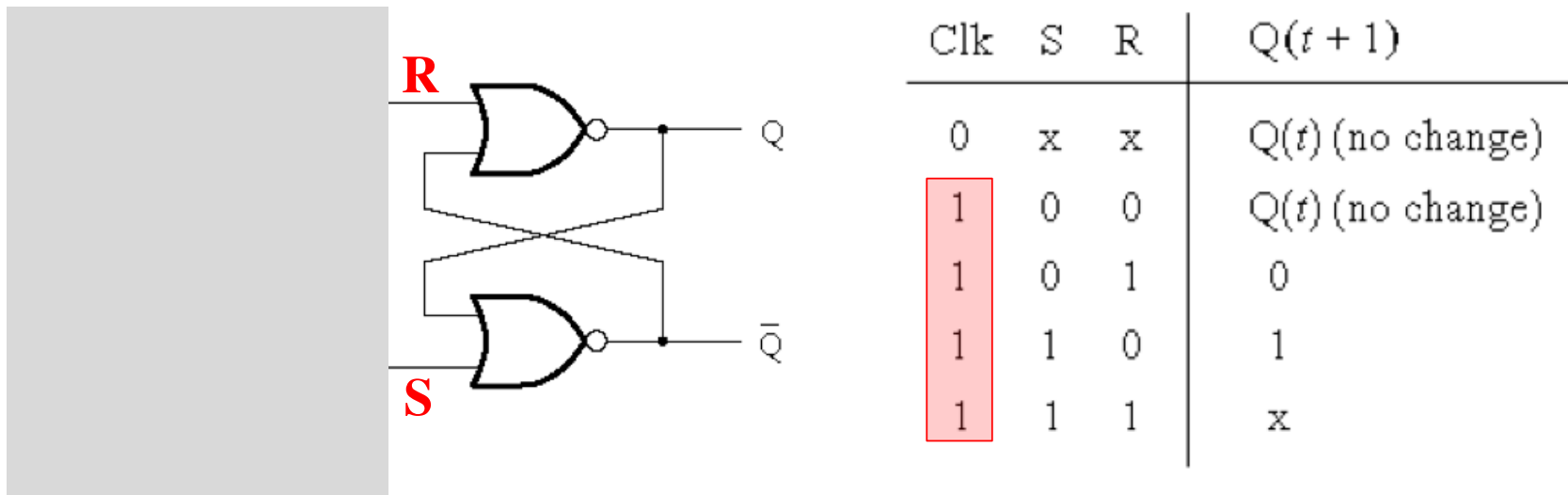
# Circuit Diagram and Characteristic Table for the Gated SR Latch





When Clk = 1 this circuit behaves like a basic latch.  
As if this part in gray were not even there.

# Circuit Diagram and Graphical Symbol for the Gated SR Latch

  


[ Figure 5.5a,c from the textbook ]

# Timing Diagram for the Gated SR Latch

  


[ Figure 5.5c from the textbook ]

# Gated SR latch with NAND gates

 


[ Figure 5.6 from the textbook ]

# Gated SR latch with NAND gates

 

In this case, the “gate” is constructed using NAND gates! Not AND gates.


# Gated SR latch with NAND gates

 

The “snake” is also constructed with NANDs.




# Gated SR latch with NAND gates

 

Also, notice that the positions of S and R are now swapped.

# Gated SR latch with NAND gates


$\bar{S}$	$\bar{R}$	Q	$\bar{Q}$
0	0	1	1
0	1	1	0
1	0	0	1
1	1	0/1	1/0 (no change)

 

Notice that when  $\text{Clk}=1$  this turns into the basic latch with NAND gates, i.e., the  $\bar{S}\bar{R}$  Latch.


# Gated SR latch with NAND gates

$\bar{S}$	$\bar{R}$	Q	$\bar{Q}$
0	0	1	1
0	1	1	0
1	0	0	1
1	1	0/1	1/0 (no change)

 


When Clk=0 this circuit holds the previous output values.


## Gated SR latch with NOR gates

 


## Gated SR latch with NAND gates

 

## Gated SR latch with NOR gates

 


## Gated SR latch with NAND gates

 


Graphical symbols are the same

## Gated SR latch with NOR gates

 

Clk	S	R	$Q(t+1)$
0	x	x	$Q(t)$ (no change)
1	0	0	$Q(t)$ (no change)
1	0	1	0
1	1	0	1
1	1	1	x (undesirable)

## Gated SR latch with NAND gates

 

Clk	S	R	$Q(t+1)$
0	x	x	$Q(t)$ (no change)
1	0	0	$Q(t)$ (no change)
1	0	1	0
1	1	0	1
1	1	1	x (undesirable)

Characteristic tables are the same


# **Gated D Latch**

# Motivation

- **Dealing with two inputs (S and R) could be messy. For example, we may have to reset the latch before some operations in order to store a specific value but the reset may not be necessary depending on the current state of the latch.**
- **Why not have just one input and call it D.**
- **The D latch can be constructed using a simple modification of the SR latch.**




# Circuit Diagram for the Gated D Latch

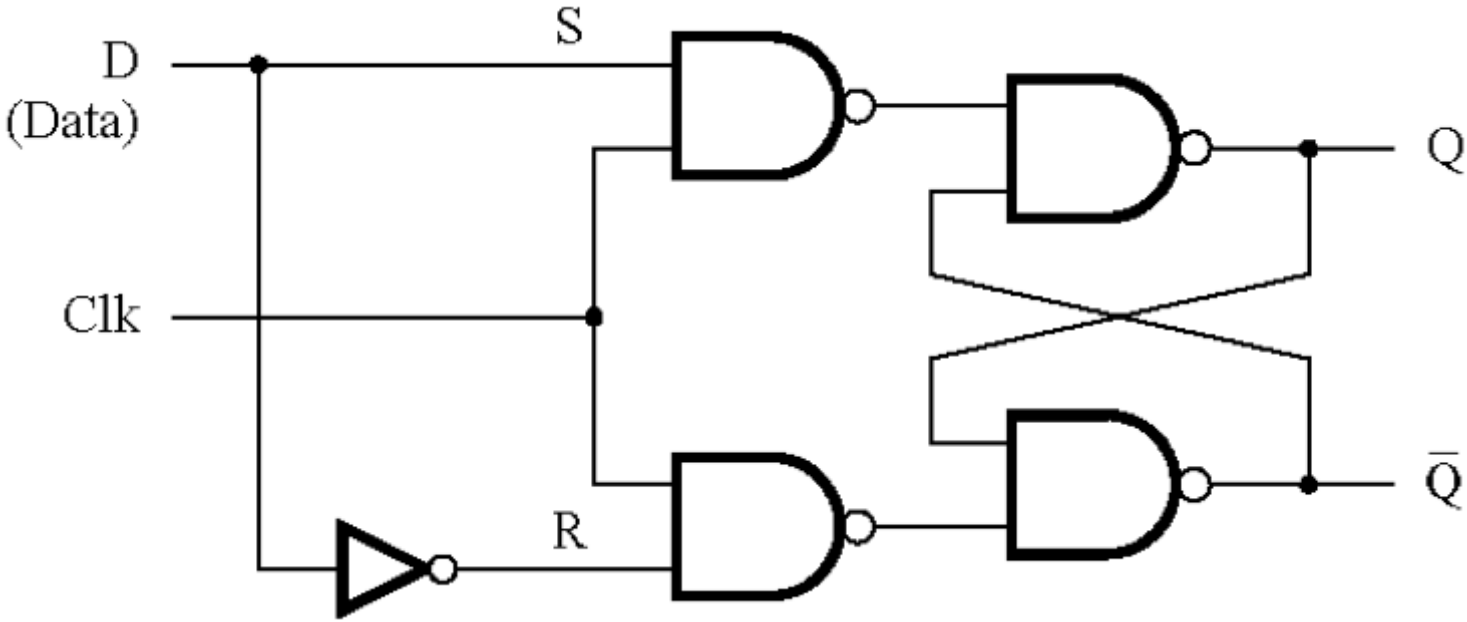


[ Figure 5.7a from the textbook ]

# Circuit Diagram for the Gated D Latch

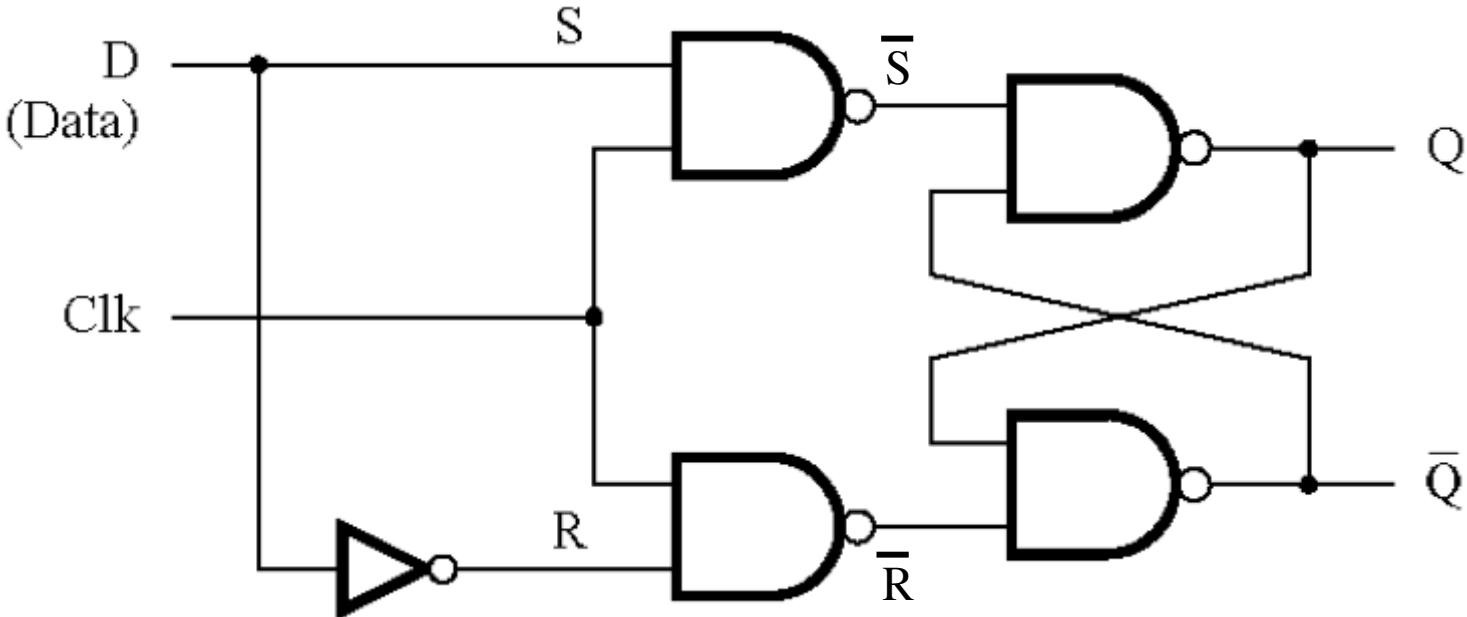

[ Figure 5.7a from the textbook ]


# Circuit Diagram for the Gated D Latch

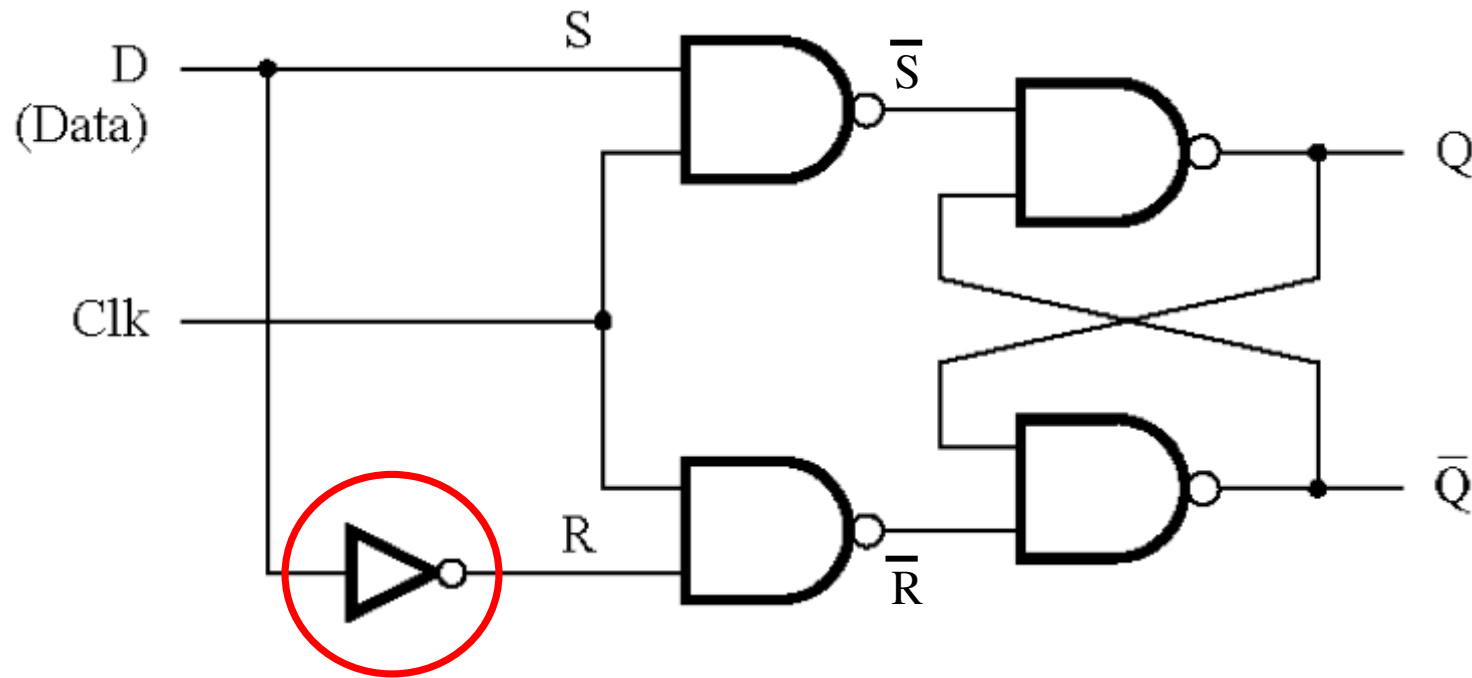

This is the only  
new thing here.


[ Figure 5.7a from the textbook ]

# Circuit Diagram for the Gated D Latch

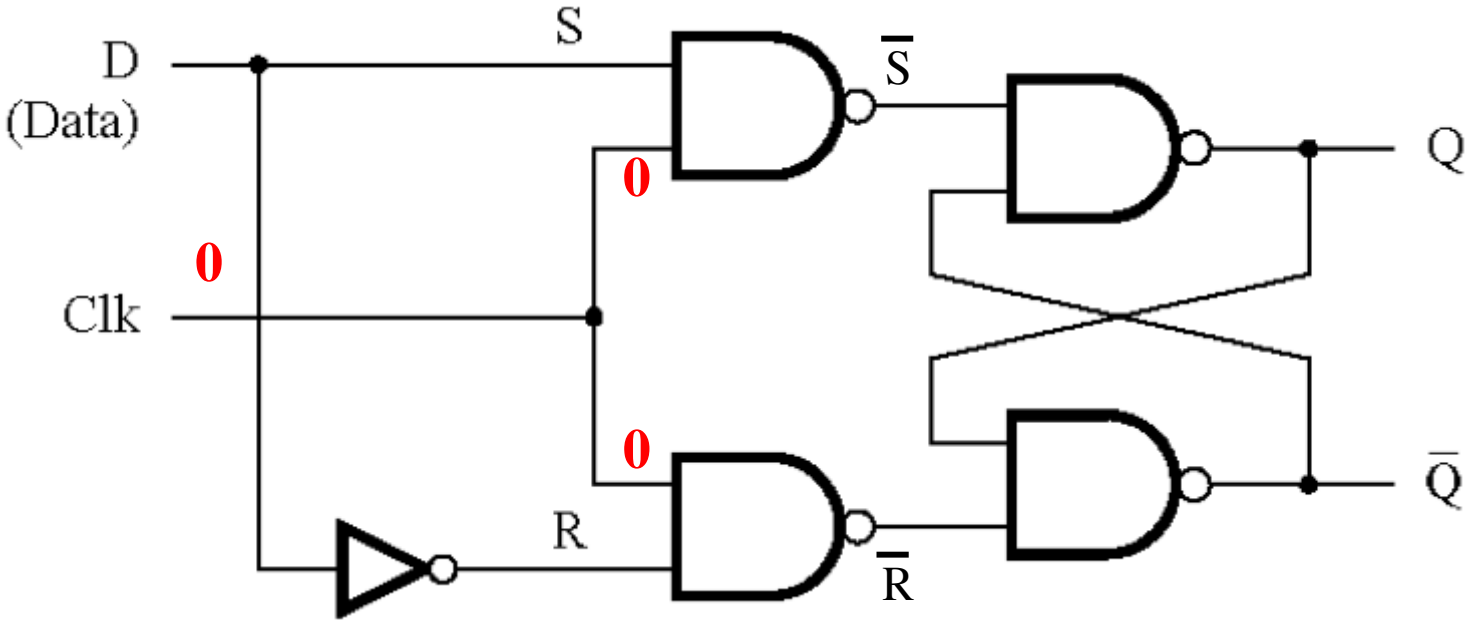

[ Figure 5.7a from the textbook ]


# Circuit Diagram for the Gated D Latch

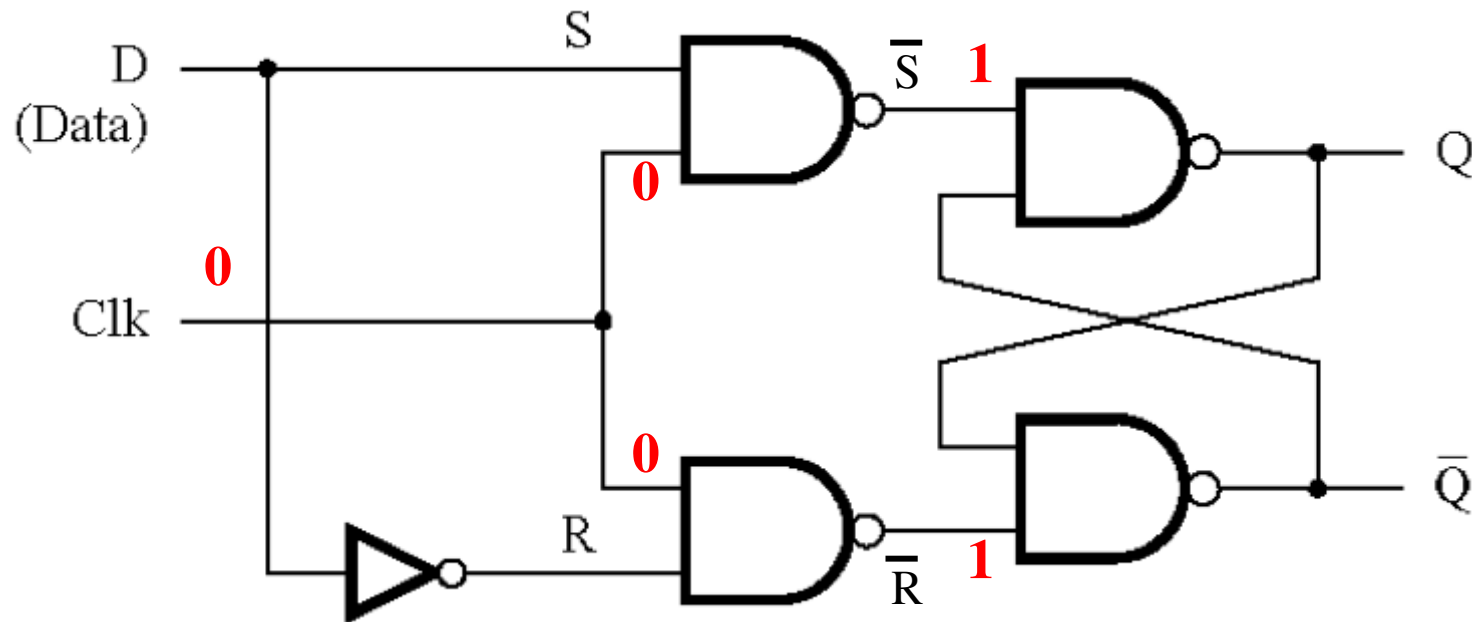

$\bar{S}$	$\bar{R}$	Q	$\bar{Q}$
0	0	1	1
0	1	1	0
1	0	0	1
1	1	0/1	1/0 (no change)

[ Figure 5.7a from the textbook ]

# Circuit Diagram for the Gated D Latch

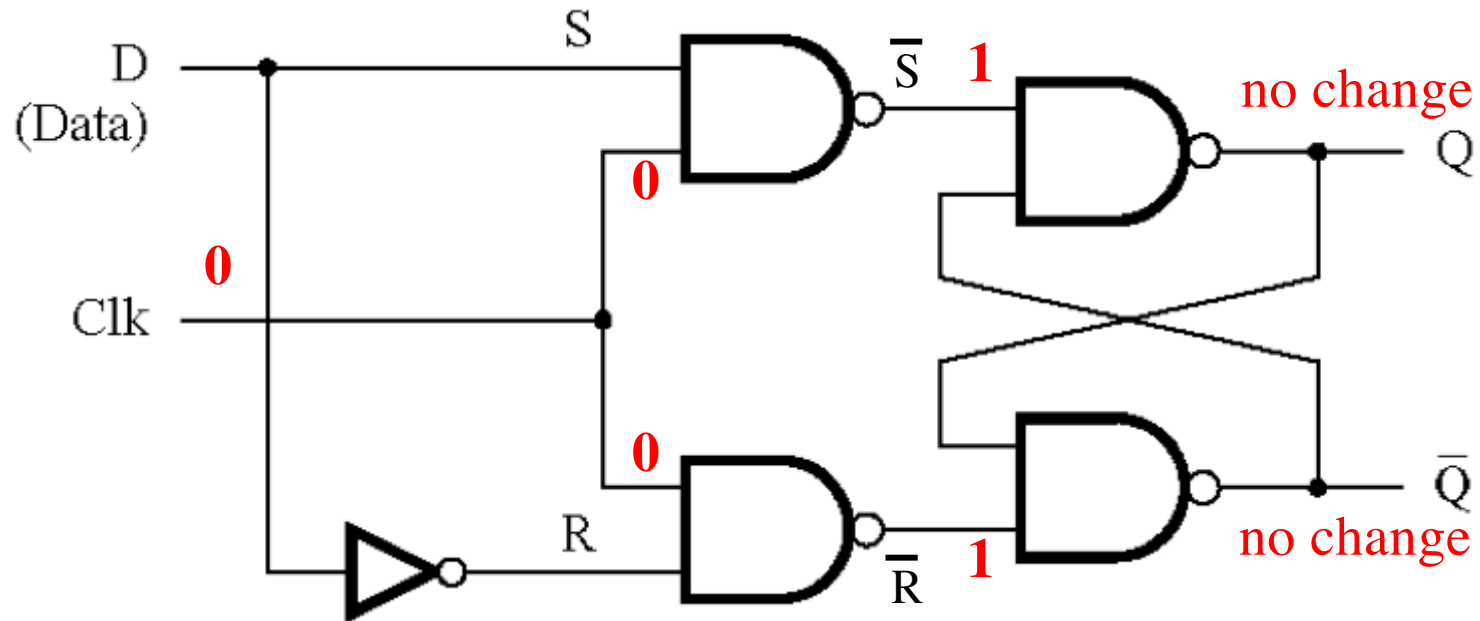


$\bar{S}$	$\bar{R}$	Q	$\bar{Q}$
0	0	1	1
0	1	1	0
1	0	0	1
1	1	0/1	1/0 (no change)

[ Figure 5.7a from the textbook ]




# Circuit Diagram for the Gated D Latch

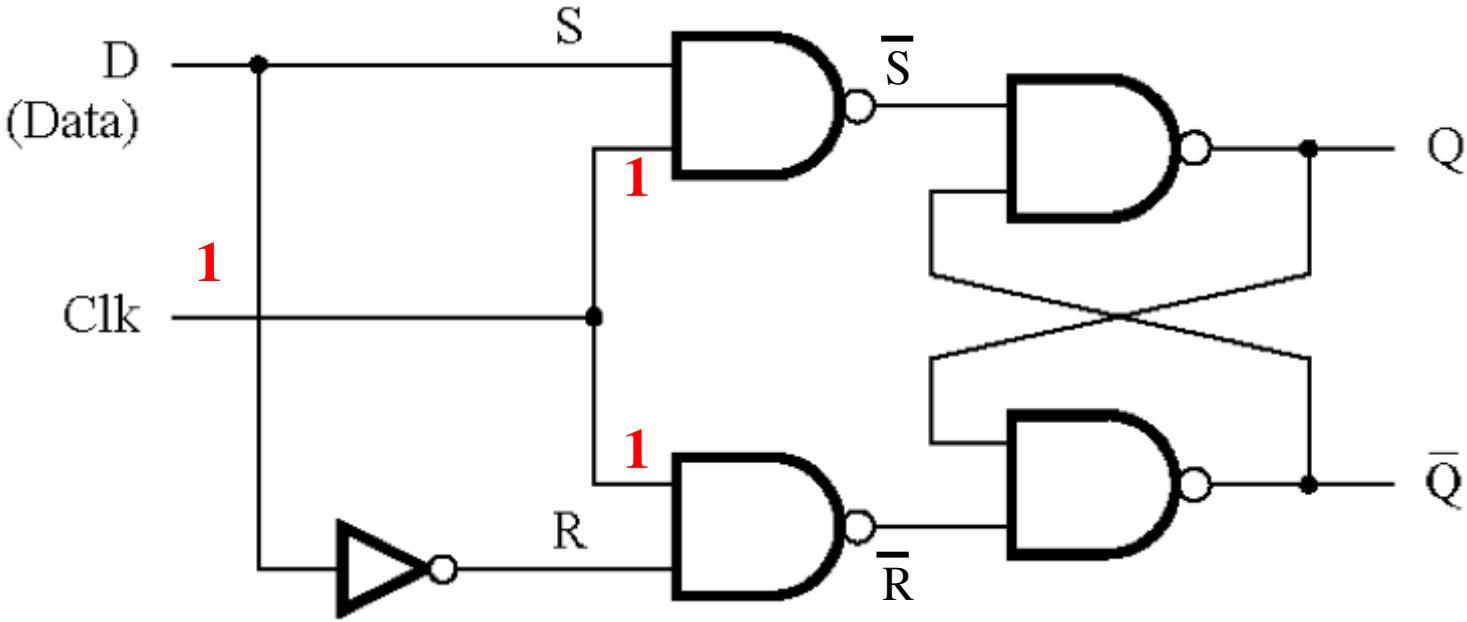

[ Figure 5.7a from the textbook ]




# Circuit Diagram for the Gated D Latch

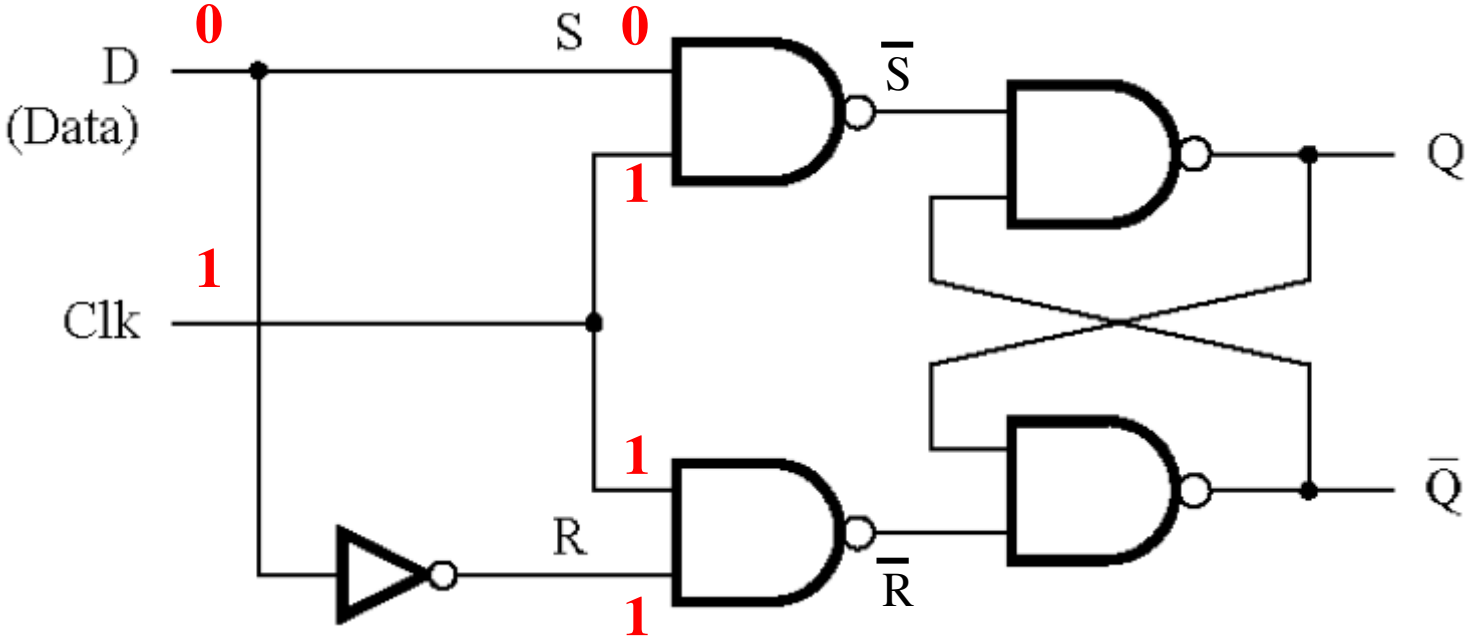

[ Figure 5.7a from the textbook ]


# Circuit Diagram for the Gated D Latch

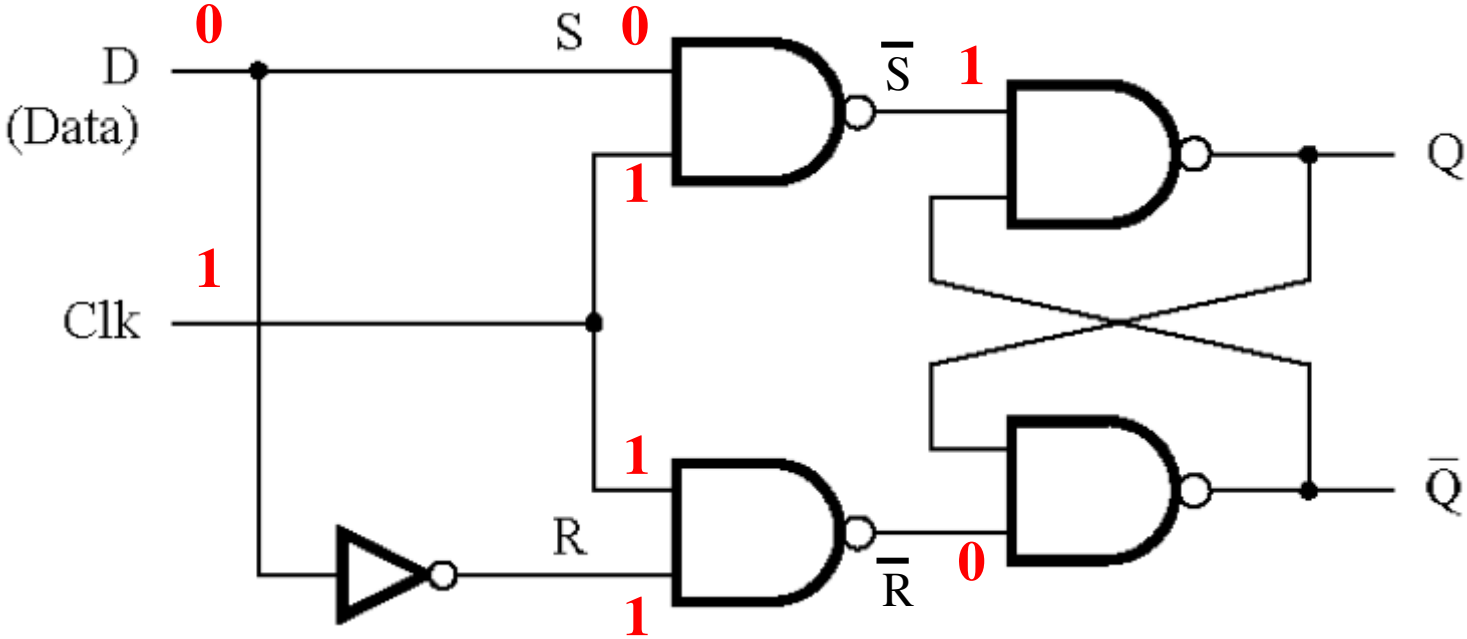

$\bar{S}$	$\bar{R}$	Q	$\bar{Q}$
0	0	1	1
0	1	1	0
1	0	0	1
1	1	0/1	1/0 (no change)

[ Figure 5.7a from the textbook ]

# Circuit Diagram for the Gated D Latch

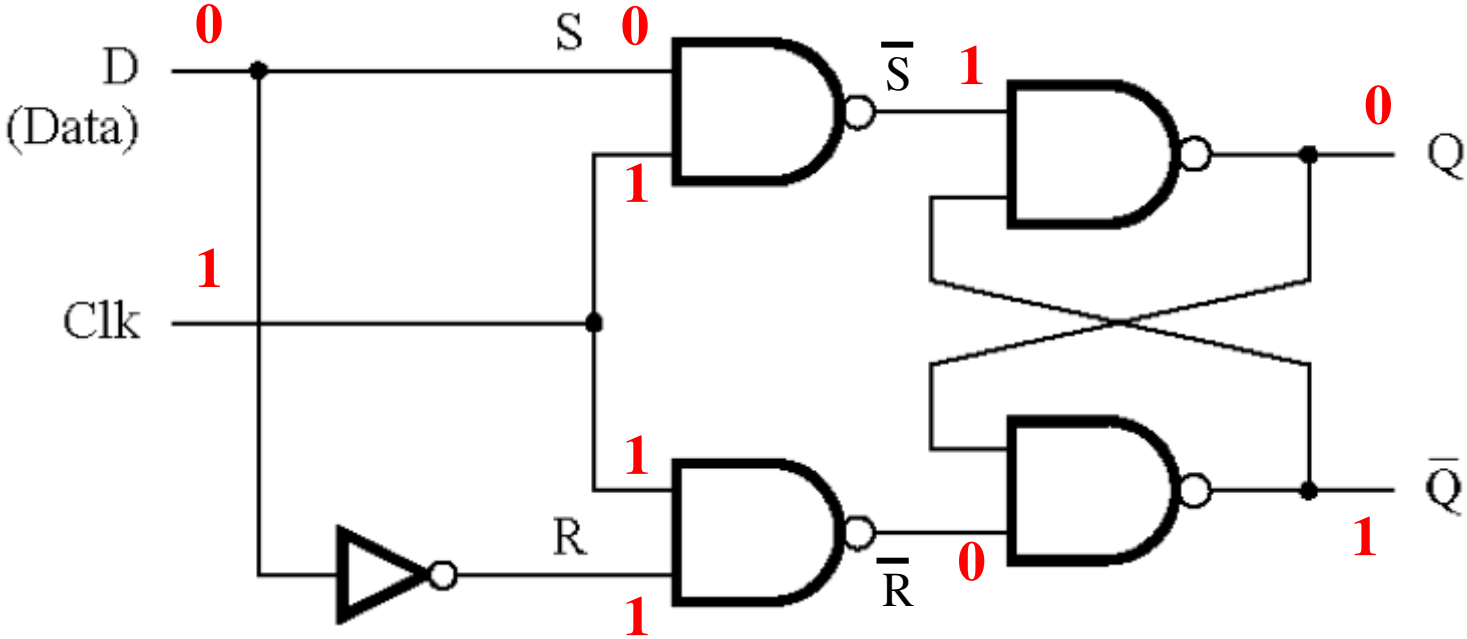


$\bar{S}$	$\bar{R}$	Q	$\bar{Q}$
0	0	1	1
0	1	1	0
1	0	0	1
1	1	0/1	1/0 (no change)

[ Figure 5.7a from the textbook ]




# Circuit Diagram for the Gated D Latch

 


[ Figure 5.7a from the textbook ]

# Circuit Diagram for the Gated D Latch

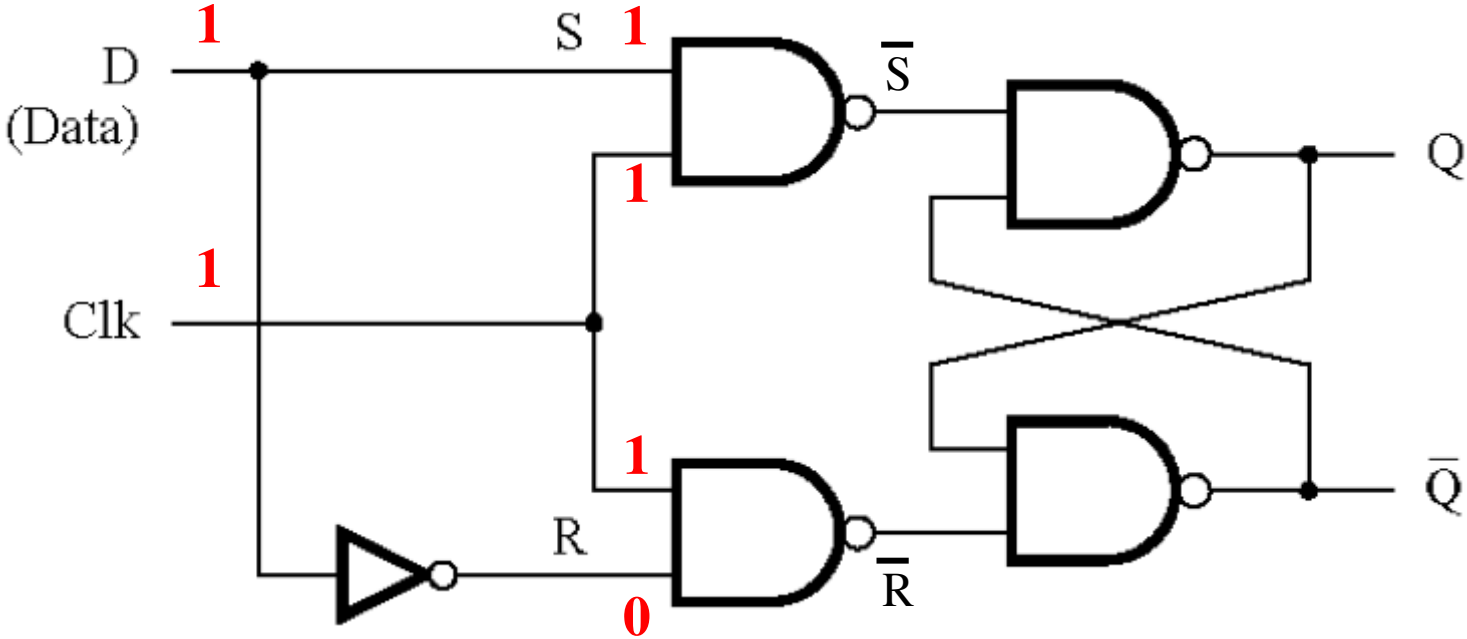

[ Figure 5.7a from the textbook ]


# Circuit Diagram for the Gated D Latch

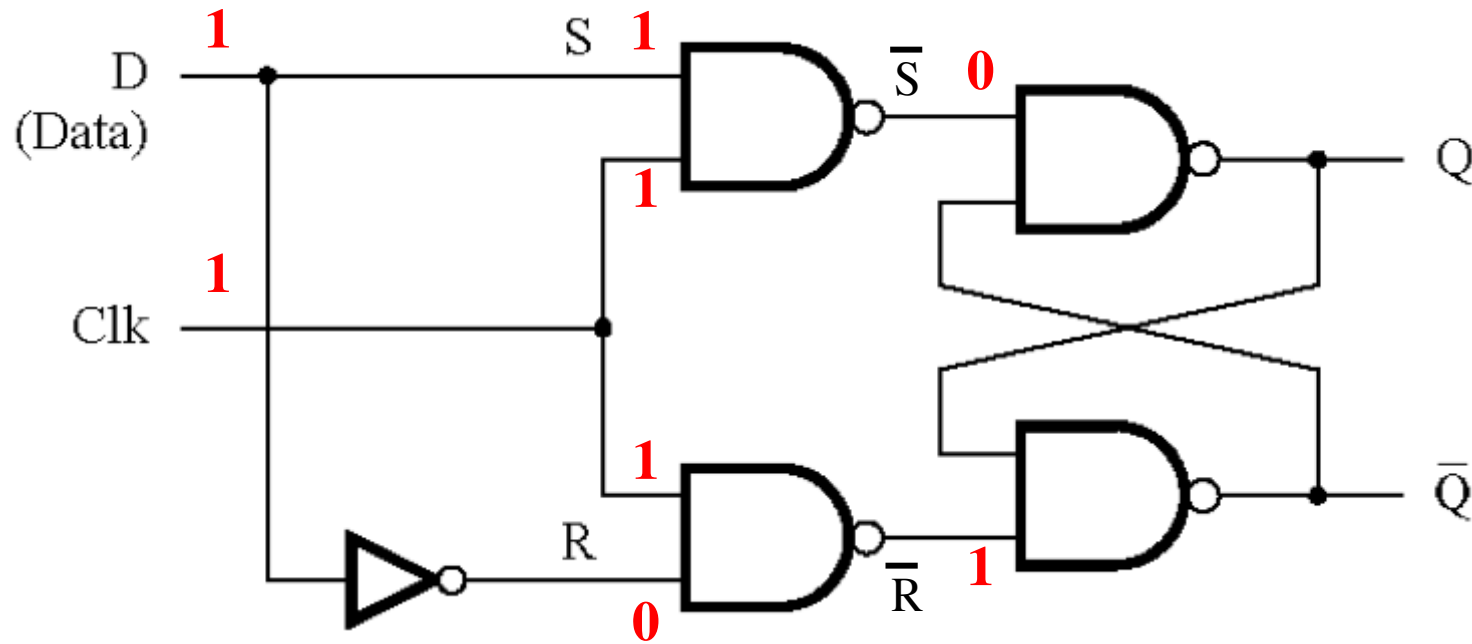

$\bar{S}$	$\bar{R}$	Q	$\bar{Q}$
0	0	1	1
0	1	1	0
1	0	0	1
1	1	0/1	1/0 (no change)

[ Figure 5.7a from the textbook ]

# Circuit Diagram for the Gated D Latch

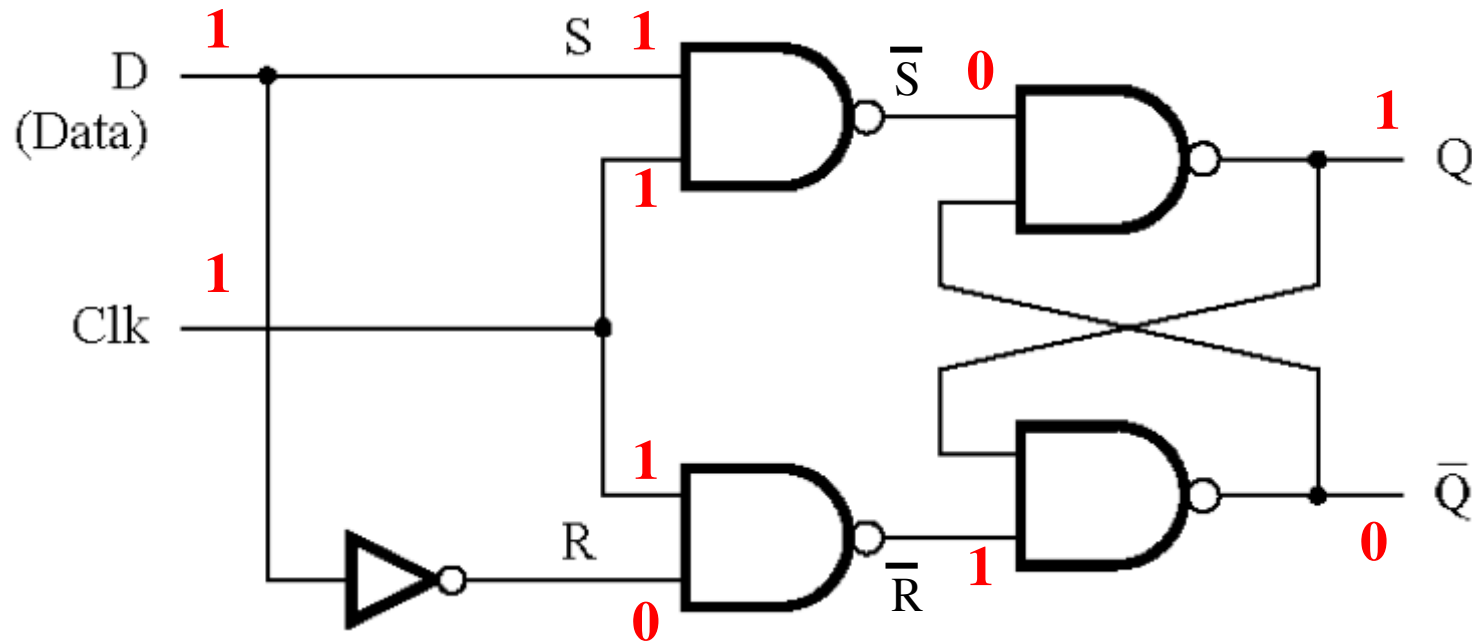


$\bar{S}$	$\bar{R}$	Q	$\bar{Q}$
0	0	1	1
0	1	1	0
1	0	0	1
1	1	0/1	1/0 (no change)

[ Figure 5.7a from the textbook ]



 
# Circuit Diagram and Characteristic Table for the Gated D Latch



Clk	D	$Q(t+1)$
0	x	$Q(t)$
1	0	0
1	1	1

Note that it is now impossible to have  $S=R=1$ .


 
# Circuit Diagram and Characteristic Table for the Gated D Latch



Clk	D	$Q(t+1)$
0	x	$Q(t)$
1	0	0
1	1	1



When Clk=1 the output follows the D input.  
When Clk=0 the output cannot be changed.

# Circuit Diagram and Graphical Symbol for the Gated D Latch

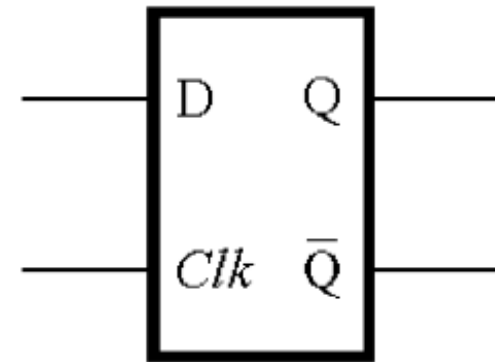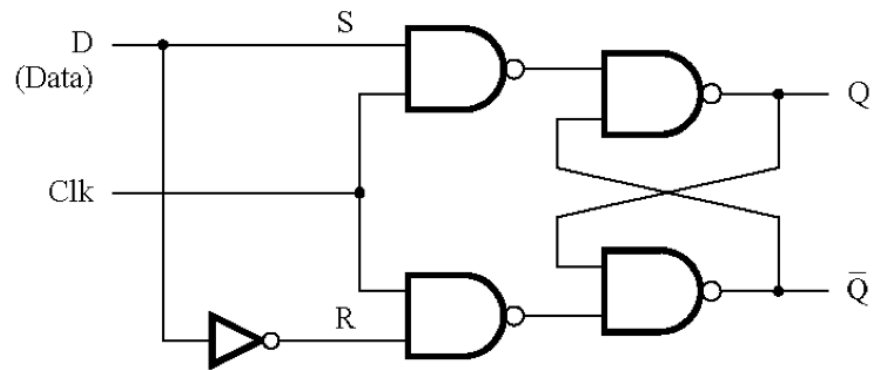


[ Figure 5.7a,c from the textbook ]

# Timing Diagram for the Gated D Latch

  


[ Figure 5.7d from the textbook ]

# Timing Diagram for the Gated D Latch

 


Clk=0

the gate is closed

 


[ Figure 5.7d from the textbook ]

# Timing Diagram for the Gated D Latch

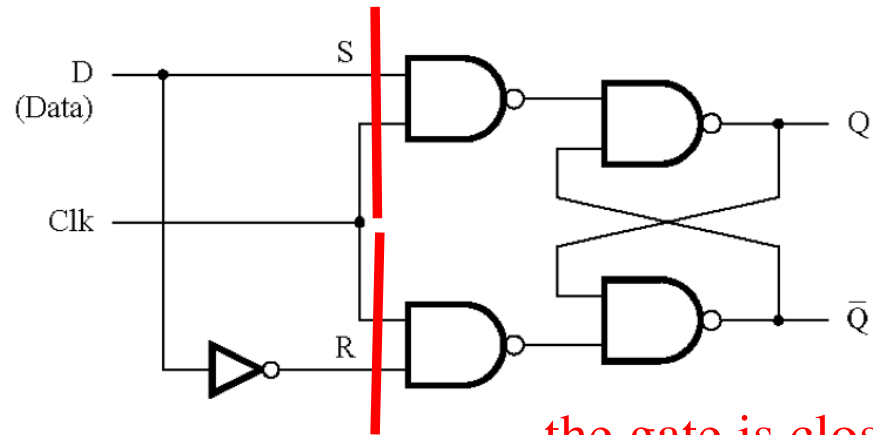

Clk=0

the gate is closed

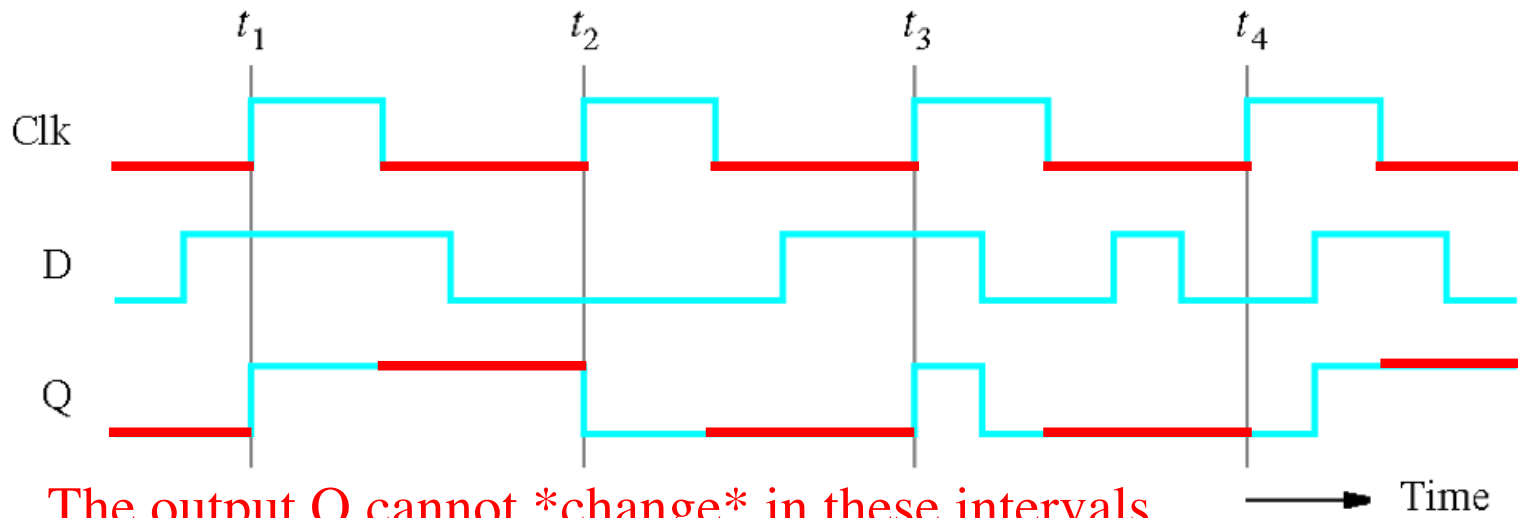


The output Q cannot \*change\* in these intervals.

Time


[ Figure 5.7d from the textbook ]

# Timing Diagram for the Gated D Latch

 


Clk=1

the gate is open

 


[ Figure 5.7d from the textbook ]

# Timing Diagram for the Gated D Latch

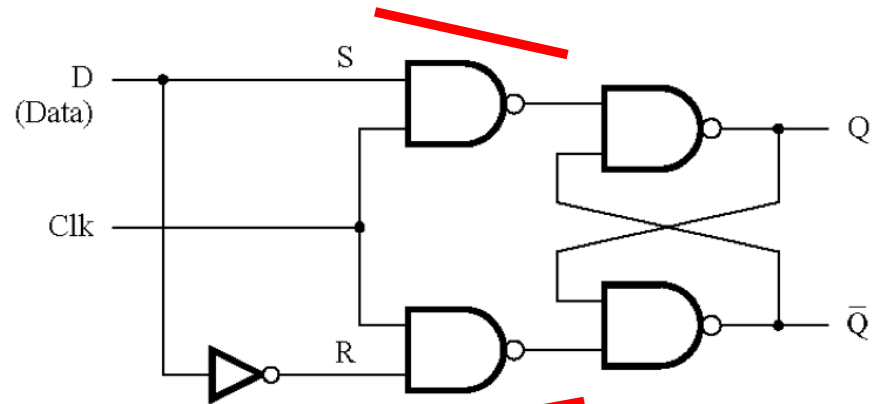

Clk=1

the gate is open

 


The output Q is equal to D in these intervals.

Time

[ Figure 5.7d from the textbook ]




# Setup and hold times

 


Setup time ( $t_{su}$ ) – the minimum time that the D signal must be stable prior to the the negative edge of the Clock signal.

Hold time ( $t_h$ ) – the minimum time that the D signal must remain stable after the the negative edge of the Clock signal.

 
## Circuit Diagram for the Gated D Latch (with the latch implemented using NORs)



# Circuit Diagram for the Gated D Latch (with the latch implemented using NORs)


 


[ Figure 5.7a from the textbook ]

 

[[https://en.wikibooks.org/wiki/Digital\\_Circuits/Latches](https://en.wikibooks.org/wiki/Digital_Circuits/Latches)]
  
# Circuit Diagram for the Gated D Latch (with the latch implemented using NORs)




The NOT gate is now in a different place.  
Also, S and R are swapped.

[ Figure 5.7a from the textbook ]

[[https://en.wikibooks.org/wiki/Digital\\_Circuits/Latches](https://en.wikibooks.org/wiki/Digital_Circuits/Latches)]


# **Alternative Design for the Gated D Latch**

# Circuit Diagram for the Gated D Latch

 

[ Figure 5.7a from the textbook ]

# Gated D Latch: Alternative Design

 


# **Master-Slave D Flip-Flop**




# Constructing a Master-Slave D Flip-Flop From Two D Latches

Latch #1

 


# Constructing a Master-Slave D Flip-Flop From **Two** D Latches


Latch #1

 


Latch #2

 

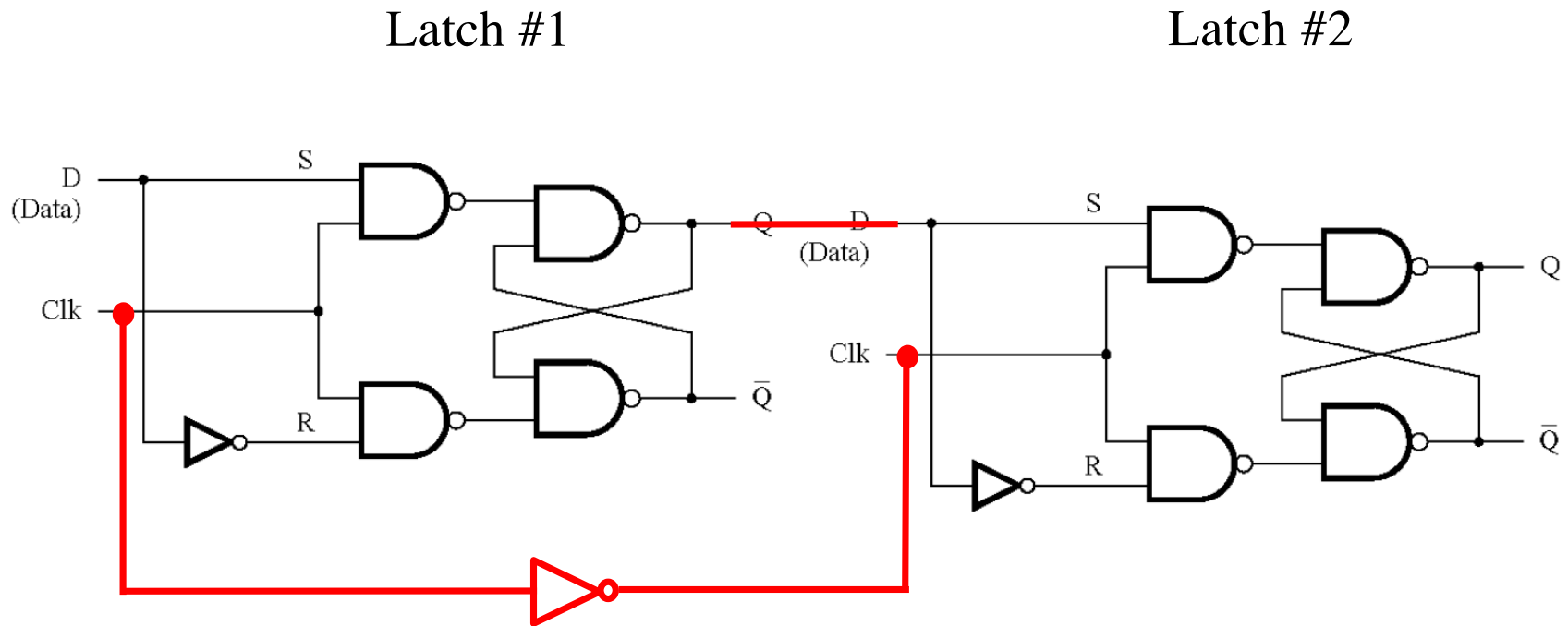
# Constructing a Master-Slave D Flip-Flop From Two D Latches


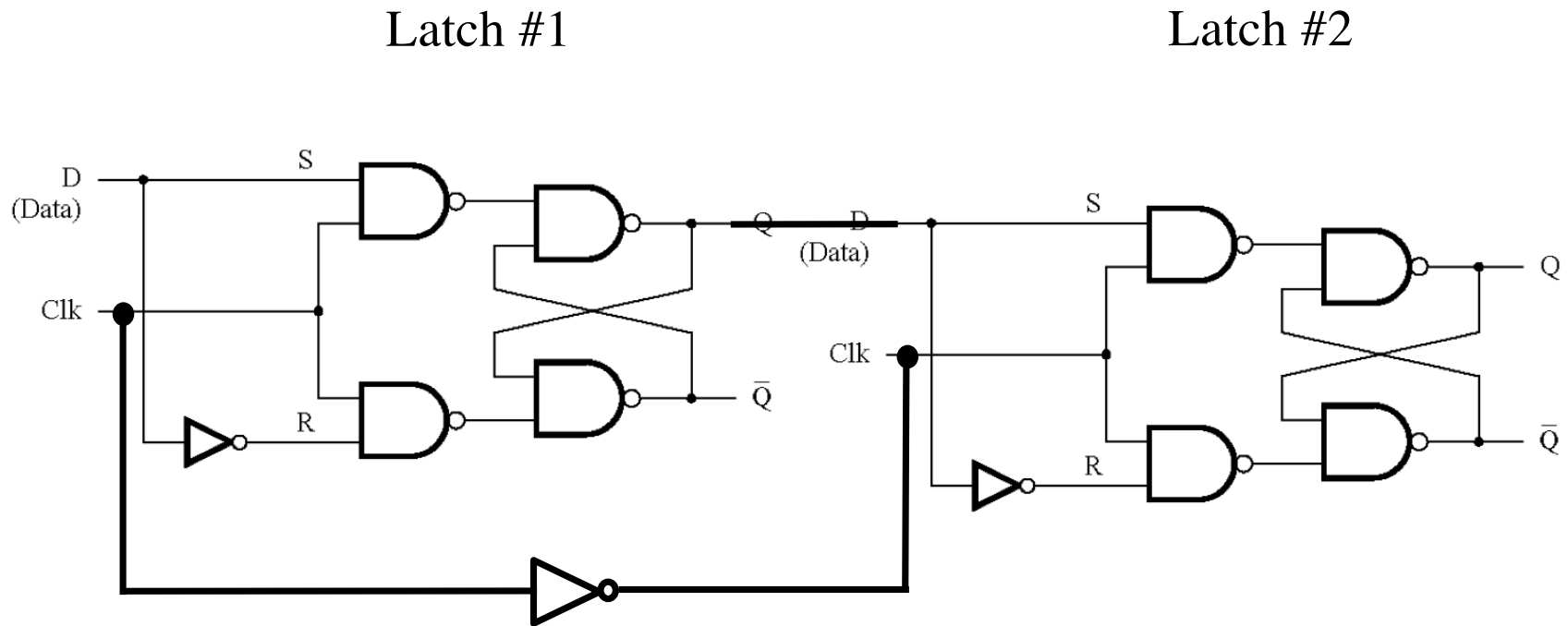
# Constructing a Master-Slave D Flip-Flop From Two D Latches



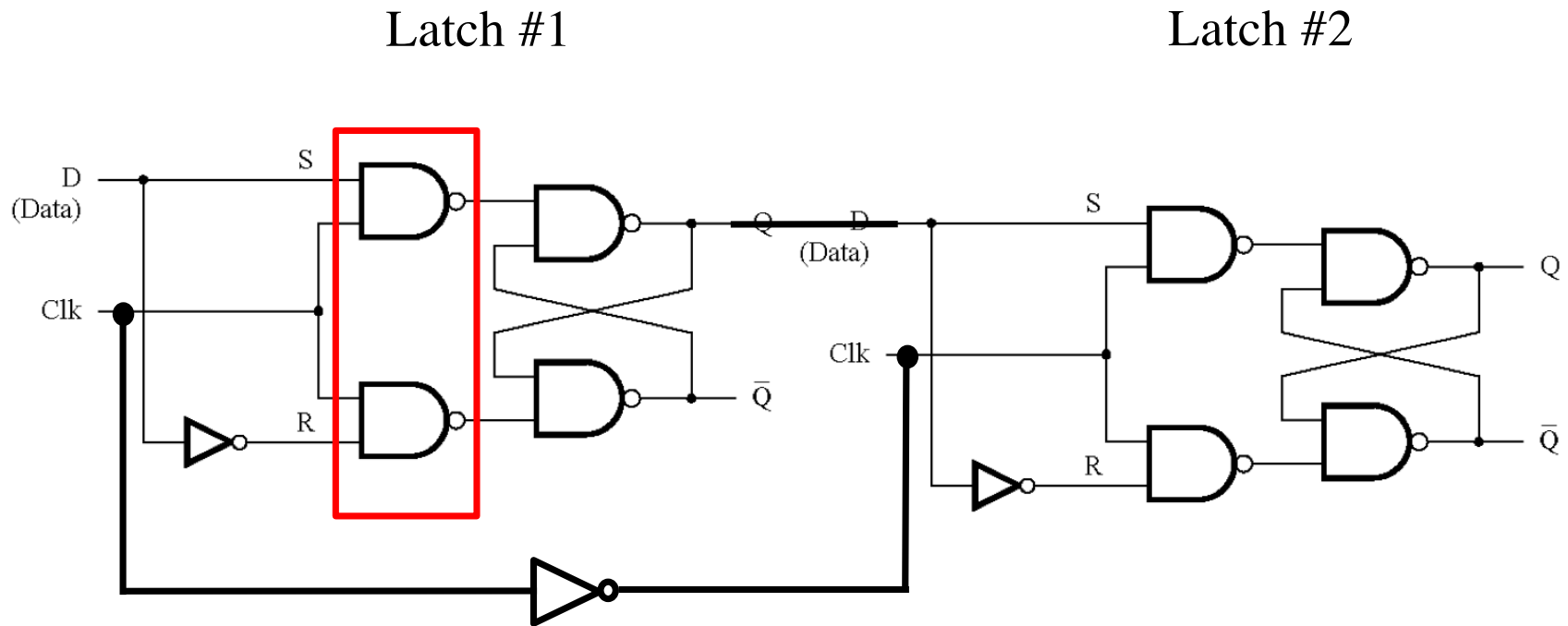
# Constructing a Master-Slave D Flip-Flop From Two D Latches




This is the  
first “gate”
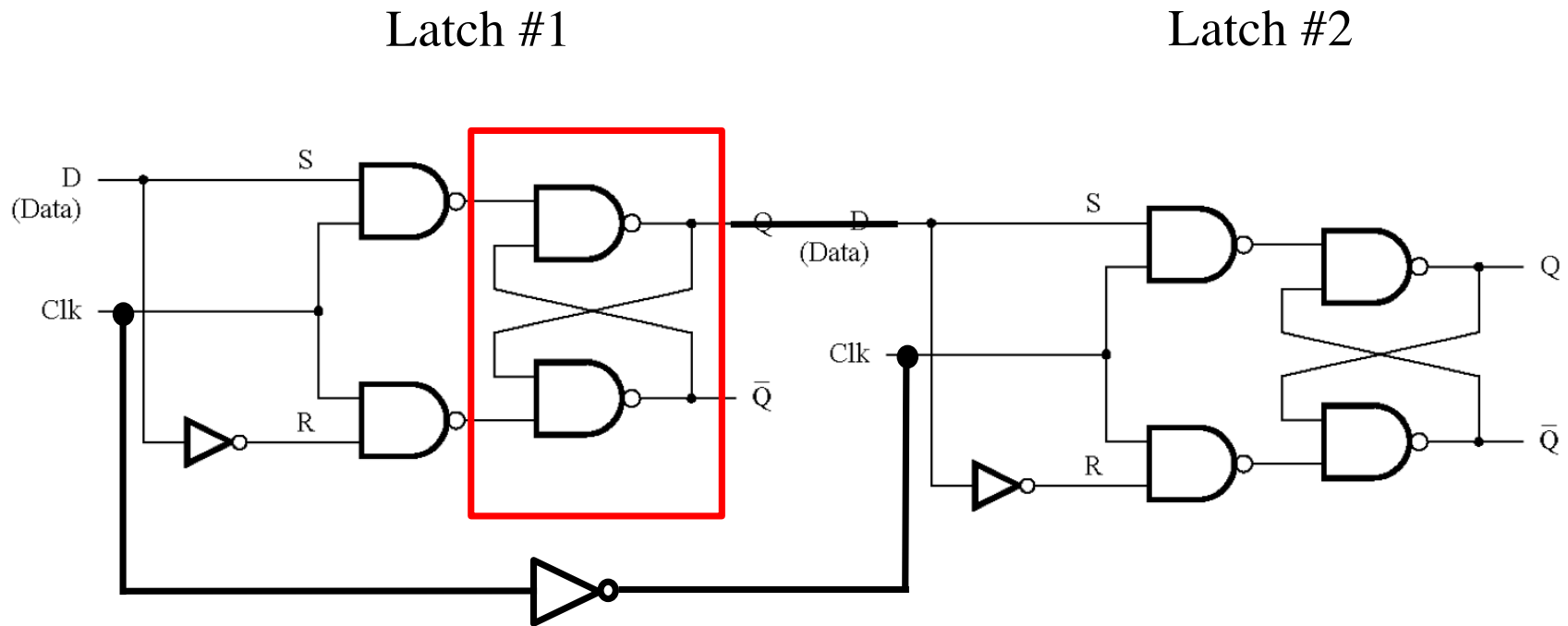
# Constructing a Master-Slave D Flip-Flop From Two D Latches




This is the  
first “snake”
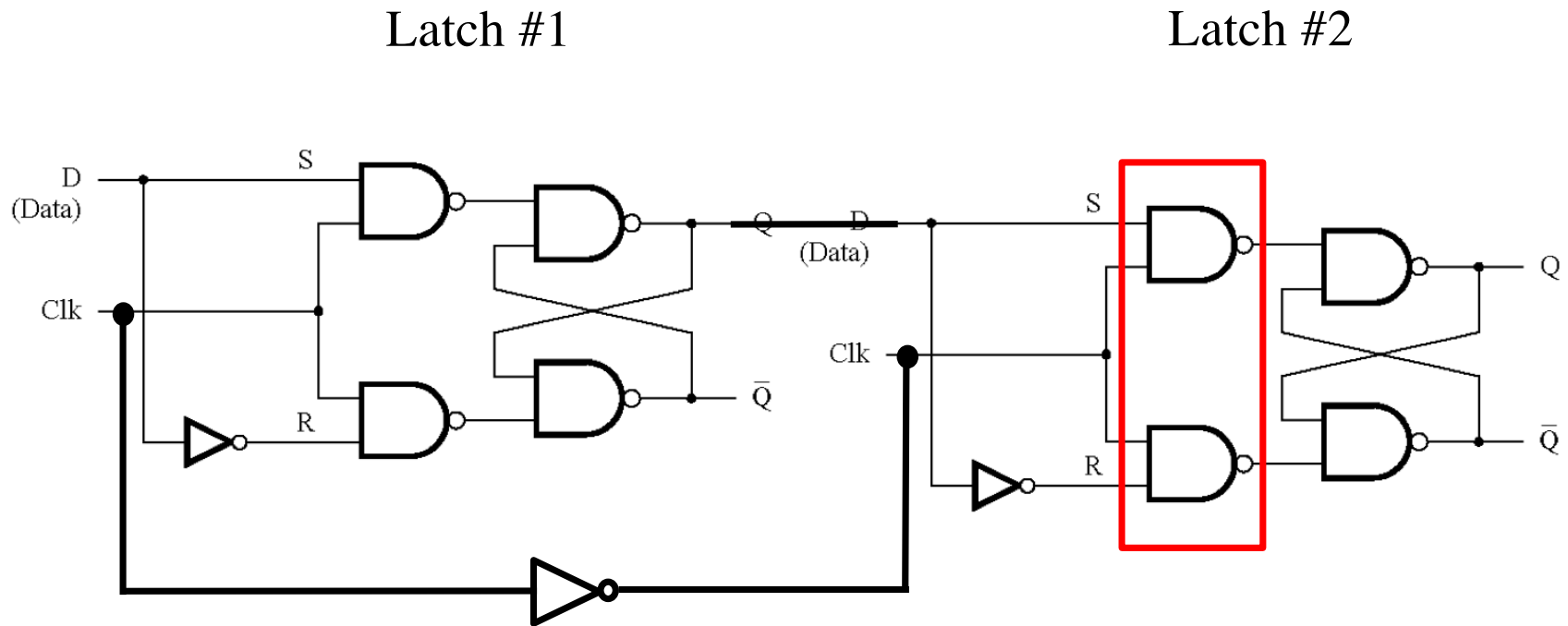
# Constructing a Master-Slave D Flip-Flop From Two D Latches



This is the  
second "gate"

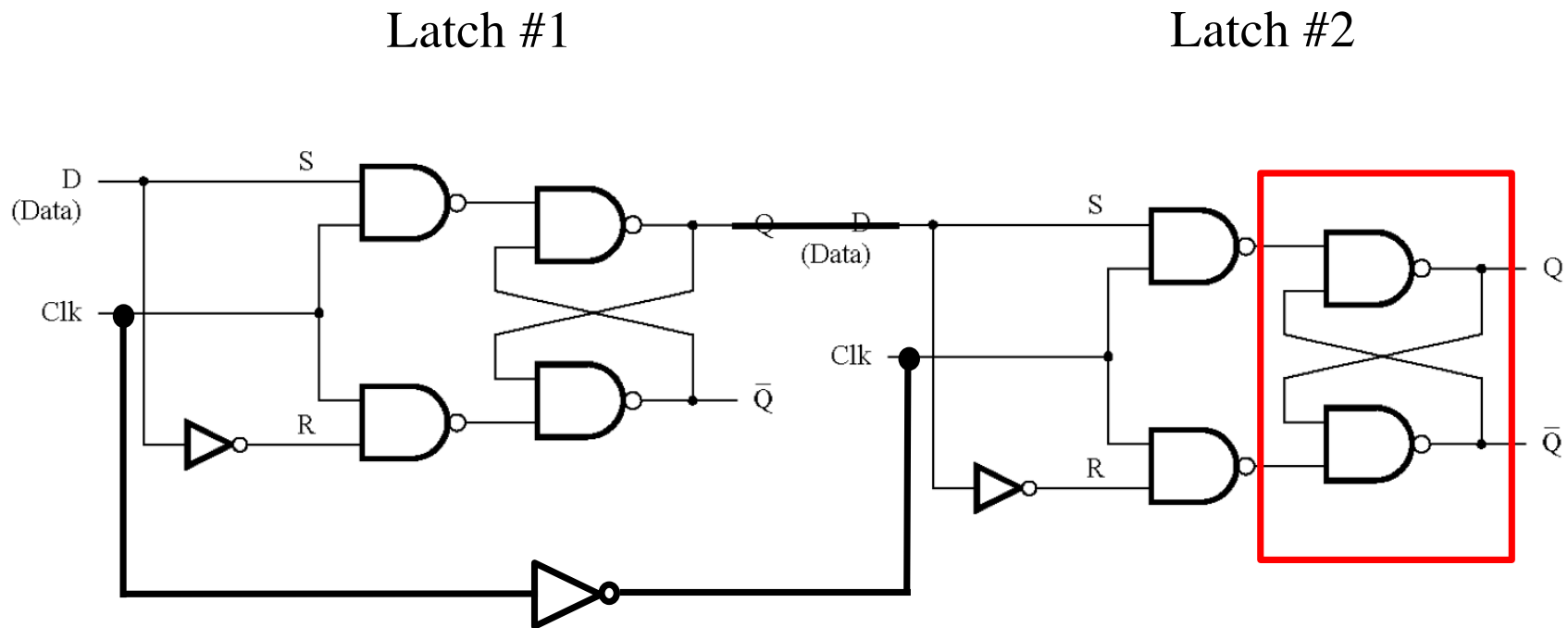
# Constructing a Master-Slave D Flip-Flop From Two D Latches



This is the  
second “snake”



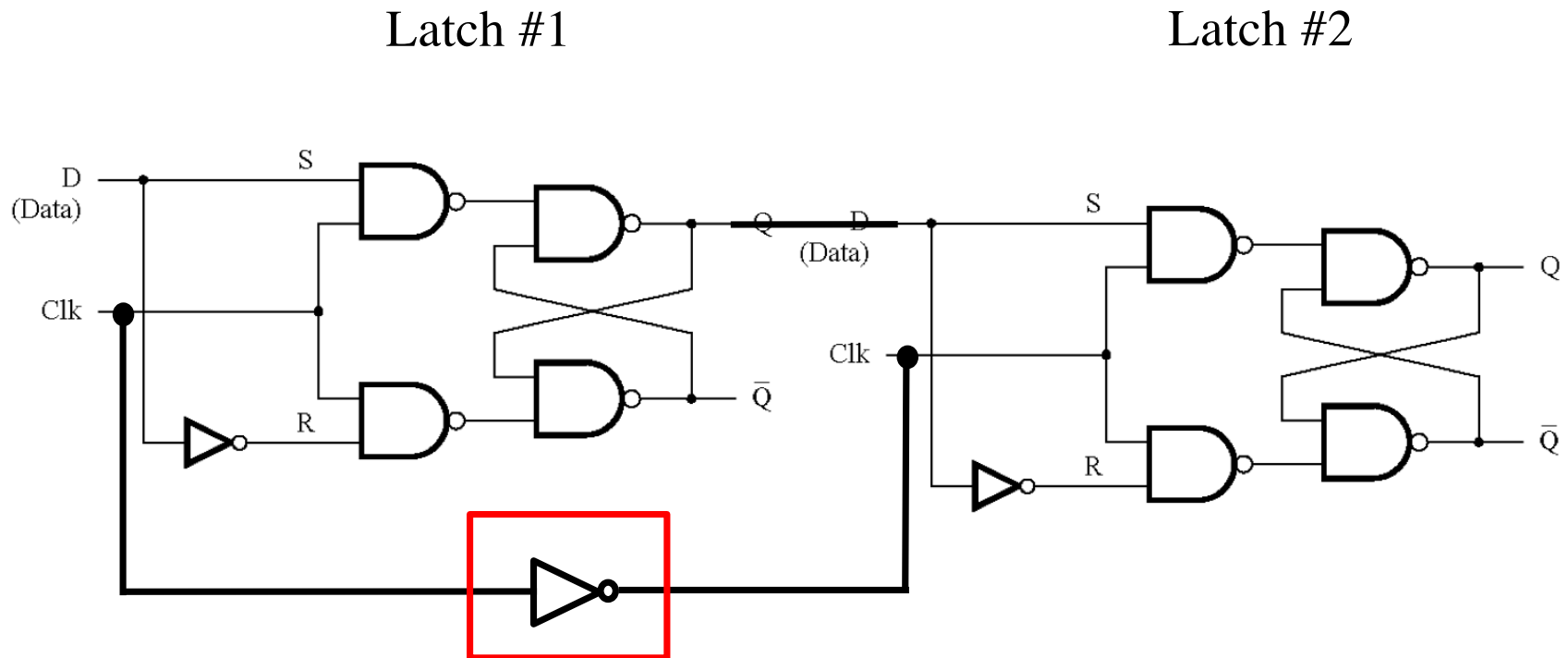
# Constructing a Master-Slave D Flip-Flop From Two D Latches




This imposes mutual exclusivity:  
only one gate is open at a time.
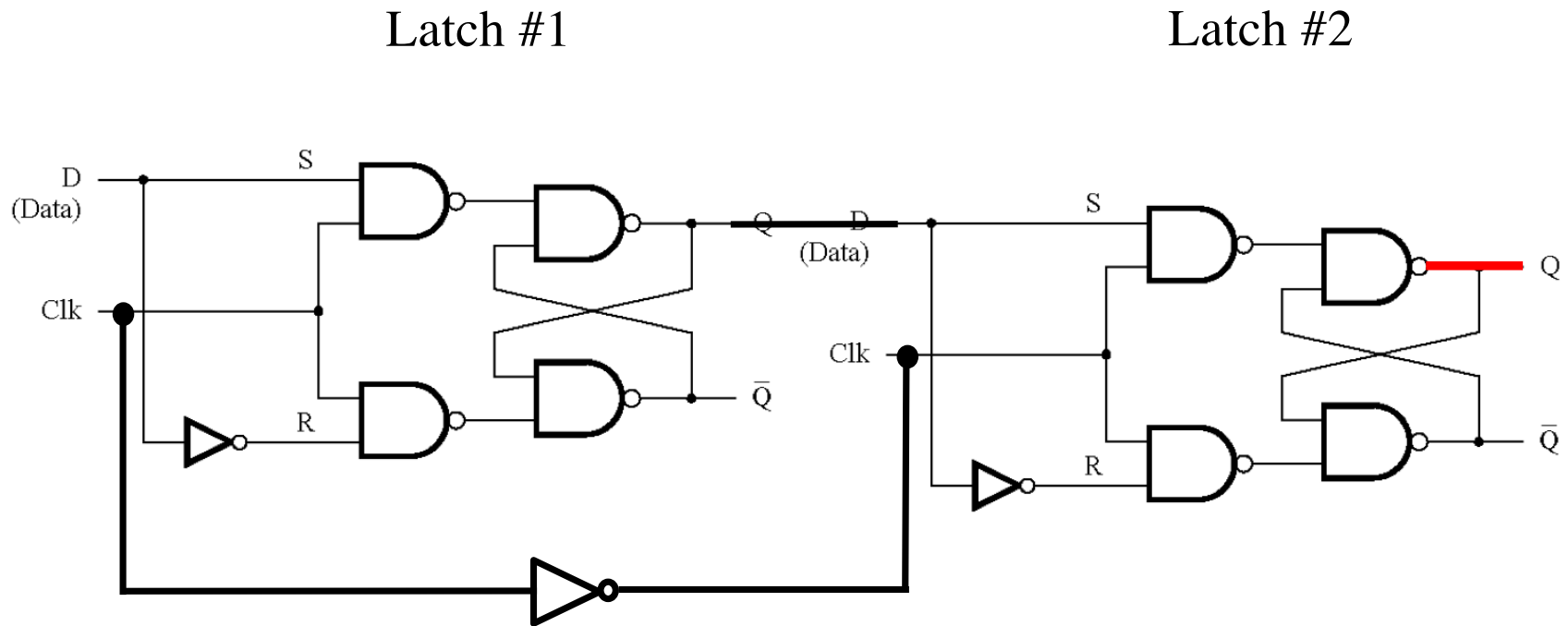
# Constructing a Master-Slave D Flip-Flop From Two D Latches




We need all of this  
to store only one bit here.
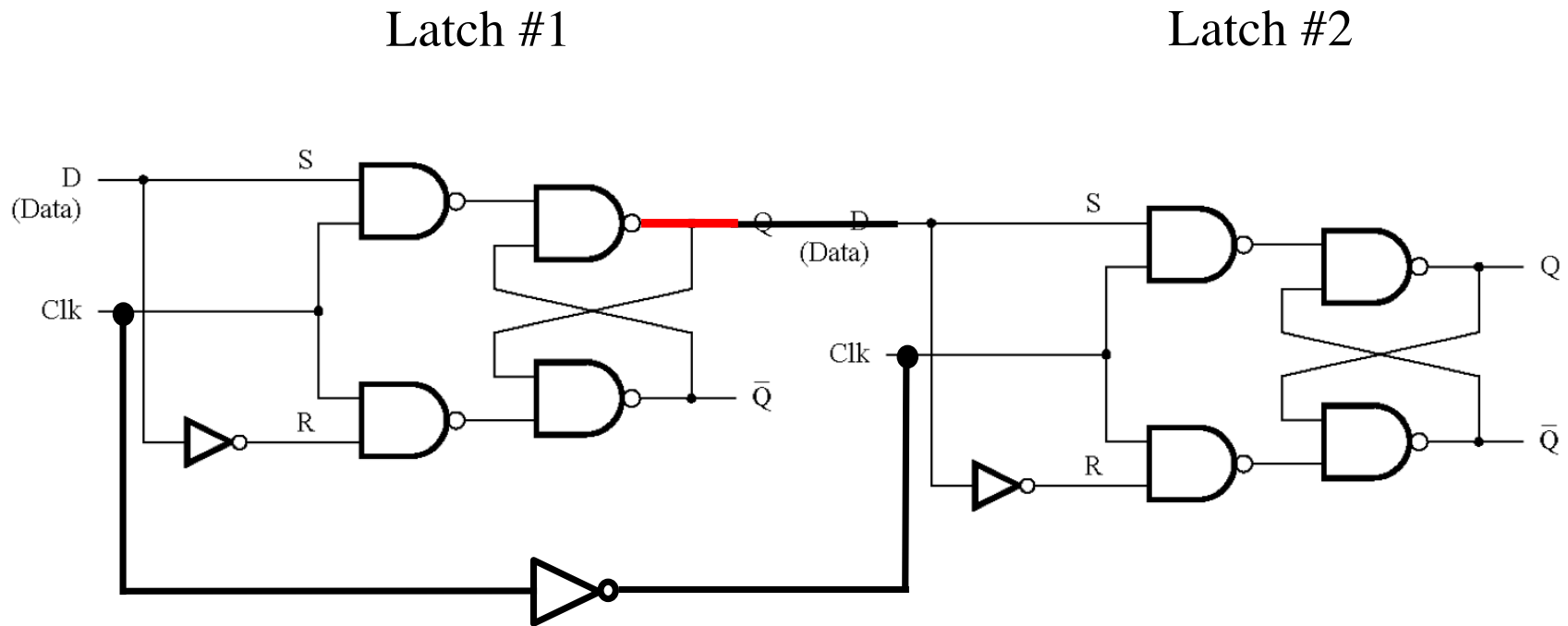
# Constructing a Master-Slave D Flip-Flop From Two D Latches




This also has the capacity to store one bit,  
but it is used to update the main output.
 
# Constructing a Master-Slave D Flip-Flop From Two D Latches




Only this bit is visible  
to the user of this circuit.

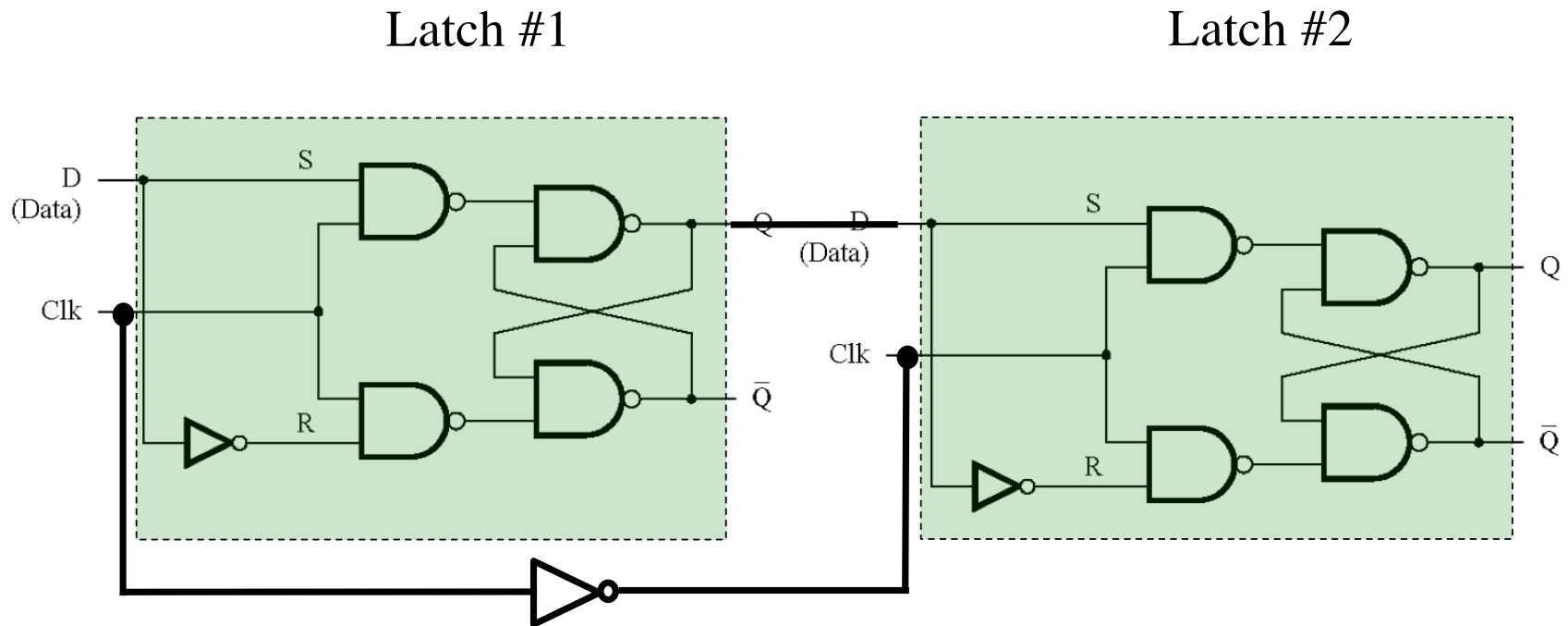
# Constructing a Master-Slave D Flip-Flop From Two D Latches



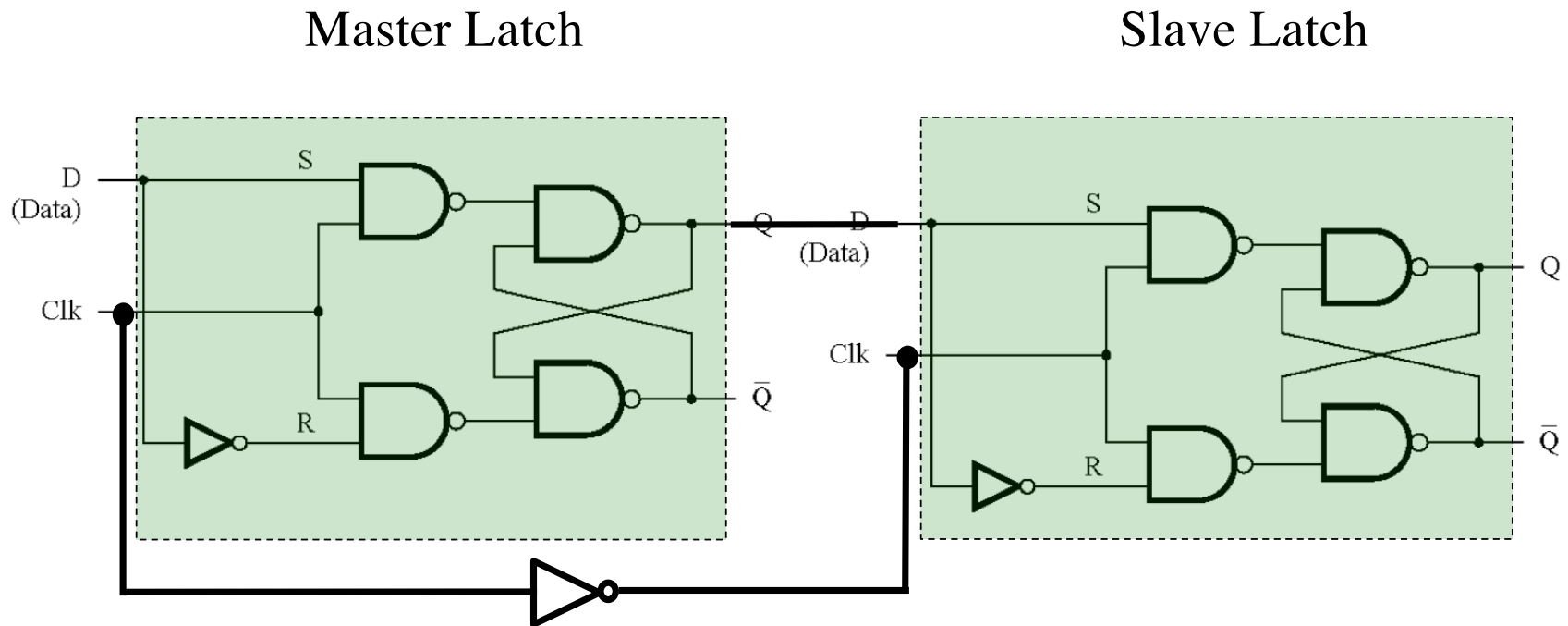
# Constructing a Master-Slave D Flip-Flop From Two D Latches


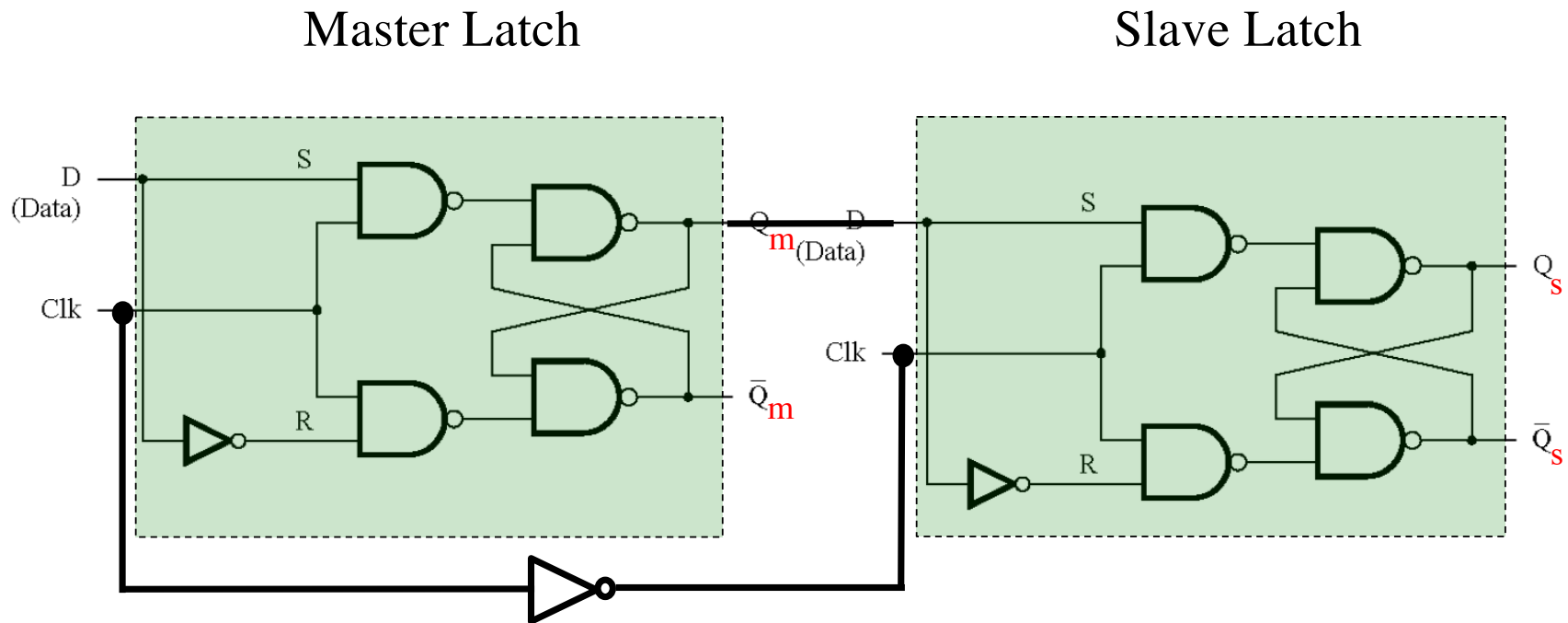
# Constructing a Master-Slave D Flip-Flop From Two D Latches




# Constructing a Master-Slave D Flip-Flop From Two D Latches

 

[ Figure 5.9a from the textbook ]




# Clock is used for the D Flip-Flop

 

[ Figure 5.9a from the textbook ]

# Clock is used for the D Flip-Flop, but **Clk** is used for each D Latch

 


[ Figure 5.9a from the textbook ]


# Constructing a Master-Slave D Flip-Flop From one D Latch and one Gated SR Latch

(This version uses one less NOT gate)

Master Latch

 


Slave Latch

 


# Constructing a Master-Slave D Flip-Flop From one D Latch and one Gated SR Latch

(This version uses one less NOT gate)

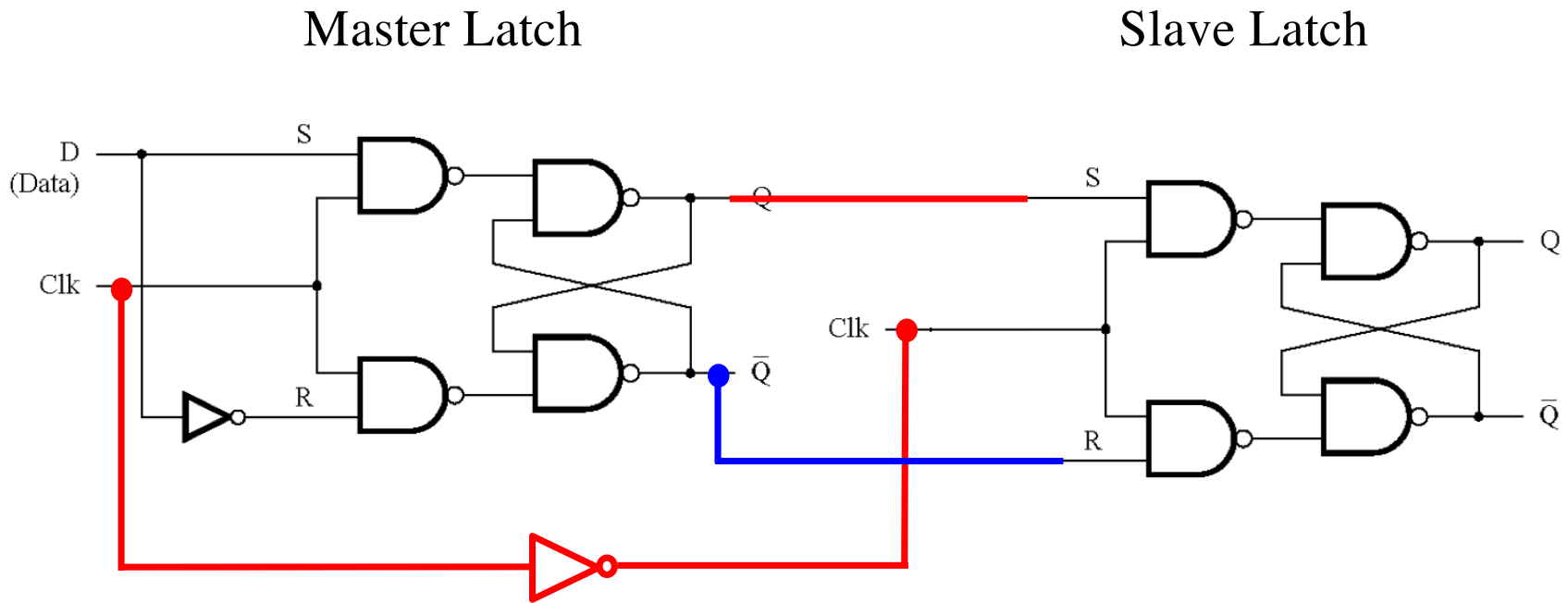


# Constructing a Master-Slave D Flip-Flop From one D Latch and one Gated SR Latch

(This version uses one less NOT gate)

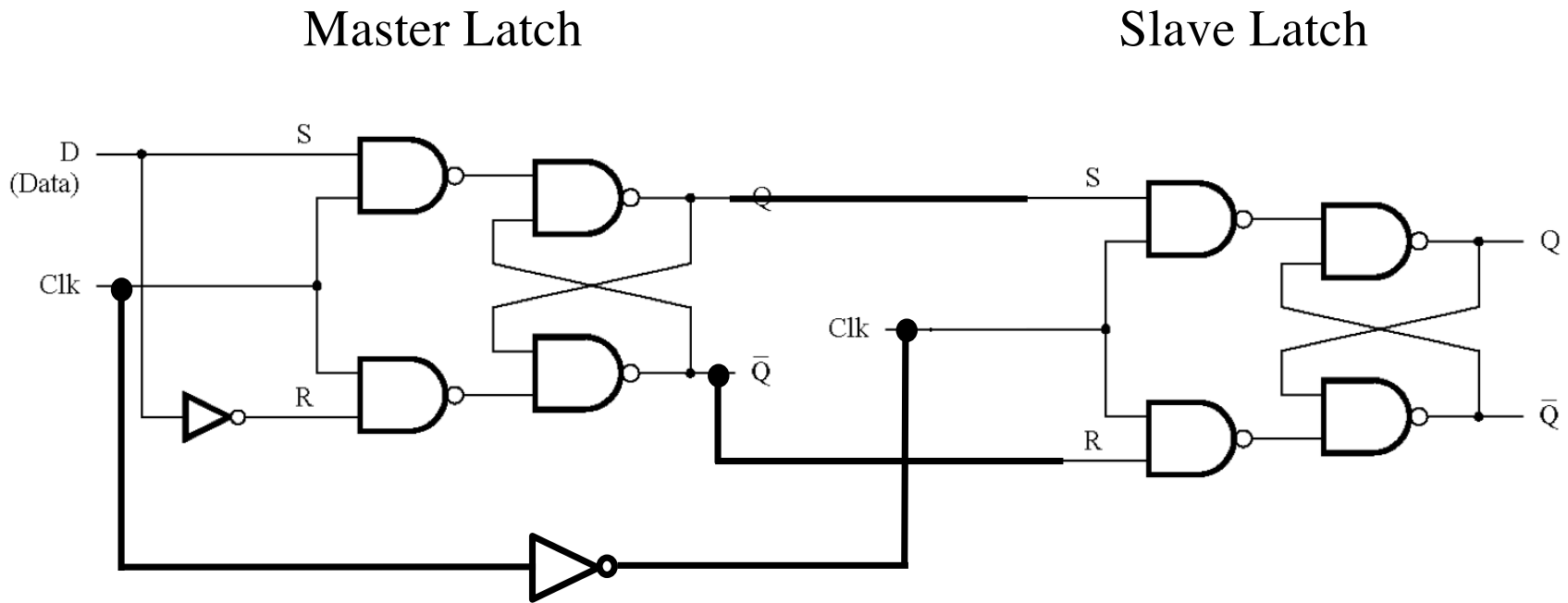

# Constructing a Master-Slave D Flip-Flop From one D Latch and one Gated SR Latch

(This version uses one less NOT gate)

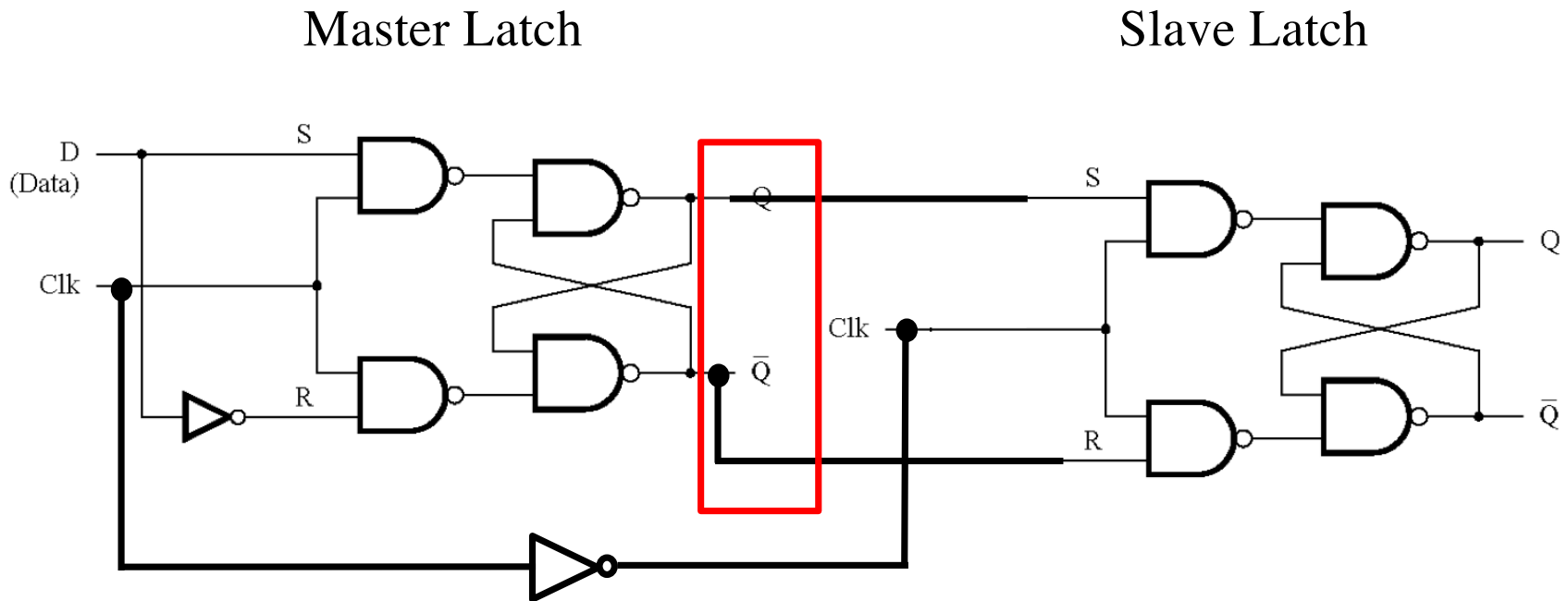

This uses the fact that  $Q$  and  $\bar{Q}$  are inverses of each other.

# Flip-Flop



[<https://www.ebay.com/itm/223956811053?chn=ps&mkevt=1&mkcid=28&var=522710005842>]

# Latch





**You need 2 latches to make a flip-flop**




**=**



# You need 2 latches to make a flip-flop

Master Latch


Slave Latch

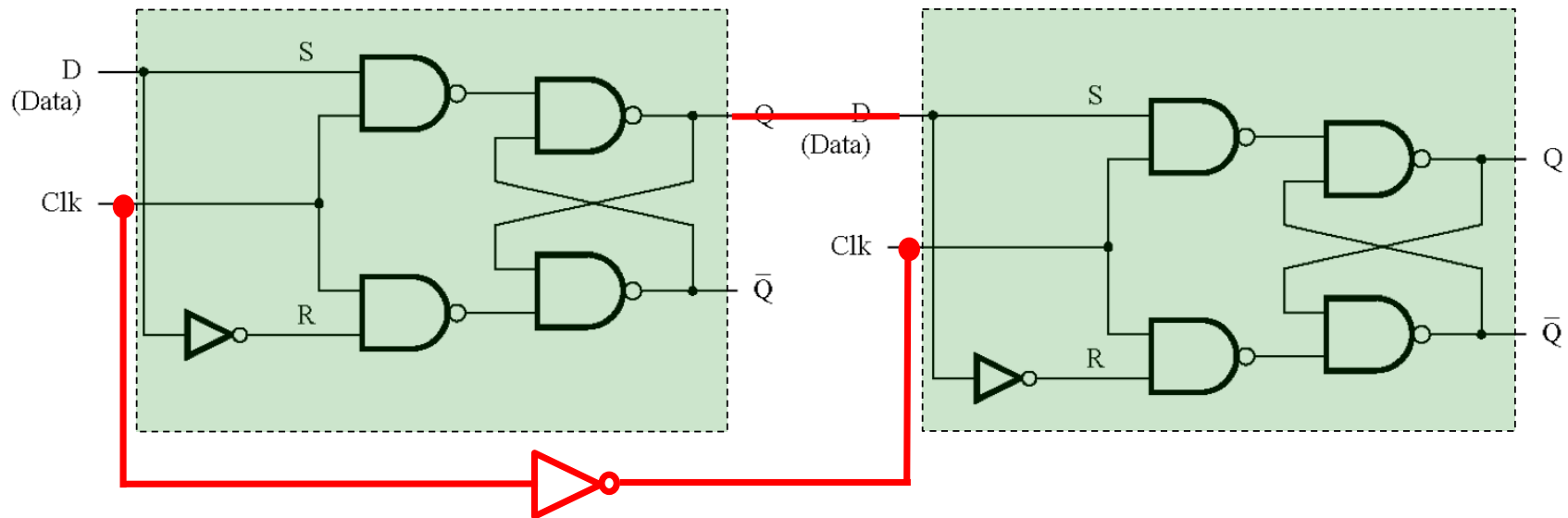

# You need 2 latches to make a flip-flop

Master Latch

Slave Latch

 

# You need 2 latches to make a flip-flop




# **Edge-Triggered D Flip-Flops**

# Motivation

**In some cases, we need to use a memory storage device that can change its state no more than once during each clock cycle.**



# Master-Slave D Flip-Flop

 

(a) Circuit

[ Figure 5.9a from the textbook ]


# Timing Diagram for the Master-Slave D Flip-Flop

  

[ Figure 5.9a,b from the textbook ]




# Graphical Symbol for the Master-Slave D Flip-Flop

 

[ Figure 5.9c from the textbook ]

 
# Graphical Symbol for the Master-Slave D Flip-Flop




The > means that this is edge-triggered

The small circle means that it is the negative edge

 
# Negative-Edge-Triggered Master-Slave D Flip-Flop



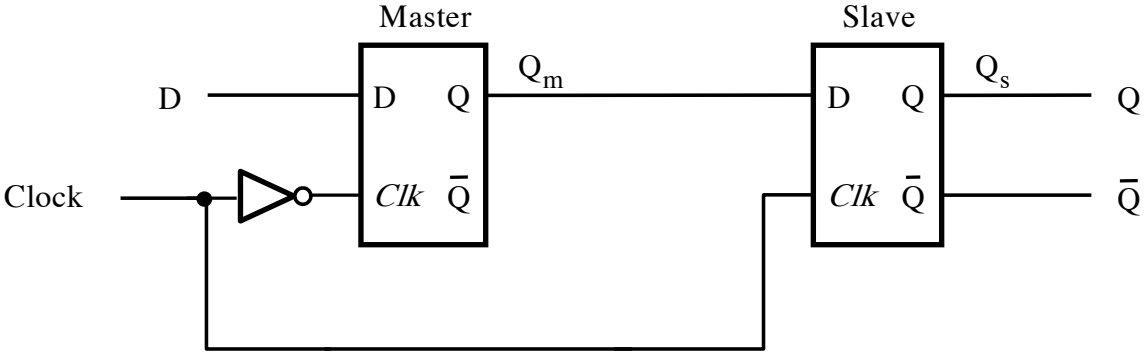
# Positive-Edge-Triggered Master-Slave D Flip-Flop



 
## Negative-Edge-Triggered Master-Slave D Flip-Flop


 
## Positive-Edge-Triggered Master-Slave D Flip-Flop




 
# Negative-Edge-Triggered Master-Slave D Flip-Flop



negative edge  
(of the Clock)

  
# Positive-Edge-Triggered Master-Slave D Flip-Flop




positive edge  
(of the Clock)

# **D Flip-Flop: A Double Door Analogy**
 
# Negative-Edge-Triggered Master-Slave D Flip-Flop



 
# Negative-Edge-Triggered Master-Slave D Flip-Flop






 
# Negative-Edge-Triggered Master-Slave D Flip-Flop



 
# Negative-Edge-Triggered Master-Slave D Flip-Flop



 
# Negative-Edge-Triggered Master-Slave D Flip-Flop


 
# Negative-Edge-Triggered Master-Slave D Flip-Flop



 
# Negative-Edge-Triggered Master-Slave D Flip-Flop





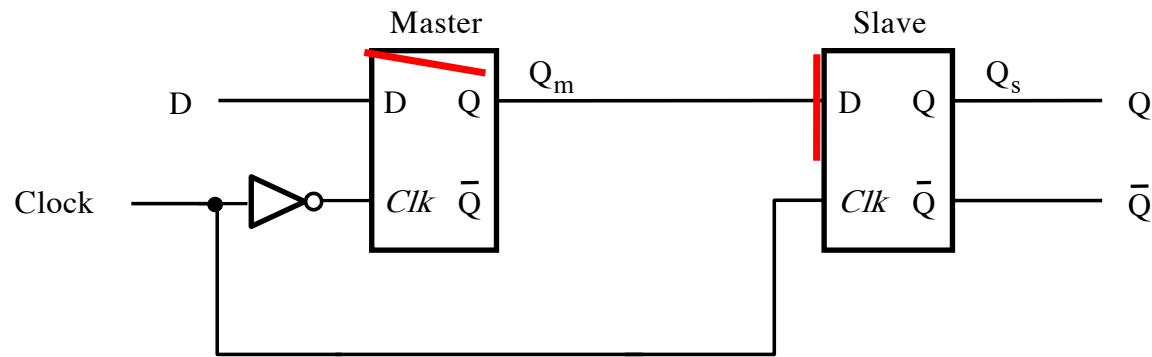
# Positive-Edge-Triggered Master-Slave D Flip-Flop



 
# Positive-Edge-Triggered Master-Slave D Flip-Flop






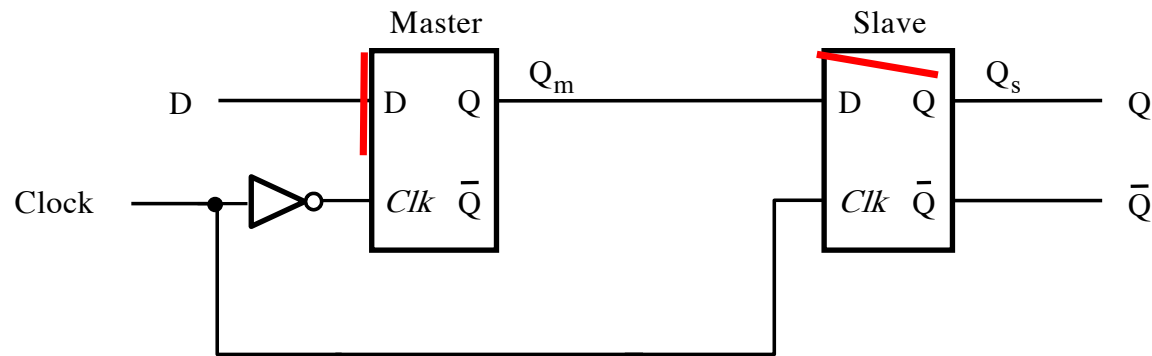
# Positive-Edge-Triggered Master-Slave D Flip-Flop



 
# Positive-Edge-Triggered Master-Slave D Flip-Flop



 
# Positive-Edge-Triggered Master-Slave D Flip-Flop


 
# Positive-Edge-Triggered Master-Slave D Flip-Flop



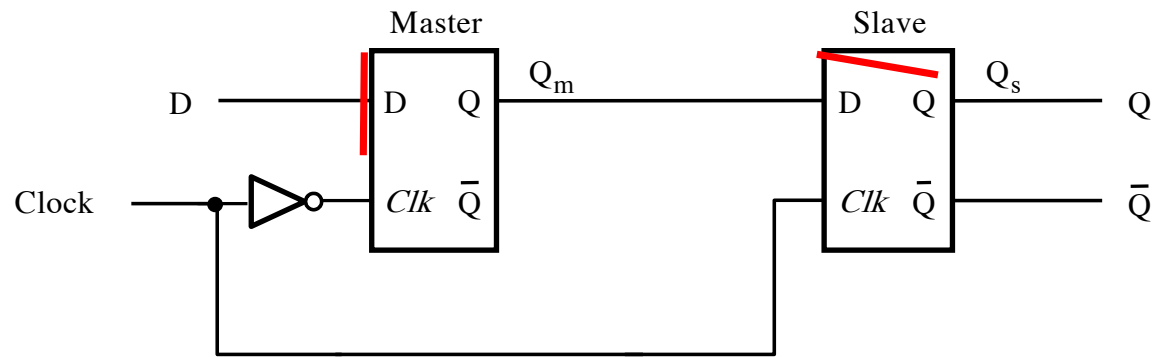
# Positive-Edge-Triggered Master-Slave D Flip-Flop




# **Adding the Data Line**
 
# Positive-Edge-Triggered Master-Slave D Flip-Flop




 
# Positive-Edge-Triggered Master-Slave D Flip-Flop







  
# Positive-Edge-Triggered Master-Slave D Flip-Flop



  
# Positive-Edge-Triggered Master-Slave D Flip-Flop



 
# Positive-Edge-Triggered Master-Slave D Flip-Flop


 
# Positive-Edge-Triggered Master-Slave D Flip-Flop





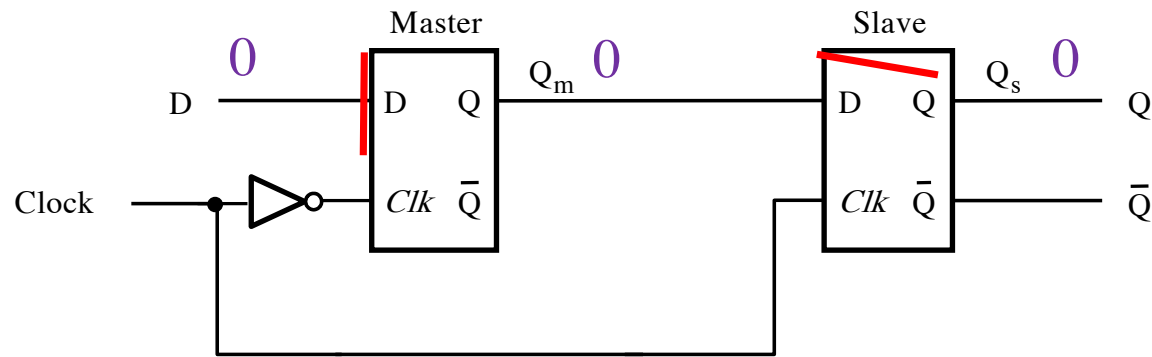
# Positive-Edge-Triggered Master-Slave D Flip-Flop



# **Level-Sensitive v.s. Edge-Triggered**

  
# Comparison of level-sensitive and edge-triggered D storage elements



 

 
## Comparison of level-sensitive and edge-triggered D storage elements

The D Latch is Level-Sensitive  
(the output mirrors the D input when Clk=1)






 
# Comparison of level-sensitive and edge-triggered D storage elements



 
Positive-edge-triggered D Flip-Flop  
(the output is equal to the value of D right at the positive edge of the clock signal)


 
# Comparison of level-sensitive and edge-triggered D storage elements




 Negative-edge-triggered D Flip-Flop  
(the output is equal to the value of D right at the negative edge of the clock signal)




# Summary

 
# The Complete Wiring Diagram for a Positive-Edge-Triggered D Flip-Flop


 
# The Complete Wiring Diagram for a **Negative**-Edge-Triggered D Flip-Flop


 
# The Complete Wiring Diagram for a **Negative**-Edge-Triggered D Flip-Flop



# Terminology

- **Basic Latch** – is a feedback connection of two NOR gates or two NAND gates, which can store one bit of information (it has two outputs, but they are inverses of each other). The primary output can be set to 1 using the S input and reset to 0 using the R input.
- **Gated Latch** – is a basic latch that includes input gating with a control input signal. The latch retains its existing state when the control input is equal to 0. Its state may be changed through the S and R inputs when the control signal is equal to 1.

# Terminology

- **Two types of gated latches**  
(the control input is the clock):
- **Gated SR Latch** – uses the S and R inputs to set the latch to 1 or reset it to 0.
- **Gated D Latch** – uses the D input to force the latch into a state that has the same logic value as the D input.



# Terminology

- **Flip-Flop** – is a storage element that can have its output state changed only on the edge of the controlling clock signal.
- **Positive-edge triggered** – if the state changes when the clock signal goes from 0 to 1.
- **Negative-edge triggered** – if the state changes when the clock signal goes from 1 to 0.

# Terminology

Both **latches** and **flip-flops** are storage elements. Each of them can store only one bit of information. However, they use different mechanisms to change the value of that bit.

A **latch** is level-sensitive, whereas a **flip-flop** is edge-sensitive. When a latch is enabled it becomes transparent, meaning that its output can be changed immediately given appropriate values of the inputs. And the output can change multiple times while the latch is enabled.

On the other hand, the output of a **flip-flop** changes only on a single type of clock edge (either positive going or negative going edge). The new output depends on the input values at the time of the clock edge.

[[http://en.wikipedia.org/wiki/Flip-flop\\_\(electronics\)](http://en.wikipedia.org/wiki/Flip-flop_(electronics))]

**Questions?**

**THE END**

**THE END**