

CprE 2810: Digital Logic

Instructor: Alexander Stoytchev

<http://www.ece.iastate.edu/~alexs/classes/>


Mealy State Model

*CprE 2810: Digital Logic
Iowa State University, Ames, IA
Copyright © Alexander Stoytchev*

Administrative Stuff


- **Homework 10 is due on Monday Nov 11 @ 10 pm**
- **Homework 11 is due on Monday Nov 18 @ 10 pm**

The general form of a synchronous sequential circuit

 


[Figure 6.1 from the textbook]

Moore Type

 

Mealy Type

 


Sample Problem


Implement a 11 detector. In other words, the output should be equal to 1 if two consecutive 1's have been detected on the input line.

The output should become 1 as soon as the second 1 is detected in the input.


Moore Machine Implementation

 


Clockcycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
w :	0	1	0	1	1	0	1	1	1	0	1
z :	0	0	0	0	0	1	0	0	1	1	0

 


Clockcycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
w :	0	1	0	1	1	0	1	1	1	0	1
z :	0	0	0	0	0	1	0	0	1	1	0

 


Clockcycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
w :	0	1	0	1	1	0	1	1	1	0	1
z :	0	0	0	0	0	1	0	0	1	1	0

 


Clockcycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
w :	0	1	0	1	1	0	1	1	1	0	1
z :	0	0	0	0	0	1	0	0	1	1	0

 


Clockcycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
w :	0	1	0	1	1	0	1	1	1	0	1
z :	0	0	0	0	0	1	0	0	1	1	0

 


Clockcycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
w :	0	1	0	1	1	0	1	1	1	0	1
z :	0	0	0	0	0	1	0	0	1	1	0

 


Clockcycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
w :	0	1	0	1	1	0	1	1	1	0	1
z :	0	0	0	0	0	1	0	0	1	1	0

 


Clockcycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
w :	0	1	0	1	1	0	1	1	1	0	1
z :	0	0	0	0	0	1	0	0	1	1	0

 


Clockcycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
w :	0	1	0	1	1	0	1	1	1	0	1
z :	0	0	0	0	0	1	0	0	1	1	0

 


Clockcycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
w :	0	1	0	1	1	0	1	1	1	0	1
z :	0	0	0	0	0	1	0	0	1	1	0

 

Clockcycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
w :	0	1	0	1	1	0	1	1	1	0	1
z :	0	0	0	0	0	1	0	0	1	1	0

 


Clockcycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
w :	0	1	0	1	1	0	1	1	1	0	1
z :	0	0	0	0	0	1	0	0	1	1	0

 


Clockcycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
w :	0	1	0	1	1	0	1	1	1	0	1
z :	0	0	0	0	0	1	0	0	1	1	0

Inferring the States

 

Clockcycle:	t ₀	t ₁	t ₂	t ₃	t ₄	t ₅	t ₆	t ₇	t ₈	t ₉	t ₁₀
w:	0	1	0	1	1	0	1	1	1	0	1
z:	0	0	0	0	0	1	0	0	1	1	0

 


[Figure 6.8 from the textbook]

The New and Improved Circuit Diagram

$$Y_1(w, y_2, y_1) = w$$

$$Y_2(w, y_2, y_1) = wy_1$$


$$z(y_2, y_1) = y_2$$

 

[Figure 6.17 from the textbook]

Mealy Machine Implementation


State diagram of an FSM that realizes the task

 

[Figure 6.23 from the textbook]


Let's Do a Simulation

Clock cycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}	
input w :	<input type="checkbox"/>	0	1	0	1	1	0	1	1	1	0	1
output z :	0	0	0	0	1	0	0	1	1	0	0	

 


Let's Do a Simulation

Clock cycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
input w :	0	1	0	1	1	0	1	1	1	0	1
output z :	0	0	0	0	1	0	0	1	1	0	0

 


Let's Do a Simulation

Clock cycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
input w :	0	1	0	1	1	0	1	1	1	0	1
output z :	0	0	0	0	1	0	0	1	1	0	0

 


Let's Do a Simulation

Clock cycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
input w :	0	1	0	1	1	0	1	1	1	0	1
output z :	0	0	0	0	1	0	0	1	1	0	0

 


Let's Do a Simulation

Clock cycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
input w :	0	1	0	1	1	0	1	1	1	0	1
output z :	0	0	0	0	1	0	0	1	1	0	0

 


Let's Do a Simulation

Clock cycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
input w :	0	1	0	1	1	0	1	1	1	0	1
output z :	0	0	0	0	1	0	0	1	1	0	0

 


Let's Do a Simulation

Clock cycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
input w :	0	1	0	1	1	0	1	1	1	0	1
output z :	0	0	0	0	1	0	0	1	1	0	0

 


Let's Do a Simulation

Clock cycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
input w :	0	1	0	1	1	0	1	1	1	0	1
output z :	0	0	0	0	1	0	0	1	1	0	0

 


Let's Do a Simulation

Clock cycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
input w :	0	1	0	1	1	0	1	1	1	0	1
output z :	0	0	0	0	1	0	0	1	1	0	0

 


Let's Do a Simulation

Clock cycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
input w :	0	1	0	1	1	0	1	1	1	0	1
output z :	0	0	0	0	1	0	0	1	1	0	0

 


Let's Do a Simulation

Clock cycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
input w :	0	1	0	1	1	0	1	1	1	0	1
output z :	0	0	0	0	1	0	0	1	1	0	0

 


Let's Do a Simulation

Clock cycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
input w :	0	1	0	1	1	0	1	1	1	0	1
output z :	0	0	0	0	1	0	0	1	1	0	0

 


Let's Do a Simulation

Clock cycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
input w :	0	1	0	1	1	0	1	1	1	0	1
output z :	0	0	0	0	1	0	0	1	1	0	0

 


Let's Do a Simulation

Clock cycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
input w :	0	1	0	1	1	0	1	1	1	0	1
output z :	0	0	0	0	1	0	0	1	1	0	0

 


Let's Do a Simulation

Clock cycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
input w :	0	1	0	1	1	0	1	1	1	0	1
output z :	0	0	0	0	1	0	0	1	1	0	0

 


Let's Do a Simulation

Clock cycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
input w :	0	1	0	1	1	0	1	1	1	0	1
output z :	0	0	0	0	1	0	0	1	1	0	0

 


Let's Do a Simulation

Clock cycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
input w :	0	1	0	1	1	0	1	1	1	0	1
output z :	0	0	0	0	1	0	0	1	1	0	0

 


Let's Do a Simulation

Clock cycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
input w :	0	1	0	1	1	0	1	1	1	0	1
output z :	0	0	0	0	1	0	0	1	1	0	0

 


Let's Do a Simulation

Clock cycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
input w :	0	1	0	1	1	0	1	1	1	0	1
output z :	0	0	0	0	1	0	0	1	1	0	0

 


 Now Let's Do the State Table for this FSM



Present state	Next state		Output z	
	$w = 0$	$w = 1$	$w = 0$	$w = 1$
A				
B				

 Now Let's Do the State Table for this FSM



Present state	Next state		Output z	
	$w = 0$	$w = 1$	$w = 0$	$w = 1$
A	A	B	0	0
B	A	B	0	1

The State Table for this FSM

Present state	Next state		Output z	
	$w = 0$	$w = 1$	$w = 0$	$w = 1$
A	A	B	0	0
B	A	B	0	1

[Figure 6.24 from the textbook]

Let's Do the State-assigned Table

Present state	Next state		Output z	
	$w = 0$	$w = 1$	$w = 0$	$w = 1$
A	A	B	0	0
B	A	B	0	1

Present state	Next state		Output	
	$w = 0$	$w = 1$	$w = 0$	$w = 1$
y	Y	Y	z	z
A 0				
B 1				

Let's Do the State-assigned Table

Present state	Next state		Output z	
	$w = 0$	$w = 1$	$w = 0$	$w = 1$
A	A	B	0	0
B	A	B	0	1

Present state	Next state		Output	
	$w = 0$	$w = 1$	$w = 0$	$w = 1$
y	Y	Y	z	z
A	0	1	0	0
B	1	1	0	1

The State-assigned Table

	Present state	Next state		Output	
		$w = 0$	$w = 1$	$w = 0$	$w = 1$
	y	Y	Y	z	z
A	0	0	1	0	0
B	1	0	1	0	1

[Figure 6.25 from the textbook]

The State-assigned Table

	Present state	Next state		Output	
		$w = 0$	$w = 1$	$w = 0$	$w = 1$
	y	Y	Y	z	z
A	0	0	1	0	0
B	1	0	1	0	1

$$Y = D = w \quad z = wy$$

[Figure 6.25 from the textbook]

The State-assigned Table


	Present state	Next state		Output	
		$w = 0$	$w = 1$	$w = 0$	$w = 1$
	y	Y	Y	z	z
A	0	0	1	0	0
B	1	0	1	0	1

$$Y = D = w \quad z = wy$$

This assumes D flip-flop

[Figure 6.25 from the textbook]


Circuit Implementation of the FSM

 


$$Y = D = w \quad z = wy$$

[Figure 6.26 from the textbook]

Circuit & Timing Diagram

 

(a) Circuit

 


(b) Timing diagram

[Figure 6.26 from the textbook]


What if we wanted the output signal to be delayed by 1 clock cycle?

Circuit Implementation of the Modified FSM

 

[Figure 6.27a from the textbook]

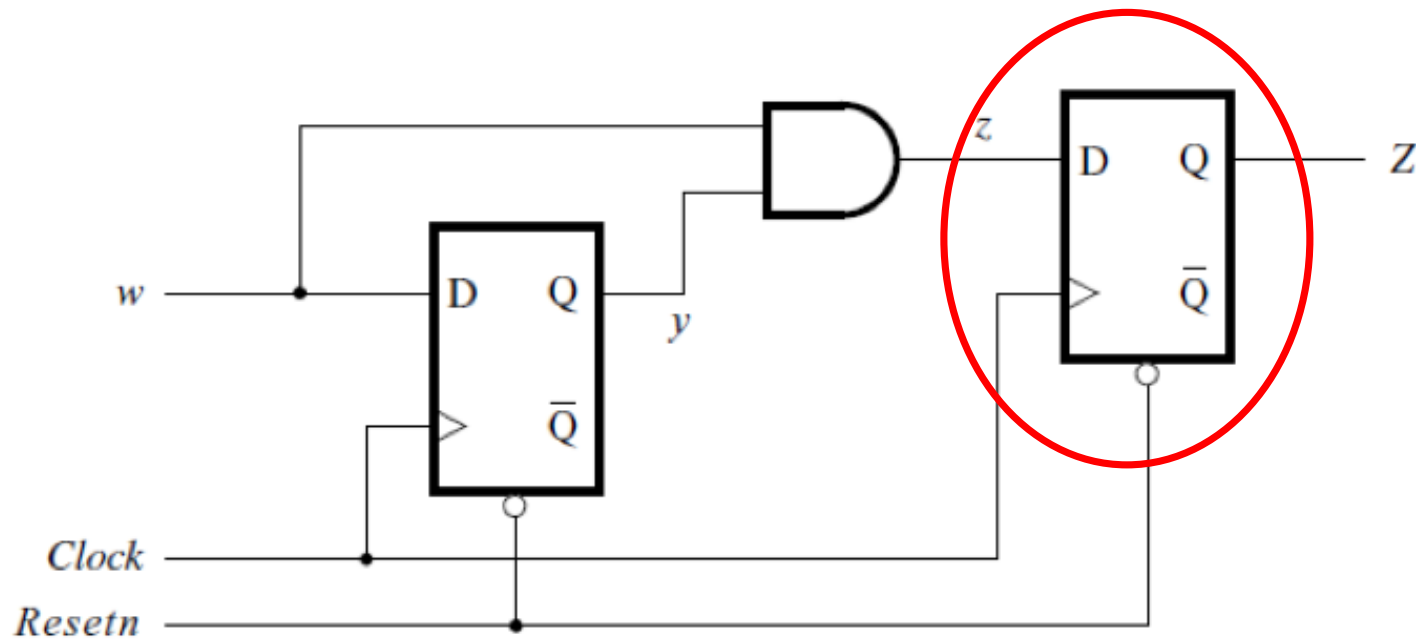Circuit Implementation of the Modified FSM



This flip-flop delays the output signal by one clock cycle


[Figure 6.27a from the textbook]

We Have Seen This Diagram Before

$$Y_1(w, y_2, y_1) = w$$


$$Y_2(w, y_2, y_1) = wy_1$$

$$z(y_2, y_1) = y_2$$

 


[Figure 6.17 from the textbook]

Circuit & Timing Diagram

 


(a) Circuit

 


[Figure 6.27 from the textbook]

The general form of a synchronous sequential circuit

 


[Figure 6.1 from the textbook]


Moore Type

 


Mealy Type

 



Moore

 



Mealy

 


Moore

  


Mealy

  

Mealy

 


Moore

 


Notice that the output of the Moore machine is delayed by one clock cycle

Mealy

 

Moore

 

Notice that the output of the Moore machine is delayed by one clock cycle

Mealy

Clock cycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
input w :	0	1	0	1	1	0	1	1	1	0	1
output z :	0	0	0	0	1	0	0	1	1	0	0

Moore

Clockcycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
input w :	0	1	0	1	1	0	1	1	1	0	1
output z :	0	0	0	0	0	1	0	0	1	1	0

Questions?

THE END