

P1. (10 points) Given the functions $f_1 = \bar{x}y\bar{z} + xy + xz$ and $f_2 = x(y + z) + \bar{x}(\bar{y} + \bar{z})$


- Draw the truth table for each function.
- Draw the Venn diagram for each function.

P2. (10 points) Prove the following using Boolean Algebra:

A. $(A + B)(A + C)(A + D) + \bar{A}BC + BCD = A + BC$

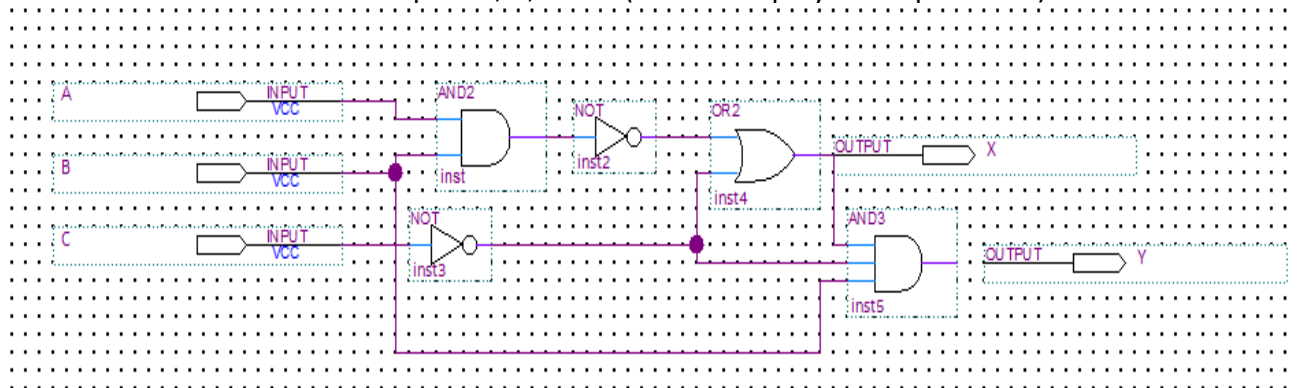B. $\overline{(AB + CD)} + \overline{ACD} + \overline{BCD} = \bar{A} + \bar{B} + \bar{C} + \bar{D}$

P3. (10 points) Given the circuit below, find the Boolean expressions for the two outputs X and Y in terms of the three inputs A, B, and C (do not simplify the expressions):



P4. (20 points) Given the following truth table, show the following:

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

- Canonical Sum-of-Products expression
- Shorthand Notation for SOP
- Canonical Products-of-Sum expression
- Shorthand Notation for POS

P5. **(15 points)** Given the following function $F = AB + \overline{B}C$

- A. Draw the circuit using only AND, OR, or NOT gates
- B. Convert F into Canonical POS expression
- C. Draw the new circuit using the expression you created in part B

P6. **(15 points)** Given the following function $F = (\overline{A} + B)(\overline{B} + C)C$

- A. Draw the circuit using only AND, OR, or NOT gates
- B. Convert F into an SOP expression (need not be the Canonical SOP expression)
- C. Draw the new circuit using the expression you created in part B

P7. **(20 points)** Consider the logic function $f(w, x, y, z) = \sum m(0,1,2,6,7,8,12,13,14,15)$.

- A. Write the canonical Sum-Of-Products for the function above.
- B. Simplify f using Boolean algebra.
- C. Draw the logic circuit for the simplified version of f in Part B.
- D. Let the cost of a logic circuit be the total number of gates plus the total number of inputs to all gates in the circuit. What is the cost of the simplified circuit?