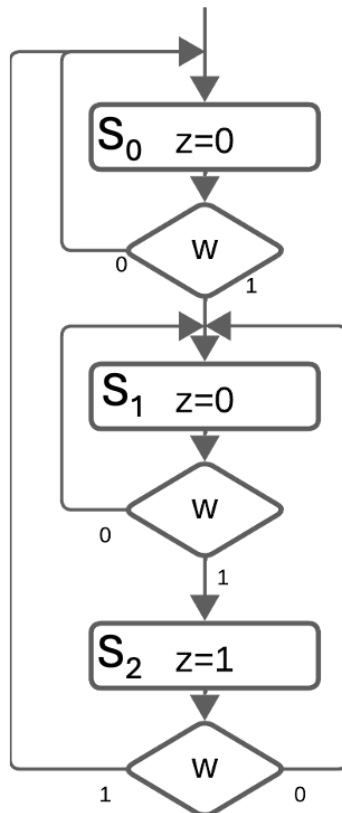


## Instructions

Complete the questions below to the best of your ability. Upload a PDF of your work to canvas.

## Questions

**P1 (15 points):** The following ASM chart describes the control logic of a micro-chip.




- a) (5 points) Is this a Moore or a Mealy machine? Justify your answer.
- b) (5 points) Draw an equivalent state diagram of this chip.
- c) (5 points) Derive the state table for this chip.

**P2 (20 points):** Design a synchronous 3-bit counter that cycles through the following sequence:  $2 \rightarrow 4 \rightarrow 6 \rightarrow 1 \rightarrow 3 \rightarrow 5 \rightarrow 7$  and then repeats. Use JK Flip-Flops.

 - a) (5 points) Draw the state diagram.
- b) (10 points) Derive the state-assigned table and the JK excitation table for all three Flip-Flops.
- c) (5 points) Write the simplified logic expressions for the J and K inputs of the most significant bit (MSB) Flip-Flop.

**P3 (15 points):** Derive the state table for the following circuit that uses positive-edge-triggered D Flip-Flops. What sequence of input values (W) causes the output Z to become 1? Assume the initial state (after reset) is  $Q1\ Q0 = 00$ .



- (10 points) Derive the state-assigned table and state table. (Present State  $Q1\ Q0$ , Input  $w$ , Next State  $Y1\ Y0$ , Output  $z$ ).
- (5 points) Draw the state diagram of this circuit.

**P4 (20 points):** Design an FSM with a single input  $W$  and an output  $Z$ . The circuit should detect three consecutive 1s on  $W$ . If  $W=1$  for three or more consecutive clock cycles,  $Z$  should be 1. Otherwise,  $Z$  should be 0. Your circuit must use two positive-edge-triggered T Flip-Flops and a minimal number of other gates.

- (5 points) Draw the state diagram. Don't forget the reset signal. Label states clearly (e.g.,  $S0, S1, S2$ ).
- (10 points) Derive the state-assigned table. This table must include the present state, input, next state, output, and the excitation values for the T Flip-Flops.
- (5 points) Write the simplified logic expressions for the T inputs ( $T1, T0$ ) and the output  $Z$ .

**P5 (30 points):** Consider a counter that has a special counting sequence: 0,4,5,1,0,4,5,1, and so on. Design this counter with minimal number of states.

- (5 points) Draw the state diagram for the counter
- (5 points) Construct the state-assigned table including the next state and output
- (10 points) Draw the circuit diagram using T flip-flops
- (10 points) Draw the circuit diagram using JK flip-flops