

CprE 2810: Digital Logic

Instructor: Alexander Stoytchev

<http://www.ece.iastate.edu/~alexs/classes/>

Synthesis

Using AND, OR, and NOT Gates

CprE 2810: Digital Logic
Iowa State University, Ames, IA
Copyright © Alexander Stoytchev

Administrative Stuff


- **HW2 is due on Monday Sep 8 @ 10pm**
- **Please write clearly on the first page the following three things:**
 - **Your First and Last Name**
 - **Your Student ID Number**
 - **Your Lab Section Letter**
- **Submit on Canvas as *one* PDF file.**
- **Please orient your pages such that the text can be read without the need to rotate the page.**

Administrative Stuff


- **Next week we will start with Lab2**
- **Read the lab assignment and do the prelab at home.**
- **Complete the prelab on paper before you go to the lab. Otherwise you'll lose 20% of your grade for that lab.**

Quick Review


The Three Basic Logic Gates

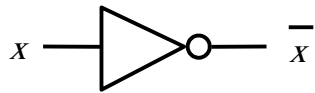

NOT gate

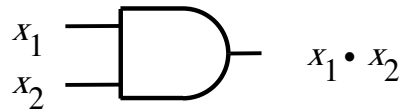


AND gate

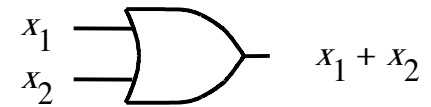


OR gate

Truth Table for NOT

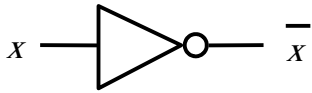


x	\overline{x}
0	1
1	0

Truth Table for AND

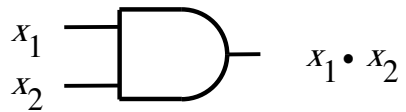

x_1	x_2	$x_1 \cdot x_2$
0	0	0
0	1	0
1	0	0
1	1	1

Truth Table for OR

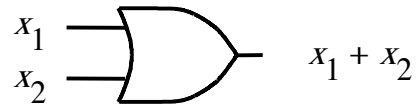

x_1	x_2	$x_1 + x_2$
0	0	0
0	1	1
1	0	1
1	1	1


Truth Tables for AND and OR

x_1	x_2	$x_1 \cdot x_2$	$x_1 + x_2$
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	1

AND

OR

Boolean Algebra

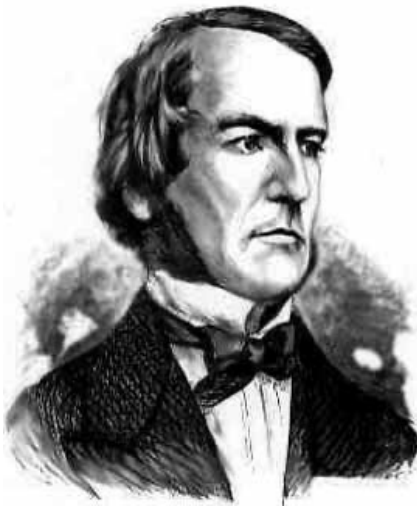

George Boole
1815-1864

- **An algebraic structure consists of**
 - a set of elements $\{0, 1\}$
 - binary operators $\{+, \bullet\}$
 - and a unary operator $\{ ' \}$ or $\{ \neg \}$ or $\{ \sim \}$
- **Introduced by George Boole in 1854**
- **An effective means of describing circuits built with switches**
- **A powerful tool that can be used for designing and analyzing logic circuits**

Different Notations for Negation

- All three of these mean “negate x”

- x'

- \overline{x}

- $\sim x$

Operator Precedence

- In regular arithmetic and algebra, multiplication takes precedence over addition.
- This is also true in Boolean algebra.
- For example, $x + y \cdot z$ means
multiply y by z and add the product to x .
- In other words, $x + y \cdot z$ is equal to $x + (y \cdot z)$,
not $(x + y) \cdot z$.

The multiplication dot is optional

- In regular algebra, the multiplication operator is often omitted to shorten the equations.
- This is also true in Boolean algebra.
- Both of these mean the same thing:
 xy is equal to $x \cdot y$

Operator Precedence

(three different ways to write the same)

$$x_1 \cdot x_2 + \bar{x}_1 \cdot \bar{x}_2$$

$$(x_1 \cdot x_2) + ((\bar{x}_1) \cdot (\bar{x}_2))$$

$$x_1 x_2 + \bar{x}_1 \bar{x}_2$$

Operator Precedence

- Negation of a single variable takes precedence over multiplication of that variable with another variable.
- For example,

$\overline{A} B$ means negate A first and then multiply \overline{A} by B

Operator Precedence

- However, a horizontal bar over a product of two variables means that the negation is performed after the product is computed.
- For example,

$\overline{A B}$ means multiply A and B and then negate

Operator Precedence

- Note that these two expressions are different:

$\overline{A B}$ is not equal to $\overline{A} \overline{B}$

$\overline{A B}$ means multiply A and B and then negate

$\overline{A} \overline{B}$ means negate A and B separately and then multiply

Operator Precedence

- Note that these two expressions are different:

\overline{AB} is not equal to $\overline{A}\overline{B}$

A	B	\overline{AB}
0	0	1
0	1	1
1	0	1
1	1	0

A	B	$\overline{A}\overline{B}$
0	0	1
0	1	0
1	0	0
1	1	0

DeMorgan's Theorem

$$15a. \quad \overline{x \cdot y} = \bar{x} + \bar{y}$$

$$15b. \quad \overline{x + y} = \bar{x} \cdot \bar{y}$$

Proof of DeMorgan's theorem

15a. $\overline{x \cdot y} = \bar{x} + \bar{y}$

x	y	$x \cdot y$	$\overline{x \cdot y}$	\bar{x}	\bar{y}	$\bar{x} + \bar{y}$
0	0	0	1	1	1	1
0	1	0	1	1	0	1
1	0	0	1	0	1	1
1	1	1	0	0	0	0

⏟

LHS

⏟

RHS

Proof of DeMorgan's theorem

$$15a. \quad \overline{x \cdot y} = \bar{x} + \bar{y}$$

x	y	$x \cdot y$	$\overline{x \cdot y}$	\bar{x}	\bar{y}	$\bar{x} + \bar{y}$
0	0	0	1	1	1	1
0	1	0	1	1	0	1
1	0	0	1	0	1	1
1	1	1	0	0	0	0
			LHS		RHS	


These two columns are equal. Therefore, the theorem is true.

How to remember DeMorgan's theorem

$$\overline{x \cdot y}$$

start with the
left-hand side

How to remember DeMorgan's theorem

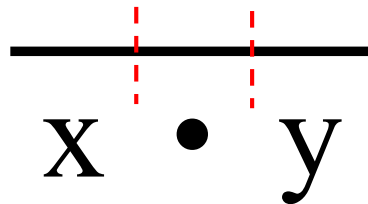

divide the bar
into 3 equal parts

How to remember DeMorgan's theorem

$$\overline{x} \cdot \overline{y}$$

erase the
middle segment

How to remember DeMorgan's theorem

$$\overline{x} + \overline{y}$$

change the
product to a sum

How to remember DeMorgan's theorem

$$\overline{x} + \overline{y}$$

this is the
right-hand side


How to remember DeMorgan's theorem

$$\overline{x \cdot y} = \overline{x} + \overline{y}$$


Proof of the other DeMorgan's theorem

15b. $\overline{x + y} = \bar{x} \cdot \bar{y}$

x	y	$x + y$	$\overline{x + y}$	\bar{x}	\bar{y}	$\bar{x} \cdot \bar{y}$
0	0	0	1	1	1	1
0	1	1	0	1	0	0
1	0	1	0	0	1	0
1	1	1	0	0	0	0



LHS



RHS

Proof of the other DeMorgan's theorem

15b. $\overline{x + y} = \bar{x} \cdot \bar{y}$

x	y	$x + y$	$\overline{x + y}$	\bar{x}	\bar{y}	$\bar{x} \cdot \bar{y}$
0	0	0	1	1	1	1
0	1	1	0	1	0	0
1	0	1	0	0	1	0
1	1	1	0	0	0	0


LHS

RHS


These two columns are equal. Therefore, the theorem is true.

A Short Digression


The 2D Plane

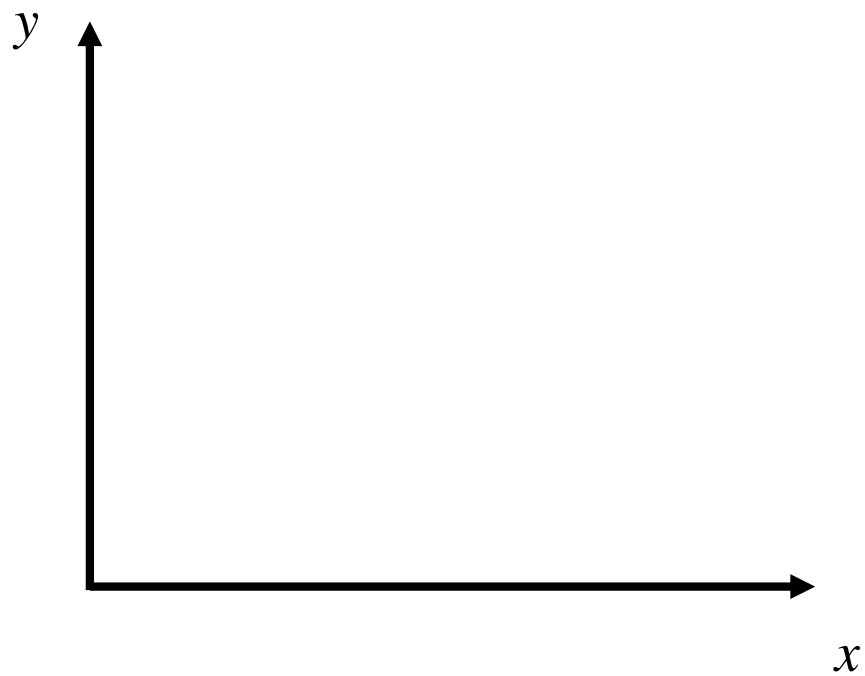


The 2D Plane

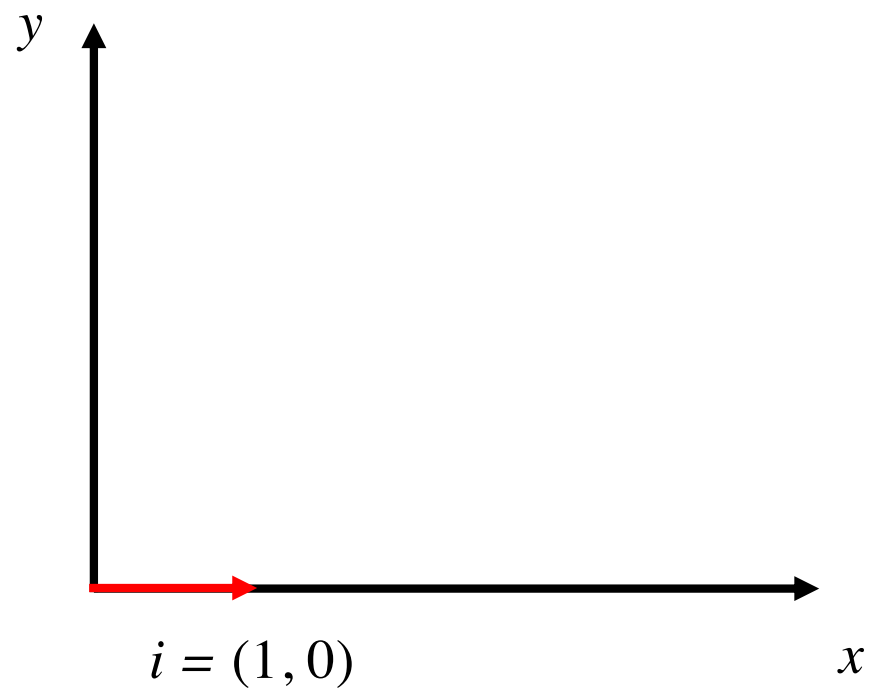


The 2D Plane

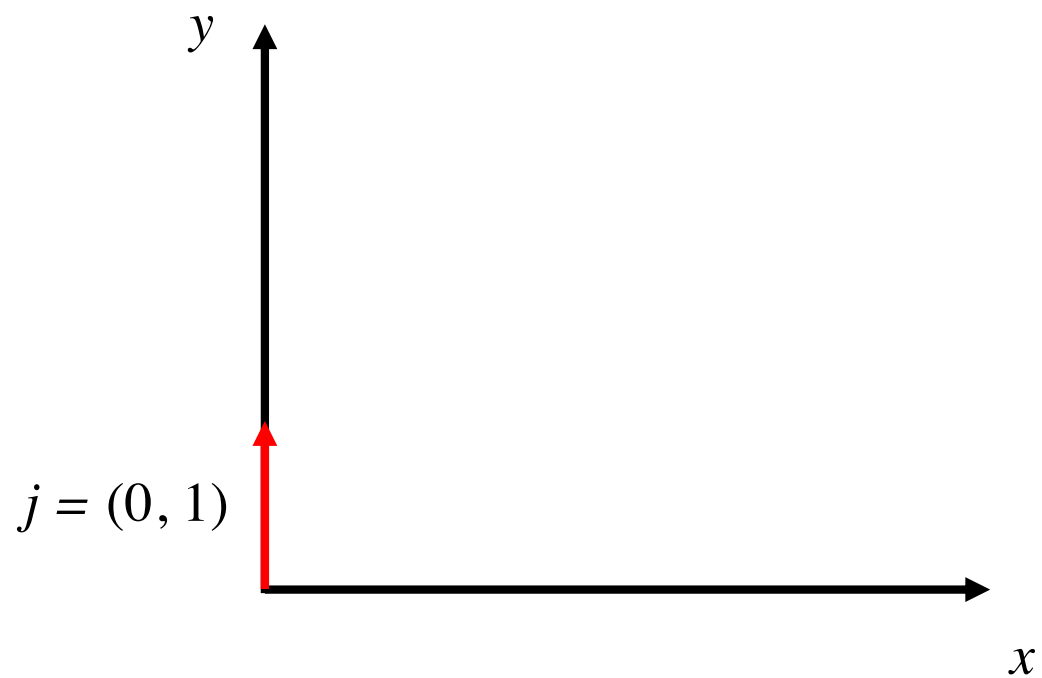

The 2D Plane

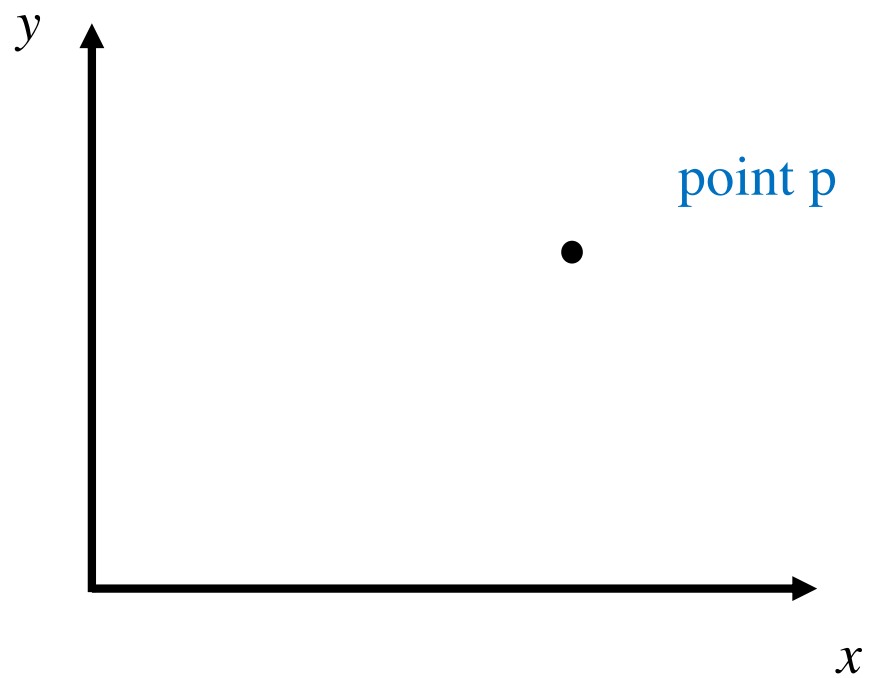

The 2D Plane

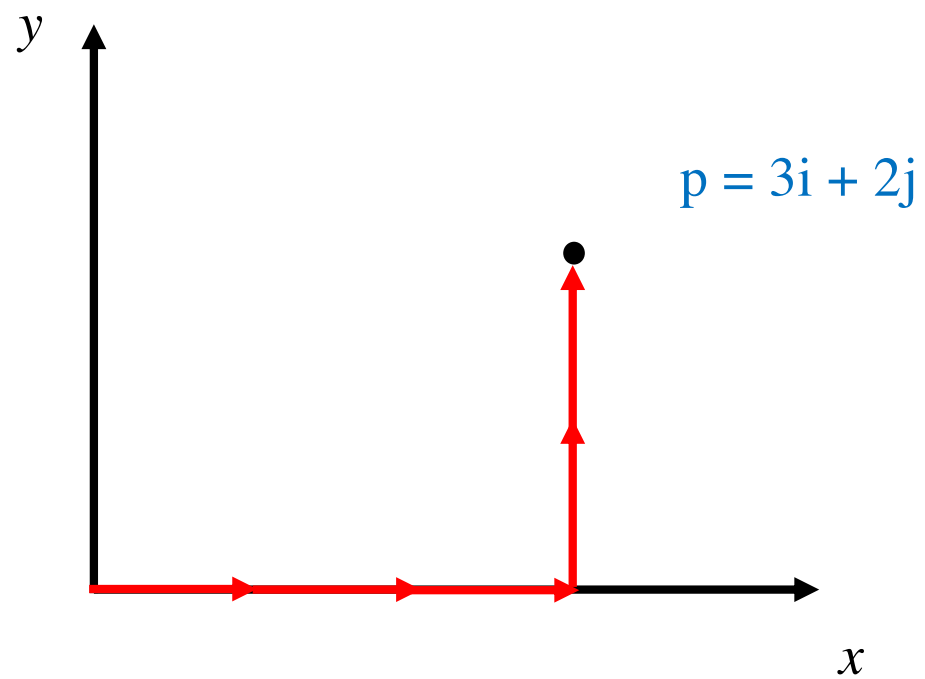

The unit vectors \mathbf{i} and \mathbf{j} form a basis


- Any point in the 2D plane can be represented as a linear combination of these two vectors.

$$\mathbf{i} = (1, 0)$$


$$\mathbf{j} = (0, 1)$$

Note that there is only one 1 in each.

3D Space

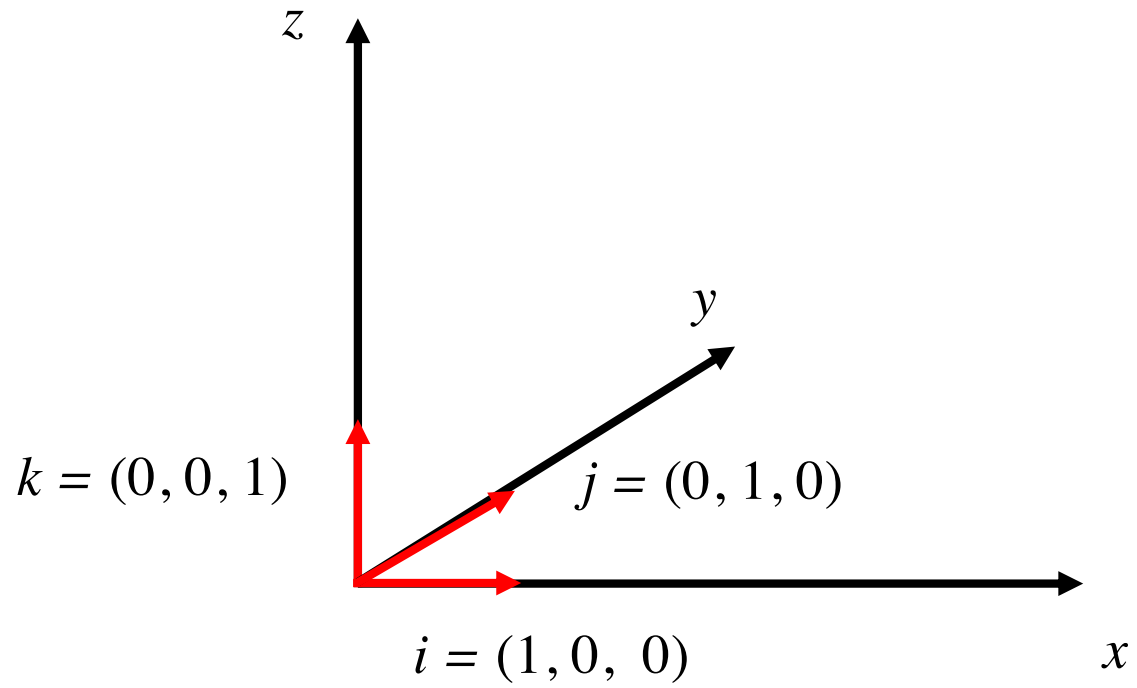

3D Space

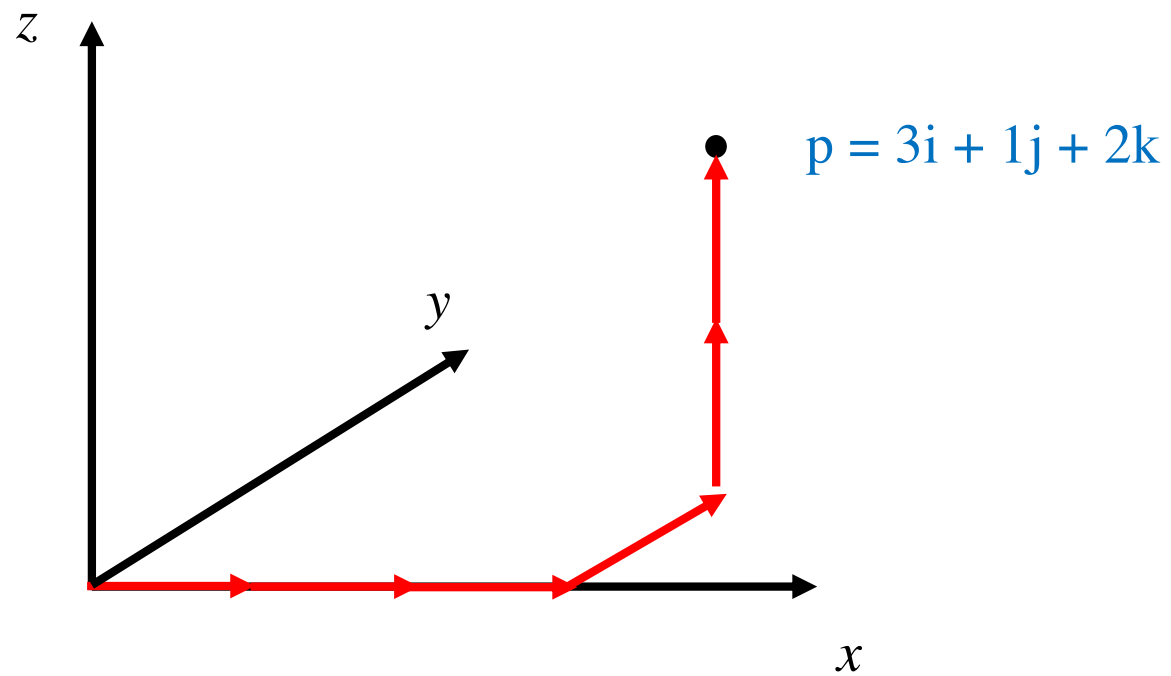

The 3D Basis

- In 3D we have \mathbf{i} , \mathbf{j} , and \mathbf{k}

$$\mathbf{i} = (1, 0, 0)$$

$$\mathbf{j} = (0, 1, 0)$$

$$\mathbf{k} = (0, 0, 1)$$

Note that there is only one 1 in each.

Any point in the 3D space can be represented as a linear combination of these three basis vectors.

The 4D Basis

- In 4D we have four vectors

$$\mathbf{x}^1 = (1, 0, 0, 0)$$

$$\mathbf{x}^2 = (0, 1, 0, 0)$$

$$\mathbf{x}^3 = (0, 0, 1, 0)$$

$$\mathbf{x}^4 = (0, 0, 0, 1)$$

Note that there is only one 1 in each.

Any point in this 4D space can be represented as a linear combination of these four basis vectors.

Basis Functions (for two variables)

The Four Basis Functions

x	y	f_{00}
0	0	1
0	1	0
1	0	0
1	1	0

$f_{00}(x, y)$

x	y	f_{01}
0	0	0
0	1	1
1	0	0
1	1	0

$f_{01}(x, y)$

x	y	f_{10}
0	0	0
0	1	0
1	0	1
1	1	0

$f_{10}(x, y)$

x	y	f_{11}
0	0	0
0	1	0
1	0	0
1	1	1

$f_{11}(x, y)$

The Four Basis Functions

x	y	f_{00}
0	0	1
0	1	0
1	0	0
1	1	0

$f_{00}(x, y)$

x	y	f_{01}
0	0	0
0	1	1
1	0	0
1	1	0

$f_{01}(x, y)$

x	y	f_{10}
0	0	0
0	1	0
1	0	1
1	1	0

$f_{10}(x, y)$

x	y	f_{11}
0	0	0
0	1	0
1	0	0
1	1	1

$f_{11}(x, y)$




The Four Basis Functions

x	y		$f_{00}(x, y)$	$f_{01}(x, y)$	$f_{10}(x, y)$	$f_{11}(x, y)$
0	0		1	0	0	0
0	1		0	1	0	0
1	0		0	0	1	0
1	1		0	0	0	1

The Four Basis Functions

x	y		$\bar{x}\bar{y}$	$\bar{x}y$	$x\bar{y}$	xy
0	0		1	0	0	0
0	1		0	1	0	0
1	0		0	0	1	0
1	1		0	0	0	1

Circuits for the four basis functions

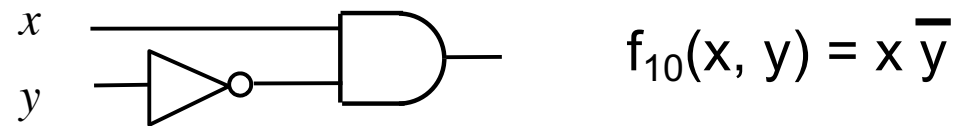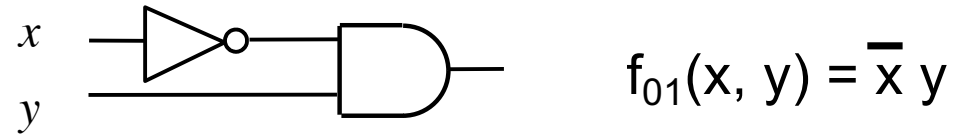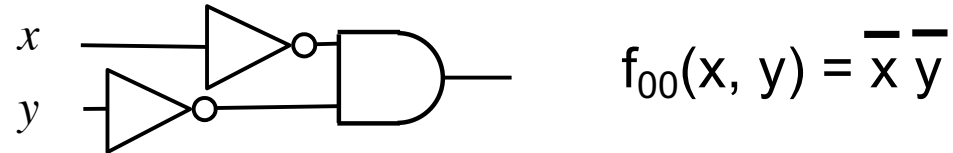

The Four Basis Functions

x	y	f ₀₀
0	0	1
0	1	0
1	0	0
1	1	0

x	y	f ₀₁
0	0	0
0	1	1
1	0	0
1	1	0

x	y	f ₁₀
0	0	0
0	1	0
1	0	1
1	1	0

x	y	f ₁₁
0	0	0
0	1	0
1	0	0
1	1	1

$$f_{00}(x, y) = \bar{x} \bar{y}$$

$$f_{01}(x, y) = \bar{x} y$$

$$f_{10}(x, y) = x \bar{y}$$

$$f_{11}(x, y) = x y$$

The Four Basis Functions

x	y	f ₀₀
0	0	1
0	1	0
1	0	0
1	1	0

x	y	f ₀₁
0	0	0
0	1	1
1	0	0
1	1	0

x	y	f ₁₀
0	0	0
0	1	0
1	0	1
1	1	0

x	y	f ₁₁
0	0	0
0	1	0
1	0	0
1	1	1

$$f_{00}(x, y) = \overline{x} \overline{y}$$

$$f_{01}(x, y) = \overline{x} y$$

$$f_{10}(x, y) = x \overline{y}$$

$$f_{11}(x, y) = x y$$

Negate the variable if the corresponding subscript of f is 0.

The Four Basis Functions

x	y	f ₀₀
0	0	1
0	1	0
1	0	0
1	1	0

x	y	f ₀₁
0	0	0
0	1	1
1	0	0
1	1	0

x	y	f ₁₀
0	0	0
0	1	0
1	0	1
1	1	0

x	y	f ₁₁
0	0	0
0	1	0
1	0	0
1	1	1

$$f_{00}(x, y) = \bar{x} \bar{y}$$

$$f_{\textcolor{red}{0}1}(x, y) = \bar{x} y$$

$$f_{10}(x, y) = x \bar{y}$$

$$f_{11}(x, y) = x y$$

Negate the variable if the corresponding subscript of f is 0.

The Four Basis Functions

x	y	f ₀₀
0	0	1
0	1	0
1	0	0
1	1	0

x	y	f ₀₁
0	0	0
0	1	1
1	0	0
1	1	0

x	y	f ₁₀
0	0	0
0	1	0
1	0	1
1	1	0

x	y	f ₁₁
0	0	0
0	1	0
1	0	0
1	1	1

$$f_{00}(x, y) = \bar{x} \bar{y}$$

$$f_{01}(x, y) = \bar{x} y$$

$$f_{10}(x, y) = x \bar{y}$$

$$f_{11}(x, y) = x y$$

Negate the variable if the corresponding subscript of f is 0.

minterms
(an alternative name for
the set of basis functions)

The Four Basis Functions

x	y	f ₀₀
0	0	1
0	1	0
1	0	0
1	1	0

$$f_{00}(x, y) = \bar{x} \bar{y}$$

x	y	f ₀₁
0	0	0
0	1	1
1	0	0
1	1	0

$$f_{01}(x, y) = \bar{x} y$$

x	y	f ₁₀
0	0	0
0	1	0
1	0	1
1	1	0

$$f_{10}(x, y) = x \bar{y}$$

x	y	f ₁₁
0	0	0
0	1	0
1	0	0
1	1	1

$$f_{11}(x, y) = x y$$

The Four Basis Functions (alternative names)

x	y	f ₀₀
0	0	1
0	1	0
1	0	0
1	1	0

$$f_{00}(x, y) = \bar{x} \bar{y}$$

m₀

x	y	f ₀₁
0	0	0
0	1	1
1	0	0
1	1	0

$$f_{01}(x, y) = \bar{x} y$$

m₁

x	y	f ₁₀
0	0	0
0	1	0
1	0	1
1	1	0

$$f_{10}(x, y) = x \bar{y}$$

m₂

x	y	f ₁₁
0	0	0
0	1	0
1	0	0
1	1	1

$$f_{11}(x, y) = x y$$

m₃

The Four Basis Functions (minterms)

x	y	m_0
0	0	1
0	1	0
1	0	0
1	1	0

$$f_{00}(x, y) = \bar{x} \bar{y}$$

m_0

x	y	m_1
0	0	0
0	1	1
1	0	0
1	1	0

$$f_{01}(x, y) = \bar{x} y$$

m_1

x	y	m_2
0	0	0
0	1	0
1	0	1
1	1	0

$$f_{10}(x, y) = x \bar{y}$$

m_2

x	y	m_3
0	0	0
0	1	0
1	0	0
1	1	1

$$f_{11}(x, y) = x y$$

m_3

The Four Basis Functions (minterms)

x	y		$\overline{x} \overline{y}$	$\overline{x} y$	$x \overline{y}$	$x y$
0	0		1	0	0	0
0	1		0	1	0	0
1	0		0	0	1	0
1	1		0	0	0	1

Expressions for the minterms

$$m_0 = \bar{x} \bar{y}$$

$$m_1 = \bar{x} y$$

$$m_2 = x \bar{y}$$

$$m_3 = x y$$

Expressions for the minterms

$$0 \quad 0 \qquad m_0 = \bar{x} \bar{y}$$

$$0 \quad 1 \qquad m_1 = \bar{x} y$$

$$1 \quad 0 \qquad m_2 = x \bar{y}$$

$$1 \quad 1 \qquad m_3 = x y$$

The bars coincide
with the 0's
in the binary expansion
of the minterm sub-index

Expressions for the minterms

$$\begin{matrix} 0 & 0 \\ 0 & 1 \\ 1 & 0 \\ 1 & 1 \end{matrix} \quad m_0 = \bar{x} \bar{y}$$

$$m_1 = \bar{x} y$$

$$m_2 = x \bar{y}$$

$$m_3 = x y$$

The bars coincide
with the 0's
in the binary expansion
of the minterm sub-index

Function Synthesis Example (with two variables)

Synthesize the Following Function

x_1	x_2	$f(x_1, x_2)$
0	0	1
0	1	1
1	0	0
1	1	1

1) Split the function into a sum of 4 functions

x_1	x_2	$f(x_1, x_2)$		$f_{00}(x_1, x_2)$	$f_{01}(x_1, x_2)$	$f_{10}(x_1, x_2)$	$f_{11}(x_1, x_2)$
0	0	1		1	0	0	0
0	1	1		0	1	0	0
1	0	0		0	0	1	0
1	1	1		0	0	0	1

1) Split the function into a sum of 4 functions

x_1	x_2	$f(x_1, x_2)$		$f_{00}(x_1, x_2)$	$f_{01}(x_1, x_2)$	$f_{10}(x_1, x_2)$	$f_{11}(x_1, x_2)$
0	0	1		1	0	0	0
0	1	1		0	1	0	0
1	0	0		0	0	1	0
1	1	1		0	0	0	1

$$f(x_1, x_2) = 1 \cdot f_{00} + 1 \cdot f_{01} + 0 \cdot f_{10} + 1 \cdot f_{11}$$

2) Write the expressions for all four

x_1	x_2	$f(x_1, x_2)$		$f_{00}(x_1, x_2)$	$f_{01}(x_1, x_2)$	$f_{10}(x_1, x_2)$	$f_{11}(x_1, x_2)$
0	0	1		1	0	0	0
0	1	1		0	1	0	0
1	0	0		0	0	1	0
1	1	1		0	0	0	1

$$f(x_1, x_2) = \underbrace{1 \cdot f_{00}} + \underbrace{1 \cdot f_{01}} + \underbrace{0 \cdot f_{10}} + \underbrace{1 \cdot f_{11}}$$

2) Write the expressions for all four

x_1	x_2	$f(x_1, x_2)$		$f_{00}(x_1, x_2)$	$f_{01}(x_1, x_2)$	$f_{10}(x_1, x_2)$	$f_{11}(x_1, x_2)$
0	0	1		1	0	0	0
0	1	1		0	1	0	0
1	0	0		0	0	1	0
1	1	1		0	0	0	1

$$f(x_1, x_2) = \underbrace{1 \cdot f_{00}}_{\bar{x}_1 \bar{x}_2} + \underbrace{1 \cdot f_{01}}_{\bar{x}_1 x_2} + \underbrace{0 \cdot f_{10}}_0 + \underbrace{1 \cdot f_{11}}_{x_1 x_2}$$

3) Then just add them together

x_1	x_2	$f(x_1, x_2)$		$f_{00}(x_1, x_2)$	$f_{01}(x_1, x_2)$	$f_{10}(x_1, x_2)$	$f_{11}(x_1, x_2)$
0	0	1		1	0	0	0
0	1	1		0	1	0	0
1	0	0		0	0	1	0
1	1	1		0	0	0	1

$$f(x_1, x_2) = \underbrace{1 \cdot f_{00}} + \underbrace{1 \cdot f_{01}} + \underbrace{0 \cdot f_{10}} + \underbrace{1 \cdot f_{11}}$$

$$f(x_1, x_2) = \bar{x}_1\bar{x}_2 + \bar{x}_1x_2 + 0 + x_1x_2$$

3) Then just add them together

x_1	x_2	$f(x_1, x_2)$		$f_{00}(x_1, x_2)$	$f_{01}(x_1, x_2)$	$f_{10}(x_1, x_2)$	$f_{11}(x_1, x_2)$
0	0	1		1	0	0	0
0	1	1		0	1	0	0
1	0	0		0	0	1	0
1	1	1		0	0	0	1

$$f(x_1, x_2) = \bar{x}_1\bar{x}_2 + \bar{x}_1x_2 + 0 + x_1x_2$$

A function to be synthesized

x_1	x_2	$f(x_1, x_2)$
0	0	1
0	1	1
1	0	0
1	1	1

[Figure 2.19 from the textbook]

**Let's look at it row by row.
How can we express the last row?**

x_1	x_2	$f(x_1, x_2)$
0	0	1
0	1	1
1	0	0
1	1	1

**Let's look at it row by row.
How can we express the last row?**


x_1	x_2	$f(x_1, x_2)$
0	0	1
0	1	1
1	0	0
1	1	1

x_1x_2

**Let's look at it row by row.
How can we express the last row?**

x_1	x_2	$f(x_1, x_2)$
0	0	1
0	1	1
1	0	0
1	1	1

1

x_1
 x_2 


What about this row?

x_1	x_2	$f(x_1, x_2)$
0	0	1
0	1	1
1	0	0
1	1	1



What about this row?



x_1	x_2	$f(x_1, x_2)$
0	0	1
0	1	1
1	0	0
1	1	1

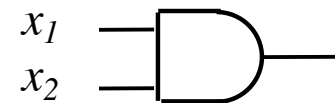

$$\bar{x}_1 x_2$$



What about this row?

x_1	x_2	$f(x_1, x_2)$
0	0	1
0	1	1
1	0	0
1	1	1

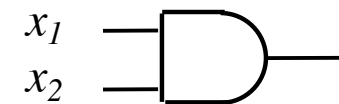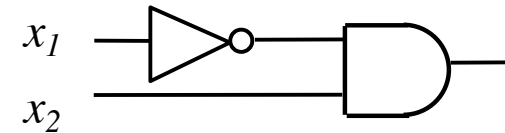

What about the first row?


x_1	x_2	$f(x_1, x_2)$
0	0	1
0	1	1
1	0	0
1	1	1

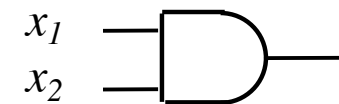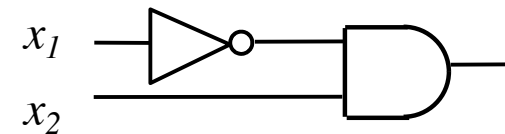


What about the first row?

x_1	x_2	$f(x_1, x_2)$
0	0	1
0	1	1
1	0	0
1	1	1

$\bar{x}_1\bar{x}_2$

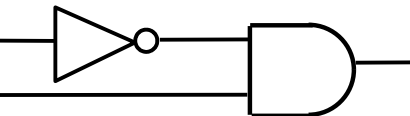x_1 

x_2

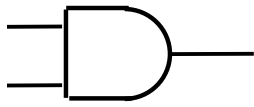x_1 

x_2

What about the first row?

x_1	x_2	$f(x_1, x_2)$
0	0	1
0	1	1
1	0	0
1	1	1

Logic circuit diagrams for the first three rows of the truth table:

- For the first row ($x_1=0, x_2=0$), the output is 1. The circuit uses two inverters (NOT gates) on the inputs x_1 and x_2 , followed by an AND gate.
- For the second row ($x_1=0, x_2=1$), the output is 1. The circuit uses one inverter on the input x_1 , followed by an AND gate with input x_2 .
- For the third row ($x_1=1, x_2=0$), the output is 0. The circuit uses an AND gate with inputs x_1 and x_2 .

Finally, what about the zero?


x_1	x_2	$f(x_1, x_2)$
0	0	1
0	1	1
1	0	0
1	1	1

Diagram illustrating the logic implementation of the function $f(x_1, x_2)$ for the input combination $x_1=1, x_2=0$ (highlighted in green in the table):


The function is implemented using three logic gates:

- Top circuit: A NOT gate on x_1 and a NOT gate on x_2 are connected to an AND gate. This circuit outputs 1 for $(1, 0)$.
- Middle circuit: A NOT gate on x_1 is connected to an AND gate along with x_2 . This circuit outputs 1 for $(0, 1)$.
- Bottom circuit: An AND gate with inputs x_1 and x_2 . This circuit outputs 1 for $(1, 1)$.


Putting it all together

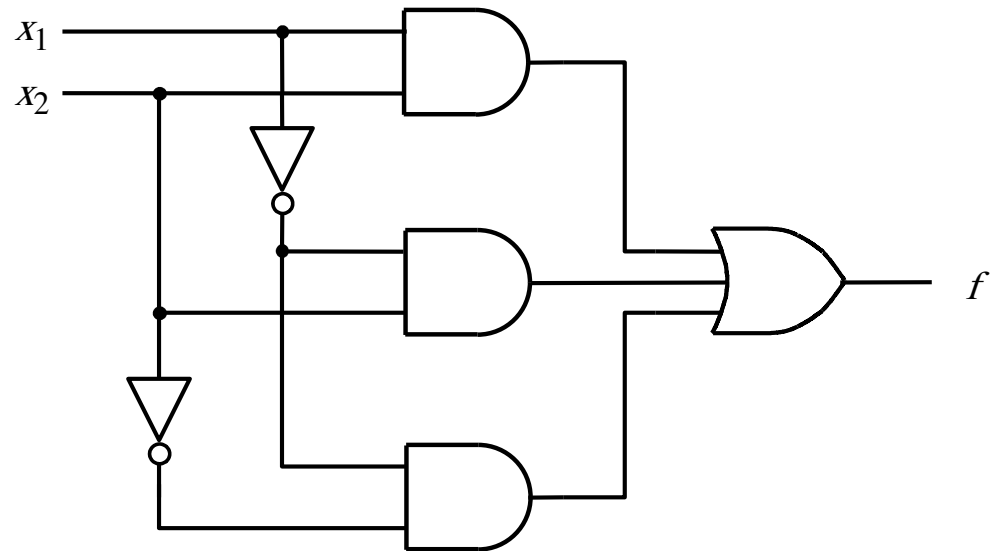

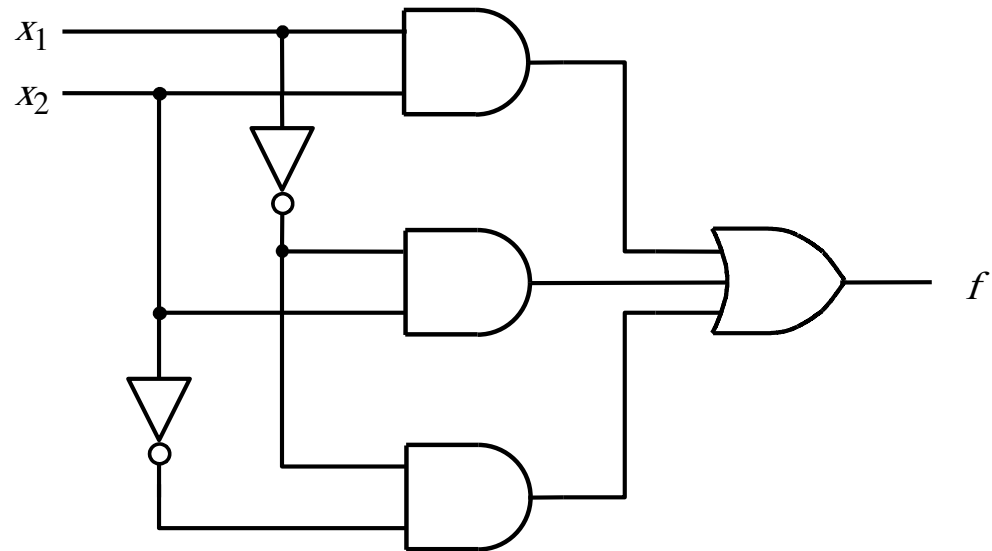
**Let's verify that this circuit implements
correctly the target truth table**



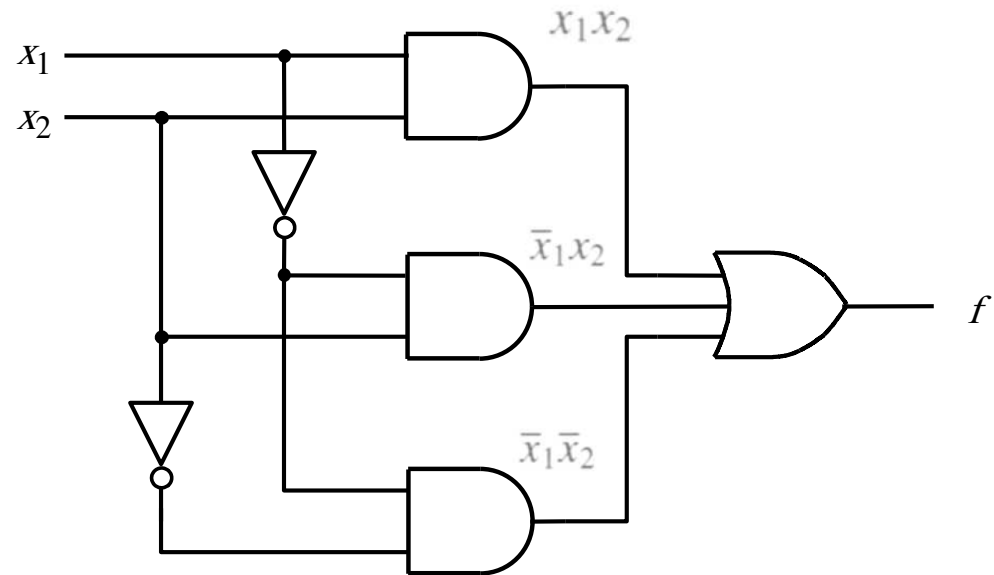
Let's verify that this circuit implements correctly the target truth table



Putting it all together

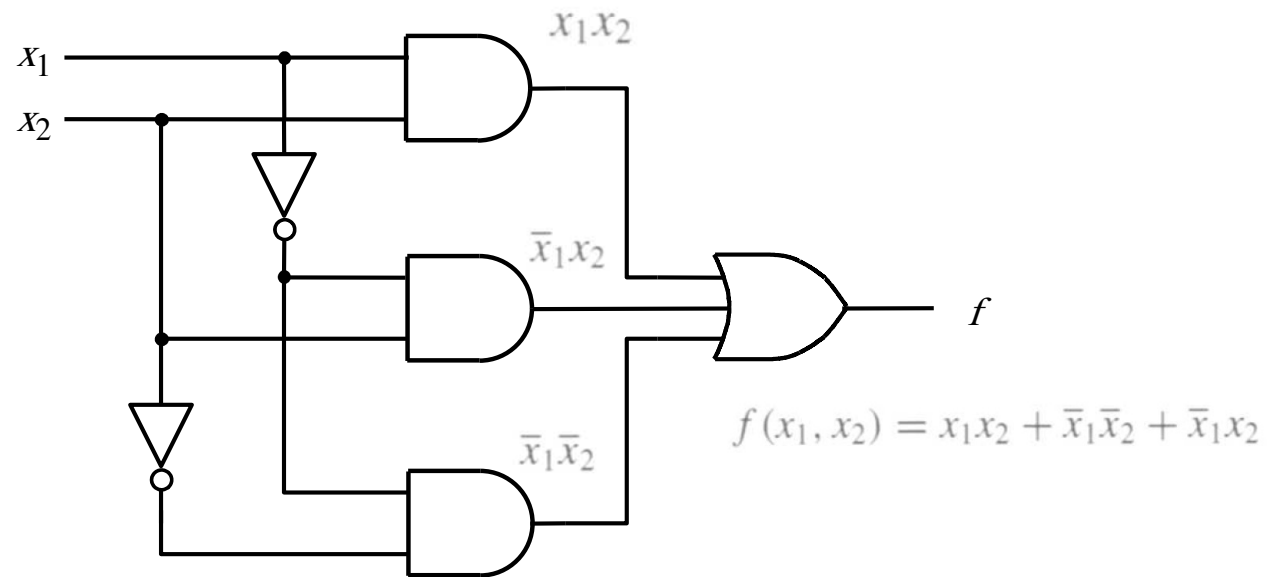

Canonical Sum-Of-Products (SOP)

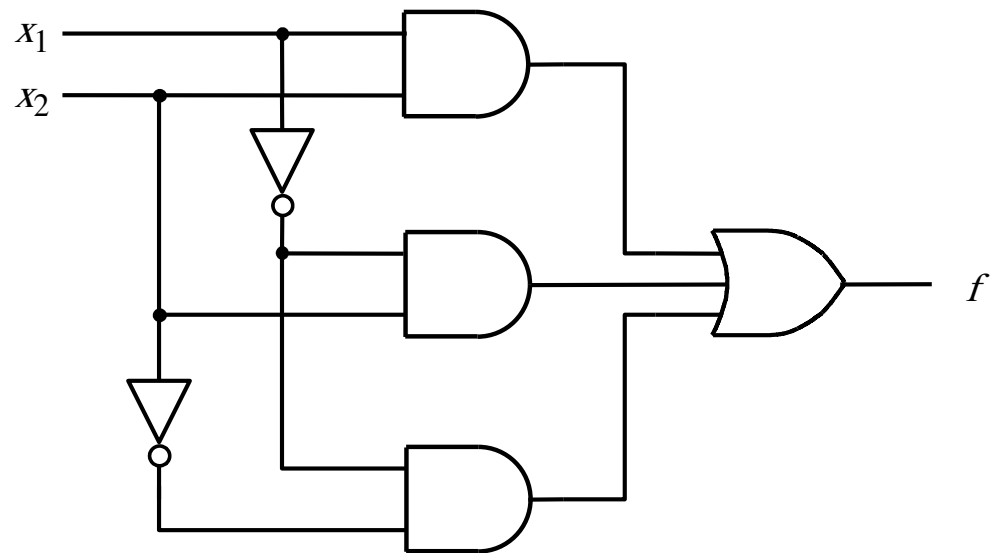

$$f(x_1, x_2) = x_1x_2 + \bar{x}_1\bar{x}_2 + \bar{x}_1x_2$$

[Figure 2.20a from the textbook]

Summary of This Procedure

- Get the truth table of the function
- Form a product term (AND gate) for each row of the table for which the function is 1
- Each product term contains all input variables
- In each row, if $x_i=1$ enter it as x_i , otherwise use $\overline{x_i}$
- Sum all of these products (OR gate) to get the function

Simplification Steps

$$f(x_1, x_2) = x_1x_2 + \bar{x}_1\bar{x}_2 + \bar{x}_1x_2$$

Simplification Steps

$$f(x_1, x_2) = x_1x_2 + \bar{x}_1\bar{x}_2 + \bar{x}_1x_2$$

replicate
this term


$$f(x_1, x_2) = x_1x_2 + \bar{x}_1\bar{x}_2 + \bar{x}_1x_2 + \bar{x}_1x_2$$

Simplification Steps

$$f(x_1, x_2) = x_1x_2 + \bar{x}_1\bar{x}_2 + \bar{x}_1x_2$$

group these terms

$$f(x_1, x_2) = \boxed{x_1x_2} + \boxed{\bar{x}_1\bar{x}_2} + \boxed{\bar{x}_1x_2} + \boxed{\bar{x}_1x_2}$$

$$f(x_1, x_2) = (x_1 + \bar{x}_1)x_2 + \bar{x}_1(\bar{x}_2 + x_2)$$


Simplification Steps

$$f(x_1, x_2) = x_1x_2 + \bar{x}_1\bar{x}_2 + \bar{x}_1x_2$$

$$f(x_1, x_2) = x_1x_2 + \bar{x}_1\bar{x}_2 + \bar{x}_1x_2 + \bar{x}_1x_2$$

These two terms are trivially equal to 1

$$f(x_1, x_2) = (x_1 + \bar{x}_1)x_2 + \bar{x}_1(\bar{x}_2 + x_2)$$

$$f(x_1, x_2) = 1 \cdot x_2 + \bar{x}_1 \cdot 1$$

Simplification Steps

$$f(x_1, x_2) = x_1x_2 + \bar{x}_1\bar{x}_2 + \bar{x}_1x_2$$

$$f(x_1, x_2) = x_1x_2 + \bar{x}_1\bar{x}_2 + \bar{x}_1x_2 + \bar{x}_1x_2$$

$$f(x_1, x_2) = (x_1 + \bar{x}_1)x_2 + \bar{x}_1(\bar{x}_2 + x_2)$$


$$f(x_1, x_2) = \boxed{1} \cdot x_2 + \bar{x}_1 \cdot \boxed{1}$$

Drop the 1's

$$f(x_1, x_2) = x_2 + \bar{x}_1$$


Minimal-cost realization

$$f(x_1, x_2) = x_2 + \bar{x}_1$$

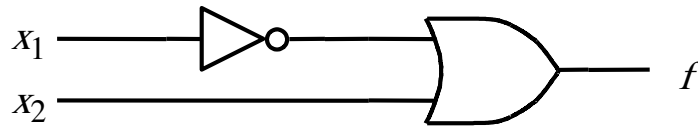


[Figure 2.20b from the textbook]

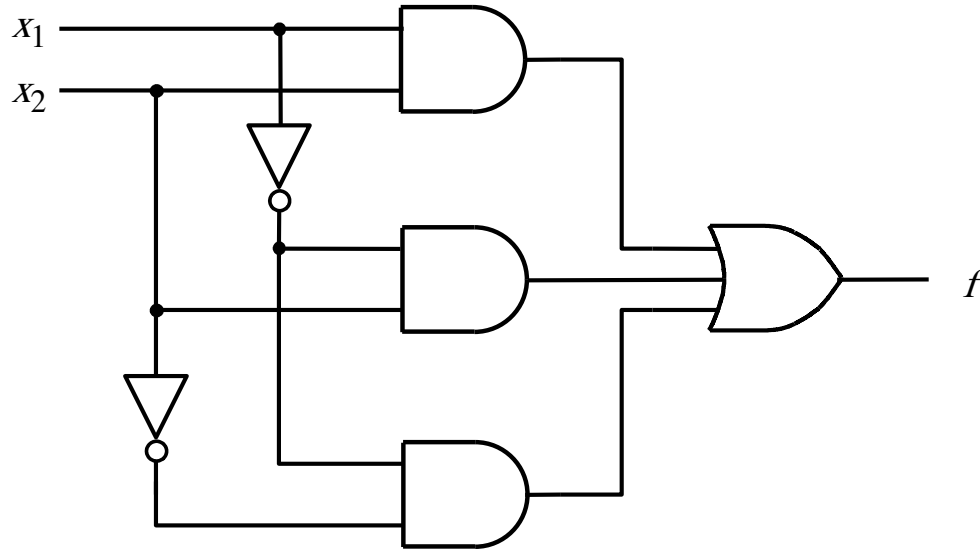Two implementations for the same function



(a) Canonical sum-of-products

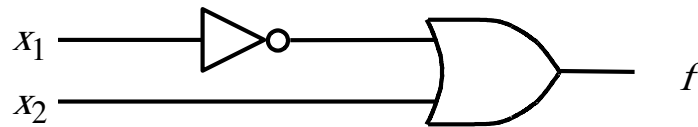

(b) Minimal-cost realization

[Figure 2.20 from the textbook]

Basis Functions / minterms (for three variables)

The Eight Basis Functions

x	y	z	f_{000}	f_{001}	f_{010}	f_{011}	f_{100}	f_{101}	f_{110}	f_{111}
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

The Eight Basis Functions

x	y	z	f_{000}	f_{001}	f_{010}	f_{011}	f_{100}	f_{101}	f_{110}	f_{111}
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

The Eight minterms

x	y	z	m ₀	m ₁	m ₂	m ₃	m ₄	m ₅	m ₆	m ₇
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

Expressions for the minterms

$$m_0 = \bar{x} \bar{y} \bar{z}$$

$$m_1 = \bar{x} \bar{y} z$$

$$m_2 = \bar{x} y \bar{z}$$

$$m_3 = \bar{x} y z$$

$$m_4 = x \bar{y} \bar{z}$$

$$m_5 = x \bar{y} z$$

$$m_6 = x y \bar{z}$$

$$m_7 = x y z$$

Expressions for the minterms

$$0 \ 0 \ 0 \quad m_0 = \bar{x} \ \bar{y} \ \bar{z}$$

$$0 \ 0 \ 1 \quad m_1 = \bar{x} \ \bar{y} \ z$$

$$0 \ 1 \ 0 \quad m_2 = \bar{x} \ y \ \bar{z}$$

$$0 \ 1 \ 1 \quad m_3 = \bar{x} \ y \ z$$

$$1 \ 0 \ 0 \quad m_4 = x \ \bar{y} \ \bar{z}$$

$$1 \ 0 \ 1 \quad m_5 = x \ \bar{y} \ z$$


$$1 \ 1 \ 0 \quad m_6 = x \ y \ \bar{z}$$

$$1 \ 1 \ 1 \quad m_7 = x \ y \ z$$

The bars coincide
with the 0's
in the binary expansion
of the minterm sub-index

Function Synthesis Example (with three variables)

Let's look at another problem

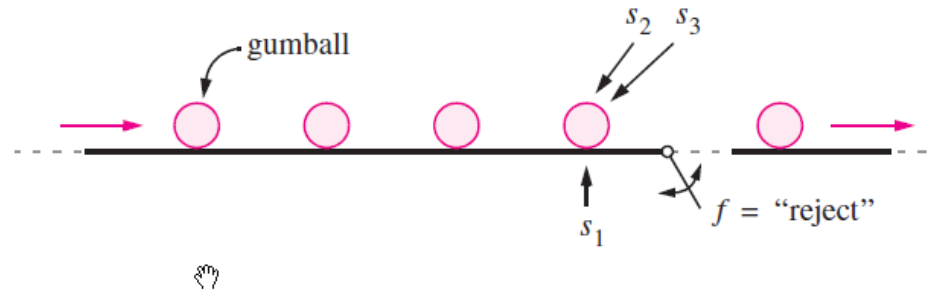

(a) Conveyor and sensors

s_1	s_2	s_3	f
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

(b) Truth table

[Figure 2.21 from the textbook]

Let's look at another problem

s_1	s_2	s_3	f
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

[Figure 2.21b from the textbook]

Let's look at another problem

s_1	s_2	s_3	f
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Let's look at another problem

s_1	s_2	s_3	f	
0	0	0	0	
0	0	1	1	$\bar{s}_1 \bar{s}_2 s_3$
0	1	0	0	
0	1	1	1	$\bar{s}_1 s_2 s_3$
1	0	0	0	
1	0	1	1	$s_1 \bar{s}_2 s_3$
1	1	0	1	$s_1 s_2 \bar{s}_3$
1	1	1	1	$s_1 s_2 s_3$

Let's look at another problem

s_1	s_2	s_3	f	
0	0	0	0	
<u>0</u>	<u>0</u>	1	1	$\bar{s}_1 \bar{s}_2 s_3$
0	1	0	0	
0	1	1	1	$\bar{s}_1 s_2 s_3$
1	0	0	0	
1	0	1	1	$s_1 \bar{s}_2 s_3$
1	1	0	1	$s_1 s_2 \bar{s}_3$
1	1	1	1	$s_1 s_2 s_3$

Let's look at another problem

s_1	s_2	s_3	f	
0	0	0	0	
<u>0</u>	<u>0</u>	1	1	$\bar{s}_1 \bar{s}_2 s_3$
0	1	0	0	
<u>0</u>	1	1	1	$\bar{s}_1 s_2 s_3$
1	0	0	0	
1	0	1	1	$s_1 \bar{s}_2 s_3$
1	1	0	1	$s_1 s_2 \bar{s}_3$
1	1	1	1	$s_1 s_2 s_3$

Let's look at another problem

s_1	s_2	s_3	f	
0	0	0	0	
<u>0</u>	<u>0</u>	1	1	$\bar{s}_1 \bar{s}_2 s_3$
0	1	0	0	
<u>0</u>	1	1	1	$\bar{s}_1 s_2 s_3$
1	0	0	0	
1	<u>0</u>	1	1	$s_1 \bar{s}_2 s_3$
1	1	0	1	$s_1 s_2 \bar{s}_3$
1	1	1	1	$s_1 s_2 s_3$

Let's look at another problem

s_1	s_2	s_3	f	
0	0	0	0	
<u>0</u>	<u>0</u>	1	1	$\bar{s}_1 \bar{s}_2 s_3$
0	1	0	0	
<u>0</u>	1	1	1	$\bar{s}_1 s_2 s_3$
1	0	0	0	
1	<u>0</u>	1	1	$s_1 \bar{s}_2 s_3$
1	1	<u>0</u>	1	$s_1 s_2 \bar{s}_3$
1	1	1	1	$s_1 s_2 s_3$

Let's look at another problem

s_1	s_2	s_3	f	
0	0	0	0	
0	0	1	1	$\bar{s}_1\bar{s}_2s_3$
0	1	0	0	
0	1	1	1	$\bar{s}_1s_2s_3$
1	0	0	0	
1	0	1	1	$s_1\bar{s}_2s_3$
1	1	0	1	$s_1s_2\bar{s}_3$
1	1	1	1	$s_1s_2s_3$


$$f = \bar{s}_1\bar{s}_2s_3 + \bar{s}_1s_2s_3 + s_1\bar{s}_2s_3 + s_1s_2\bar{s}_3 + s_1s_2s_3$$

Let's look at another problem (minimization)

$$\begin{aligned}f &= \bar{s}_1\bar{s}_2s_3 + \bar{s}_1s_2s_3 + s_1\bar{s}_2s_3 + s_1s_2s_3 + s_1s_2\bar{s}_3 + s_1s_2s_3 \\&= \bar{s}_1s_3(\bar{s}_2 + s_2) + s_1s_3(\bar{s}_2 + s_2) + s_1s_2(\bar{s}_3 + s_3) \\&= \bar{s}_1s_3 + s_1s_3 + s_1s_2 \\&= s_3 + s_1s_2\end{aligned}$$

Let's look at another problem (minimization)
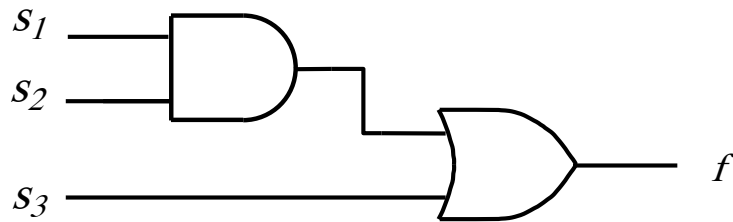
$$\begin{aligned} f &= \bar{s}_1\bar{s}_2s_3 + \bar{s}_1s_2s_3 + s_1\bar{s}_2s_3 + s_1s_2s_3 + s_1s_2\bar{s}_3 + s_1s_2s_3 \\ &= \bar{s}_1s_3(\bar{s}_2 + s_2) + s_1s_3(\bar{s}_2 + s_2) + s_1s_2(\bar{s}_3 + s_3) \\ &= \bar{s}_1s_3 + s_1s_3 + s_1s_2 \\ &= s_3 + s_1s_2 \end{aligned}$$



Maxterms
(an alternative set of basis functions)

The Four Maxterms

x	y	M_0
0	0	0
0	1	1
1	0	1
1	1	1

$M_0(x, y)$

x	y	M_1
0	0	1
0	1	0
1	0	1
1	1	1

$M_1(x, y)$

x	y	M_2
0	0	1
0	1	1
1	0	0
1	1	1

$M_2(x, y)$

x	y	M_3
0	0	1
0	1	1
1	0	1
1	1	0

$M_3(x, y)$

The Four Maxterms

x	y	M_0
0	0	0
0	1	1
1	0	1
1	1	1

$M_0(x, y)$

x	y	M_1
0	0	1
0	1	0
1	0	1
1	1	1

$M_1(x, y)$

x	y	M_2
0	0	1
0	1	1
1	0	0
1	1	1

$M_2(x, y)$

x	y	M_3
0	0	1
0	1	1
1	0	1
1	1	0

$M_3(x, y)$

The Four Maxterms

x	y		$M_0(x, y)$	$M_1(x, y)$	$M_2(x, y)$	$M_3(x, y)$
0	0		0	1	1	1
0	1		1	0	1	1
1	0		1	1	0	1
1	1		1	1	1	0

The Four Maxterms

x	y		$x + y$	$x + \bar{y}$	$\bar{x} + y$	$\bar{x} + \bar{y}$
0	0		0	1	1	1
0	1		1	0	1	1
1	0		1	1	0	1
1	1		1	1	1	0

Expressions for the Maxterms

$$M_0 = x + y$$

$$M_1 = x + \bar{y}$$

$$M_2 = \bar{x} + y$$

$$M_3 = \bar{x} + \bar{y}$$

Expressions for the Maxterms

$$M_0 = x + y$$

$$M_1 = x + \bar{y}$$

$$M_2 = \bar{x} + y$$

$$M_3 = \bar{x} + \bar{y}$$

Note that these are now
sums, not products.

Expressions for the Maxterms

$$0 \quad 0 \quad M_0 = x + y$$

$$0 \quad 1 \quad M_1 = x + \bar{y}$$

$$1 \quad 0 \quad M_2 = \bar{x} + y$$

$$1 \quad 1 \quad M_3 = \bar{x} + \bar{y}$$

The bars coincide
with the 1's
in the binary expansion
of the maxterm sub-index

Expressions for the Maxterms

$$0 \ 0 \quad M_0 = x + y$$


$$0 \ 1 \quad M_1 = x + \overline{y}$$

$$1 \ 0 \quad M_2 = \overline{x} + y$$


$$1 \ 1 \quad M_3 = \overline{x} + \overline{y}$$

The bars coincide
with the 1's
in the binary expansion
of the maxterm sub-index


Circuits for the four Maxterms

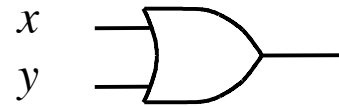


$$M_0(x, y) = x + y$$

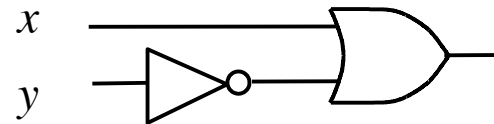

$$M_1(x, y) = x + \bar{y}$$

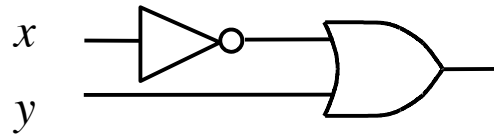

$$M_2(x, y) = \bar{x} + y$$

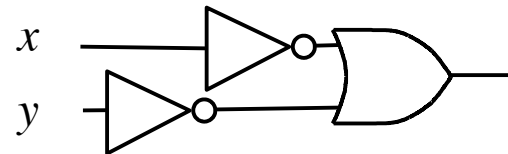

$$M_3(x, y) = \bar{x} + \bar{y}$$

Minterms and Maxterms

Row number	x_1	x_2	Minterm	Maxterm
0	0	0	$m_0 = \bar{x}_1 \bar{x}_2$	$M_0 = x_1 + x_2$
1	0	1	$m_1 = \bar{x}_1 x_2$	$M_1 = x_1 + \bar{x}_2$
2	1	0	$m_2 = x_1 \bar{x}_2$	$M_2 = \bar{x}_1 + x_2$
3	1	1	$m_3 = x_1 x_2$	$M_3 = \bar{x}_1 + \bar{x}_2$

Minterms and Maxterms

Row number	x_1	x_2	Minterm	Maxterm
0	0	0	$m_0 = \bar{x}_1 \bar{x}_2$	$M_0 = x_1 + x_2$
1	0	1	$m_1 = \bar{x}_1 x_2$	$M_1 = x_1 + \bar{x}_2$
2	1	0	$m_2 = x_1 \bar{x}_2$	$M_2 = \bar{x}_1 + x_2$
3	1	1	$m_3 = x_1 x_2$	$M_3 = \bar{x}_1 + \bar{x}_2$

Use these for
Sum-of-Products
Minimization
(1's of the function)

Use these for
Product-of-Sums
Minimization
(0's of the function)

Minterms and Maxterms

Row number	x_1	x_2	Minterm	Maxterm
0	0	0	$m_0 = \bar{x}_1 \bar{x}_2$	$M_0 = x_1 + x_2$
1	0	1	$m_1 = \bar{x}_1 x_2$	$M_1 = x_1 + \bar{x}_2$
2	1	0	$m_2 = x_1 \bar{x}_2$	$M_2 = \bar{x}_1 + x_2$
3	1	1	$m_3 = x_1 x_2$	$M_3 = \bar{x}_1 + \bar{x}_2$

Use these for
Sum-of-Products
 Minimization
 (1's of the function)

Use these for
Product-of-Sums
 Minimization
 (0's of the function)

Sum-of-Products Form

(uses the **ones** of the function)

Sum-of-Products Form

(for the AND logic function)

Row number	x_1	x_2	Minterm	$f(x_1, x_2)$
0	0	0	$m_0 = \overline{x_1}\overline{x_2}$	0
1	0	1	$m_1 = \overline{x_1}x_2$	0
2	1	0	$m_2 = x_1\overline{x_2}$	0
3	1	1	$m_3 = x_1x_2$	1

Sum-of-Products Form

(for the AND logic function)

Row number	x_1	x_2	Minterm	$f(x_1, x_2)$
0	0	0	$m_0 = \overline{x_1}\overline{x_2}$	0
1	0	1	$m_1 = \overline{x_1}x_2$	0
2	1	0	$m_2 = x_1\overline{x_2}$	0
3	1	1	$m_3 = x_1x_2$	1

Sum-of-Products Form

(for the AND logic function)

Row number	x_1	x_2	Minterm	$f(x_1, x_2)$
0	0	0	$m_0 = \bar{x}_1 \bar{x}_2$	0
1	0	1	$m_1 = \bar{x}_1 x_2$	0
2	1	0	$m_2 = x_1 \bar{x}_2$	0
3	1	1	$m_3 = x_1 x_2$	1

$$f(x_1, x_2) = m_3 = x_1 x_2$$

(In this case there is just one product and there is no need for a sum)

Another Example

Sum-of-Products Form

Row number	x_1	x_2	Minterm	$f(x_1, x_2)$
0	0	0	$m_0 = \overline{x_1}\overline{x_2}$	1
1	0	1	$m_1 = \overline{x_1}x_2$	1
2	1	0	$m_2 = x_1\overline{x_2}$	0
3	1	1	$m_3 = x_1x_2$	1

Sum-of-Products Form

Row number	x_1	x_2	Minterm	$f(x_1, x_2)$
0	0	0	$m_0 = \overline{x_1}\overline{x_2}$	1
1	0	1	$m_1 = \overline{x_1}x_2$	1
2	1	0	$m_2 = x_1\overline{x_2}$	0
3	1	1	$m_3 = x_1x_2$	1

Sum-of-Products Form

Row number	x_1	x_2	Minterm	$f(x_1, x_2)$
0	0	0	$m_0 = \bar{x}_1\bar{x}_2$	1
1	0	1	$m_1 = \bar{x}_1x_2$	1
2	1	0	$m_2 = x_1\bar{x}_2$	0
3	1	1	$m_3 = x_1x_2$	1

$$\begin{aligned}
 f &= m_0 \cdot 1 + m_1 \cdot 1 + m_2 \cdot 0 + m_3 \cdot 1 \\
 &= m_0 + m_1 + m_3 \\
 &= \bar{x}_1\bar{x}_2 + \bar{x}_1x_2 + x_1x_2
 \end{aligned}$$

Product-of-Sums Form

(uses the **zeros** of the function)

Product-of-Sums Form

(for the OR logic function)

Row number	x_1	x_2	Maxterm	$f(x_1, x_2)$
0	0	0	$M_0 = x_1 + x_2$	0
1	0	1	$M_1 = x_1 + \bar{x}_2$	1
2	1	0	$M_2 = \bar{x}_1 + x_2$	1
3	1	1	$M_3 = \bar{x}_1 + \bar{x}_2$	1

Product-of-Sums Form

(for the OR logic function)

Row number	x_1	x_2	Maxterm	$f(x_1, x_2)$
0	0	0	$M_0 = x_1 + x_2$	0
1	0	1	$M_1 = x_1 + \bar{x}_2$	1
2	1	0	$M_2 = \bar{x}_1 + x_2$	1
3	1	1	$M_3 = \bar{x}_1 + \bar{x}_2$	1

Product-of-Sums Form

(for the OR logic function)

Row number	x_1	x_2	Maxterm	$f(x_1, x_2)$
0	0	0	$M_0 = x_1 + x_2$	0
1	0	1	$M_1 = x_1 + \bar{x}_2$	1
2	1	0	$M_2 = \bar{x}_1 + x_2$	1
3	1	1	$M_3 = \bar{x}_1 + \bar{x}_2$	1

$$f(x_1, x_2) = M_0 = x_1 + x_2$$

(In this case there is just one sum and there is no need for a product)

Another Example

Product-of-Sums Form

(for this logic function)

Row number	x_1	x_2	Maxterm	$f(x_1, x_2)$
0	0	0	$M_0 = x_1 + x_2$	0
1	0	1	$M_1 = x_1 + \bar{x}_2$	1
2	1	0	$M_2 = \bar{x}_1 + x_2$	0
3	1	1	$M_3 = \bar{x}_1 + \bar{x}_2$	1

Product-of-Sums Form

(for this logic function)

Row number	x_1	x_2	Maxterm	$f(x_1, x_2)$
0	0	0	$M_0 = x_1 + x_2$	0
1	0	1	$M_1 = x_1 + \bar{x}_2$	1
2	1	0	$M_2 = \bar{x}_1 + x_2$	0
3	1	1	$M_3 = \bar{x}_1 + \bar{x}_2$	1

Product-of-Sums Form

(for this logic function)

Row number	x_1	x_2	Maxterm	$f(x_1, x_2)$
0	0	0	$M_0 = x_1 + x_2$	0
1	0	1	$M_1 = x_1 + \bar{x}_2$	1
2	1	0	$M_2 = \bar{x}_1 + x_2$	0
3	1	1	$M_3 = \bar{x}_1 + \bar{x}_2$	1

$$f(x_1, x_2) = M_0 \cdot M_2 = (x_1 + x_2) \cdot (\bar{x}_1 + x_2)$$

Yet Another Example

Product-of-Sums Form

Row number	x_1	x_2	Maxterm	$f(x_1, x_2)$
0	0	0	$M_0 = x_1 + x_2$	1
1	0	1	$M_1 = x_1 + \bar{x}_2$	1
2	1	0	$M_2 = \bar{x}_1 + x_2$	0
3	1	1	$M_3 = \bar{x}_1 + \bar{x}_2$	1

We need to minimize using the zeros of the function f .
 But let's first minimize the inverse of f , i.e., \bar{f} .

Product-of-Sums Form

Row number	x_1	x_2	Maxterm	$f(x_1, x_2)$	$\overline{f}(x_1, x_2)$
0	0	0	$M_0 = x_1 + x_2$	1	0
1	0	1	$M_1 = x_1 + \overline{x_2}$	1	0
2	1	0	$M_2 = \overline{x_1} + x_2$	0	1
3	1	1	$M_3 = \overline{x_1} + \overline{x_2}$	1	0

Product-of-Sums Form

Row number	x_1	x_2	Maxterm	$f(x_1, x_2)$	$\overline{f}(x_1, x_2)$
0	0	0	$M_0 = x_1 + x_2$	1	0
1	0	1	$M_1 = x_1 + \overline{x_2}$	1	0
2	1	0	$M_2 = \overline{x_1} + x_2$	0	1
3	1	1	$M_3 = \overline{x_1} + \overline{x_2}$	1	0

Product-of-Sums Form

Row number	x_1	x_2	Maxterm	$f(x_1, x_2)$	$\overline{f}(x_1, x_2)$
0	0	0	$M_0 = x_1 + x_2$	1	0
1	0	1	$M_1 = x_1 + \overline{x}_2$	1	0
2	1	0	$M_2 = \overline{x}_1 + x_2$	0	1
3	1	1	$M_3 = \overline{x}_1 + \overline{x}_2$	1	0

$$\begin{aligned}\overline{f}(x_1, x_2) &= m_2 \\ &= x_1 \overline{x}_2\end{aligned}$$

Product-of-Sums Form

Row number	x_1	x_2	Maxterm	$f(x_1, x_2)$	$\overline{f}(x_1, x_2)$
0	0	0	$M_0 = x_1 + x_2$	1	0
1	0	1	$M_1 = x_1 + \overline{x}_2$	1	0
2	1	0	$M_2 = \overline{x}_1 + x_2$	0	1
3	1	1	$M_3 = \overline{x}_1 + \overline{x}_2$	1	0

$$\begin{aligned}\overline{\overline{f}} &= f = \overline{x_1 \overline{x}_2} \\ &= \overline{x}_1 + x_2\end{aligned}$$

$$\begin{aligned}\overline{f}(x_1, x_2) &= m_2 \\ &= x_1 \overline{x}_2\end{aligned}$$

Product-of-Sums Form

Row number	x_1	x_2	Maxterm	$f(x_1, x_2)$	$\overline{f}(x_1, x_2)$
0	0	0	$M_0 = x_1 + x_2$	1	0
1	0	1	$M_1 = x_1 + \overline{x}_2$	1	0
2	1	0	$M_2 = \overline{x}_1 + x_2$	0	1
3	1	1	$M_3 = \overline{x}_1 + \overline{x}_2$	1	0

$$\begin{aligned} \overline{\overline{f}} = f &= \overline{x_1 \overline{x}_2} & \overline{f}(x_1, x_2) &= m_2 \\ &= \overline{x}_1 + x_2 & &= x_1 \overline{x}_2 \end{aligned}$$

$$f = \overline{m}_2 = M_2$$

**minterms
(for three variables)**

The Eight minterms

x	y	z	m ₀	m ₁	m ₂	m ₃	m ₄	m ₅	m ₆	m ₇
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

The Eight minterms

x	y	z	m ₀	m ₁	m ₂	m ₃	m ₄	m ₅	m ₆	m ₇
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

Expressions for the minterms

$$m_0 = \bar{x} \bar{y} \bar{z}$$

$$m_1 = \bar{x} \bar{y} z$$

$$m_2 = \bar{x} y \bar{z}$$

$$m_3 = \bar{x} y z$$

$$m_4 = x \bar{y} \bar{z}$$

$$m_5 = x \bar{y} z$$

$$m_6 = x y \bar{z}$$

$$m_7 = x y z$$

Expressions for the minterms

$$0 \ 0 \ 0 \quad m_0 = \bar{x} \ \bar{y} \ \bar{z}$$

$$0 \ 0 \ 1 \quad m_1 = \bar{x} \ \bar{y} \ z$$

$$0 \ 1 \ 0 \quad m_2 = \bar{x} \ y \ \bar{z}$$

$$0 \ 1 \ 1 \quad m_3 = \bar{x} \ y \ z$$

$$1 \ 0 \ 0 \quad m_4 = x \ \bar{y} \ \bar{z}$$

$$1 \ 0 \ 1 \quad m_5 = x \ \bar{y} \ z$$

$$1 \ 1 \ 0 \quad m_6 = x \ y \ \bar{z}$$

$$1 \ 1 \ 1 \quad m_7 = x \ y \ z$$

The bars coincide
with the 0's
in the binary expansion
of the minterm sub-index

Maxterms (for three variables)

The Eight Maxterms

[illegible]

The Eight Maxterms

[illegible]

Expressions for the Maxterms

$$M_0 = x + y + z$$

$$M_1 = x + y + \bar{z}$$

$$M_2 = x + \bar{y} + z$$

$$M_3 = x + \bar{y} + \bar{z}$$

$$M_4 = \bar{x} + y + z$$

$$M_5 = \bar{x} + y + \bar{z}$$

$$M_6 = \bar{x} + \bar{y} + z$$

$$M_7 = \bar{x} + \bar{y} + \bar{z}$$

Expressions for the Maxterms

$$0 \ 0 \ 0 \quad M_0 = x + y + z$$

$$0 \ 0 \ 1 \quad M_1 = x + y + \bar{z}$$

$$0 \ 1 \ 0 \quad M_2 = x + \bar{y} + z$$

$$0 \ 1 \ 1 \quad M_3 = x + \bar{y} + \bar{z}$$

$$1 \ 0 \ 0 \quad M_4 = \bar{x} + y + z$$

$$1 \ 0 \ 1 \quad M_5 = \bar{x} + y + \bar{z}$$

$$1 \ 1 \ 0 \quad M_6 = \bar{x} + \bar{y} + z$$

$$1 \ 1 \ 1 \quad M_7 = \bar{x} + \bar{y} + \bar{z}$$

The bars coincide
with the 1's
in the binary expansion
of the maxterm sub-index

minterms and Maxterms (for three variables)

minterms and Maxterms

$$m_0 = \bar{x} \bar{y} \bar{z}$$

$$m_1 = \bar{x} \bar{y} z$$

$$m_2 = \bar{x} y \bar{z}$$

$$m_3 = \bar{x} y z$$

$$m_4 = x \bar{y} \bar{z}$$

$$m_5 = x \bar{y} z$$

$$m_6 = x y \bar{z}$$

$$m_7 = x y z$$

$$M_0 = x + y + z$$

$$M_1 = x + y + \bar{z}$$

$$M_2 = x + \bar{y} + z$$

$$M_3 = x + \bar{y} + \bar{z}$$

$$M_4 = \bar{x} + y + z$$

$$M_5 = \bar{x} + y + \bar{z}$$

$$M_6 = \bar{x} + \bar{y} + z$$

$$M_7 = \bar{x} + \bar{y} + \bar{z}$$

minterms and Maxterms (with three variables)

Row number	x_1	x_2	x_3	Minterm	Maxterm
0	0	0	0	$m_0 = \bar{x}_1\bar{x}_2\bar{x}_3$	$M_0 = x_1 + x_2 + x_3$
1	0	0	1	$m_1 = \bar{x}_1\bar{x}_2x_3$	$M_1 = x_1 + x_2 + \bar{x}_3$
2	0	1	0	$m_2 = \bar{x}_1x_2\bar{x}_3$	$M_2 = x_1 + \bar{x}_2 + x_3$
3	0	1	1	$m_3 = \bar{x}_1x_2x_3$	$M_3 = x_1 + \bar{x}_2 + \bar{x}_3$
4	1	0	0	$m_4 = x_1\bar{x}_2\bar{x}_3$	$M_4 = \bar{x}_1 + x_2 + x_3$
5	1	0	1	$m_5 = x_1\bar{x}_2x_3$	$M_5 = \bar{x}_1 + x_2 + \bar{x}_3$
6	1	1	0	$m_6 = x_1x_2\bar{x}_3$	$M_6 = \bar{x}_1 + \bar{x}_2 + x_3$
7	1	1	1	$m_7 = x_1x_2x_3$	$M_7 = \bar{x}_1 + \bar{x}_2 + \bar{x}_3$

[Figure 2.22 from the textbook]

Examples with three-variable functions

A three-variable function

Row number	x_1	x_2	x_3	$f(x_1, x_2, x_3)$
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	0
4	1	0	0	1
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

[Figure 2.23 from the textbook]

Sum-of-Products (SOP)

Row number	x_1	x_2	x_3	$f(x_1, x_2, x_3)$
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	0
4	1	0	0	1
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

Sum-of-Products (SOP)

Row number	x_1	x_2	x_3	$f(x_1, x_2, x_3)$
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	0
4	1	0	0	1
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

$$f(x_1, x_2, x_3) = \bar{x}_1\bar{x}_2x_3 + x_1\bar{x}_2\bar{x}_3 + x_1\bar{x}_2x_3 + x_1x_2\bar{x}_3$$


Sum-of-Products (SOP)

Row number	x_1	x_2	x_3	$f(x_1, x_2, x_3)$
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	0
4	1	0	0	1
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

$$f(x_1, x_2, x_3) = \bar{x}_1\bar{x}_2x_3 + x_1\bar{x}_2\bar{x}_3 + x_1\bar{x}_2x_3 + x_1x_2\bar{x}_3$$

$$\begin{aligned}
 f &= (\bar{x}_1 + x_1)\bar{x}_2x_3 + x_1(\bar{x}_2 + x_2)\bar{x}_3 \\
 &= 1 \cdot \bar{x}_2x_3 + x_1 \cdot 1 \cdot \bar{x}_3 \\
 &= \bar{x}_2x_3 + x_1\bar{x}_3
 \end{aligned}$$

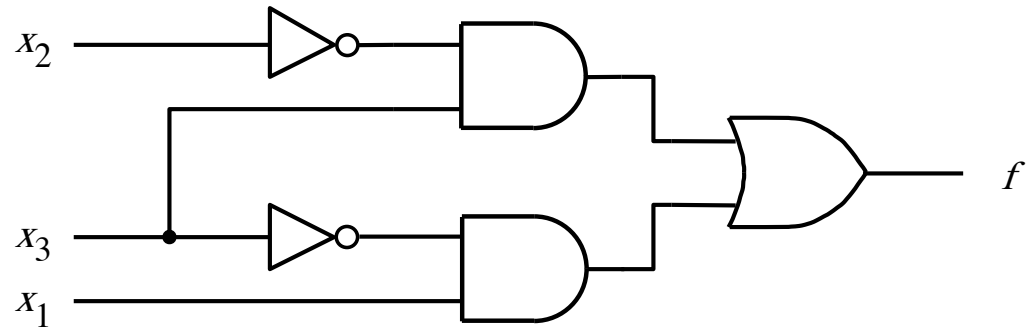Sum-of-products realization of this function



$$f = \overline{x_2} x_3 + x_1 \overline{x_3}$$

[Figure 2.24a from the textbook]

A three-variable function

Row number	x_1	x_2	x_3	$f(x_1, x_2, x_3)$
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	0
4	1	0	0	1
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

[Figure 2.23 from the textbook]

Product-of-Sums (POS)

Row number	x_1	x_2	x_3	$f(x_1, x_2, x_3)$
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	0
4	1	0	0	1
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

Product-of-Sums (POS)

Row number	x_1	x_2	x_3	$f(x_1, x_2, x_3)$
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	0
4	1	0	0	1
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

$$\begin{aligned}
 f &= \overline{m_0 + m_2 + m_3 + m_7} \\
 &= \overline{m_0} \cdot \overline{m_2} \cdot \overline{m_3} \cdot \overline{m_7} \\
 &= M_0 \cdot M_2 \cdot M_3 \cdot M_7 \\
 &= (x_1 + x_2 + x_3)(x_1 + \bar{x}_2 + x_3)(x_1 + \bar{x}_2 + \bar{x}_3)(\bar{x}_1 + \bar{x}_2 + \bar{x}_3)
 \end{aligned}$$


Product-of-Sums (POS)

Row number	x_1	x_2	x_3	$f(x_1, x_2, x_3)$
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	0
4	1	0	0	1
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

$$f = ((x_1 + x_3) + x_2)((x_1 + x_3) + \bar{x}_2)(x_1 + (\bar{x}_2 + \bar{x}_3))(\bar{x}_1 + (\bar{x}_2 + \bar{x}_3))$$

$$f = (x_1 + x_3)(\bar{x}_2 + \bar{x}_3)$$

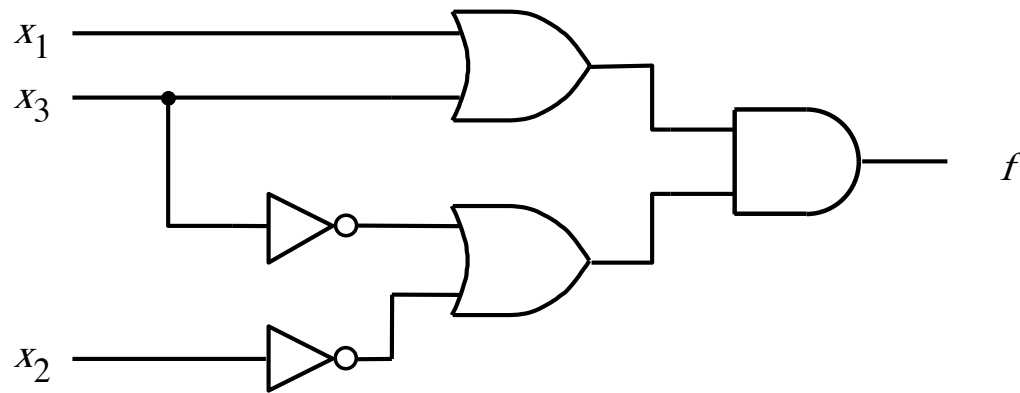
Product-of-sums realization of this function




$$f = (x_1 + x_3) \cdot (\overline{x_2} + \overline{x_3})$$

[Figure 2.24b from the textbook]

Two realizations of this function

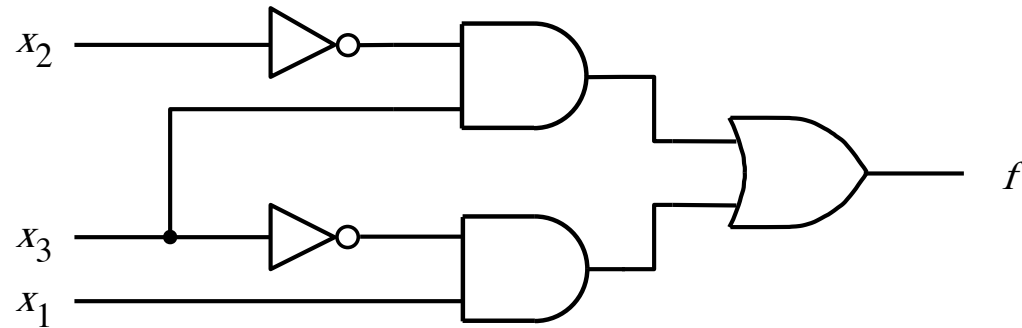

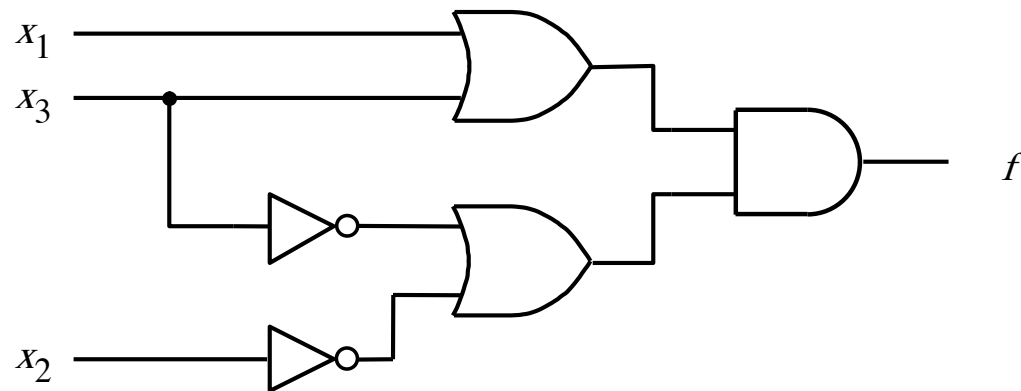(a) A minimal sum-of-products realization



(b) A minimal product-of-sums realization

[Figure 2.24 from the textbook]

Shorthand Notation for SOP

Row number	x_1	x_2	x_3	$f(x_1, x_2, x_3)$
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	0
4	1	0	0	1
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

$$f(x_1, x_2, x_3) = \sum (m_1, m_4, m_5, m_6)$$

or

$$f(x_1, x_2, x_3) = \sum m(1, 4, 5, 6)$$

Shorthand Notation for POS

Row number	x_1	x_2	x_3	$f(x_1, x_2, x_3)$
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	0
4	1	0	0	1
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

$$f(x_1, x_2, x_3) = \Pi(M_0, M_2, M_3, M_7)$$

or

$$f(x_1, x_2, x_3) = \Pi M(0, 2, 3, 7)$$

Shorthand Notation

- **Sum-of-Products (SOP)**

$$f(x_1, x_2, x_3) = \sum (m_1, m_4, m_5, m_6)$$

or

$$f(x_1, x_2, x_3) = \sum m(1, 4, 5, 6)$$

- **Product-of-Sums (POS)**

$$f(x_1, x_2, x_3) = \Pi(M_0, M_2, M_3, M_7)$$


or

$$f(x_1, x_2, x_3) = \Pi M(0, 2, 3, 7)$$


The Cost of a Circuit

- **Count all gates**
- **Count all inputs/wires to the gates**
- **Add the two partial counts. That is the cost.**

What is the cost of this circuit?

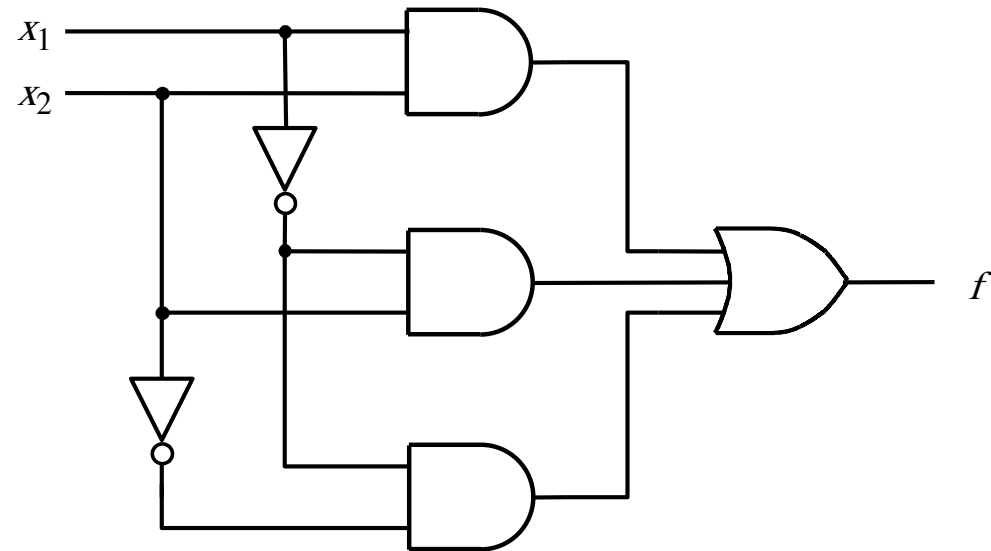


What is the cost of this circuit?

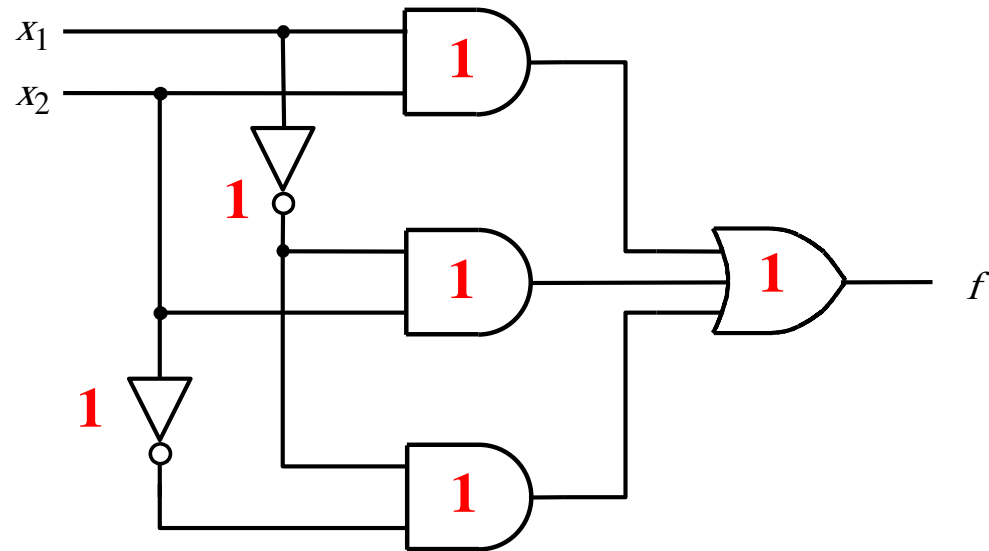

There are 6 gates.


What is the cost of this circuit?

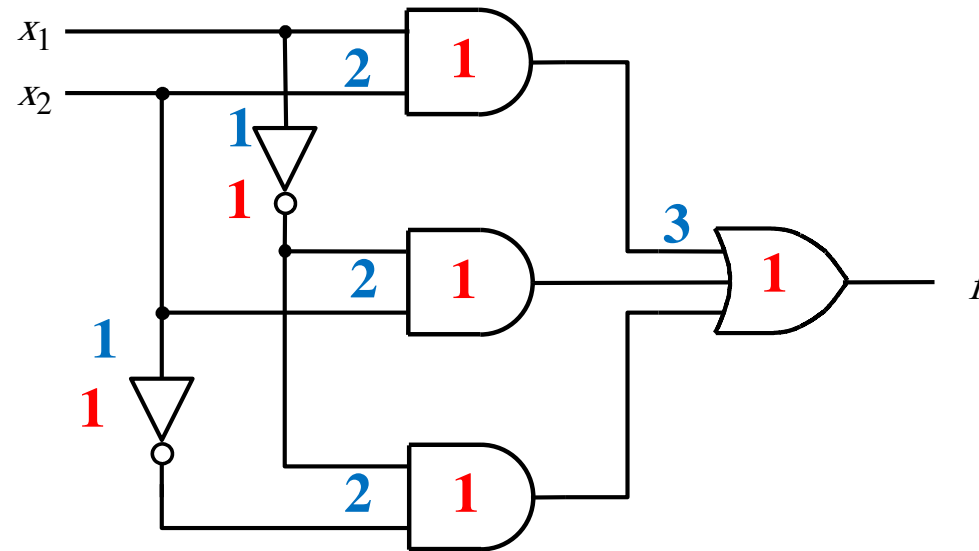


There are 6 gates and 11 inputs.

The total cost is 17.

What is the cost of each circuit?

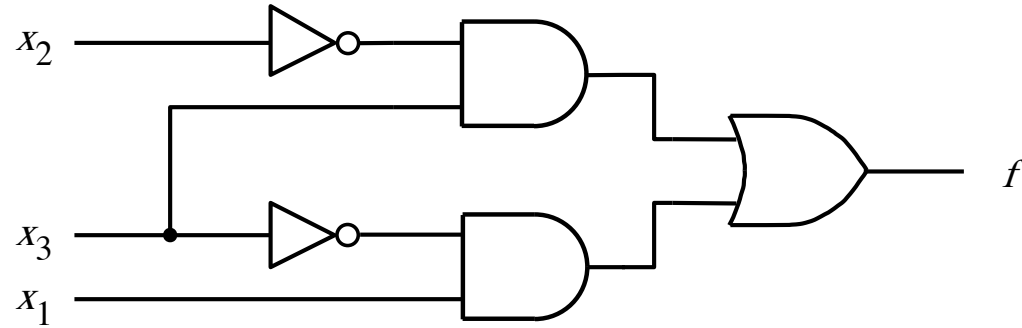

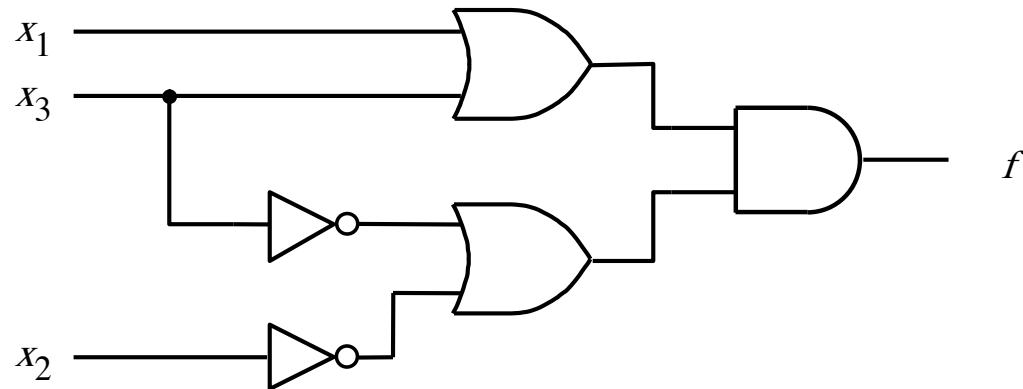(a) A minimal sum-of-products realization



(b) A minimal product-of-sums realization

Questions?

THE END