

# **CprE 2810: Digital Logic**

**Instructor: Alexander Stoytchev**

**<http://www.ece.iastate.edu/~alexs/classes/>**

# **NAND and NOR Logic Networks**

*CprE 2810: Digital Logic  
Iowa State University, Ames, IA  
Copyright © Alexander Stoytchev*

# **Administrative Stuff**

- **HW2 is due today, Sep 8 @ 10pm**
- **Please write clearly on the first page the following three things:**
  - **Your First and Last Name**
  - **Your Student ID Number**
  - **Your Lab Section Letter**
- **Submit on Canvas as \*one\* PDF file.**
- **Please orient your pages such that the text can be read without the need to rotate the page.**

# **Administrative Stuff**

- **This week we will start with Lab2**
- **Read the lab assignment and do the prelab at home.**
- **Complete the prelab on paper before you go to the lab. Otherwise, you'll lose 20% of your grade for that lab.**

# **Quick Review**

**Minterms**  
**(a set of basis functions)**

# The Four Basis Functions

x	y	$f_{00}$
0	0	1
0	1	0
1	0	0
1	1	0

$f_{00}(x, y)$

x	y	$f_{01}$
0	0	0
0	1	1
1	0	0
1	1	0

$f_{01}(x, y)$

x	y	$f_{10}$
0	0	0
0	1	0
1	0	1
1	1	0

$f_{10}(x, y)$

x	y	$f_{11}$
0	0	0
0	1	0
1	0	0
1	1	1

$f_{11}(x, y)$

# The Four Basis Functions

x	y	$f_{00}$
0	0	1
0	1	0
1	0	0
1	1	0

$f_{00}(x, y)$

x	y	$f_{01}$
0	0	0
0	1	1
1	0	0
1	1	0

$f_{01}(x, y)$

x	y	$f_{10}$
0	0	0
0	1	0
1	0	1
1	1	0

$f_{10}(x, y)$

x	y	$f_{11}$
0	0	0
0	1	0
1	0	0
1	1	1

$f_{11}(x, y)$



# The Four Basis Functions

x	y		$f_{00}(x, y)$	$f_{01}(x, y)$	$f_{10}(x, y)$	$f_{11}(x, y)$
0	0		1	0	0	0
0	1		0	1	0	0
1	0		0	0	1	0
1	1		0	0	0	1

# The Four Basis Functions

x	y		$\bar{x}\bar{y}$	$\bar{x}y$	$x\bar{y}$	$xy$
0	0		1	0	0	0
0	1		0	1	0	0
1	0		0	0	1	0
1	1		0	0	0	1

# Expressions for the minterms

$$m_0 = \bar{x} \bar{y}$$

$$m_1 = \bar{x} y$$

$$m_2 = x \bar{y}$$

$$m_3 = x y$$

# Expressions for the minterms

$$\begin{matrix} 0 & 0 \end{matrix} \quad m_0 = \overline{x} \overline{y}$$




$$\begin{matrix} 0 & 1 \end{matrix} \quad m_1 = \overline{x} y$$

$$\begin{matrix} 1 & 0 \end{matrix} \quad m_2 = x \overline{y}$$

$$\begin{matrix} 1 & 1 \end{matrix} \quad m_3 = x y$$

The bars coincide  
with the 0's  
in the binary expansion  
of the minterm sub-index

# Circuits for the four basis functions

   

# The Four Basis Functions

x	y	f <sub>00</sub>
0	0	1
0	1	0
1	0	0
1	1	0

$$f_{00}(x, y) = \bar{x} \bar{y}$$

x	y	f <sub>01</sub>
0	0	0
0	1	1
1	0	0
1	1	0

$$f_{01}(x, y) = \bar{x} y$$

x	y	f <sub>10</sub>
0	0	0
0	1	0
1	0	1
1	1	0

$$f_{10}(x, y) = x \bar{y}$$

x	y	f <sub>11</sub>
0	0	0
0	1	0
1	0	0
1	1	1

$$f_{11}(x, y) = x y$$

# The Four Basis Functions (alternative names)

x	y	f <sub>00</sub>
0	0	1
0	1	0
1	0	0
1	1	0

$$f_{00}(x, y) = \bar{x} \bar{y}$$

m<sub>0</sub>

x	y	f <sub>01</sub>
0	0	0
0	1	1
1	0	0
1	1	0

$$f_{01}(x, y) = \bar{x} y$$

m<sub>1</sub>

x	y	f <sub>10</sub>
0	0	0
0	1	0
1	0	1
1	1	0

$$f_{10}(x, y) = x \bar{y}$$

m<sub>2</sub>

x	y	f <sub>11</sub>
0	0	0
0	1	0
1	0	0
1	1	1

$$f_{11}(x, y) = x y$$

m<sub>3</sub>

# The Four Basis Functions ( minterms )

x	y	$m_0$
0	0	1
0	1	0
1	0	0
1	1	0

$$f_{00}(x, y) = \bar{x} \bar{y}$$

$m_0$

x	y	$m_1$
0	0	0
0	1	1
1	0	0
1	1	0

$$f_{01}(x, y) = \bar{x} y$$

$m_1$

x	y	$m_2$
0	0	0
0	1	0
1	0	1
1	1	0

$$f_{10}(x, y) = x \bar{y}$$

$m_2$

x	y	$m_3$
0	0	0
0	1	0
1	0	0
1	1	1

$$f_{11}(x, y) = x y$$

$m_3$



**Maxterms**  
**(an alternative set of basis functions)**

# The Four Maxterms

x	y	$M_0$
0	0	0
0	1	1
1	0	1
1	1	1

$M_0(x, y)$

x	y	$M_1$
0	0	1
0	1	0
1	0	1
1	1	1

$M_1(x, y)$

x	y	$M_2$
0	0	1
0	1	1
1	0	0
1	1	1

$M_2(x, y)$

x	y	$M_3$
0	0	1
0	1	1
1	0	1
1	1	0

$M_3(x, y)$

# The Four Maxterms

x	y	$M_0$
0	0	0
0	1	1
1	0	1
1	1	1

$M_0(x, y)$

x	y	$M_1$
0	0	1
0	1	0
1	0	1
1	1	1

$M_1(x, y)$

x	y	$M_2$
0	0	1
0	1	1
1	0	0
1	1	1

$M_2(x, y)$

x	y	$M_3$
0	0	1
0	1	1
1	0	1
1	1	0

$M_3(x, y)$

# The Four Maxterms

x	y		$M_0(x, y)$	$M_1(x, y)$	$M_2(x, y)$	$M_3(x, y)$
0	0		0	1	1	1
0	1		1	0	1	1
1	0		1	1	0	1
1	1		1	1	1	0

# The Four Maxterms

x	y		$x + y$	$x + \bar{y}$	$\bar{x} + y$	$\bar{x} + \bar{y}$
0	0		0	1	1	1
0	1		1	0	1	1
1	0		1	1	0	1
1	1		1	1	1	0

# Expressions for the Maxterms

$$M_0 = x + y$$

$$M_1 = x + \bar{y}$$

$$M_2 = \bar{x} + y$$

$$M_3 = \bar{x} + \bar{y}$$

# Expressions for the Maxterms

$$M_0 = x + y$$

$$M_1 = x + \bar{y}$$

$$M_2 = \bar{x} + y$$

$$M_3 = \bar{x} + \bar{y}$$

Note that these are now  
sums, not products.

# Expressions for the Maxterms

$$0 \ 0 \quad M_0 = x + y$$

$$0 \ 1 \quad M_1 = x + \overline{y}$$


$$1 \ 0 \quad M_2 = \overline{x} + y$$

$$1 \ 1 \quad M_3 = \overline{x} + \overline{y}$$


The bars coincide  
with the 1's  
in the binary expansion  
of the maxterm sub-index




# Circuits for the four Maxterms

 


$$M_0(x, y) = x + y$$

 

$$M_1(x, y) = x + \bar{y}$$

 

$$M_2(x, y) = \bar{x} + y$$

 

$$M_3(x, y) = \bar{x} + \bar{y}$$

# Minterms and Maxterms

Row number	$x_1$	$x_2$	Minterm	Maxterm
0	0	0	$m_0 = \bar{x}_1 \bar{x}_2$	$M_0 = x_1 + x_2$
1	0	1	$m_1 = \bar{x}_1 x_2$	$M_1 = x_1 + \bar{x}_2$
2	1	0	$m_2 = x_1 \bar{x}_2$	$M_2 = \bar{x}_1 + x_2$
3	1	1	$m_3 = x_1 x_2$	$M_3 = \bar{x}_1 + \bar{x}_2$

# Minterms and Maxterms

Row number	$x_1$	$x_2$	Minterm	Maxterm
0	0	0	$m_0 = \bar{x}_1 \bar{x}_2$	$M_0 = x_1 + x_2$
1	0	1	$m_1 = \bar{x}_1 x_2$	$M_1 = x_1 + \bar{x}_2$
2	1	0	$m_2 = x_1 \bar{x}_2$	$M_2 = \bar{x}_1 + x_2$
3	1	1	$m_3 = x_1 x_2$	$M_3 = \bar{x}_1 + \bar{x}_2$

Use these for  
**Sum-of-Products**  
 Minimization  
 (1's of the function)

Use these for  
**Product-of-Sums**  
 Minimization  
 (0's of the function)

# Sum-of-Products Form

(uses the **ones** of the function)

# Sum-of-Products Form

Row number	$x_1$	$x_2$	Minterm	$f(x_1, x_2)$
0	0	0	$m_0 = \overline{x_1}\overline{x_2}$	1
1	0	1	$m_1 = \overline{x_1}x_2$	1
2	1	0	$m_2 = x_1\overline{x_2}$	0
3	1	1	$m_3 = x_1x_2$	1

# Sum-of-Products Form

Row number	$x_1$	$x_2$	Minterm	$f(x_1, x_2)$
0	0	0	$m_0 = \overline{x_1}\overline{x_2}$	1
1	0	1	$m_1 = \overline{x_1}x_2$	1
2	1	0	$m_2 = x_1\overline{x_2}$	0
3	1	1	$m_3 = x_1x_2$	1

# Sum-of-Products Form

Row number	$x_1$	$x_2$	Minterm	$f(x_1, x_2)$
0	0	0	$m_0 = \bar{x}_1\bar{x}_2$	1
1	0	1	$m_1 = \bar{x}_1x_2$	1
2	1	0	$m_2 = x_1\bar{x}_2$	0
3	1	1	$m_3 = x_1x_2$	1

$$\begin{aligned}
 f &= m_0 \cdot 1 + m_1 \cdot 1 + m_2 \cdot 0 + m_3 \cdot 1 \\
 &= m_0 + m_1 + m_3 \\
 &= \bar{x}_1\bar{x}_2 + \bar{x}_1x_2 + x_1x_2
 \end{aligned}$$

# Product-of-Sums Form

(uses the **zeros** of the function)



# Product-of-Sums Form

(for this logic function)

Row number	$x_1$	$x_2$	Maxterm	$f(x_1, x_2)$
0	0	0	$M_0 = x_1 + x_2$	0
1	0	1	$M_1 = x_1 + \bar{x}_2$	1
2	1	0	$M_2 = \bar{x}_1 + x_2$	0
3	1	1	$M_3 = \bar{x}_1 + \bar{x}_2$	1

# Product-of-Sums Form

(for this logic function)

Row number	$x_1$	$x_2$	Maxterm	$f(x_1, x_2)$
0	0	0	$M_0 = x_1 + x_2$	0
1	0	1	$M_1 = x_1 + \bar{x}_2$	1
2	1	0	$M_2 = \bar{x}_1 + x_2$	0
3	1	1	$M_3 = \bar{x}_1 + \bar{x}_2$	1

# Product-of-Sums Form

(for this logic function)

Row number	$x_1$	$x_2$	Maxterm	$f(x_1, x_2)$
0	0	0	$M_0 = x_1 + x_2$	0
1	0	1	$M_1 = x_1 + \bar{x}_2$	1
2	1	0	$M_2 = \bar{x}_1 + x_2$	0
3	1	1	$M_3 = \bar{x}_1 + \bar{x}_2$	1

$$f(x_1, x_2) = M_0 \bullet M_2 = (x_1 + x_2) \bullet (\bar{x}_1 + x_2)$$

# Shorthand Notation

- **Sum-of-Products (SOP)**

$$f(x_1, x_2, x_3) = \sum (m_1, m_4, m_5, m_6)$$

or

$$f(x_1, x_2, x_3) = \sum m(1, 4, 5, 6)$$

- **Product-of-Sums (POS)**

$$f(x_1, x_2, x_3) = \Pi(M_0, M_2, M_3, M_7)$$

or

$$f(x_1, x_2, x_3) = \Pi M(0, 2, 3, 7)$$

# Shorthand Notation for SOP

Row number	$x_1$	$x_2$	$x_3$	$f(x_1, x_2, x_3)$
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	0
4	1	0	0	1
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

$$f(x_1, x_2, x_3) = \sum (m_1, m_4, m_5, m_6)$$

or

$$f(x_1, x_2, x_3) = \sum m(1, 4, 5, 6)$$

# Shorthand Notation

Row number	$x_1$	$x_2$	$x_3$	Minterm	Maxterm
0	0	0	0	$m_0 = \bar{x}_1\bar{x}_2\bar{x}_3$	$M_0 = x_1 + x_2 + x_3$
1	0	0	1	$m_1 = \bar{x}_1\bar{x}_2x_3$	$M_1 = x_1 + x_2 + \bar{x}_3$
2	0	1	0	$m_2 = \bar{x}_1x_2\bar{x}_3$	$M_2 = x_1 + \bar{x}_2 + x_3$
3	0	1	1	$m_3 = \bar{x}_1x_2x_3$	$M_3 = x_1 + \bar{x}_2 + \bar{x}_3$
4	1	0	0	$m_4 = x_1\bar{x}_2\bar{x}_3$	$M_4 = \bar{x}_1 + x_2 + x_3$
5	1	0	1	$m_5 = x_1\bar{x}_2x_3$	$M_5 = \bar{x}_1 + x_2 + \bar{x}_3$
6	1	1	0	$m_6 = x_1x_2\bar{x}_3$	$M_6 = \bar{x}_1 + \bar{x}_2 + x_3$
7	1	1	1	$m_7 = x_1x_2x_3$	$M_7 = \bar{x}_1 + \bar{x}_2 + \bar{x}_3$

$$f(x_1, x_2, x_3) = \sum (m_1, m_4, m_5, m_6)$$

$$f(x_1, x_2, x_3) = \sum m(1, 4, 5, 6)$$

# Shorthand Notation for POS

Row number	$x_1$	$x_2$	$x_3$	$f(x_1, x_2, x_3)$
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	0
4	1	0	0	1
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

$$f(x_1, x_2, x_3) = \Pi(M_0, M_2, M_3, M_7)$$

or

$$f(x_1, x_2, x_3) = \Pi M(0, 2, 3, 7)$$

# Shorthand Notation

Row number	$x_1$	$x_2$	$x_3$	Minterm	Maxterm
0	0	0	0	$m_0 = \bar{x}_1\bar{x}_2\bar{x}_3$	$M_0 = x_1 + x_2 + x_3$
1	0	0	1	$m_1 = \bar{x}_1\bar{x}_2x_3$	$M_1 = x_1 + x_2 + \bar{x}_3$
2	0	1	0	$m_2 = \bar{x}_1x_2\bar{x}_3$	$M_2 = x_1 + \bar{x}_2 + x_3$
3	0	1	1	$m_3 = \bar{x}_1x_2x_3$	$M_3 = x_1 + \bar{x}_2 + \bar{x}_3$
4	1	0	0	$m_4 = x_1\bar{x}_2\bar{x}_3$	$M_4 = \bar{x}_1 + x_2 + x_3$
5	1	0	1	$m_5 = x_1\bar{x}_2x_3$	$M_5 = \bar{x}_1 + x_2 + \bar{x}_3$
6	1	1	0	$m_6 = x_1x_2\bar{x}_3$	$M_6 = \bar{x}_1 + \bar{x}_2 + x_3$
7	1	1	1	$m_7 = x_1x_2x_3$	$M_7 = \bar{x}_1 + \bar{x}_2 + \bar{x}_3$

$$f(x_1, x_2, x_3) = \Pi(M_0, M_2, M_3, M_7)$$

$$f(x_1, x_2, x_3) = \Pi M(0, 2, 3, 7)$$




# Shorthand Notation

Row number	$x_1$	$x_2$	$x_3$	Minterm	Maxterm
0	0	0	0	$m_0 = \bar{x}_1\bar{x}_2\bar{x}_3$	$M_0 = x_1 + x_2 + x_3$
1	0	0	1	$m_1 = \bar{x}_1\bar{x}_2x_3$	$M_1 = x_1 + x_2 + \bar{x}_3$
2	0	1	0	$m_2 = \bar{x}_1x_2\bar{x}_3$	$M_2 = x_1 + \bar{x}_2 + x_3$
3	0	1	1	$m_3 = \bar{x}_1x_2x_3$	$M_3 = x_1 + \bar{x}_2 + \bar{x}_3$
4	1	0	0	$m_4 = x_1\bar{x}_2\bar{x}_3$	$M_4 = \bar{x}_1 + x_2 + x_3$
5	1	0	1	$m_5 = x_1\bar{x}_2x_3$	$M_5 = \bar{x}_1 + x_2 + \bar{x}_3$
6	1	1	0	$m_6 = x_1x_2\bar{x}_3$	$M_6 = \bar{x}_1 + \bar{x}_2 + x_3$
7	1	1	1	$m_7 = x_1x_2x_3$	$M_7 = \bar{x}_1 + \bar{x}_2 + \bar{x}_3$


Notice that the red and the green are nicely separated and that they cover all possible rows (no gaps).

# **Two New Logic Gates**


# The Three Basic Logic Gates

 

NOT gate

 


AND gate

 


OR gate

# NAND Gate

 


$x_1$	$x_2$	f
0	0	1
0	1	1
1	0	1
1	1	0

# NOR Gate

 


$x_1$	$x_2$	f
0	0	1
0	1	0
1	0	0
1	1	0

# AND vs NAND

 


$x_1$	$x_2$	f
0	0	0
0	1	0
1	0	0
1	1	1

 


$x_1$	$x_2$	f
0	0	1
0	1	1
1	0	1
1	1	0

# AND followed by NOT = NAND

 


$x_1$	$x_2$	f
0	0	0
0	1	0
1	0	0
1	1	1

f
1
1
1
0

 


$x_1$	$x_2$	f
0	0	1
0	1	1
1	0	1
1	1	0

# NAND followed by NOT = AND

 

$x_1$	$x_2$	f
0	0	1
0	1	1
1	0	1
1	1	0



f
0
0
0
1

 

$x_1$	$x_2$	f
0	0	0
0	1	0
1	0	0
1	1	1




# OR vs NOR

  

$x_1$	$x_2$	f
0	0	0
0	1	1
1	0	1
1	1	1


$x_1$	$x_2$	f
0	0	1
0	1	0
1	0	0
1	1	0

# OR followed by NOT = NOR

 


$x_1$	$x_2$	f
0	0	0
0	1	1
1	0	1
1	1	1

f
1
0
0
0

 


$x_1$	$x_2$	f
0	0	1
0	1	0
1	0	0
1	1	0

# NOR followed by NOT = OR

 

$x_1$	$x_2$	f
0	0	1
0	1	0
1	0	0
1	1	0

f
0
1
1
1

 

$x_1$	$x_2$	f
0	0	0
0	1	1
1	0	1
1	1	1


**Why do we need two more gates?**

**Why do we need two more gates?**


**They can be implemented with fewer transistors.**

**They are simpler to implement,  
but are they also useful?**

# Building a NOT Gate with NAND

 


$x$	$\bar{x}$
0	1
1	0

 


$x$	$x$	$f$
0	0	1
0	1	1
1	0	1
1	1	0

# Building a NOT Gate with NAND

 

$x$	$\bar{x}$
0	1
1	0

 


$x$	$x$	$f$
0	0	1
1	1	0


impossible  
combinations



# Building a NOT Gate with NAND

 

$x$	$\bar{x}$
0	1
1	0


 


$x$	$x$	$f$
0	0	1
1	1	0

impossible  
combinations

Thus, the two truth tables are equal!

# Building a NOT Gate with NAND

  

$$\overline{x \cdot x} = \bar{x}$$

Another way to think about this.


# Building an AND gate with NAND gates

**Desired AND Gate**



$$Q = A \text{ AND } B$$

**NAND Construction**

 

$$= \text{NOT}(\text{NOT}(A \text{ AND } B))$$

**Truth Table**

Input A	Input B	Output Q
0	0	0
0	1	0
1	0	0
1	1	1


# Building an OR gate with NAND gates

Desired OR Gate



$$Q = A \text{ OR } B$$

NAND Construction

 

$$= \text{NOT} [ \text{NOT}(A \text{ AND } A) \text{ AND } \text{NOT}(B \text{ AND } B) ]$$

Truth Table

Input A	Input B	Output Q
0	0	0
0	1	1
1	0	1
1	1	1

# Implications

# Implications

**Any Boolean function can be implemented  
with only NAND gates!**


# NOR gate with NAND gates

Desired NOR Gate



$$Q = \text{NOT}(A \text{ OR } B)$$

NAND Construction

 

$$= \text{NOT}\{ \text{NOT}[ \text{NOT}(A \text{ AND } A) \text{ AND } \text{NOT}(B \text{ AND } B)] \}$$

Truth Table

Input A	Input B	Output Q
0	0	1
0	1	0
1	0	0
1	1	0


# XOR gate with NAND gates

Desired XOR Gate



$$Q = A \text{ XOR } B$$

NAND Construction

 

$$= \text{NOT} [ \text{NOT} \{ A \text{ AND } \text{NOT} (A \text{ AND } B) \} \text{ AND } \text{NOT} \{ B \text{ AND } \text{NOT} (A \text{ AND } B) \} ]$$

Truth Table

Input A	Input B	Output Q
0	0	0
0	1	1
1	0	1
1	1	0




# XNOR gate with NAND gates

Desired XNOR Gate



$$Q = \text{NOT}(A \text{ XOR } B)$$

NAND Construction

 


$$= \text{NOT} [ \text{NOT} [ \text{NOT} \{ A \text{ AND } \text{NOT} (A \text{ AND } B) \} \text{ AND } \text{NOT} \{ B \text{ AND } \text{NOT} (A \text{ AND } B) \} ] ]$$

Truth Table

Input A	Input B	Output Q
0	0	1
0	1	0
1	0	0
1	1	1



# Building a NOT Gate with NOR

 


$x$	$\overline{x}$
0	1
1	0



$x$	$x$	$f$
0	0	1
0	1	0
1	0	0
1	1	0

# Building a NOT Gate with NOR

 


$x$	$\overline{x}$
0	1
1	0



$x$	$x$	$f$
0	0	1
1	1	0

impossible  
combinations

# Building a NOT Gate with NOR

 

$x$	$\overline{x}$
0	1
1	0




$x$	$x$	$f$
0	0	1
1	1	0

impossible  
combinations

Thus, the two truth tables are equal!

# Building a NOT Gate with NOR

 

$$\overline{X + X} = \overline{X}$$


Another way to think about this.

# Building an OR gate with NOR gates

**Desired Gate**



**NOR Construction**

 


**Truth Table**

Input A	Input B	Output Q
0	0	0
0	1	1
1	0	1
1	1	1

**Let's build an AND gate with NOR gates**



# Let's build an AND gate with NOR gates

 

**Truth Table**

Input A	Input B	Output Q
0	0	0
0	1	0
1	0	0
1	1	1

# Implications

# Implications


**Any Boolean function can be implemented  
with only NOR gates!**

# NAND gate with NOR gates

**Desired Gate**




**NOR Construction**

 

**Truth Table**

Input A	Input B	Output Q
0	0	1
0	1	1
1	0	1
1	1	0

# XOR gate with NOR gates

 

Truth Table


Input A	Input B	Output Q
0	0	0
0	1	1
1	0	1
1	1	0

# XNOR gate with NOR gates

Desired XNOR Gate



NOR Construction

 


Truth Table

Input A	Input B	Output Q
0	0	1
0	1	0
1	0	0
1	1	1


The following examples came from this book



 


[ Platt 2009 ]



 


[ Platt 2009 ]

 


[ Platt 2009 ]



 


[ Platt 2009 ]

 

[ Platt 2009 ]




 

[ Platt 2009 ]


# **DeMorgan's Theorem Revisited**
 
## DeMorgan's theorem (in terms of logic gates)



$$\overline{x \cdot y} = \overline{x} + \overline{y}$$
 
## The other DeMorgan's theorem (in terms of logic gates)




$$\overline{x + y} = \overline{x} \cdot \overline{y}$$




# Shortcut Notation

# DeMorgan's theorem in terms of logic gates

 


(Theorem 15.a)  $\overline{x \cdot y} = \overline{x} + \overline{y}$

# DeMorgan's theorem in terms of logic gates


 


(Theorem 15.b)  $\overline{x + y} = \overline{x} \cdot \overline{y}$




## Two NOTs in a row

 

## Two NOTs in a row

  


# Two NOTs in a row

   


# **NAND-NAND Implementation of Sum-of-Products Expressions**

# NAND followed by NOT = AND

 

$x_1$	$x_2$	f
0	0	1
0	1	1
1	0	1
1	1	0

f
0
0
0
1

 

$x_1$	$x_2$	f
0	0	0
0	1	0
1	0	0
1	1	1




## DeMorgan's Theorem


15a.  $\overline{x \cdot y} = \bar{x} + \bar{y}$
 
# DeMorgan's Theorem



**15a.**       $\overline{x \cdot y} = \bar{x} + \bar{y}$





# Sum-Of-Products

 


# Sum-Of-Products

  



# Sum-Of-Products

  



# Sum-Of-Products

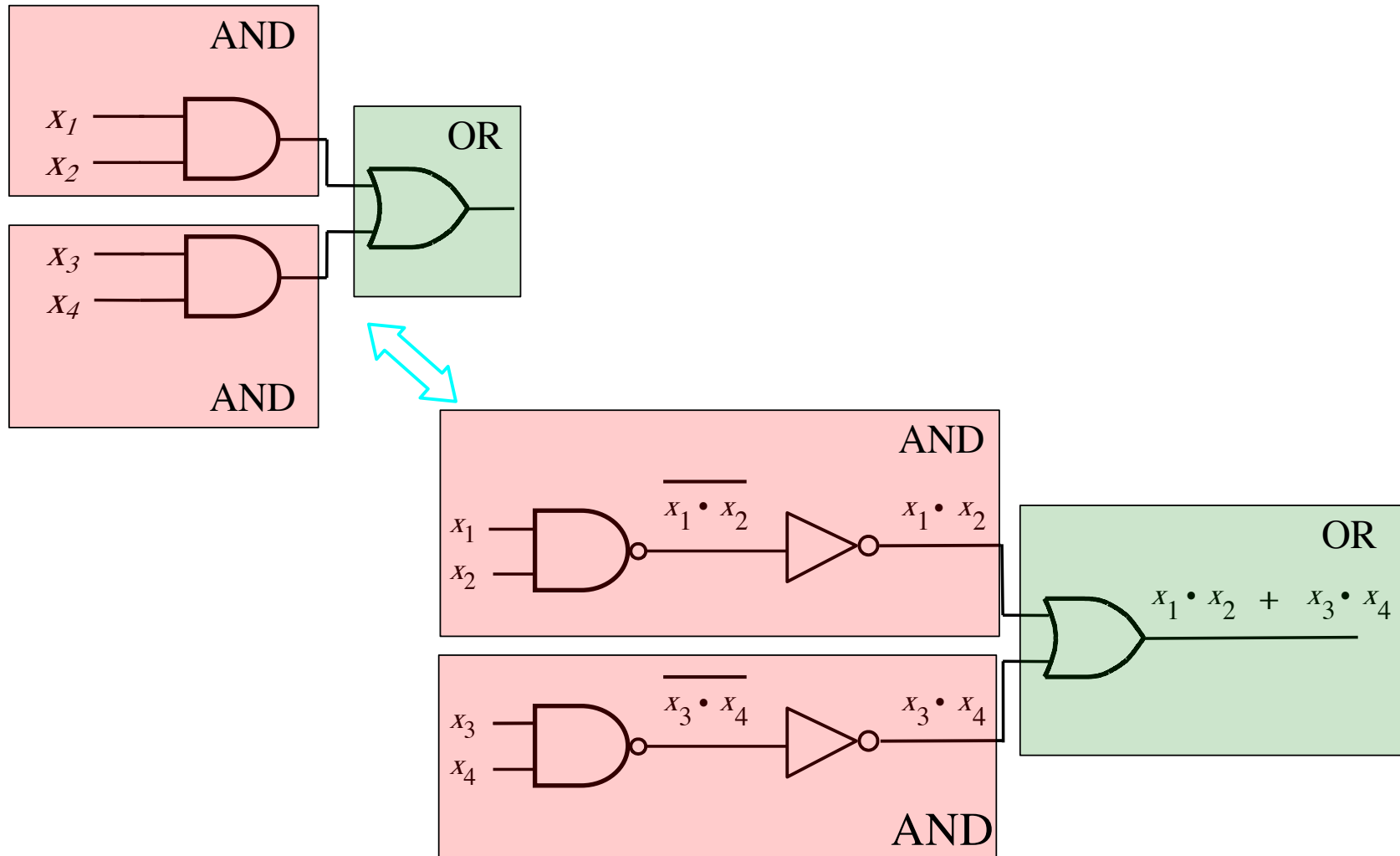

# Sum-Of-Products

 
 


# Sum-Of-Products

  




# Sum-Of-Products

 
 


# Sum-Of-Products

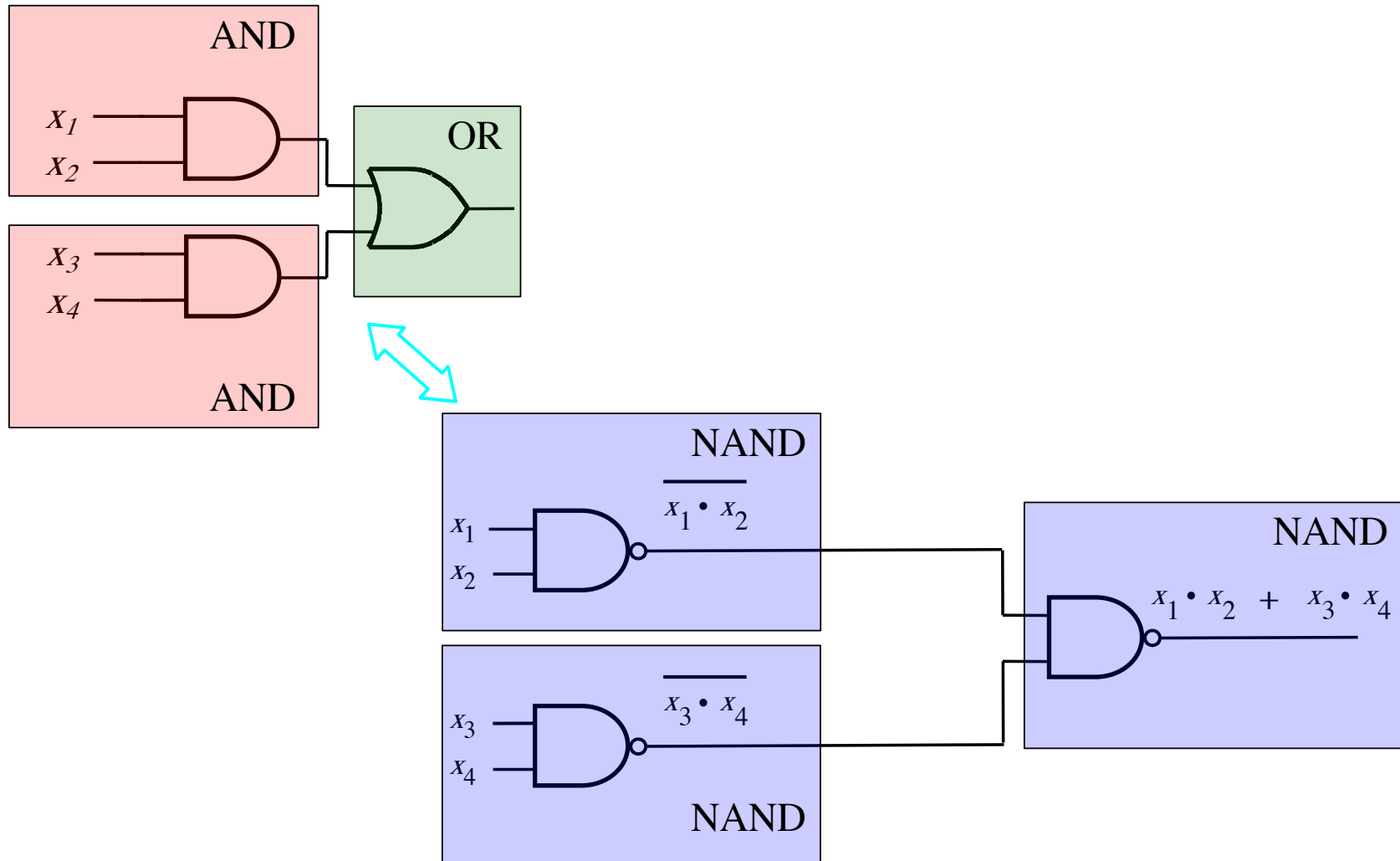


This circuit uses only NANDs

# Sum-Of-Products


 
 


This circuit uses only NANDs

## Another SOP Example

 

This circuit uses ANDs & OR

   


This circuit uses only NANDs

[ Figure 2.27 from the textbook ]


# **NOR-NOR Implementation of Product-of-Sums Expressions**

# NOR followed by NOT = OR

 

$x_1$	$x_2$	f
0	0	1
0	1	0
1	0	0
1	1	0

f
0
1
1
1

 


$x_1$	$x_2$	f
0	0	0
0	1	1
1	0	1
1	1	1

## DeMorgan's Theorem

$$\mathbf{15b.} \quad \overline{\mathbf{x + y}} = \overline{\mathbf{x}} \cdot \overline{\mathbf{y}}$$

 
# DeMorgan's Theorem

**15b.**      $\overline{x + y} = \bar{x} \cdot \bar{y}$









# Product-Of-Sums

 



# Product-Of-Sums

  



# Product-Of-Sums

  



# Product-Of-Sums

  



# Product-Of-Sums

  


# Product-Of-Sums

  

# Product-Of-Sums

  



# Product-Of-Sums

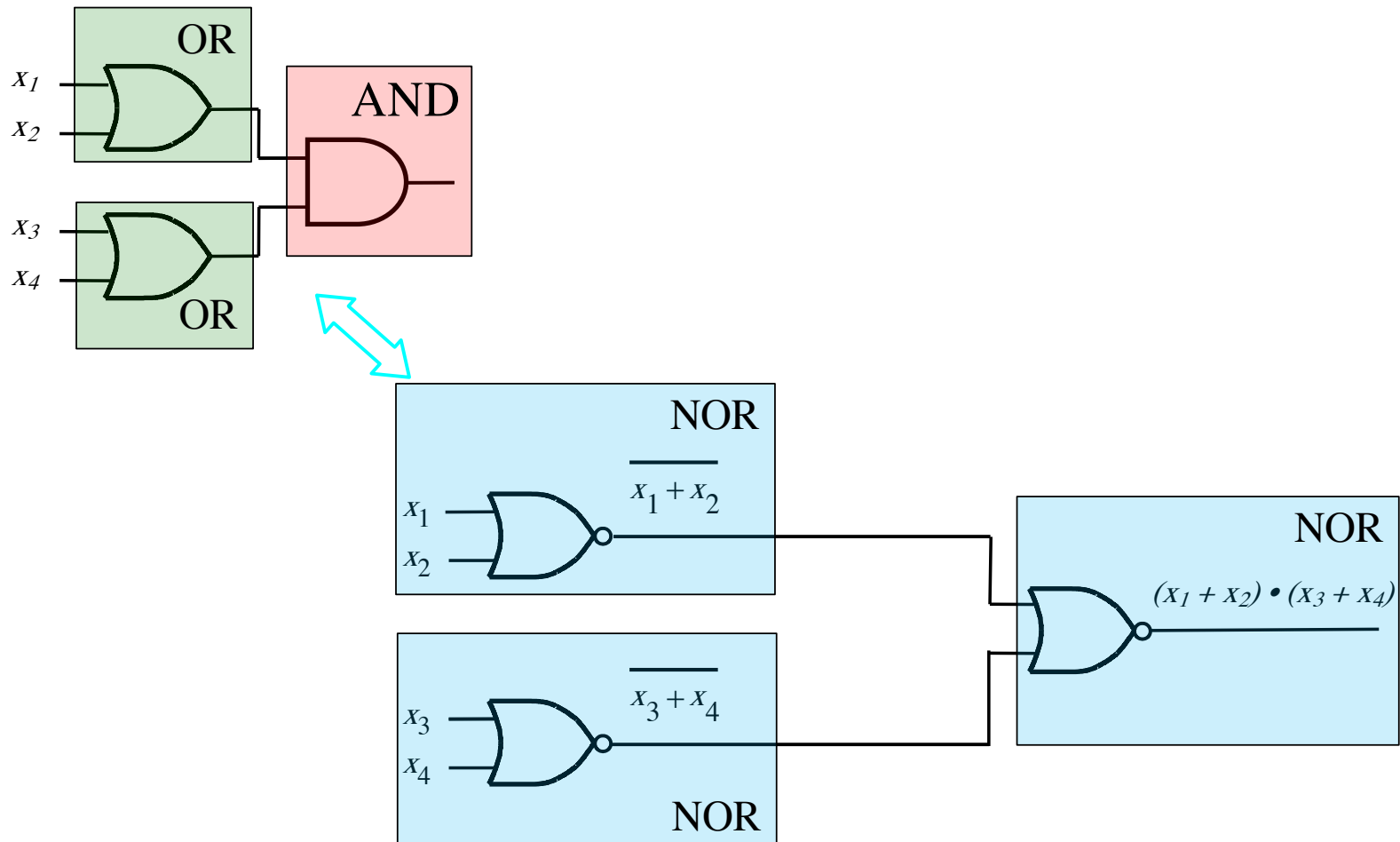

This circuit uses only NORs




# Product-Of-Sums

  

This circuit uses only NORs

# Another POS Example

 

This circuit uses ORs & AND

This circuit uses only NORs

[ Figure 2.28 from the textbook ]

# Summary

- **Sum-of-Products (SOP) expressions are directly mappable to NAND-NAND implementation.**
- **Product-of-Sums (POS) expressions are directly mappable to NOR-NOR implementation.**
- **Going from SOP to NOR-NOR is not that easy.**
- **Similarly, converting from POS to NAND-NAND implementation requires extra work.**

**Questions?**

**THE END**