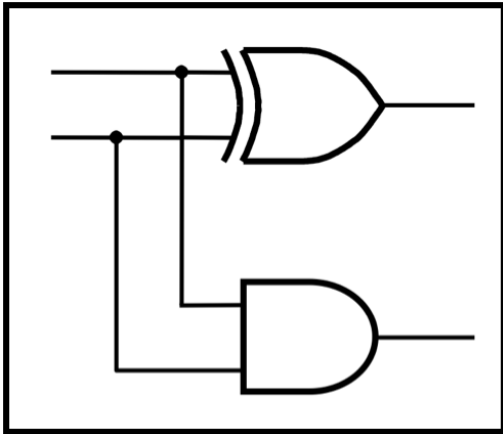




CprE 281: Digital Logic

Instructor: Alexander Stoytchev

<http://www.ece.iastate.edu/~alexs/classes/>

Integer Subtraction, Overflow Detection, and Fast Adders

*CprE 2810: Digital Logic
Iowa State University, Ames, IA
Copyright © Alexander Stoytchev*

Administrative Stuff

- **No HW is due next Monday**
- **HW 6 will is due on Monday Oct. 13 @ 10 pm.**

Administrative Stuff

- **Labs next week**
- **Mini-Project**
- **This is worth 3% of your grade (x2 labs)**
- **https://www.ece.iastate.edu/~alexs/classes/2025_Fall_2810/labs/Project-Mini/**

Three Different Methods to Represent Negative Integer Numbers

- **Sign and magnitude**
- **1's complement**
- **2's complement**

Three Different Methods to Represent Negative Integer Numbers

- Sign and magnitude
- 1's complement
- 2's complement

only this method is used
in modern computers

Interpretation of four-bit signed integers

$b_3b_2b_1b_0$	Sign and magnitude	1's complement	2's complement
0111	+7	+7	+7
0110	+6	+6	+6
0101	+5	+5	+5
0100	+4	+4	+4
0011	+3	+3	+3
0010	+2	+2	+2
0001	+1	+1	+1
0000	+0	+0	+0
1000	-0	-7	-8
1001	-1	-6	-7
1010	-2	-5	-6
1011	-3	-4	-5
1100	-4	-3	-4
1101	-5	-2	-3
1110	-6	-1	-2
1111	-7	-0	-1

[Table 3.2 from the textbook]

Interpretation of four-bit signed integers

$b_3b_2b_1b_0$	Sign and magnitude	1's complement	2's complement
0111	+7	+7	+7
0110	+6	+6	+6
0101	+5	+5	+5
0100	+4	+4	+4
0011	+3	+3	+3
0010	+2	+2	+2
0001	+1	+1	+1
0000	+0	+0	+0
1000	-0	-7	-8
1001	-1	-6	-7
1010	-2	-5	-6
1011	-3	-4	-5
1100	-4	-3	-4
1101	-5	-2	-3
1110	-6	-1	-2
1111	-7	-0	-1


Note that each table includes both positive and negative integers.

[Table 3.2 from the textbook]

2's complement representation (4-bit)

$b_3b_2b_1b_0$	2's complement
0111	+7
0110	+6
0101	+5
0100	+4
0011	+3
0010	+2
0001	+1
0000	+0
1000	-8
1001	-7
1010	-6
1011	-5
1100	-4
1101	-3
1110	-2
1111	-1

The number circle for 2's complement

 

[Figure 3.11a from the textbook]

Addition of two numbers stored
in 2's complement representation

There are four cases to consider

- $(+5) + (+2)$
- $(-5) + (+2)$
- $(+5) + (-2)$
- $(-5) + (-2)$

There are four cases to consider

- $(+5) + (+2)$ positive plus positive
- $(-5) + (+2)$ negative plus positive
- $(+5) + (-2)$ positive plus negative
- $(-5) + (-2)$ negative plus negative

Positive plus positive

$$\begin{array}{r}
 (+5) \\
 + (+2) \\
 \hline
 (+7)
 \end{array}
 \qquad
 \begin{array}{r}
 \textcolor{red}{0101} \\
 + \textcolor{green}{0010} \\
 \hline
 \textcolor{blue}{0111}
 \end{array}$$

$b_3b_2b_1b_0$	2's complement
0111	+7
0110	+6
0101	+5
0100	+4
0011	+3
0010	+2
0001	+1
0000	+0
1000	-8
1001	-7
1010	-6
1011	-5
1100	-4
1101	-3
1110	-2
1111	-1

[Figure 3.9 from the textbook]

Negative plus positive

$$\begin{array}{r}
 (-5) \\
 + (+2) \\
 \hline
 (-3)
 \end{array}
 \qquad
 \begin{array}{r}
 \textcolor{red}{1011} \\
 + \textcolor{green}{0010} \\
 \hline
 \textcolor{blue}{1101}
 \end{array}$$

$b_3b_2b_1b_0$	2's complement
0111	+7
0110	+6
0101	+5
0100	+4
0011	+3
0010	+2
0001	+1
0000	+0
1000	-8
1001	-7
1010	-6
1011	-5
1100	-4
1101	-3
1110	-2
1111	-1

[Figure 3.9 from the textbook]

Positive plus negative

$$\begin{array}{r}
 (+5) \\
 + (-2) \\
 \hline
 (+3)
 \end{array}
 \qquad
 \begin{array}{r}
 0101 \\
 + 1110 \\
 \hline
 1011
 \end{array}$$


 ignore

$b_3b_2b_1b_0$	2's complement
0111	+7
0110	+6
0101	+5
0100	+4
0011	+3
0010	+2
0001	+1
0000	+0
1000	-8
1001	-7
1010	-6
1011	-5
1100	-4
1101	-3
1110	-2
1111	-1

[Figure 3.9 from the textbook]

Negative plus negative

$$\begin{array}{r}
 (-5) \\
 + (-2) \\
 \hline
 (-7)
 \end{array}
 \qquad
 \begin{array}{r}
 1011 \\
 + 1110 \\
 \hline
 11001
 \end{array}$$


 ignore

$b_3b_2b_1b_0$	2's complement
0111	+7
0110	+6
0101	+5
0100	+4
0011	+3
0010	+2
0001	+1
0000	+0
1000	-8
1001	-7
1010	-6
1011	-5
1100	-4
1101	-3
1110	-2
1111	-1

[Figure 3.9 from the textbook]

Subtraction of two numbers stored
in 2's complement representation

There are four cases to consider

a) positive minus positive

b) negative minus positive

c) positive minus negative

d) negative minus negative

There are four cases to consider

a) $(+5) - (+2)$

b) $(-5) - (+2)$

c) $(+5) - (-2)$

d) $(-5) - (-2)$

There are four cases to consider

$$\text{a) } (+5) - (+2) = (+5) + (-2)$$

$$\text{b) } (-5) - (+2) = (-5) + (-2)$$

$$\text{c) } (+5) - (-2) = (+5) + (+2)$$

$$\text{d) } (-5) - (-2) = (-5) + (+2)$$

There are four cases to consider

$$\text{a) } (+5) - (+2) = (+5) + (-2)$$

$$\text{b) } (-5) - (+2) = (-5) + (-2)$$

$$\text{c) } (+5) - (-2) = (+5) + (+2)$$

$$\text{d) } (-5) - (-2) = (-5) + (+2)$$

We can change subtraction into addition ...

There are four cases to consider

$$\text{a) } (+5) - (+2) = (+5) + (-2)$$

$$\text{b) } (-5) - (+2) = (-5) + (-2)$$

$$\text{c) } (+5) - (-2) = (+5) + (+2)$$

$$\text{d) } (-5) - (-2) = (-5) + (+2)$$

... if we negate the second number.

There are four cases to consider

$$\text{a) } (+5) - (+2) = (+5) + (-2)$$

$$\text{b) } (-5) - (+2) = (-5) + (-2)$$

$$\text{c) } (+5) - (-2) = (+5) + (+2)$$

$$\text{d) } (-5) - (-2) = (-5) + (+2)$$

These are the four addition cases
(arranged in a shuffled order)

Case a) Start with positive minus positive

$$\begin{array}{r}
 (+5) \\
 - (+2) \\
 \hline
 (+3)
 \end{array}
 \quad
 \begin{array}{r}
 \text{0 1 0 1} \\
 - \text{0 0 1 0} \\
 \hline
 \end{array}$$

$b_3b_2b_1b_0$	2's complement
0111	+7
0110	+6
0101	+5
0100	+4
0011	+3
0010	+2
0001	+1
0000	+0
1000	-8
1001	-7
1010	-6
1011	-5
1100	-4
1101	-3
1110	-2
1111	-1

[Figure 3.10 from the textbook]

Case a) Convert to positive plus negative

$$\begin{array}{r}
 (+5) \\
 - (+2) \\
 \hline
 (+3)
 \end{array}
 \quad
 \begin{array}{c}
 \boxed{0101} \\
 \ominus \boxed{0010}
 \end{array}
 \Rightarrow
 \begin{array}{c}
 \boxed{0101} \\
 \oplus \boxed{1110}
 \end{array}$$

Notice that the operation changes to addition.

$\Rightarrow$ means negate

$b_3b_2b_1b_0$	2's complement
0111	+7
0110	+6
0101	+5
0100	+4
0011	+3
0010	+2
0001	+1
0000	+0
1000	-8
1001	-7
1010	-6
1011	-5
1100	-4
1101	-3
1110	-2
1111	-1

[Figure 3.10 from the textbook]

Case a) Perform the addition and ignore that extra bit

$$\begin{array}{r}
 (+5) \\
 - (+2) \\
 \hline
 (+3)
 \end{array}
 \quad
 \begin{array}{r}
 \text{0 1 0 1} \\
 - \text{0 0 1 0} \\
 \hline
 \end{array}
 \Rightarrow
 \begin{array}{r}
 \text{0 1 0 1} \\
 + \text{1 1 1 0} \\
 \hline
 1 \text{ 0 0 1 1}
 \end{array}
 \quad
 \begin{array}{r}
 (+5) \\
 + (-2) \\
 \hline
 (+3)
 \end{array}$$




 ignore

$b_3b_2b_1b_0$	2's complement
0111	+7
0110	+6
0101	+5
0100	+4
0011	+3
0010	+2
0001	+1
0000	+0
1000	-8
1001	-7
1010	-6
1011	-5
1100	-4
1101	-3
1110	-2
1111	-1

[Figure 3.10 from the textbook]

 Graphical interpretation of four-bit 2's complement numbers



(a) The number circle

(b) Subtracting 2 by adding its 2's complement

[Figure 3.11 from the textbook]

Case b) Start with negative minus positive

$$\begin{array}{r}
 (-5) \\
 - (+2) \\
 \hline
 (-7)
 \end{array}
 \qquad
 \begin{array}{r}
 \text{1 0 1 1} \\
 - \text{0 0 1 0} \\
 \hline
 \end{array}$$

$b_3b_2b_1b_0$	2's complement
0111	+7
0110	+6
0101	+5
0100	+4
0011	+3
0010	+2
0001	+1
0000	+0
1000	-8
1001	-7
1010	-6
1011	-5
1100	-4
1101	-3
1110	-2
1111	-1

[Figure 3.10 from the textbook]

case b) Convert to negative plus negative

$$\begin{array}{r}
 (-5) \\
 - (+2) \\
 \hline
 (-7)
 \end{array}
 \quad
 \begin{array}{r}
 \boxed{1011} \\
 - \boxed{0010} \\
 \hline
 \end{array}
 \Rightarrow
 \begin{array}{r}
 \boxed{1011} \\
 + \boxed{1110} \\
 \hline
 1 \boxed{1001} \\
 \uparrow \\
 \text{ignore}
 \end{array}
 \quad
 \begin{array}{r}
 (-5) \\
 + (-2) \\
 \hline
 (-7)
 \end{array}$$

$b_3b_2b_1b_0$	2's complement
0111	+7
0110	+6
0101	+5
0100	+4
0011	+3
0010	+2
0001	+1
0000	+0
1000	-8
1001	-7
1010	-6
1011	-5
1100	-4
1101	-3
1110	-2
1111	-1

[Figure 3.10 from the textbook]

Case c) Start with positive minus negative

$$\begin{array}{r}
 (+5) \\
 - (-2) \\
 \hline
 (+7)
 \end{array}
 \quad
 \begin{array}{r}
 \text{0 1 0 1} \\
 - \text{1 1 1 0} \\
 \hline
 \end{array}$$

$b_3b_2b_1b_0$	2's complement
0111	+7
0110	+6
0101	+5
0100	+4
0011	+3
0010	+2
0001	+1
0000	+0
1000	-8
1001	-7
1010	-6
1011	-5
1100	-4
1101	-3
1110	-2
1111	-1

[Figure 3.10 from the textbook]

Case c) Convert to positive plus positive

$$\begin{array}{r}
 (+5) \quad \quad 0101 \\
 - (-2) \quad \quad \underline{1110} \\
 \hline
 (+7)
 \end{array}
 \Rightarrow
 \begin{array}{r}
 (+5) \quad \quad 0101 \\
 + \quad \quad \underline{0010} \\
 \hline
 (+7) \quad \quad 0111
 \end{array}$$

$b_3b_2b_1b_0$	2's complement
0111	+7
0110	+6
0101	+5
0100	+4
0011	+3
0010	+2
0001	+1
0000	+0
1000	-8
1001	-7
1010	-6
1011	-5
1100	-4
1101	-3
1110	-2
1111	-1

[Figure 3.10 from the textbook]

Case d) Start with negative minus negative

$$\begin{array}{r}
 (-5) \\
 - (-2) \\
 \hline
 (-3)
 \end{array}
 \qquad
 \begin{array}{r}
 \text{1 0 1 1} \\
 - \text{1 1 1 0} \\
 \hline
 \end{array}$$

$b_3b_2b_1b_0$	2's complement
0111	+7
0110	+6
0101	+5
0100	+4
0011	+3
0010	+2
0001	+1
0000	+0
1000	-8
1001	-7
1010	-6
1011	-5
1100	-4
1101	-3
1110	-2
1111	-1

[Figure 3.10 from the textbook]

Case d) Convert to negative plus positive

$$\begin{array}{r}
 (-5) \\
 - (-2) \\
 \hline
 (-3)
 \end{array}
 \quad
 \begin{array}{r}
 \boxed{1\ 0\ 1\ 1} \\
 - \boxed{1\ 1\ 1\ 0} \\
 \hline
 \end{array}
 \Rightarrow
 \begin{array}{r}
 \boxed{1\ 0\ 1\ 1} \\
 + \boxed{0\ 0\ 1\ 0} \\
 \hline
 \boxed{1\ 1\ 0\ 1}
 \end{array}
 \quad
 \begin{array}{r}
 (-5) \\
 + (+2) \\
 \hline
 (-3)
 \end{array}$$

$b_3b_2b_1b_0$	2's complement
0111	+7
0110	+6
0101	+5
0100	+4
0011	+3
0010	+2
0001	+1
0000	+0
1000	-8
1001	-7
1010	-6
1011	-5
1100	-4
1101	-3
1110	-2
1111	-1


[Figure 3.10 from the textbook]

Take Home Message

Take Home Message

- Subtraction can be performed by simply negating the second number and adding it to the first, regardless of the signs of the two numbers.
- Thus, the same adder circuit can be used to perform both addition and subtraction !!!


Adder / Subtractor

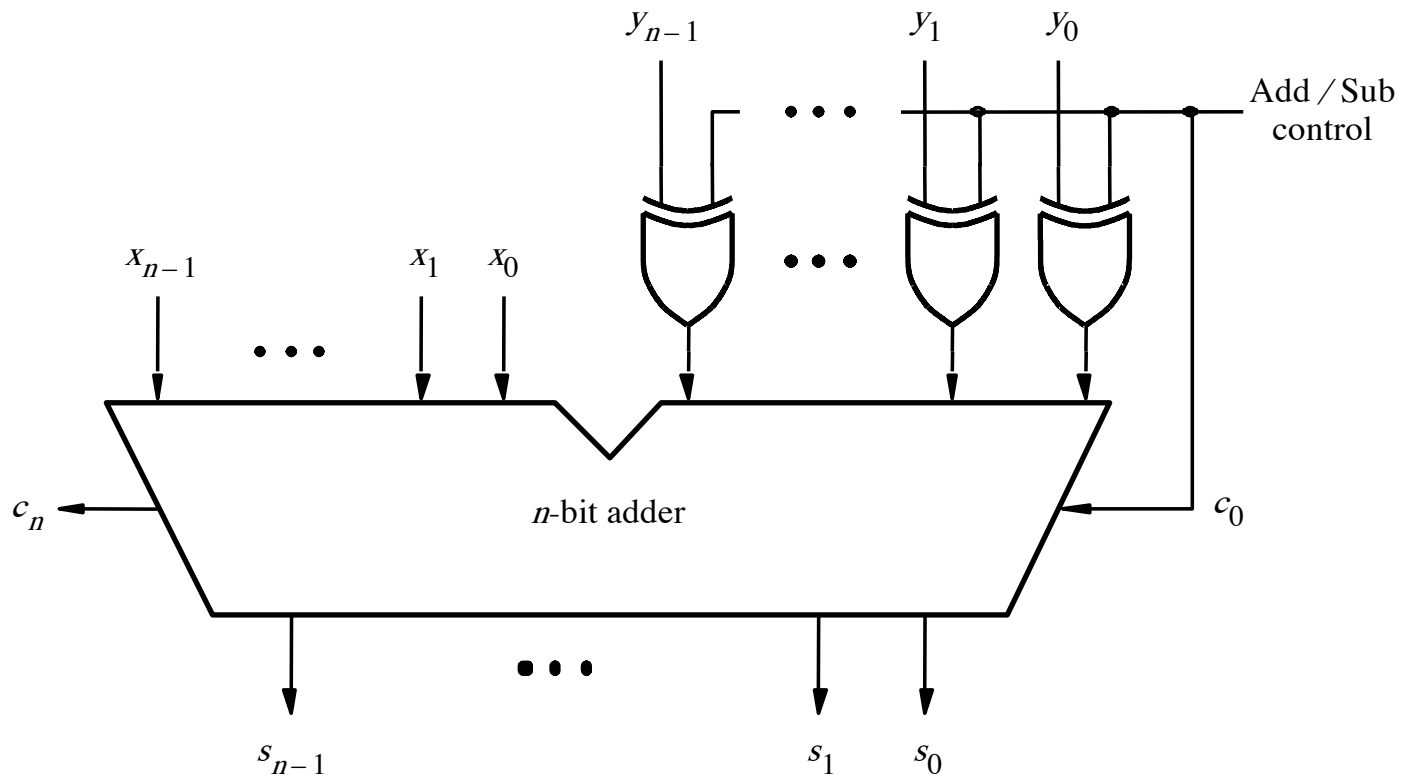

[Figure 3.12 from the textbook]


XOR Tricks

control	y	out
0	0	0
0	1	1
1	0	1
1	1	0

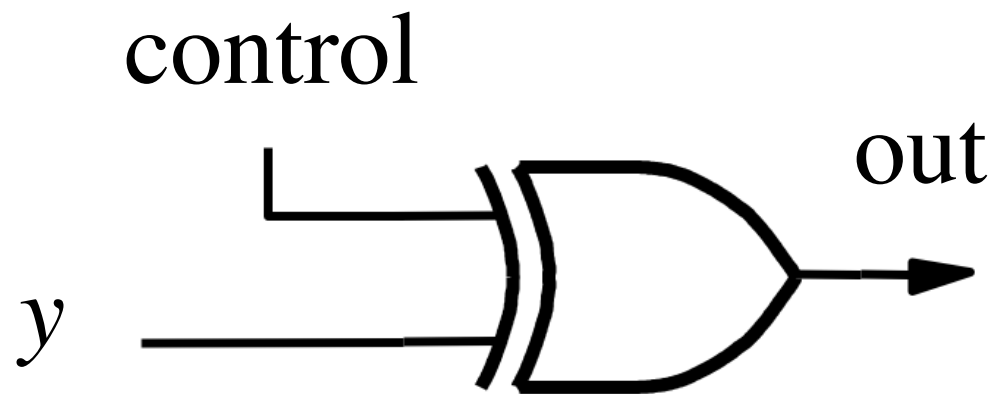

XOR as a repeater

control	y	out
0	0	0
0	1	1

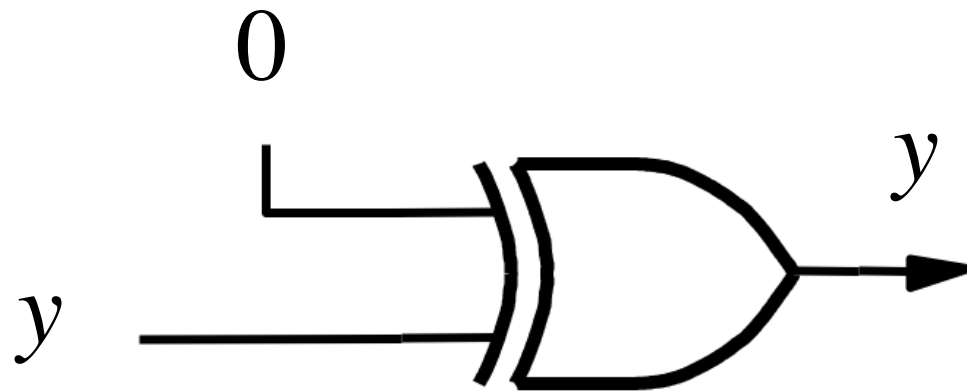


XOR as a repeater

control	y	out
0	0	0
0	1	1




XOR as an inverter

control	y	out
1	0	1
1	1	0

 


XOR as an inverter

control	y	out
1	0	1
1	1	0

 


Addition: when control = 0

 


[Figure 3.12 from the textbook]

Addition: when control = 0

 


[Figure 3.12 from the textbook]

Addition: when control = 0

 


[Figure 3.12 from the textbook]

Subtraction: when control = 1

 


[Figure 3.12 from the textbook]

Subtraction: when control = 1

 


[Figure 3.12 from the textbook]

Subtraction: when control = 1

 

[Figure 3.12 from the textbook]

Subtraction: when control = 1

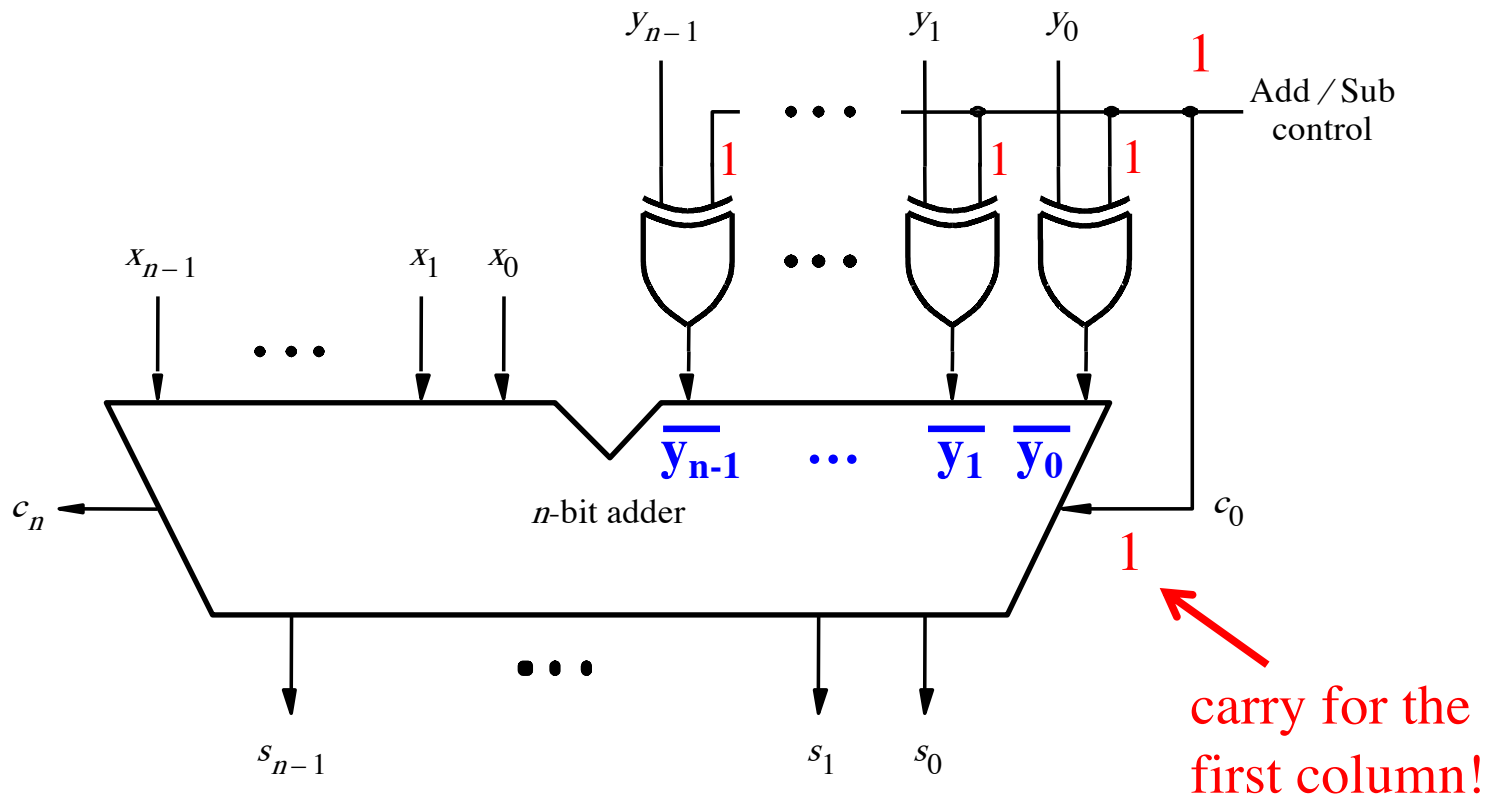


[Figure 3.12 from the textbook]


Addition Examples:

**all inputs and outputs are given in
2's complement representation**


Addition: $5 + 6 = 11$

 


Addition: **5** + **6** = **11**

 


Addition: **5** + **6** = **11**

 


Addition: **5** + **6** = **11**

 


Addition: **5** + **6** = **11**

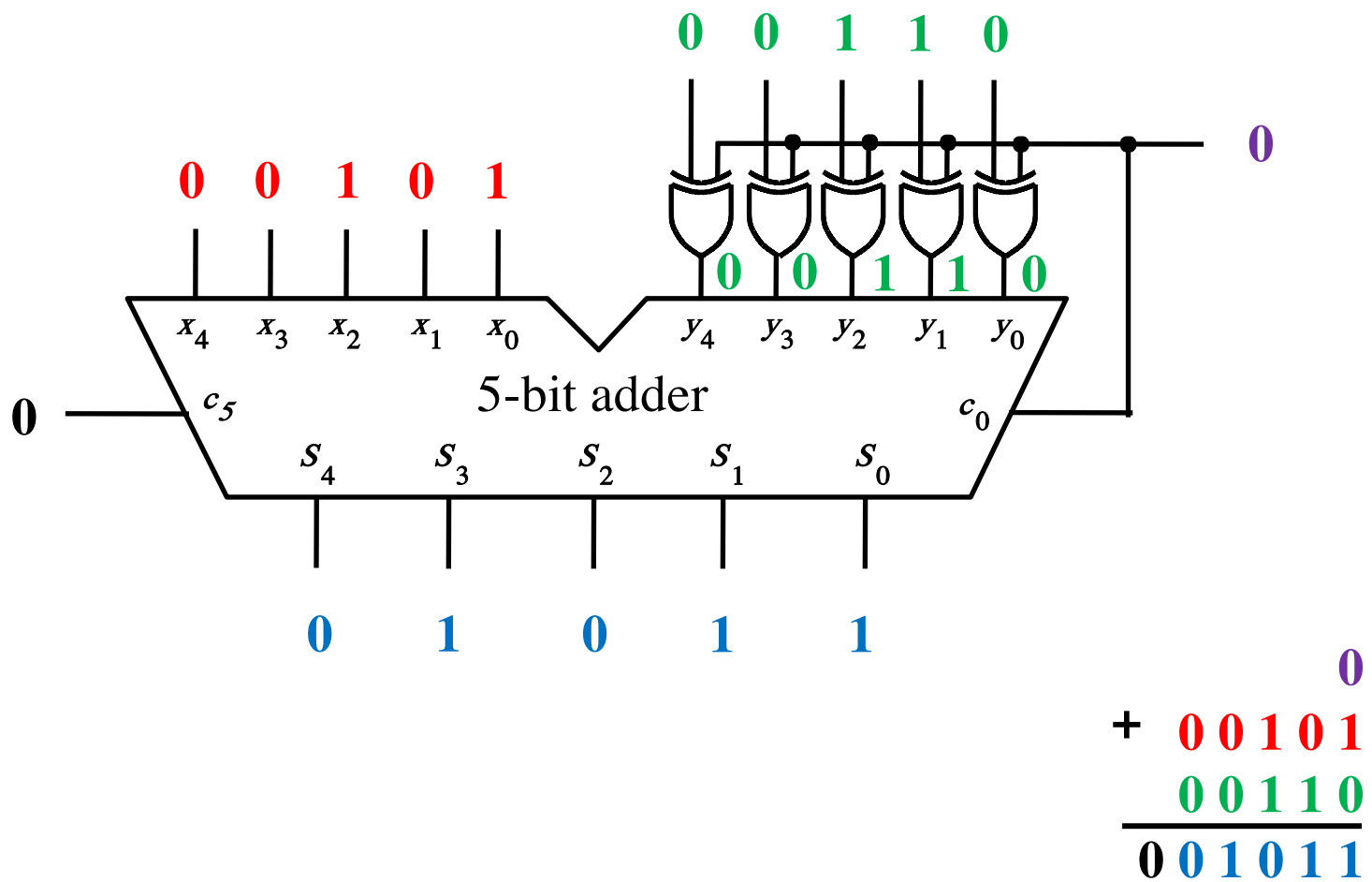


Addition: **4** + **(-7)** = **-3**

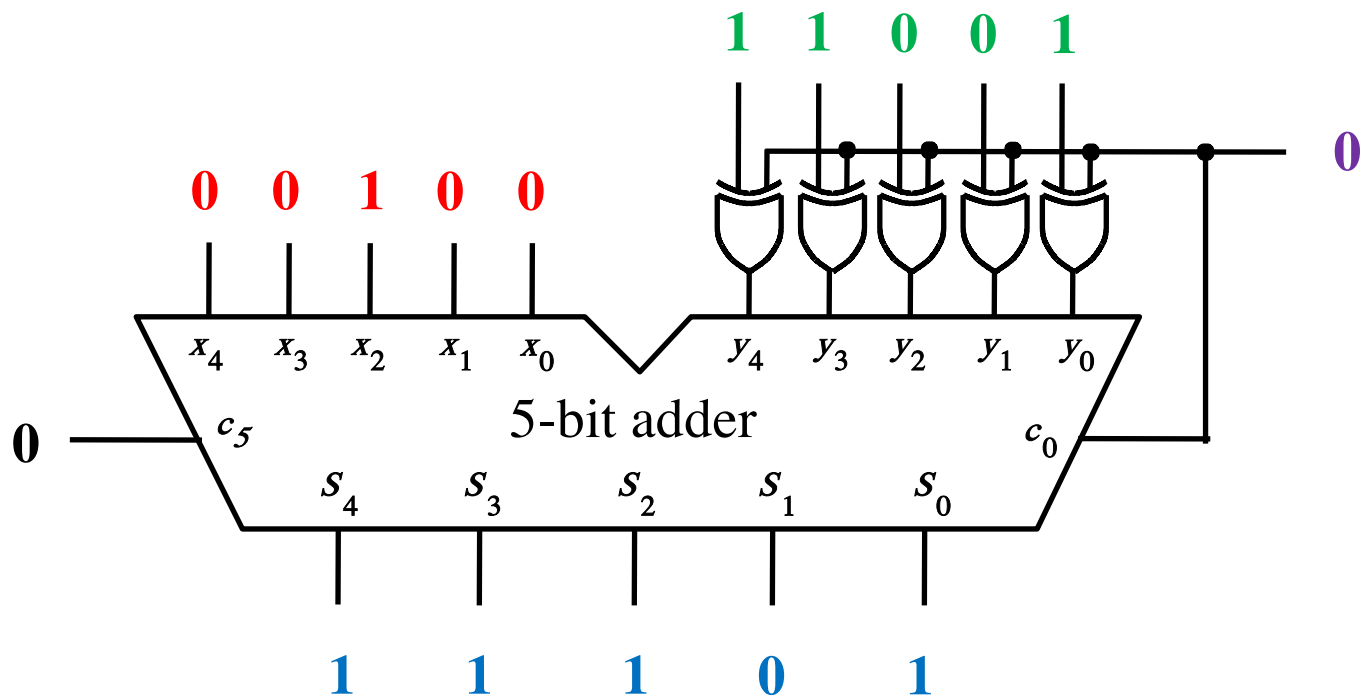

Addition: **4** + **(-7)** = **-3**

 


Addition: **4** + **(-7)** = **-3**

 


Subtraction Examples:
all inputs and outputs are given in
2's complement representation


Subtraction: **7** - **3** = **4**

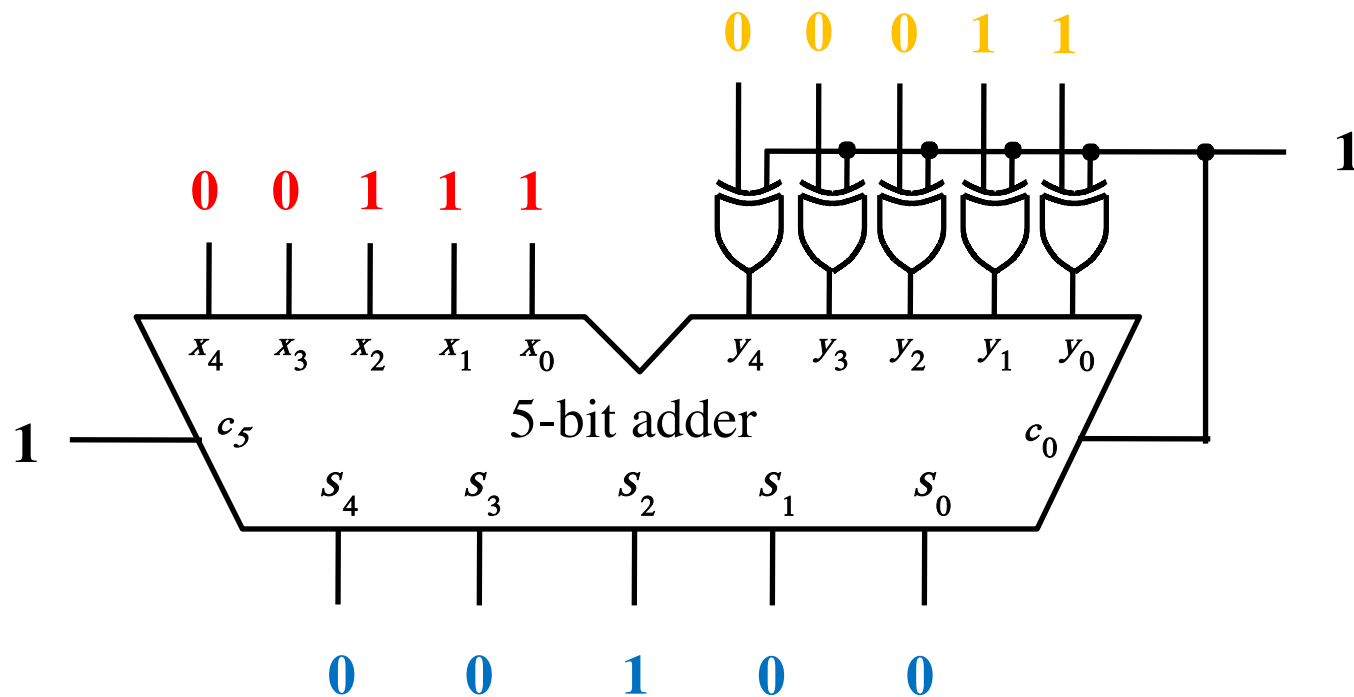


Subtraction: **7** - **3** = **4**

 


Subtraction: **7** - **3** = **4**

 

Subtraction: **7** - **3** = **4**

 

Subtraction: **7** - **3** = **4**

 

$$\begin{array}{r}
 & & & & & & 1 \\
 + & 0 & 0 & 1 & 1 & 1 \\
 & 1 & 1 & 1 & 0 & 0 \\
 \hline
 & 1 & 0 & 0 & 1 & 0 & 0
 \end{array}$$

Ignore

Analogy: Another Way to Do Subtraction

$$\textcircled{82} - \textcircled{64} = \textcircled{82} + \overset{\text{9's complement}}{\textcircled{(99 - 64)}} \textcircled{+1} - 100$$

$$= 82 + \textcircled{35 + 1} - 100$$

10's complement


$$= 82 + 36 - 100 \quad // \text{ Add the first two.}$$

$$= \textcircled{1}18 - 100 \quad // \text{ Just delete the leading 1.}$$


// No need to subtract 100.

$$= 18$$


Subtraction: $(-2) - (-5) = 3$

 


Subtraction: $(-2) - (-5) = 3$

 

Subtraction: $(-2) - (-5) = 3$

 

Subtraction: $(-2) - (-5) = 3$

 

Detecting Overflow

Examples of determination of overflow

$$\begin{array}{r}
 (+7) \\
 + (+2) \\
 \hline
 (+9)
 \end{array}
 \quad + \quad
 \begin{array}{r}
 0111 \\
 0010 \\
 \hline
 1001
 \end{array}$$

$$\begin{array}{r}
 (-7) \\
 + (+2) \\
 \hline
 (-5)
 \end{array}
 \quad + \quad
 \begin{array}{r}
 1001 \\
 0010 \\
 \hline
 1011
 \end{array}$$

$$\begin{array}{r}
 (+7) \\
 + (-2) \\
 \hline
 (+5)
 \end{array}
 \quad + \quad
 \begin{array}{r}
 0111 \\
 1110 \\
 \hline
 10101
 \end{array}$$

$$\begin{array}{r}
 (-7) \\
 + (-2) \\
 \hline
 (-9)
 \end{array}
 \quad + \quad
 \begin{array}{r}
 1001 \\
 1110 \\
 \hline
 10111
 \end{array}$$

[Figure 3.13 from the textbook]

Examples of determination of overflow

$$\begin{array}{r} (+7) \\ + (+2) \\ \hline (+9) \end{array} \quad + \quad \begin{array}{r} 0111 \\ 0010 \\ \hline 1001 \end{array}$$

$$\begin{array}{r} (-7) \\ + (+2) \\ \hline (-5) \end{array} \quad + \quad \begin{array}{r} 1001 \\ 0010 \\ \hline 1011 \end{array}$$

$$\begin{array}{r} (+7) \\ + (-2) \\ \hline (+5) \end{array} \quad + \quad \begin{array}{r} 0111 \\ 1110 \\ \hline 10101 \end{array}$$

$$\begin{array}{r} (-7) \\ + (-2) \\ \hline (-9) \end{array} \quad + \quad \begin{array}{r} 1001 \\ 1110 \\ \hline 10111 \end{array}$$

In 2's complement, both +9 and -9 are not representable with 4 bits.

Examples of determination of overflow

$$\begin{array}{r}
 (+7) \quad 01100 \\
 + (+2) \quad 0111 \\
 \hline
 (+9) \quad 1001
 \end{array}$$

$$\begin{array}{r}
 (-7) \quad 00000 \\
 + (+2) \quad 1001 \\
 \hline
 (-5) \quad 0010
 \end{array}$$

$$\begin{array}{r}
 (+7) \quad 11100 \\
 + (-2) \quad 0111 \\
 \hline
 (+5) \quad 1110
 \end{array}$$

$$\begin{array}{r}
 (-7) \quad 10000 \\
 + (-2) \quad 1001 \\
 \hline
 (-9) \quad 1001
 \end{array}$$

Include the carry bits: $c_4 \ c_3 \ c_2 \ c_1 \ c_0$

Examples of determination of overflow

$$\begin{array}{r}
 (+7) \\
 + (+2) \\
 \hline
 (+9)
 \end{array}
 \quad
 \begin{array}{r}
 \boxed{01}100 \\
 + \quad 0111 \\
 \quad 0010 \\
 \hline
 1001
 \end{array}$$

$$\begin{array}{r}
 (-7) \\
 + (+2) \\
 \hline
 (-5)
 \end{array}
 \quad
 \begin{array}{r}
 \boxed{00}000 \\
 + \quad 1001 \\
 \quad 0010 \\
 \hline
 1011
 \end{array}$$

$$\begin{array}{r}
 (+7) \\
 + (-2) \\
 \hline
 (+5)
 \end{array}
 \quad
 \begin{array}{r}
 \boxed{11}100 \\
 + \quad 0111 \\
 \quad 1110 \\
 \hline
 10101
 \end{array}$$

$$\begin{array}{r}
 (-7) \\
 + (-2) \\
 \hline
 (-9)
 \end{array}
 \quad
 \begin{array}{r}
 \boxed{10}000 \\
 + \quad 1001 \\
 \quad 1110 \\
 \hline
 10111
 \end{array}$$

Include the carry bits: $\boxed{c_4 \ c_3} c_2 \ c_1 \ c_0$

Examples of determination of overflow

$$\begin{aligned} c_4 &= 0 \\ c_3 &= 1 \end{aligned}$$

$$\begin{array}{r} (+7) \\ + (+2) \\ \hline (+9) \end{array} \quad + \quad \begin{array}{r} \boxed{01}100 \\ 0111 \\ 0010 \\ \hline 1001 \end{array}$$

$$\begin{array}{r} (-7) \\ + (+2) \\ \hline (-5) \end{array} \quad + \quad \begin{array}{r} \boxed{00}000 \\ 1001 \\ 0010 \\ \hline 1011 \end{array}$$

$$\begin{aligned} c_4 &= 0 \\ c_3 &= 0 \end{aligned}$$

$$\begin{aligned} c_4 &= 1 \\ c_3 &= 1 \end{aligned}$$

$$\begin{array}{r} (+7) \\ + (-2) \\ \hline (+5) \end{array} \quad + \quad \begin{array}{r} \boxed{11}100 \\ 0111 \\ 1110 \\ \hline 10101 \end{array}$$

$$\begin{array}{r} (-7) \\ + (-2) \\ \hline (-9) \end{array} \quad + \quad \begin{array}{r} \boxed{10}000 \\ 1001 \\ 1110 \\ \hline 10111 \end{array}$$

$$\begin{aligned} c_4 &= 1 \\ c_3 &= 0 \end{aligned}$$

Include the carry bits: $\boxed{c_4 c_3} c_2 c_1 c_0$

Examples of determination of overflow

$$\begin{matrix} c_4 = 0 \\ c_3 = 1 \end{matrix}$$

$$\begin{array}{r} (+7) \\ + (+2) \\ \hline (+9) \end{array} \quad + \quad \begin{array}{r} \boxed{01}100 \\ 0111 \\ 0010 \\ \hline 1001 \end{array}$$

$$\begin{array}{r} (-7) \\ + (+2) \\ \hline (-5) \end{array} \quad + \quad \begin{array}{r} \boxed{00}000 \\ 1001 \\ 0010 \\ \hline 1011 \end{array}$$

$$\begin{matrix} c_4 = 0 \\ c_3 = 0 \end{matrix}$$

$$\begin{matrix} c_4 = 1 \\ c_3 = 1 \end{matrix}$$

$$\begin{array}{r} (+7) \\ + (-2) \\ \hline (+5) \end{array} \quad + \quad \begin{array}{r} \boxed{11}100 \\ 0111 \\ 1110 \\ \hline 10101 \end{array}$$

$$\begin{array}{r} (-7) \\ + (-2) \\ \hline (-9) \end{array} \quad + \quad \begin{array}{r} \boxed{10}000 \\ 1001 \\ 1110 \\ \hline 10111 \end{array}$$

$$\begin{matrix} c_4 = 1 \\ c_3 = 0 \end{matrix}$$

Overflow occurs only in these two cases.

Examples of determination of overflow

$$\begin{matrix} c_4 = 0 \\ c_3 = 1 \end{matrix}$$

$$\begin{array}{r} (+7) \\ + (+2) \\ \hline (+9) \end{array} \quad + \quad \begin{array}{r} \boxed{01}100 \\ 0111 \\ 0010 \\ \hline 1001 \end{array}$$

$$\begin{array}{r} (-7) \\ + (+2) \\ \hline (-5) \end{array} \quad + \quad \begin{array}{r} \boxed{00}000 \\ 1001 \\ 0010 \\ \hline 1011 \end{array}$$

$$\begin{matrix} c_4 = 0 \\ c_3 = 0 \end{matrix}$$

$$\begin{matrix} c_4 = 1 \\ c_3 = 1 \end{matrix}$$

$$\begin{array}{r} (+7) \\ + (-2) \\ \hline (+5) \end{array} \quad + \quad \begin{array}{r} \boxed{11}100 \\ 0111 \\ 1110 \\ \hline 10101 \end{array}$$

$$\begin{array}{r} (-7) \\ + (-2) \\ \hline (-9) \end{array} \quad + \quad \begin{array}{r} \boxed{10}000 \\ 1001 \\ 1110 \\ \hline 10111 \end{array}$$

$$\begin{matrix} c_4 = 1 \\ c_3 = 0 \end{matrix}$$

$$\text{Overflow} = c_3 \bar{c}_4 + \bar{c}_3 c_4$$

Examples of determination of overflow

$$\begin{matrix} c_4 = 0 \\ c_3 = 1 \end{matrix}$$

$$\begin{array}{r} (+7) \\ + (+2) \\ \hline (+9) \end{array} \quad + \quad \begin{array}{r} \boxed{01}100 \\ 0111 \\ 0010 \\ \hline 1001 \end{array}$$

$$\begin{array}{r} (-7) \\ + (+2) \\ \hline (-5) \end{array} \quad + \quad \begin{array}{r} \boxed{00}000 \\ 1001 \\ 0010 \\ \hline 1011 \end{array}$$

$$\begin{matrix} c_4 = 0 \\ c_3 = 0 \end{matrix}$$

$$\begin{matrix} c_4 = 1 \\ c_3 = 1 \end{matrix}$$

$$\begin{array}{r} (+7) \\ + (-2) \\ \hline (+5) \end{array} \quad + \quad \begin{array}{r} \boxed{11}100 \\ 0111 \\ 1110 \\ \hline 10101 \end{array}$$

$$\begin{array}{r} (-7) \\ + (-2) \\ \hline (-9) \end{array} \quad + \quad \begin{array}{r} \boxed{10}000 \\ 1001 \\ 1110 \\ \hline 10111 \end{array}$$

$$\begin{matrix} c_4 = 1 \\ c_3 = 0 \end{matrix}$$

$$\text{Overflow} = c_3 \bar{c}_4 + \bar{c}_3 c_4$$

XOR


Calculating overflow for 4-bit numbers with only three significant bits

$$\begin{aligned}\text{Overflow} &= c_3 \bar{c}_4 + \bar{c}_3 c_4 \\ &= c_3 \oplus c_4\end{aligned}$$


Calculating overflow for n-bit numbers with only n-1 significant bits

$$\text{Overflow} = c_{n-1} \oplus c_n$$


Detecting Overflow

 

Detecting Overflow (with one extra XOR)

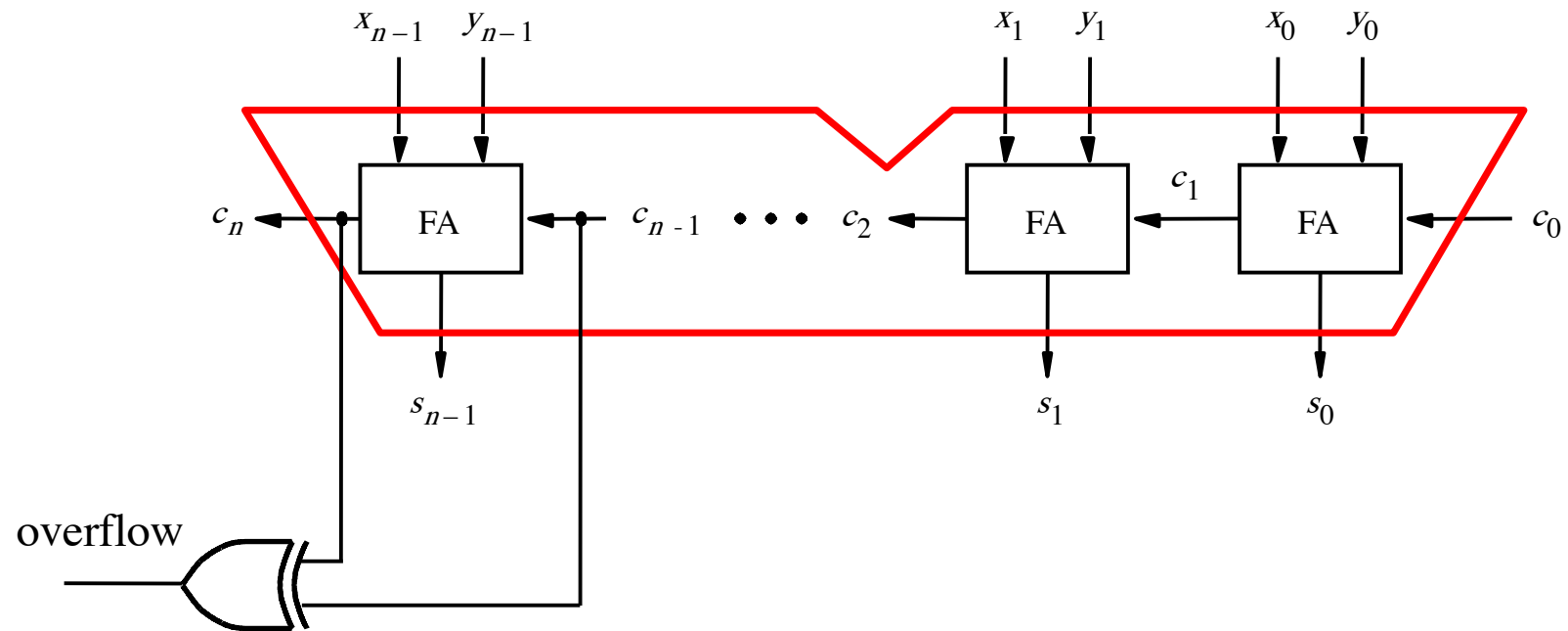

Detecting Overflow (with one extra XOR)

 


This method detects overflow
for both addition and subtraction.

Detecting Overflow

(alternative method)

Used if you don't have access to the internal carries of the adder.

Detecting Overflow (with one extra XOR)

 

If the adder is implemented on a chip,
then this line is not available.
So the first method can't be used.

Another way to look at the overflow issue

$$\begin{array}{rcccccl} & + & X = & x_3 & x_2 & x_1 & x_0 \\ & & Y = & y_3 & y_2 & y_1 & y_0 \\ \hline & & S = & s_3 & s_2 & s_1 & s_0 \end{array}$$

Another way to look at the overflow issue

$$\begin{array}{rcccc} + & X = & x_3 & x_2 & x_1 & x_0 \\ & Y = & y_3 & y_2 & y_1 & y_0 \\ \hline & S = & s_3 & s_2 & s_1 & s_0 \end{array}$$

If both numbers that we are adding have the same sign but the sum does not, then we have an overflow.

Examples of determination of overflow

$$\begin{array}{rcl}
 (+7) & & 0111 \\
 + (+2) & + & 0010 \\
 \hline
 (+9) & & 1001
 \end{array}$$

$$\begin{array}{rcl}
 (-7) & & 1001 \\
 + (+2) & + & 0010 \\
 \hline
 (-5) & & 1011
 \end{array}$$

$$\begin{array}{rcl}
 (+7) & & 0111 \\
 + (-2) & + & 1110 \\
 \hline
 (+5) & & 10101
 \end{array}$$

$$\begin{array}{rcl}
 (-7) & & 1001 \\
 + (-2) & + & 1110 \\
 \hline
 (-9) & & 10111
 \end{array}$$

Examples of determination of overflow

$$\begin{array}{r}
 (+7) \\
 + (+2) \\
 \hline
 (+9)
 \end{array}
 +
 \begin{array}{r}
 \boxed{0}111 \\
 0010 \\
 \hline
 \boxed{1}001
 \end{array}$$

$$\begin{array}{r}
 (-7) \\
 + (+2) \\
 \hline
 (-5)
 \end{array}
 +
 \begin{array}{r}
 \boxed{1}001 \\
 0010 \\
 \hline
 \boxed{1}011
 \end{array}$$

$$\begin{array}{r}
 (+7) \\
 + (-2) \\
 \hline
 (+5)
 \end{array}
 +
 \begin{array}{r}
 \boxed{0}111 \\
 1110 \\
 \hline
 1\boxed{0}101
 \end{array}$$

$$\begin{array}{r}
 (-7) \\
 + (-2) \\
 \hline
 (-9)
 \end{array}
 +
 \begin{array}{r}
 \boxed{1}001 \\
 1110 \\
 \hline
 1\boxed{0}111
 \end{array}$$

Examples of determination of overflow

$$x_3 = 0$$

$$y_3 = 0$$

$$s_3 = 1$$

$$\begin{array}{r} (+7) \\ + (+2) \\ \hline (+9) \end{array} \quad + \quad \begin{array}{r} \boxed{0}111 \\ 0010 \\ \hline \boxed{1}001 \end{array}$$

$$\begin{array}{r} (-7) \\ + (+2) \\ \hline (-5) \end{array} \quad + \quad \begin{array}{r} \boxed{1}001 \\ 0010 \\ \hline \boxed{1}011 \end{array}$$

$$x_3 = 1$$

$$y_3 = 0$$

$$s_3 = 1$$

$$x_3 = 0$$

$$y_3 = 1$$

$$s_3 = 0$$

$$\begin{array}{r} (+7) \\ + (-2) \\ \hline (+5) \end{array} \quad + \quad \begin{array}{r} \boxed{0}111 \\ 1110 \\ \hline 1\boxed{0}101 \end{array}$$

$$\begin{array}{r} (-7) \\ + (-2) \\ \hline (-9) \end{array} \quad + \quad \begin{array}{r} \boxed{1}001 \\ 1110 \\ \hline 1\boxed{0}111 \end{array}$$

$$x_3 = 1$$

$$y_3 = 1$$

$$s_3 = 0$$

Examples of determination of overflow

$$x_3 = 0$$

$$y_3 = 0$$

$$s_3 = 1$$

$$\begin{array}{r} (+7) \\ + (+2) \\ \hline (+9) \end{array} + \begin{array}{|c|c|c|c|} \hline 0 & 1 & 1 & 1 \\ \hline 0 & 0 & 1 & 0 \\ \hline 1 & 0 & 0 & 1 \\ \hline \end{array}$$

$$\begin{array}{r} (-7) \\ + (+2) \\ \hline (-5) \end{array} + \begin{array}{|c|c|c|c|} \hline 1 & 0 & 0 & 1 \\ \hline 0 & 0 & 1 & 0 \\ \hline 1 & 0 & 1 & 1 \\ \hline \end{array}$$

$$x_3 = 1$$

$$y_3 = 0$$

$$s_3 = 1$$

$$x_3 = 0$$

$$y_3 = 1$$

$$s_3 = 0$$

$$\begin{array}{r} (+7) \\ + (-2) \\ \hline (+5) \end{array} + \begin{array}{|c|c|c|c|} \hline 0 & 1 & 1 & 1 \\ \hline 1 & 1 & 1 & 0 \\ \hline 1 & 0 & 1 & 0 & 1 \\ \hline \end{array}$$

$$\begin{array}{r} (-7) \\ + (-2) \\ \hline (-9) \end{array} + \begin{array}{|c|c|c|c|} \hline 1 & 0 & 0 & 1 \\ \hline 1 & 1 & 1 & 0 \\ \hline 1 & 0 & 1 & 1 & 1 \\ \hline \end{array}$$

$$x_3 = 1$$

$$y_3 = 1$$

$$s_3 = 0$$

In 2's complement, both +9 and -9 are not representable with 4 bits.

Examples of determination of overflow

$$\begin{array}{l} x_3 = 0 \\ y_3 = 0 \\ s_3 = 1 \end{array}$$

$$\begin{array}{r} (+7) \\ + (+2) \\ \hline (+9) \end{array}$$

$$+ \begin{array}{r} 0111 \\ 0010 \\ \hline 1001 \end{array}$$

$$\begin{array}{r} (-7) \\ + (+2) \\ \hline (-5) \end{array}$$

$$+ \begin{array}{r} 1001 \\ 0010 \\ \hline 1011 \end{array}$$

$$\begin{array}{l} x_3 = 1 \\ y_3 = 0 \\ s_3 = 1 \end{array}$$

$$\begin{array}{l} x_3 = 0 \\ y_3 = 1 \\ s_3 = 0 \end{array}$$

$$\begin{array}{r} (+7) \\ + (-2) \\ \hline (+5) \end{array}$$

$$+ \begin{array}{r} 0111 \\ 1110 \\ \hline 10101 \end{array}$$

$$\begin{array}{r} (-7) \\ + (-2) \\ \hline (-9) \end{array}$$

$$+ \begin{array}{r} 1001 \\ 1110 \\ \hline 10111 \end{array}$$

$$\begin{array}{l} x_3 = 1 \\ y_3 = 1 \\ s_3 = 0 \end{array}$$

Overflow occurs only in these two cases.

Examples of determination of overflow

$$\begin{array}{l} x_3 = 0 \\ y_3 = 0 \\ s_3 = 1 \end{array}$$

$$\begin{array}{r} (+7) \\ + (+2) \\ \hline (+9) \end{array}$$

$$+ \begin{array}{r} 0111 \\ 0010 \\ \hline 1001 \end{array}$$

$$\begin{array}{r} (-7) \\ + (+2) \\ \hline (-5) \end{array}$$

$$+ \begin{array}{r} 1001 \\ 0010 \\ \hline 1011 \end{array}$$

$$\begin{array}{l} x_3 = 1 \\ y_3 = 0 \\ s_3 = 1 \end{array}$$

$$\begin{array}{l} x_3 = 0 \\ y_3 = 1 \\ s_3 = 0 \end{array}$$

$$\begin{array}{r} (+7) \\ + (-2) \\ \hline (+5) \end{array}$$

$$+ \begin{array}{r} 0111 \\ 1110 \\ \hline 10101 \end{array}$$

$$\begin{array}{r} (-7) \\ + (-2) \\ \hline (-9) \end{array}$$

$$+ \begin{array}{r} 1001 \\ 1110 \\ \hline 10111 \end{array}$$

$$\begin{array}{l} x_3 = 1 \\ y_3 = 1 \\ s_3 = 0 \end{array}$$

$$\text{Overflow} = \overline{x}_3 \overline{y}_3 s_3 + x_3 y_3 \overline{s}_3$$


Another way to look at the overflow issue

$$\begin{array}{rcccc} + & X = & x_3 & x_2 & x_1 & x_0 \\ & Y = & y_3 & y_2 & y_1 & y_0 \\ \hline & S = & s_3 & s_2 & s_1 & s_0 \end{array}$$


If both numbers that we are adding have the same sign but the sum does not, then we have an overflow.

$$\text{Overflow} = \bar{x}_3 \bar{y}_3 s_3 + x_3 y_3 \bar{s}_3$$


Overflow Detection

 


Overflow Detection

 


Overflow Detection

 


Overflow Detection

 

Overflow detection for a 5-bit adder

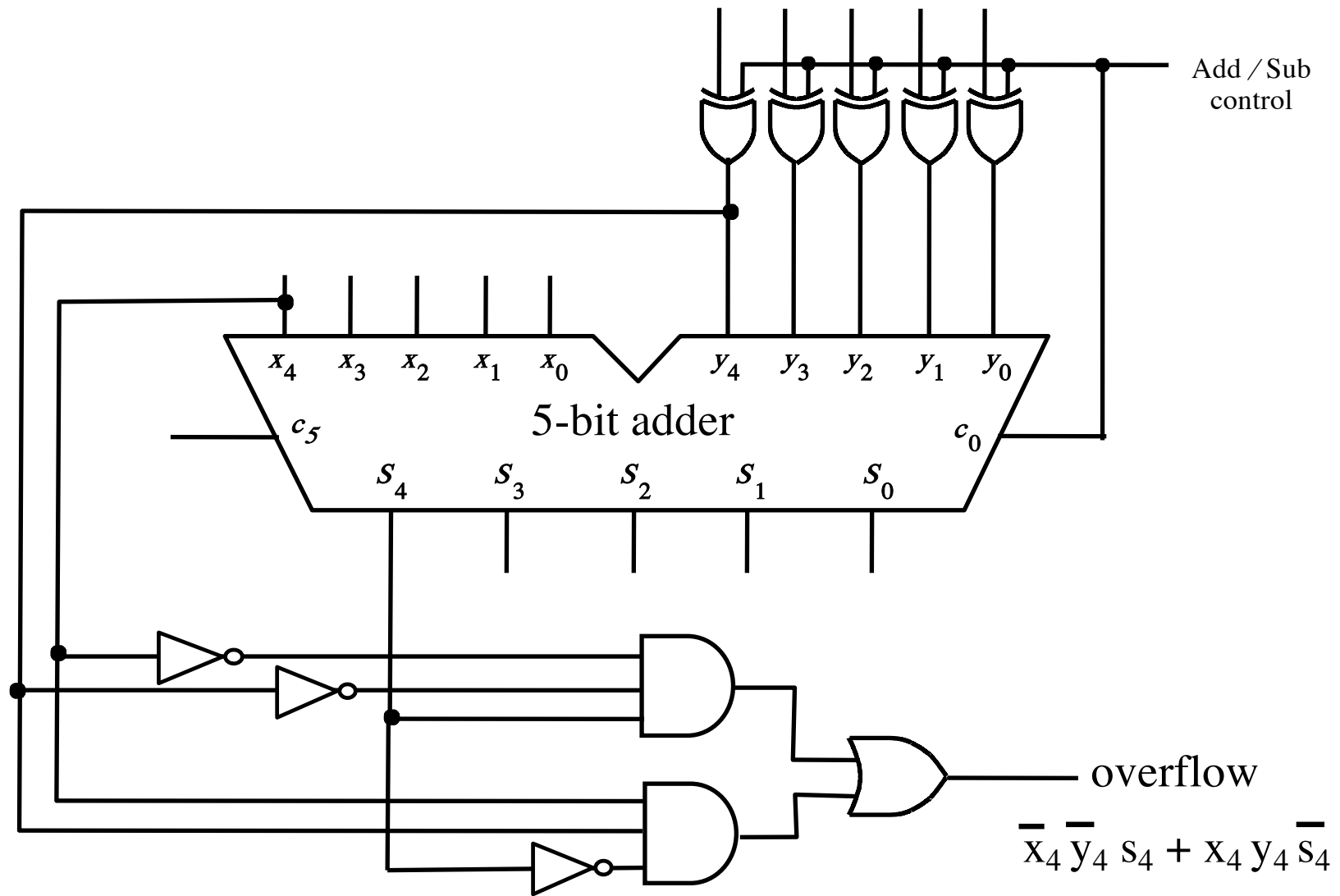

Overflow detection for a 4-bit adder

 


New Topic:


Fast Adders

A ripple-carry adder

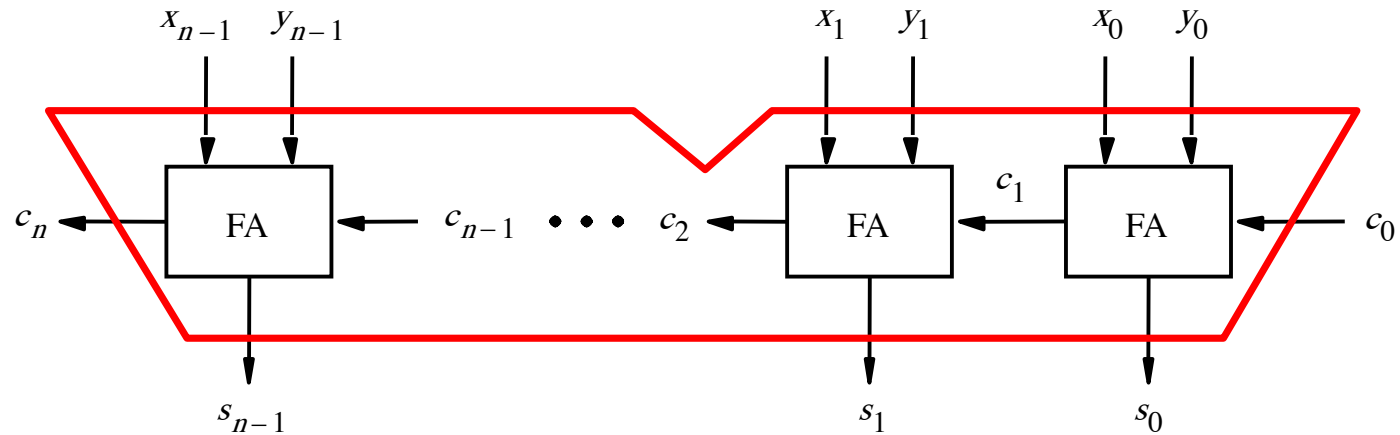
**How long does it take to compute all
sum bits and all carry bits?**



 Delays through the modular implementation of the full-adder circuit




(a) Block diagram

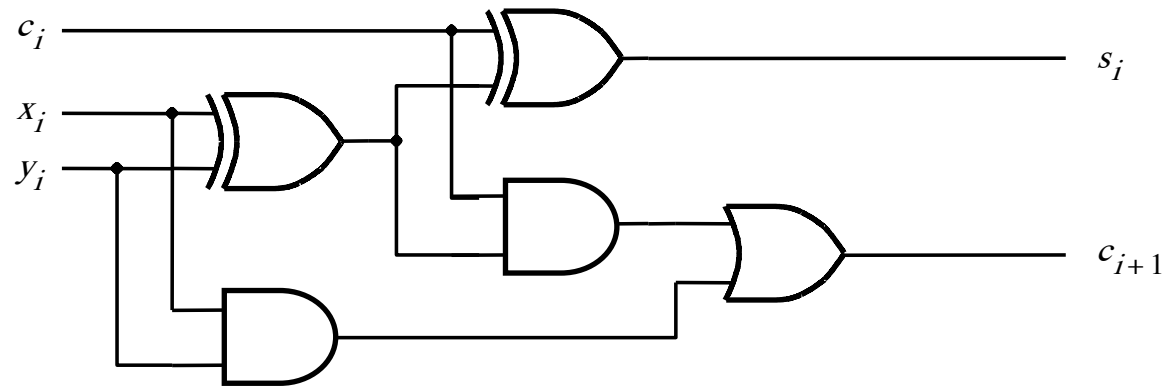

 
(b) Detailed diagram

[Figure 3.4 from the textbook]

Delays through the modular implementation of the full-adder circuit




(a) Block diagram

 

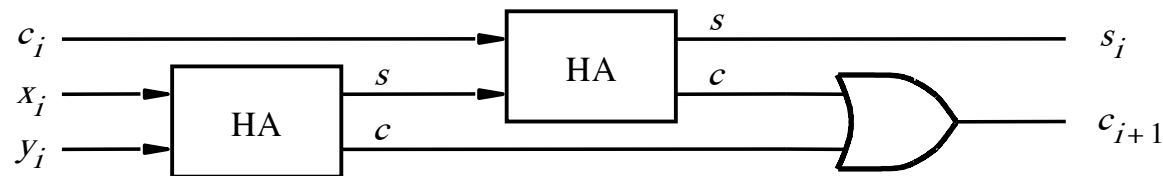
(b) Detailed diagram

[Figure 3.4 from the textbook]

Delays through the modular implementation of the full-adder circuit




(a) Block diagram

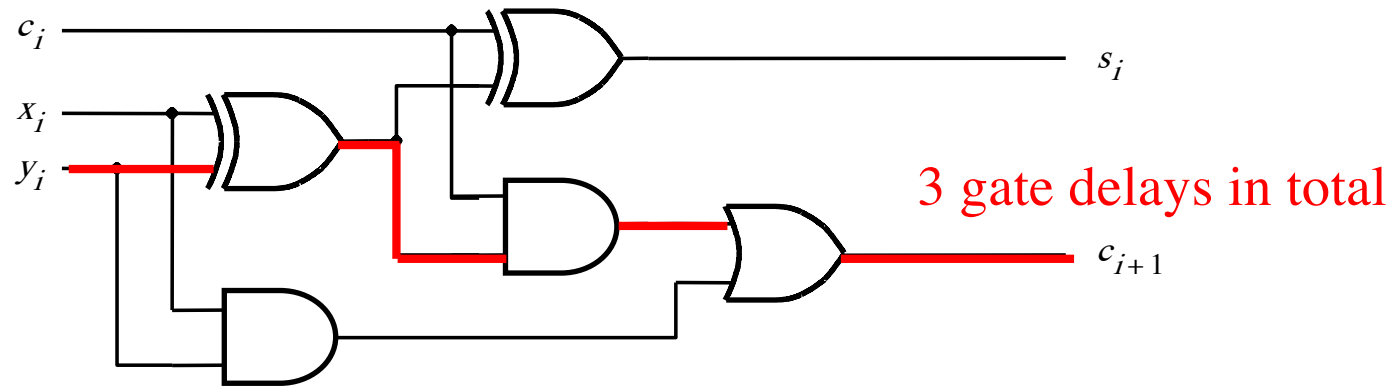

 (b) Detailed diagram


[Figure 3.4 from the textbook]

How long does it take to compute all sum bits and all carry bits in this case?




It takes $3n$ gate delays?

Delays through the Full-Adder circuit

 


[Figure 3.3c from the textbook]

Delays through the Full-Adder circuit

 


[Figure 3.3c from the textbook]

Delays through the Full-Adder circuit

 

[Figure 3.3c from the textbook]

 How long does it take to compute all sum bits and all carry bits?



It takes $2n$ gate delays?

Can we perform addition even faster?


The goal is to evaluate very fast if the carry from the previous stage will be equal to 0 or 1.

Can we perform addition even faster?

The goal is to evaluate very fast if the carry from the previous stage will be equal to 0 or 1.


To accomplish this goal we will have to redesign the full-adder circuit yet again.

The Full-Adder Circuit

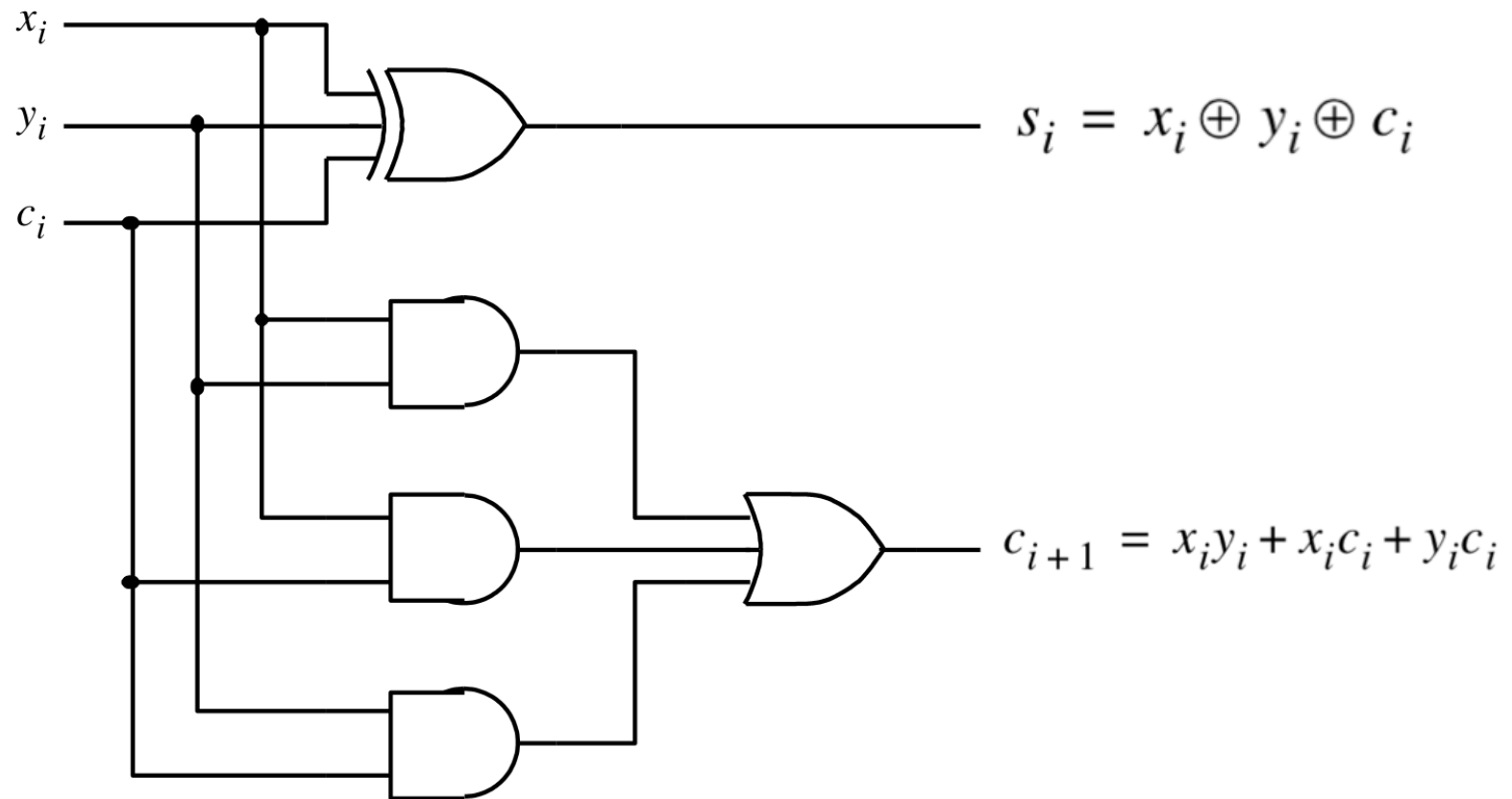

[Figure 3.3c from the textbook]

The Full-Adder Circuit

 

Decomposing the Carry Expression

$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

Decomposing the Carry Expression


$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

$$c_{i+1} = x_i y_i + (x_i + y_i)c_i$$

Decomposing the Carry Expression

$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$


$$c_{i+1} = x_i y_i + (x_i + y_i) c_i$$

 

Another Way to Draw the Full-Adder Circuit


$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

$$c_{i+1} = x_i y_i + (x_i + y_i)c_i$$

 


Another Way to Draw the Full-Adder Circuit

$$c_{i+1} = x_i y_i + (x_i + y_i)c_i$$

 

Another Way to Draw the Full-Adder Circuit
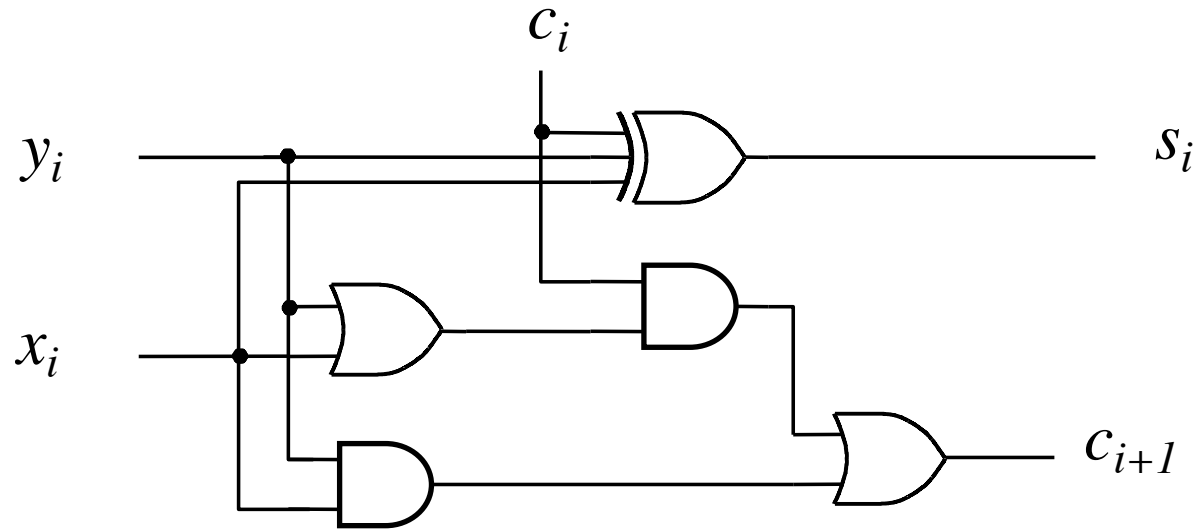
$$c_{i+1} = \underbrace{x_i y_i}_{g_i} + \underbrace{(x_i + y_i)}_{p_i} c_i$$




Another Way to Draw the Full-Adder Circuit


g - generate

p - propagate

 
$$c_{i+1} = \underbrace{x_i y_i}_{g_i} + \underbrace{(x_i + y_i)}_{p_i} c_i$$



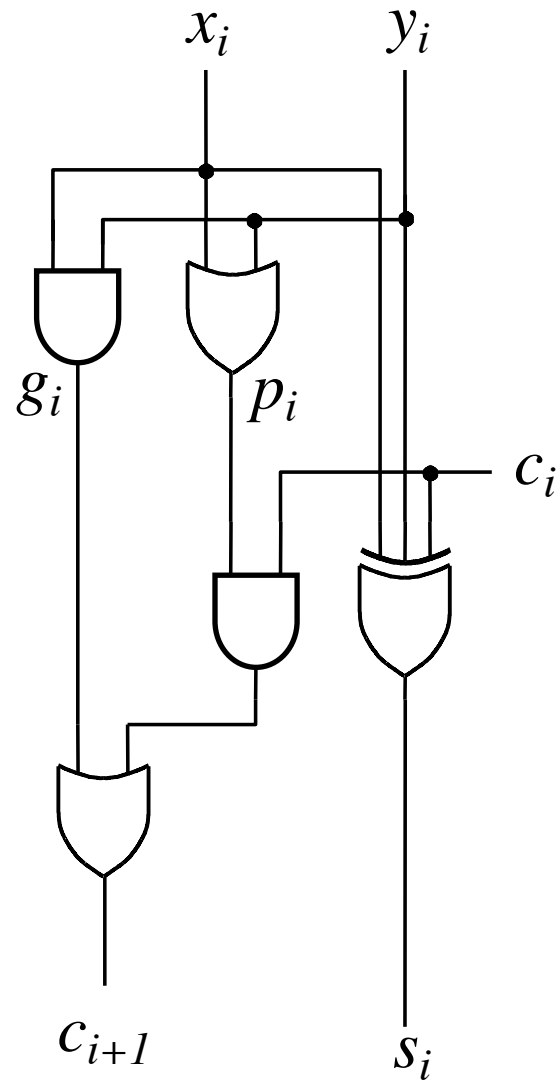Yet Another Way to Draw It (Just Rotate It)




Now we can Build a Ripple-Carry Adder

 


[Figure 3.14 from the textbook]

Now we can Build a Ripple-Carry Adder

 


[Figure 3.14 from the textbook]

 2-bit ripple-carry adder: 5 gate delays (1+2+2)



 n-bit ripple-carry adder: $2n+1$ gate delays



n-bit Ripple-Carry Adder

- **It takes 1 gate delay to generate all g_i and p_i signals**
- **+2 more gate delays to generate carry 1**
- **+2 more gate delay to generate carry 2**
- **...**
- **+2 more gate delay to generate carry n**
- **Thus, the total delay through an n-bit ripple-carry adder is $2n+1$ gate delays!**

n-bit Ripple-Carry Adder

- It takes 1 gate delay to generate all g_i and p_i signals
- +2 more gate delays to generate carry 1
- +2 more gate delay to generate carry 2
- ...
- +2 more gate delay to generate carry n
- Thus, the total delay through an n-bit ripple-carry adder is $2n+1$ gate delays!

This is slower by 1 than the original design?!

A carry-lookahead adder

Decomposing the Carry Expression

$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

Decomposing the Carry Expression

$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

$$c_{i+1} = \underbrace{x_i y_i}_{g_i} + \underbrace{(x_i + y_i)}_{p_i} c_i$$


Decomposing the Carry Expression

$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

$$c_{i+1} = \underbrace{x_i y_i}_{g_i} + \underbrace{(x_i + y_i)}_{p_i} c_i$$


(1 gate delay) (1 gate delay)

It takes 1 gate delay to compute all p_i signals

 

[Figure 3.14 from the textbook]

It takes 1 gate delay to compute all g_i signals

 

[Figure 3.14 from the textbook]

Decomposing the Carry Expression

$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

$$c_{i+1} = \underbrace{x_i y_i}_{g_i} + \underbrace{(x_i + y_i)}_{p_i} c_i$$

Decomposing the Carry Expression

$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

$$c_{i+1} = \underbrace{x_i y_i}_{g_i} + \underbrace{(x_i + y_i)}_{p_i} c_i$$

$$c_{i+1} = g_i + p_i c_i$$

Decomposing the Carry Expression

$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

$$c_{i+1} = \underbrace{x_i y_i}_{g_i} + \underbrace{(x_i + y_i)}_{p_i} c_i$$

$$c_{i+1} = g_i + p_i c_i$$

recursive
expansion of
 c_i

$$c_{i+1} = g_i + p_i (g_{i-1} + p_{i-1} c_{i-1})$$

Decomposing the Carry Expression

$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

$$c_{i+1} = \underbrace{x_i y_i}_{g_i} + \underbrace{(x_i + y_i)}_{p_i} c_i$$

$$c_{i+1} = g_i + p_i c_i$$

$$c_{i+1} = g_i + p_i (g_{i-1} + p_{i-1} c_{i-1})$$

$$c_{i+1} = g_i + p_i g_{i-1} + p_i p_{i-1} c_{i-1}$$

Expanding the Carry Expression for C_3

$$c_{i+1} = g_i + p_i c_i$$

$$c_3 = g_2 + p_2 c_2$$

$$= g_2 + p_2 (g_1 + p_1 c_1)$$

$$= g_2 + p_2 g_1 + p_2 p_1 c_1$$

$$= g_2 + p_2 g_1 + p_2 p_1 (g_0 + p_0 c_0)$$

$$= g_2 + p_2 g_1 + p_2 p_1 g_0 + p_2 p_1 p_0 c_0$$


Carry for the first three stages

$$c_1 = g_0 + p_0 c_0$$

$$c_2 = g_1 + p_1 g_0 + p_1 p_0 c_0$$


$$c_3 = g_2 + p_2 g_1 + p_2 p_1 g_0 + p_2 p_1 p_0 c_0$$

Now we can Build a **Carry-Lookahead** Adder

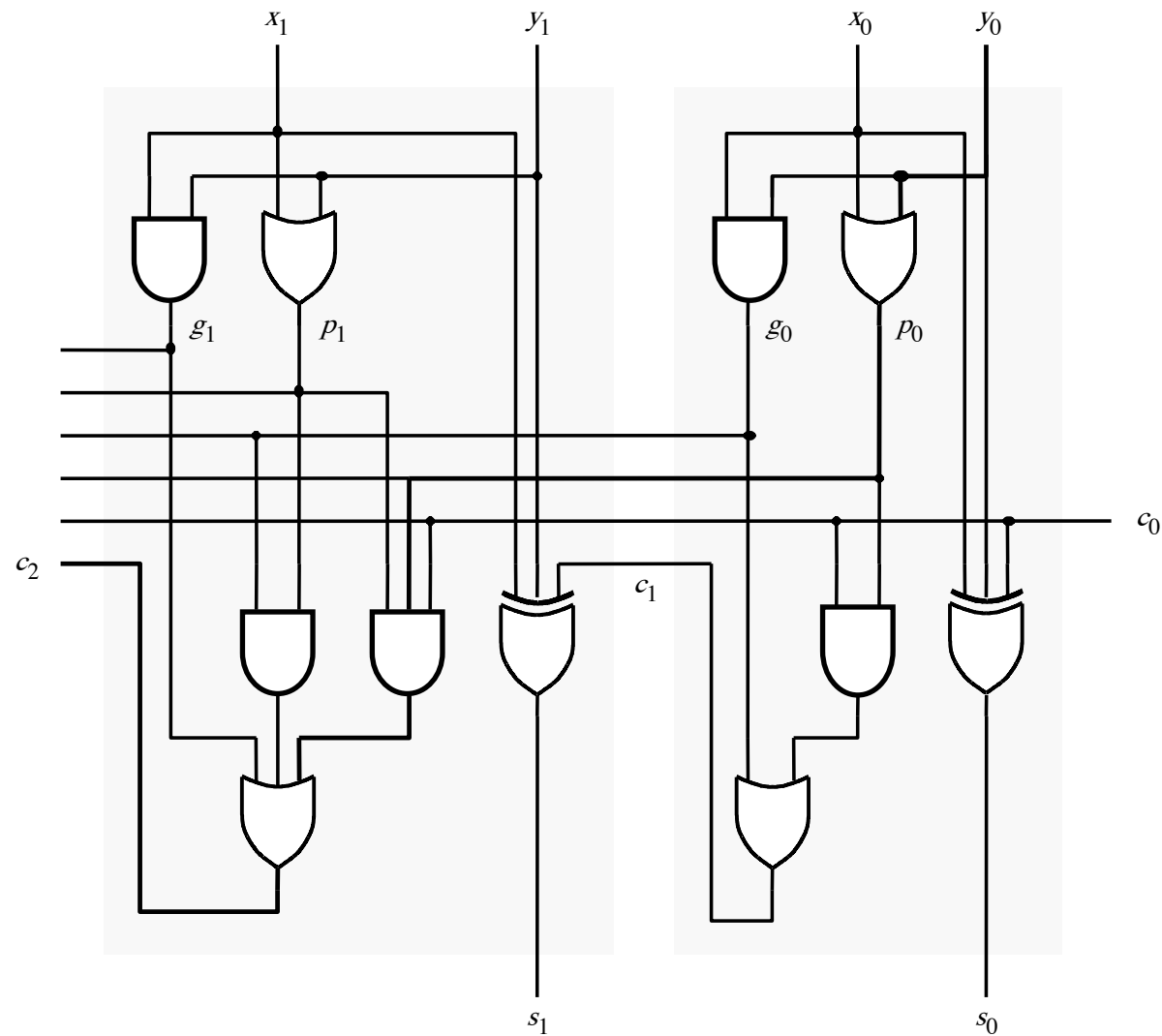

[Figure 3.15 from the textbook]

The first two stages of a carry-lookahead adder

 


[Figure 3.15 from the textbook]

Carry for the first stage

$$c_1 = g_0 + p_0 c_0$$


Carry for the first stage

 

Carry for the second stage

$$c_2 = g_1 + p_1g_0 + p_1p_0c_0$$

Carry for the second stage

 

Carry for the first two stages

$$c_1 = g_0 + p_0 c_0$$

$$c_2 = g_1 + p_1 g_0 + p_1 p_0 c_0$$

Carry for the first two stages

$$c_1 = g_0 + p_0 c_0$$

$$c_2 = g_1 + \underline{p_1} g_0 + \underline{p_1 p_0} c_0$$

Carry for the first two stages

$$c_1 = g_0 + p_0 c_0$$

$$c_2 = g_1 + \underline{p_1} g_0 + \underline{p_1 p_0} c_0$$

$$= g_1 + p_1 \underbrace{(g_0 + p_0 c_0)}_{c_1}$$

Carry for the first two stages


$$c_1 = g_0 + p_0 c_0$$

$$c_2 = g_1 + p_1 g_0 + p_1 p_0 c_0$$

$$= g_1 + p_1 \underbrace{(g_0 + p_0 c_0)}_{c_1}$$


$$= g_1 + p_1 c_1$$

The first two stages of a carry-lookahead adder

 


[Figure 3.15 from the textbook]


It takes 3 gate delays to generate c_1

 


It takes 3 gate delays to generate c_2

 

 
The first two stages of a carry-lookahead adder



It takes 4 gate delays to generate s_1

 

It takes 4 gate delays to generate s_2

 

N-bit Carry-Lookahead Adder

- **It takes 1 gate delay to generate all g_i and p_i signals**
- **It takes 2 more gate delays to generate all carry signals**
- **It takes 1 more gate delay to generate all sum bits**
- **Thus, the total delay through an
n-bit carry-lookahead adder is only 4 gate delays!**

N-bit Carry-Lookahead Adder

- It takes 1 gate delay to generate all g_i and p_i signals
- It takes 2 more gate delays to generate all carry signals
- It takes 1 more gate delay to generate all sum bits
- Thus, the total delay through an n-bit carry-lookahead adder is **only 4 gate delays!**

Expanding the Carry Expression

$$c_{i+1} = g_i + p_i c_i$$

$$c_1 = g_0 + p_0 c_0$$

$$c_2 = g_1 + p_1 g_0 + p_1 p_0 c_0$$

$$c_3 = g_2 + p_2 g_1 + p_2 p_1 g_0 + p_2 p_1 p_0 c_0$$

...

$$\begin{aligned} c_8 = & g_7 + p_7 g_6 + p_7 p_6 g_5 + p_7 p_6 p_5 g_4 \\ & + p_7 p_6 p_5 p_4 g_3 + p_7 p_6 p_5 p_4 p_3 g_2 \\ & + p_7 p_6 p_5 p_4 p_3 p_2 g_1 + p_7 p_6 p_5 p_4 p_3 p_2 p_1 g_0 \\ & + p_7 p_6 p_5 p_4 p_3 p_2 p_1 p_0 c_0 \end{aligned}$$

Expanding the Carry Expression


$$c_{i+1} = g_i + p_i c_i$$

$$c_1 = g_0 + p_0 c_0$$

$$c_2 = g_1 + p_1 g_0 + p_1 p_0 c_0$$

$$c_3 = g_2 + p_2 g_1 + p_2 p_1 g_0 + p_2 p_1 p_0 c_0$$

...

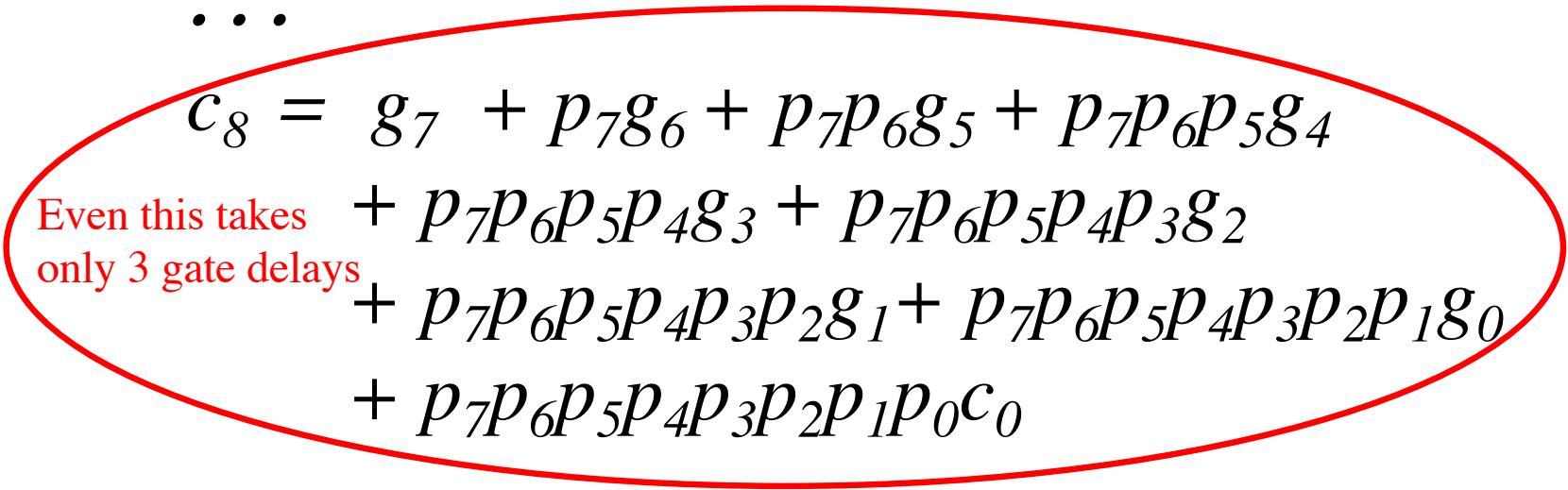


Even this takes only 3 gate delays


$$\begin{aligned} c_8 = & g_7 + p_7 g_6 + p_7 p_6 g_5 + p_7 p_6 p_5 g_4 \\ & + p_7 p_6 p_5 p_4 g_3 + p_7 p_6 p_5 p_4 p_3 g_2 \\ & + p_7 p_6 p_5 p_4 p_3 p_2 g_1 + p_7 p_6 p_5 p_4 p_3 p_2 p_1 g_0 \\ & + p_7 p_6 p_5 p_4 p_3 p_2 p_1 p_0 c_0 \end{aligned}$$

**A hierarchical carry-lookahead adder
with ripple-carry between blocks**

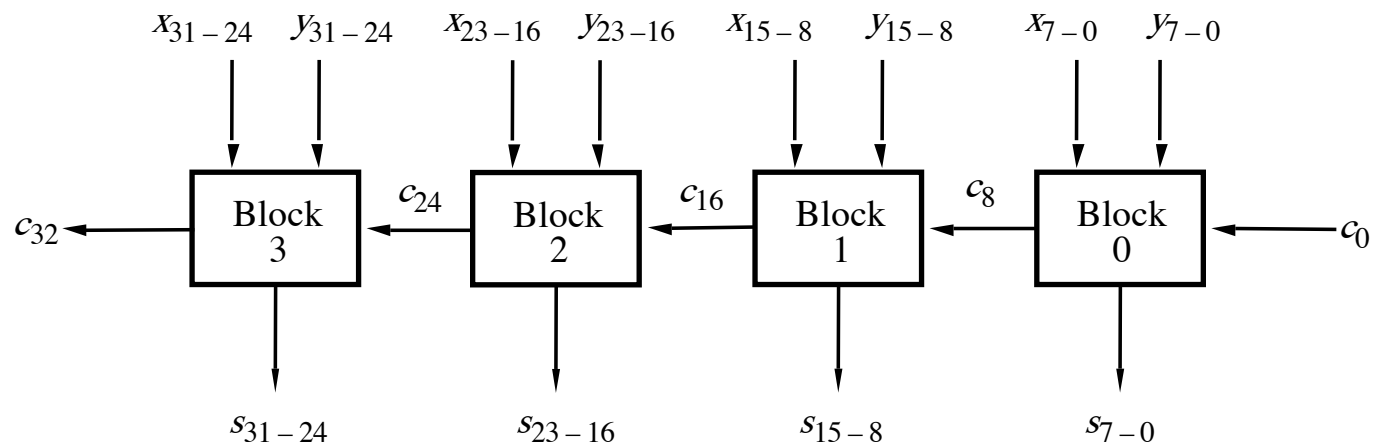
A hierarchical carry-lookahead adder with ripple-carry between blocks



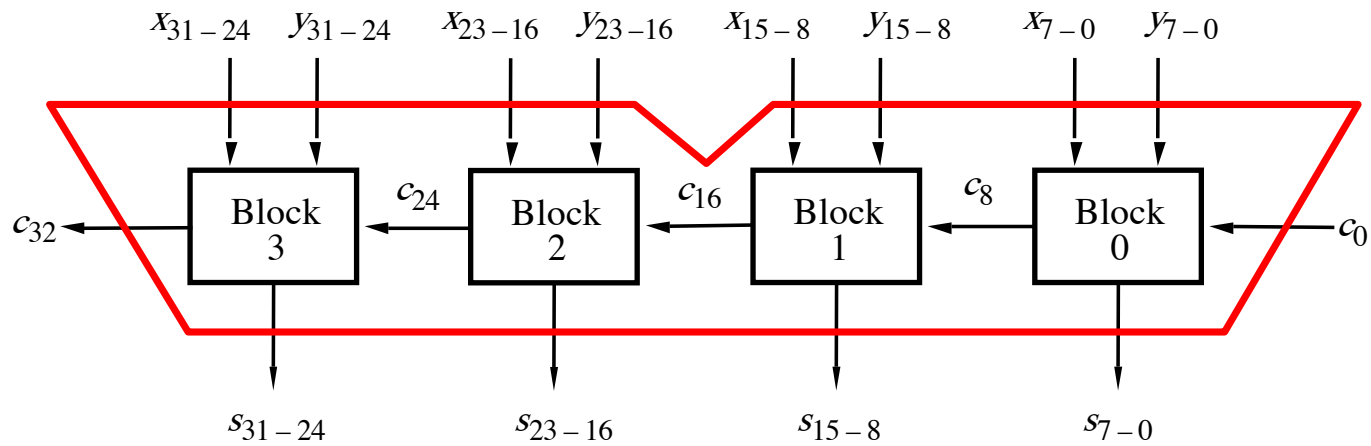A hierarchical carry-lookahead adder with ripple-carry between blocks




 A hierarchical carry-lookahead adder with ripple-carry between blocks




A hierarchical carry-lookahead adder

A hierarchical carry-lookahead adder with ripple-carry between blocks

 


[Figure 3.16 from the textbook]

A hierarchical carry-lookahead adder

 


[Figure 3.17 from the textbook]


A hierarchical carry-lookahead adder

 

A hierarchical carry-lookahead adder

 

A hierarchical carry-lookahead adder

 

The Hierarchical Carry Expression

$$\begin{aligned} c_8 = & g_7 + p_7 g_6 + p_7 p_6 g_5 + p_7 p_6 p_5 g_4 \\ & + p_7 p_6 p_5 p_4 g_3 + p_7 p_6 p_5 p_4 p_3 g_2 \\ & + p_7 p_6 p_5 p_4 p_3 p_2 g_1 + p_7 p_6 p_5 p_4 p_3 p_2 p_1 g_0 \\ & + p_7 p_6 p_5 p_4 p_3 p_2 p_1 p_0 c_0 \end{aligned}$$

The Hierarchical Carry Expression

$$\begin{aligned} c_8 = & g_7 + p_7g_6 + p_7p_6g_5 + p_7p_6p_5g_4 \\ & + p_7p_6p_5p_4g_3 + p_7p_6p_5p_4p_3g_2 \\ & + p_7p_6p_5p_4p_3p_2g_1 + p_7p_6p_5p_4p_3p_2p_1g_0 \\ & + p_7p_6p_5p_4p_3p_2p_1p_0c_0 \end{aligned}$$

The Hierarchical Carry Expression

$$\begin{aligned} c_8 = & g_7 + p_7 g_6 + p_7 p_6 g_5 + p_7 p_6 p_5 g_4 \\ & + p_7 p_6 p_5 p_4 g_3 + p_7 p_6 p_5 p_4 p_3 g_2 \\ & + p_7 p_6 p_5 p_4 p_3 p_2 g_1 + p_7 p_6 p_5 p_4 p_3 p_2 p_1 g_0 \\ & + p_7 p_6 p_5 p_4 p_3 p_2 p_1 p_0 c_0 \end{aligned}$$

G_0 points to the first four terms of the expression.

P_0 points to the final term of the expression, $p_7 p_6 p_5 p_4 p_3 p_2 p_1 p_0 c_0$.

The Hierarchical Carry Expression

$$\begin{aligned} c_8 = & g_7 + p_7 g_6 + p_7 p_6 g_5 + p_7 p_6 p_5 g_4 \\ & + p_7 p_6 p_5 p_4 g_3 + p_7 p_6 p_5 p_4 p_3 g_2 \\ & + p_7 p_6 p_5 p_4 p_3 p_2 g_1 + p_7 p_6 p_5 p_4 p_3 p_2 p_1 g_0 \\ & + p_7 p_6 p_5 p_4 p_3 p_2 p_1 p_0 c_0 \end{aligned}$$

G_0 points to the first four terms of the expression.

P_0 points to the product term $p_7 p_6 p_5 p_4 p_3 p_2 p_1 p_0$.

$$c_8 = G_0 + P_0 c_0$$

The Hierarchical Carry Expression

3-gate delays

$$\begin{aligned}
 c_8 = & g_7 + p_7 g_6 + p_7 p_6 g_5 + p_7 p_6 p_5 g_4 \\
 & + p_7 p_6 p_5 p_4 g_3 + p_7 p_6 p_5 p_4 p_3 g_2 \\
 & + p_7 p_6 p_5 p_4 p_3 p_2 g_1 + p_7 p_6 p_5 p_4 p_3 p_2 p_1 g_0 \\
 & + \boxed{p_7 p_6 p_5 p_4 p_3 p_2 p_1 p_0} c_0
 \end{aligned}$$

G_0 points to the first four terms of the expansion.

P_0 points to the product term $p_7 p_6 p_5 p_4 p_3 p_2 p_1 p_0$.

2-gate delays

$$c_8 = G_0 + P_0 c_0$$

The Hierarchical Carry Expression

3-gate delays

$$c_8 = g_7 + p_7g_6 + p_7p_6g_5 + p_7p_6p_5g_4 + p_7p_6p_5p_4g_3 + p_7p_6p_5p_4p_3g_2 + p_7p_6p_5p_4p_3p_2g_1 + p_7p_6p_5p_4p_3p_2p_1g_0 + p_7p_6p_5p_4p_3p_2p_1p_0c_0$$

G_0 points to the first seven terms of the expression.

P_0 points to the last term of the expression, $p_7p_6p_5p_4p_3p_2p_1p_0c_0$.

2-gate delays

$$c_8 = \underbrace{G_0}_{\substack{\text{3-gate} \\ \text{delays}}} + \underbrace{P_0}_{\substack{\text{2-gate} \\ \text{delays}}} c_0$$

The Hierarchical Carry Expression

3-gate delays

$$c_8 = g_7 + p_7g_6 + p_7p_6g_5 + p_7p_6p_5g_4 + p_7p_6p_5p_4g_3 + p_7p_6p_5p_4p_3g_2 + p_7p_6p_5p_4p_3p_2g_1 + p_7p_6p_5p_4p_3p_2p_1g_0 + p_7p_6p_5p_4p_3p_2p_1p_0c_0$$

G_0 points to the first seven terms of the expression.

P_0 points to the last term $p_7p_6p_5p_4p_3p_2p_1p_0c_0$, which is enclosed in a red box labeled "2-gate delays".

$$c_8 = \underbrace{G_0}_{\text{3-gate delays}} + \underbrace{P_0 c_0}_{\text{3-gate delays}}$$

The Hierarchical Carry Expression

3-gate delays

$$\begin{aligned}
 c_8 = & g_7 + p_7g_6 + p_7p_6g_5 + p_7p_6p_5g_4 \\
 & + p_7p_6p_5p_4g_3 + p_7p_6p_5p_4p_3g_2 \\
 & + p_7p_6p_5p_4p_3p_2g_1 + p_7p_6p_5p_4p_3p_2p_1g_0 \\
 & + \boxed{p_7p_6p_5p_4p_3p_2p_1p_0}c_0
 \end{aligned}$$

G_0 points to the first four terms of the expression.

P_0 points to the term $p_7p_6p_5p_4p_3p_2p_1p_0$.

2-gate delays

$$c_8 = G_0 + P_0 c_0$$

4-gate delays

The Hierarchical Carry Expression

$$\begin{aligned}c_8 = & g_7 + p_7g_6 + p_7p_6g_5 + p_7p_6p_5g_4 \\& + p_7p_6p_5p_4g_3 + p_7p_6p_5p_4p_3g_2 \\& + p_7p_6p_5p_4p_3p_2g_1 + p_7p_6p_5p_4p_3p_2p_1g_0 \\& + p_7p_6p_5p_4p_3p_2p_1p_0c_0\end{aligned}$$

$$\begin{aligned}c_{16} = & g_{15} + p_{15}g_{14} + p_{15}p_{14}g_{13} + p_{15}p_{14}p_{13}g_{12} \\& + p_{15}p_{14}p_{13}p_{12}g_{11} + p_{15}p_{14}p_{13}p_{12}p_{11}g_{10} \\& + p_{15}p_{14}p_{13}p_{12}p_{11}p_{10}g_9 + p_{15}p_{14}p_{13}p_{12}p_{11}p_{10}p_9g_8 \\& + p_{15}p_{14}p_{13}p_{12}p_{11}p_{10}p_9p_8c_8\end{aligned}$$

The Hierarchical Carry Expression

$$\begin{aligned}c_8 = & g_7 + p_7g_6 + p_7p_6g_5 + p_7p_6p_5g_4 \\& + p_7p_6p_5p_4g_3 + p_7p_6p_5p_4p_3g_2 \\& + p_7p_6p_5p_4p_3p_2g_1 + p_7p_6p_5p_4p_3p_2p_1g_0 \\& + p_7p_6p_5p_4p_3p_2p_1p_0c_0\end{aligned}$$

The same expression, just add 8 to all subscripts

$$\begin{aligned}c_{16} = & g_{15} + p_{15}g_{14} + p_{15}p_{14}g_{13} + p_{15}p_{14}p_{13}g_{12} \\& + p_{15}p_{14}p_{13}p_{12}g_{11} + p_{15}p_{14}p_{13}p_{12}p_{11}g_{10} \\& + p_{15}p_{14}p_{13}p_{12}p_{11}p_{10}g_9 + p_{15}p_{14}p_{13}p_{12}p_{11}p_{10}p_9g_8 \\& + p_{15}p_{14}p_{13}p_{12}p_{11}p_{10}p_9p_8c_8\end{aligned}$$

The Hierarchical Carry Expression

3-gate delays

$$c_8 = g_7 + p_7g_6 + p_7p_6g_5 + p_7p_6p_5g_4$$

$$+ p_7p_6p_5p_4g_3 + p_7p_6p_5p_4p_3g_2$$

$$+ p_7p_6p_5p_4p_3p_2g_1 + p_7p_6p_5p_4p_3p_2p_1g_0$$

$$+ p_7p_6p_5p_4p_3p_2p_1p_0c_0$$

G_0 points to the first four terms of the expression for c_8 .

P_0 points to the term $p_7p_6p_5p_4p_3p_2p_1p_0c_0$.

2-gate delays

$$c_{16} = g_{15} + p_{15}g_{14} + p_{15}p_{14}g_{13} + p_{15}p_{14}p_{13}g_{12}$$

$$+ p_{15}p_{14}p_{13}p_{12}g_{11} + p_{15}p_{14}p_{13}p_{12}p_{11}g_{10}$$

$$+ p_{15}p_{14}p_{13}p_{12}p_{11}p_{10}g_9 + p_{15}p_{14}p_{13}p_{12}p_{11}p_{10}p_9g_8$$

$$+ p_{15}p_{14}p_{13}p_{12}p_{11}p_{10}p_9p_8c_8$$

The Hierarchical Carry Expression

$$\begin{aligned}
 c_8 = & g_7 + p_7g_6 + p_7p_6g_5 + p_7p_6p_5g_4 \\
 & + p_7p_6p_5p_4g_3 + p_7p_6p_5p_4p_3g_2 \\
 & + p_7p_6p_5p_4p_3p_2g_1 + p_7p_6p_5p_4p_3p_2p_1g_0 \\
 & + p_7p_6p_5p_4p_3p_2p_1p_0c_0
 \end{aligned}$$

3-gate delays

$$\begin{aligned}
 c_{16} = & g_{15} + p_{15}g_{14} + p_{15}p_{14}g_{13} + p_{15}p_{14}p_{13}g_{12} \\
 & + p_{15}p_{14}p_{13}p_{12}g_{11} + p_{15}p_{14}p_{13}p_{12}p_{11}g_{10} \\
 & + p_{15}p_{14}p_{13}p_{12}p_{11}p_{10}g_9 + p_{15}p_{14}p_{13}p_{12}p_{11}p_{10}p_9g_8 \\
 & + p_{15}p_{14}p_{13}p_{12}p_{11}p_{10}p_9p_8c_8
 \end{aligned}$$

G₁

P₁

2-gate delays

The Hierarchical Carry Expression

$$c_8 = G_0 + P_0 c_0$$

The Hierarchical Carry Expression

$$c_8 = \underbrace{(G_0)}_{\text{3-gate delays}} + P_0 c_0$$

The Hierarchical Carry Expression

$$c_8 = G_0 + \underbrace{P_0}_{\text{2-gate delays}} c_0$$

The Hierarchical Carry Expression

$$c_8 = G_0 + \underbrace{P_0 c_0}_{\text{3-gate delays}}$$

The Hierarchical Carry Expression

$$c_8 = \underbrace{G_0 + P_0 c_0}_{\text{4-gate delays}}$$

The Hierarchical Carry Expression

$$c_8 = G_0 + P_0 c_0$$

$$\begin{aligned} c_{16} &= G_1 + P_1 c_8 \\ &= G_1 + P_1 G_0 + P_1 P_0 c_0 \end{aligned}$$

The Hierarchical Carry Expression

$$c_8 = \underbrace{G_0}_{\text{3-gate delays}} + P_0 c_0$$

$$\begin{aligned} c_{16} &= G_1 + P_1 c_8 \\ &= G_1 + P_1 \underbrace{G_0}_{\text{3-gate delays}} + P_1 P_0 c_0 \end{aligned}$$

The Hierarchical Carry Expression

$$c_8 = \textcircled{G_0} + P_0 c_0$$

3-gate delays

$$\begin{aligned} c_{16} &= G_1 + P_1 c_8 \\ &= \textcircled{G_1} + P_1 G_0 + P_1 P_0 c_0 \end{aligned}$$

3-gate delays

The Hierarchical Carry Expression

$$c_8 = G_0 + P_0 c_0$$

$$\begin{aligned} c_{16} &= G_1 + P_1 c_8 \\ &= G_1 + P_1 \underbrace{G_0}_{\text{3-gate delays}} + P_1 P_0 c_0 \end{aligned}$$

The Hierarchical Carry Expression

$$c_8 = G_0 + P_0 c_0$$

$$\begin{aligned} c_{16} &= G_1 + P_1 c_8 \\ &= G_1 + \underbrace{P_1}_{\text{2-gate delays}} G_0 + P_1 P_0 c_0 \end{aligned}$$

The Hierarchical Carry Expression

$$c_8 = G_0 + P_0 c_0$$

$$\begin{aligned} c_{16} &= G_1 + P_1 c_8 \\ &= G_1 + \underbrace{P_1 G_0}_{\text{4-gate delays}} + P_1 P_0 c_0 \end{aligned}$$

The Hierarchical Carry Expression

$$c_8 = G_0 + P_0 c_0$$

$$\begin{aligned} c_{16} &= G_1 + P_1 c_8 \\ &= G_1 + P_1 G_0 + \underbrace{P_1}_{\text{2-gate delays}} P_0 c_0 \end{aligned}$$

The Hierarchical Carry Expression

$$c_8 = G_0 + P_0 c_0$$

$$\begin{aligned} c_{16} &= G_1 + P_1 c_8 \\ &= G_1 + P_1 G_0 + P_1 P_0 c_0 \end{aligned}$$

2-gate delays

The Hierarchical Carry Expression

$$c_8 = G_0 + P_0 c_0$$

$$\begin{aligned} c_{16} &= G_1 + P_1 c_8 \\ &= G_1 + P_1 G_0 + \underbrace{P_1 P_0 c_0}_{\text{3-gate delays}} \end{aligned}$$

The Hierarchical Carry Expression

$$c_8 = G_0 + P_0 c_0$$

$$\begin{aligned} c_{16} &= G_1 + P_1 c_8 \\ &= G_1 + P_1 G_0 + P_1 P_0 c_0 \end{aligned}$$

5-gate delays

The Hierarchical Carry Expression

$$c_8 = G_0 + P_0 c_0$$

$$\begin{aligned} c_{16} &= G_1 + P_1 c_8 \\ &= G_1 + P_1 G_0 + P_1 P_0 c_0 \end{aligned}$$

$$c_{24} = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 c_0$$

$$c_{32} = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 c_0$$

The Hierarchical Carry Expression

$$c_8 = G_0 + P_0 c_0$$

4-gate delays

$$\begin{aligned} c_{16} &= G_1 + P_1 c_8 \\ &= G_1 + P_1 G_0 + P_1 P_0 c_0 \end{aligned}$$

5-gate delays


$$c_{24} = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 c_0$$

5-gate delays

$$c_{32} = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 c_0$$


5-gate delays

A hierarchical carry-lookahead adder

 

[Figure 3.17 from the textbook]

A hierarchical carry-lookahead adder

 

[Figure 3.17 from the textbook]


Total Gate Delay Through a Hierarchical Carry-Lookahead Adder

- **The total delay is 8 gates:**
 - **3 to generate all G_i and P_i signals**
 - **+2 to generate c_8 , c_{16} , c_{24} , and c_{32}**
 - **+2 to generate internal carries in the blocks**
 - **+1 to generate the sum bits (one extra XOR)**


Total Gate Delay Through a Hierarchical Carry-Lookahead Adder

- The total delay is 8 gates:
 - 3 to generate all G_i and P_i signals
 - +2 to generate c_8 , c_{16} , c_{24} , and c_{32}
 - +2 to generate internal carries in the blocks
 - +1 to generate the sum bits (one extra XOR)

 2 more gate delays for the internal carries within a block



 2 more gate delays for the internal carries within a block



Hierarchical Carry-Lookahead Adder (Carry Logic)


C8 – 4 gate delays

C16 – 5 gate delays

C24 – 5 Gate delays

C32 – 5 Gate delays

**SECOND
LEVEL
HIERARCHY**

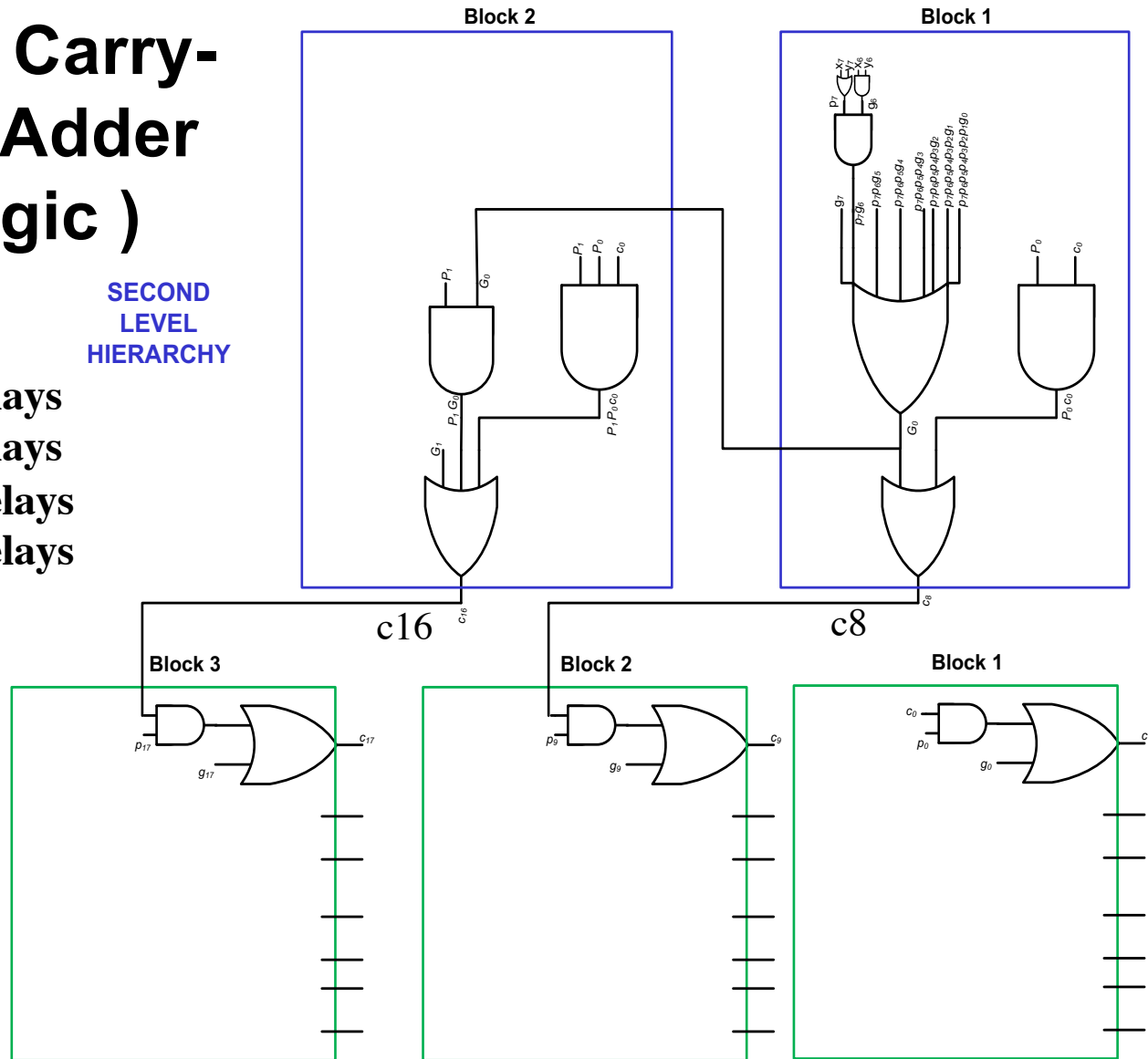

FIRST LEVEL HIERARCHY

Hierarchical Carry-Lookahead Adder (Critical Path)


SECOND
LEVEL
HIERARCHY

C1 - 3 gate delays

C9 - 6 gate delays

C17 - 7 gate delays

C25 - 7 Gate delays

 

Total Gate Delay Through a Hierarchical Carry-Lookahead Adder

- The total delay is **8 gates**:
 - 3 to generate all G_i and P_i signals
 - +2 to generate c_8 , c_{16} , c_{24} , and c_{32}
 - +2 to generate internal carries in the blocks
 - +1 to generate the sum bits (one extra XOR)

Questions?

THE END