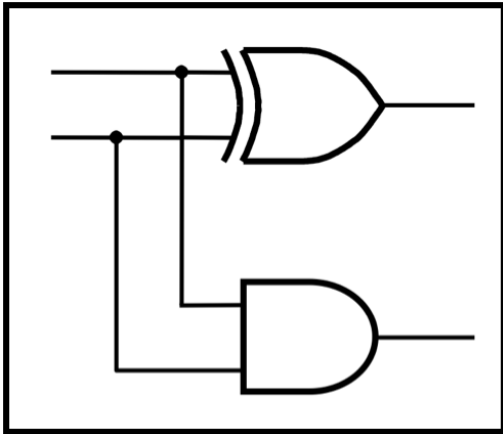




CprE 2810: Digital Logic

Instructor: Alexander Stoytchev

<http://www.ece.iastate.edu/~alexs/classes/>

Multiplexers

CprE 2810: Digital Logic
Iowa State University, Ames, IA
Copyright © Alexander Stoytchev

Administrative Stuff


- **HW 6 is due on Monday Oct 13 @ 10pm**
- **HW 7 is due on Monday Oct 20 @ 10pm**
- **Next week: Lab 6 + TTL2**
- **Midterm progress report grades are due next week**

2-to-1 Multiplexer

2-to-1 Multiplexer (Definition)

- **Has two inputs: x_1 and x_2**
- **Also has another input line s**
- **If $s=0$, then the output is equal to x_1**
- **If $s=1$, then the output is equal to x_2**

Graphical Symbol for a 2-to-1 Multiplexer

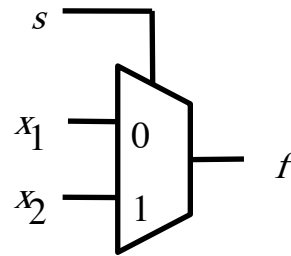


[Figure 2.33c from the textbook]

Analogy: Railroad Switch




http://en.wikipedia.org/wiki/Railroad_switch]

Analogy: Railroad Switch

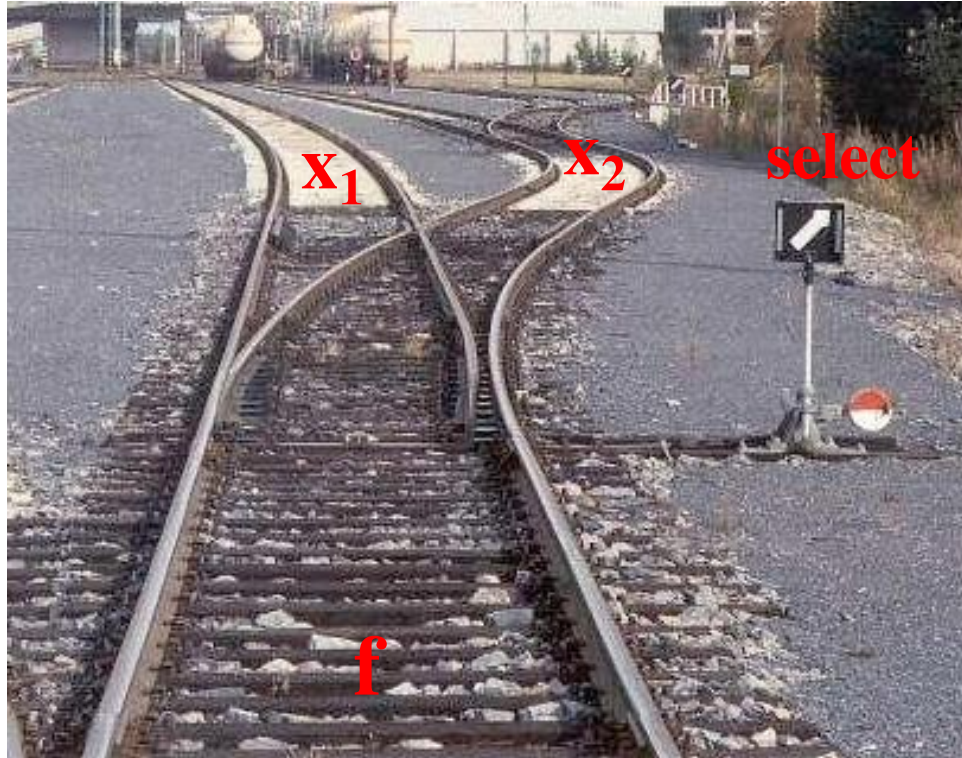

http://en.wikipedia.org/wiki/Railroad_switch]

Analogy: Railroad Switch

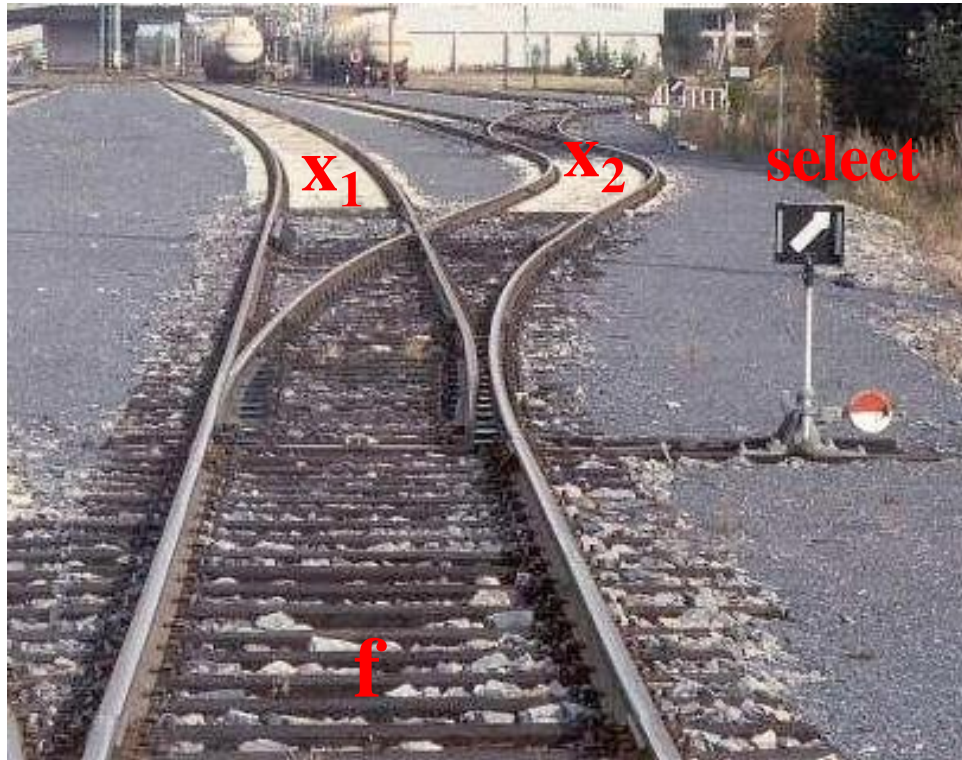

This is not a perfect analogy because the trains can go in either direction, while the multiplexer would only allow them to go from top to bottom.

http://en.wikipedia.org/wiki/Railroad_switch]

Truth Table for a 2-to-1 Multiplexer

$s \ x_1 \ x_2$	$f(s, x_1, x_2)$
0 0 0	0
0 0 1	0
0 1 0	1
0 1 1	1
1 0 0	0
1 0 1	1
1 1 0	0
1 1 1	1

[Figure 2.33a from the textbook]

Let's Derive the SOP form

$s \ x_1 \ x_2$	$f(s, x_1, x_2)$
0 0 0	0
0 0 1	0
0 1 0	1
0 1 1	1
1 0 0	0
1 0 1	1
1 1 0	0
1 1 1	1

Let's Derive the SOP form

$s \ x_1 \ x_2$	$f(s, x_1, x_2)$
0 0 0	0
0 0 1	0
0 1 0	1
0 1 1	1
1 0 0	0
1 0 1	1
1 1 0	0
1 1 1	1

Let's Derive the SOP form

$s \ x_1 \ x_2$	$f(s, x_1, x_2)$
0 0 0	0
0 0 1	0
0 1 0	1
0 1 1	1
1 0 0	0
1 0 1	1
1 1 0	0
1 1 1	1

Where should we
put the negation signs?

$s \ x_1 \ x_2$

$s \ x_1 \ x_2$

$s \ x_1 \ x_2$

$s \ x_1 \ x_2$

Let's Derive the SOP form

$s \ x_1 \ x_2$	$f(s, x_1, x_2)$
0 0 0	0
0 0 1	0
0 1 0	1
0 1 1	1
1 0 0	0
1 0 1	1
1 1 0	0
1 1 1	1

$$\overline{s} \ x_1 \ \overline{x}_2$$

$$\overline{s} \ x_1 \ x_2$$

$$s \ \overline{x}_1 \ x_2$$

$$s \ x_1 \ x_2$$

Let's Derive the SOP form

$s \ x_1 \ x_2$	$f(s, x_1, x_2)$	
0 0 0	0	
0 0 1	0	
0 1 0	1	$\overline{s} \ x_1 \ \overline{x}_2$
0 1 1	1	$\overline{s} \ x_1 \ x_2$
1 0 0	0	
1 0 1	1	$s \ \overline{x}_1 \ x_2$
1 1 0	0	
1 1 1	1	$s \ x_1 \ x_2$

$$f(s, x_1, x_2) = \overline{s} \ x_1 \ \overline{x}_2 + \overline{s} \ x_1 \ x_2 + s \ \overline{x}_1 \ x_2 + s \ x_1 \ x_2$$

Let's simplify this expression

$$f(s, x_1, x_2) = \overline{s} x_1 \overline{x_2} + \overline{s} x_1 x_2 + s \overline{x_1} x_2 + s x_1 x_2$$

Let's simplify this expression

$$f(s, x_1, x_2) = \bar{s} x_1 \bar{x}_2 + \bar{s} x_1 x_2 + s \bar{x}_1 x_2 + s x_1 x_2$$

$$f(s, x_1, x_2) = \bar{s} x_1 (\bar{x}_2 + x_2) + s (\bar{x}_1 + x_1) x_2$$


Let's simplify this expression

$$f(s, x_1, x_2) = \bar{s} x_1 \bar{x}_2 + \bar{s} x_1 x_2 + s \bar{x}_1 x_2 + s x_1 x_2$$


$$f(s, x_1, x_2) = \bar{s} x_1 (\bar{x}_2 + x_2) + s (\bar{x}_1 + x_1) x_2$$

$$f(s, x_1, x_2) = \bar{s} x_1 + s x_2$$

Circuit for 2-1 Multiplexer

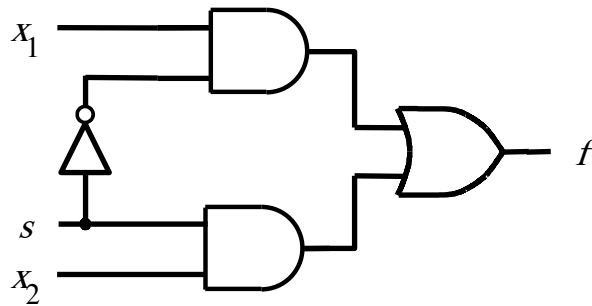


(b) Circuit

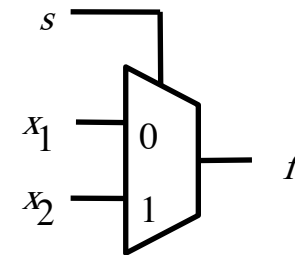

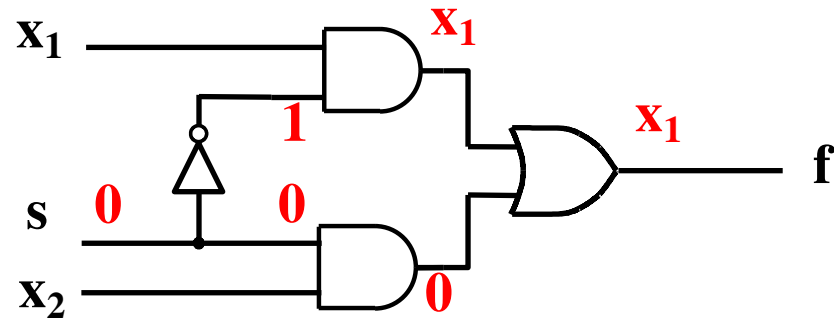
(c) Graphical symbol

$$f(s, x_1, x_2) = \overline{s} x_1 + s x_2$$


Analysis of the 2-to-1 Multiplexer (when the input $s=0$)



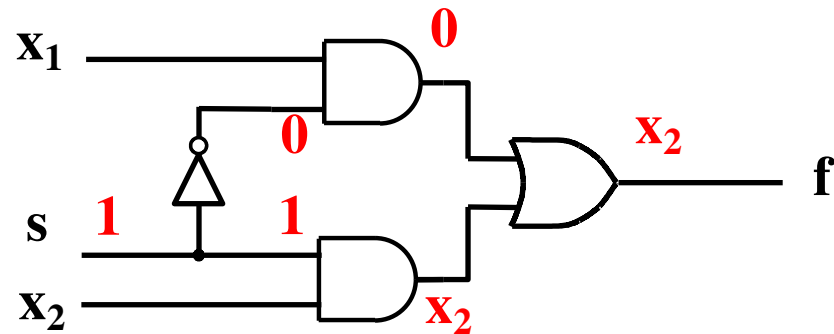
Analysis of the 2-to-1 Multiplexer (when the input $s=1$)



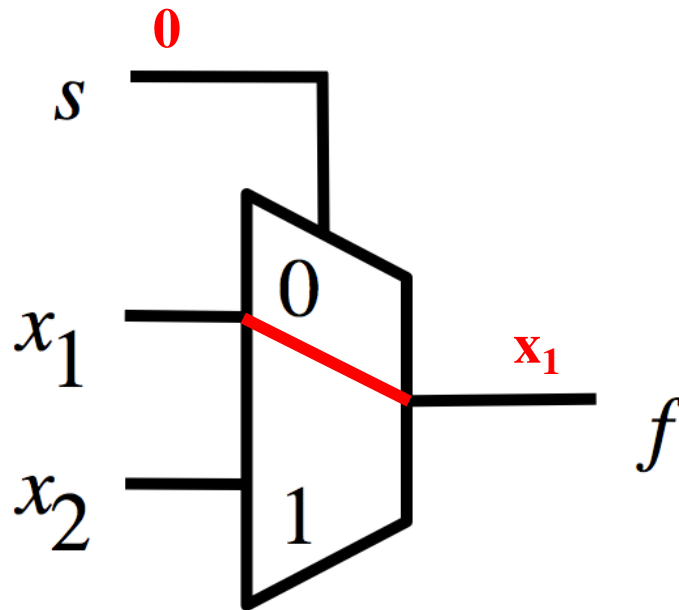Analysis of the 2-to-1 Multiplexer (when the input $s=0$)



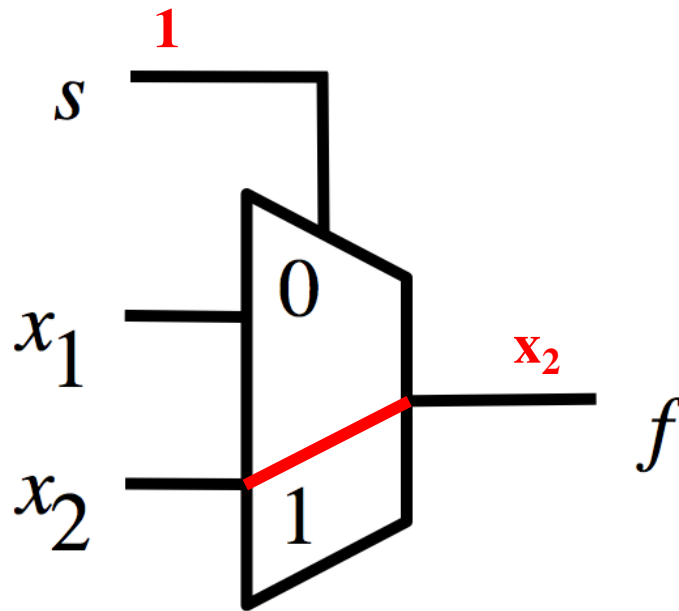Analysis of the 2-to-1 Multiplexer (when the input $s=1$)



More Compact Truth-Table Representation

$s \ x_1 \ x_2$	$f(s, x_1, x_2)$
0 0 0	0
0 0 1	0
0 1 0	1
0 1 1	1
1 0 0	0
1 0 1	1
1 1 0	0
1 1 1	1

(a) Truth table


s	$f(s, x_1, x_2)$
0	x_1
1	x_2

4-to-1 Multiplexer

4-to-1 Multiplexer (Definition)

- Has four inputs: w_0 , w_1 , w_2 , w_3
- Also has two select lines: s_1 and s_0
- If $s_1=0$ and $s_0=0$, then the output f is equal to w_0
- If $s_1=0$ and $s_0=1$, then the output f is equal to w_1
- If $s_1=1$ and $s_0=0$, then the output f is equal to w_2
- If $s_1=1$ and $s_0=1$, then the output f is equal to w_3

Graphical Symbol and Truth Table

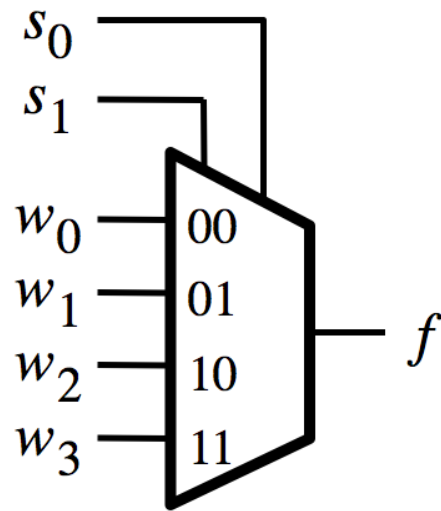

(a) Graphic symbol

s_1	s_0	f
0	0	w_0
0	1	w_1
1	0	w_2
1	1	w_3

(b) Truth table

The long-form truth table

The long-form truth table

S ₁ S ₀	I ₃ I ₂ I ₁ I ₀	F	S ₁ S ₀	I ₃ I ₂ I ₁ I ₀	F	S ₁ S ₀	I ₃ I ₂ I ₁ I ₀	F	S ₁ S ₀	I ₃ I ₂ I ₁ I ₀	F
0 0	0 0 0 0	0	0 1	0 0 0 0	0	1 0	0 0 0 0	0	1 1	0 0 0 0	0
	0 0 0 1	1		0 0 0 1	0		0 0 0 1	0		0 0 0 1	0
	0 0 1 0	0		0 0 1 0	1		0 0 1 0	0		0 0 1 0	0
	0 0 1 1	1		0 0 1 1	1		0 0 1 1	0		0 0 1 1	0
	0 1 0 0	0		0 1 0 0	0		0 1 0 0	1		0 1 0 0	0
	0 1 0 1	1		0 1 0 1	0		0 1 0 1	1		0 1 0 1	0
	0 1 1 0	0		0 1 1 0	1		0 1 1 0	1		0 1 1 0	0
	0 1 1 1	1		0 1 1 1	1		0 1 1 1	1		0 1 1 1	0
	1 0 0 0	0		1 0 0 0	0		1 0 0 0	0		1 0 0 0	1
	1 0 0 1	1		1 0 0 1	0		1 0 0 1	0		1 0 0 1	1
	1 0 1 0	0		1 0 1 0	1		1 0 1 0	0		1 0 1 0	1
	1 0 1 1	1		1 0 1 1	1		1 0 1 1	0		1 0 1 1	1
	1 1 0 0	0		1 1 0 0	0		1 1 0 0	1		1 1 0 0	1
	1 1 0 1	1		1 1 0 1	0		1 1 0 1	1		1 1 0 1	1
	1 1 1 0	0		1 1 1 0	1		1 1 1 0	1		1 1 1 0	1
	1 1 1 1	1		1 1 1 1	1		1 1 1 1	1		1 1 1 1	1

[<http://www.absoluteastronomy.com/topics/Multiplexer>]

The long-form truth table

S ₁ S ₀	I ₃	I ₂	I ₁	I ₀	F	S ₁ S ₀	I ₃	I ₂	I ₁	I ₀	F	S ₁ S ₀	I ₃	I ₂	I ₁	I ₀	F	S ₁ S ₀	I ₃	I ₂	I ₁	I ₀	F
0 0	0	0	0	0	0	0 1	0	0	0	0	0	1 0	0	0	0	0	0	1 1	0	0	0	0	0
	0	0	0	1	1		0	0	0	1	0		0	0	0	1	0		0	0	0	1	0
	0	0	1	0	0		0	0	1	0	1		0	0	1	0	0		0	0	1	0	0
	0	0	1	1	1		0	0	1	1	1		0	0	1	1	0		0	0	1	1	0
	0	1	0	0	0		0	1	0	0	0		0	1	0	0	1		0	1	0	0	0
	0	1	0	1	1		0	1	0	1	0		0	1	0	1	1		0	1	0	1	0
	0	1	1	0	0		0	1	1	0	1		0	1	1	0	1		0	1	1	0	0
	0	1	1	1	1		0	1	1	1	1		0	1	1	1	1		0	1	1	1	0
	1	0	0	0	0		1	0	0	0	0		1	0	0	0	0		1	0	0	0	1
	1	0	0	1	1		1	0	0	1	0		1	0	0	1	0		1	0	0	1	1
	1	0	1	0	0		1	0	1	0	1		1	0	1	0	0		1	0	1	0	1
	1	0	1	1	1		1	0	1	1	1		1	0	1	1	0		1	0	1	1	1
	1	1	0	0	0		1	1	0	0	0		1	1	0	0	1		1	1	0	0	1
	1	1	0	1	1		1	1	0	1	0		1	1	0	1	1		1	1	0	1	1
	1	1	1	0	0		1	1	1	0	1		1	1	1	0	1		1	1	1	0	1
	1	1	1	1	1		1	1	1	1	1		1	1	1	1	1		1	1	1	1	1

identical

[<http://www.absoluteastronomy.com/topics/Multiplexer>]

The long-form truth table

S ₁ S ₀	I ₃ I ₂ I ₁ I ₀	F	S ₁ S ₀	I ₃ I ₂ I ₁ I ₀	F	S ₁ S ₀	I ₃ I ₂ I ₁ I ₀	F	S ₁ S ₀	I ₃ I ₂ I ₁ I ₀	F
0 0	0 0 0 0	0	0 1	0 0 0 0	0	1 0	0 0 0 0	0	1 1	0 0 0 0	0
	0 0 0 1	1		0 0 0 1	0		0 0 0 1	0		0 0 0 1	0
	0 0 1 0	0		0 0 1 0	1		0 0 1 0	0		0 0 1 0	0
	0 0 1 1	1		0 0 1 1	1		0 0 1 1	0		0 0 1 1	0
	0 1 0 0	0		0 1 0 0	0		0 1 0 0	1		0 1 0 0	0
	0 1 0 1	1		0 1 0 1	0		0 1 0 1	1		0 1 0 1	0
	0 1 1 0	0		0 1 1 0	1		0 1 1 0	1		0 1 1 0	0
	0 1 1 1	1		0 1 1 1	1		0 1 1 1	1		0 1 1 1	0
	1 0 0 0	0		1 0 0 0	0		1 0 0 0	0		1 0 0 0	1
	1 0 0 1	1		1 0 0 1	0		1 0 0 1	0		1 0 0 1	1
	1 0 1 0	0		1 0 1 0	1		1 0 1 0	0		1 0 1 0	1
	1 0 1 1	1		1 0 1 1	1		1 0 1 1	0		1 0 1 1	1
	1 1 0 0	0		1 1 0 0	0		1 1 0 0	1		1 1 0 0	1
	1 1 0 1	1		1 1 0 1	0		1 1 0 1	1		1 1 0 1	1
	1 1 1 0	0		1 1 1 0	1		1 1 1 0	1		1 1 1 0	1
	1 1 1 1	1		1 1 1 1	1		1 1 1 1	1		1 1 1 1	1

identical

[<http://www.absoluteastronomy.com/topics/Multiplexer>]

The long-form truth table

S ₁ S ₀	I ₃ I ₂ I ₁ I ₀	F	S ₁ S ₀	I ₃ I ₂ I ₁ I ₀	F	S ₁ S ₀	I ₃ I ₂ I ₁ I ₀	F	S ₁ S ₀	I ₃ I ₂ I ₁ I ₀	F
0 0	0 0 0 0	0	0 1	0 0 0 0	0	1 0	0 0 0 0	0	1 1	0 0 0 0	0
	0 0 0 1	1		0 0 0 1	0		0 0 0 1	0		0 0 0 1	0
	0 0 1 0	0		0 0 1 0	1		0 0 1 0	0		0 0 1 0	0
	0 0 1 1	1		0 0 1 1	1		0 0 1 1	0		0 0 1 1	0
	0 1 0 0	0		0 1 0 0	0		0 1 0 0	1		0 1 0 0	0
	0 1 0 1	1		0 1 0 1	0		0 1 0 1	1		0 1 0 1	0
	0 1 1 0	0		0 1 1 0	1		0 1 1 0	1		0 1 1 0	0
	0 1 1 1	1		0 1 1 1	1		0 1 1 1	1		0 1 1 1	0
	1 0 0 0	0		1 0 0 0	0		1 0 0 0	0		1 0 0 0	1
	1 0 0 1	1		1 0 0 1	0		1 0 0 1	0		1 0 0 1	1
	1 0 1 0	0		1 0 1 0	1		1 0 1 0	0		1 0 1 0	1
	1 0 1 1	1		1 0 1 1	1		1 0 1 1	0		1 0 1 1	1
	1 1 0 0	0		1 1 0 0	0		1 1 0 0	1		1 1 0 0	1
	1 1 0 1	1		1 1 0 1	0		1 1 0 1	1		1 1 0 1	1
	1 1 1 0	0		1 1 1 0	1		1 1 1 0	1		1 1 1 0	1
	1 1 1 1	1		1 1 1 1	1		1 1 1 1	1		1 1 1 1	1

identical

[<http://www.absoluteastronomy.com/topics/Multiplexer>]


The long-form truth table

S ₁ S ₀	I ₃ I ₂ I ₁ I ₀	F	S ₁ S ₀	I ₃ I ₂ I ₁ I ₀	F	S ₁ S ₀	I ₃ I ₂ I ₁ I ₀	F	S ₁ S ₀	I ₃ I ₂ I ₁ I ₀	F
0 0	0 0 0 0	0	0 1	0 0 0 0	0	1 0	0 0 0 0	0	1 1	0 0 0 0	0
	0 0 0 1	1		0 0 0 1	0		0 0 0 1	0		0 0 0 1	0
	0 0 1 0	0		0 0 1 0	1		0 0 1 0	0		0 0 1 0	0
	0 0 1 1	1		0 0 1 1	1		0 0 1 1	0		0 0 1 1	0
	0 1 0 0	0		0 1 0 0	0		0 1 0 0	1		0 1 0 0	0
	0 1 0 1	1		0 1 0 1	0		0 1 0 1	1		0 1 0 1	0
	0 1 1 0	0		0 1 1 0	1		0 1 1 0	1		0 1 1 0	0
	0 1 1 1	1		0 1 1 1	1		0 1 1 1	1		0 1 1 1	0
	1 0 0 0	0		1 0 0 0	0		1 0 0 0	0		1 0 0 0	1
	1 0 0 1	1		1 0 0 1	0		1 0 0 1	0		1 0 0 1	1
	1 0 1 0	0		1 0 1 0	1		1 0 1 0	0		1 0 1 0	1
	1 0 1 1	1		1 0 1 1	1		1 0 1 1	0		1 0 1 1	1
	1 1 0 0	0		1 1 0 0	0		1 1 0 0	1		1 1 0 0	1
	1 1 0 1	1		1 1 0 1	0		1 1 0 1	1		1 1 0 1	1
	1 1 1 0	0		1 1 1 0	1		1 1 1 0	1		1 1 1 0	1
	1 1 1 1	1		1 1 1 1	1		1 1 1 1	1		1 1 1 1	1

identical

[<http://www.absoluteastronomy.com/topics/Multiplexer>]

Graphical Symbol and Truth Table

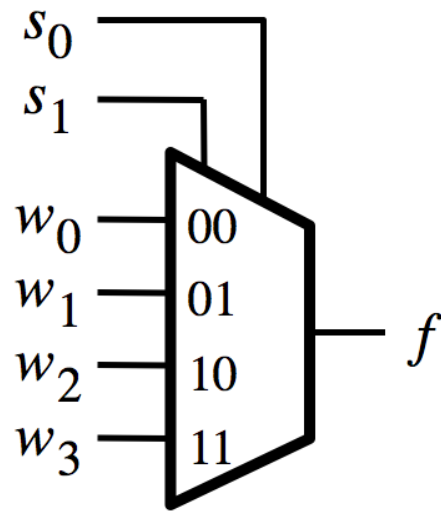


(a) Graphic symbol

s_1	s_0	f
0	0	w_0
0	1	w_1
1	0	w_2
1	1	w_3

(b) Truth table


4-to-1 Multiplexer (SOP circuit)

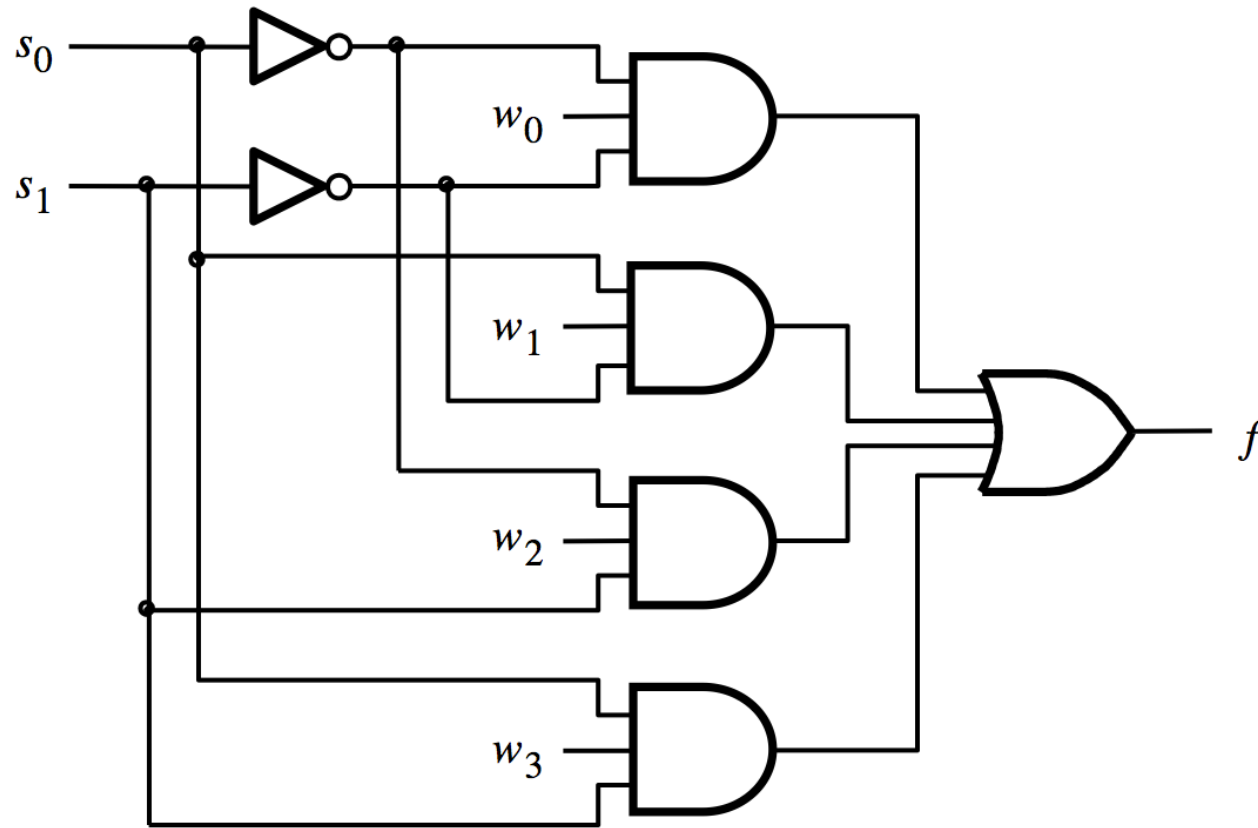

$$f = \overline{s_1} \overline{s_0} w_0 + \overline{s_1} s_0 w_1 + s_1 \overline{s_0} w_2 + s_1 s_0 w_3$$

[Figure 4.2c from the textbook]


4-to-1 Multiplexer (SOP circuit)

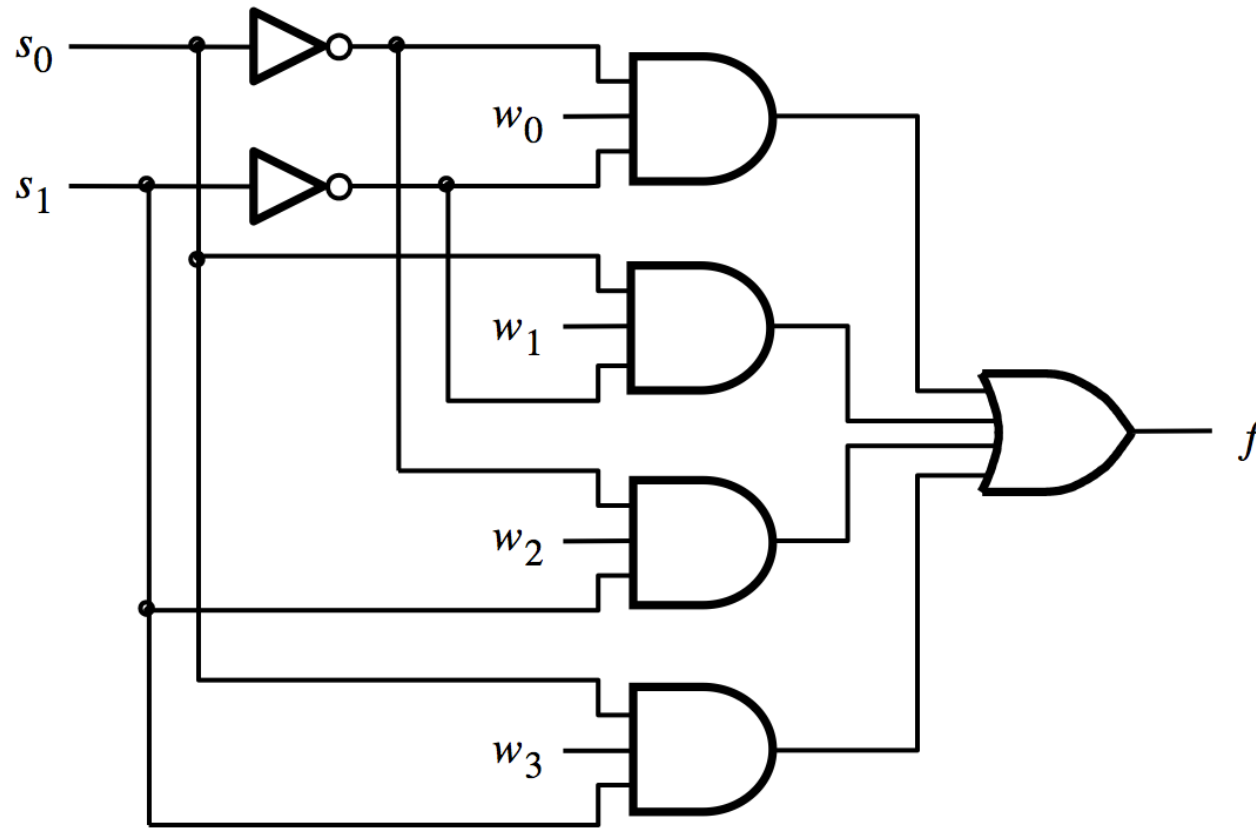

$$f = \overline{s_1} \overline{s_0} w_0 + \overline{s_1} s_0 w_1 + s_1 \overline{s_0} w_2 + s_1 s_0 w_3$$

these are the four minterms in terms of s_1 and s_2


4-to-1 Multiplexer (SOP circuit)

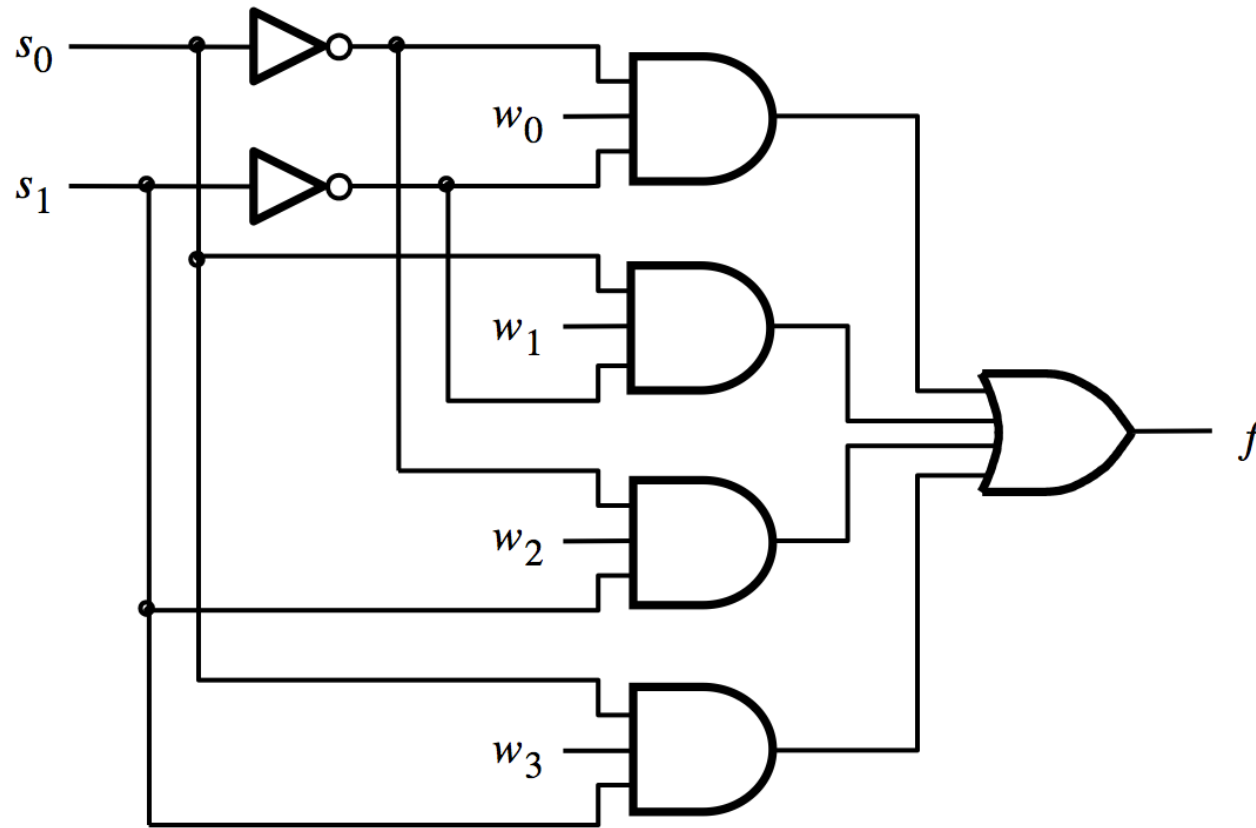


$$f = \overline{s_1} \overline{s_0} w_0 + \overline{s_1} s_0 w_1 + s_1 \overline{s_0} w_2 + s_1 s_0 w_3$$

these are the four w inputs to the 4-to-1 MUX

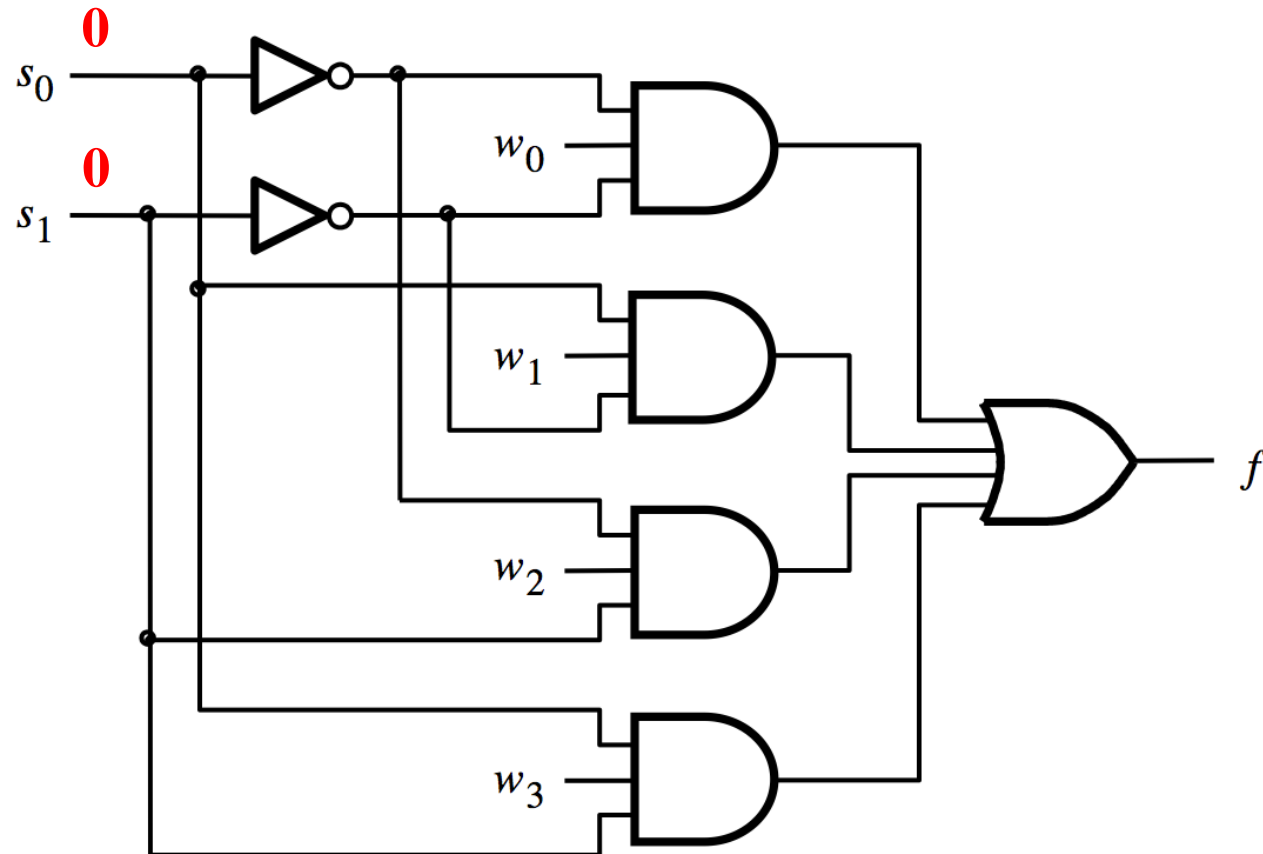
Analysis of the 4-to-1 Multiplexer ($s_1=0$ and $s_0=0$)



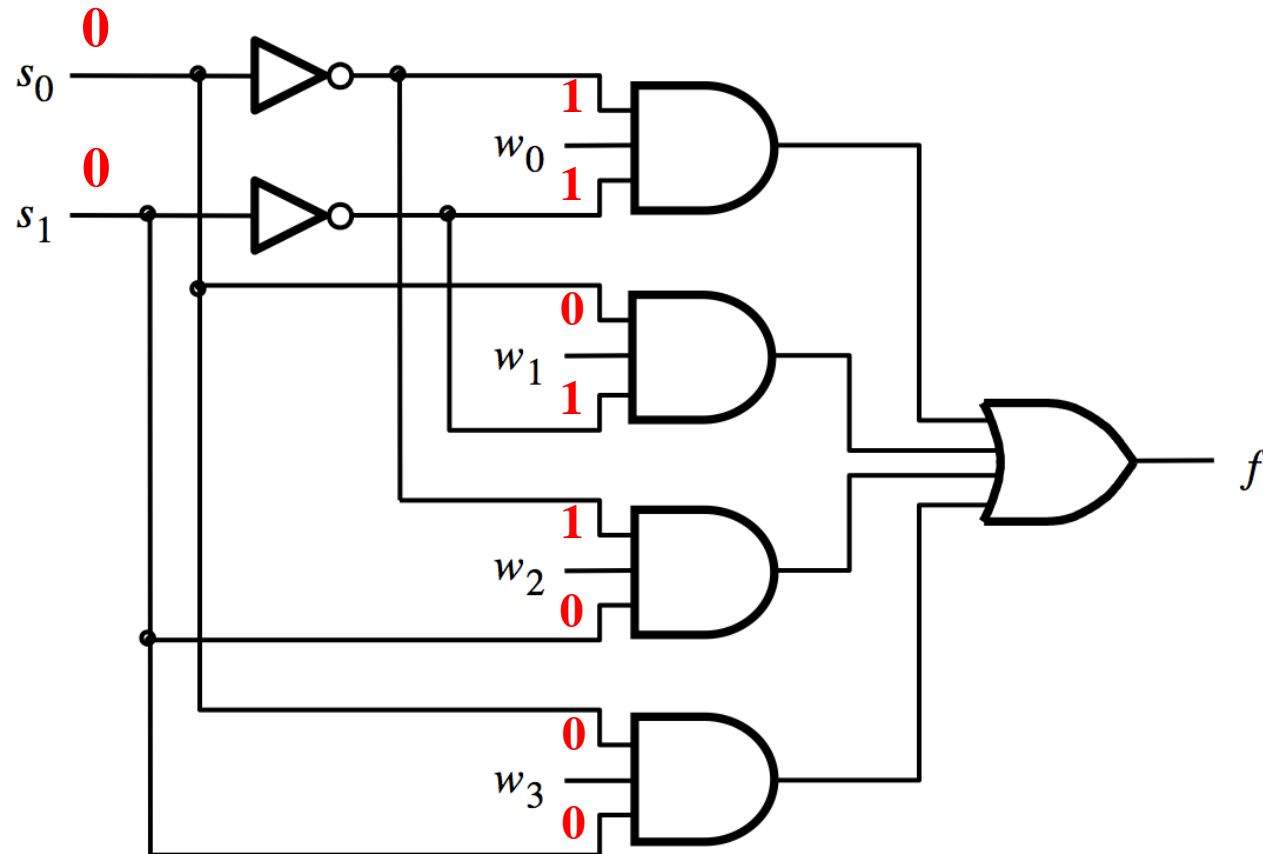
Analysis of the 4-to-1 Multiplexer ($s_1=0$ and $s_0=0$)



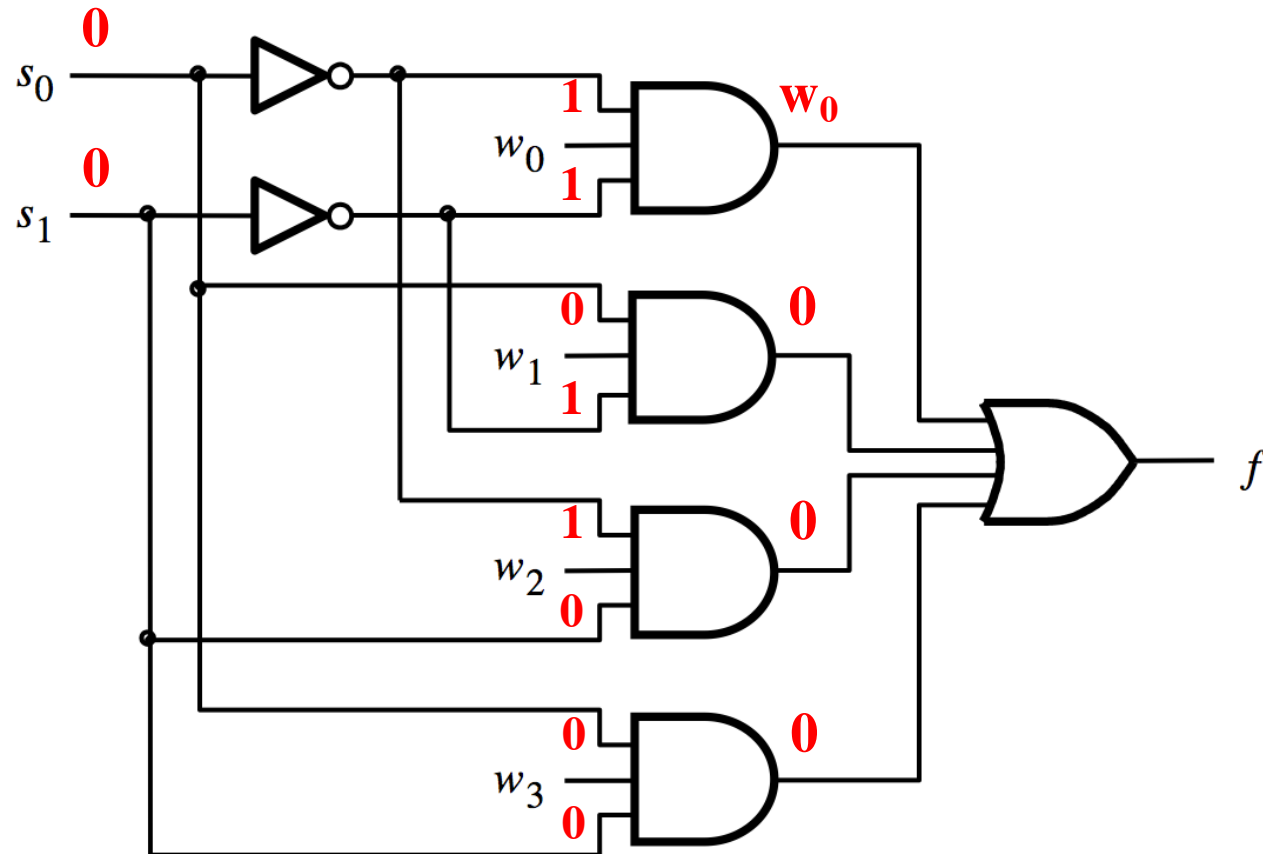
Analysis of the 4-to-1 Multiplexer ($s_1=0$ and $s_0=0$)



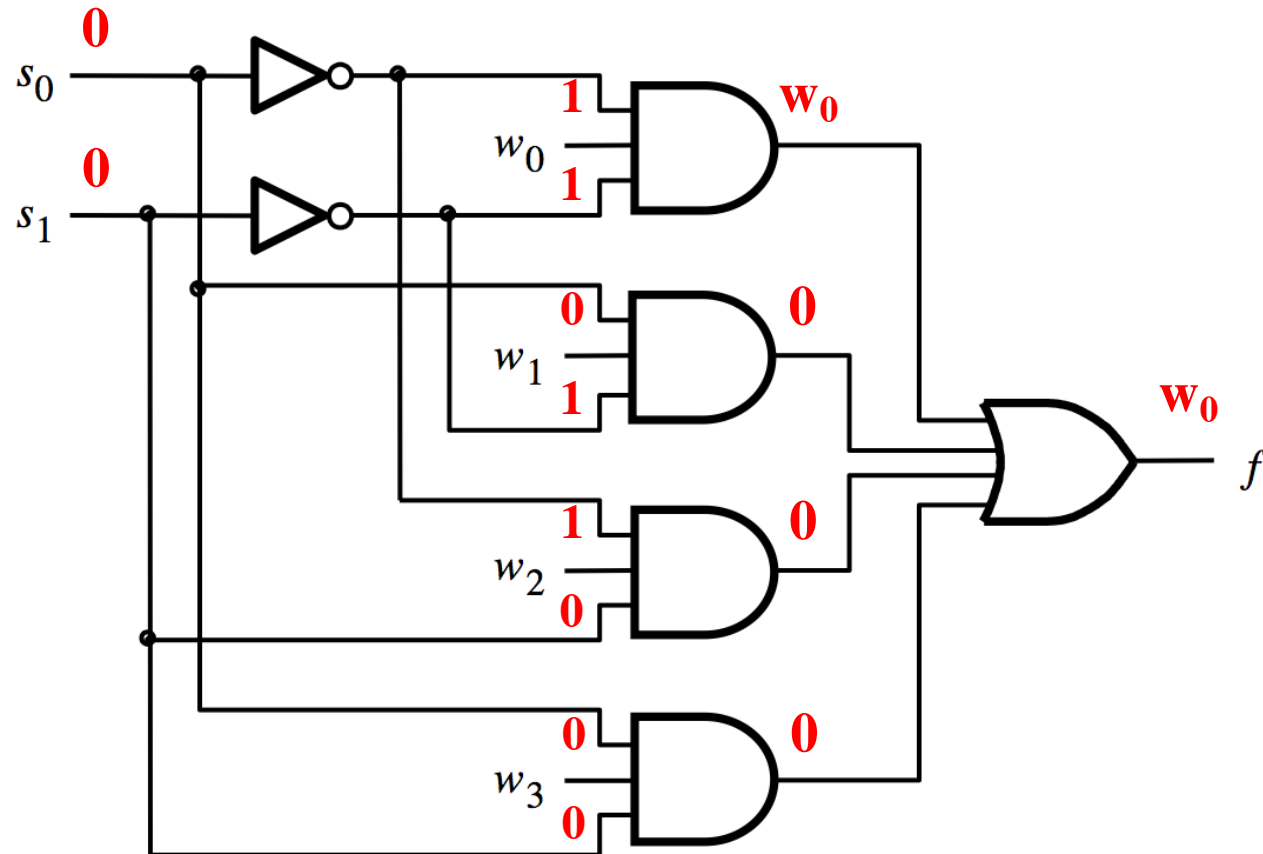
Analysis of the 4-to-1 Multiplexer ($s_1=0$ and $s_0=0$)



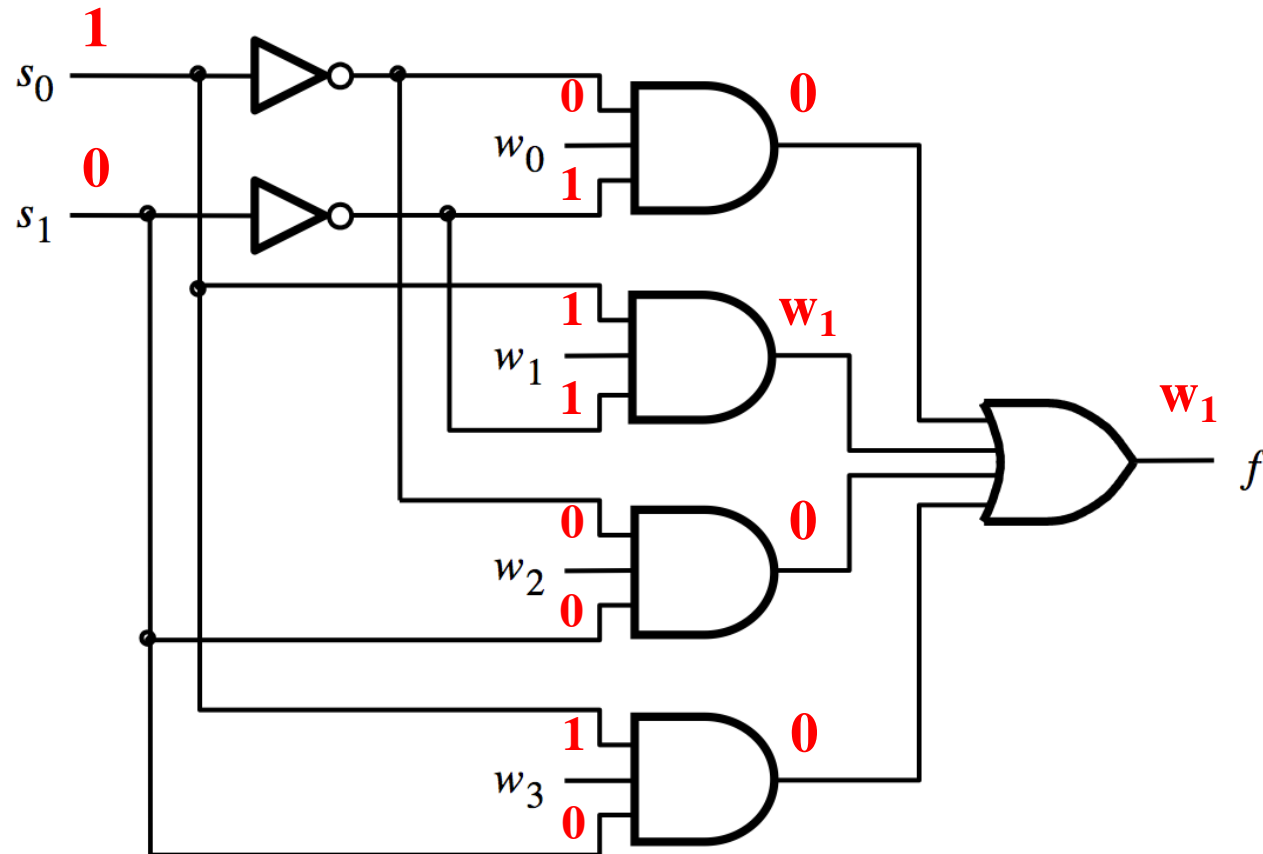
Analysis of the 4-to-1 Multiplexer ($s_1=0$ and $s_0=1$)



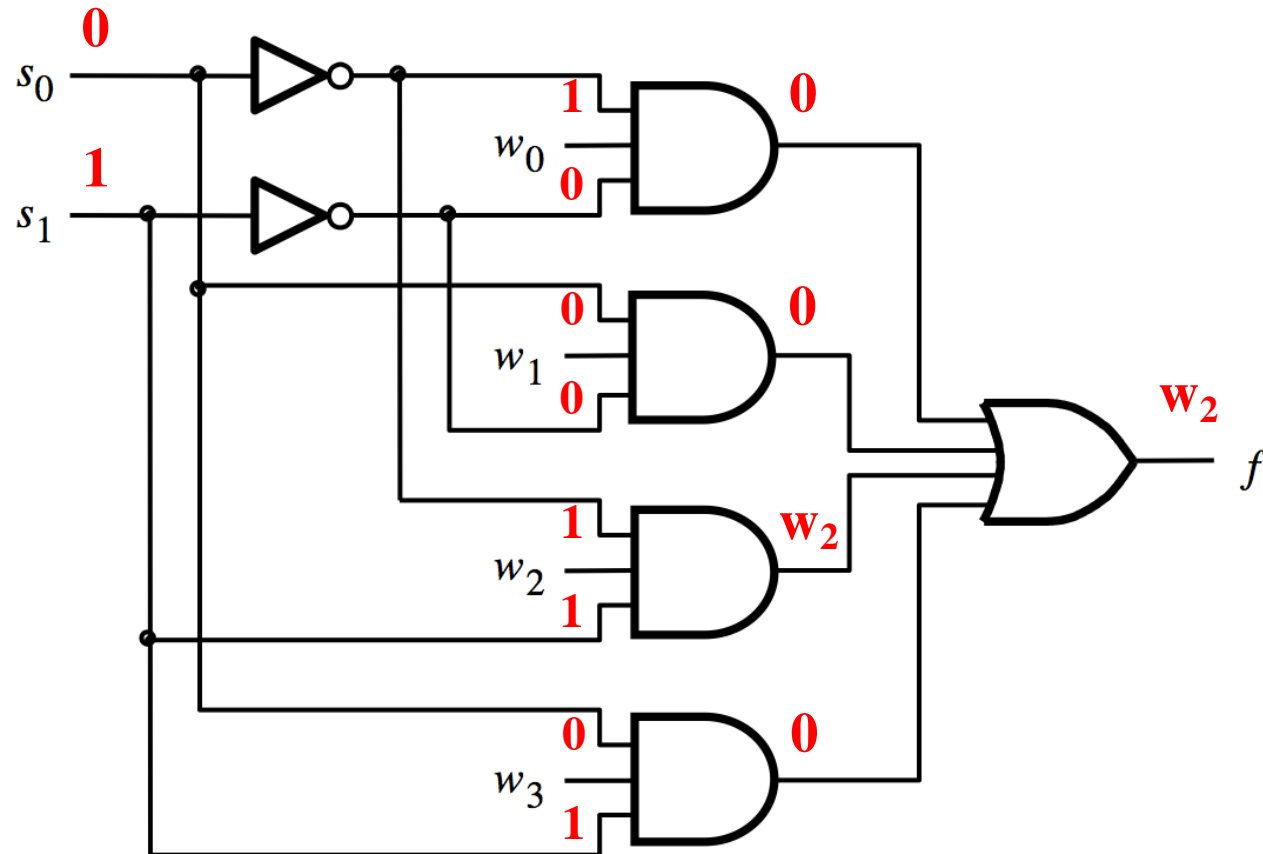
Analysis of the 4-to-1 Multiplexer ($s_1=1$ and $s_0=0$)



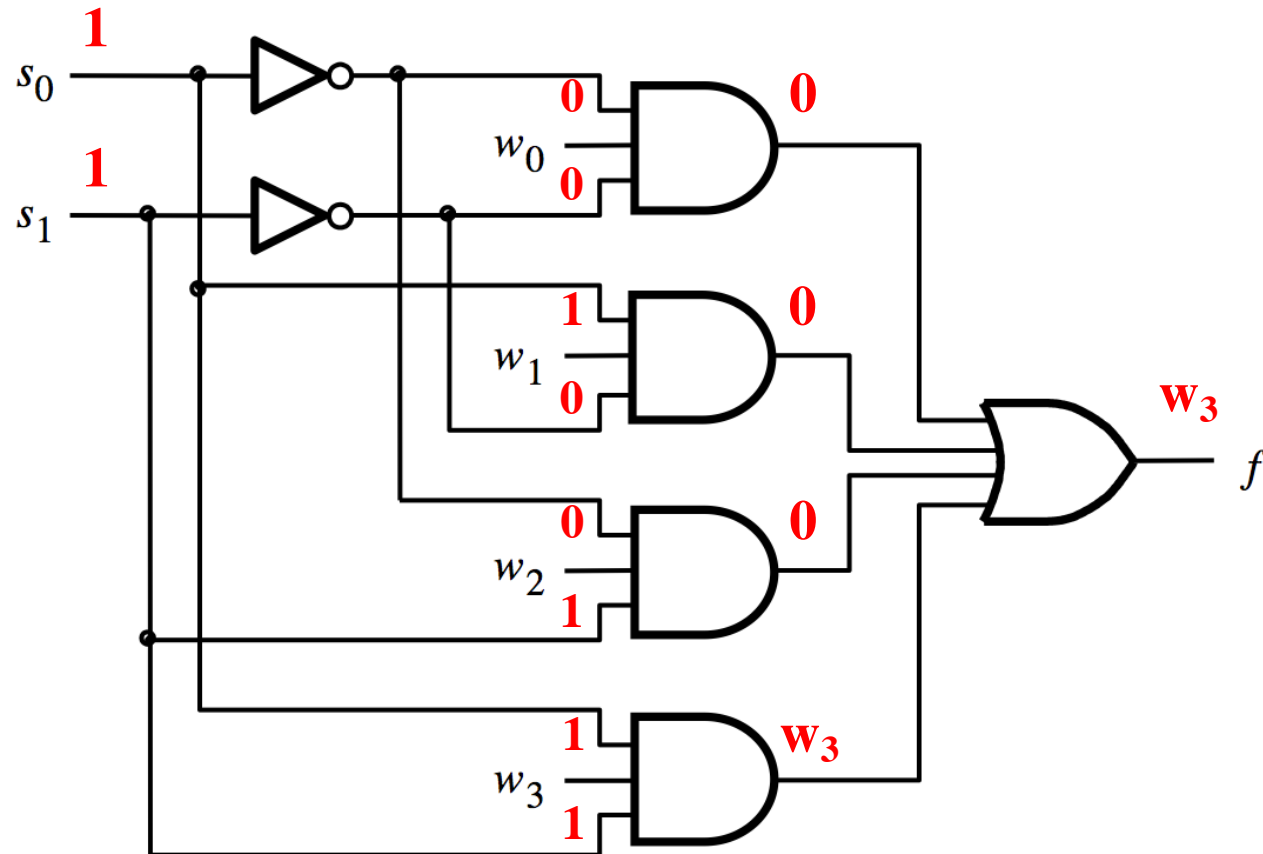
Analysis of the 4-to-1 Multiplexer ($s_1=1$ and $s_0=1$)



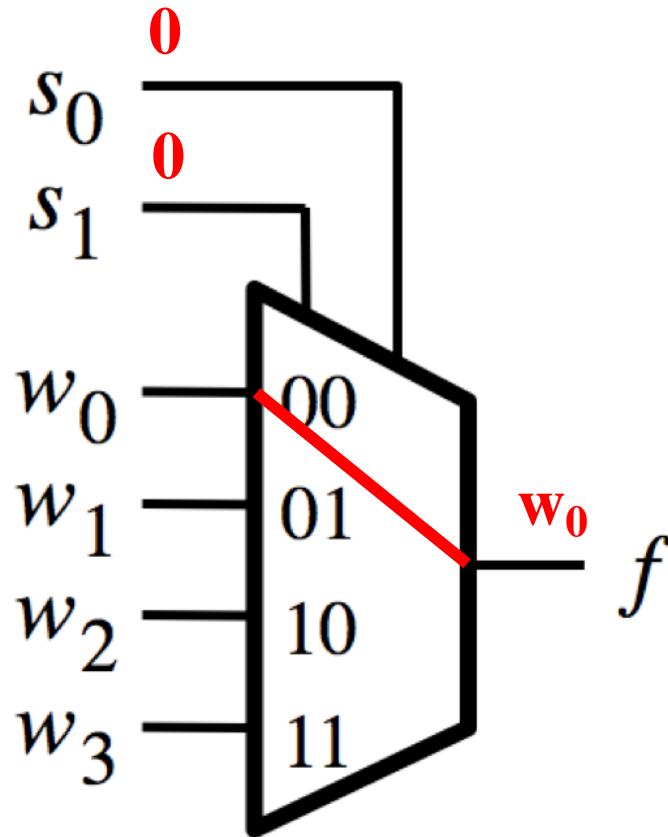
Analysis of the 4-to-1 Multiplexer ($s_1=0$ and $s_0=0$)



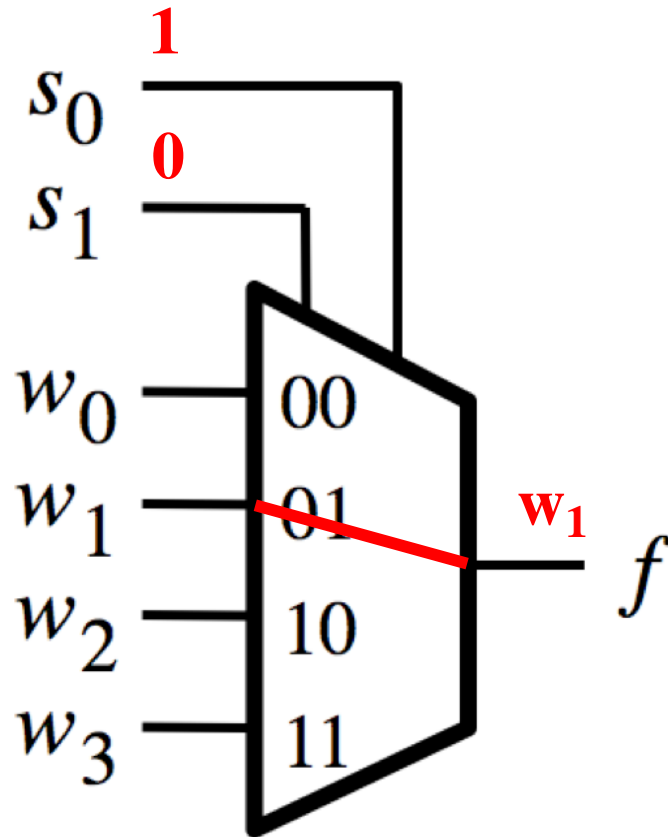
Analysis of the 4-to-1 Multiplexer ($s_1=0$ and $s_0=1$)



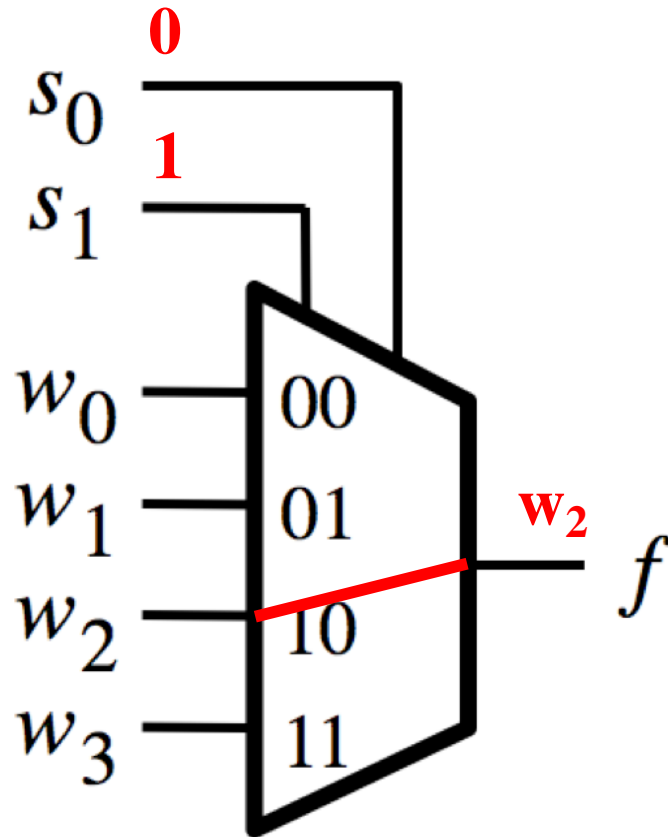
Analysis of the 4-to-1 Multiplexer ($s_1=1$ and $s_0=0$)



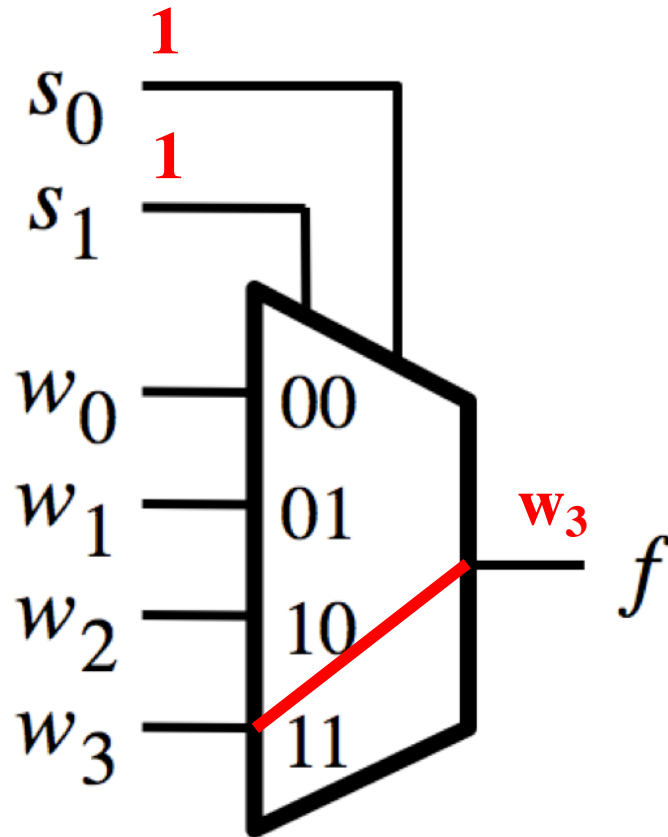Analysis of the 4-to-1 Multiplexer ($s_1=1$ and $s_0=1$)



Using three 2-to-1 multiplexers to build one 4-to-1 multiplexer

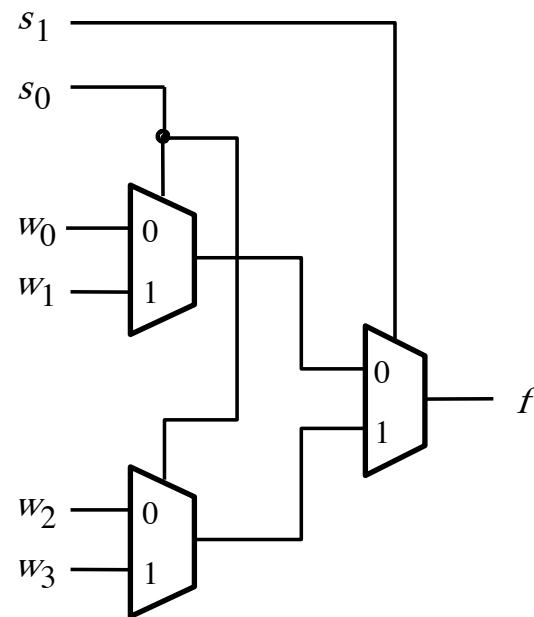




[Figure 4.3 from the textbook]

Analogy: Railroad Switches





http://en.wikipedia.org/wiki/Railroad_switch]

Analogy: Railroad Switches

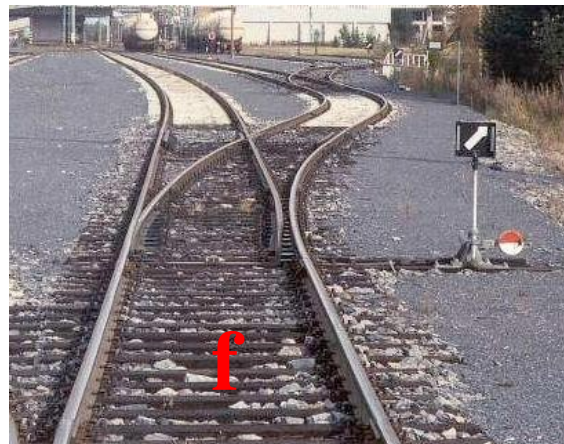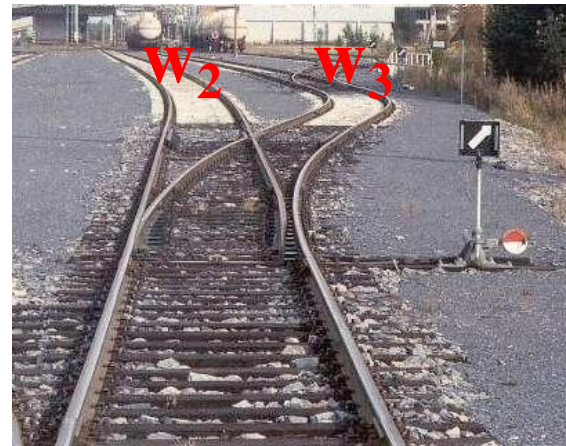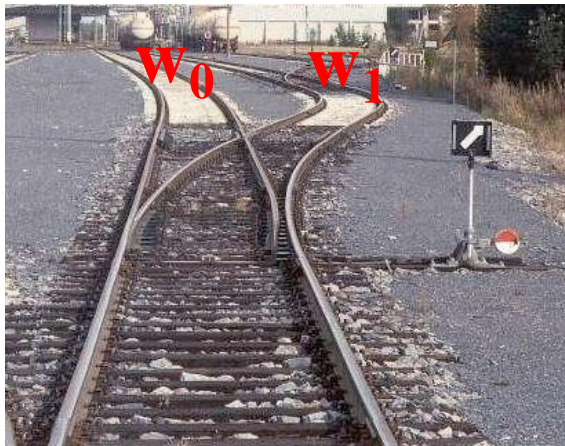


http://en.wikipedia.org/wiki/Railroad_switch

Analogy: Railroad Switches

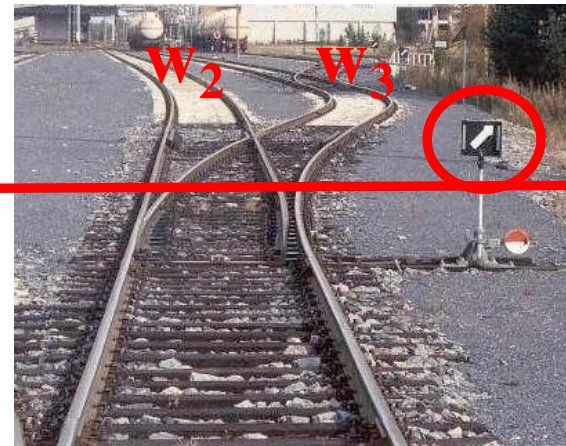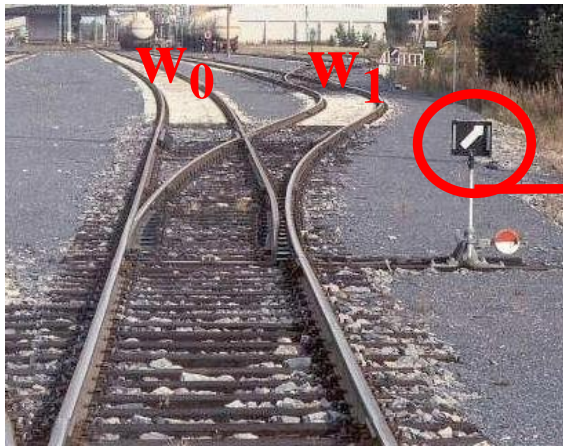

S_0

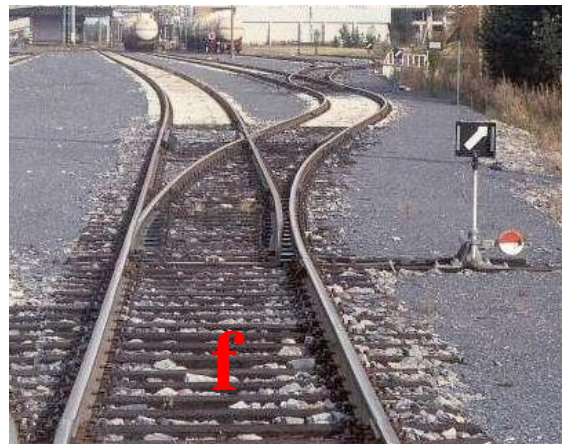
these two
switches are
controlled
together




S_1

http://en.wikipedia.org/wiki/Railroad_switch]

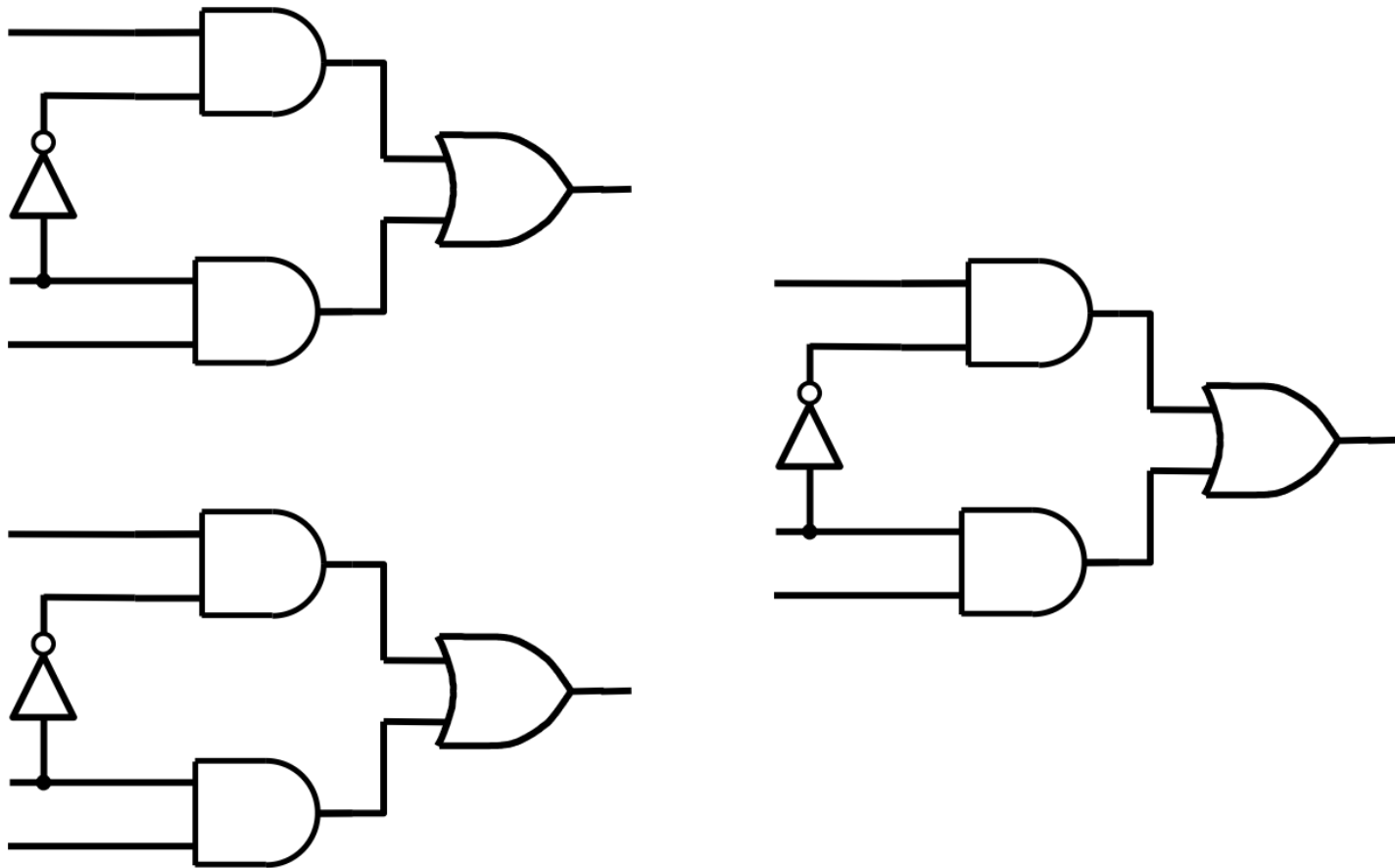
Using three 2-to-1 multiplexers to build one 4-to-1 multiplexer



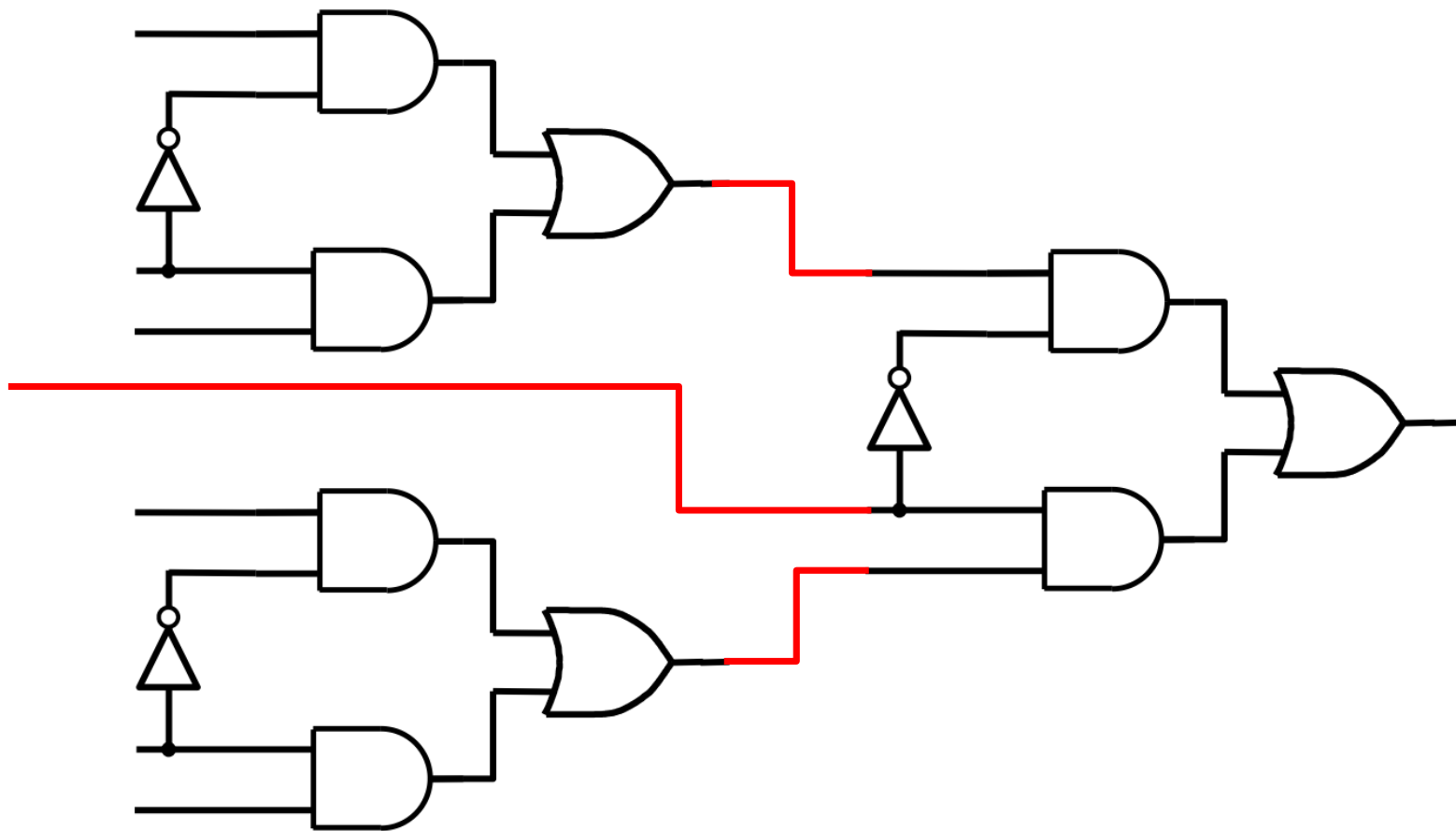
Using three 2-to-1 multiplexers to build one 4-to-1 multiplexer



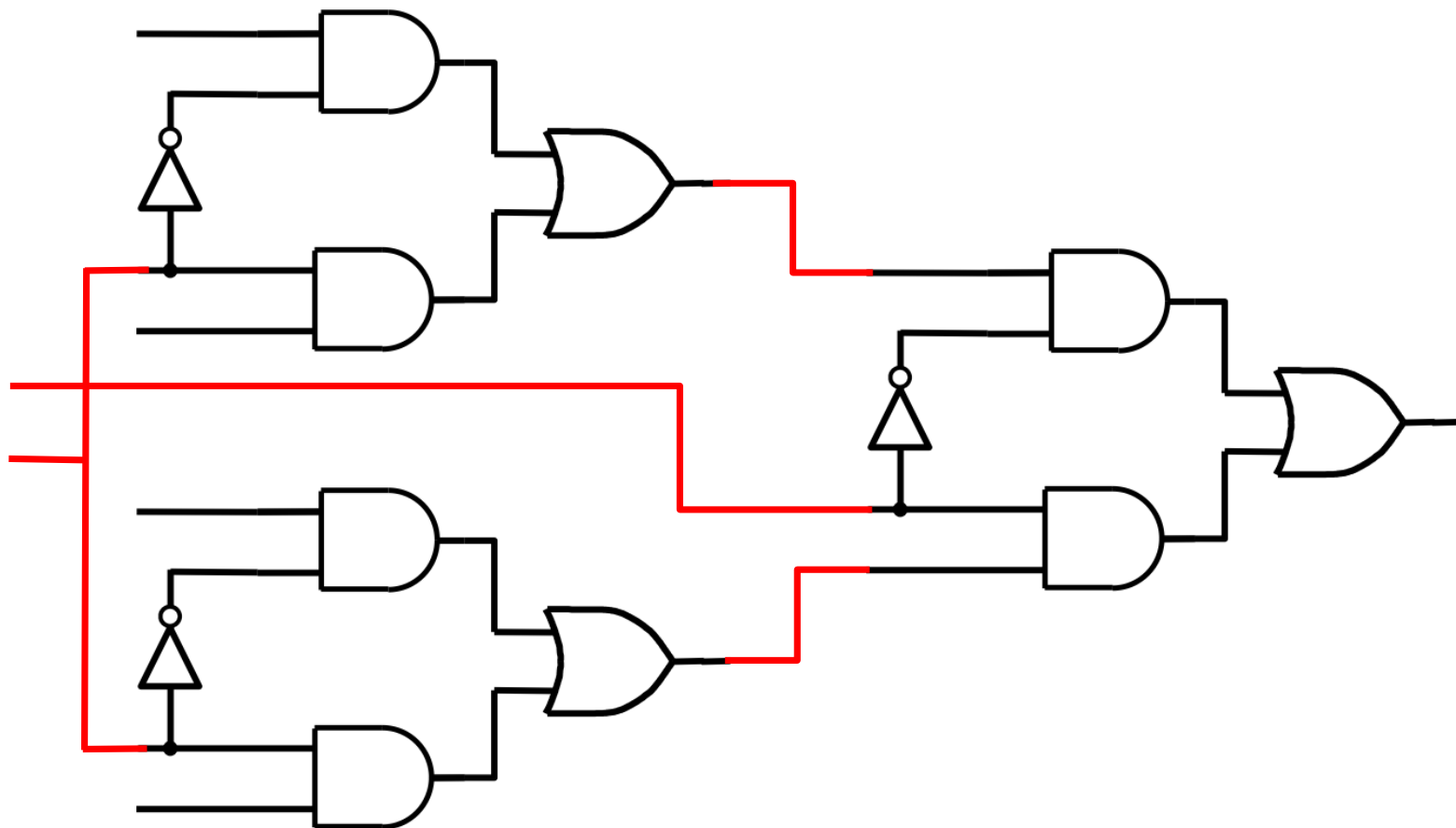
Using three 2-to-1 multiplexers to build one 4-to-1 multiplexer



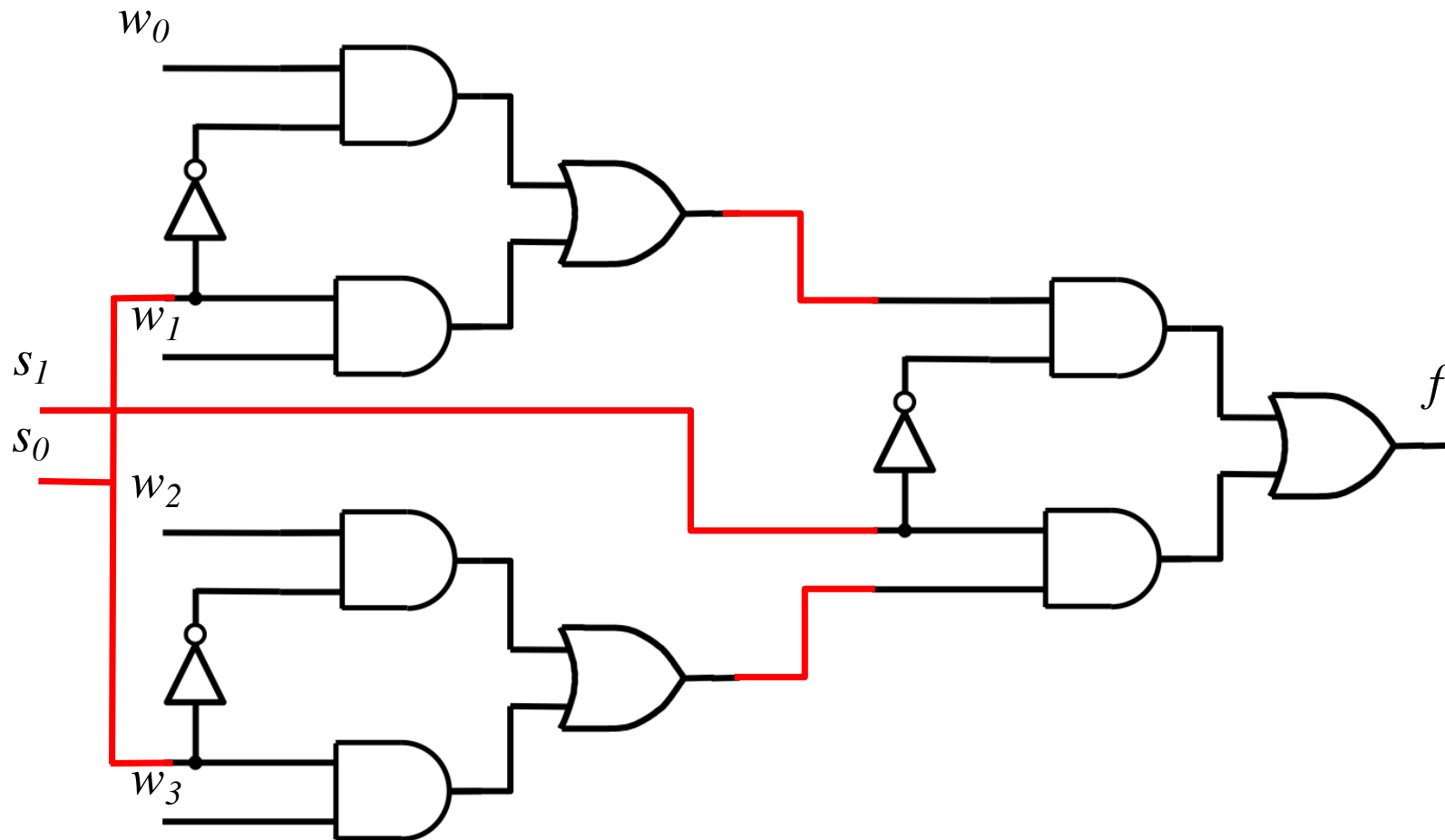
Using three 2-to-1 multiplexers to build one 4-to-1 multiplexer



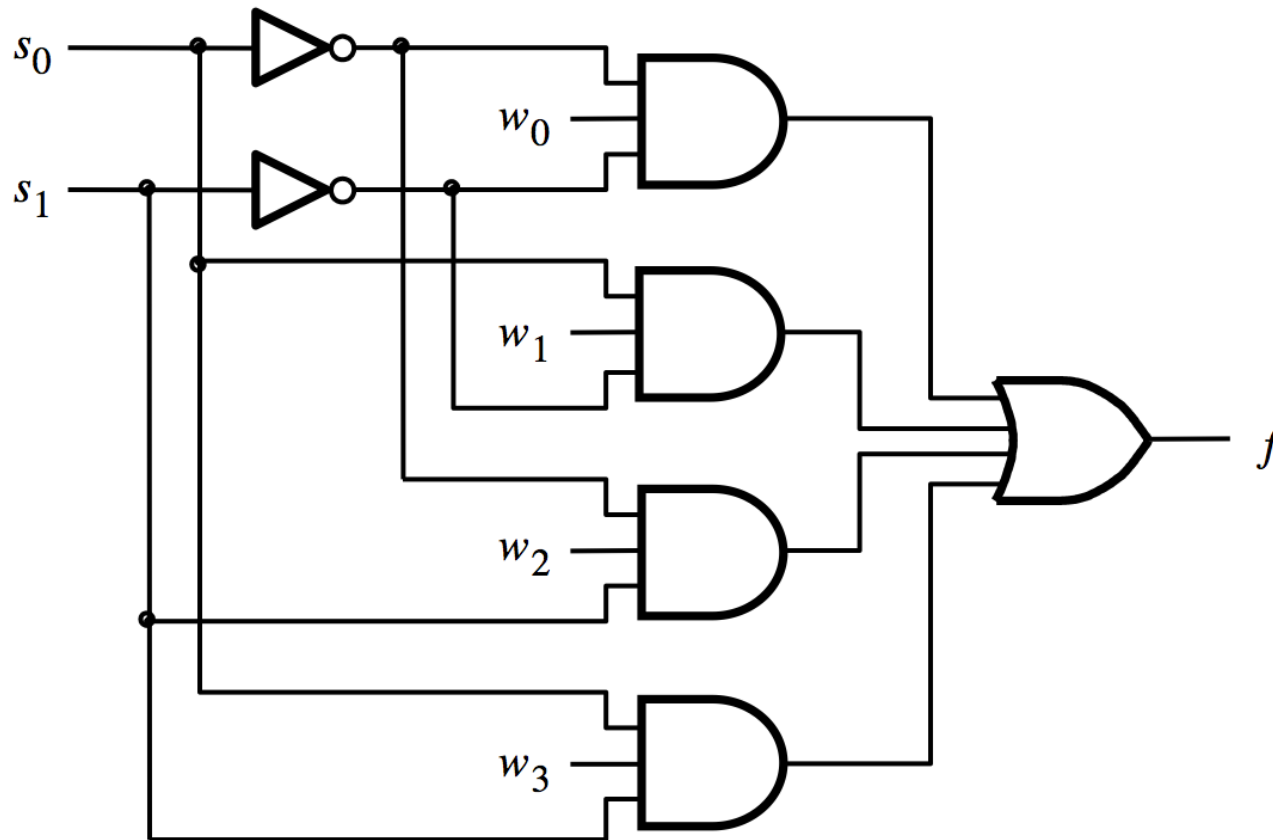That is different from the SOP form of the 4-to-1 multiplexer shown below, which uses fewer gates




Analysis of the Hierarchical Implementation ($s_1=0$ and $s_0=0$)

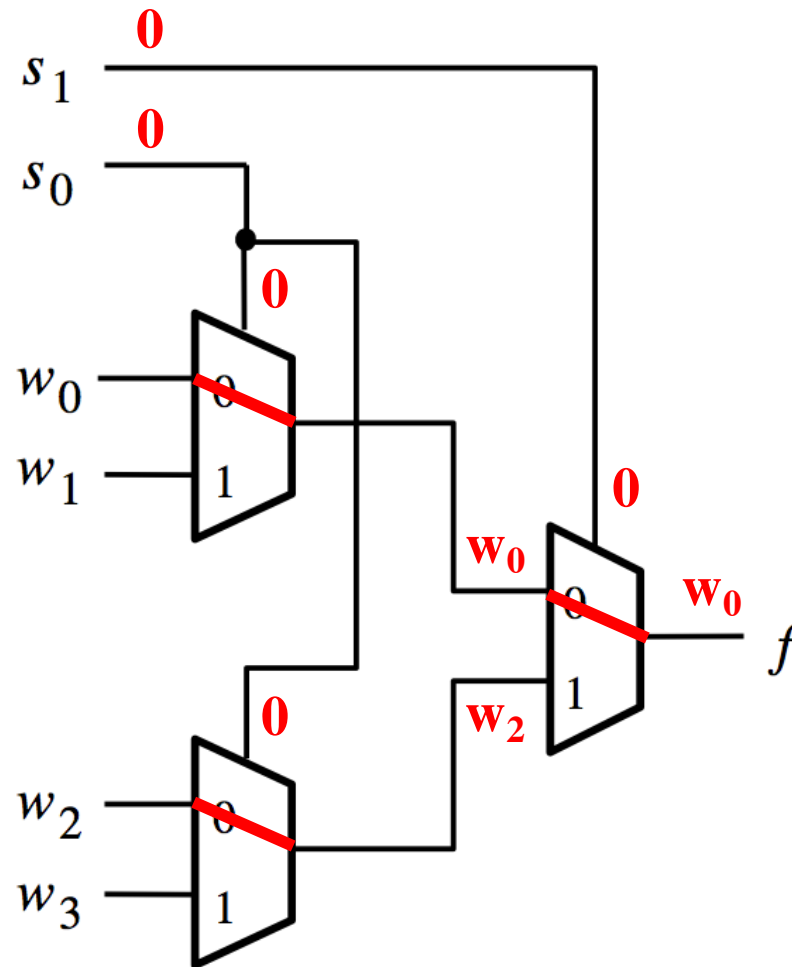

[Figure 4.3 from the textbook]


Analysis of the Hierarchical Implementation

($s_1=0$ and $s_0=1$)

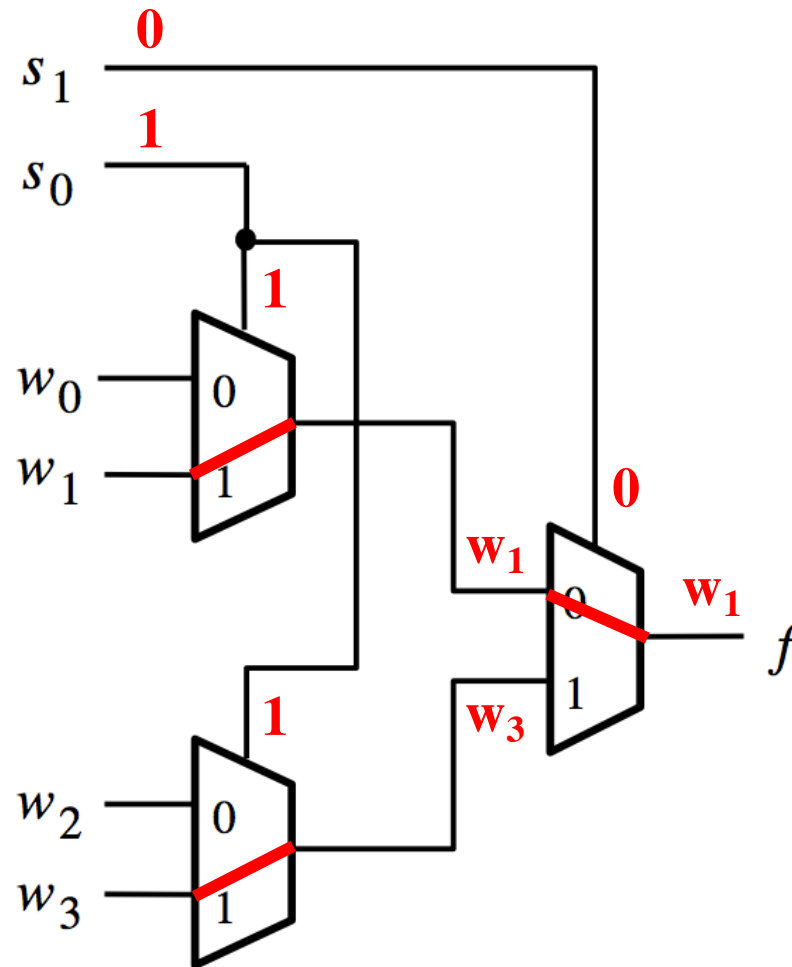


[Figure 4.3 from the textbook]

Analysis of the Hierarchical Implementation ($s_1=1$ and $s_0=0$)

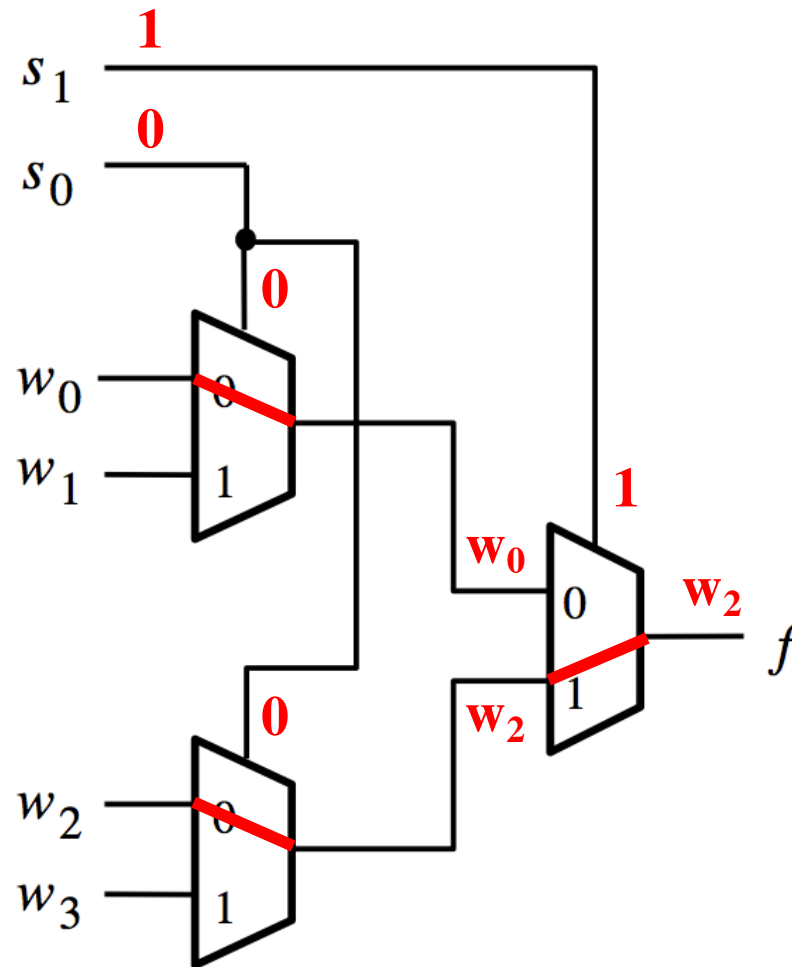

[Figure 4.3 from the textbook]


Analysis of the Hierarchical Implementation ($s_1=1$ and $s_0=1$)

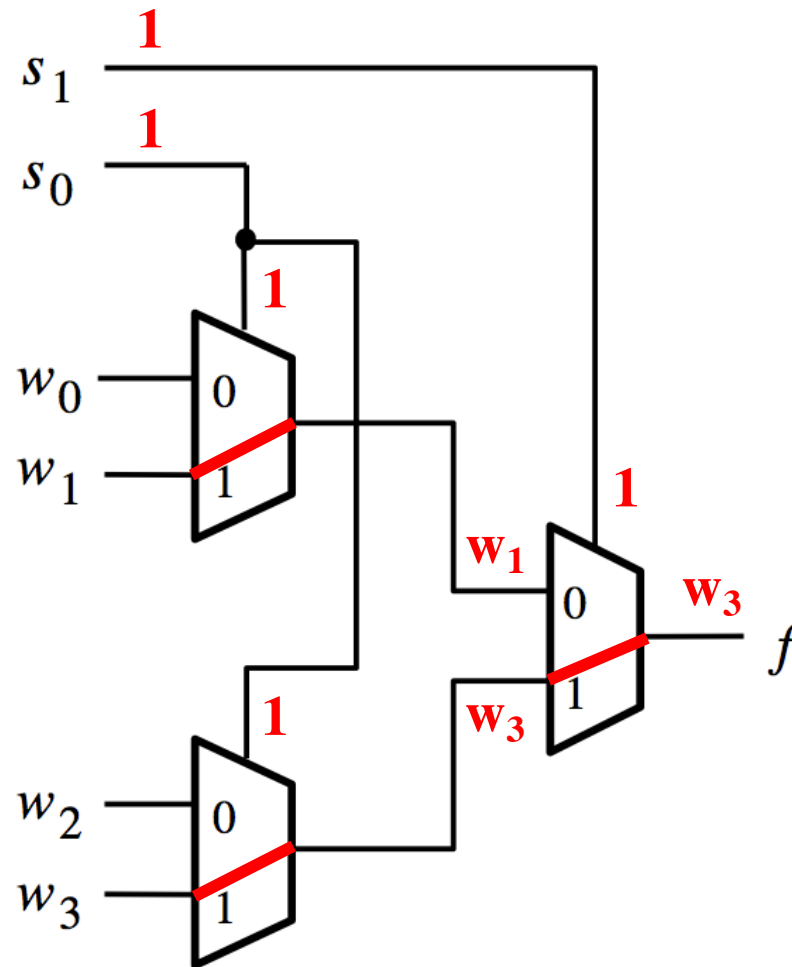

[Figure 4.3 from the textbook]


16-to-1 Multiplexer

16-1 Multiplexer

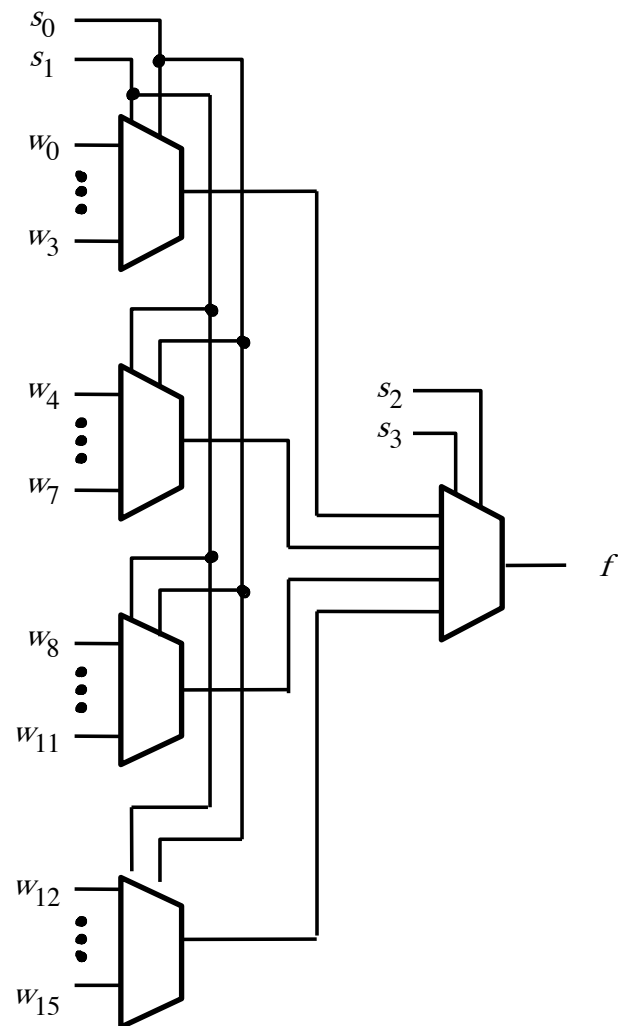


[Figure 4.4 from the textbook]

16-1 Multiplexer

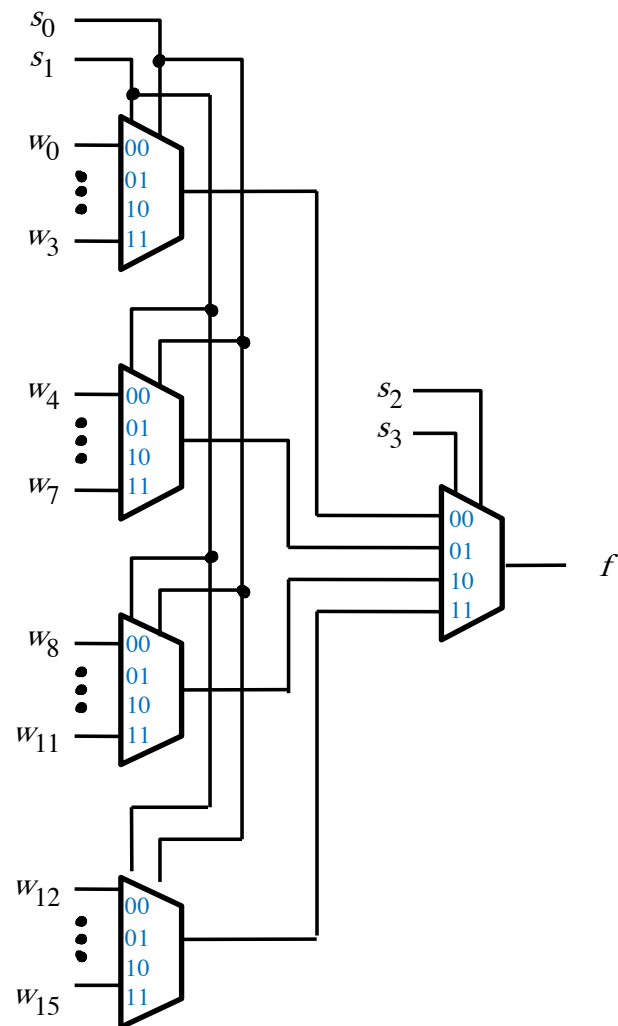


[Figure 4.4 from the textbook]


16-1 Multiplexer

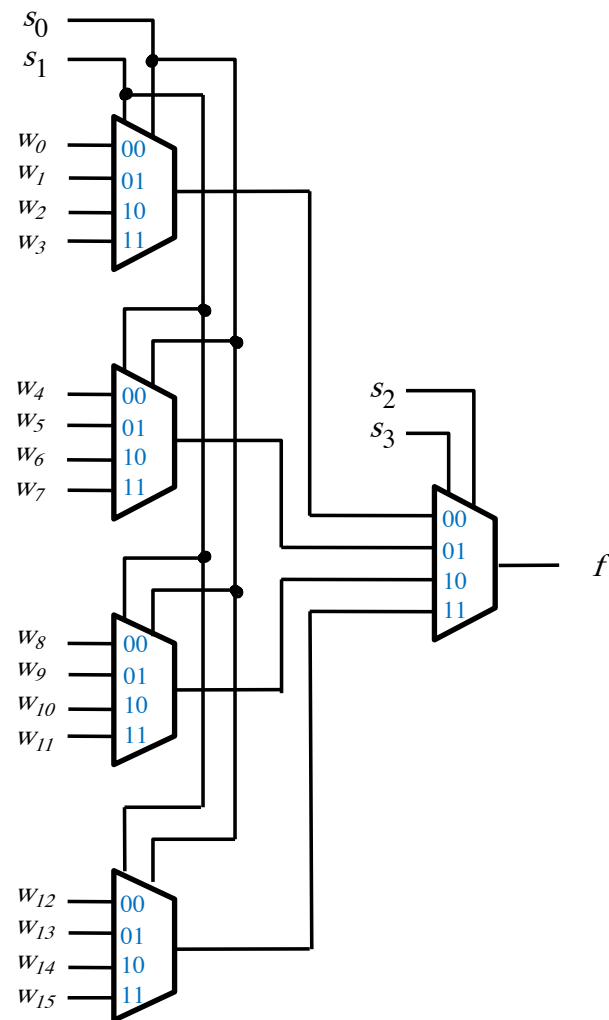

16-1 Multiplexer

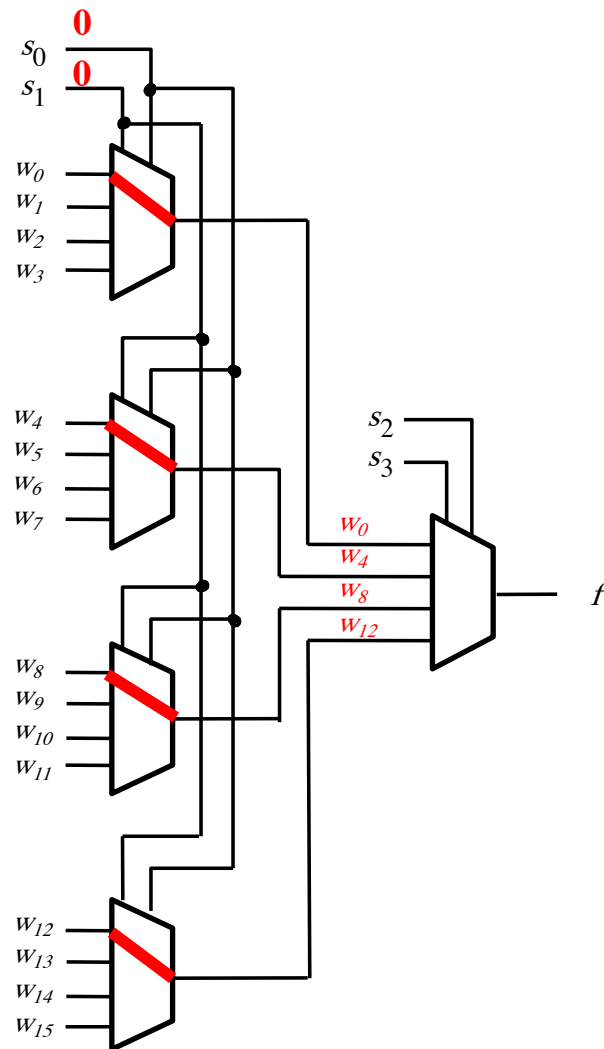


16-1 Multiplexer

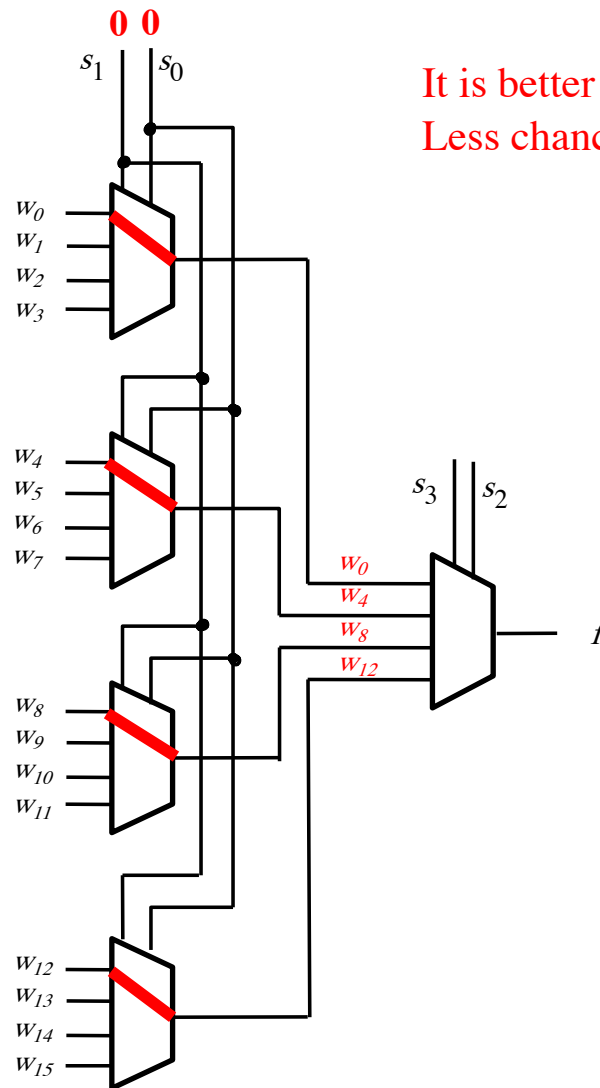


It is better to draw the select lines like this.
Less chance to confuse their order.


16-1 Multiplexer

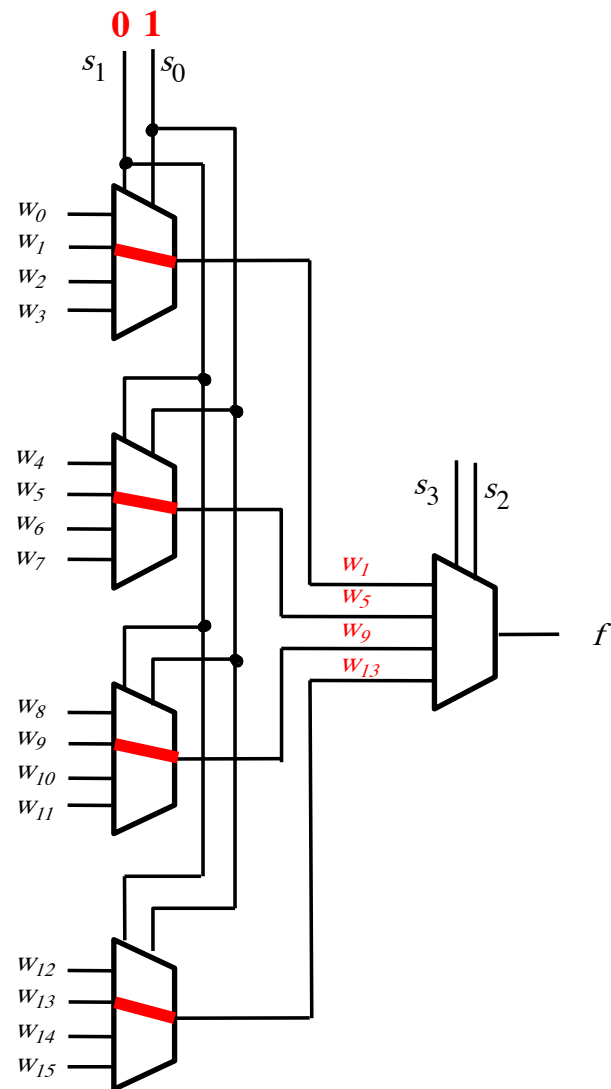


16-1 Multiplexer

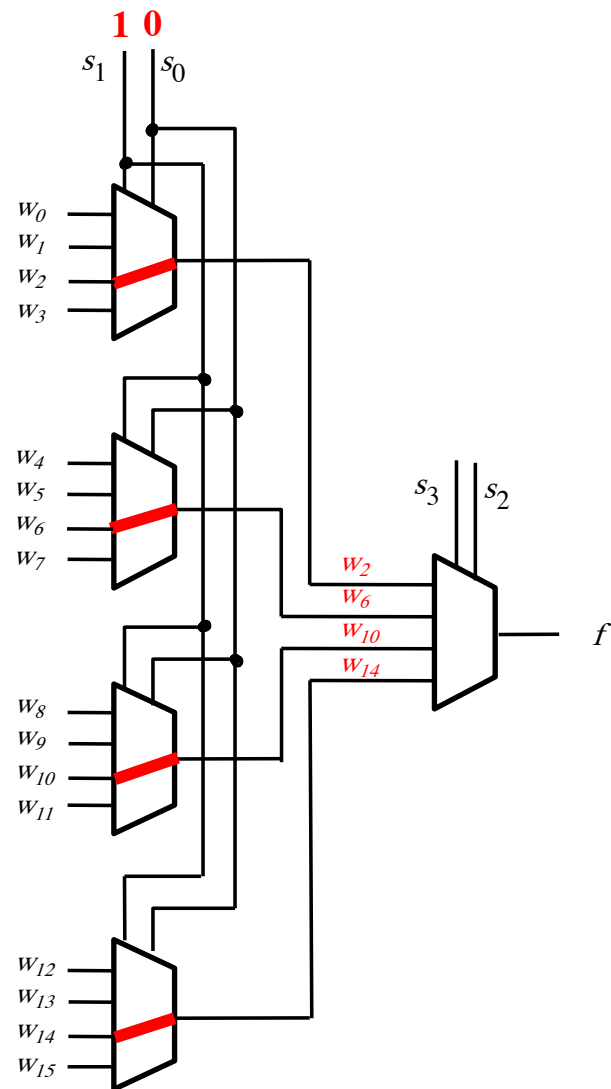


16-1 Multiplexer

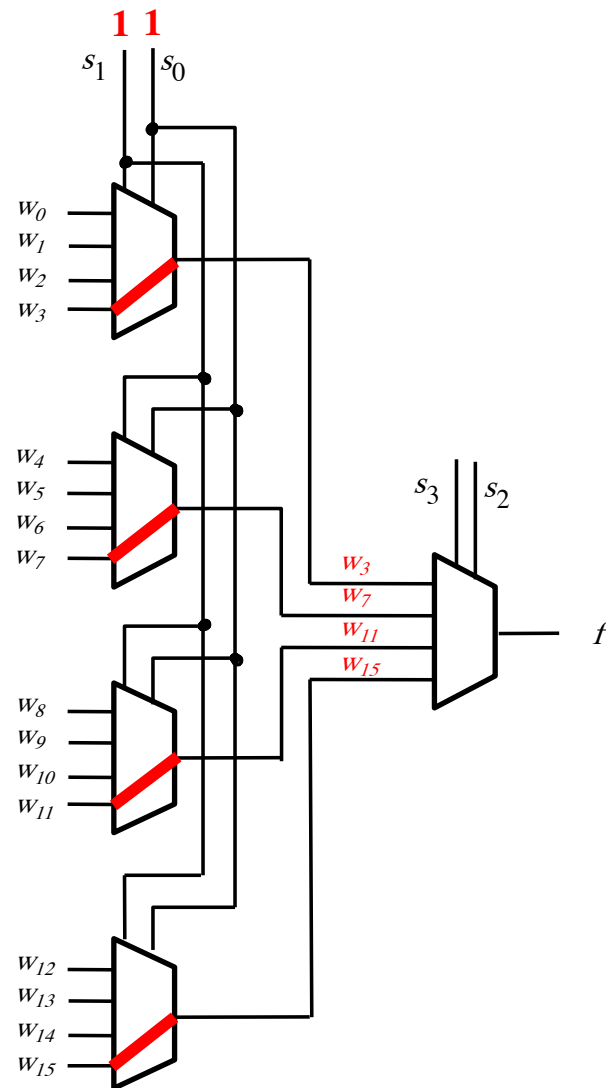


16-1 Multiplexer

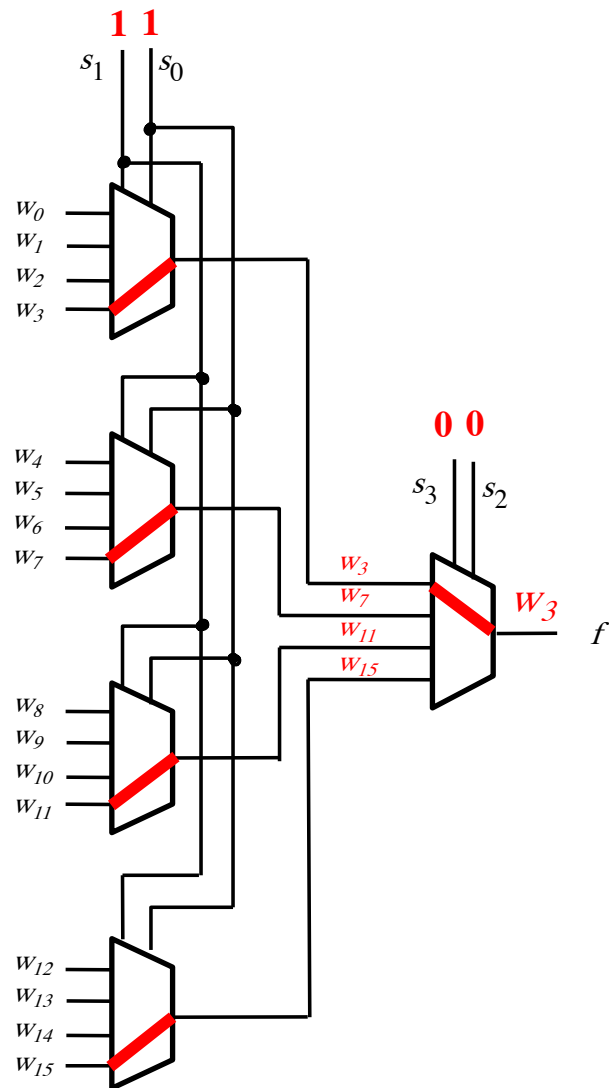


16-1 Multiplexer

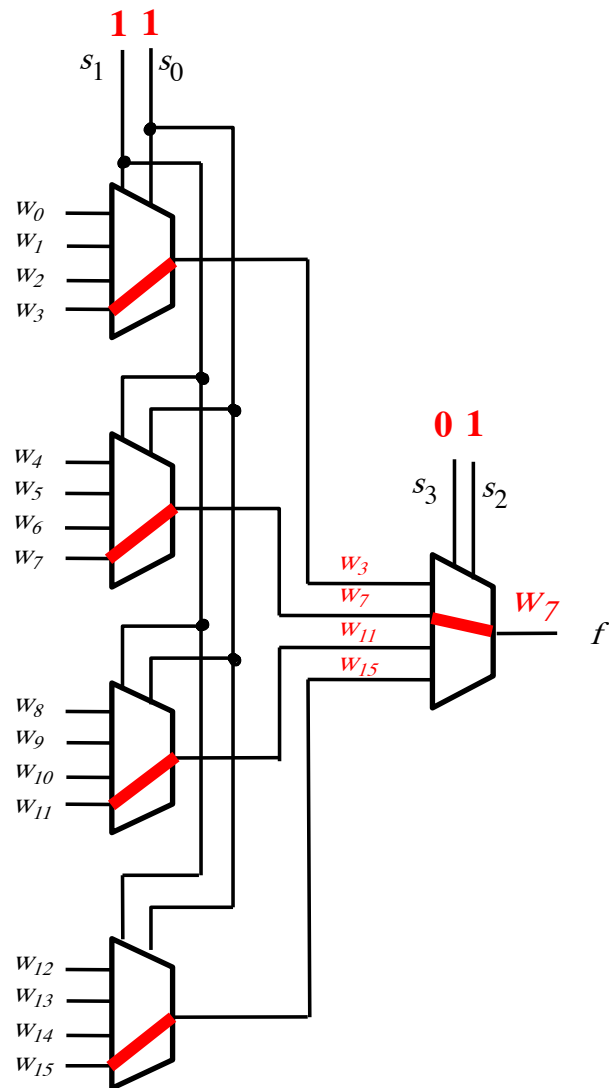

16-1 Multiplexer

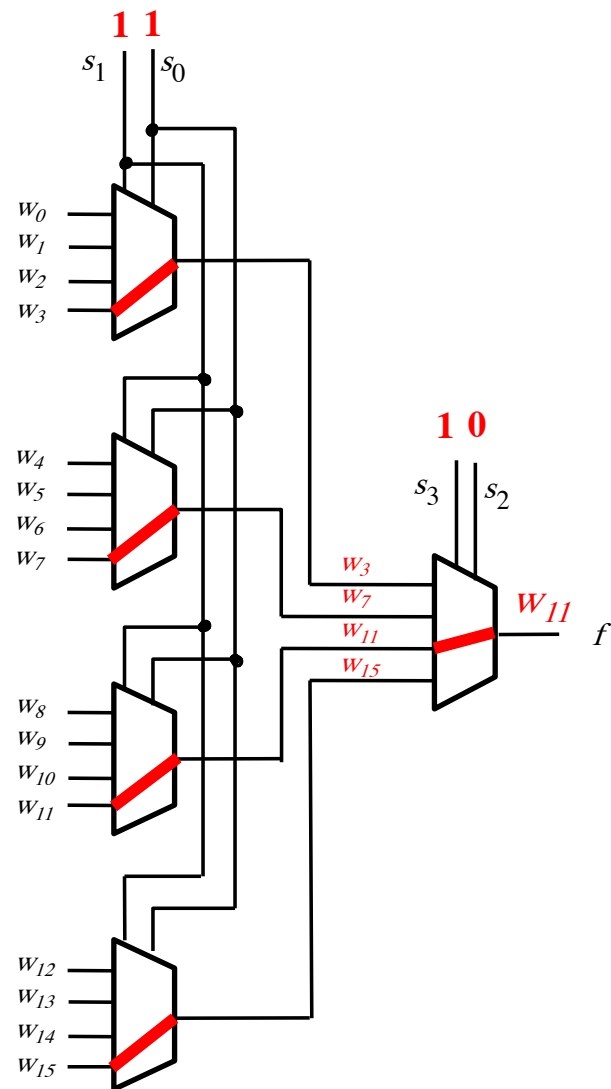

16-1 Multiplexer

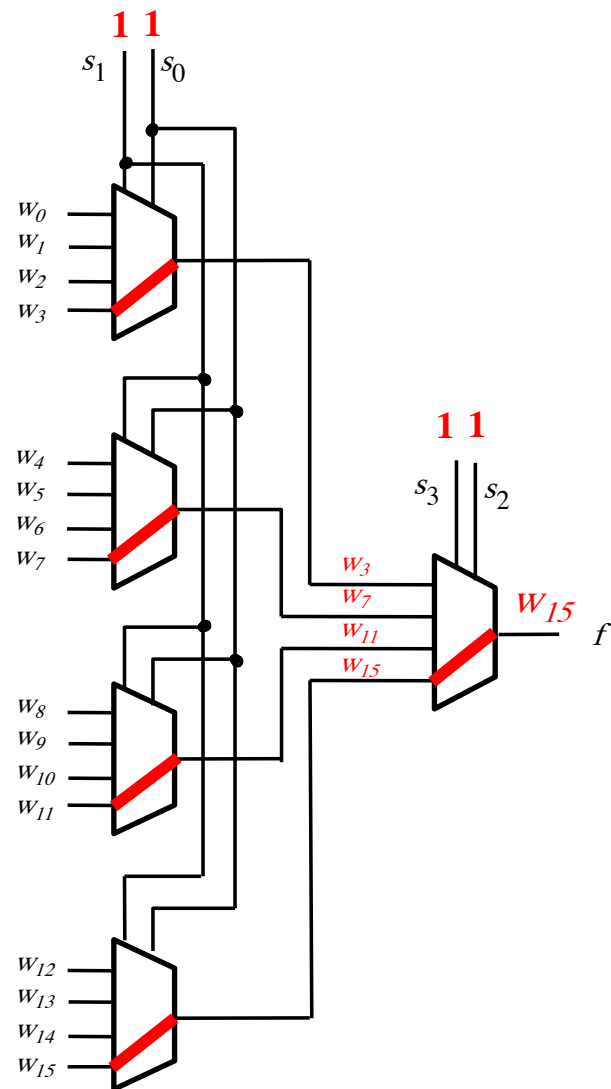





[<http://upload.wikimedia.org/wikipedia/commons/2/26/SunsetTracksCrop.JPG>]

Multiplexers Are Special


The Three Basic Logic Gates

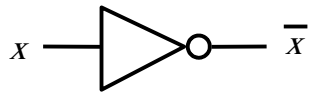

NOT gate

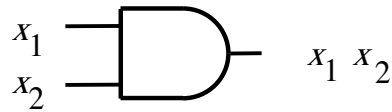


AND gate

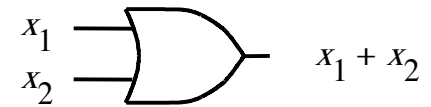


OR gate

Truth Table for NOT

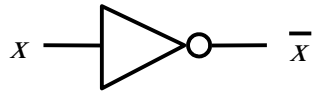


x	$\bar{x}$
0	1
1	0

Truth Table for AND

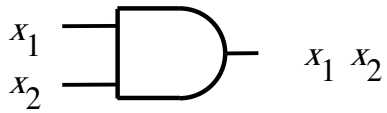


x_1	x_2	$x_1 \cdot x_2$
0	0	0
0	1	0
1	0	0
1	1	1

Truth Table for OR

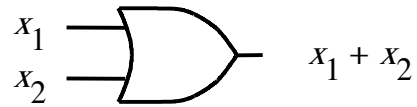


x_1	x_2	$x_1 + x_2$
0	0	0
0	1	1
1	0	1
1	1	1


Building an AND Gate with 4-to-1 Mux

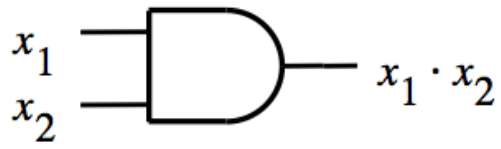

x_1	x_2	$x_1 \cdot x_2$
0	0	0
0	1	0
1	0	0
1	1	1

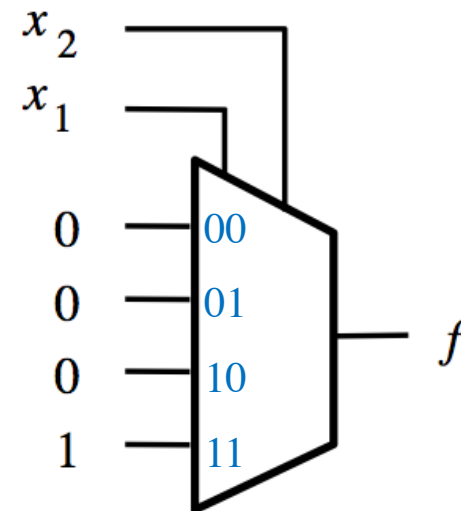


Building an AND Gate with 4-to-1 Mux

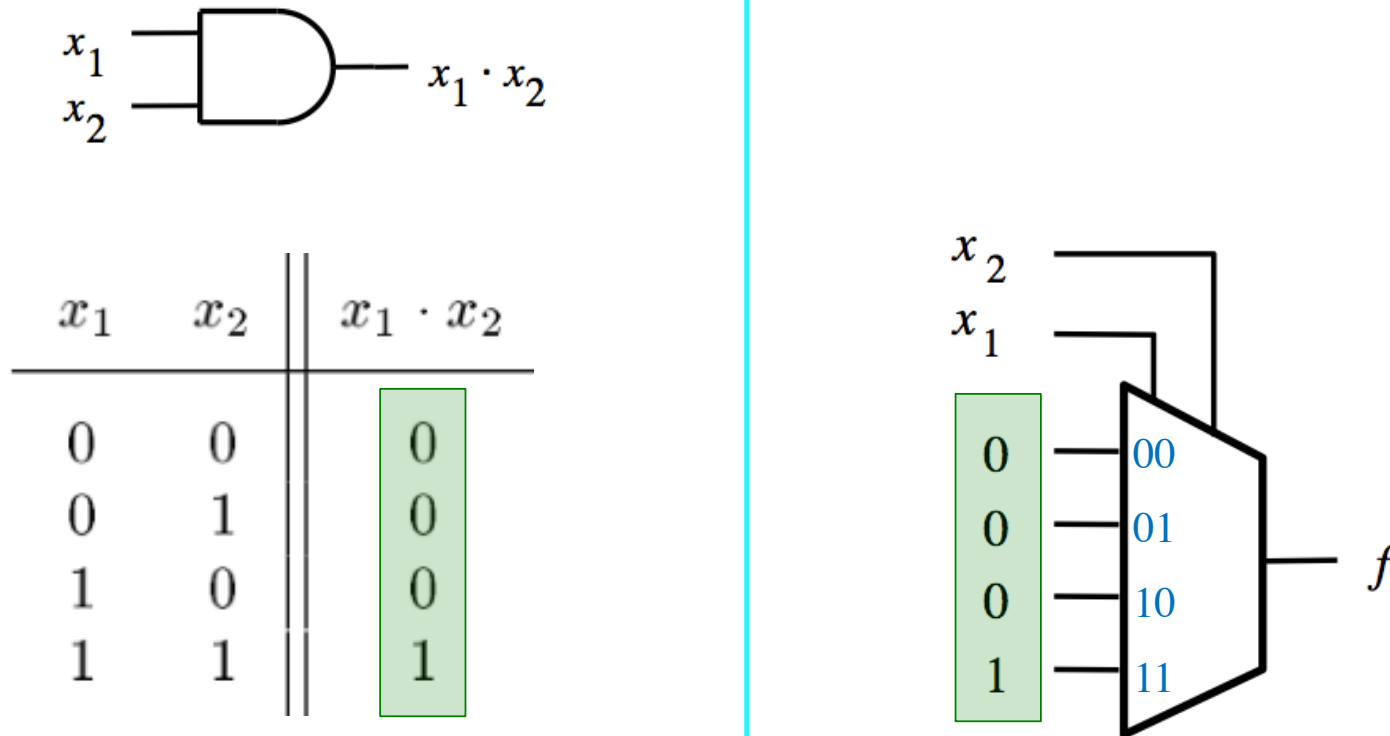

These two are the same.


Building an AND Gate with 4-to-1 Mux

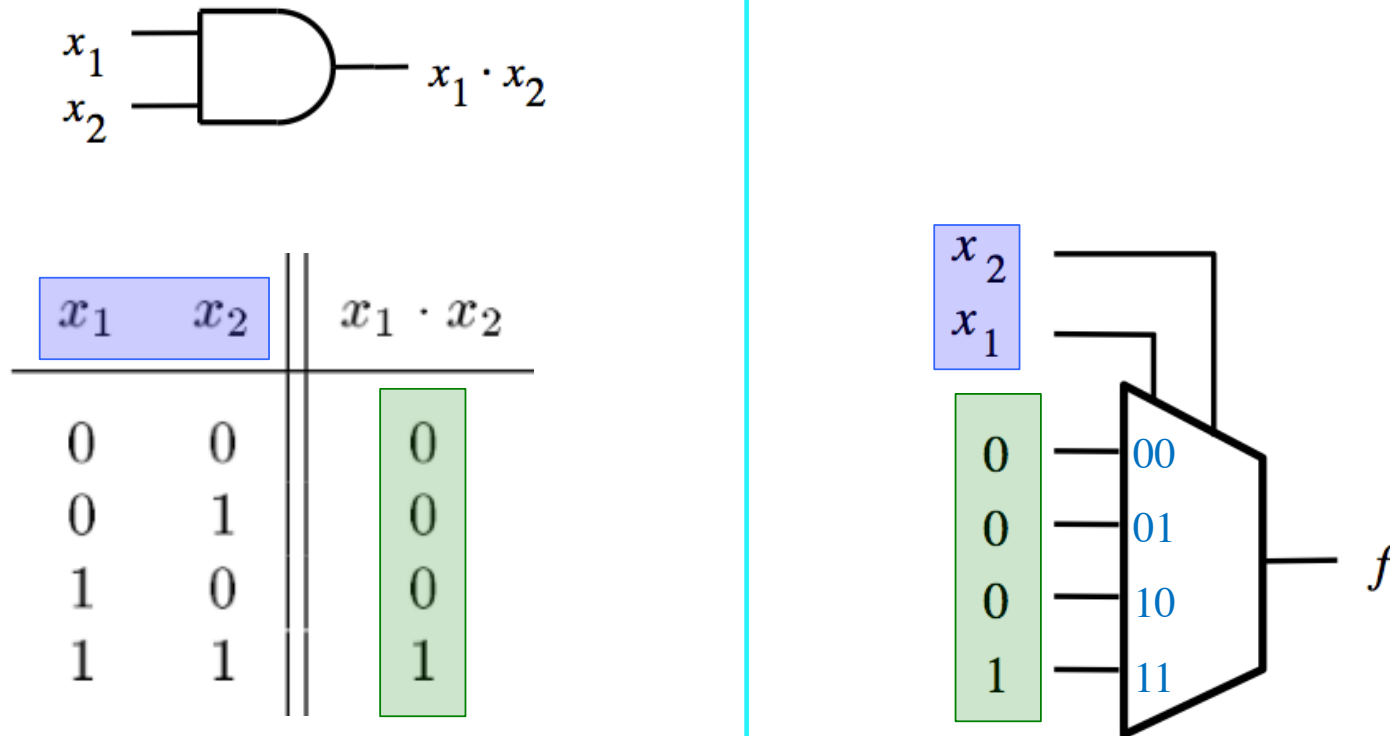


These two are the same.

And so are these two.


Building an OR Gate with 4-to-1 Mux

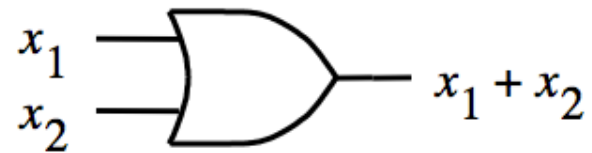


x_1	x_2	$x_1 + x_2$
0	0	0
0	1	1
1	0	1
1	1	1

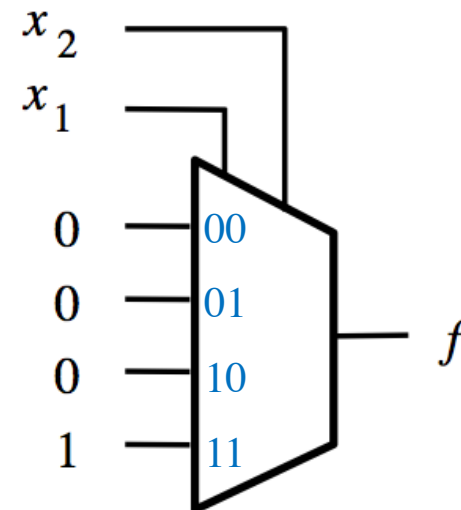

Building an OR Gate with 4-to-1 Mux

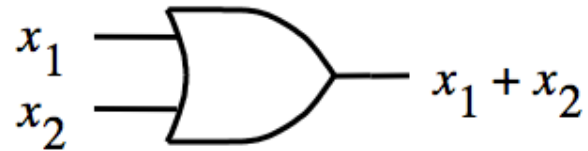


x_1	x_2	$x_1 + x_2$
0	0	0
0	1	1
1	0	1
1	1	1

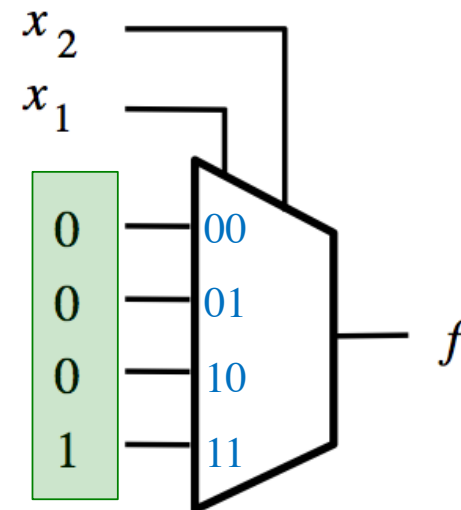


These two are the same.

Building an OR Gate with 4-to-1 Mux

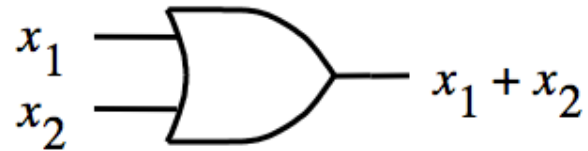


x_1	x_2	$x_1 + x_2$
0	0	0
0	1	1
1	0	1
1	1	1

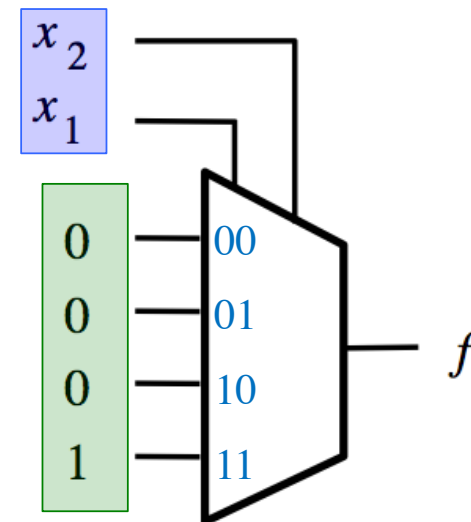


These two are the same.

And so are these two.


Building a NOT Gate with 4-to-1 Mux

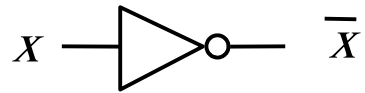


x	$\bar{x}$
0	1
1	0

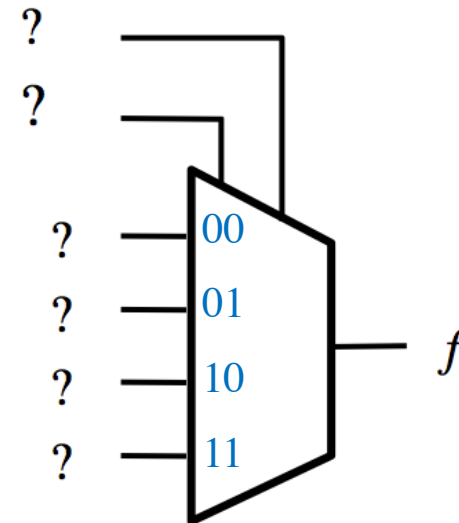

Building a NOT Gate with 4-to-1 Mux

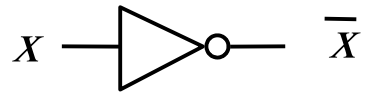


x	y	f
0	0	1
0	1	1
1	0	0
1	1	0

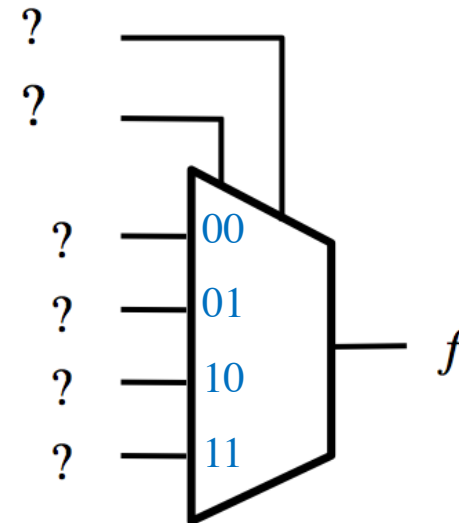


Introduce a dummy variable y .


Building a NOT Gate with 4-to-1 Mux

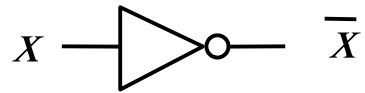


x	y	f
0	0	1
0	1	1
1	0	0
1	1	0

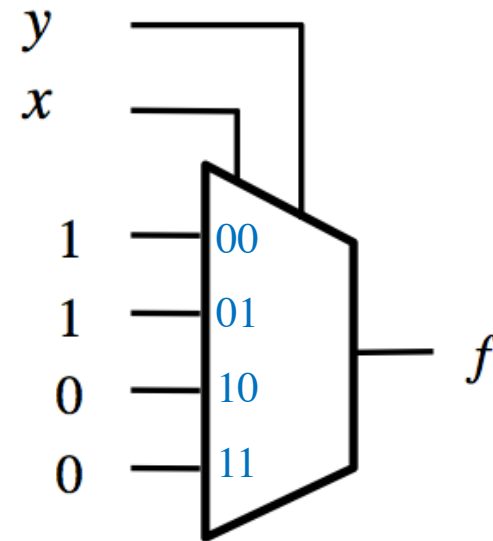

Building a NOT Gate with 4-to-1 Mux

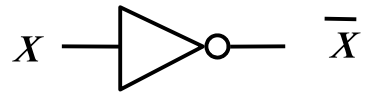


x	y	f
0	0	1
0	1	1
1	0	0
1	1	0


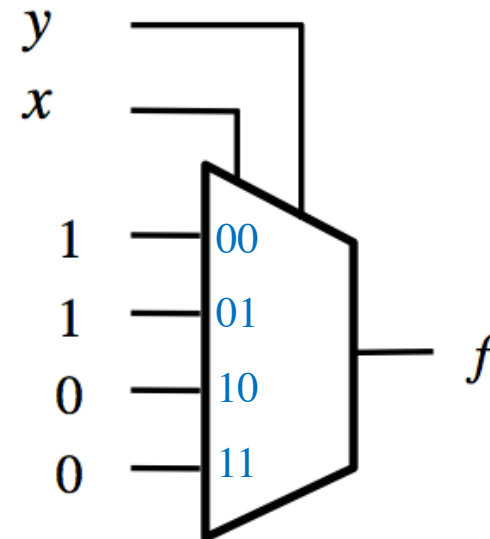


Now set y to either 0 or 1 (both will work). Why?

Building a NOT Gate with 4-to-1 Mux

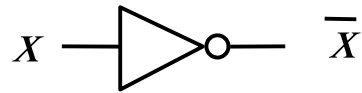

x	$\bar{x}$
0	1
1	0

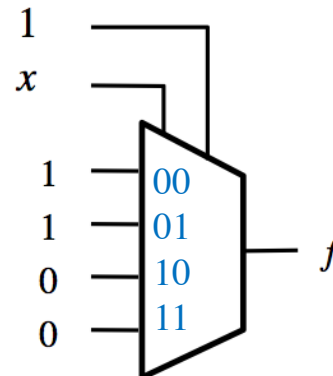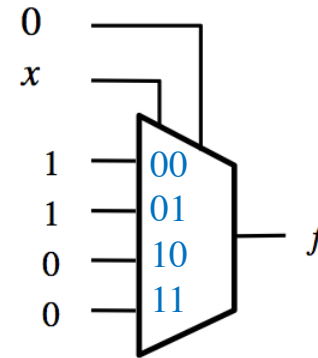


Two alternative solutions.


Implications

**Any Boolean function can be implemented
using only 4-to-1 multiplexers!**


Building an AND Gate with 2-to-1 Mux

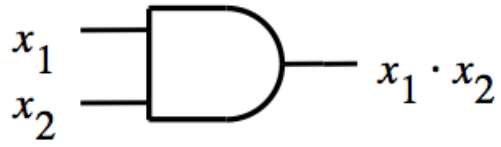


x_1	x_2	$x_1 \cdot x_2$
0	0	0
0	1	0
1	0	0
1	1	1

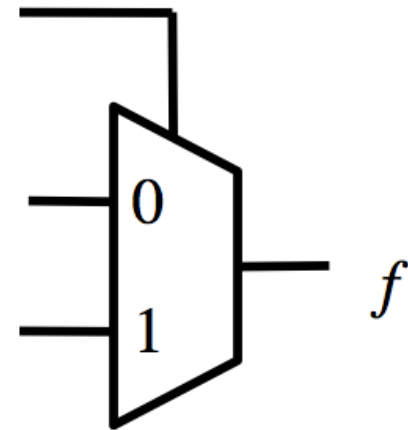


Building an AND Gate with 2-to-1 Mux

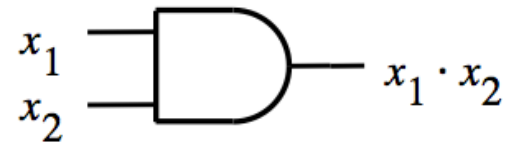

x_1	x_2	$x_1 \cdot x_2$
0	0	0
0	1	0
1	0	0
1	1	1

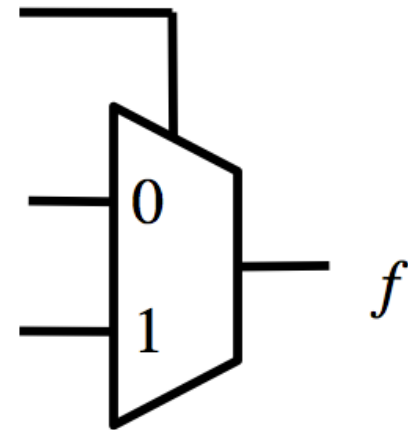


Building an AND Gate with 2-to-1 Mux

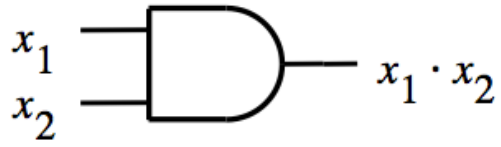


x_1	x_2	$x_1 \cdot x_2$
0	0	0
0	1	0
1	0	0
1	1	1

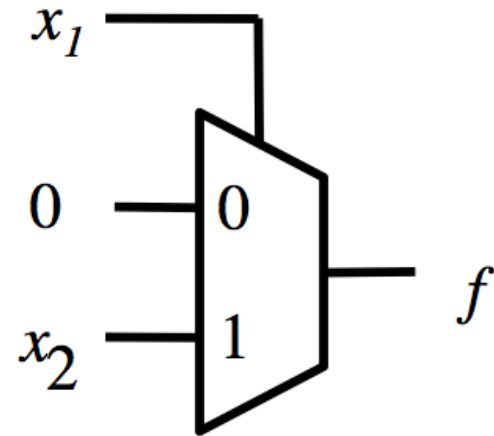
Red annotations: A red vertical line separates the input columns. A red horizontal line is under the row (1, 0). Red curly braces group the output values: the first two rows (0, 0) and (0, 1) are grouped and labeled with a red '0'; the last two rows (1, 0) and (1, 1) are grouped and labeled with a red x_2 .




Building an OR Gate with 2-to-1 Mux

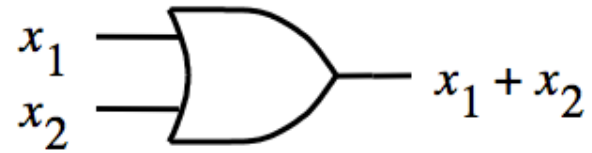


x_1	x_2	$x_1 + x_2$
0	0	0
0	1	1
1	0	1
1	1	1

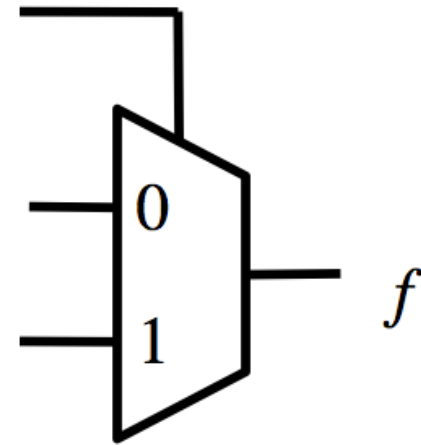


Building an OR Gate with 2-to-1 Mux

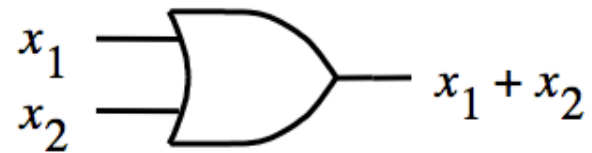

x_1	x_2	$x_1 + x_2$
0	0	0
0	1	1
1	0	1
1	1	1

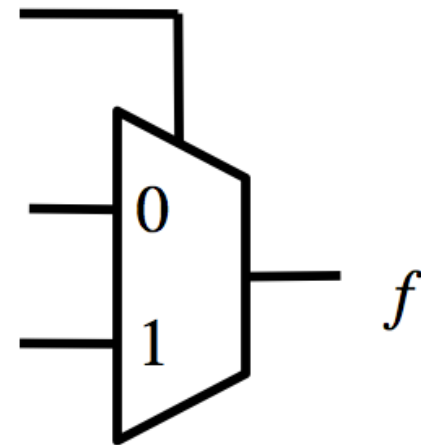


Building an OR Gate with 2-to-1 Mux

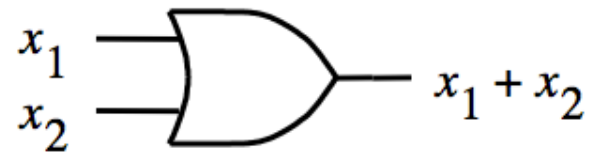


x_1	x_2	$x_1 + x_2$
0	0	0
0	1	1
1	0	1
1	1	1

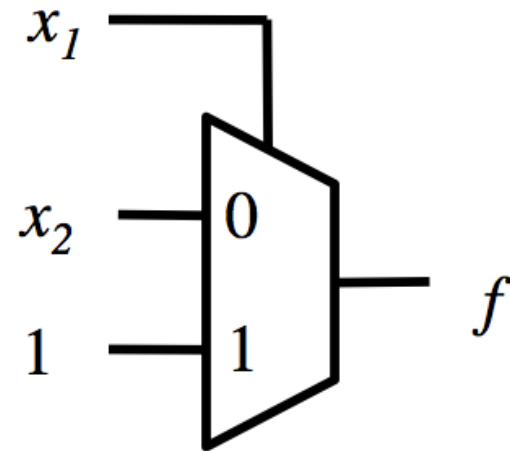
Red annotations: A vertical red line separates the input columns. A horizontal red line separates the first two rows from the last two. Red curly braces on the right group the output values: the first two rows are grouped and labeled x_2 , and the last two rows are grouped and labeled 1 .




Building a NOT Gate with 2-to-1 Mux

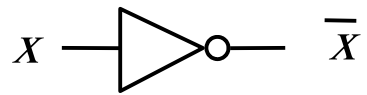


x	$\overline{x}$
0	1
1	0

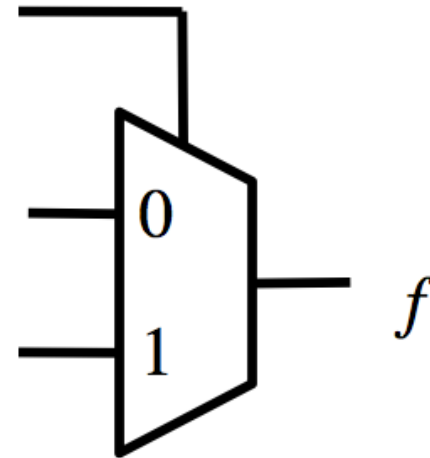

Building a NOT Gate with 2-to-1 Mux

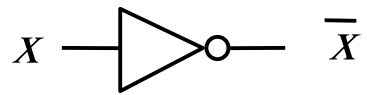


x	$\overline{x}$
0	1
1	0

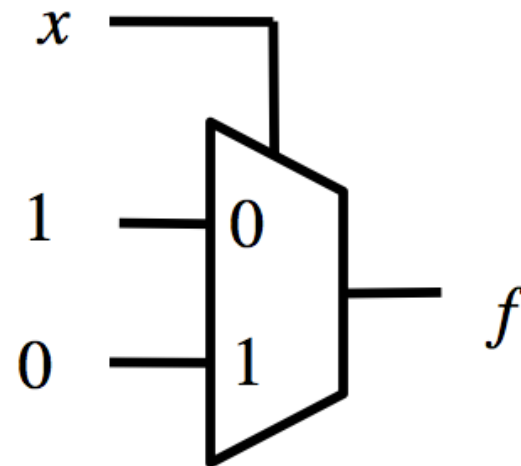


Implications

**Any Boolean function can be implemented
using only 2-to-1 multiplexers!**


AND

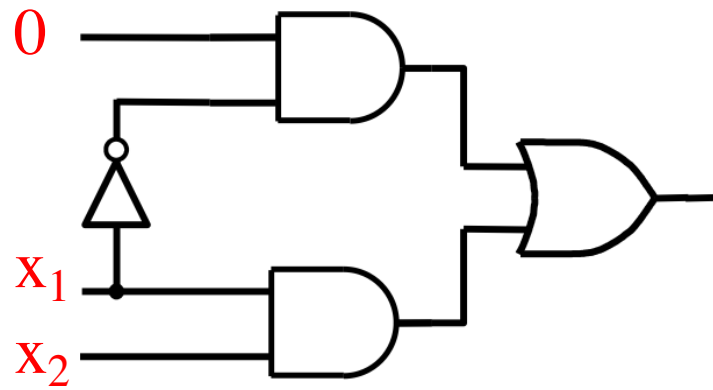


OR

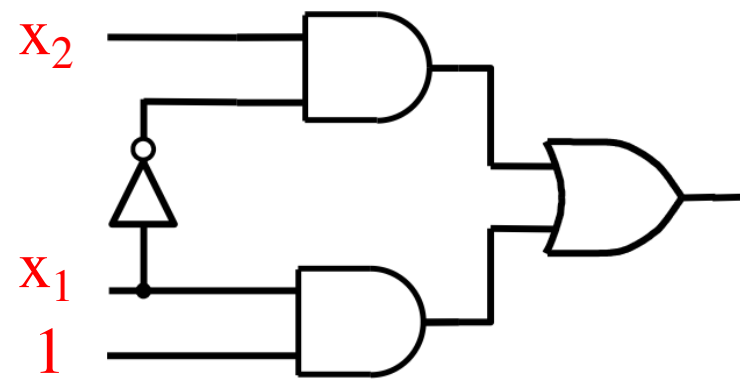


NOT

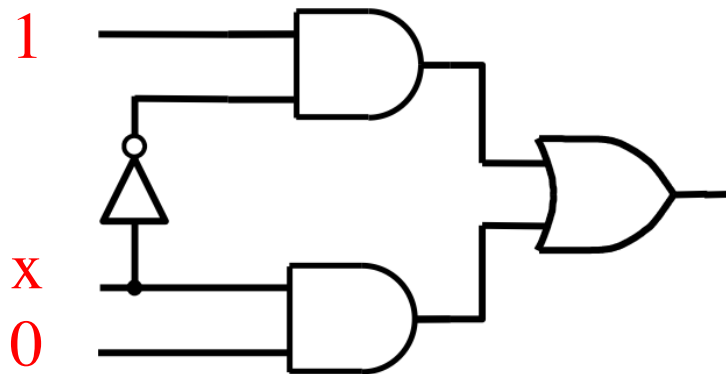


AND

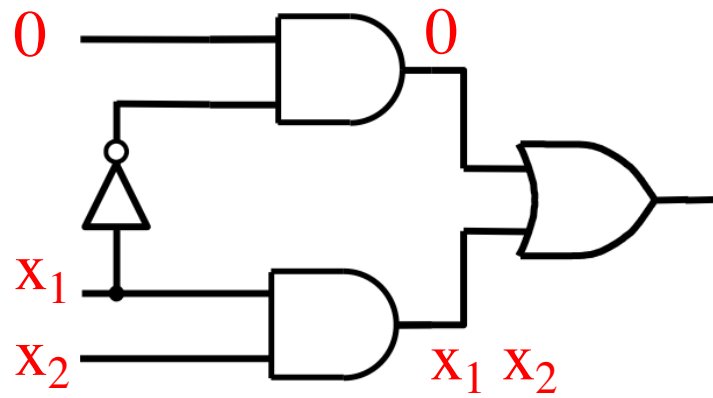


OR

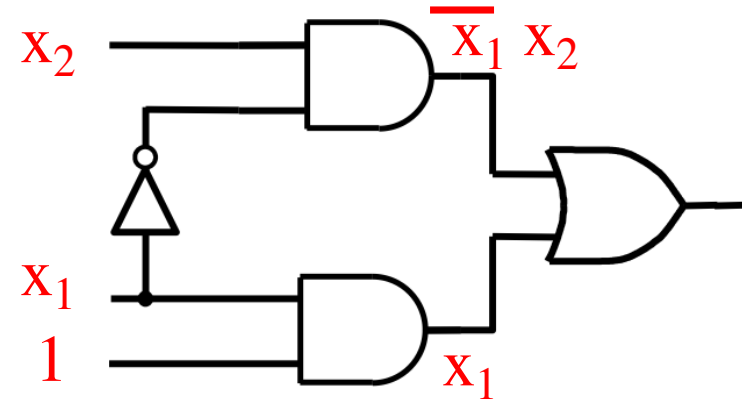


NOT

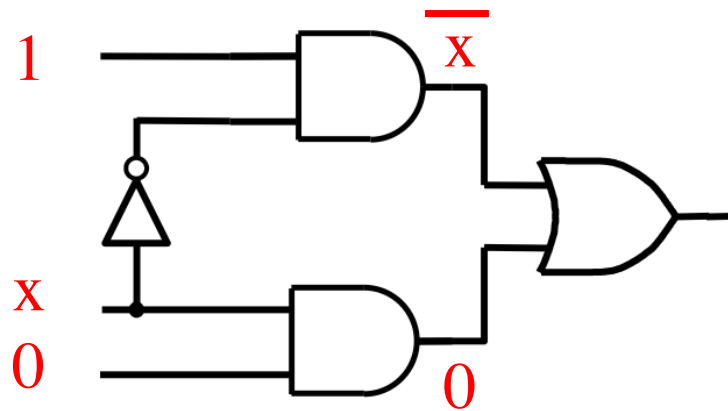


AND

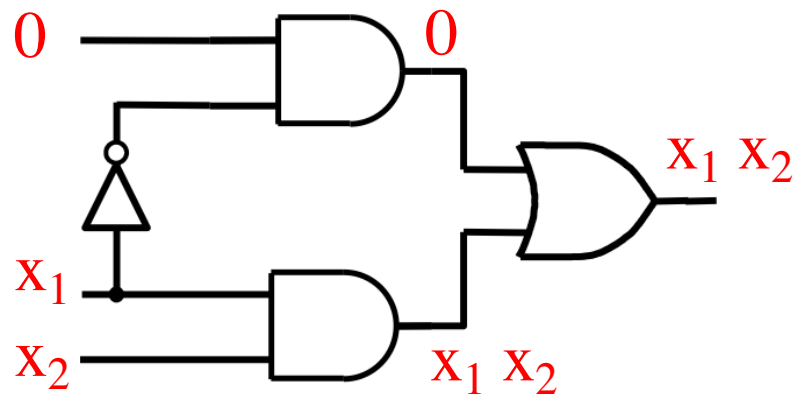

OR

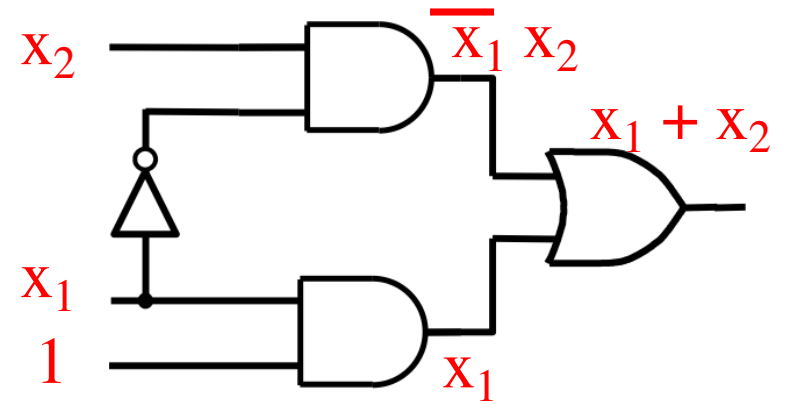


NOT

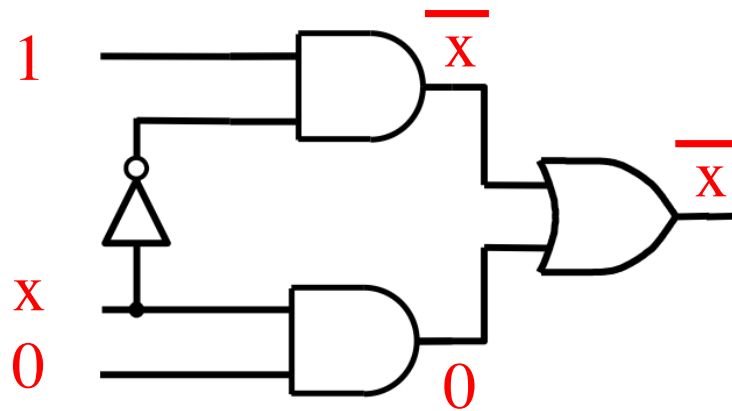



Switch Circuit

2 x 2 Crossbar switch

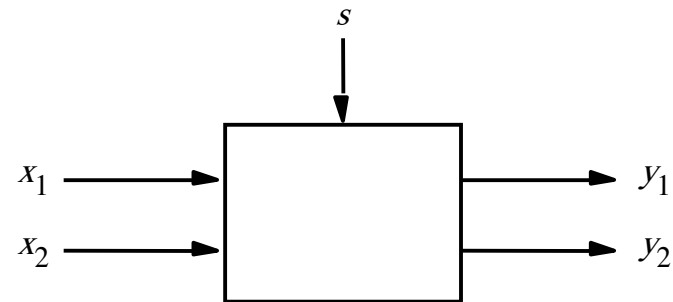


[Figure 4.5a from the textbook]

2 x 2 Crossbar switch

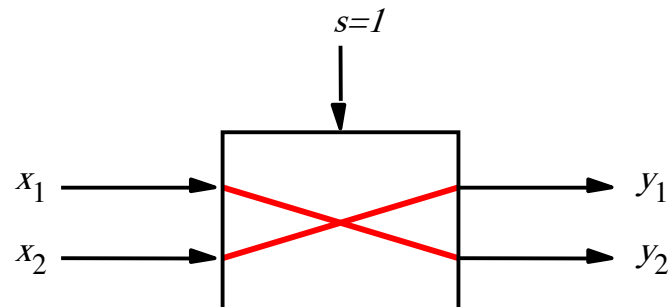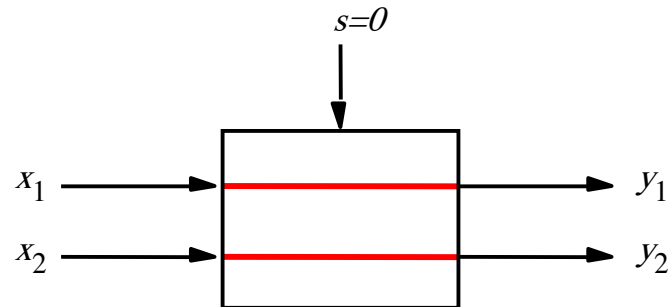


Implementation of a 2 x 2 crossbar switch with multiplexers

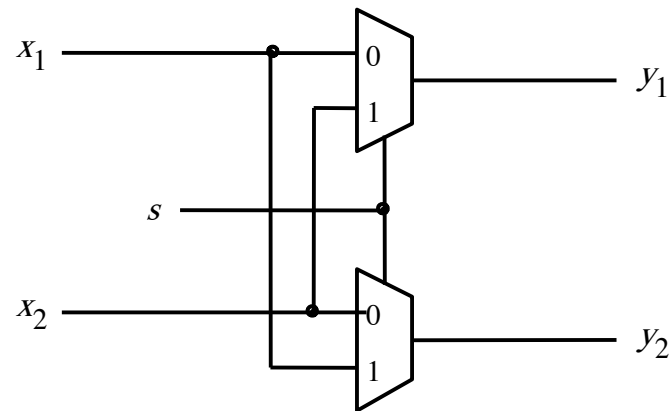


[Figure 4.5b from the textbook]

Implementation of a 2 x 2 crossbar switch with multiplexers

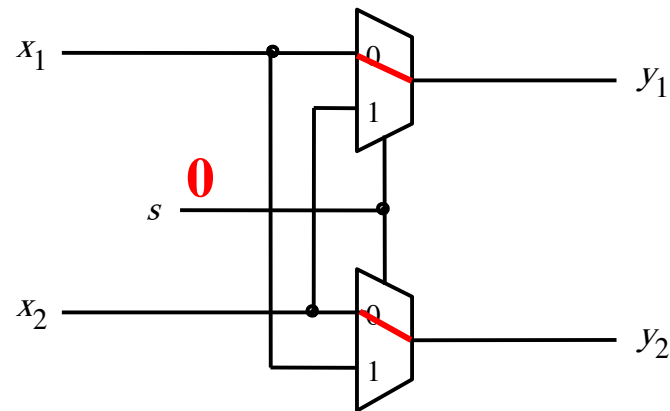


[Figure 4.5b from the textbook]

Implementation of a 2 x 2 crossbar switch with multiplexers

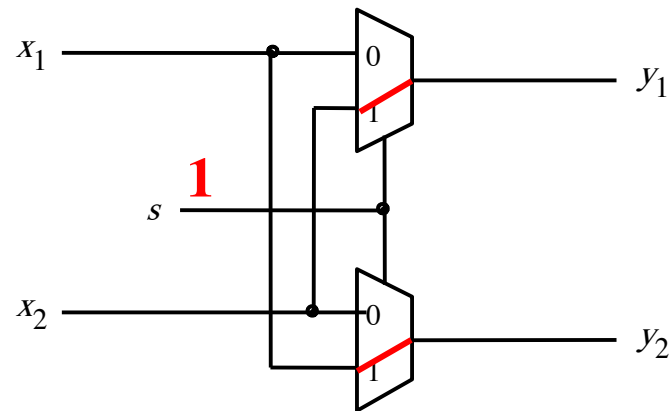


[Figure 4.5b from the textbook]

Implementation of a 2 x 2 crossbar switch with multiplexers

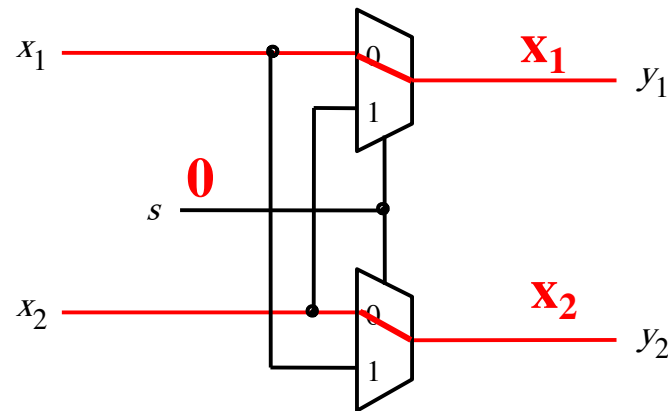



[Figure 4.5b from the textbook]

Implementation of a 2 x 2 crossbar switch with multiplexers

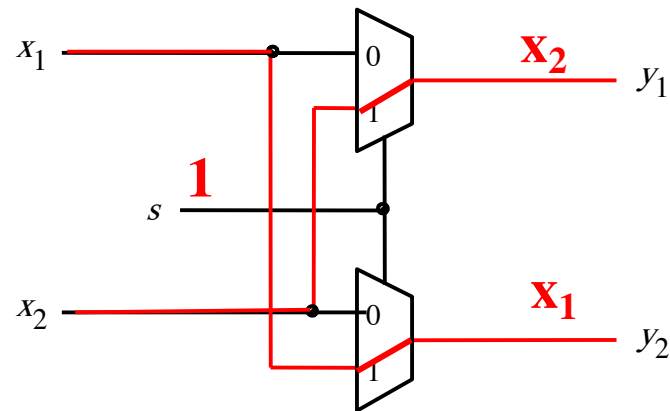


[Figure 4.5b from the textbook]

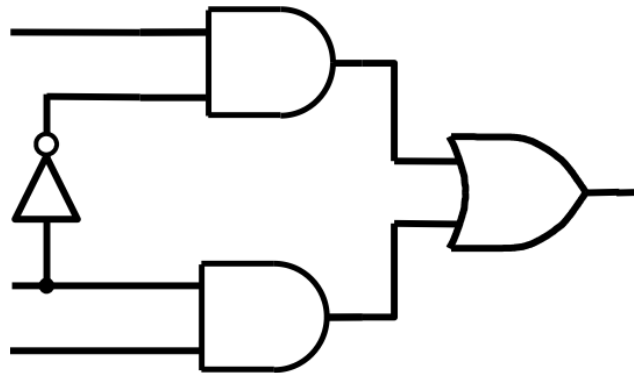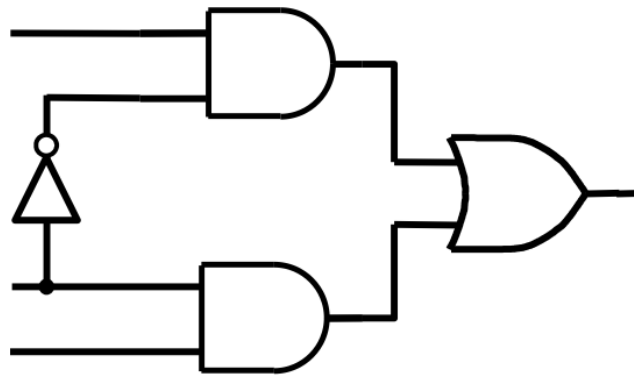Implementation of a 2 x 2 crossbar switch with multiplexers



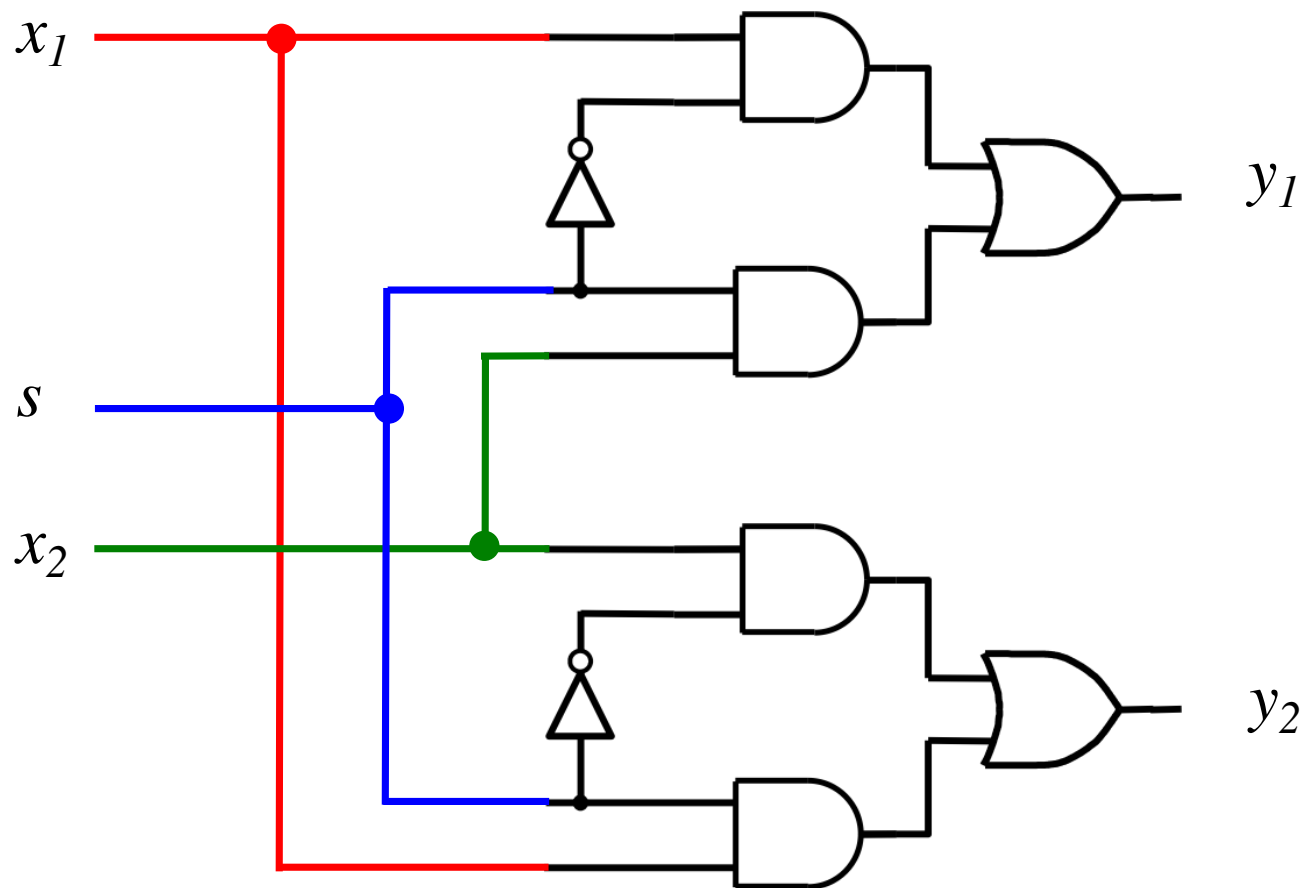Implementation of a 2 x 2 crossbar switch with multiplexers




Synthesis of Logic Circuits Using Multiplexers

Synthesis of Logic Circuits Using Multiplexers

**Note: This method is NOT the same as simply replacing each logic gate with a multiplexer!
It is a lot more efficient.**

The XOR Logic Gate

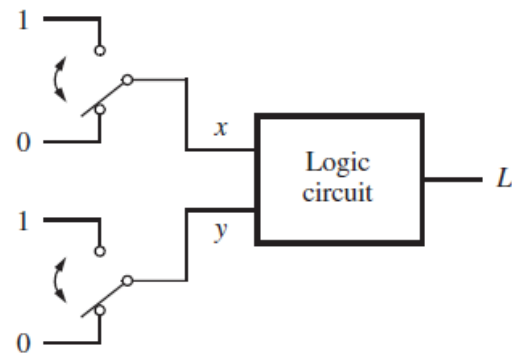


(a) Two switches that control a light

x	y	L
0	0	0
0	1	1
1	0	1
1	1	0

(b) Truth table


The XOR Logic Gate

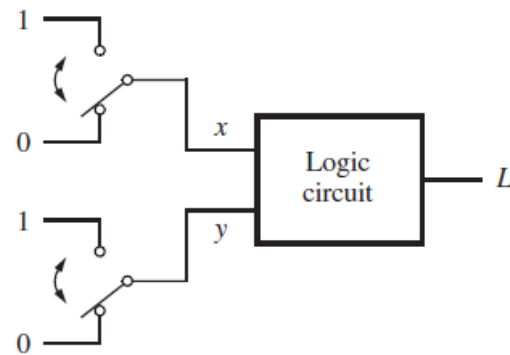

(a) Two switches that control a light

x	y	L
0	0	0
0	1	1
1	0	1
1	1	0

(b) Truth table

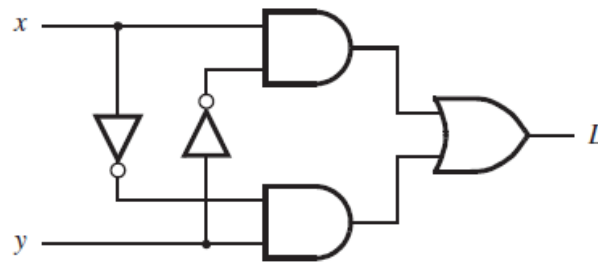


(c) Logic network



(d) XOR gate symbol

Implementation of a logic function with a 4-to-1 multiplexer

w_1	w_2	f
0	0	0
0	1	1
1	0	1
1	1	0

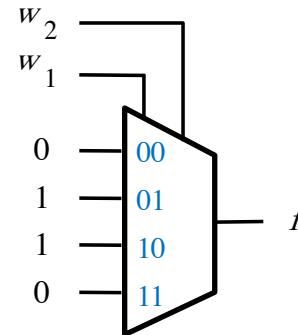


[Figure 4.6a from the textbook]

Implementation of the same logic function with a 2-to-1 multiplexer


w_1	w_2	f		w_1	f
0	0	0	}	0	w_2
0	1	1		1	$\overline{w_2}$
1	0	1	}		
1	1	0			

(b) Modified truth table

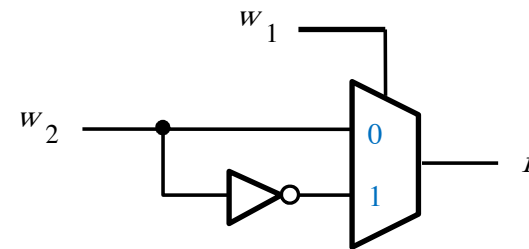


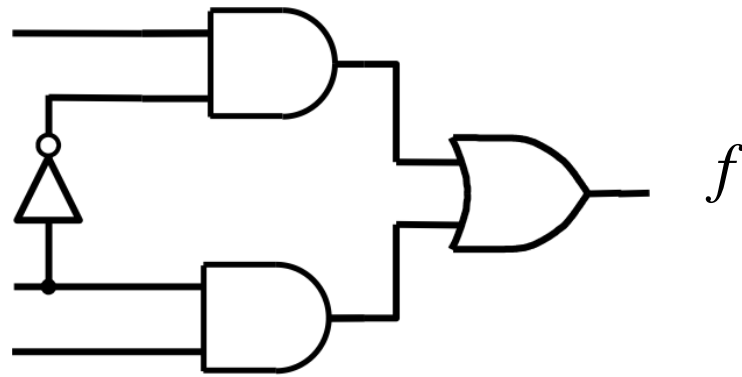(c) Circuit


Implementation of the XOR Logic Gate with a 2-to-1 multiplexer and one NOT



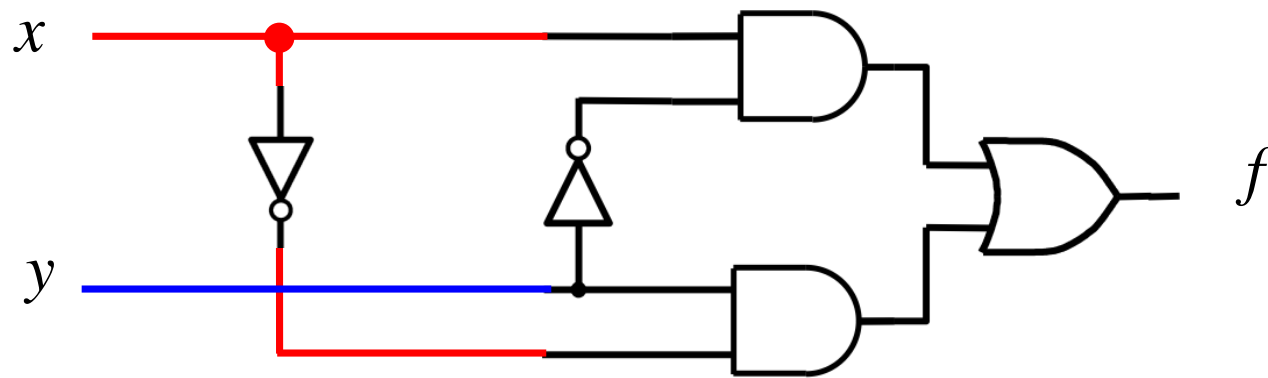
Implementation of the XOR Logic Gate with a 2-to-1 multiplexer and one NOT





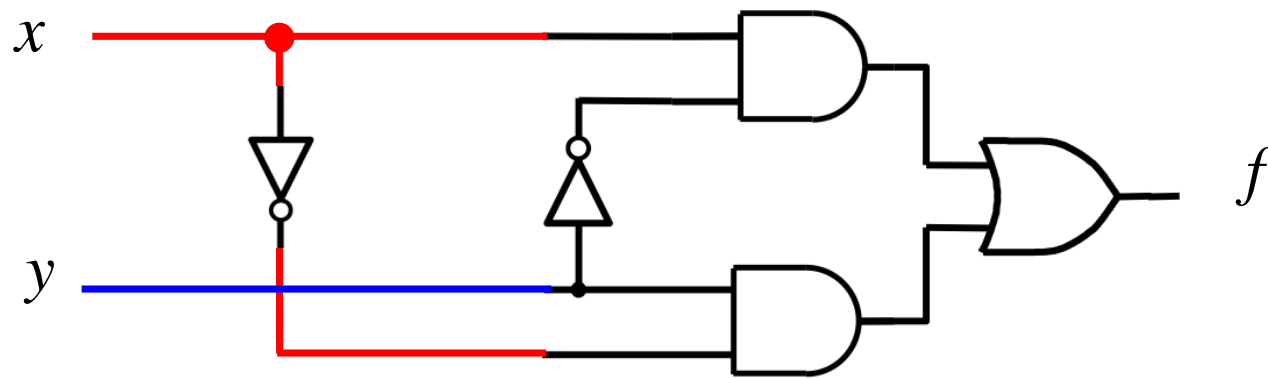
Implementation of the XOR Logic Gate with a 2-to-1 multiplexer and one NOT



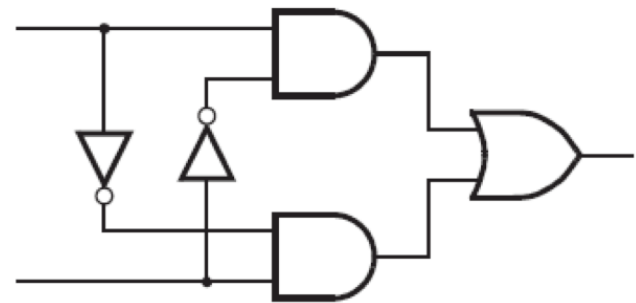These two circuits are equivalent
(the wires of the bottom AND gate are flipped)



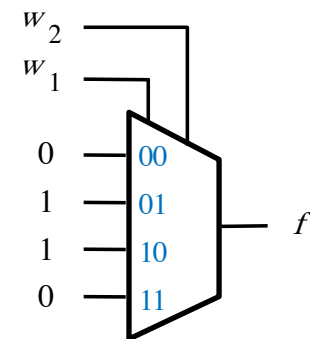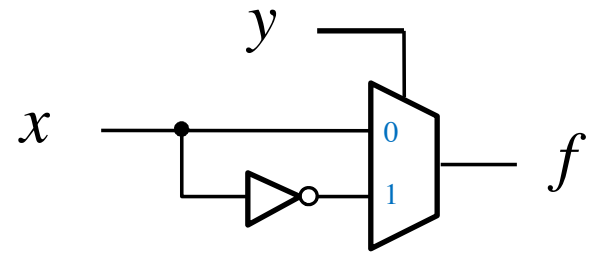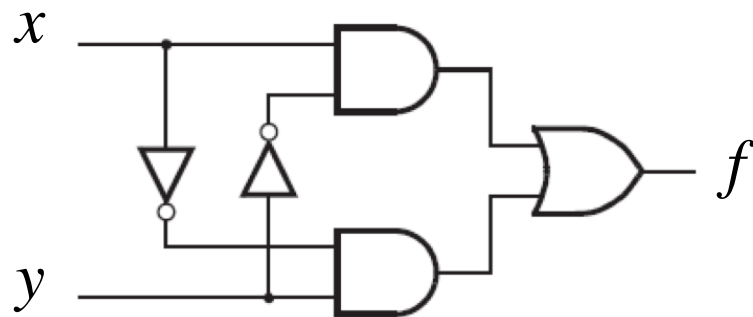**In other words,
all four of these are equivalent!**



Implementation of another logic function

w_1	w_2	w_3	f
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1


[Figure 4.7 from the textbook]

Implementation of another logic function

w_1	w_2	w_3	f
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

[Figure 4.7 from the textbook]


Implementation of another logic function

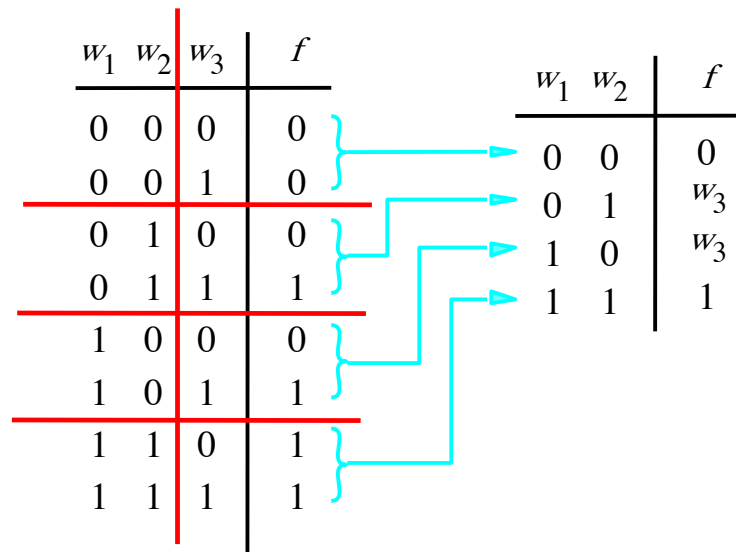

[Figure 4.7 from the textbook]

Implementation of another logic function

w_1	w_2	w_3	f		w_1	w_2	f
0	0	0	0	}	0	0	0
0	0	1	0		0	1	w_3
0	1	0	0	}	1	0	w_3
0	1	1	1		1	1	1
1	0	0	0	}			
1	0	1	1				
1	1	0	1	}			
1	1	1	1				

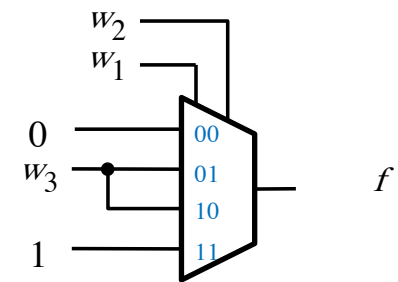

[Figure 4.7 from the textbook]

Another Example (3-input XOR)

Implementation of 3-input XOR with 2-to-1 Multiplexers

w_1	w_2	w_3	f
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

[Figure 4.8a from the textbook]

Implementation of 3-input XOR with 2-to-1 Multiplexers

w_1	w_2	w_3	f
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1


Red annotations in the original image:

- A red vertical line separates the w_1 column from the w_2, w_3 columns.
- A red horizontal line separates the $w_1 = 0$ rows from the $w_1 = 1$ rows.
- Red curly braces group the output values for $w_1 = 0$ and $w_1 = 1$.
 - For $w_1 = 0$, the outputs are 0, 1, 1, 0, which are grouped by the expression $w_2 \oplus w_3$.
 - For $w_1 = 1$, the outputs are 1, 0, 0, 1, which are grouped by the expression $\overline{w_2 \oplus w_3}$.

Implementation of 3-input XOR with 2-to-1 Multiplexers

w_1	w_2	w_3	f
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

(a) Truth table

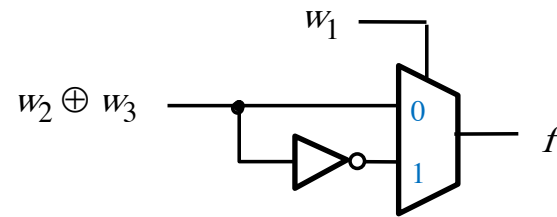


(b) Circuit

Implementation of 3-input XOR with 2-to-1 Multiplexers

w_1	w_2	w_3	f
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

(a) Truth table

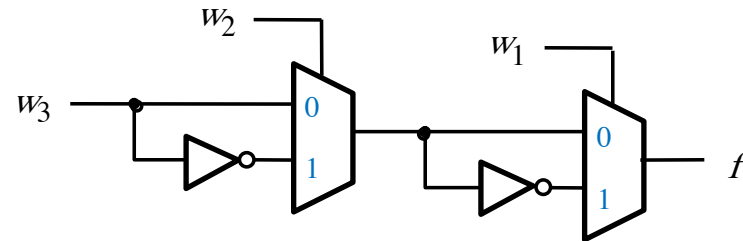

(b) Circuit

Implementation of 3-input XOR with a 4-to-1 Multiplexer

w_1	w_2	w_3	f
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

[Figure 4.9a from the textbook]

Implementation of 3-input XOR with a 4-to-1 Multiplexer

w_1	w_2	w_3	f
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

[Figure 4.9a from the textbook]

Implementation of 3-input XOR with a 4-to-1 Multiplexer


w_1	w_2	w_3	f	
0	0	0	0	} w_3
0	0	1	1	
0	1	0	1	} $\overline{w_3}$
0	1	1	0	
1	0	0	1	} $\overline{w_3}$
1	0	1	0	
1	1	0	0	} w_3
1	1	1	1	

[Figure 4.9a from the textbook]

Implementation of 3-input XOR with a 4-to-1 Multiplexer

w_1	w_2	w_3	f
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

(a) Truth table

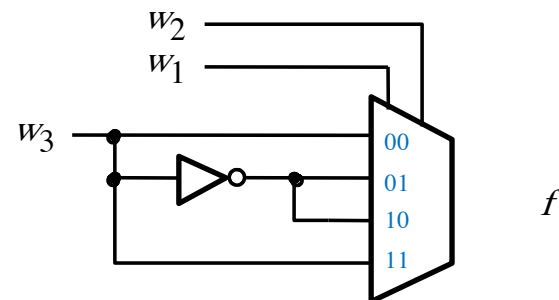

(b) Circuit

Circuit Synthesis with Multiplexers Using Shannon's Expansion

Three-input majority function

w_1	w_2	w_3	f
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

[Figure 4.10a from the textbook]

Three-input majority function

w_1	w_2	w_3	f
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

SOP expression for f :

$$f = \bar{w}_1 w_2 w_3 + w_1 \bar{w}_2 w_3 + w_1 w_2 \bar{w}_3 + w_1 w_2 w_3$$

Three-input majority function

w_1	w_2	w_3	f
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

w_1	f
0	0
1	1

Divide-and-conquer method (a.k.a., Shannon's expansion)

Three-input majority function

w_1	w_2	w_3	f								
0	0	0	0	}	<table><tr><th>w_1</th><th>f</th></tr><tr><td>0</td><td>$w_2 w_3$</td></tr><tr><td>1</td><td>$w_2 + w_3$</td></tr></table>	w_1	f	0	$w_2 w_3$	1	$w_2 + w_3$
w_1	f										
0	$w_2 w_3$										
1	$w_2 + w_3$										
0	0	1	0								
0	1	0	0								
0	1	1	1								
1	0	0	0	}							
1	0	1	1								
1	1	0	1								
1	1	1	1								


[Figure 4.10a from the textbook]

Three-input majority function

w_1	w_2	w_3	f
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

w_1	f
0	$w_2 w_3$
1	$w_2 + w_3$

(b) Truth table

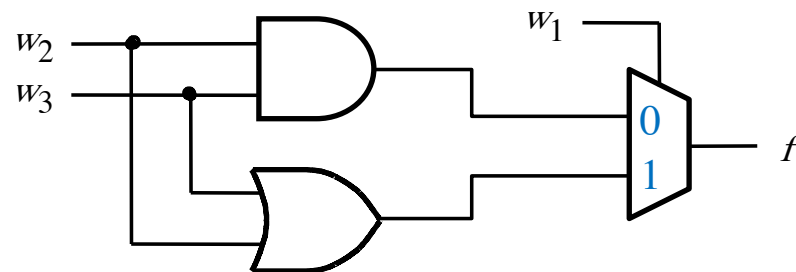

(b) Circuit


[Figure 4.10a from the textbook]

Three-input majority function

w_1	w_2	w_3	f
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

w_1	f
0	$w_2 w_3$
1	$w_2 + w_3$

(b) Truth table

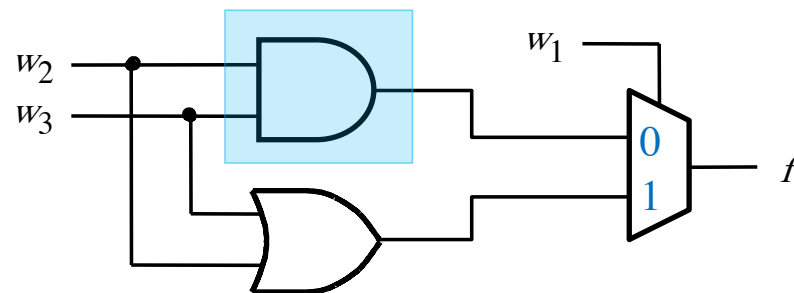

(b) Circuit


[Figure 4.10a from the textbook]

Three-input majority function

w_1	w_2	w_3	f
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

w_1	f
0	$w_2 w_3$
1	$w_2 + w_3$

(b) Truth table

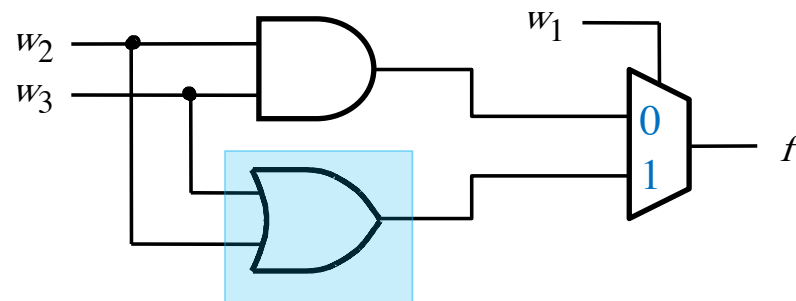


(b) Circuit

[Figure 4.10a from the textbook]

Three-input majority function

$$f = \bar{w}_1 w_2 w_3 + w_1 \bar{w}_2 w_3 + w_1 w_2 \bar{w}_3 + w_1 w_2 w_3$$

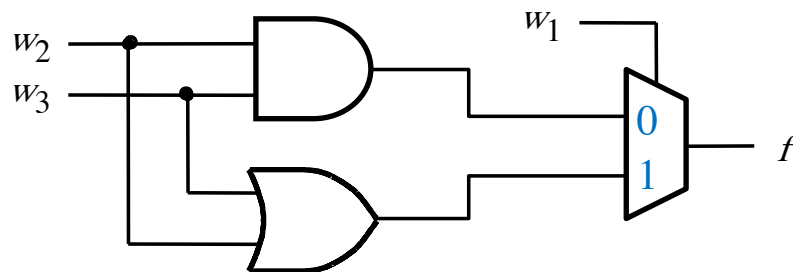
$$\begin{aligned} f &= \bar{w}_1 (w_2 w_3) + w_1 (\bar{w}_2 w_3 + w_2 \bar{w}_3 + w_2 w_3) \\ &= \bar{w}_1 (w_2 w_3) + w_1 (w_2 + w_3) \end{aligned}$$



Three-input majority function

$$f = \bar{w}_1 w_2 w_3 + w_1 \bar{w}_2 w_3 + w_1 w_2 \bar{w}_3 + w_1 w_2 w_3$$

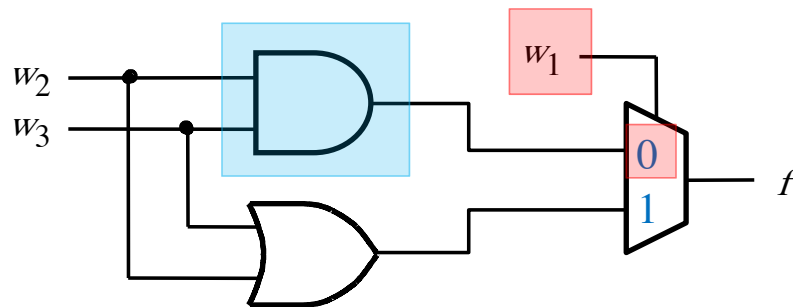
$$\begin{aligned} f &= \bar{w}_1 (w_2 w_3) + w_1 (\bar{w}_2 w_3 + w_2 \bar{w}_3 + w_2 w_3) \\ &= \bar{w}_1 (w_2 w_3) + w_1 (w_2 + w_3) \end{aligned}$$



Three-input majority function

$$f = \bar{w}_1 w_2 w_3 + w_1 \bar{w}_2 w_3 + w_1 w_2 \bar{w}_3 + w_1 w_2 w_3$$
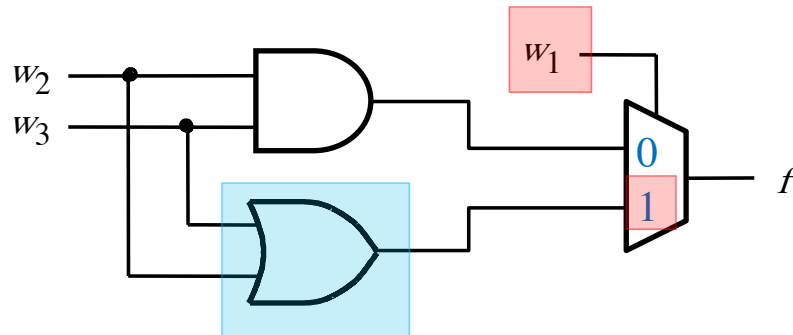
$$\begin{aligned} f &= \bar{w}_1 (w_2 w_3) + w_1 (\bar{w}_2 w_3 + w_2 \bar{w}_3 + w_2 w_3) \\ &= \bar{w}_1 (w_2 w_3) + w_1 (w_2 + w_3) \end{aligned}$$



Shannon's Expansion Theorem

Shannon's Expansion Theorem

Any Boolean function $f(w_1, \dots, w_n)$ can be rewritten in the form:

$$f(w_1, w_2, \dots, w_n) = \overline{w}_1 \cdot f(0, w_2, \dots, w_n) + w_1 \cdot f(1, w_2, \dots, w_n)$$

Shannon's Expansion Theorem

Any Boolean function $f(w_1, \dots, w_n)$ can be rewritten in the form:

$$f(w_1, w_2, \dots, w_n) = \bar{w}_1 \cdot f(0, w_2, \dots, w_n) + w_1 \cdot f(1, w_2, \dots, w_n)$$

$$f = \bar{w}_1 f_{\bar{w}_1} + w_1 f_{w_1}$$

Shannon's Expansion Theorem

Any Boolean function $f(w_1, \dots, w_n)$ can be rewritten in the form:

$$f(w_1, w_2, \dots, w_n) = \bar{w}_1 \cdot f(0, w_2, \dots, w_n) + w_1 \cdot f(1, w_2, \dots, w_n)$$

$$f = \bar{w}_1 f_{\bar{w}_1} + w_1 f_{w_1}$$

cofactor

cofactor

Shannon's Expansion Theorem
(example with only one select variable)
(used for 2-to-1 mux implementation)

Factor and implement the following function with a 2-to-1 multiplexer


$$f = \overline{w_1}\overline{w_3} + w_1w_2 + w_1w_3$$

Factor and implement the following function with a 2-to-1 multiplexer

$$f = \overline{w}_1 \overline{w}_3 + w_1 w_2 + w_1 w_3$$

$$\begin{aligned} f &= \overline{w}_1 f_{\overline{w}_1} + w_1 f_{w_1} \\ &= \overline{w}_1 (\overline{w}_3) + w_1 (w_2 + w_3) \end{aligned}$$

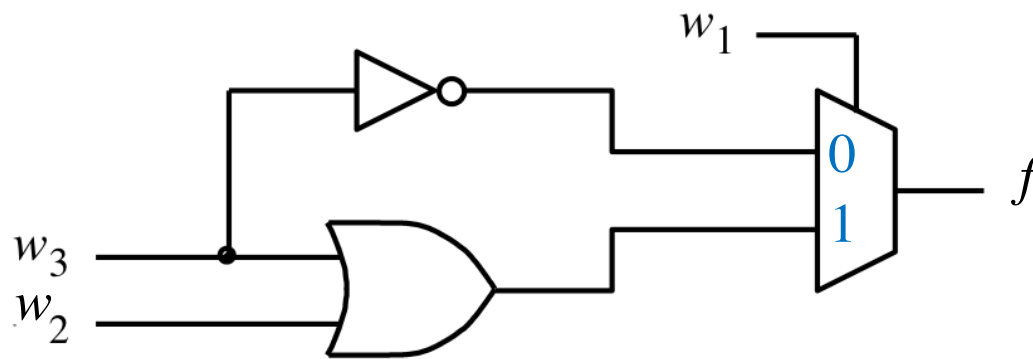Factor and implement the following function with a 2-to-1 multiplexer



$$\begin{aligned} f &= \bar{w}_1 f_{\bar{w}_1} + w_1 f_{w_1} \\ &= \bar{w}_1 (\bar{w}_3) + w_1 (w_2 + w_3) \end{aligned}$$

[Figure 4.11a from the textbook]

Another Example

Shannon's Expansion Theorem Example

$$f(w_1, w_2, w_3) = w_1 w_2 + w_1 w_3 + w_2 w_3$$

Shannon's Expansion Theorem Example

set $w_1 = 0$



$$f(w_1, w_2, w_3) = w_1 w_2 + w_1 w_3 + w_2 w_3$$

Shannon's Expansion Theorem Example

set $w_1 = 0$



$$f(w_1, w_2, w_3) = w_1 w_2 + w_1 w_3 + w_2 w_3$$

$$\underbrace{f(\underbrace{0}_{w_1}, w_2, w_3) = 0 \cdot w_2 + 0 \cdot w_3 + w_2 w_3}_{w_2 w_3}$$

$w_2 w_3$

Shannon's Expansion Theorem Example

set $w_1 = 1$



$$f(w_1, w_2, w_3) = w_1 w_2 + w_1 w_3 + w_2 w_3$$

Shannon's Expansion Theorem Example

set $w_1 = 1$



$$f(w_1, w_2, w_3) = w_1 w_2 + w_1 w_3 + w_2 w_3$$

$$f(\underset{w_1}{1}, w_2, w_3) = \underbrace{1 \cdot w_2 + 1 \cdot w_3 + w_2 w_3}$$

$$w_2 + w_3$$

Shannon's Expansion Theorem Example

started with this

$$f(w_1, w_2, w_3) = w_1 w_2 + w_1 w_3 + w_2 w_3$$

Shannon's Expansion Theorem Example

$$f(w_1, w_2, w_3) = w_1 w_2 + w_1 w_3 + w_2 w_3$$

$$\begin{aligned} f &= \overline{w}_1(0 \cdot w_2 + 0 \cdot w_3 + w_2 w_3) + w_1(1 \cdot w_2 + 1 \cdot w_3 + w_2 w_3) \\ &= \overline{w}_1(w_2 w_3) + w_1(w_2 + w_3) \end{aligned}$$

factored it in this form

Shannon's Expansion Theorem Example

$$f(w_1, w_2, w_3) = w_1 w_2 + w_1 w_3 + w_2 w_3$$


$$\begin{aligned} f &= \bar{w}_1(0 \cdot w_2 + 0 \cdot w_3 + w_2 w_3) + w_1(1 \cdot w_2 + 1 \cdot w_3 + w_2 w_3) \\ &= \bar{w}_1(w_2 w_3) + w_1(w_2 + w_3) \end{aligned}$$

$$f = \bar{w}_1 f_{\bar{w}_1} + w_1 f_{w_1}$$

which fits the general formula


Shannon's Expansion Theorem Example
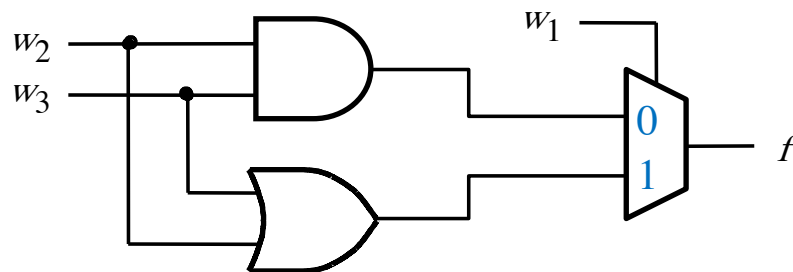
$$\begin{aligned} f &= \bar{w}_1(0 \cdot w_2 + 0 \cdot w_3 + w_2w_3) + w_1(1 \cdot w_2 + 1 \cdot w_3 + w_2w_3) \\ &= \bar{w}_1(w_2w_3) + w_1(w_2 + w_3) \end{aligned}$$




Shannon's Expansion Theorem Example
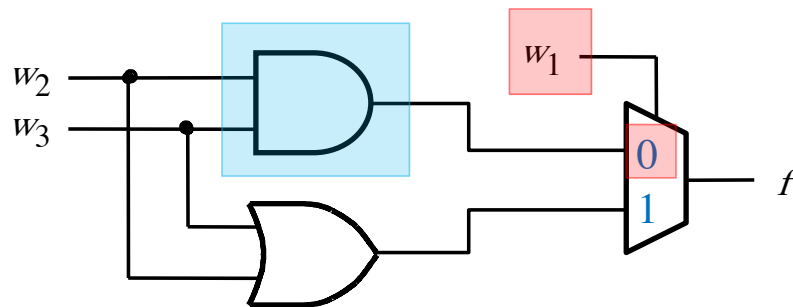
$$\begin{aligned} f &= \bar{w}_1(0 \cdot w_2 + 0 \cdot w_3 + w_2w_3) + w_1(1 \cdot w_2 + 1 \cdot w_3 + w_2w_3) \\ &= \bar{w}_1(w_2w_3) + w_1(w_2 + w_3) \end{aligned}$$



Shannon's Expansion Theorem Example

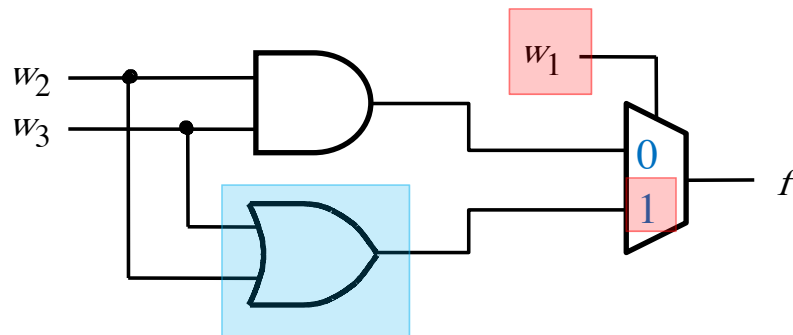
$$\begin{aligned} f &= \bar{w}_1(0 \cdot w_2 + 0 \cdot w_3 + w_2w_3) + w_1(1 \cdot w_2 + 1 \cdot w_3 + w_2w_3) \\ &= \bar{w}_1(w_2w_3) + \boxed{w_1} \boxed{(w_2 + w_3)} \end{aligned}$$



Earlier we derived the same result from the truth table using the divide-and-conquer method (a.k.a., Shannon's theorem)

w_1	w_2	w_3	f		w_1	f
0	0	0	0	}	0	$w_2 w_3$
0	0	1	0			
0	1	0	0			
0	1	1	1			
1	0	0	0	}	1	$w_2 + w_3$
1	0	1	1			
1	1	0	1			
1	1	1	1			

(b) Truth table

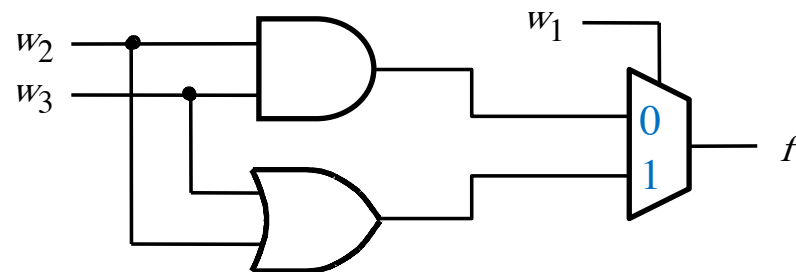

(b) Circuit

[Figure 4.10a from the textbook]

Shannon's Expansion Theorem
(example with two select variables)
(used for 4-to-1 mux implementation)

Shannon's Expansion Theorem (In terms of more than one variable)

$$\begin{aligned} f(w_1, \dots, w_n) = & \bar{w}_1 \bar{w}_2 \cdot f(0, 0, w_3, \dots, w_n) + \bar{w}_1 w_2 \cdot f(0, 1, w_3, \dots, w_n) \\ & + w_1 \bar{w}_2 \cdot f(1, 0, w_3, \dots, w_n) + w_1 w_2 \cdot f(1, 1, w_3, \dots, w_n) \end{aligned}$$

This form is suitable for implementation with a 4x1 multiplexer.

Factor and implement the following function with a 4-to-1 multiplexer

$$f(w_1, w_2, w_3) = \overline{w_1}\overline{w_3} + w_1w_2 + w_1w_3$$

Factor and implement the following function with a 4-to-1 multiplexer

$$f(w_1, w_2, w_3) = \underbrace{1 \cdot \bar{w}_3 + 0 \cdot 0 + 0 \cdot w_3}_{\bar{w}_3}$$

Note: In the original image, red arrows point from $w_1 = 0$ and $w_2 = 0$ to the 0s in the expression above.

Factor and implement the following function with a 4-to-1 multiplexer

$$\begin{array}{c} w_1 = 0 \quad w_2 = 1 \\ \downarrow \quad \downarrow \\ f(w_1, w_2, w_3) = \underbrace{1 \cdot \overline{w}_3 + 0 \cdot 1 + 0 \cdot w_3}_{\overline{w}_3} \end{array}$$

Factor and implement the following function with a 4-to-1 multiplexer

$$\begin{array}{c} w_1 = 1 \quad w_2 = 0 \\ \downarrow \quad \downarrow \\ f(w_1, w_2, w_3) = \underbrace{0 \cdot \bar{w}_3 + 1 \cdot 0 + 1 \cdot w_3}_{w_3} \end{array}$$

Factor and implement the following function with a 4-to-1 multiplexer

$$f(w_1, w_2, w_3) = \underbrace{0 \cdot \bar{w}_3 + 1 \cdot 1 + 1 \cdot w_3}_1$$

Note: In the original image, red arrows point from $w_1 = 1$ and $w_2 = 1$ to the terms $1 \cdot 1$ and $1 \cdot w_3$ respectively in the equation above.

Factor and implement the following function with a 4-to-1 multiplexer

$$f = \overline{w}_1 \overline{w}_3 + w_1 w_2 + w_1 w_3$$

$$\begin{aligned} f &= \overline{w}_1 \overline{w}_2 f_{\overline{w}_1 \overline{w}_2} + \overline{w}_1 w_2 f_{\overline{w}_1 w_2} + w_1 \overline{w}_2 f_{w_1 \overline{w}_2} + w_1 w_2 f_{w_1 w_2} \\ &= \overline{w}_1 \overline{w}_2 (\overline{w}_3) + \overline{w}_1 w_2 (\overline{w}_3) + w_1 \overline{w}_2 (w_3) + w_1 w_2 (1) \end{aligned}$$

Factor and implement the following function with a 4-to-1 multiplexer

$$f = \overline{w}_1 \overline{w}_3 + w_1 w_2 + w_1 w_3$$

$$\begin{aligned} f &= \overline{w}_1 \overline{w}_2 f_{\overline{w}_1 \overline{w}_2} + \overline{w}_1 w_2 f_{\overline{w}_1 w_2} + w_1 \overline{w}_2 f_{w_1 \overline{w}_2} + w_1 w_2 f_{w_1 w_2} \\ &= \overline{w}_1 \overline{w}_2 (\overline{w}_3) + \overline{w}_1 w_2 (\overline{w}_3) + w_1 \overline{w}_2 (w_3) + w_1 w_2 (1) \end{aligned}$$

these are the 4 minterms in terms of w_1 and w_2


Factor and implement the following function with a 4-to-1 multiplexer

$$f = \overline{w}_1 \overline{w}_3 + w_1 w_2 + w_1 w_3$$

$$\begin{aligned} f &= \overline{w}_1 \overline{w}_2 f_{\overline{w}_1 \overline{w}_2} + \overline{w}_1 w_2 f_{\overline{w}_1 w_2} + w_1 \overline{w}_2 f_{w_1 \overline{w}_2} + w_1 w_2 f_{w_1 w_2} \\ &= \overline{w}_1 \overline{w}_2 (\overline{w}_3) + \overline{w}_1 w_2 (\overline{w}_3) + w_1 \overline{w}_2 (w_3) + w_1 w_2 (1) \end{aligned}$$

these are the 4 cofactors

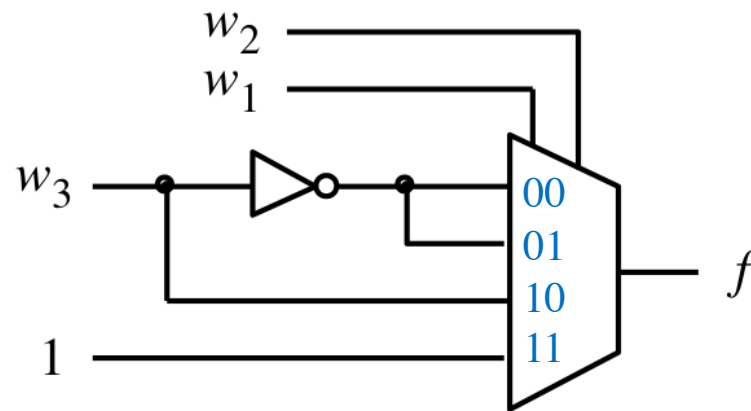Factor and implement the following function with a 4-to-1 multiplexer



$$\begin{aligned}
 f &= \bar{w}_1 \bar{w}_2 f_{\bar{w}_1 \bar{w}_2} + \bar{w}_1 w_2 f_{\bar{w}_1 w_2} + w_1 \bar{w}_2 f_{w_1 \bar{w}_2} + w_1 w_2 f_{w_1 w_2} \\
 &= \bar{w}_1 \bar{w}_2 (\bar{w}_3) + \bar{w}_1 w_2 (\bar{w}_3) + w_1 \bar{w}_2 (w_3) + w_1 w_2 (1)
 \end{aligned}$$

[Figure 4.11b from the textbook]

Alternative Derivation for the same Problem

(using Boolean Algebra to derive the cofactors)

Factor and implement the following function with a 4-to-1 multiplexer

$$f = \overline{w_1}\overline{w_3} + w_1w_2 + w_1w_3$$

Factor and implement the following function with a 4-to-1 multiplexer

$$f = \overline{w_1} \overline{w_3} + w_1 w_2 + w_1 w_3$$

$$= \overline{w_1} (\overline{w_2} + w_2) \overline{w_3} + w_1 w_2 + w_1 (\overline{w_2} + w_2) w_3$$

Factor and implement the following function with a 4-to-1 multiplexer

$$f = \overline{w_1} \overline{w_3} + w_1 w_2 + w_1 w_3$$

$$= \overline{w_1} (\overline{w_2} + w_2) \overline{w_3} + w_1 w_2 + w_1 (\overline{w_2} + w_2) w_3$$

$$= \overline{w_1} \overline{w_2} \overline{w_3} + \overline{w_1} w_2 \overline{w_3} + w_1 w_2 + w_1 \overline{w_2} w_3 + w_1 w_2 w_3$$

$$= \overline{w_1} \overline{w_2} \overline{w_3} + \overline{w_1} w_2 \overline{w_3} + w_1 \overline{w_2} w_3 + w_1 w_2 (1 + w_3)$$

$$= \overline{w_1} \overline{w_2} (\overline{w_3}) + \overline{w_1} w_2 (\overline{w_3}) + w_1 \overline{w_2} (w_3) + w_1 w_2 (1)$$

Factor and implement the following function with a 4-to-1 multiplexer

$$f = \overline{w_1} \overline{w_3} + w_1 w_2 + w_1 w_3$$

$$= \overline{w_1} (\overline{w_2} + w_2) \overline{w_3} + w_1 w_2 + w_1 (\overline{w_2} + w_2) w_3$$

$$= \overline{w_1} \overline{w_2} \overline{w_3} + \overline{w_1} w_2 \overline{w_3} + w_1 w_2 + w_1 \overline{w_2} w_3 + w_1 w_2 w_3$$

$$= \overline{w_1} \overline{w_2} \overline{w_3} + \overline{w_1} w_2 \overline{w_3} + w_1 \overline{w_2} w_3 + w_1 w_2 (1 + w_3)$$

$$= \overline{w_1} \overline{w_2} (\overline{w_3}) + \overline{w_1} w_2 (\overline{w_3}) + w_1 \overline{w_2} (w_3) + w_1 w_2 (1)$$

these are the 4 minterms in terms of w_1 and w_2

Factor and implement the following function with a 4-to-1 multiplexer

$$f = \overline{w_1} \overline{w_3} + w_1 w_2 + w_1 w_3$$

$$= \overline{w_1} (\overline{w_2} + w_2) \overline{w_3} + w_1 w_2 + w_1 (\overline{w_2} + w_2) w_3$$

$$= \overline{w_1} \overline{w_2} \overline{w_3} + \overline{w_1} w_2 \overline{w_3} + w_1 w_2 + w_1 \overline{w_2} w_3 + w_1 w_2 w_3$$

$$= \overline{w_1} \overline{w_2} \overline{w_3} + \overline{w_1} w_2 \overline{w_3} + w_1 \overline{w_2} w_3 + w_1 w_2 (1 + w_3)$$

$$= \overline{w_1} \overline{w_2} (\overline{w_3}) + \overline{w_1} w_2 (\overline{w_3}) + w_1 \overline{w_2} (w_3) + w_1 w_2 (1)$$


these are the 4 cofactors

Factor and implement the following function with a 4-to-1 multiplexer

$$f = \overline{w}_1 \overline{w}_3 + w_1 w_2 + w_1 w_3$$

$$\begin{aligned} f &= \overline{w}_1 \overline{w}_2 f_{\overline{w}_1 \overline{w}_2} + \overline{w}_1 w_2 f_{\overline{w}_1 w_2} + w_1 \overline{w}_2 f_{w_1 \overline{w}_2} + w_1 w_2 f_{w_1 w_2} \\ &= \overline{w}_1 \overline{w}_2 (\overline{w}_3) + \overline{w}_1 w_2 (\overline{w}_3) + w_1 \overline{w}_2 (w_3) + w_1 w_2 (1) \end{aligned}$$

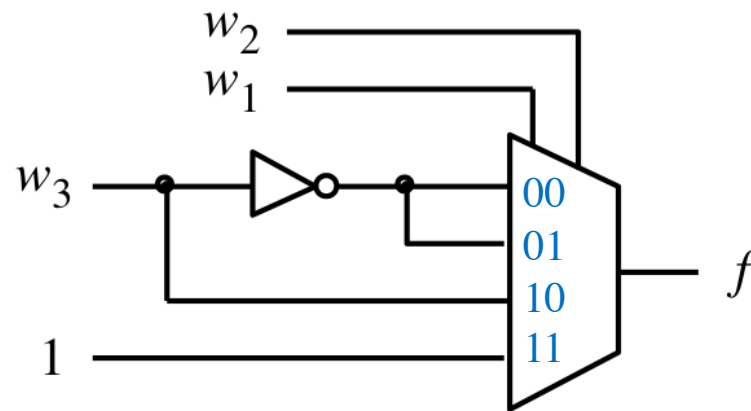Factor and implement the following function with a 4-to-1 multiplexer



$$\begin{aligned}
 f &= \bar{w}_1 \bar{w}_2 f_{\bar{w}_1 \bar{w}_2} + \bar{w}_1 w_2 f_{\bar{w}_1 w_2} + w_1 \bar{w}_2 f_{w_1 \bar{w}_2} + w_1 w_2 f_{w_1 w_2} \\
 &= \bar{w}_1 \bar{w}_2 (\bar{w}_3) + \bar{w}_1 w_2 (\bar{w}_3) + w_1 \bar{w}_2 (w_3) + w_1 w_2 (1)
 \end{aligned}$$

[Figure 4.11b from the textbook]

Yet Another Example (with hierarchical structure)

Factor and implement the following function using only 2-to-1 multiplexers

$$f = w_1w_2 + w_1w_3 + w_2w_3$$

Factor and implement the following function using only 2-to-1 multiplexers

$$f = w_1w_2 + w_1w_3 + w_2w_3$$

$$\begin{aligned} f &= \bar{w}_1(w_2w_3) + w_1(w_2 + w_3 + w_2w_3) \\ &= \bar{w}_1(w_2w_3) + w_1(w_2 + w_3) \end{aligned}$$

Factor and implement the following function using only 2-to-1 multiplexers


$$f = w_1w_2 + w_1w_3 + w_2w_3$$

$$f = \bar{w}_1(w_2w_3) + w_1(w_2 + w_3 + w_2w_3)$$

$$= \bar{w}_1(\underbrace{w_2w_3}) + w_1(\underbrace{w_2 + w_3})$$

$$g = w_2w_3 \quad h = w_2 + w_3$$

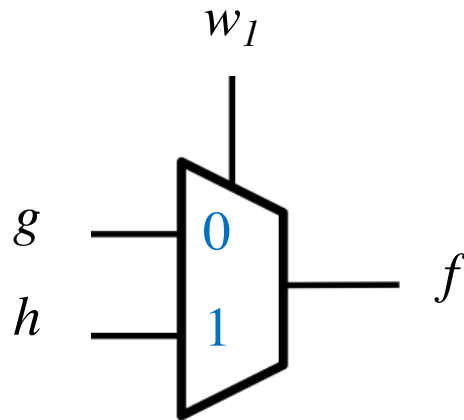Factor and implement the following function using only 2-to-1 multiplexers



$$f = \bar{w}_1(w_2w_3) + w_1(w_2 + w_3 + w_2w_3)$$

$$= \bar{w}_1(\underbrace{w_2w_3}) + w_1(\underbrace{w_2 + w_3})$$

$$g = w_2w_3 \quad h = w_2 + w_3$$

Factor and implement the following function using only 2-to-1 multiplexers

$$g = w_2 w_3$$

$$h = w_2 + w_3$$

Factor and implement the following function using only 2-to-1 multiplexers

$$g = w_2 w_3$$





$$g = \overline{w}_2(0) + w_2(w_3)$$

$$h = w_2 + w_3$$



$$h = \overline{w}_2(w_3) + w_2(1)$$

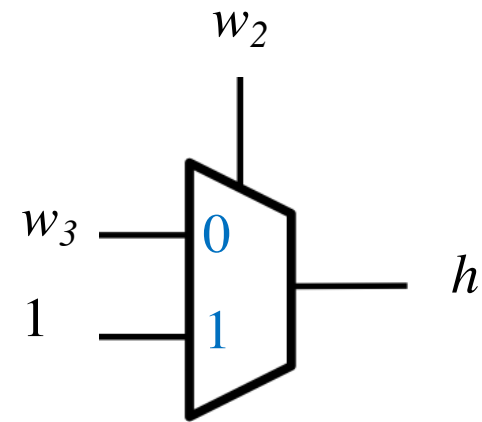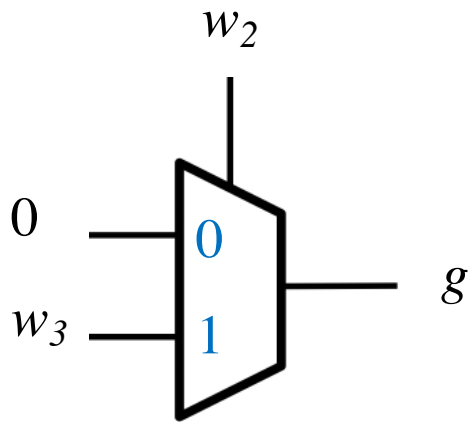
Factor and implement the following function using only 2-to-1 multiplexers




$$g = \overline{w_2}(0) + w_2(w_3)$$

$$h = \overline{w_2}(w_3) + w_2(1)$$

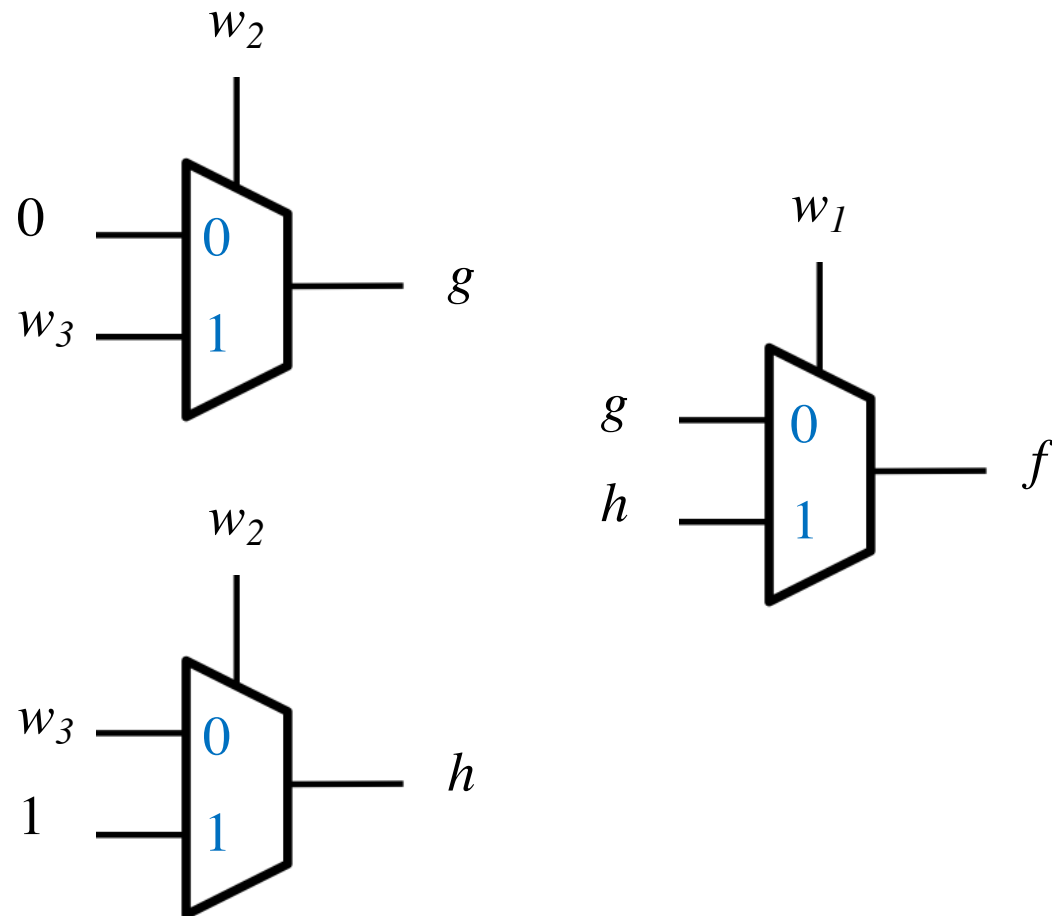
Finally, we are ready to draw the circuit



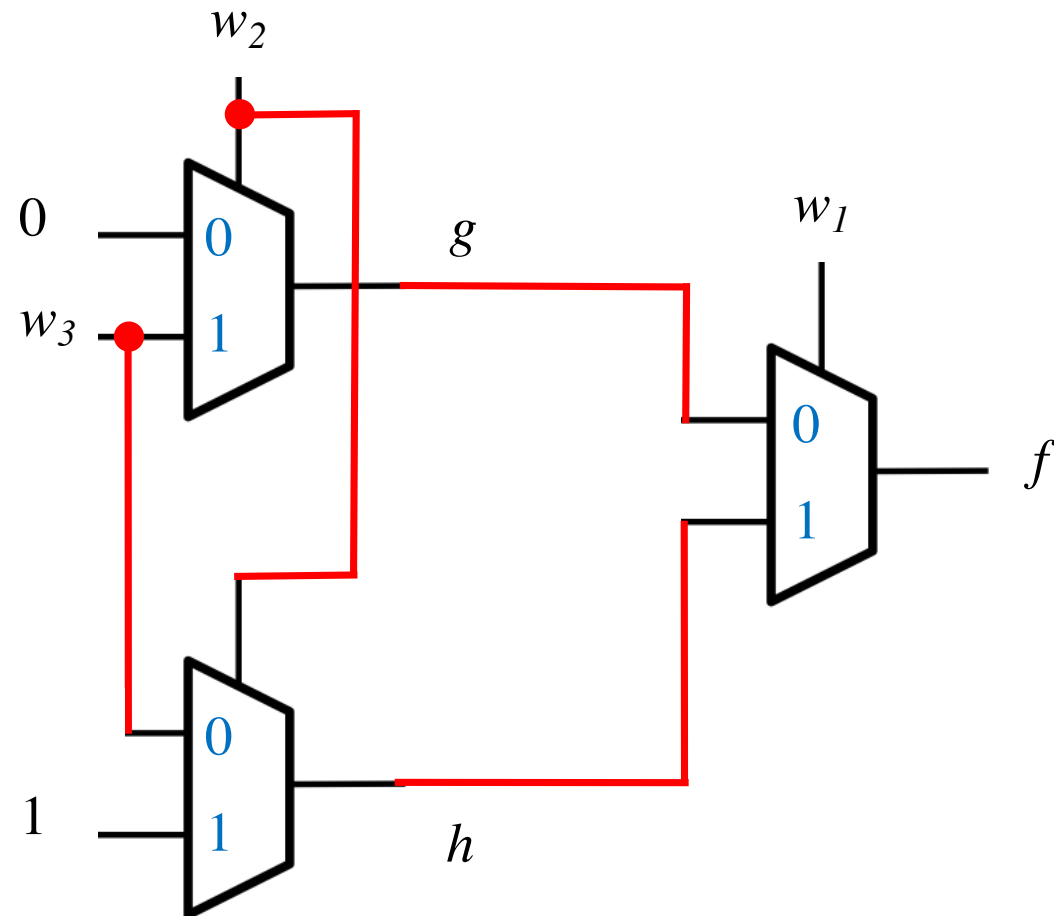Finally, we are ready to draw the circuit



Finally, we are ready to draw the circuit

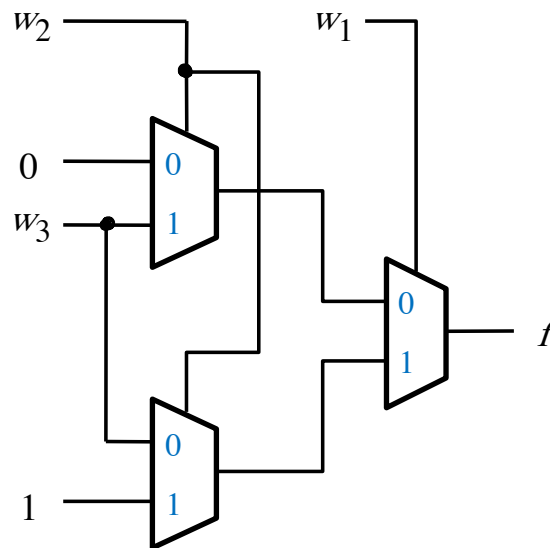

[Figure 4.12 from the textbook]

Questions?

THE END