 




CprE 2810: Digital Logic

Instructor: Alexander Stoytchev

<http://www.ece.iastate.edu/~alexs/classes/>

Latches

*CprE 2810: Digital Logic
Iowa State University, Ames, IA
Copyright © Alexander Stoytchev*

Administrative Stuff

- **HW 7 is due on Monday (Oct 20) @ 10pm**
- **Midterm grades submitted to the registrar's office**

Administrative Stuff


- **Midterm 2 is in two weeks**
- **Sample exams are posted on the class web page**

Administrative Stuff

- **Midterm Exam #2**
- **When: Friday October 31 @ 4:20pm.**
- **Where: This room**
- **What: Chapters 1, 2, 3, 4 and 5**
- **The exam will be closed book but open notes
(you can bring up to 3 sheets of handwritten notes).**

Chapter 5

Control of an alarm system

 


[Figure 5.1 from the textbook]

Motivation


- **So far, our circuits have been converting inputs to outputs without storing any data.**
- **To do more advanced things (e.g., to build computers) we need components that can store data.**
- **Can we make a component that “remembers” using the components that we know already?**

A simple memory element

 


[Figure 5.2 from the textbook]


A simple memory element with NOT Gates

 


A simple memory element with NOT Gates

 

A simple memory element with NOT Gates

 


A simple memory element with NOT Gates

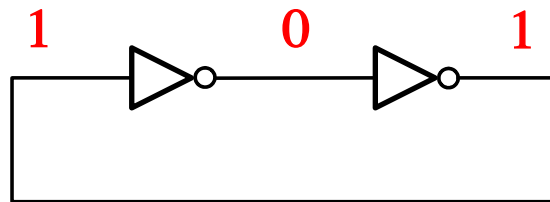


The circuit will stay in this state indefinitely.


A simple memory element with NOT Gates

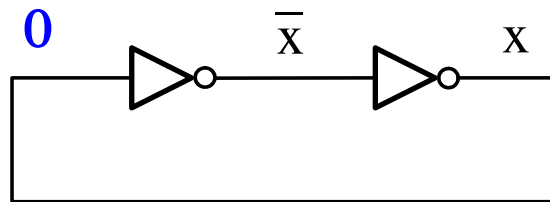

A simple memory element with NOT Gates

 

A simple memory element with NOT Gates

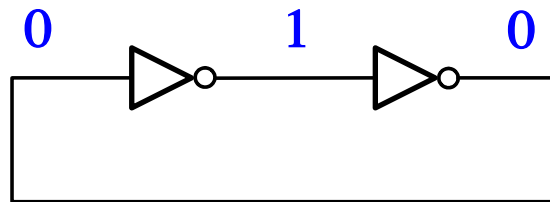



The circuit will stay in this state indefinitely.

A Strange Loop




[<http://animalsiadmire.blogspot.com/2011/07/stupid-snake-eating-itself.html>]

  
This circuit can be in two possible states



 This circuit can be in two possible states





used to store a 1

 


used to store a 0

  
This circuit can be in two possible states



Building a NOT gate with a NAND gate

 

x	$\bar{x}$
0	1
1	0

 


x	x	f
0	0	1
1	1	0


impossible
combinations

Thus, the two truth tables are equal!

A simple memory element with NAND Gates

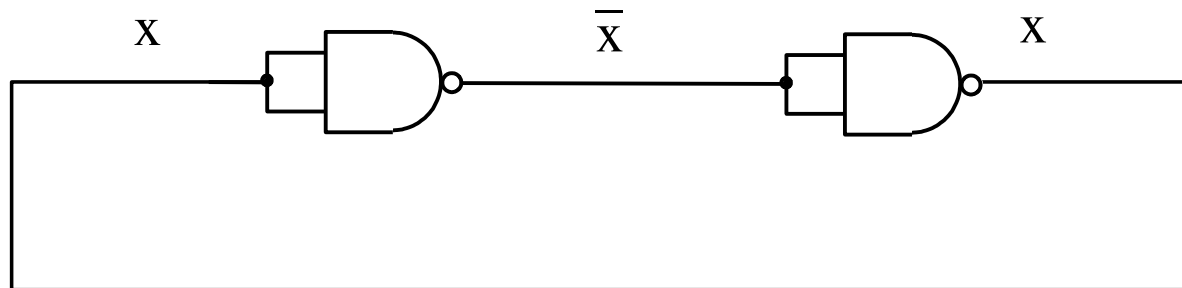

Building a NOT gate with a NOR gate

 

x	$\bar{x}$
0	1
1	0




x	x	f
0	0	1
1	1	0

impossible
combinations

Thus, the two truth tables are equal!

A simple memory element with NOR Gates

 


Basic Latch

What is a latch?




http://luxuriahardware.com/images/detailed/13/P111408_m.jpg


A simple memory element with NOR Gates

 


A simple memory element with NOR Gates

 

A simple memory element with NOR Gates


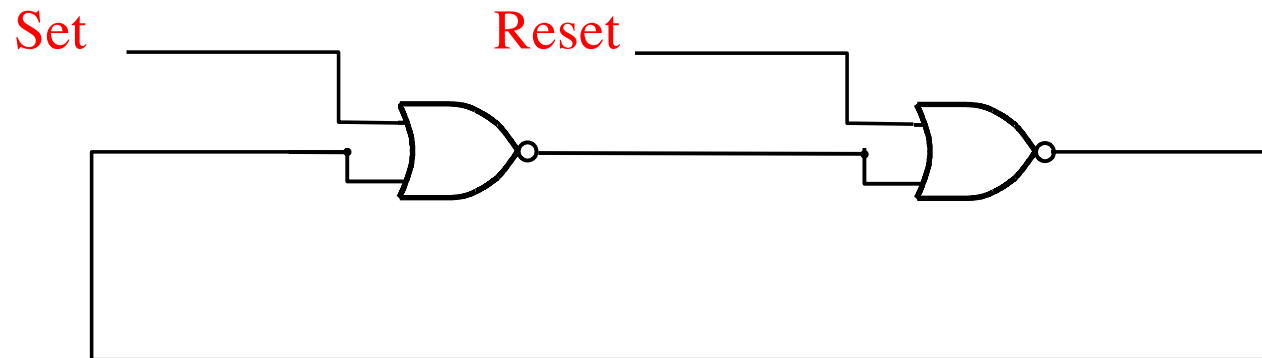


A memory element with NOR gates

 



[Figure 5.3 from the textbook]

Two Different Ways to Draw the Same Circuit

  

[Figure 5.3 & 5.4 from the textbook]


Two Different Ways to Draw the Same Circuit

  

[Figure 5.3 & 5.4 from the textbook]

**Before We Analyze the Basic Latch
Let's Look at Two Simpler
Examples with Feedback**

Let's Try to Analyze This Circuit

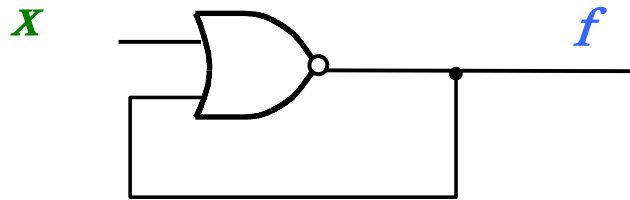


Let's Try to Analyze This Circuit


Control Line

x

Data Line

 


Let's Try to Analyze This Circuit

 


x	f_t	f_{t+1}
0	0	
0	1	
1	0	
1	1	

Let's Try to Analyze This Circuit

 


x	f_t	f_{t+1}
0	0	1
0	1	0
1	0	0
1	1	0

Let's Try to Analyze This Circuit

 

x	f_t	f_{t+1}	
0	0	1	} $\overline{f_t}$
0	1	0	
1	0	0	} 0
1	1	0	

Let's Try to Analyze This Circuit

 


x	f_t	f_{t+1}
0	0	1
0	1	0
1	0	0
1	1	0

Red annotations: A vertical red line is drawn between the x and f_t columns. A horizontal red line is drawn between the f_t and f_{t+1} columns. Red curly braces on the right group the rows: the first two rows are grouped by $\overline{f_t}$ and the last two rows are grouped by 0.

If $x = 0$, then f is negated.


If $x = 1$, then f is driven to 0.

Key Observation

 


If a NOR's **control line** is 0, then that NOR just *negates* its **data line**. If the **control line** is 1, then the NOR's output is *driven* to 0, ignoring its **data line**.

Let's Try to Analyze This Circuit

 


Let's Try to Analyze This Circuit

 


x	g_t	g_{t+1}
0	0	
0	1	
1	0	
1	1	

Let's Try to Analyze This Circuit

 

x	g_t	g_{t+1}
0	0	1
0	1	1
1	0	1
1	1	0

Let's Try to Analyze This Circuit

 


x	g_t	g_{t+1}
0	0	1
0	1	1
1	0	1
1	1	0

Red annotations: A vertical red line is to the left of the table. A horizontal red line is between the second and third rows. Red curly braces on the right group the first two rows under the label 1 and the last two rows under the label $\overline{g_t}$.

If $x = 0$, then g is driven to one.

If $x = 1$, then g is negated.


Key Observation

 

If a NAND's **control line** is 1, then that NAND just *negates* its **data line**. If the **control line** is 0, then the NAND's output is *driven* to 1, ignoring its **data line**.


Output Oscillations

 What would happen to *g* if we keep *x*=1 for a long time?




Output Oscillations

 What would happen to g if we keep $x=1$ for a long time?



Output Oscillations

 
What would happen to g if we keep $x=1$ for a long time?



t_{pd} is the propagation delay through the NAND gate, which is small, but not zero.


Back to the Basic Latch

The Basic Latch

 


[Figure 5.3 from the textbook]

The Basic Latch

 

[Figure 5.3 from the textbook]


Analyzing The Basic Latch

 

S	Q_a	$Q_b = \text{NOR}(S, Q_a)$
0	0	
0	1	
1	0	
1	1	

R	Q_b	$Q_a = \text{NOR}(R, Q_b)$
0	0	
0	1	
1	0	
1	1	


Analyzing The Basic Latch

 

S	Q_a	$Q_b = \text{NOR}(S, Q_a)$
0	0	1
0	1	0
1	0	0
1	1	0

R	Q_b	$Q_a = \text{NOR}(R, Q_b)$
0	0	1
0	1	0
1	0	0
1	1	0


Analyzing The Basic Latch

 

S	Q_a	$Q_b = \text{NOR}(S, Q_a)$	
0	0	1	} $\overline{Q_a}$
0	1	0	
1	0	0	} 0
1	1	0	

R	Q_b	$Q_a = \text{NOR}(R, Q_b)$	
0	0	1	} $\overline{Q_b}$
0	1	0	
1	0	0	} 0
1	1	0	


Analyzing The Basic Latch

 

S	Q_b
0	$\overline{Q_a}$
1	0


R	Q_a
0	$\overline{Q_b}$
1	0

Behavior of the Basic Latch

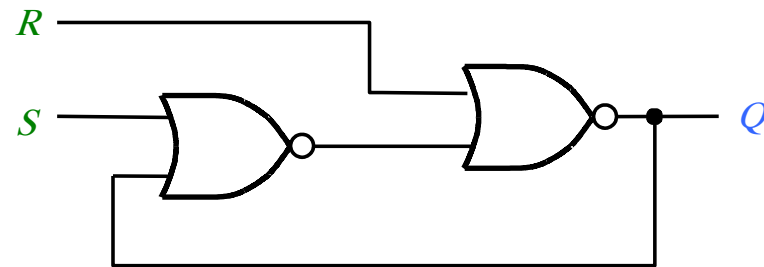


S	R	Q_{t+1}
0	0	
0	1	
1	0	
1	1	

Behavior of the Basic Latch

 


S	R	Q_{t+1}
0	0	Q_t
0	1	0
1	0	1
1	1	0

Behavior of the Basic Latch

 


S	R	$Q_a(t+1)$	$Q_b(t+1)$
0	0		
0	1		
1	0		
1	1		

Behavior of the Basic Latch

 

S	R	$Q_a(t+1)$	$Q_b(t+1)$
0	0	$Q_a(t)$	$Q_b(t)$
0	1	0	1
1	0	1	0
1	1	0	0

Behavior of the Basic Latch

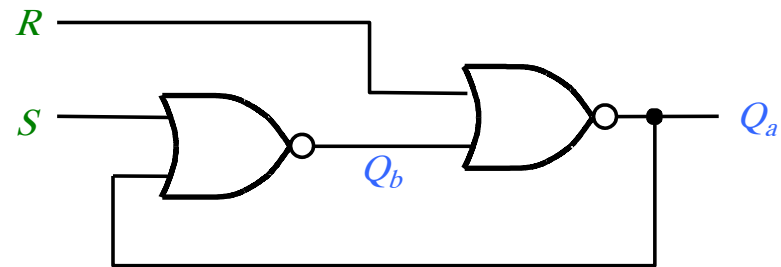

S	R	$Q_a(t+1)$	$Q_b(t+1)$
0	0	$Q_a(t)$	$Q_b(t)$
0	1	0	1
1	0	1	0
1	1	0	0


Latch

Reset

Set

Undesirable

Circuit and Characteristic Table

 


(a) Circuit

S	R	Q_a	Q_b	
0	0	0/1	1/0	(no change)
0	1	0	1	
1	0	1	0	
1	1	0	0	

(b) Characteristic table

[Figure 5.4a,b from the textbook]


NOR Gate

 

NOR Gate Truth table

x_1	x_2	f
0	0	1
0	1	0
1	0	0
1	1	0

Circuit and Characteristic Table

 

(a) Circuit

S	R	Q_a	Q_b	
0	0	0/1	1/0	(no change)
0	1	0	1	
1	0	1	0	
1	1	0	0	


(b) Characteristic table

A truth table should take the state into account.

A characteristic table takes only the inputs into account.

[Figure 5.4a,b from the textbook]


NOR Gate

 

NOR Gate Truth table

x_1	x_2	f
0	0	1
0	1	0
1	0	0
1	1	0

Circuit and Characteristic Table

 

(a) Circuit


S	R	Q_a	Q_b	
0	0	0/1	1/0	(no change)
0	1	0	1	
1	0	1	0	
1	1	0	0	

Note that Q_a and Q_b are inverses of each other!

(b) Characteristic table

[Figure 5.4a,b from the textbook]

NOR Gate

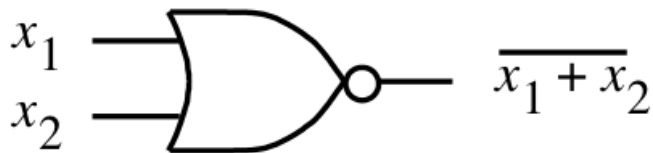

NOR Gate Truth table

x_1	x_2	f
0	0	1
0	1	0
1	0	0
1	1	0


Oscillations and Undesirable States

- When $S=1$ and $R=1$ both outputs of the latch are equal to 0, i.e., $Q_a=0$ and $Q_b=0$.
- Thus, the two outputs are no longer complements of each other.
- This is undesirable as many of the circuits that we will build later with these latches rely on the assumption that the two outputs are always complements of each other.
- (This is obviously not the case for the basic latch, but we will patch it later to eliminate this problem).

Oscillations and Undesirable States

- An even bigger problem occurs when we transition **from $S=R=1$ to $S=R=0$** .
- When $S=R=1$ we have $Q_a=Q_b=0$. After the transition to $S=R=0$, however, we get $Q_a=Q_b=1$, which would immediately cause $Q_a=Q_b=0$, and so on.
- If the gate delays and the wire lengths are identical, then this oscillation will continue forever.
- In practice, the oscillation dies down and the output settles into either $Q_a=1$ and $Q_b=0$ or $Q_a=0$ and $Q_b=1$.
- The problem is that **we can't predict** which one of these two it will settle into.

 
Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit

S	R	Q_a	Q_b	
0	0	0/1	1/0	(no change)
0	1	0	1	
1	0	1	0	
1	1	0	0	

(b) Characteristic table

 


(c) Timing diagram

→ Time

[Figure 5.4 from the textbook]

 
Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit

S	R	Q_a	Q_b	
0	0	0/1	1/0	(no change)
0	1	0	1	
1	0	1	0	
1	1	0	0	

(b) Characteristic table

 


(c) Timing diagram

→ Time

[Figure 5.4 from the textbook]

 
Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit


S	R	Q_a	Q_b	
0	0	0/1	1/0	(no change)
0	1	0	1	
1	0	1	0	
1	1	0	0	

(b) Characteristic table

 

 (c) Timing diagram


Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit


S	R	Q_a	Q_b	
0	0	0/1	1/0	(no change)
0	1	0	1	
1	0	1	0	
1	1	0	0	

(b) Characteristic table

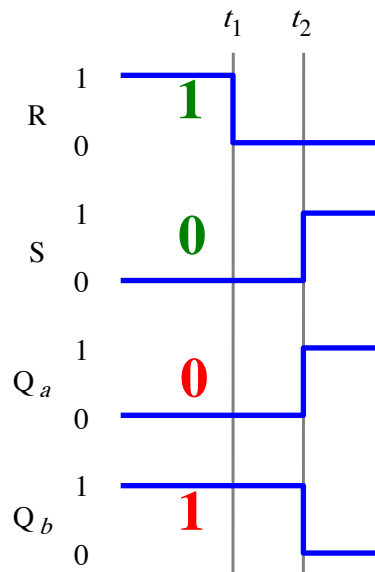

 (c) Timing diagram


Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit


S	R	Q _a	Q _b	
0	0	0/1	1/0	(no change)
0	1	0	1	
1	0	1	0	
1	1	0	0	

(b) Characteristic table

 

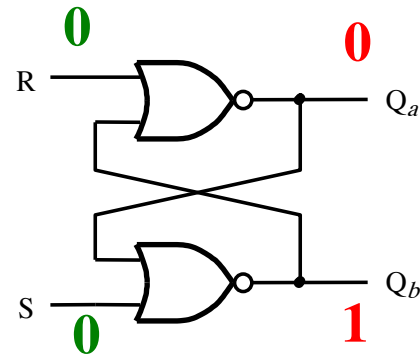(c) Timing diagram


Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit


S	R	Q_a	Q_b	
0	0	0/1	1/0	(no change)
0	1	0	1	
1	0	1	0	
1	1	0	0	

(b) Characteristic table

 

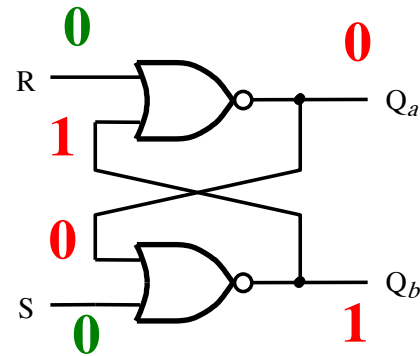(c) Timing diagram


Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit


S	R	Q _a	Q _b	
0	0	0/1	1/0	(no change)
0	1	0	1	
1	0	1	0	
1	1	0	0	

(b) Characteristic table

 

 (c) Timing diagram


Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit


S	R	Q _a	Q _b	
0	0	0/1	1/0	(no change)
0	1	0	1	
1	0	1	0	
1	1	0	0	

(b) Characteristic table

 

 (c) Timing diagram


Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit


S	R	Q_a	Q_b	
0	0	0/1	1/0	(no change)
0	1	0	1	
1	0	1	0	
1	1	0	0	

(b) Characteristic table

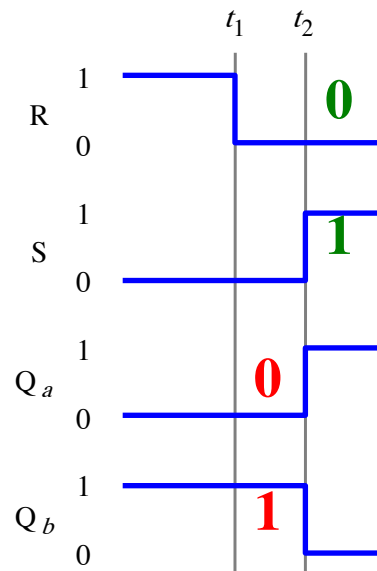

 (c) Timing diagram


Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit

S	R	Q_a	Q_b	
0	0	0/1	1/0	(no change)
0	1	0	1	
1	0	1	0	
1	1	0	0	


(b) Characteristic table

 

 (c) Timing diagram

For a brief moment the latch goes through the undesirable state $Q_a=0$ and $Q_b=0$.


Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit

S	R	Q _a	Q _b	
0	0	0/1	1/0	(no change)
0	1	0	1	
1	0	1	0	
1	1	0	0	


(b) Characteristic table

 

 (c) Timing diagram

But these zeros loop around ...


Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit

S	R	Q _a	Q _b	
0	0	0/1	1/0	(no change)
0	1	0	1	
1	0	1	0	
1	1	0	0	


(b) Characteristic table

 

 (c) Timing diagram

... and set it to Q_a=1 and Q_b=0.


Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit

S	R	Q _a	Q _b	
0	0	0/1	1/0	(no change)
0	1	0	1	
1	0	1	0	
1	1	0	0	


(b) Characteristic table

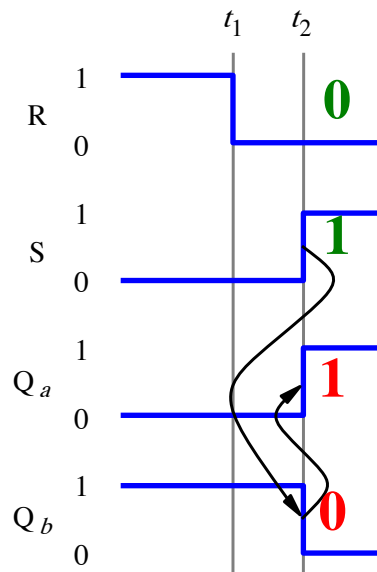

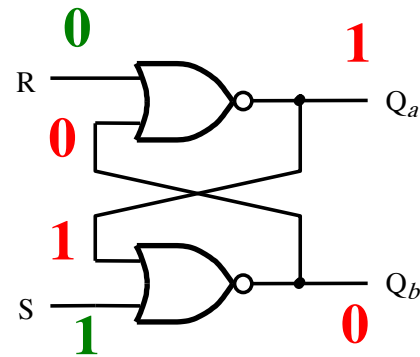(c) Timing diagram

The new values also loop around ...


Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit

S	R	Q _a	Q _b	
0	0	0/1	1/0	(no change)
0	1	0	1	
1	0	1	0	
1	1	0	0	


(b) Characteristic table

 

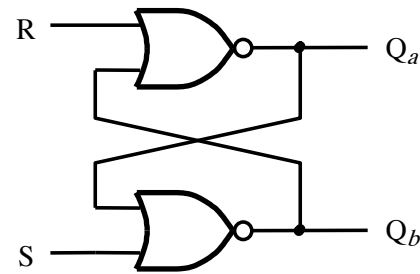(c) Timing diagram

... but they leave the outputs the same.


Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit

S	R	Q_a	Q_b	
0	0	0/1	1/0	(no change)
0	1	0	1	
1	0	1	0	
1	1	0	0	

(b) Characteristic table

 


(c) Timing diagram

→ Time

[Figure 5.4 from the textbook]

 
Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit


S	R	Q_a	Q_b	
0	0	0/1	1/0	(no change)
0	1	0	1	
1	0	1	0	
1	1	0	0	

(b) Characteristic table

 

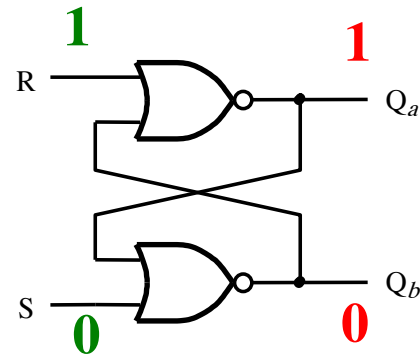(c) Timing diagram


Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit


S	R	Q_a	Q_b	
0	0	0/1	1/0	(no change)
0	1	0	1	
1	0	1	0	
1	1	0	0	

(b) Characteristic table

 

 (c) Timing diagram


Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit


S	R	Q_a	Q_b	
0	0	0/1	1/0	(no change)
0	1	0	1	
1	0	1	0	
1	1	0	0	

(b) Characteristic table

 

 (c) Timing diagram


Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit

S	R	Q_a	Q_b	
0	0	0/1	1/0	(no change)
0	1	0	1	
1	0	1	0	
1	1	0	0	


(b) Characteristic table

 

 (c) Timing diagram

For a brief moment the latch goes through the undesirable state $Q_a=0$ and $Q_b=0$.


Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit

S	R	Q _a	Q _b	
0	0	0/1	1/0	(no change)
0	1	0	1	
1	0	1	0	
1	1	0	0	


(b) Characteristic table

 

 (c) Timing diagram

But these zeros loop around ...


Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit

S	R	Q _a	Q _b	
0	0	0/1	1/0	(no change)
0	1	0	1	
1	0	1	0	
1	1	0	0	


(b) Characteristic table

 

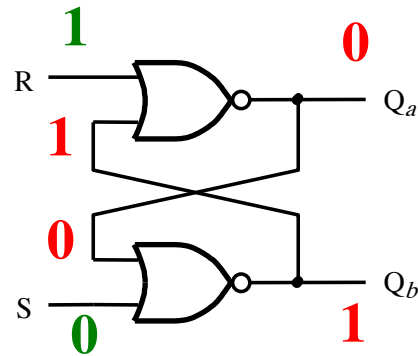(c) Timing diagram

... and set it to Q_a=0 and Q_b=1.


Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit

S	R	Q _a	Q _b	
0	0	0/1	1/0	(no change)
0	1	0	1	
1	0	1	0	
1	1	0	0	


(b) Characteristic table

 

 (c) Timing diagram

The new values also loop around ...


Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit

S	R	Q _a	Q _b	
0	0	0/1	1/0	(no change)
0	1	0	1	
1	0	1	0	
1	1	0	0	


(b) Characteristic table

 

 (c) Timing diagram

... but they leave the outputs the same.


Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit

S	R	Q_a	Q_b	
0	0	0/1	1/0	(no change)
0	1	0	1	
1	0	1	0	
1	1	0	0	

(b) Characteristic table

 


(c) Timing diagram

→ Time

[Figure 5.4 from the textbook]

 
Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit

S	R	Q_a	Q_b	
0	0	0/1	1/0	(no change)
0	1	0	1	
1	0	1	0	
1	1	0	0	

(b) Characteristic table

 


(c) Timing diagram

→ Time

[Figure 5.4 from the textbook]

 
Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit

S	R	Q_a	Q_b	
0	0	0/1	1/0	(no change)
0	1	0	1	
1	0	1	0	
1	1	0	0	

(b) Characteristic table

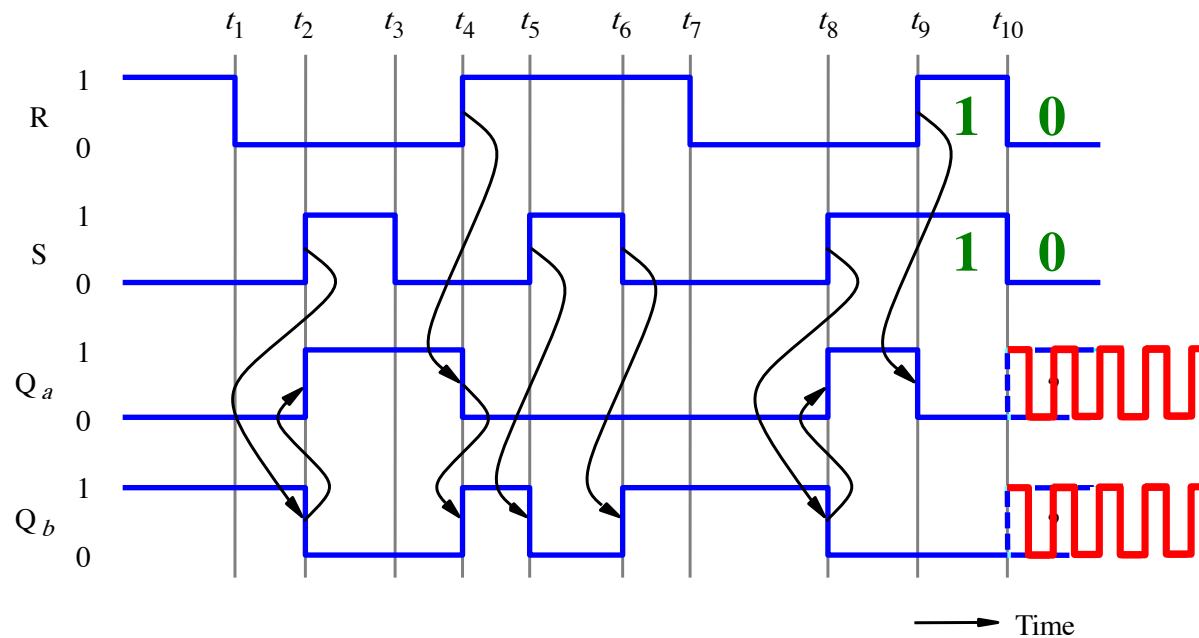


(c) Timing diagram

→ Time

[Figure 5.4 from the textbook]

 
Timing Diagram for the Basic Latch with NOR Gates



(a) Circuit

S	R	Q_a	Q_b	
0	0	0/1	1/0	(no change)
0	1	0	1	
1	0	1	0	
1	1	0	0	

(b) Characteristic table

 

(c) Timing diagram


A transition from $S=R=1$ to $S=R=0$ causes oscillations of the two output values Q_a and Q_b .

→ Time


[Figure 5.4 from the textbook]

Basic Latch with NAND Gates

 
Circuit for the Basic Latch with NAND Gates



Basic Latch (with NOR Gates)

 


Basic Latch (with NAND Gates)

 

Notice that in the NAND case the two inputs are swapped and negated.


The labels of the outputs are the same in both cases.

Basic Latch (with NOR Gates)

 


SR Latch

Basic Latch (with NAND Gates)

 

$\bar{S}\bar{R}$ Latch

Circuit and Characteristic Table

 

(a) Circuit


$\bar{S}$	$\bar{R}$	Q_a	Q_b
0	0	1	1
0	1	1	0
1	0	0	1
1	1	0/1	1/0 (no change)

(b) Characteristic table
(version 1)

S	R	Q_a	Q_b
0	0	0/1	1/0 (no change)
0	1	0	1
1	0	1	0
1	1	1	1

(c) Characteristic table
(version 2)


NAND Gate

 

NAND Gate Truth table


x_1	x_2	f
0	0	1
0	1	1
1	0	1
1	1	0

Basic Latch (with NOR Gates)

 


S	R	Q_a	Q_b	
0	0	0/1	1/0	(no change)
0	1	0	1	
1	0	1	0	
1	1	0	0	

Basic Latch (with NAND Gates)

 


S	R	Q_a	Q_b	
0	0	0/1	1/0	(no change)
0	1	0	1	
1	0	1	0	
1	1	1	1	

Basic Latch (with NOR Gates)

 


S	R	Q_a	Q_b	
0	0	0/1	1/0	(no change) Latch
0	1	0	1	Reset
1	0	1	0	Set
1	1	0	0	Undesirable

Basic Latch (with NAND Gates)

 


S	R	Q_a	Q_b	
0	0	0/1	1/0	(no change) Latch
0	1	0	1	Reset
1	0	1	0	Set
1	1	1	1	Undesirable

Basic Latch (with NOR Gates)

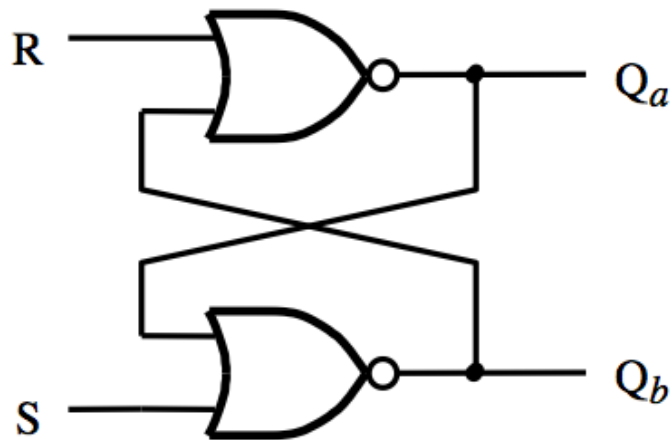

S	R	Q_a	Q_b	
0	0	0/1	1/0	(no change) Latch
0	1	0	1	Reset
1	0	1	0	Set
1	1	0	0	Undesirable

Basic Latch (with NAND Gates)

 

S	R	Q_a	Q_b	
0	0	0/1	1/0	(no change) Latch
0	1	0	1	Reset
1	0	1	0	Set
1	1	1	1	Undesirable

The two characteristic tables are the same
(except for the last row, which is the undesirable configuration).

Oscillations and Undesirable States


- The basic latch with NAND gates also suffers from oscillation problems, similar to the basic latch implemented with NOR gates.
- Try to do this analysis on your own.

Gated SR Latch

Motivation


- The basic latch changes its state when the input signals change.
- It is hard to control when these input signals will change and thus it is hard to know when the latch may change its state.
- We want to have something like an Enable input.
- In this case it is called the “Clock” input because it is desirable for the state changes to be synchronized

Circuit Diagram for the **Gated** SR Latch

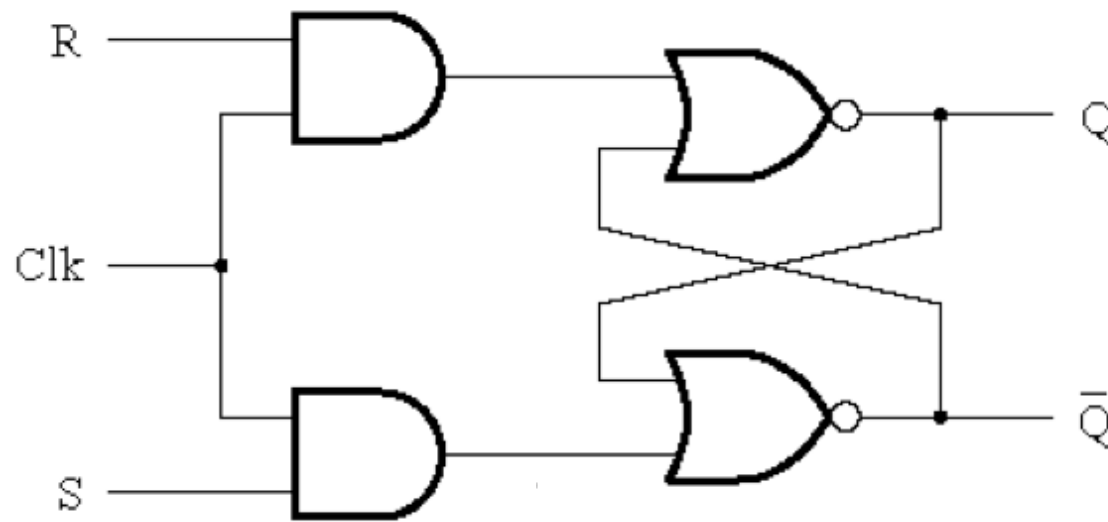


[Figure 5.5a from the textbook]

Circuit Diagram for the Gated SR Latch

 


This is the “gate”
of the gated latch

Circuit Diagram for the Gated SR Latch

 


This is the “snake”
of the gated latch

Circuit Diagram for the Gated SR Latch

 

The outputs are complements of each other

 
Circuit Diagram and Characteristic Table for the Gated SR Latch



Clk	S	R	$Q(t + 1)$
0	x	x	$Q(t)$ (no change)
1	0	0	$Q(t)$ (no change)
1	0	1	0
1	1	0	1
1	1	1	x

[Figure 5.5a-b from the textbook]

 
Circuit Diagram and Characteristic Table for the Gated SR Latch



Clk	S	R	$Q(t + 1)$
0	x	x	$Q(t)$ (no change)
1	0	0	$Q(t)$ (no change)
1	0	1	0
1	1	0	1
1	1	1	x

When $\text{Clk} = 0$ this circuit holds the previous output values, regardless of the current inputs S and R because S' and R' are 0.

 
Circuit Diagram and Characteristic Table for the Gated SR Latch



Clk	S	R	$Q(t + 1)$
0	x	x	$Q(t)$ (no change)
1	0	0	$Q(t)$ (no change)
1	0	1	0
1	1	0	1
1	1	1	x



When $\text{Clk} = 1$ this circuit behaves like a basic latch.

 Circuit Diagram and Characteristic Table for the Gated SR Latch




When $\text{Clk} = 1$ this circuit behaves like a basic latch.
As if this part in gray were not even there.

Circuit Diagram and Graphical Symbol for the Gated SR Latch

  


[Figure 5.5a,c from the textbook]

Timing Diagram for the Gated SR Latch

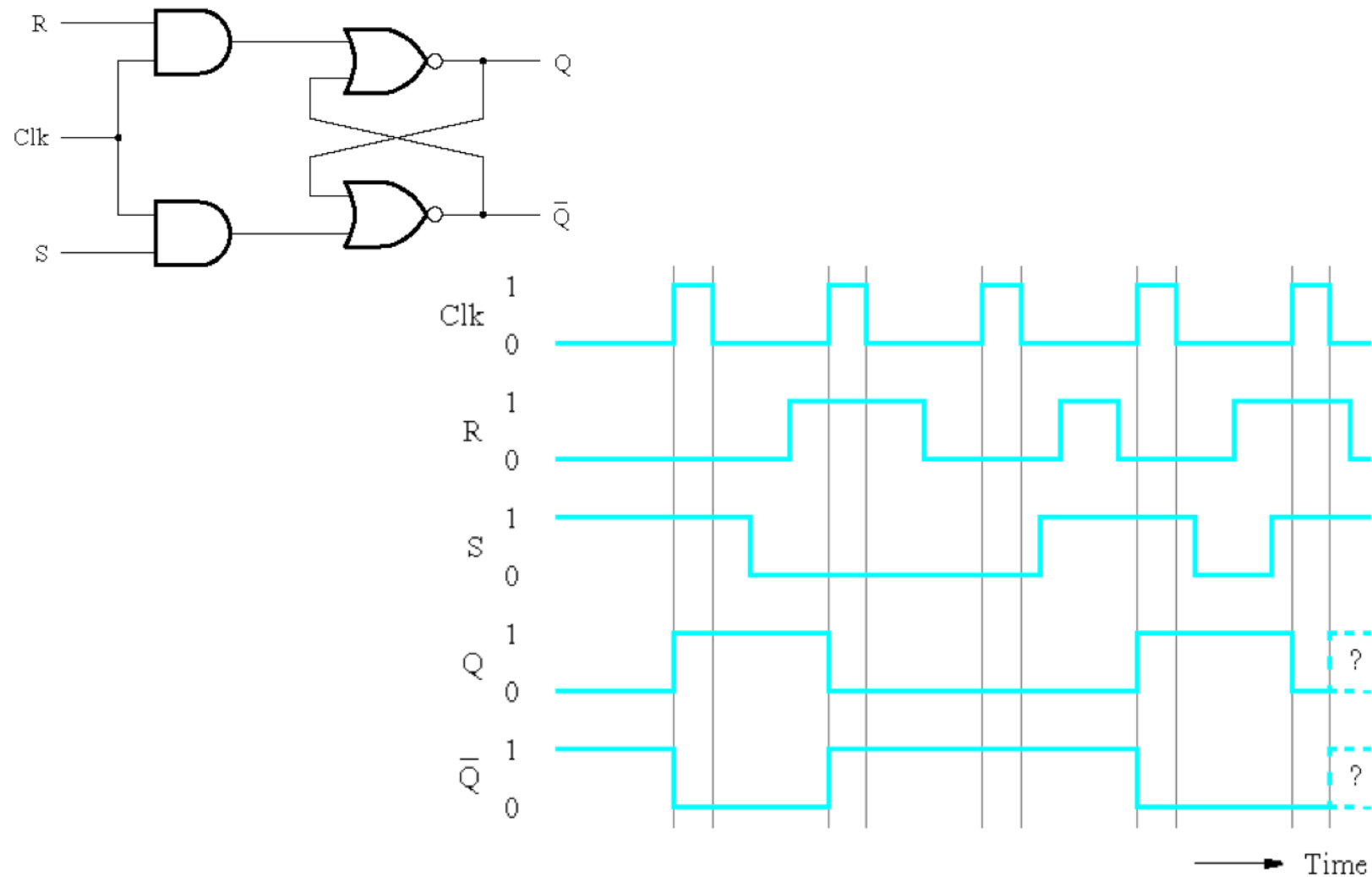


[Figure 5.5c from the textbook]

Timing Diagram for the Gated SR Latch

 


The outputs Q and $\bar{Q}$ cannot change in these intervals.

 


[Figure 5.5c from the textbook]

Timing Diagram for the Gated SR Latch

 


The outputs Q and $\bar{Q}$ may change only in these intervals.

 


[Figure 5.5c from the textbook]

Gated SR latch with NAND gates

 


[Figure 5.6 from the textbook]

Gated SR latch with NAND gates

 


In this case, the “gate” is constructed using NAND gates! Not AND gates.

Gated SR latch with NAND gates

 


The “snake” is also constructed with NANDs.

Gated SR latch with NAND gates

 


Also, notice that the positions of S and R are now swapped.

Gated SR latch with NAND gates

 


Notice that when Clk=1 this turns into the basic latch with NAND gates, i.e., the $\bar{S}\bar{R}$ Latch.

Gated SR latch with NAND gates

 


When Clk=0 this circuit holds the previous output values.


Gated SR latch with NOR gates

 


Gated SR latch with NAND gates

 

Gated SR latch with NOR gates

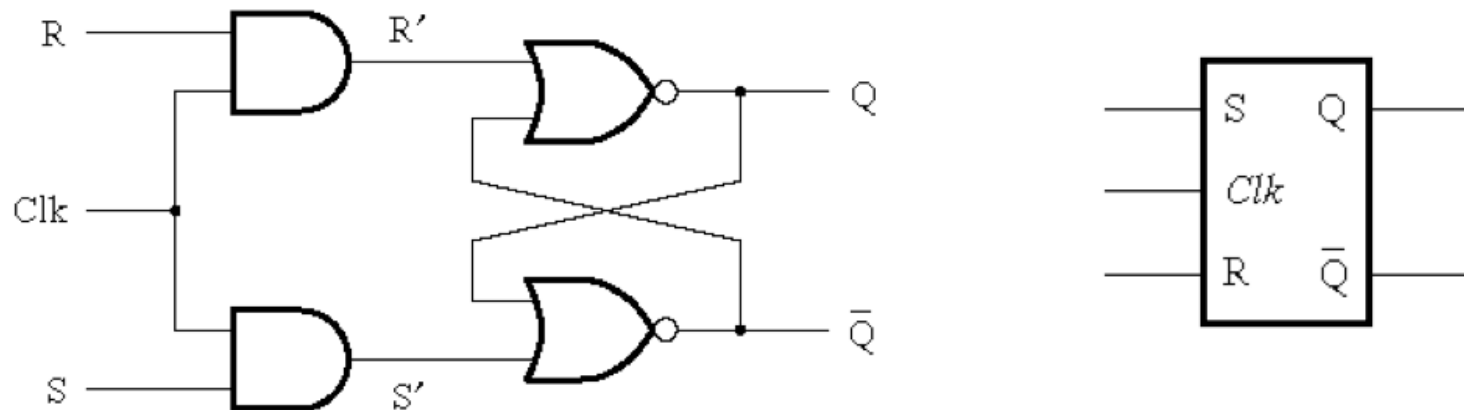


Gated SR latch with NAND gates

 


Graphical symbols are the same

Gated SR latch with NOR gates

 

Clk	S	R	$Q(t+1)$
0	x	x	$Q(t)$ (no change)
1	0	0	$Q(t)$ (no change)
1	0	1	0
1	1	0	1
1	1	1	x (undesirable)

Gated SR latch with NAND gates

 

Clk	S	R	$Q(t+1)$
0	x	x	$Q(t)$ (no change)
1	0	0	$Q(t)$ (no change)
1	0	1	0
1	1	0	1
1	1	1	x (undesirable)


Characteristic tables are the same

Gated D Latch

Motivation


- **Dealing with two inputs (S and R) could be messy. For example, we may have to reset the latch before some operations in order to store a specific value but the reset may not be necessary depending on the current state of the latch.**
- **Why not have just one input and call it D.**
- **The D latch can be constructed using a simple modification of the SR latch.**

Circuit Diagram for the Gated D Latch

 

[Figure 5.7a from the textbook]


Circuit Diagram for the Gated D Latch

 

This is the only
new thing here.

[Figure 5.7a from the textbook]

 
Circuit Diagram and Characteristic Table for the Gated D Latch



Clk	D	$Q(t+1)$
0	x	$Q(t)$
1	0	0
1	1	1

Note that it is now impossible to have $S=R=1$.


 
Circuit Diagram and Characteristic Table for the Gated D Latch



Clk	D	$Q(t+1)$
0	x	$Q(t)$
1	0	0
1	1	1



When Clk=1 the output follows the D input.
When Clk=0 the output cannot be changed.

Circuit Diagram and Graphical Symbol for the Gated D Latch

  


[Figure 5.7a,c from the textbook]

Timing Diagram for the Gated D Latch

  

[Figure 5.7d from the textbook]


Setup and hold times

 



Setup time (t_{su}) – the minimum time that the D signal must be stable prior to the negative edge of the Clock signal.

Hold time (t_h) – the minimum time that the D signal must remain stable after the negative edge of the Clock signal.

 Circuit Diagram for the Gated D Latch (with the latch implemented using NORs)





Circuit Diagram for the Gated D Latch (with the latch implemented using NORs)

 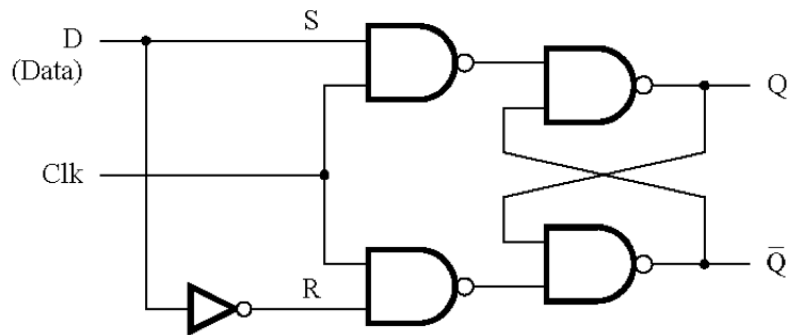

[Figure 5.7a from the textbook]

[https://en.wikibooks.org/wiki/Digital_Circuits/Latches]

  Circuit Diagram for the Gated D Latch (with the latch implemented using NORs)



The NOT gate is now in a different place.
Also, S and R are swapped.

Some Practical Examples


Different Types of Switches




(a) Single-pole—
single-throw
switch



(b) Single-pole—
double-throw
switch

 

(c) Double-pole—
single-throw
switch

 

(d) Double-pole—
double-throw
switch

Different Types of Switches


If you are building a circuit with latches you'll need to use this type of switch.




(a) Single-pole—
single-throw
switch



(b) Single-pole—
double-throw
switch

 


(c) Double-pole—
single-throw
switch

 


(d) Double-pole—
double-throw
switch

Single Pole, Double Throw = SPDT

 


[<http://electronicsclub.info/images/swabc.gif>]


Single Pole, Double Throw = SPDT

 


Single-pole—single-throw manual switch

 


Double-pole—double-throw manual switch

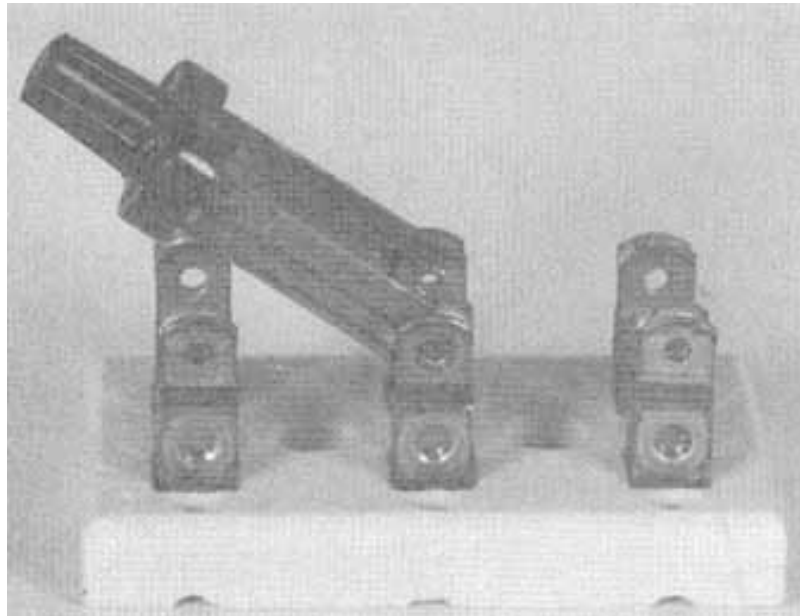

 The following examples came from this book




A Simple Circuit

 


[Platt 2009]

Let's Take a Closer Look at This

 

A Similar Example with NAND Gates

 

Questions?

THE END